



# T2

## Pipelined A/D Converters: The Basics


Aaron Buchwald, PhD

Sunday 03 Feb 2008


*ISSCC 2008 Tutorial*
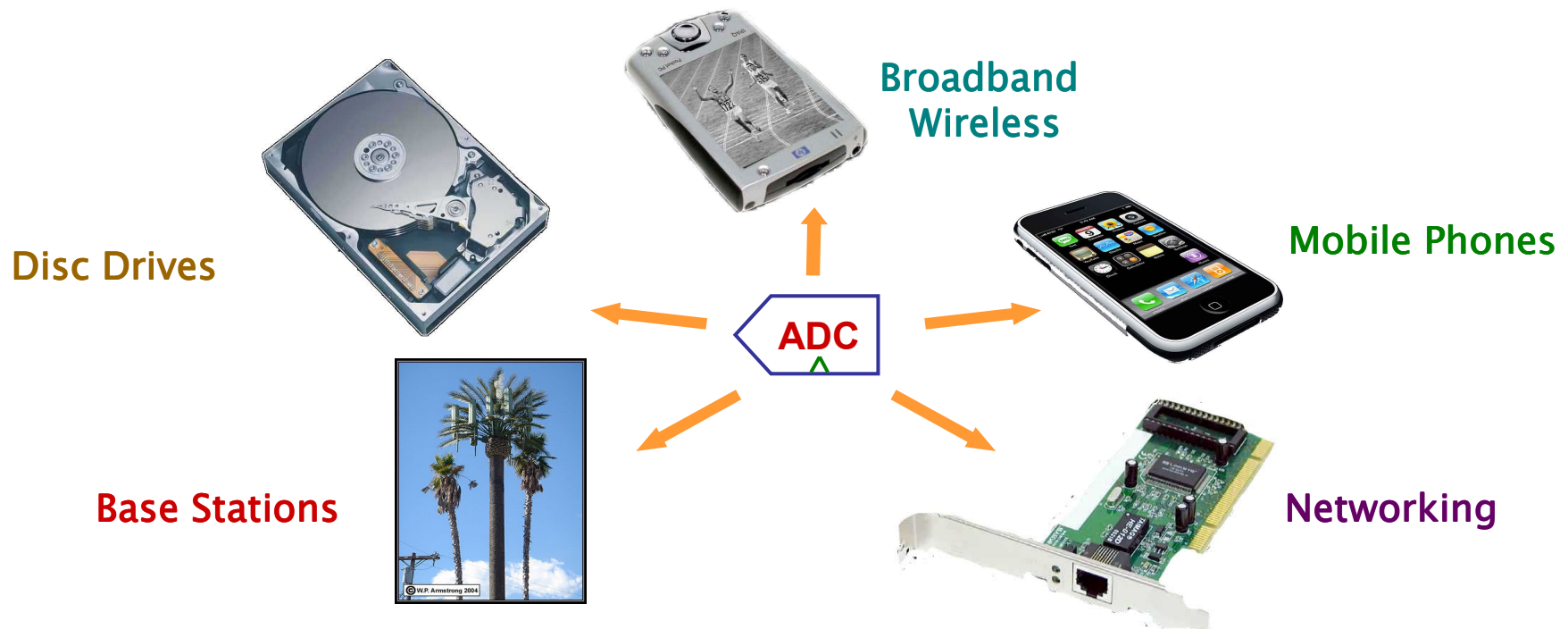
# Applications: ADC Performance is Critical


- Dramatic improvement in converter performance is required for emerging IEEE communication standards
- Data converters will be a key enabling technology to realize ICs at the appropriate power




# Architecture vs. Speed and Resolution

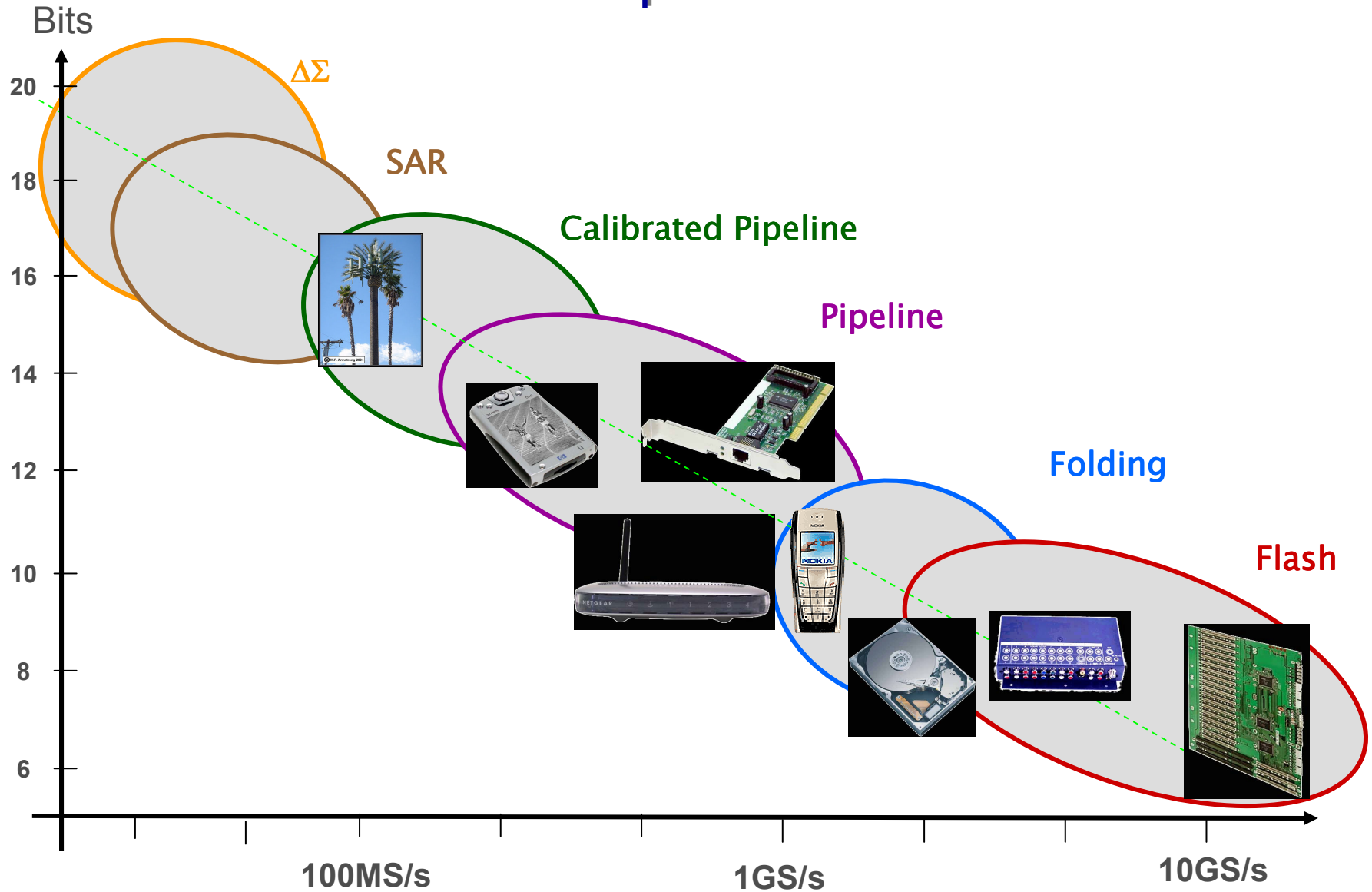

 
# Pipelined vs. Folding: A Personal History


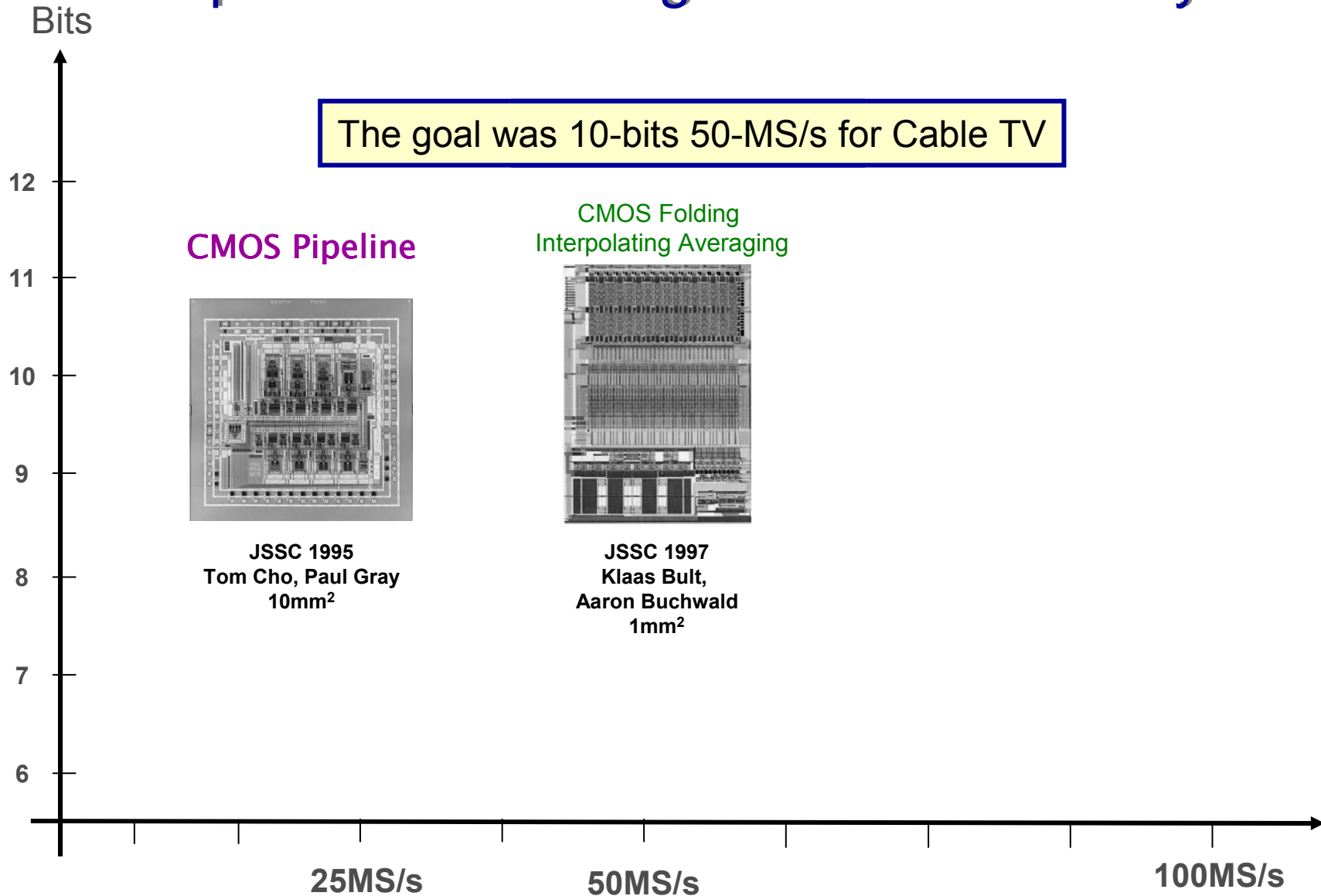
# Pipelined vs. Folding: A Personal History




# Pipelined ADCs Speed and Resolution

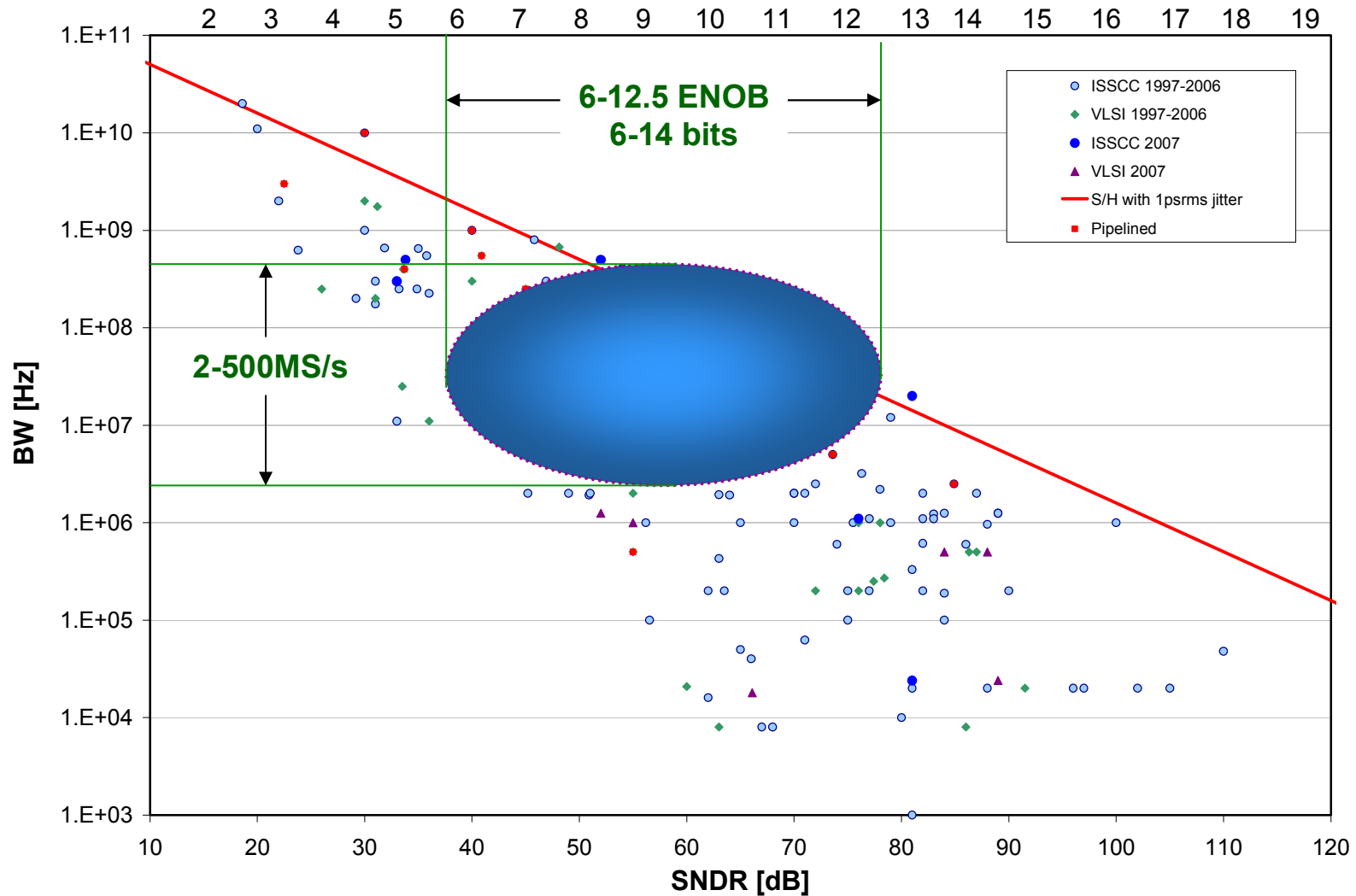

B. Murmann, "ADC Performance Survey 1997-2007," [Online]. Available: <http://www.stanford.edu/~murmann/adcsurvey.html>.


# What is a “Pipelined” ADC

 

U.S. DEPARTMENT OF THE INTERIOR, NATIONAL PARK SERVICE, EDISON NATIONAL HISTORIC SITE




# What is a “Pipelined” ADC

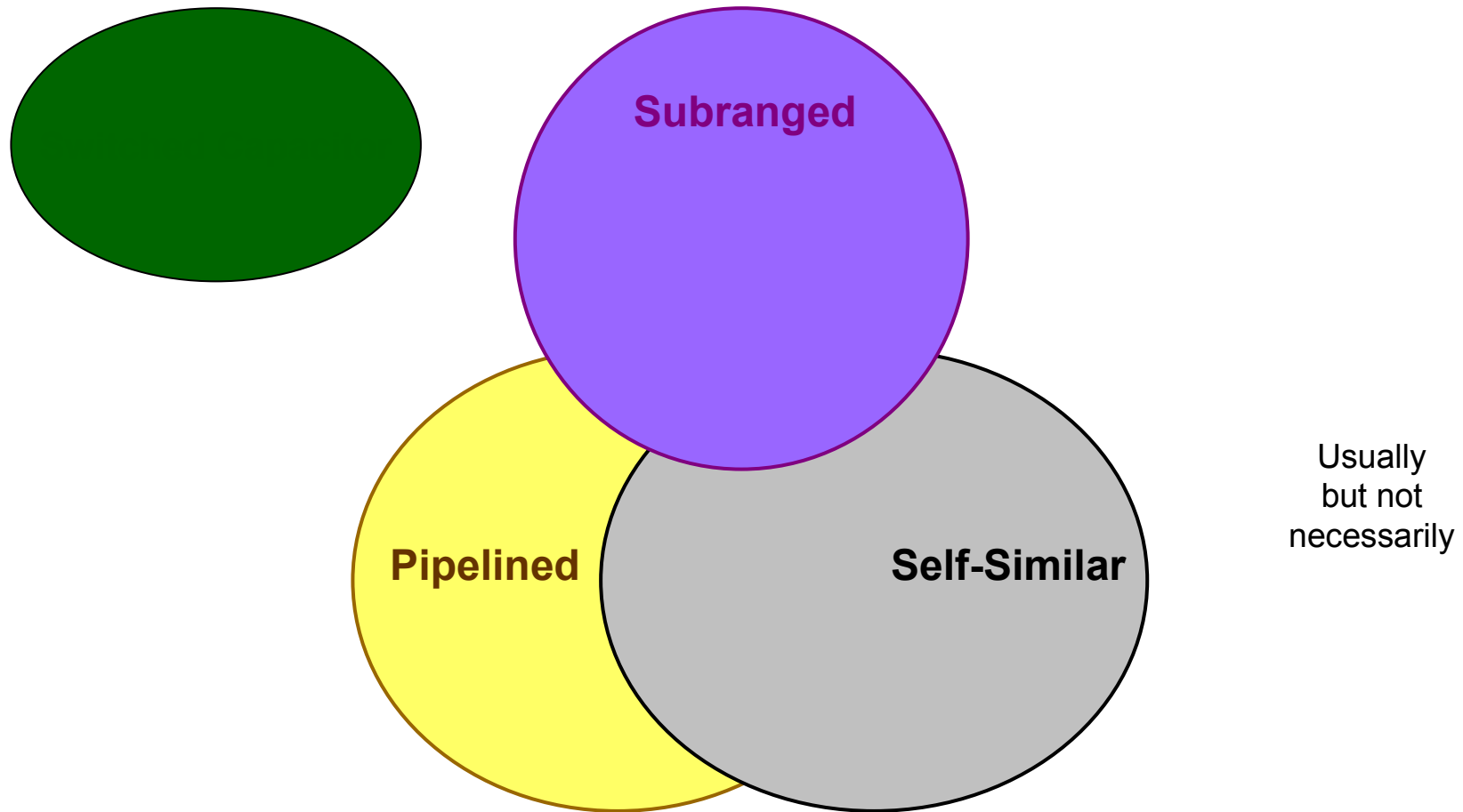

Efficient Calculation Machine Similar to Systolic Arrays – FFT Butterfly Calculation




# 5-bit Flash: Ruler Analogy

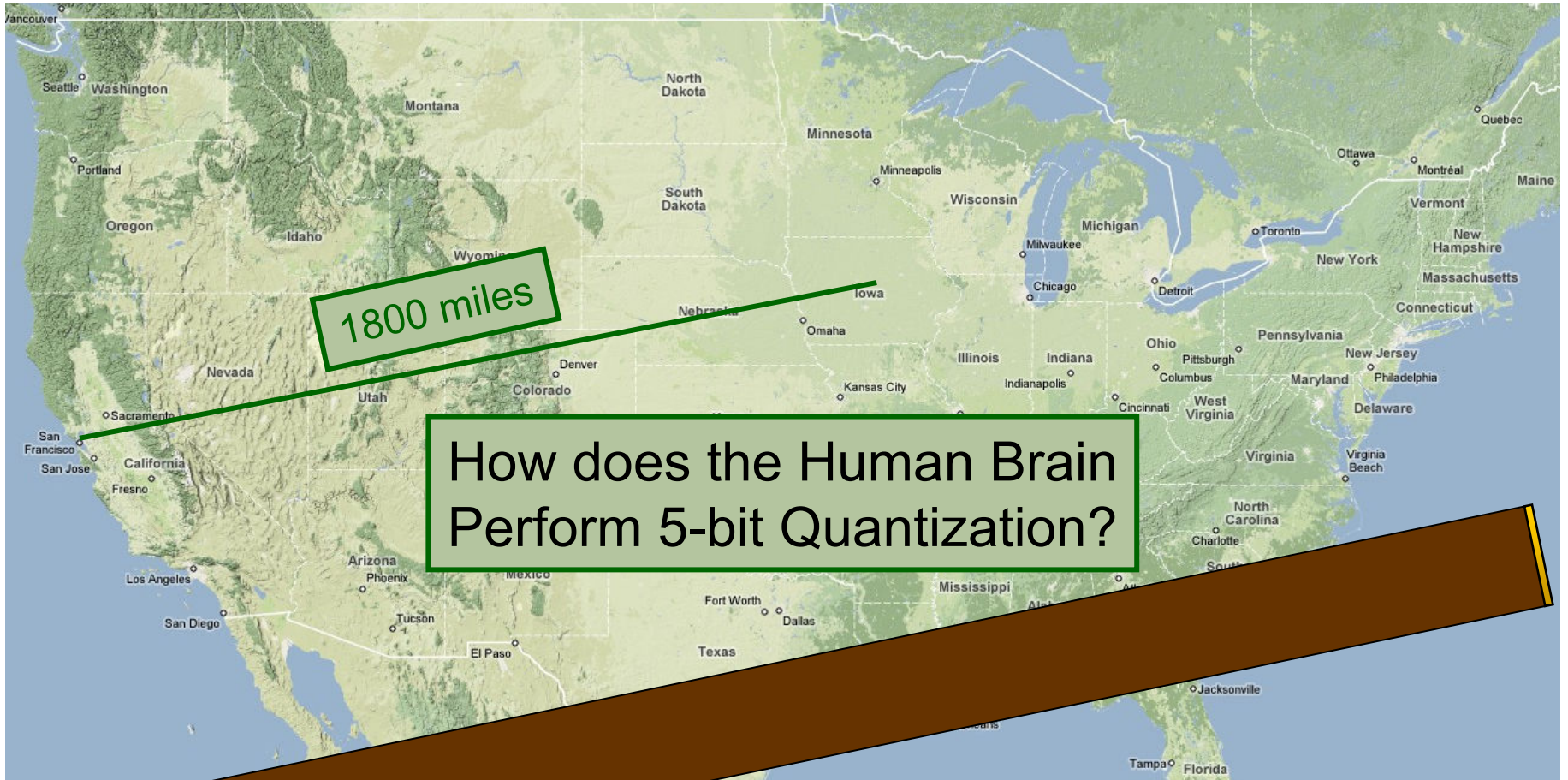


How does the Human Brain Perform 5-bit Quantization?

LSB = 1cm = 100-miles

# 15-bit Spatial Sub-Ranging ADC

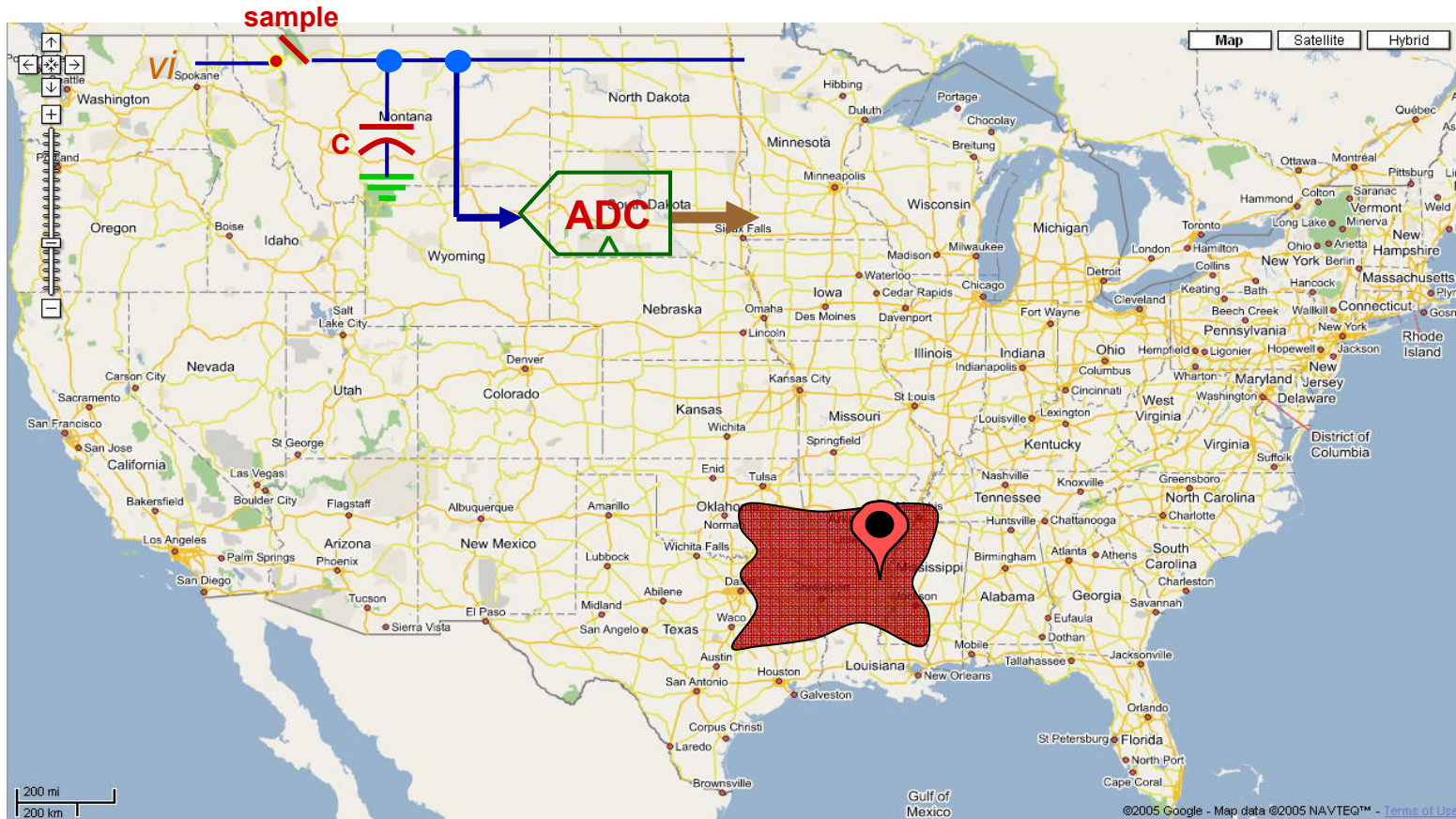


# Coarse Estimate – Center - Amplify

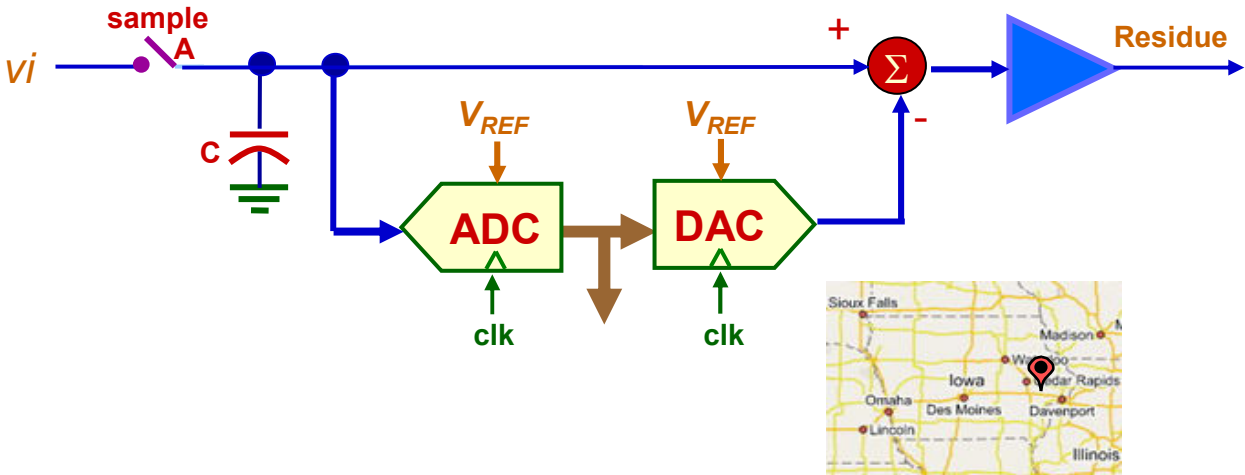






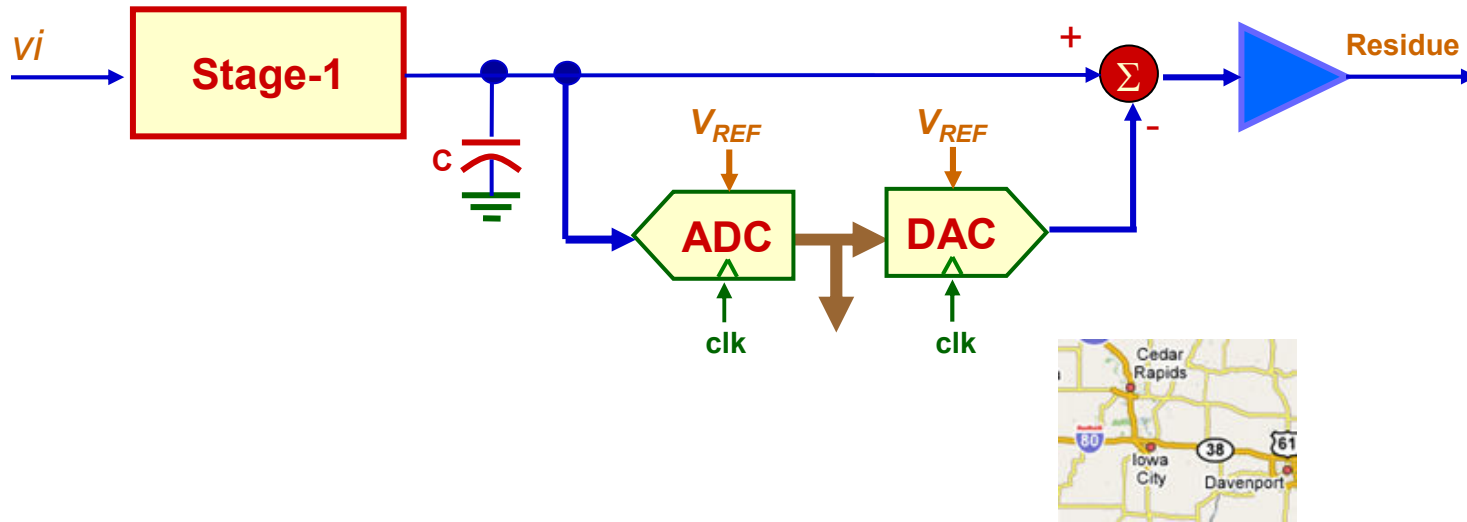
# Repeat Centering and Residue Amplification



# Self Similarity

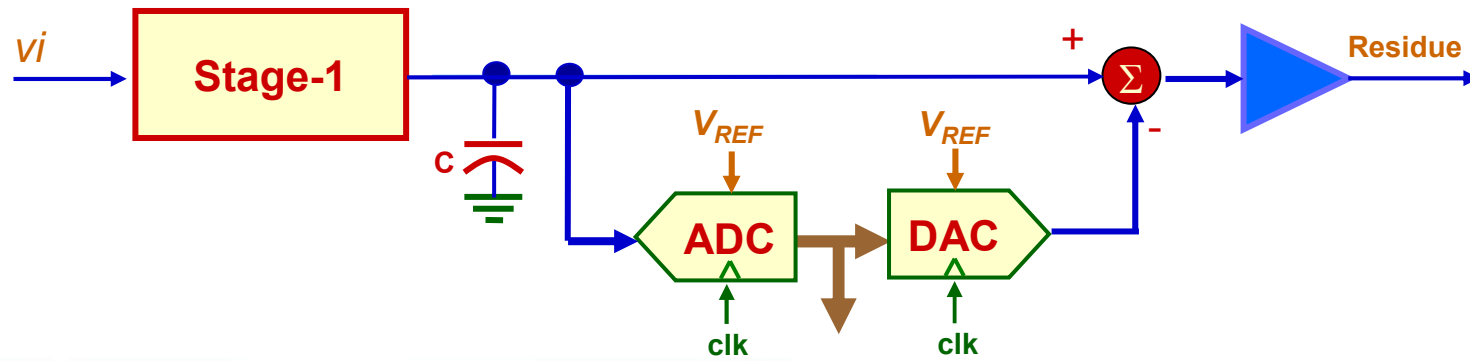


**Matryoshka / Russian Nesting Dolls**

 

**Fractal Geometry of Nature**



# 3<sup>rd</sup>-Stage Sub-range

 





# 4<sup>th</sup> Stage - Features Large Enough to Quantize








# 4-Stage 15-bit Pipeline ADC

 
 

  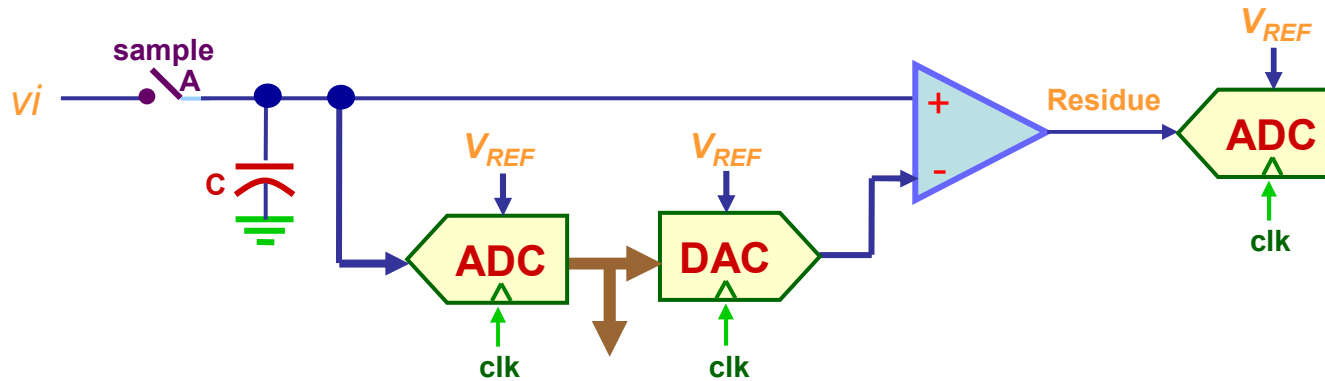
# Challenges in Pipeline ADCs: Offsets & DAC



**Limitations in accuracy due to  
Comparator Offsets & Non-Linearity in DAC**
 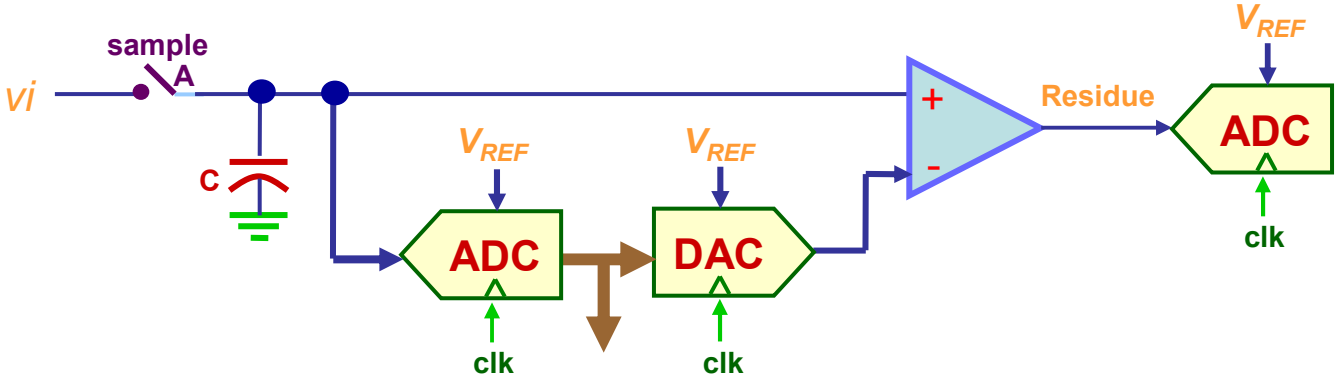
# Challenges in Pipeline ADCs: Gain and Non-linearity



Limitations in accuracy due to gain errors and amplifier non-linearity




**ADC = DAC + Comparison**

**Successive Approximation &  
Relationship to Pipelined ADCs**

---

*ISSCC 2008 Tutorial*
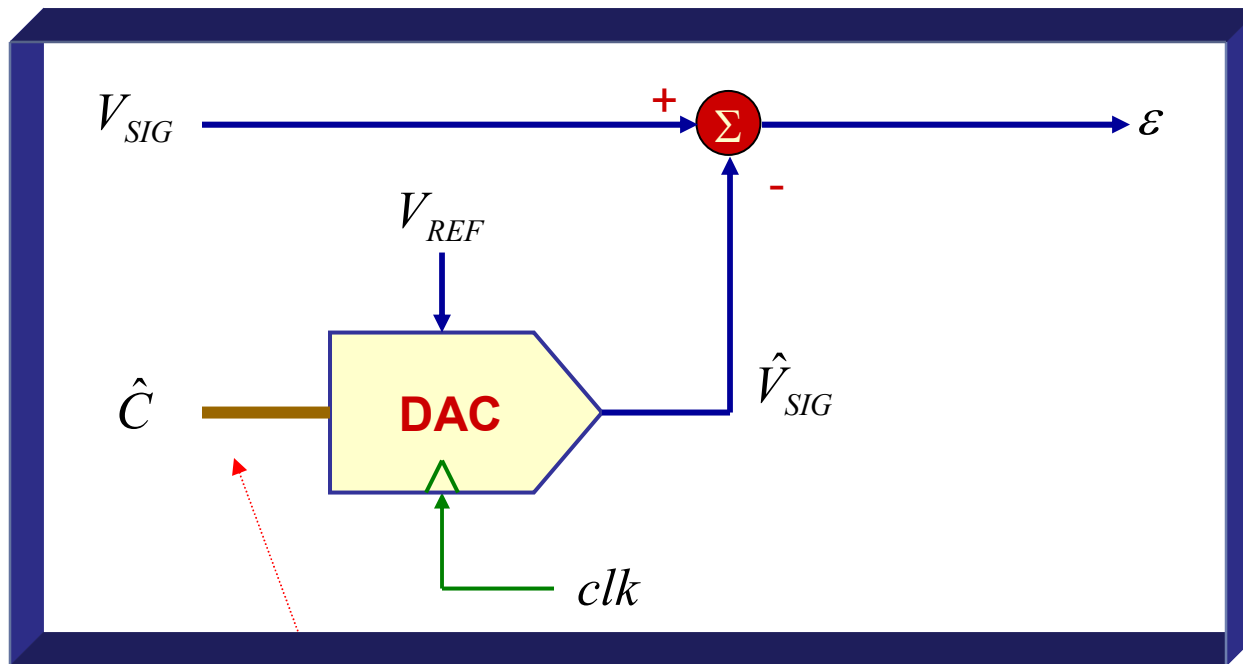
# Signal vs. DAC Comparison: Inverse Transfer Function



## Approximation Error

$$\varepsilon = V_{SIG} - \hat{C}V_{REF}$$

## Digital Output Code


for  $\varepsilon \cong 0$

$\hat{C} = \text{Digital Code}$

## DAC Limits Accuracy

- Drive DAC to minimize error
- ADC accuracy depends on DAC

# Successive Approximation ADC (SAR)

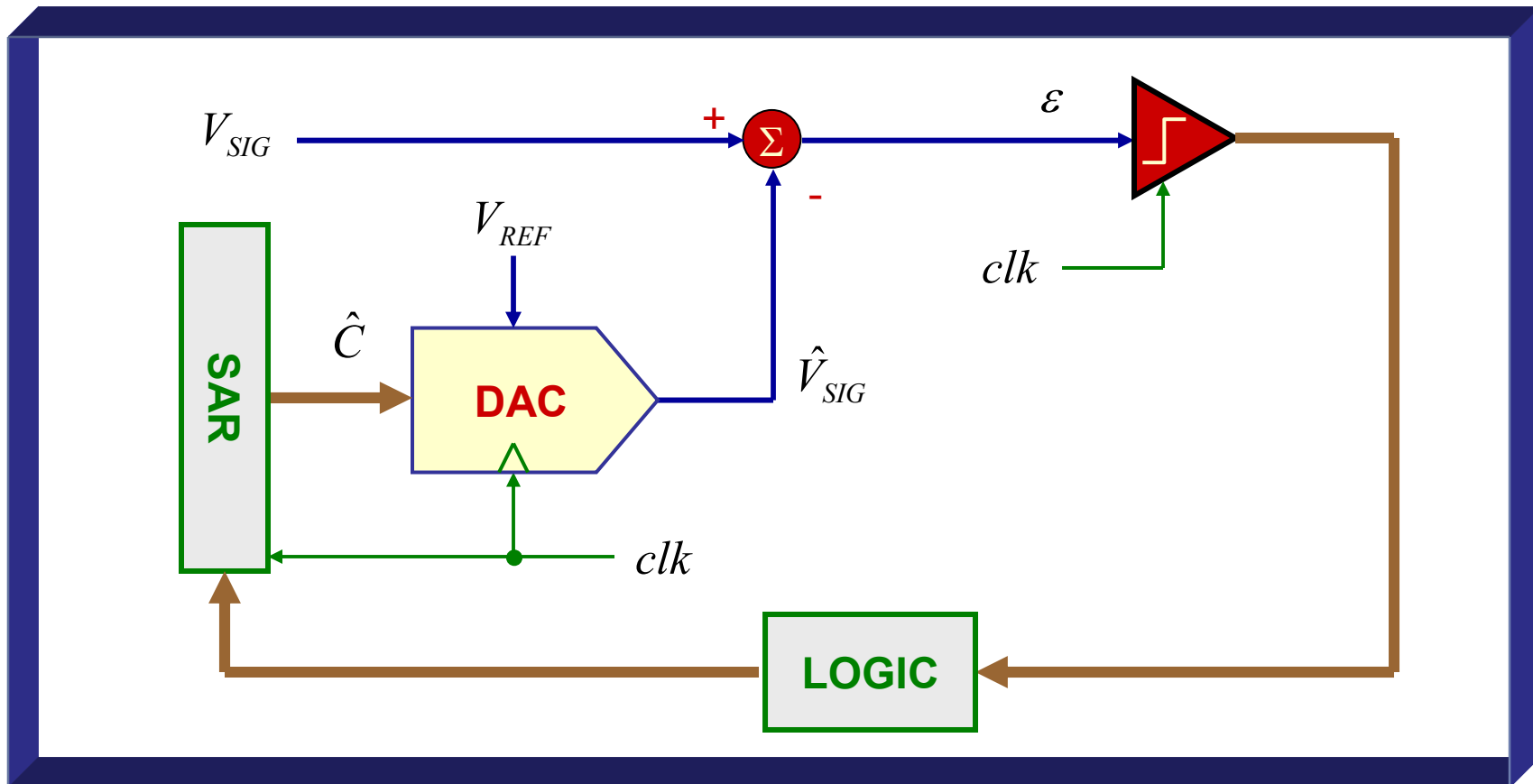


**Use Feedback to Drive Error to Zero**

- Successive Approximation
- Iteratively change DAC code until error is minimized



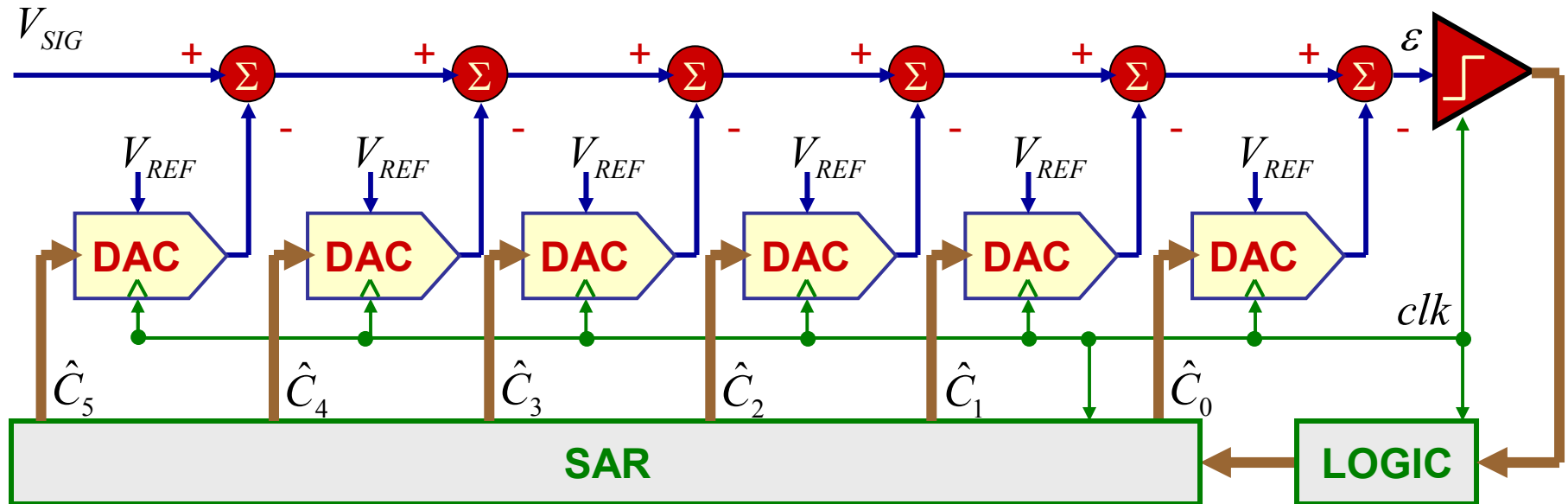
# ADC Basics: DAC Successive Approximation



## ***DACs are identical***

- Error contribution from each DAC affects performance equally
- Full precision required at each node


# ADC Basics: DAC Binary Weighting

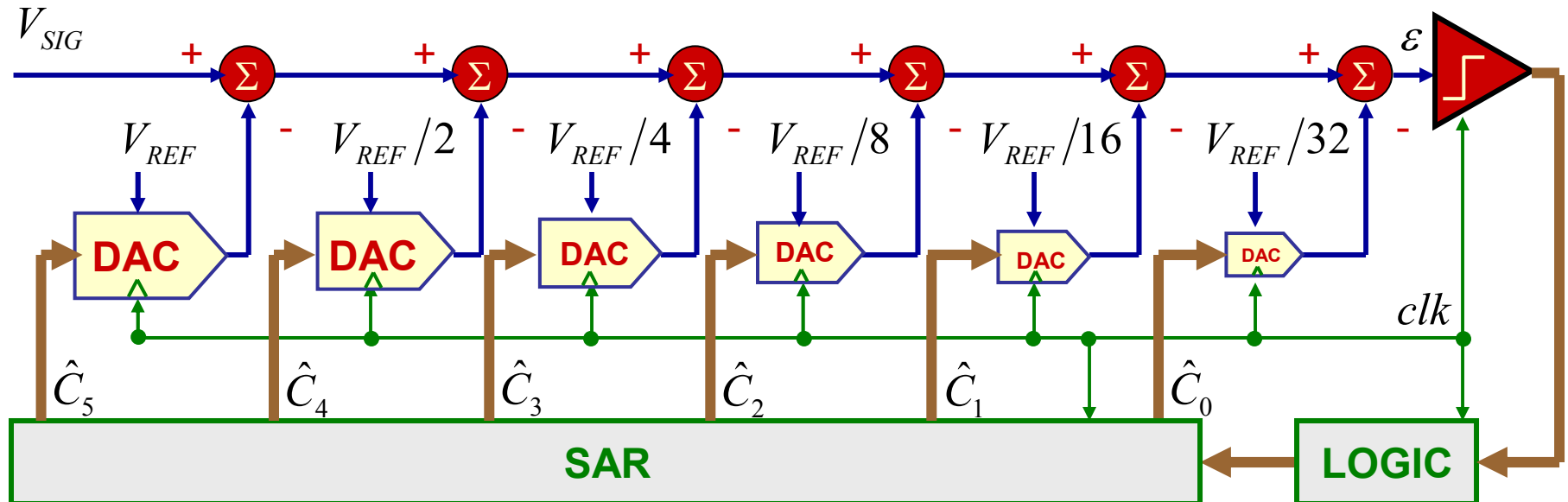

## ***DACs are Binary Weighted***

- Error contribution from DAC mismatch is scaled by reference
- MSB DACs must have better matching than LSB DACs


# Binary Weighting Using Gain Blocks

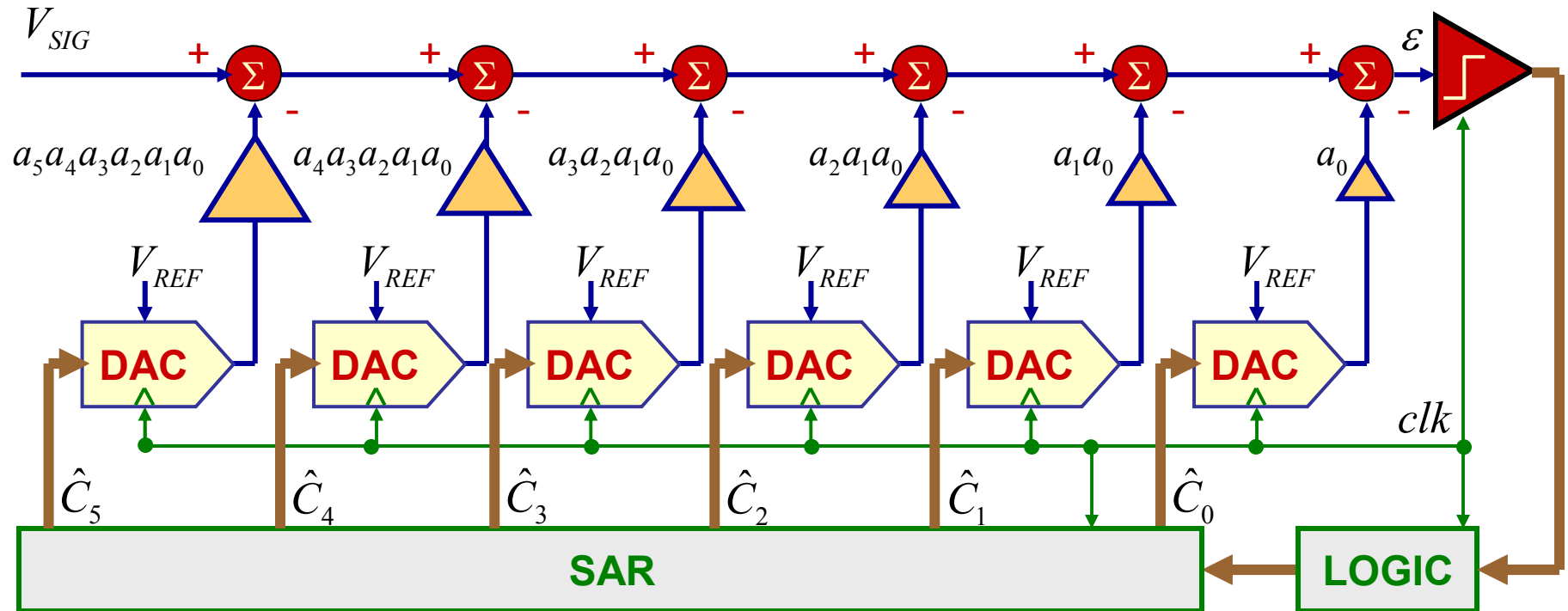

**DACs are identical, but see different gain to output**

- Error contribution from each DAC is proportional to gain in signal path
- MSB DAC is most critical

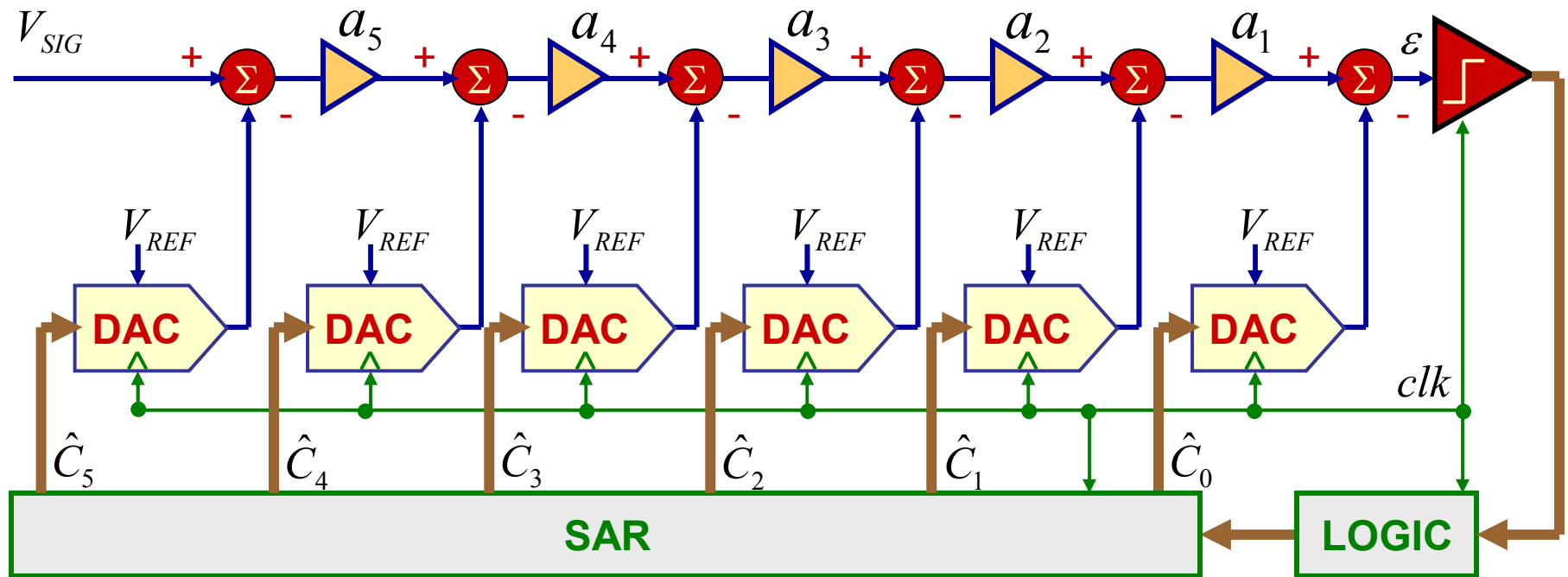
# Binary Weighting with Distributed Gain ( $a_0=1$ )



## ***DACs are identical: Gain is Distributed***

- MSB DAC most critical because it sees largest gain
- Feed-forward path is now modular. All sections are identical

# Dominant Error Sources

 


$$d_{IN} = dn_5 + \frac{dn_4}{a_5} + \frac{dn_3}{a_5 a_4} + \frac{dn_2}{a_5 a_4 a_3} + \frac{dn_1}{a_5 a_4 a_3 a_2} + \frac{dn_0}{a_5 a_4 a_3 a_2 a_1}$$

**Noise Summary**

- The larger the gain at the input less the impact of noise in distortion from subsequent stages
- Dominant Noise Term is from input stage

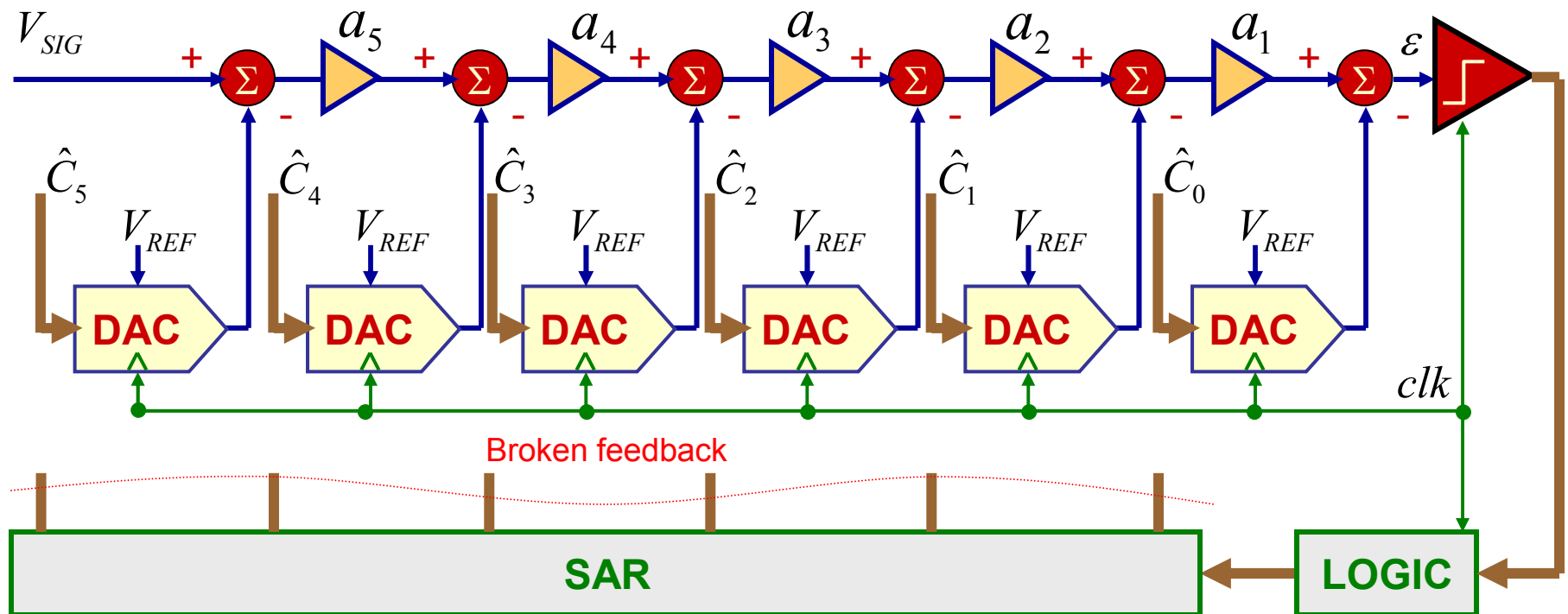
# Transition from Feedback-Based to Pipeline



## ***Feedback not allowed for pipeline design***

- Can not afford to wait for signal to propagate down the chain
- Coefficients must be set by Feed-forward path
- Error Sources and Expression of Analog Output of DACs do not change
- Problem is now is to set Coefficients without overflow of internal nodes

# Adding Analog Delay Allows Pipeline

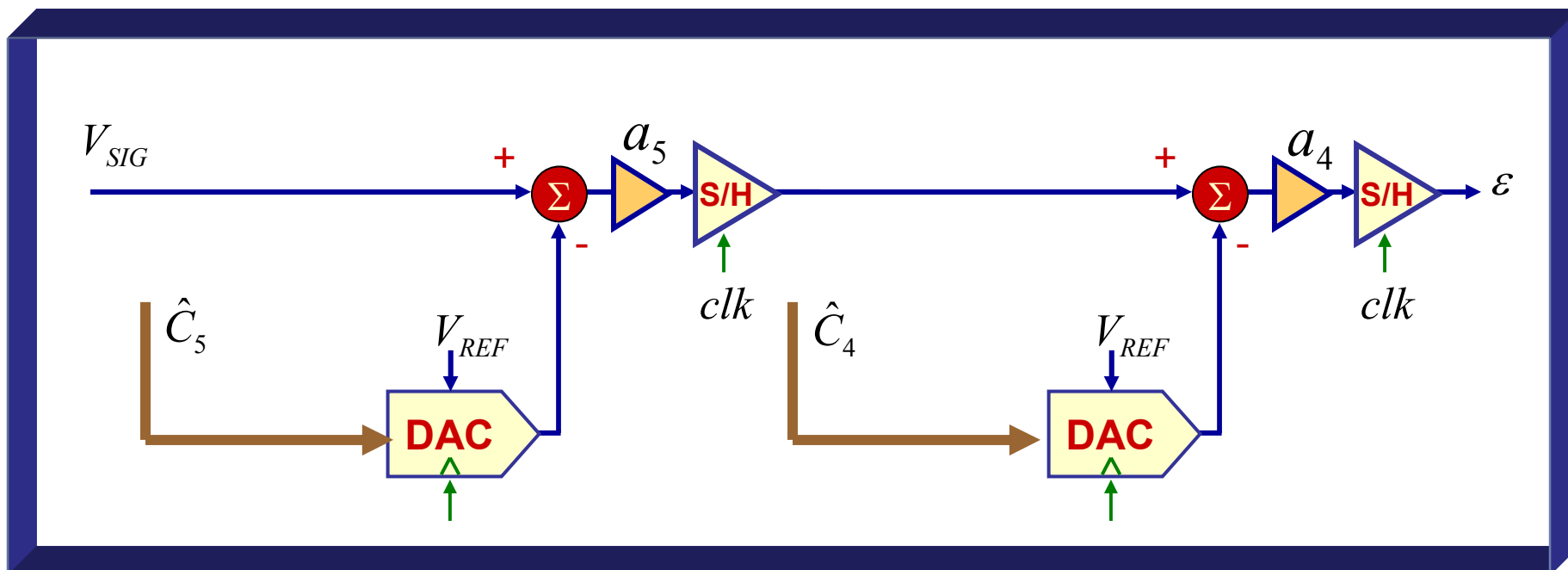


## ***Sample and Hold as an Analog Delay***

- With analog memory each section works on a single residue
- Latency increases, but throughput is high with one complete conversion per clock cycle


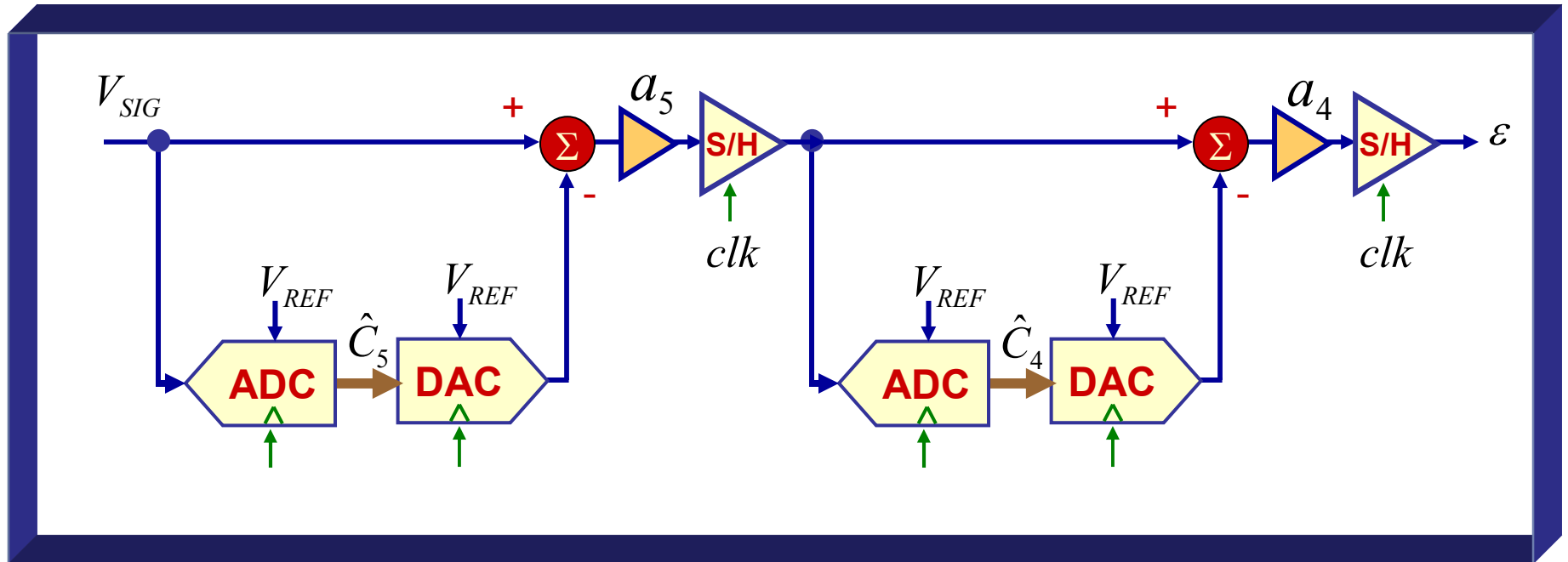
# ADCs in Feed-Forward Path Replace Feedback



**Final result does NOT depend on feed-forward ADCs**

- Provided error “e” is minimized, accuracy is identical to SAR-based ADC
- Coarse ADC job is to get “close” and avoid overflow at intermediate nodes




# Simple 1-bit-per-stage Pipelined ADC


---

*ISSCC 2008 Tutorial*


# Simple Radix-2 Pipelined ADC

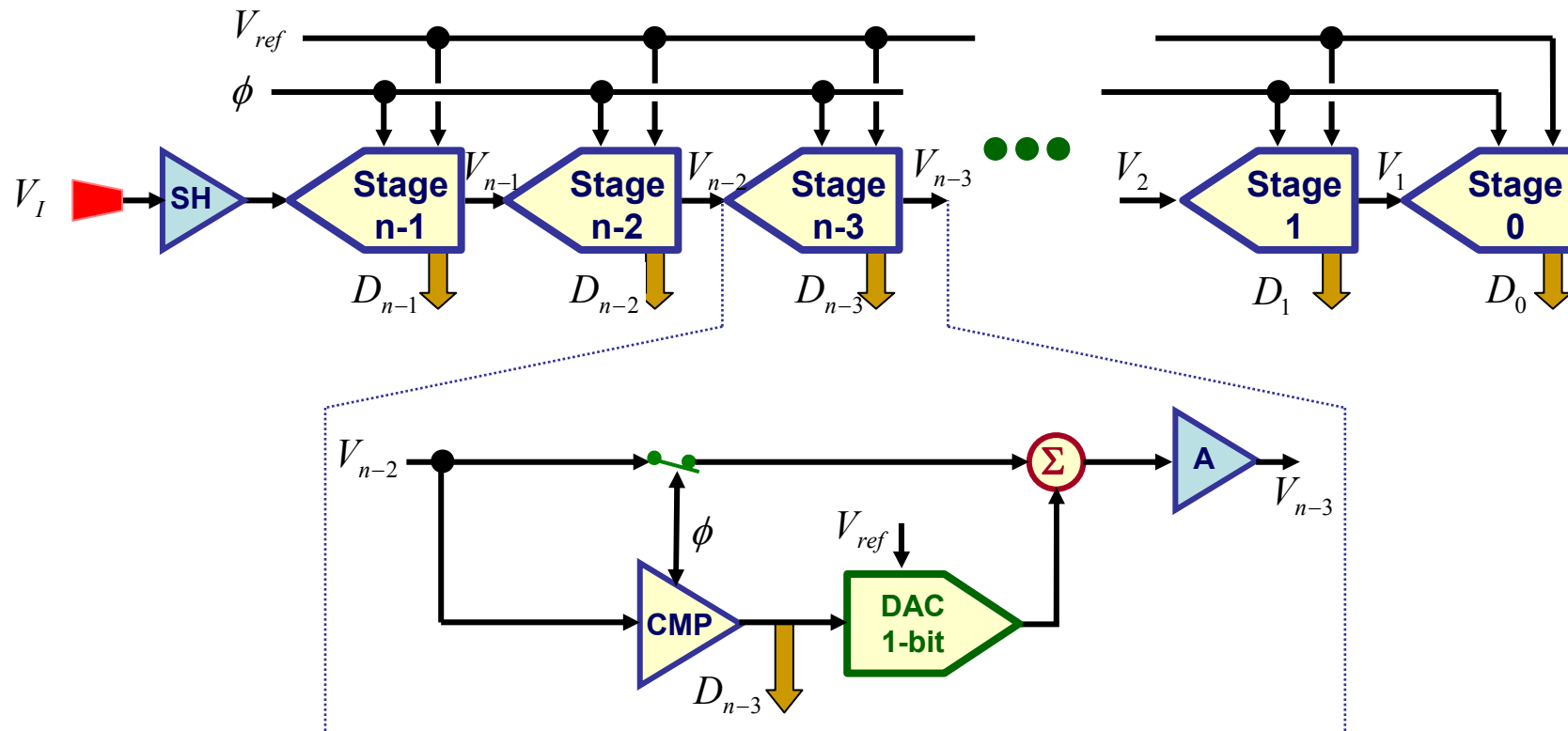

# Voltage Sub-Ranges: No Overlap

 

 
# Residue Plot: Input to Residue Transfer Function




## ***No margin in Coarse ADC***

- Offset of coarse ADC must be at full accuracy
- No over-range margin in amplitude
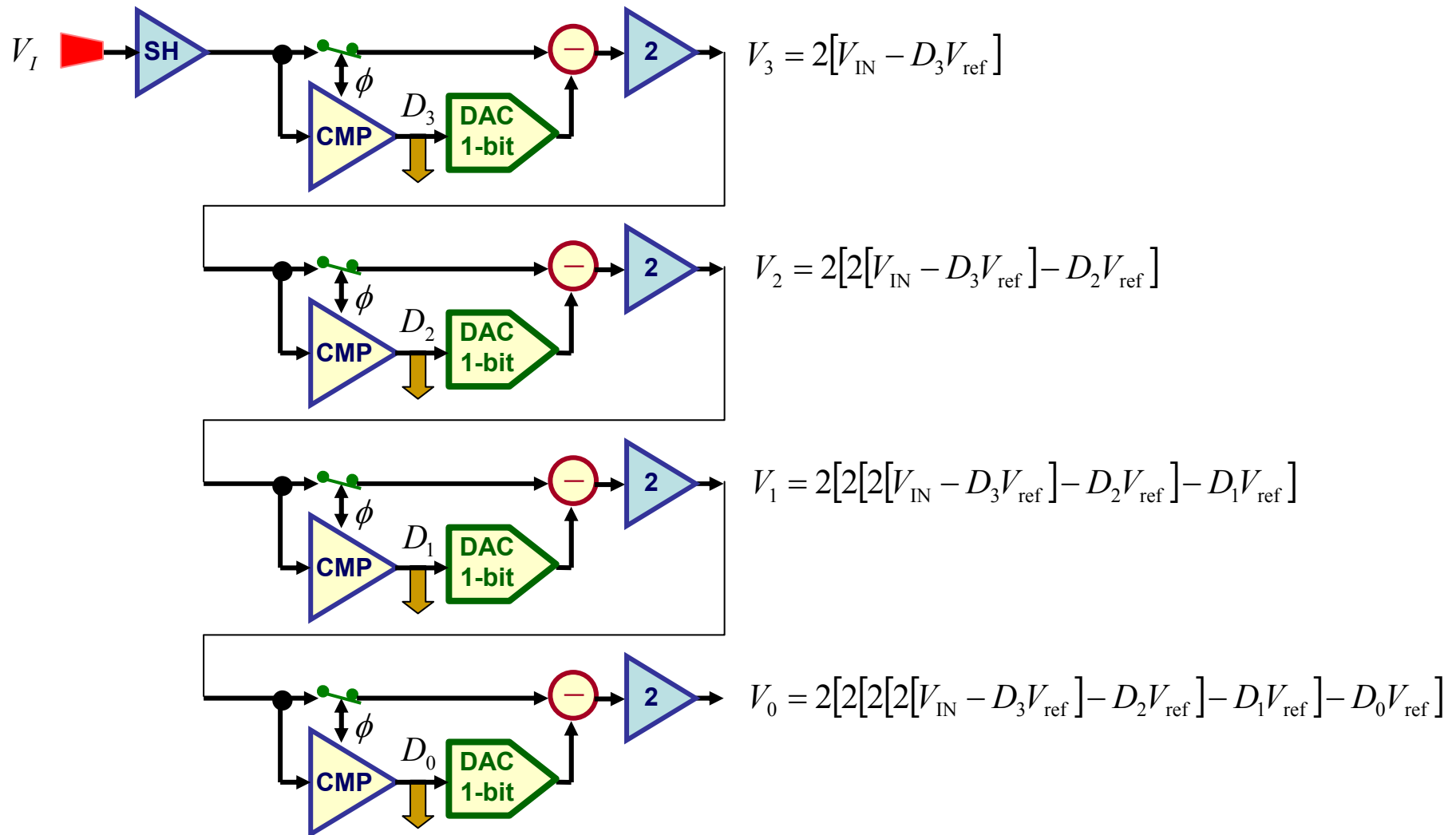
# Radix-2 Pipelined ADC: Residue Voltages



# Slice Architecture: Pipelined ADC

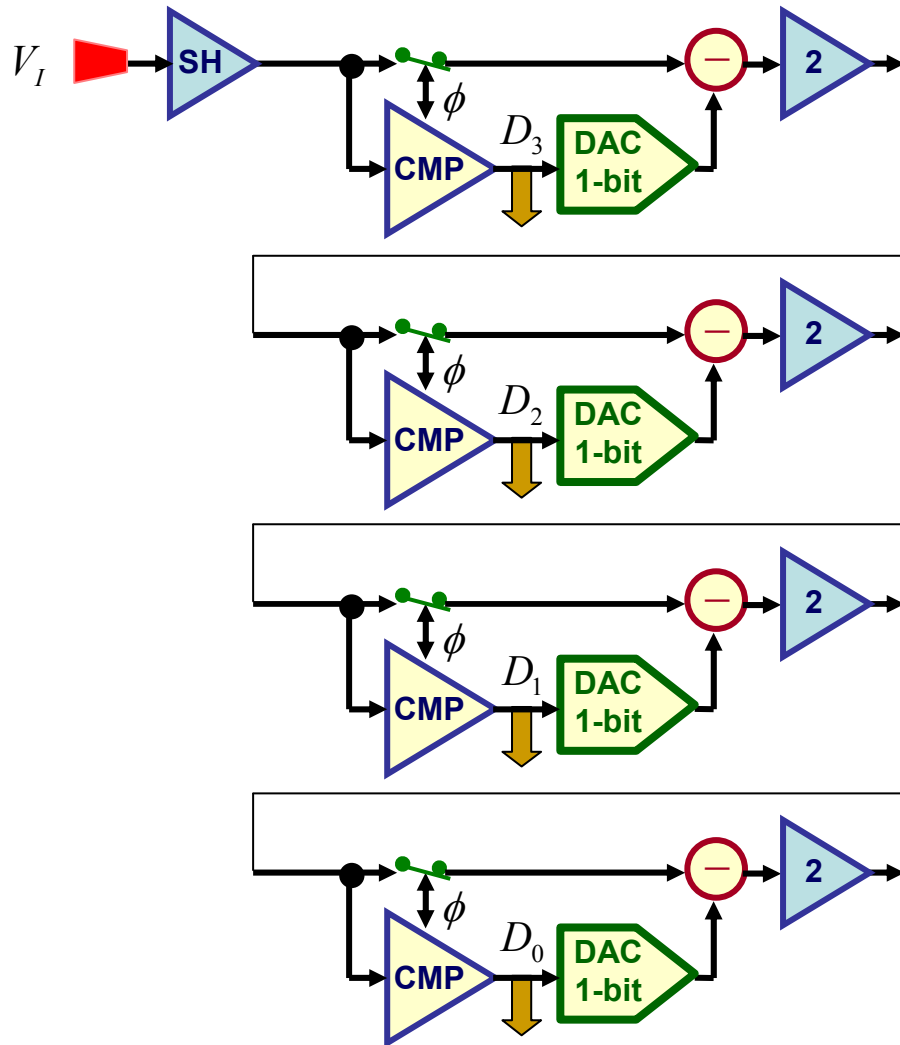


$$\frac{V_0}{2} = 8V_{\text{IN}} - V_{\text{ref}} [8D_3 + 4D_2 + 2D_1 + D_0]$$


$$\frac{V_{\text{IN}}}{V_{\text{ref}}} \approx \frac{1}{8} [D_3 \quad D_2 \quad D_1 \quad D_0] \cdot \begin{bmatrix} 8 \\ 4 \\ 2 \\ 1 \end{bmatrix}$$


 
# 1-bit-per-Stage ADC with Input Near Zero



# Voltage Sub-Ranges: Comparator Offset

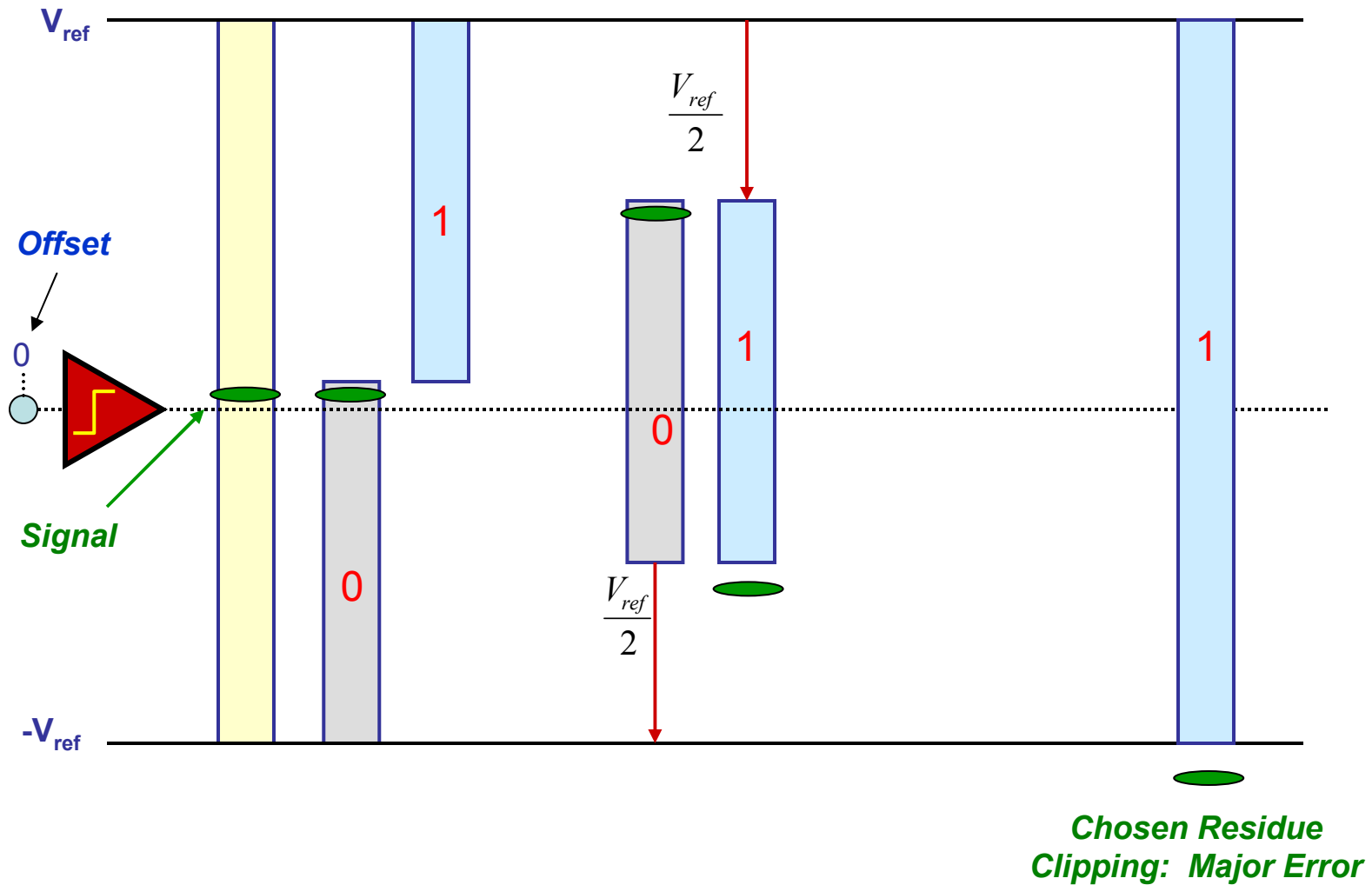




# Redundancy


*ISSCC 2008 Tutorial*
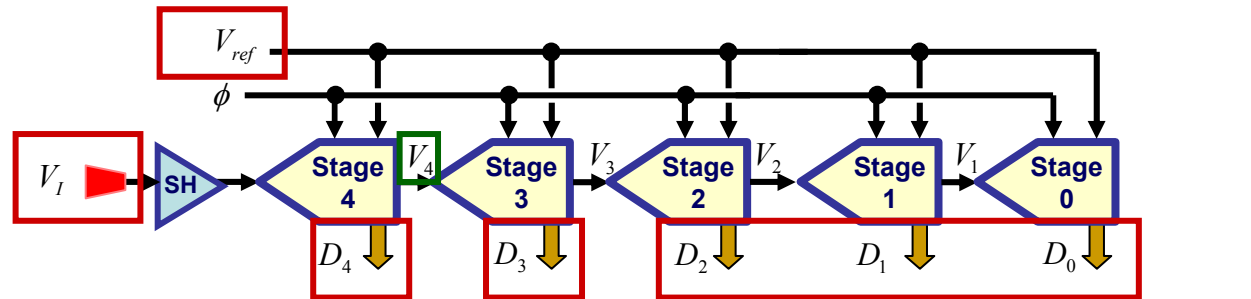
# Long Division: Natalya's 6<sup>th</sup> Grade Homework




$$\begin{array}{r}
 10 \quad \leftarrow \text{Redundancy / Overlap} \\
 3 \ .156 \\
 \hline
 102 \ \bigg| \ 4096.000 \quad = \ 40.156 \\
 \underline{306} \\
 1036 \quad \leftarrow \text{residue} \\
 \underline{1020} \\
 160 \\
 \underline{102} \\
 580 \\
 \underline{510} \\
 700 \\
 \underline{612} \\
 82
 \end{array}$$

# Voltage Sub-Ranges: With Overlap

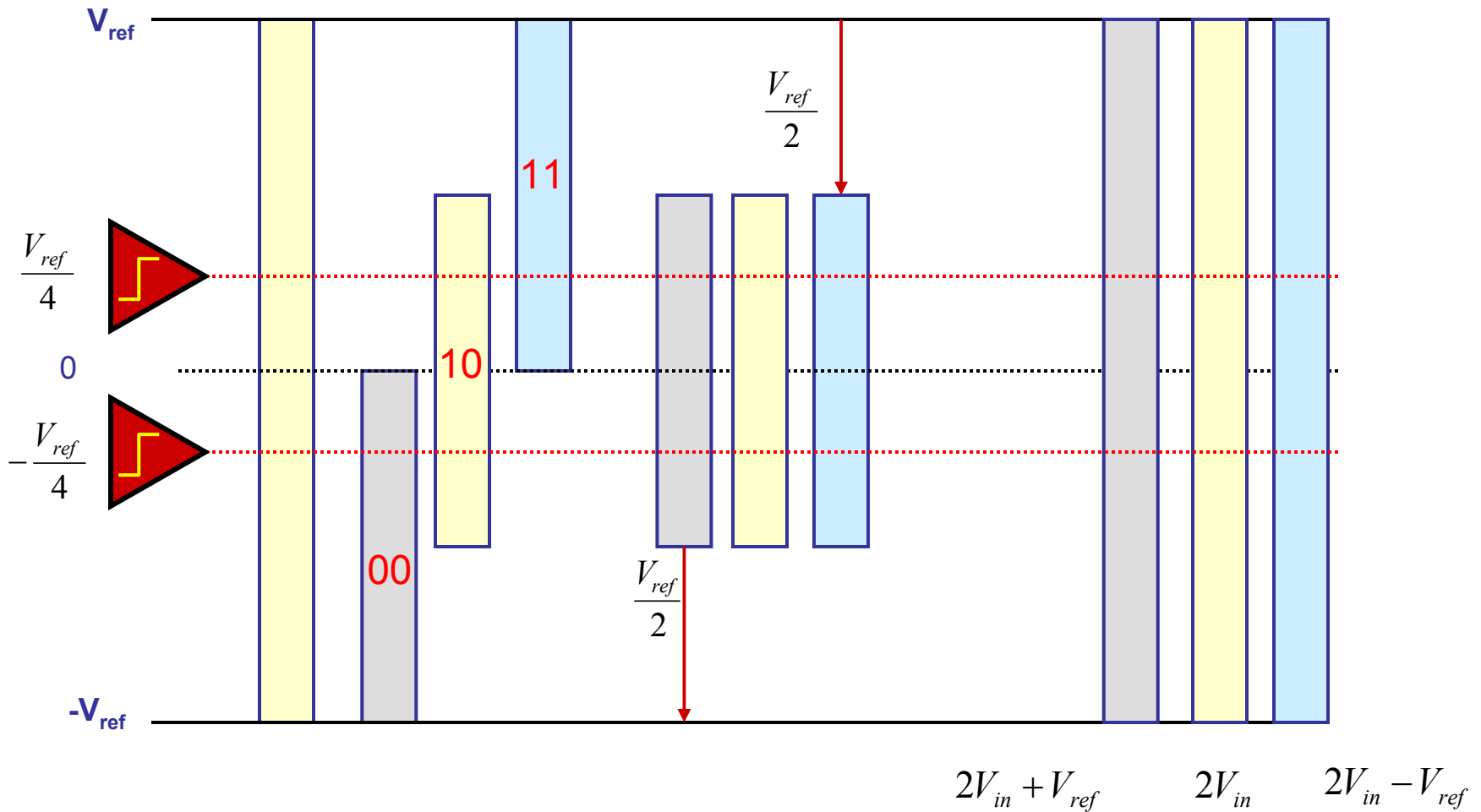


# Residue Plot: with Redundancy

 


## ***Redundancy Relaxes Coarse ADC Requirements***

- Offset of coarse ADC need only be accurate to  $V_{ref}/4$
- Half of the voltage swing is used for over-range

# Voltage Sub-Ranges: With Overlap

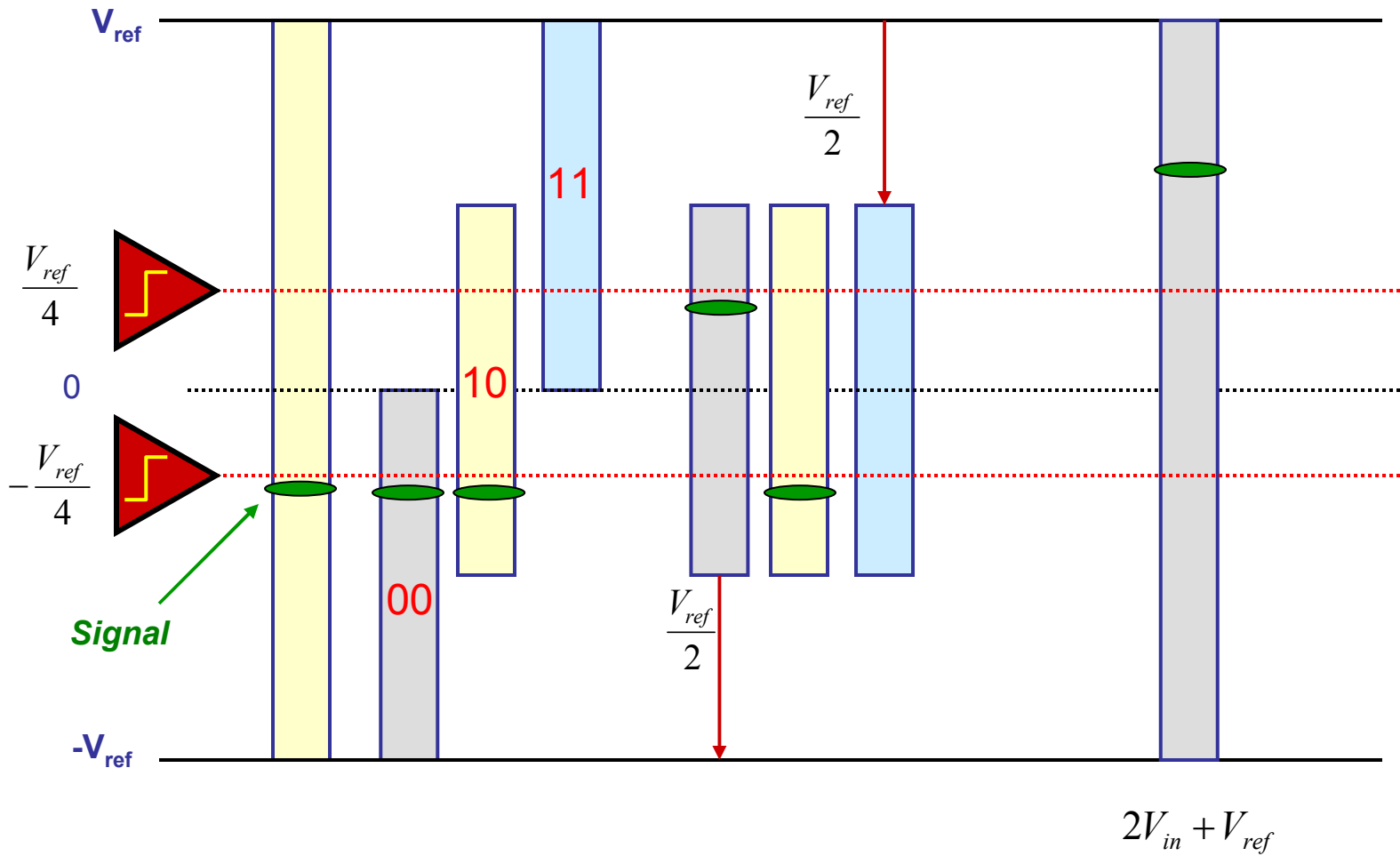

 
# Voltage Sub-Ranges: Offset Margin $\pm V_{ref}/4$







# Residue Plot: with Redundancy

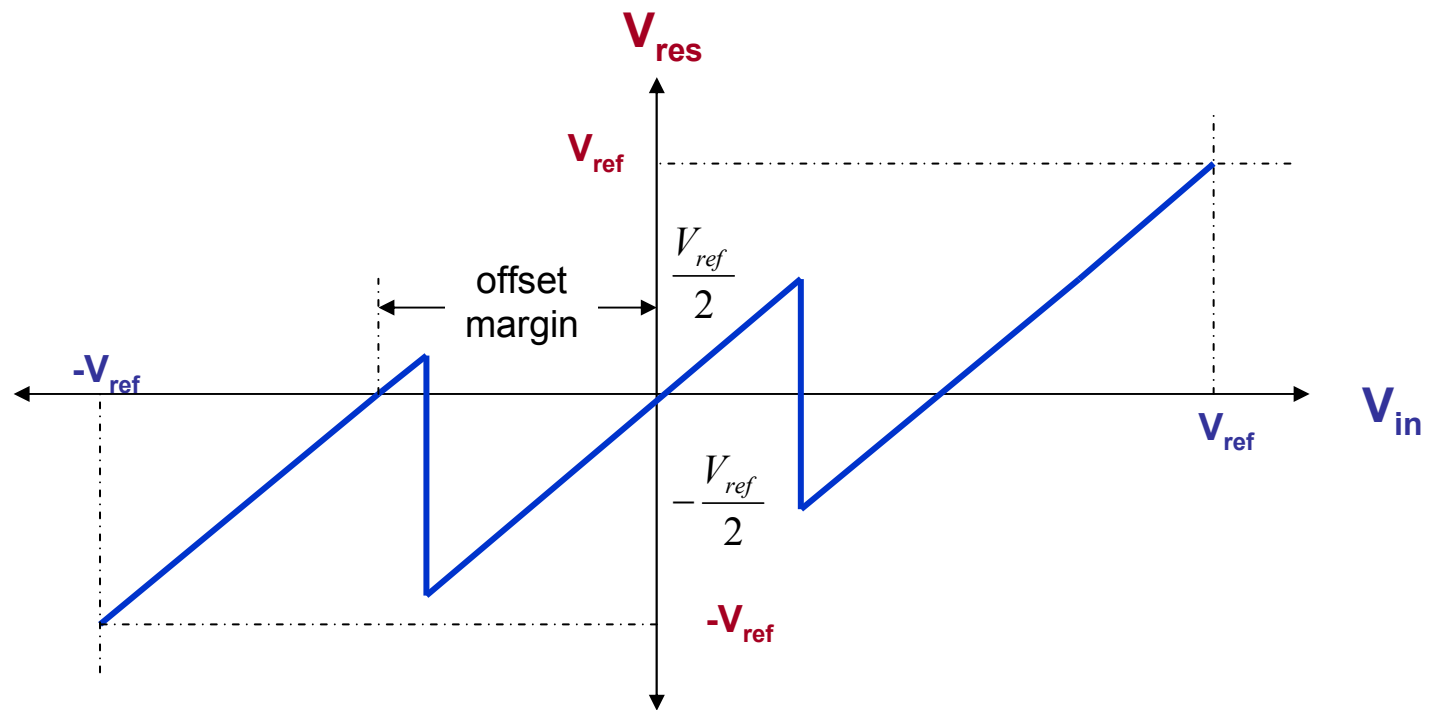

# Voltage Sub-Ranges: 2-bit (4x Gain)

 

# Voltage Sub-Ranges: 3-bit (8x Gain)

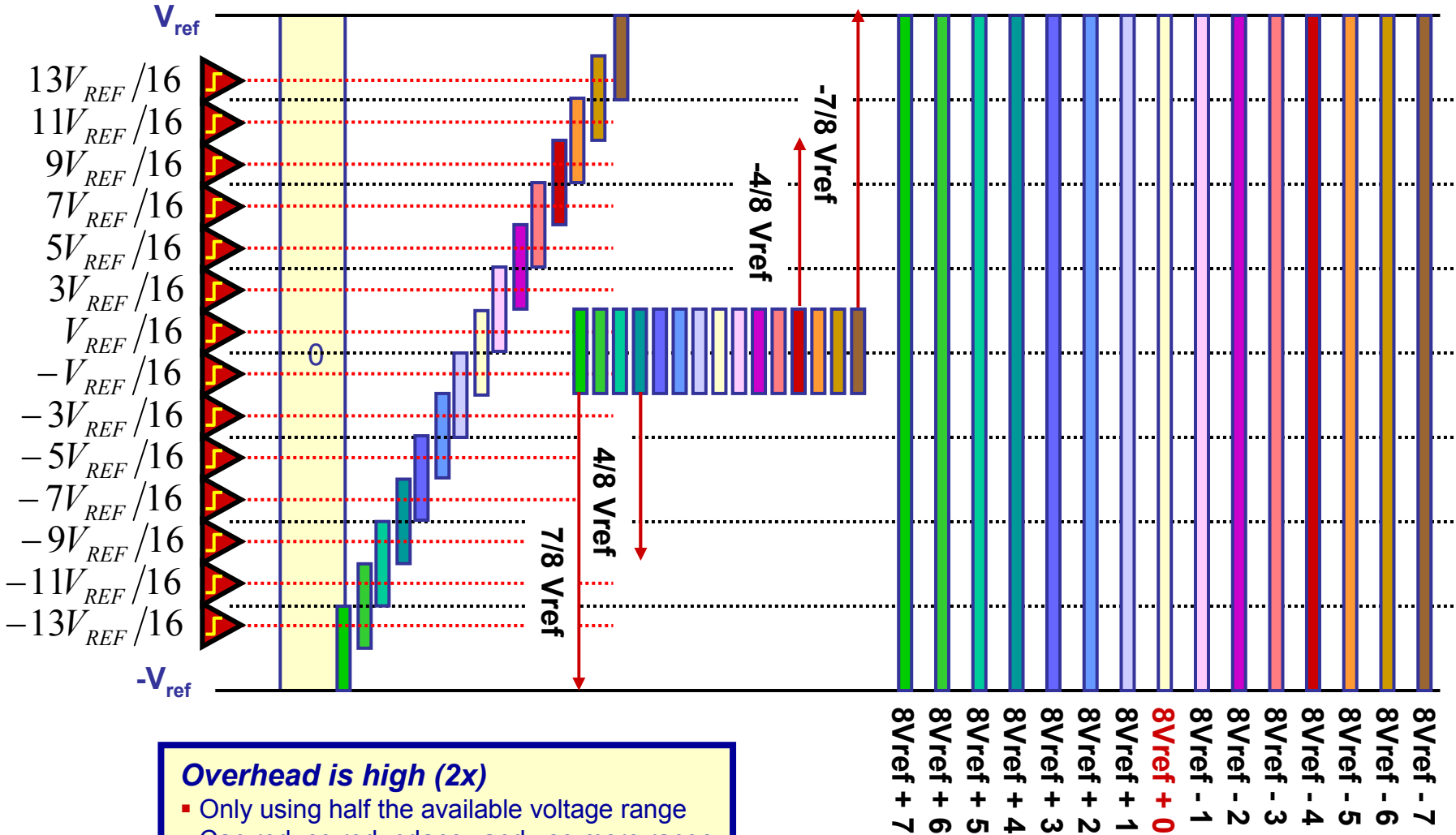

**Overhead is high (2x)**

- Only using half the available voltage range
- Can reduce redundancy and use more range at expense of potential over-range




# Less than 1-bit-per-stage Pipelined ADC


---

*ISSCC 2008 Tutorial*


# Voltage Sub-Ranges: Single Comparator

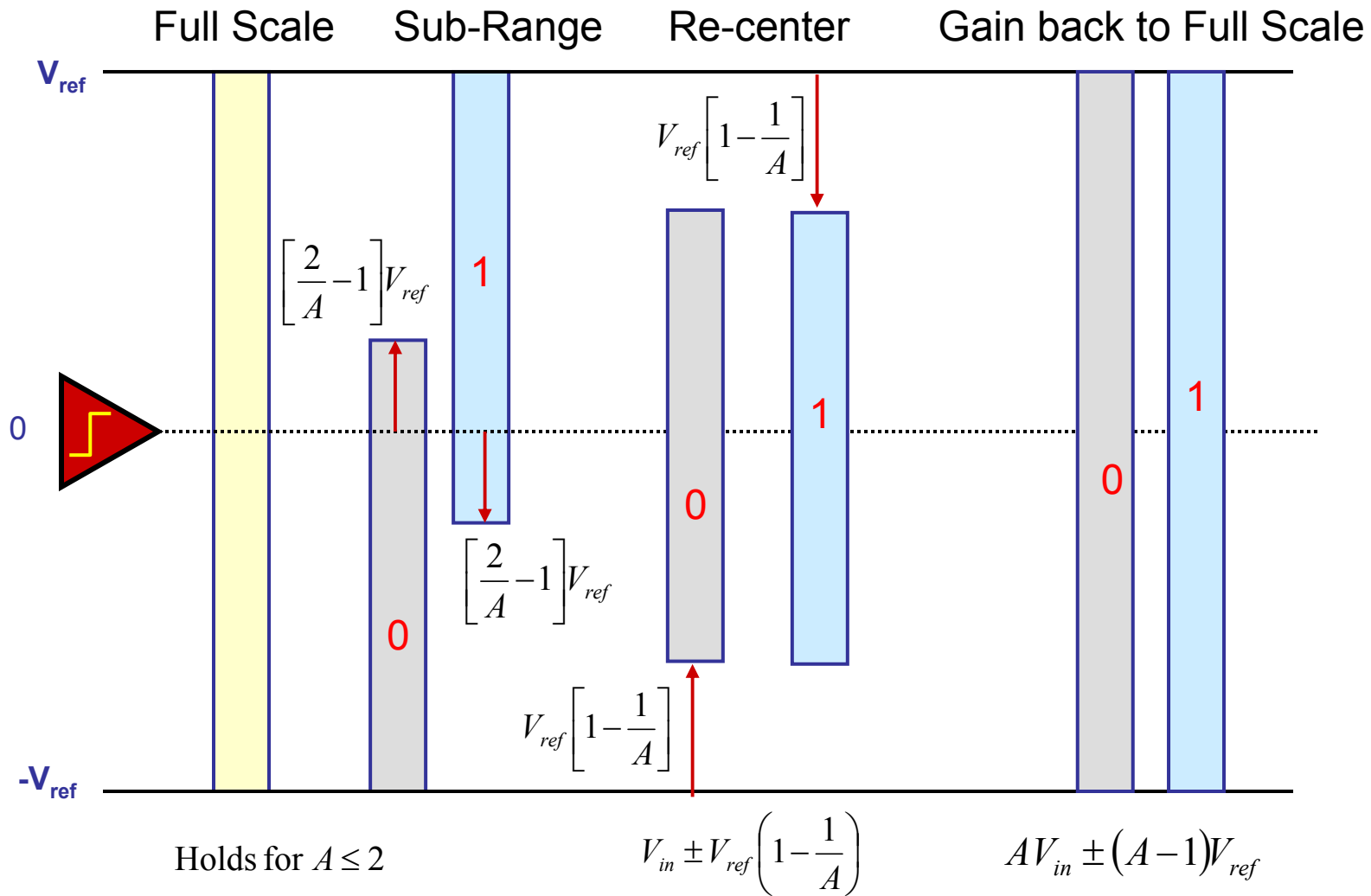


# Voltage Sub-Ranges: Example A=1.6

 

# Radix vs. Margin

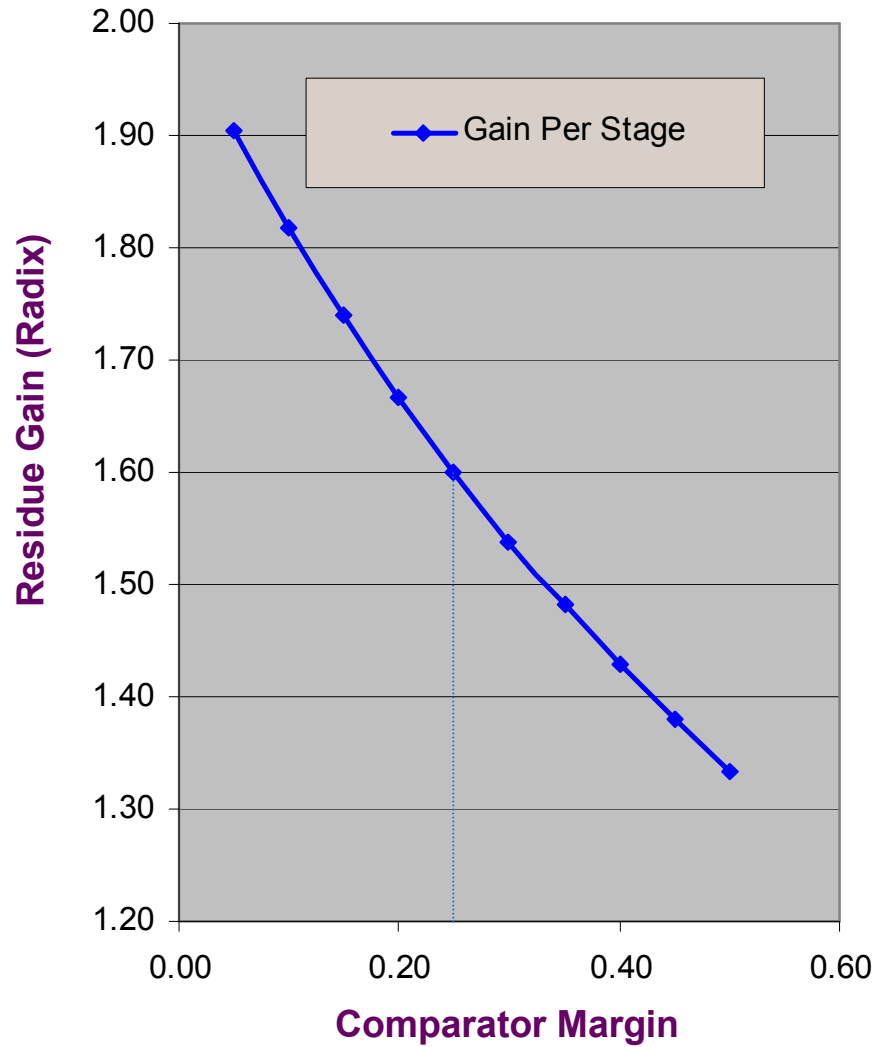

# Pipelined ADC: Radix Less Than Two

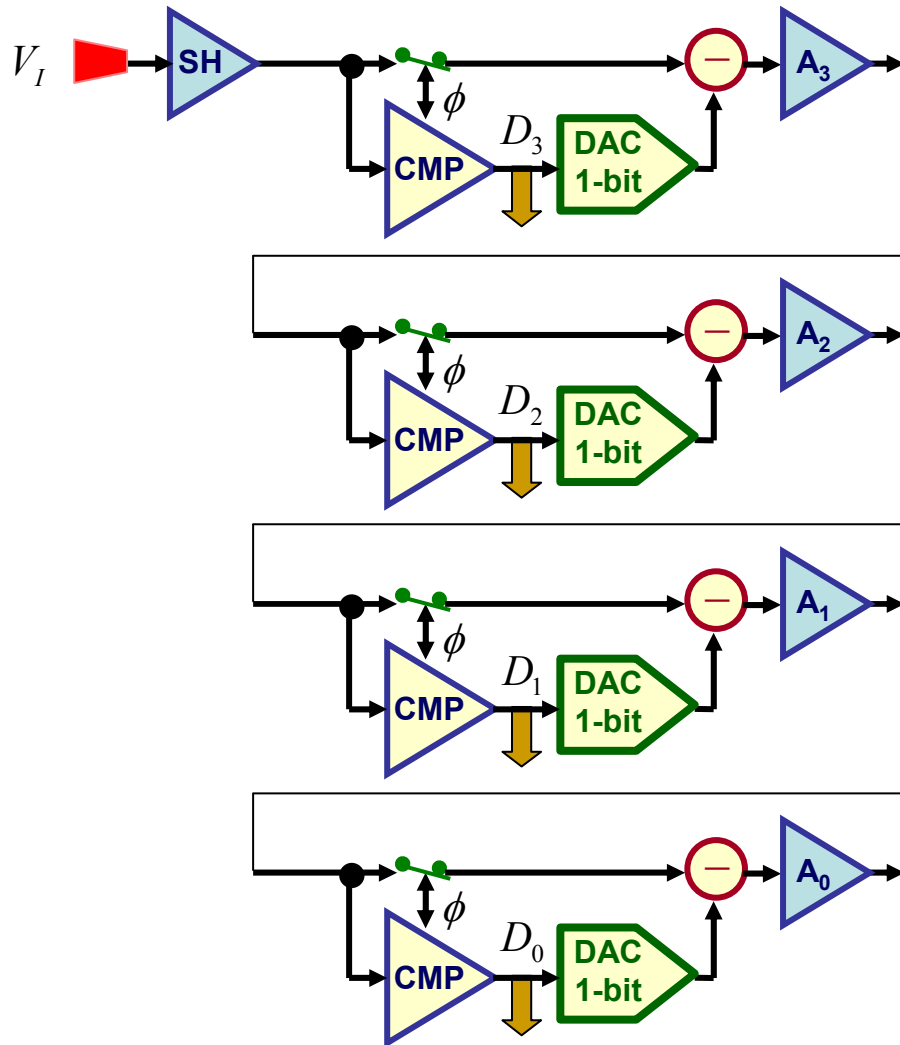


$$\frac{V_{IN}}{V_{ref}} \approx \frac{1}{A_3 A_2 A_1} [D_3 \quad D_2 \quad D_1 \quad D_0] \cdot \begin{bmatrix} A_3 A_2 A_1 \\ A_2 A_1 \\ A_1 \\ 1 \end{bmatrix}$$



# Doesn't Need to Be Switched Cap

## Pipeline ADC Block Diagram

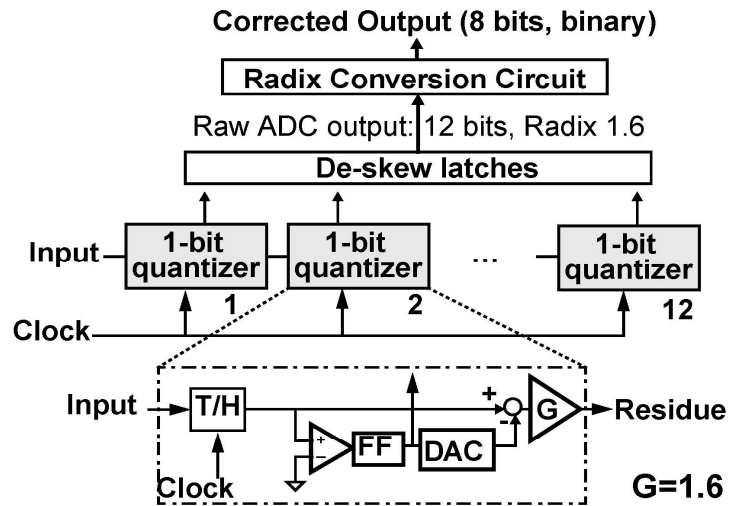


- Only 1 comparator per stage

© 2002 IEEE International Solid-State Circuits Conference

© 2002 IEEE

## Current-Mode ADC Stage

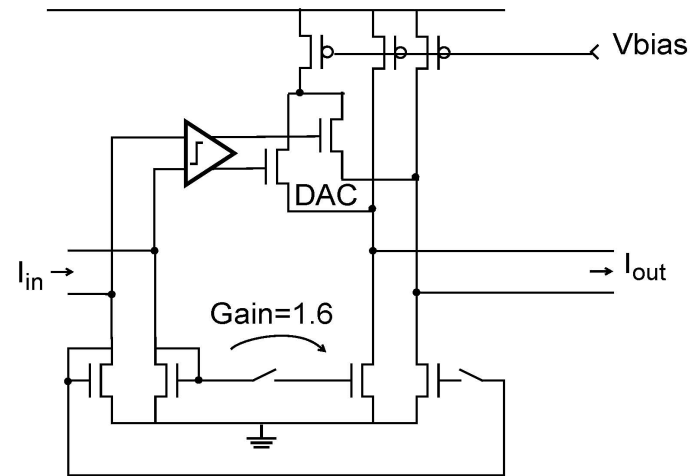


© 2002 IEEE International Solid-State Circuits Conference

© 2002 IEEE


Ken Poulton, Robert Neff, et al. , ISSCC 2002, ISSCC 2003
 
# Successive Approximation From Pipelined Ideas

Switched Capacitor Implementation  
Charge Sharing Principle



# Successive Approximation ADC

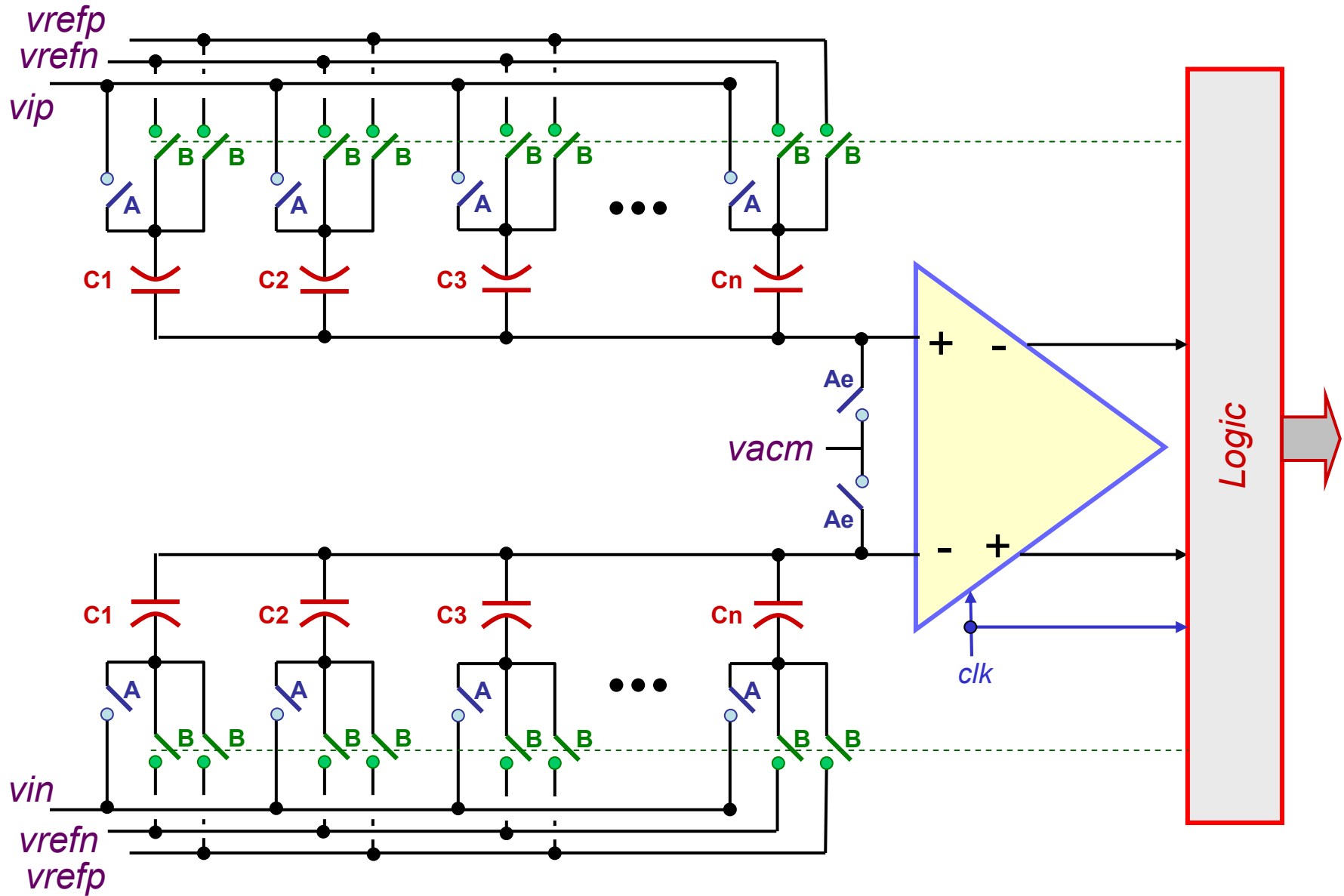

# SAR with Redundancy

**Radix 2  
No Redundancy**

- Full settling on each step
- Once mistake is made, you can't recover


Signal

**Radix 1.6  
With Redundancy**

- 3-bit settling
- Overlap of ranges allows for recovering from mistakes

Error

Signal

 



**Example Design**  
**Switched Capacitor Based**  
**10-bit**  
**200-MS/s**

---

*ISSCC 2008 Tutorial*

# Summary of Design Issues

- Capacitor size based on  $KT/C$ 
  - $C_{\text{total}} = 225\text{fF}$
- Opamp open-loop gain
  - $A_o < 60\text{dB}$
  - Calibration or correlated double-sample can reduce gain requirement
- Jitter
  - Clock jitter  $< 1.25\text{ps}$
- No Sample & Hold
  - Need care to ensure MDAC and CADC synchronization
- 2-Stage opamp
  - Dual common-mode feedback loop
  - Tail source on second-stage
- 2 bits per stage
  - 3-bit flash
- Coarse ADC
  - Use built-in reference to reduce capacitive load
  - Will require calibration





# Physical Limitations

---

*ISSCC 2008 Tutorial*


# ADC Basics: 3-Input Device

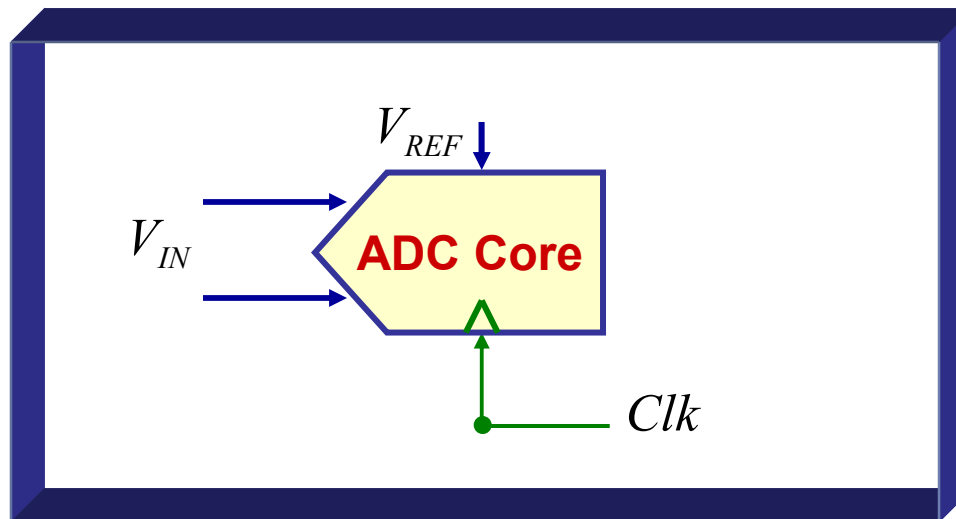 

ADC Performance depends on **ALL THREE** inputs



# Thermal Noise Limitations

 

Transfer Function

$$V_n(s) = V_r(s) \frac{1}{1 + sRC}$$

Output Noise Spectral Density

$$S_n(f) = S_r(f) \left| \frac{1}{1 + j2\pi fRC} \right|^2$$


Expected Noise Power

$$v_n^2 = 4kTR \int_0^\infty \frac{1}{1 + (2\pi fRC)^2} df = \frac{4kTR}{2\pi RC} \int_0^\infty \frac{1}{1 + x^2} dx = \frac{2kT}{\pi C} \int_0^{\pi/2} d\theta$$

$$v_n^2 = \frac{kT}{C}$$

Result is independent of R.  
Implies a more fundamental  
physical law

# Equipartition Theorem

 

Expected Value of Thermal Energy for 1-degree of freedom

$$E = \frac{1}{2} kT$$

Expected Value of Electrical Energy Stored on Capacitor


$$E = \frac{1}{2} C v_n^2$$

Expected Value of Squared Voltage on Capacitor

$$v_n^2 = \frac{kT}{C}$$
 
# RMS Quantization Noise

Quantization Error Probability Density Function



Uniform assumption for  
Quantization noise

$$V_{Q\sigma} = \frac{V_{\text{LSB}}}{\sqrt{12}} = 0.289V_{\text{LSB}}$$

rms Quantization Noise

$$V_{Q\sigma} = \frac{V_{\text{PP}}}{2^n \sqrt{12}}$$

Where  $V_{\text{PP}}$  is the full-scale  
Voltage and  $n$  is the # of bits

# Noise Requirements: Example Calculation

$$\frac{1}{2} \sigma_T^2 \cong \sigma_{\text{AMP}}^2 + \sigma_{\text{KT}}^2 = \frac{1}{2} \cdot \frac{V_{\text{LSB}}^2}{12}$$

Assume equal contribution of noise dominated from AMP and KT/C.

$$\sigma_{\text{AMP}} = \sigma_{\text{KT}} = \frac{1}{2} \cdot \frac{V_{\text{LSB}}}{\sqrt{12}} \approx \frac{V_{\text{LSB}}}{7}$$

For 1-Vpp input and a 10-bit ADC with a bandwidth of 1-GHz. The LSB is approximately 1-mV so that the rms noise requirement of the amp and KT/C is **144uV**

$$\frac{KT}{C} = (144\mu\text{V})^2$$

$$C = 225\text{fF}$$

$$4KTBR_{\text{EQ}} = (144\mu\text{V})^2$$

$$R_{\text{EQ}} = 1100\Omega$$

# Noise Requirements: 12-bit Example

For 1-V<sub>pp</sub> input and a 12-bit ADC. The LSB is approximately 0.25-mV so that the rms noise requirement of the amp and  $KT/C$  is 36 $\mu$ V

$$\frac{KT}{C} = (36\mu\text{V})^2$$

$$C = 3.6\text{pF}$$

$$4KTBR_{\text{EQ}} = (36\mu\text{V})^2$$

$$R_{\text{EQ}} = 70\Omega$$

# 12-bit Example: High Vref and High Vdd

For 2-V<sub>pp</sub> input and a 12-bit ADC. The LSB is approximately 0.5-mV so that the rms noise requirement of the amp and KT/C is 72uV

$$\frac{KT}{C} = (72\mu\text{V})^2$$

$$C = 900\text{fF}$$

$$4KTBR_{\text{EQ}} = (72\mu\text{V})^2$$

$$R_{\text{EQ}} = 275\Omega$$

## **For High Accuracy ADCs**

- The higher the Vref the better
- This requires large voltage (High Vdd is essential)
- gm of 1/70 requires a lot of current
- Good to have gain in Sample & Hold to ease noise requirements of MDAC
- Can give up some SNR performance to ease power requirements: Giving up an additional 0.5-bits of noise cuts the cap in half and doubles Req




# Minimal Capacitance for a Given Ideal SNR

Thermal Noise set to Quantization Noise

$$v_{rms} = \sqrt{\frac{kT}{C}} = \frac{V_{pp}}{2^n \sqrt{12}}$$


Minimum value of input capacitance
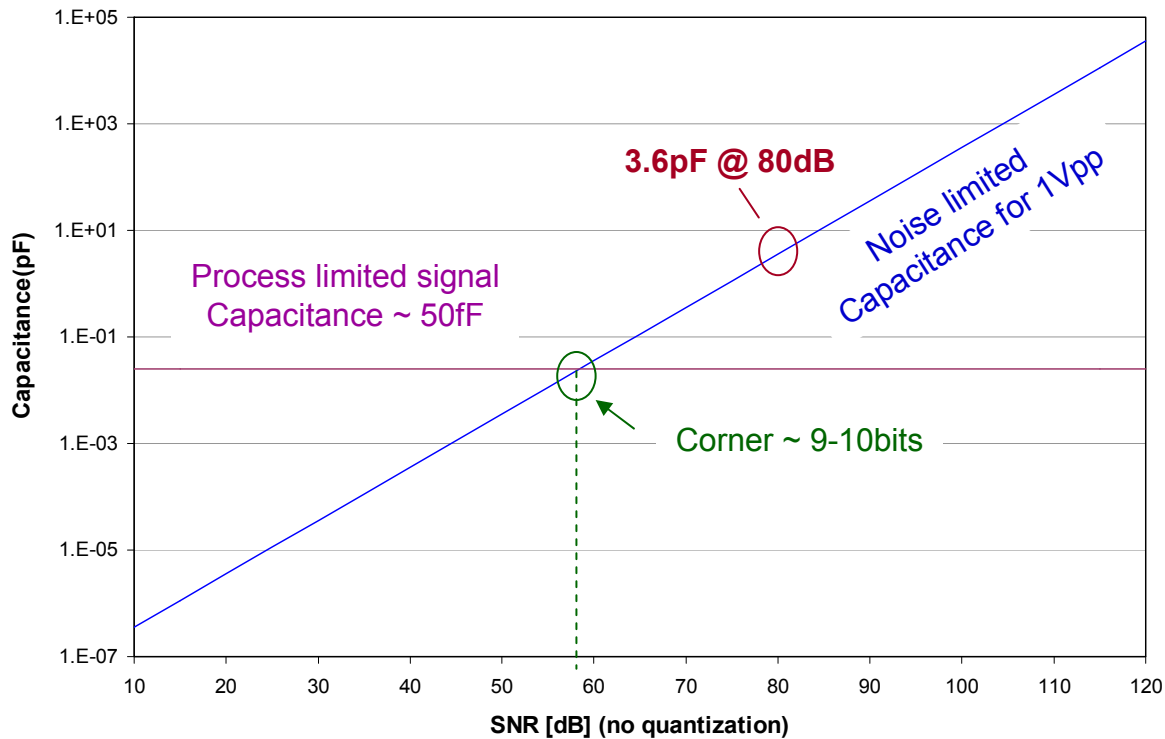
$$C = \frac{12kT}{V_{pp}^2} \cdot 2^{2n}$$




Additional Slide
 
# Limitations Due to Timing Jitter for Sine Input



$$\Delta V(t) = \Delta t(\pi f_{in}) \cdot V_{PP} \cos[2\pi f_{in} t]$$

# Expression for SNR due to Jitter

 


$$V_{inrms} = \sqrt{\text{avg} \left[ \left( \frac{V_{PP}}{2} \sin[2\pi \cdot f_{in} (t + \Delta t)] \right)^2 \right]} = \frac{V_{PP}}{2\sqrt{2}}$$

$$\Delta V_{rms} = \Delta t_{rms} (\pi f_{in}) \cdot V_{PP} \cdot \sqrt{\text{avg}(\cos^2[2\pi f_{in} t])} = 2\pi f_{in} \Delta t_{rms} \frac{V_{PP}}{2\sqrt{2}}$$

$$\frac{\Delta V_{rms}}{V_{inrms}} = \frac{1}{SNR} = 2\pi f_{in} \Delta t_{rms}$$

# Jitter Requirement for 10-bit

 

SNR due to Quantization =  $6.02(10) + 1.76 \sim 62\text{dB}$


$$\frac{1}{62\text{dB}} = 2\pi f_{\text{in}} \Delta t_{\text{rms}}$$

$f_{\text{in}} = \text{Nyquist @ } f_s = 200\text{-MHz}$

$$\Delta t_{\text{rms}} = \frac{T_s}{\pi \cdot \text{SNR}} = \frac{5\text{ns}}{\pi \cdot \text{SNR}}$$

$$\Delta t_{\text{rms}} < 1.26\text{ps}$$

# ADC Speed and Resolution

 

B. Murmann, "ADC Performance Survey 1997-2007," [Online]. Available: <http://www.stanford.edu/~murmann/adcsurvey.html>.




**Circuit Implementation  
Switched Capacitor Based  
10-bit  
200-MS/s**


---

*ISSCC 2008 Tutorial*

# Pipelined ADC Architecture

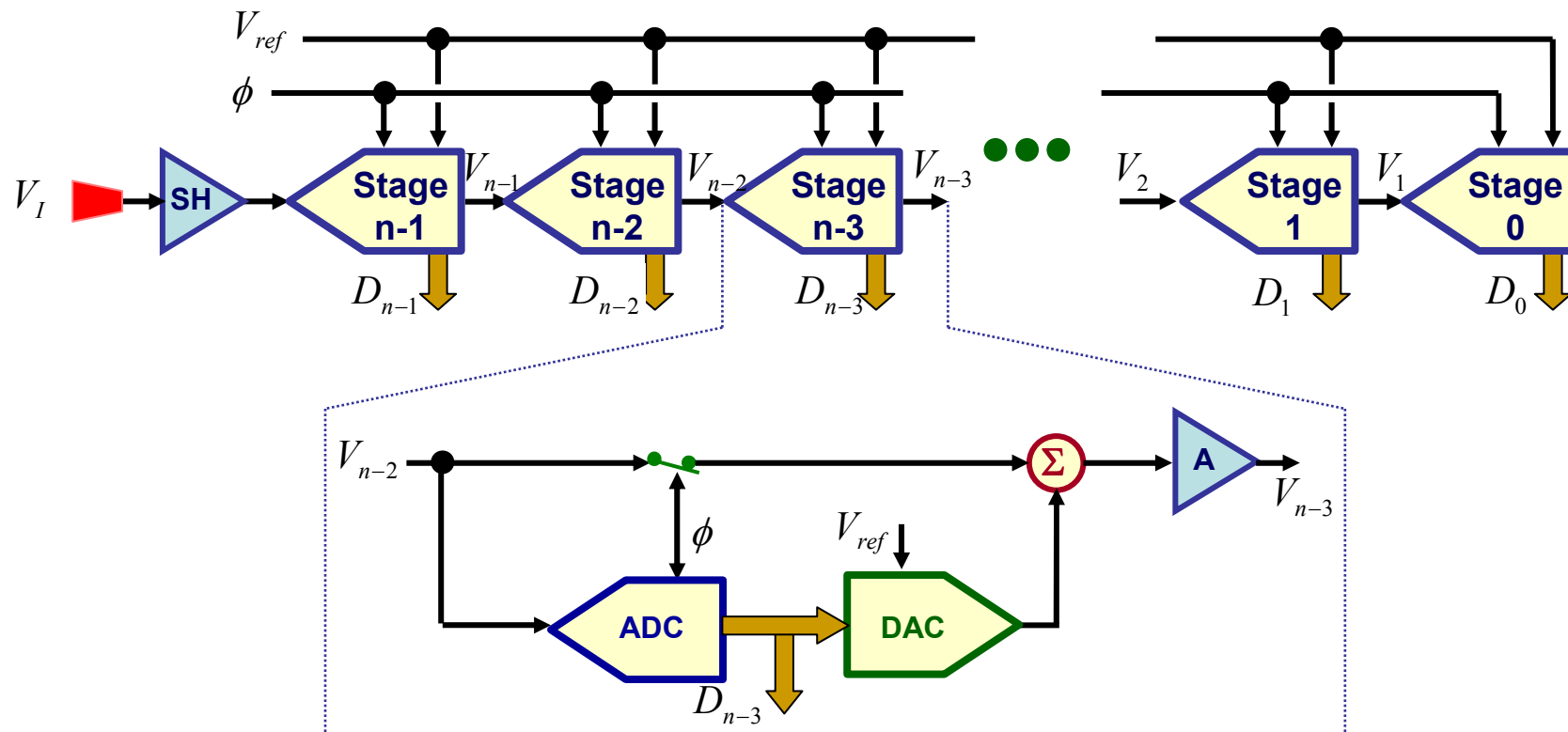


# Thick Oxide vs. Thin Oxide

 


$$C \propto \frac{1}{V_{pp}^2}$$

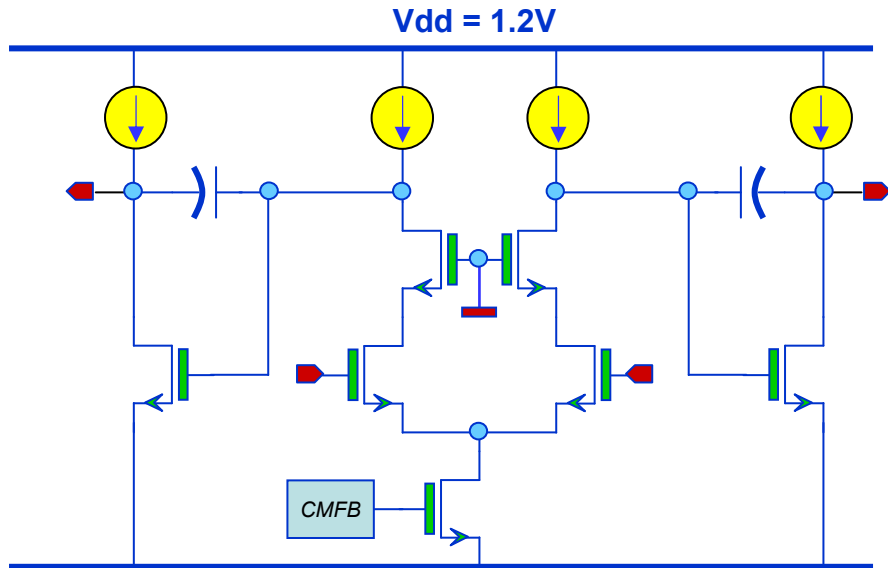Doubling voltage swing will reduce Capacitive load by factor of 4x




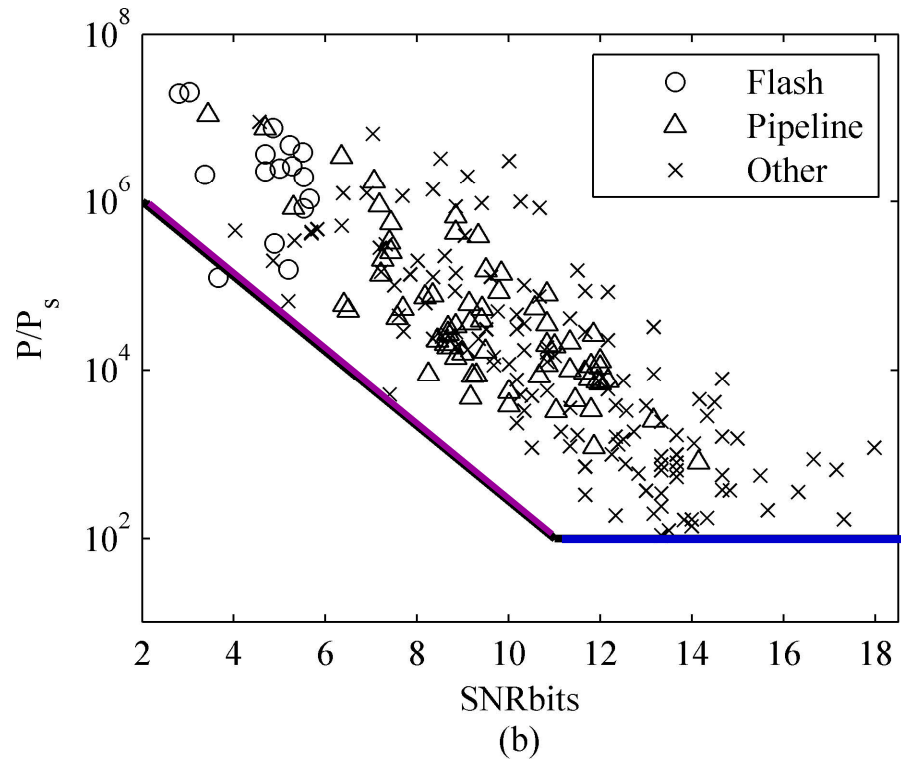
# Noise Limited Corner: Normalized Energy vs. SNR




[6] B. Murmann, T. Sundstrom and Christer Svenson, "On the Power Dissipation of High-Speed Analog-to-Digital Converters," *IEEE Trans. Circuits and Systems*, [to be published] submitted 26 Nov 2007.

Additional  
Slide

- **Normalizing ADC power by the  $KT/C$  Limit ( $P_s$ ) is useful**
  - Clearly shows State of the Art with respect to  $P_s$
  - Shows best high SNR ADCs  $\sim 100x$  Thermal Power Limit
  - Identifies noise limited circuit corner at roughly 11-bits

# Open-Loop DC Gain Requirement

 

Closed loop Gain

$$A = \frac{A_o}{1 + A_o\beta} \cong \frac{1}{\beta} \cdot \left( 1 - \frac{1}{A_o\beta} \right)$$

Normalized Gain Error

$$\varepsilon = \frac{1}{A_o\beta}$$

Accuracy Required Scales with Gain

$$\varepsilon = A\varepsilon_0 \approx \frac{\varepsilon_0}{\beta}$$


Closed Loop Gain Independent of  $\beta$

$$A_o > \frac{1}{\varepsilon_0} \approx 2^n$$




[3] 30.1 An Over-60dB True Rail-to-Rail Performance Using Correlated Level Shifting and an Opamp with 30dB Loop Gain  
1:30 PM  
B. Gregoire, U-K. Moon

# Sample & Hold: Yes or No

 

No SHA: Total Input Referred Noise Power

$$v_{TOT}^2 = v_n^2$$

 

SHA: Input Referred Noise Power

$$v_{TOT}^2 = v_{SH}^2 + v_{ADC}^2$$


To achieve  $kT/C$  Noise Performance with No SHA

$$v_{SH}^2 = v_{ADC}^2 = \frac{v_n^2}{2}$$

$$\frac{kT}{C} = \frac{kT}{2C} + \frac{kT}{2C}$$

**Total Capacitance Increases with SHA by 4x**  
 ■ Total power increase 2-4x

# Pipelined ADC with No Sample & Hold

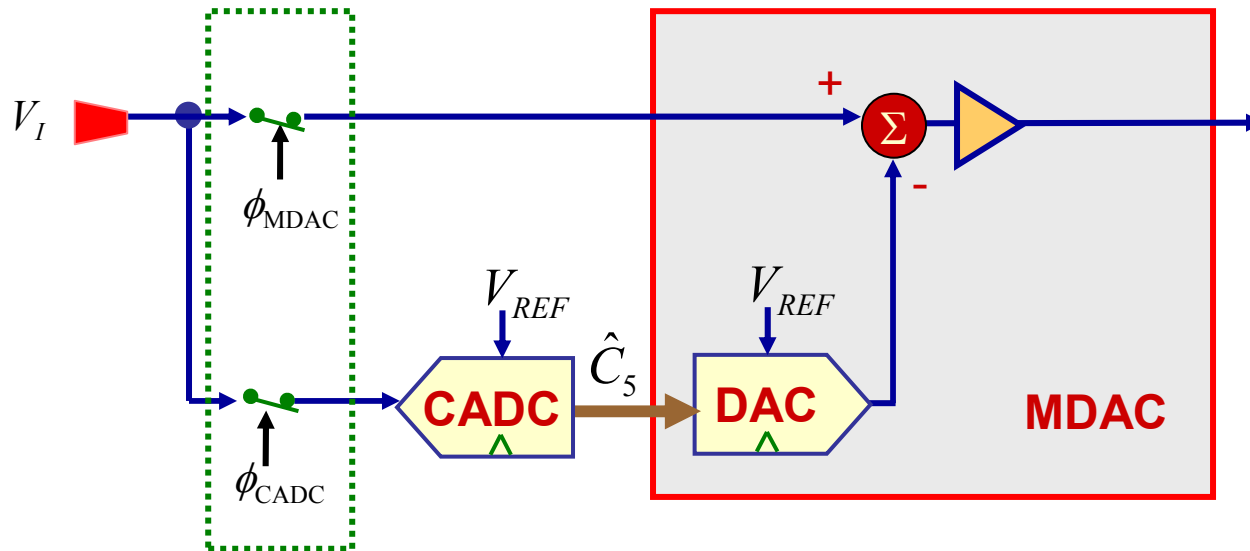

## Sampling occurs in two places

- Dual sampling must be synchronized to avoid skew




[4] I. Mehr and L. Singer, "A 55-mW 10-bit 40-Msample/s Nyquist-rate CMOS ADC," *IEEE J. Solid-State Circuits*, vol. 35, pp. 318–325, Mar. 2000.



[5] 12.6 A 14b 100MS/s Pipelined ADC with a Merged Active S/H and First MDAC 11:15 AM

B. Lee, B. Min, G. Manganaro, J. W. Valvano

# Scaling

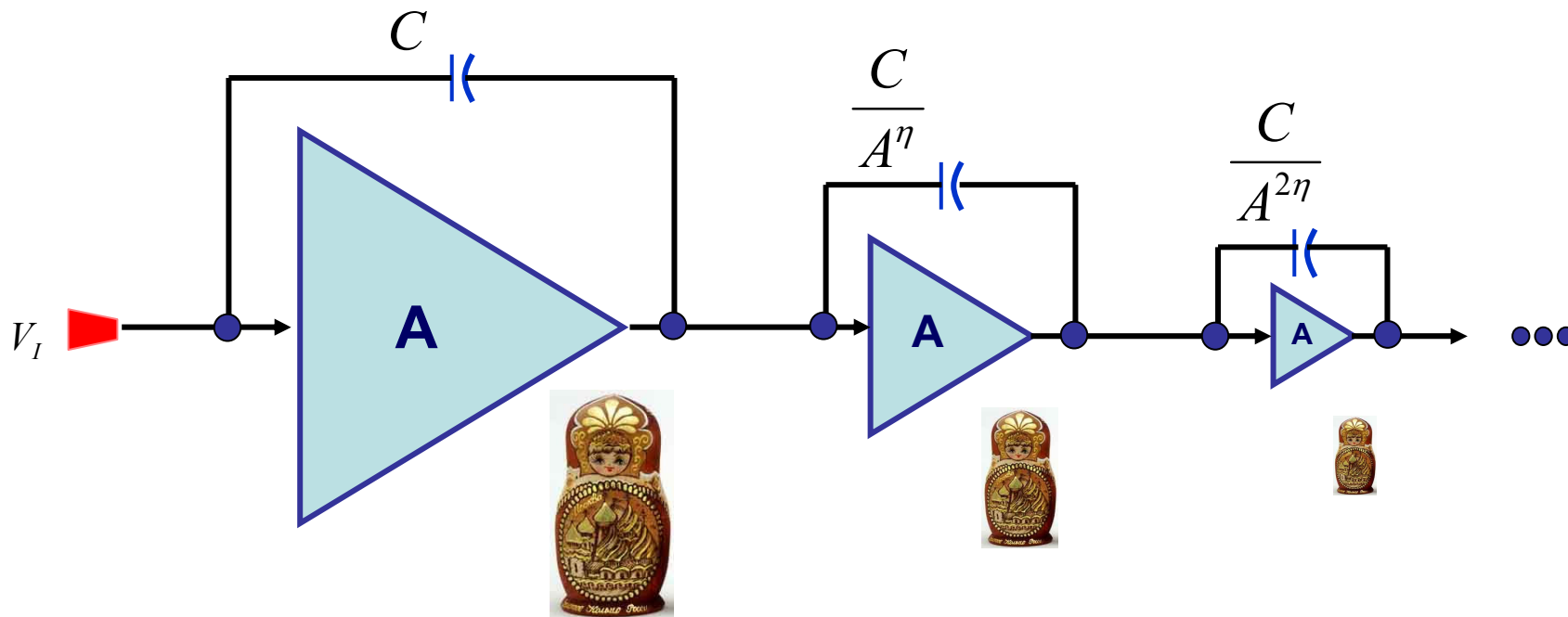

$\eta = 2$  Noise contribution (input referred) of each stage is equal


$\eta = 1$  Noise contribution is reduced by  $\sqrt{2}$  for each stage  
Recommended scaling [1,2]




[1] Y. Chiu, "High-Performance Pipeline A/D Converter Design in Deep-Submicron CMOS," *PhD Dissertation, UC Berkeley*, 2004.

[2] D. W. Cline and P. R. Gray, "A power optimized 13-b 5 MSamples/s pipelined analog-to-digital converter in 1.2 $\mu$ m CMOS," *IEEE J. Solid-State Circuits*, vol. 31, no. 3, pp. 294-303, March 1996.

# Number of Bits Resolved per Stage: Tau

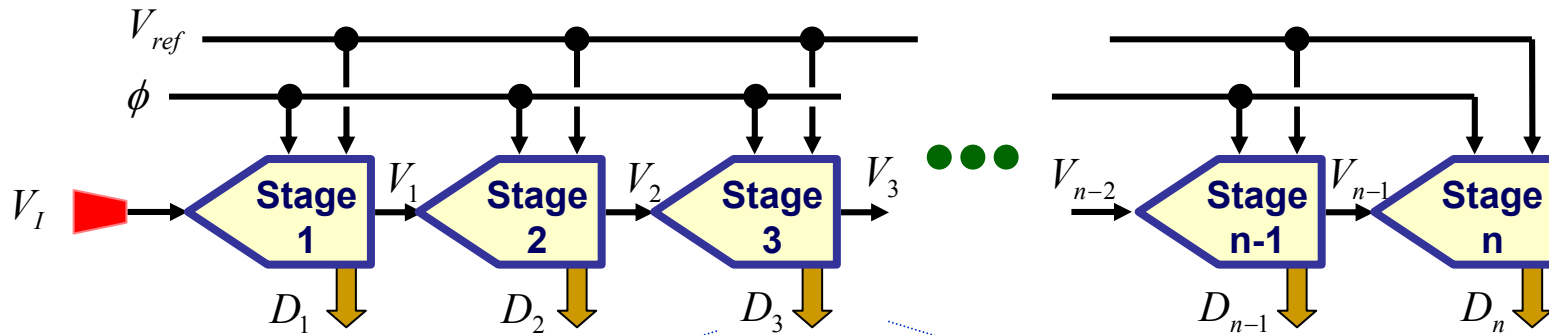

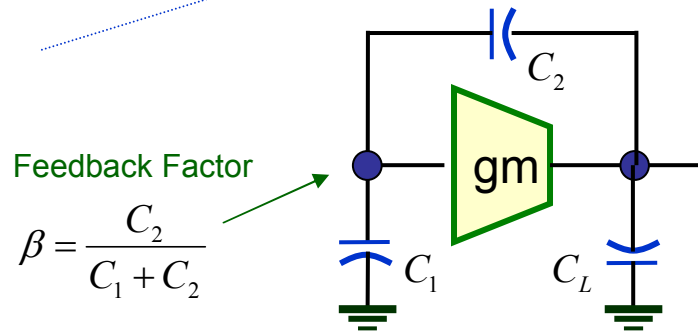Closed-loop time constant of MDAC amplifier



$$\tau = \frac{1}{g_m \beta} \cdot \left[ C_L + \frac{C_1 C_2}{C_1 + C_2} \right] ; \tau = \frac{C_L A}{g_m} + \frac{C_1}{g_m}$$


Load is reduced by scaling  $C_L A = C$

$$\tau \approx \frac{C}{g_m} + \frac{C(1-1/A)}{g_m}$$


**With scaling tau is roughly Independent of gain**

▪ slightly faster with smallest gain
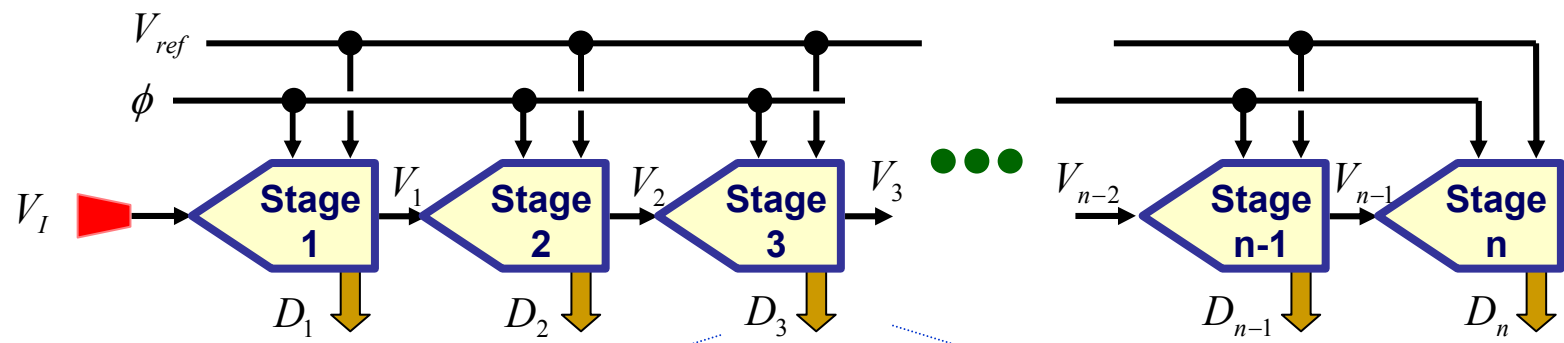
# Number of Bits Resolved per Stage: Settling



settling of MDAC amplifier

 

for $A=2$	for $A=4$
$t_2 \approx \frac{3}{2} \cdot \frac{C}{g_m} \cdot 9 \ln(2)$	$t_4 \approx \frac{7}{4} \cdot \frac{C}{g_m} \cdot 8 \ln(2)$
$t_2 \approx 9.36 \cdot \frac{C}{g_m}$	$t_4 \approx 9.7 \cdot \frac{C}{g_m}$


**2 or 3 bits per stage is best choice**

- Shown in [1,2]
- Agrees with survey of published ADCs
- Beyond 3 bits, the coarse flash becomes problematic



[1] Y. Chiu, "High-Performance Pipeline A/D Converter Design in Deep-Submicron CMOS," *PhD Dissertation, UC Berkeley*, 2004.  
 [2] D. W. Cline and P. R. Gray, "A power optimized 13-bit 5 MSamples/s pipelined analog-to-digital converter in 1.2μm CMOS," *IEEE J. Solid-State Circuits*, vol. 31, no. 3, pp. 294-303, March 1996.

# Two-Stage Amplifier with Dual CMFB

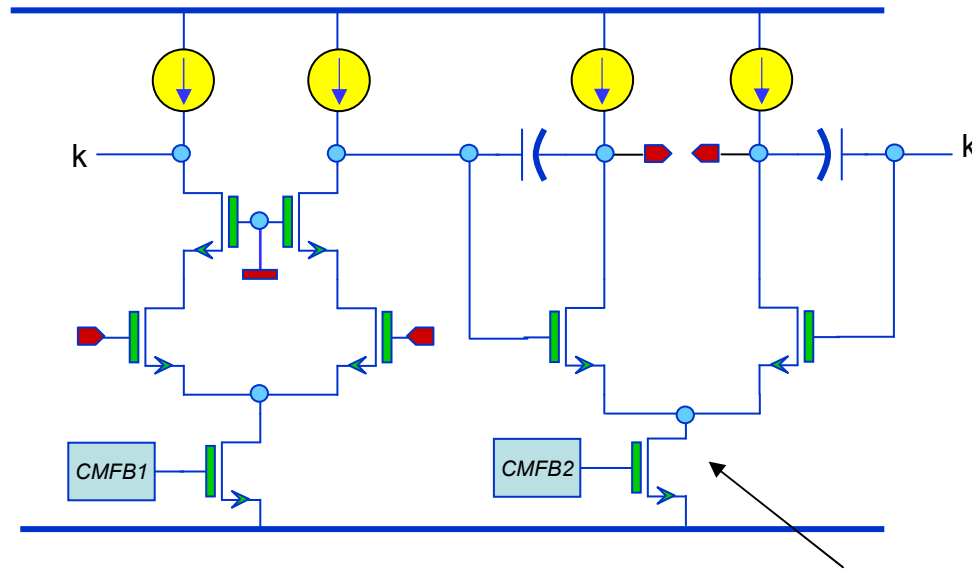

**Reduced swing due to tail source**

- dual diffpair has advantages
- common-mode does not affect bias



**[6] A 3-V 340-mW 14-b 75-Msample/s CMOS ADC With 85-dB SFDR at Nyquist Input**


Wenhua Yang, Dan Kelly, Iuri Mehr, Mark T. Sayuk, and Larry Singer, IEEE JSSC, vol. 36, no. 12, Dec 2001. pp 1931-1936.

**[7] A cost-efficient high-speed 12-bit pipeline ADC in 0.18- $\mu\text{m}$  digital CMOS**

Andersen, T.N.; Hernes, B.; Briskemyr, A.; Telsto, F.; Bjornsen, J.; Bonnerud, T.E.; Moldsvor, O. Solid-State Circuits, IEEE Journal of Volume 40, Issue 7, July 2005 Page(s): 1506 - 1513




# Pipelined ADC Switched Capacitor MDAC

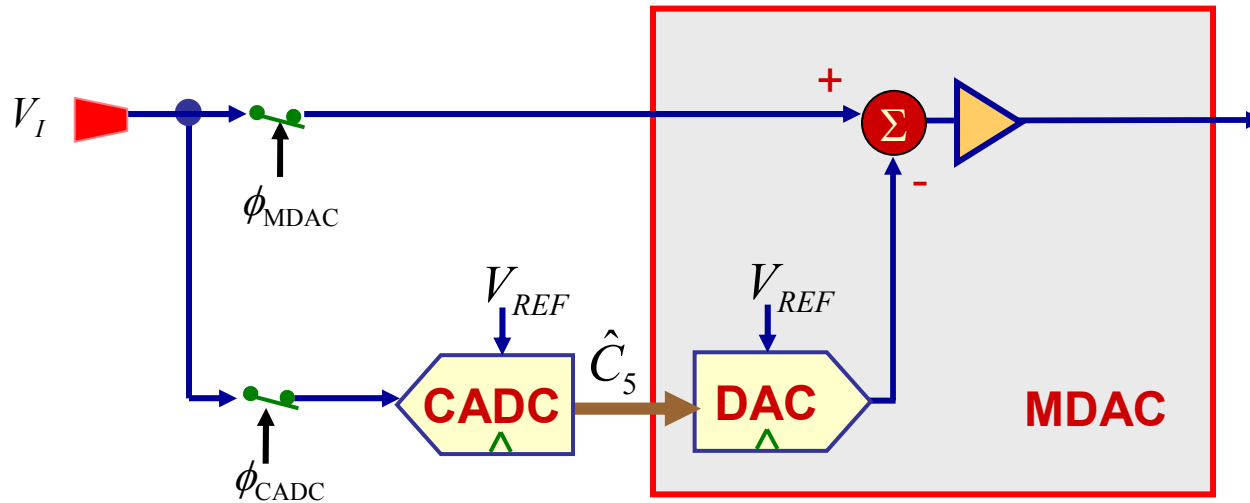


*MDAC can be implemented efficiently as a Switched Capacitor Circuit*


# 1-bit MDAC Stage

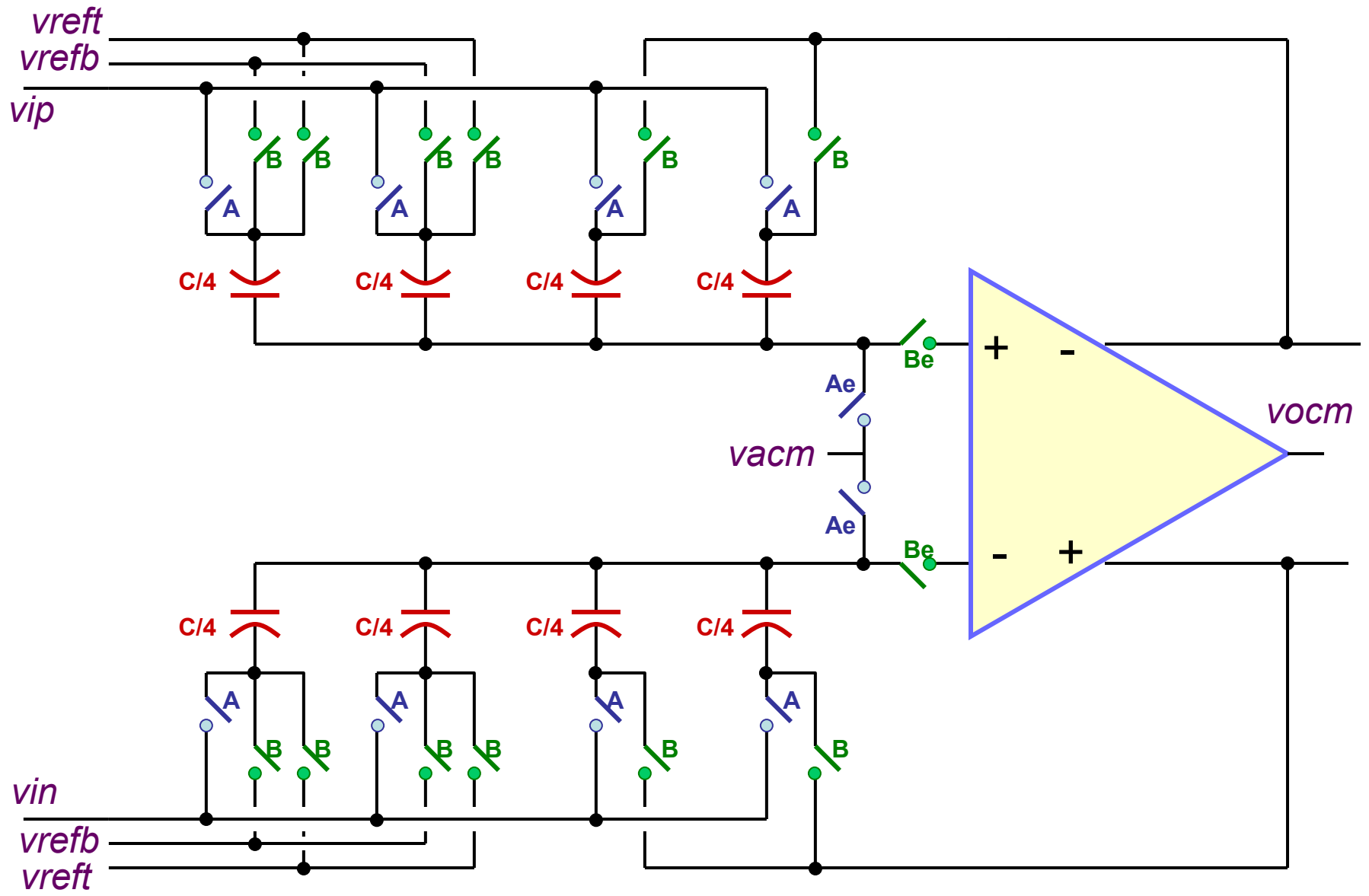


# 1-bit MDAC Stage

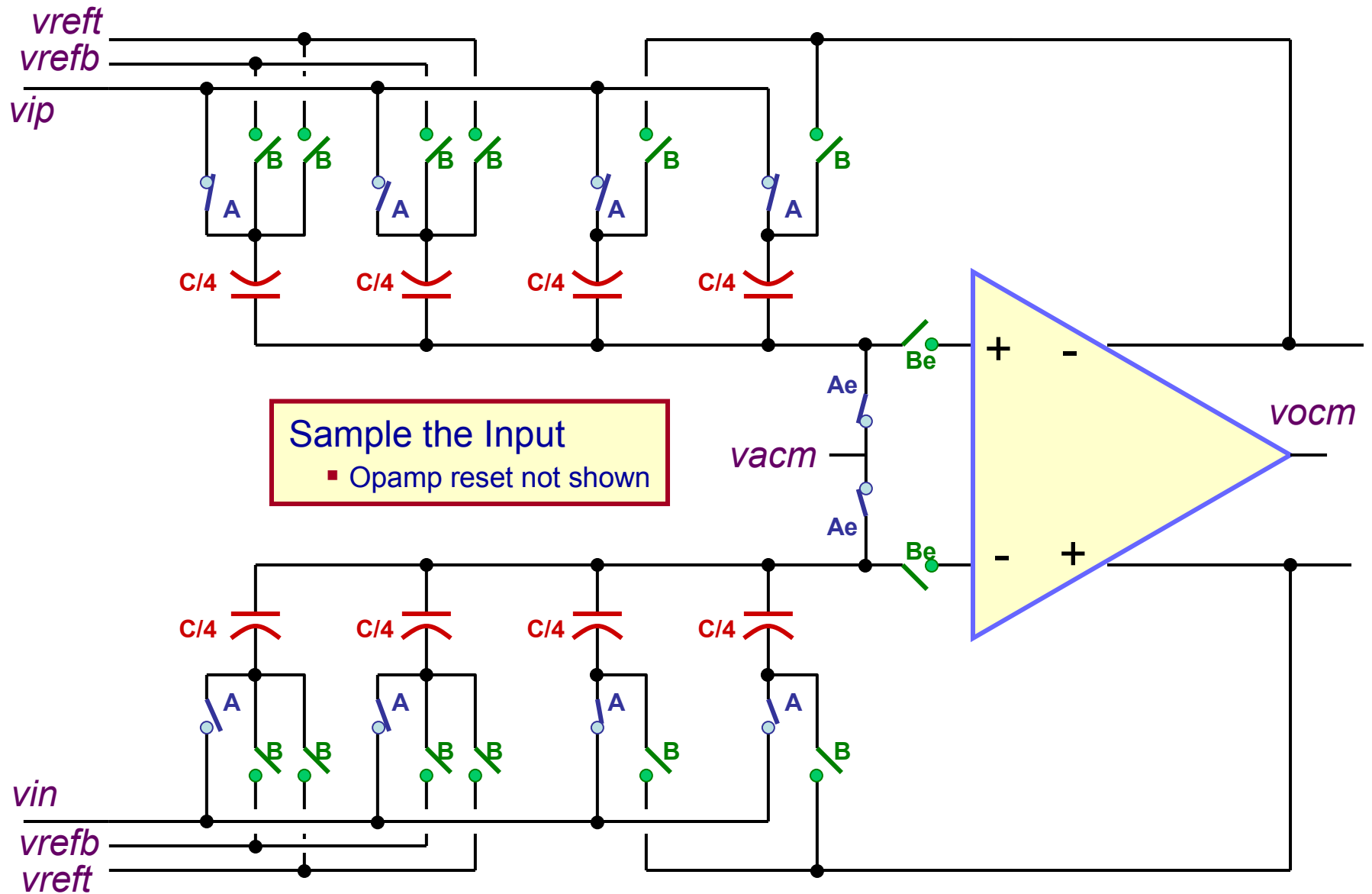


# 1-bit MDAC Stage

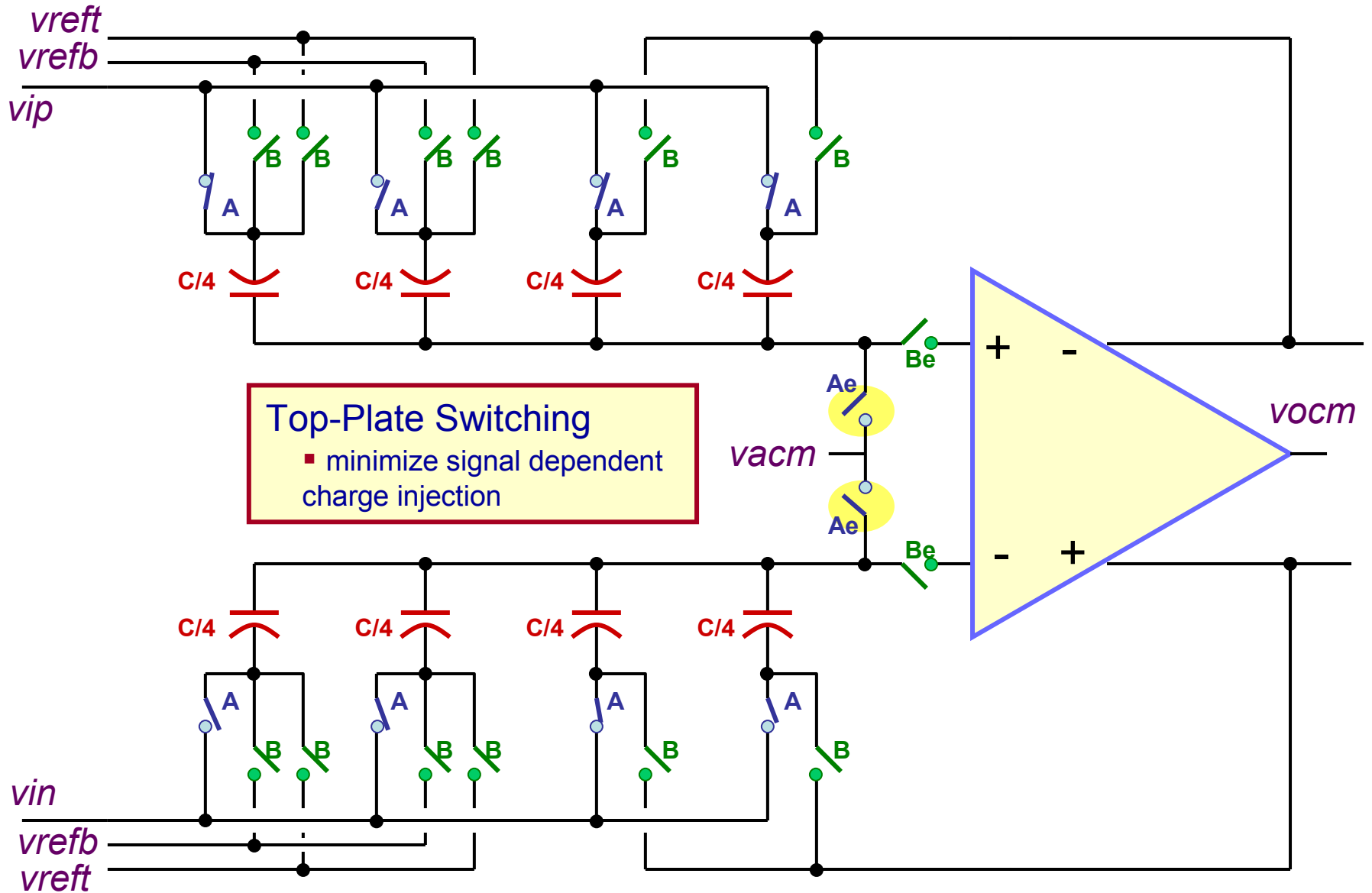


# 1-bit MDAC Stage

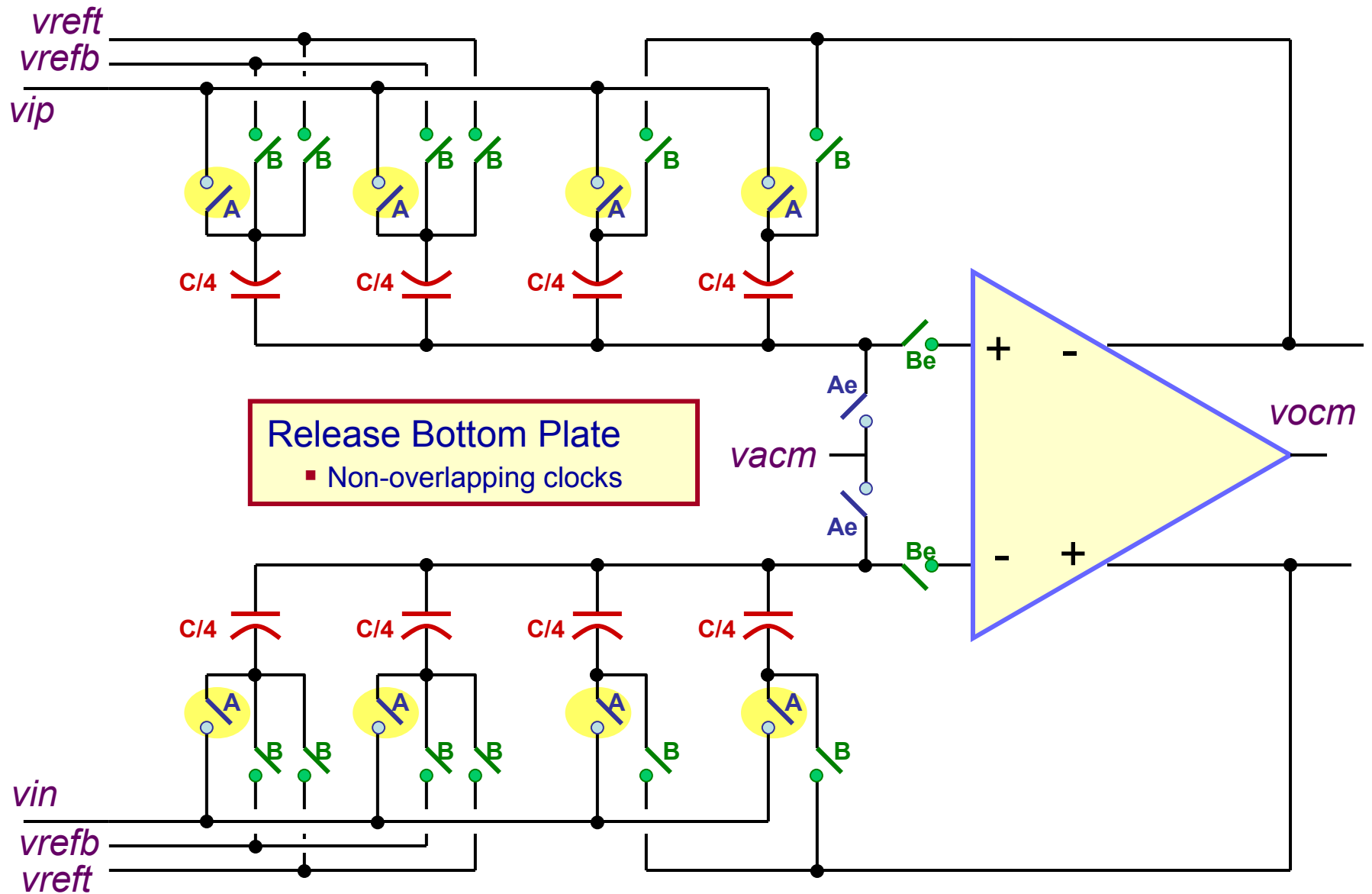


# 1-bit MDAC Stage

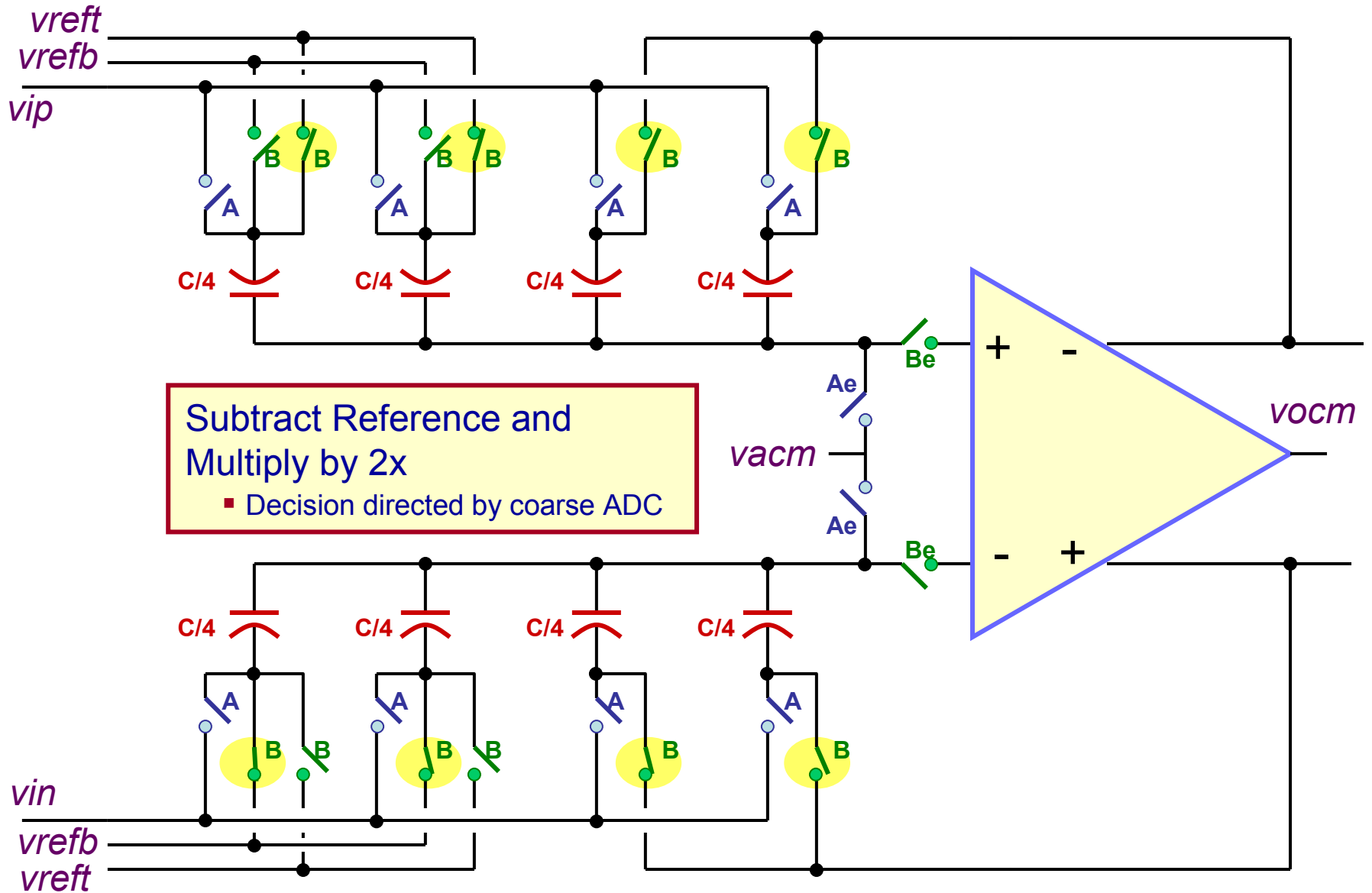

# 1-bit MDAC Stage

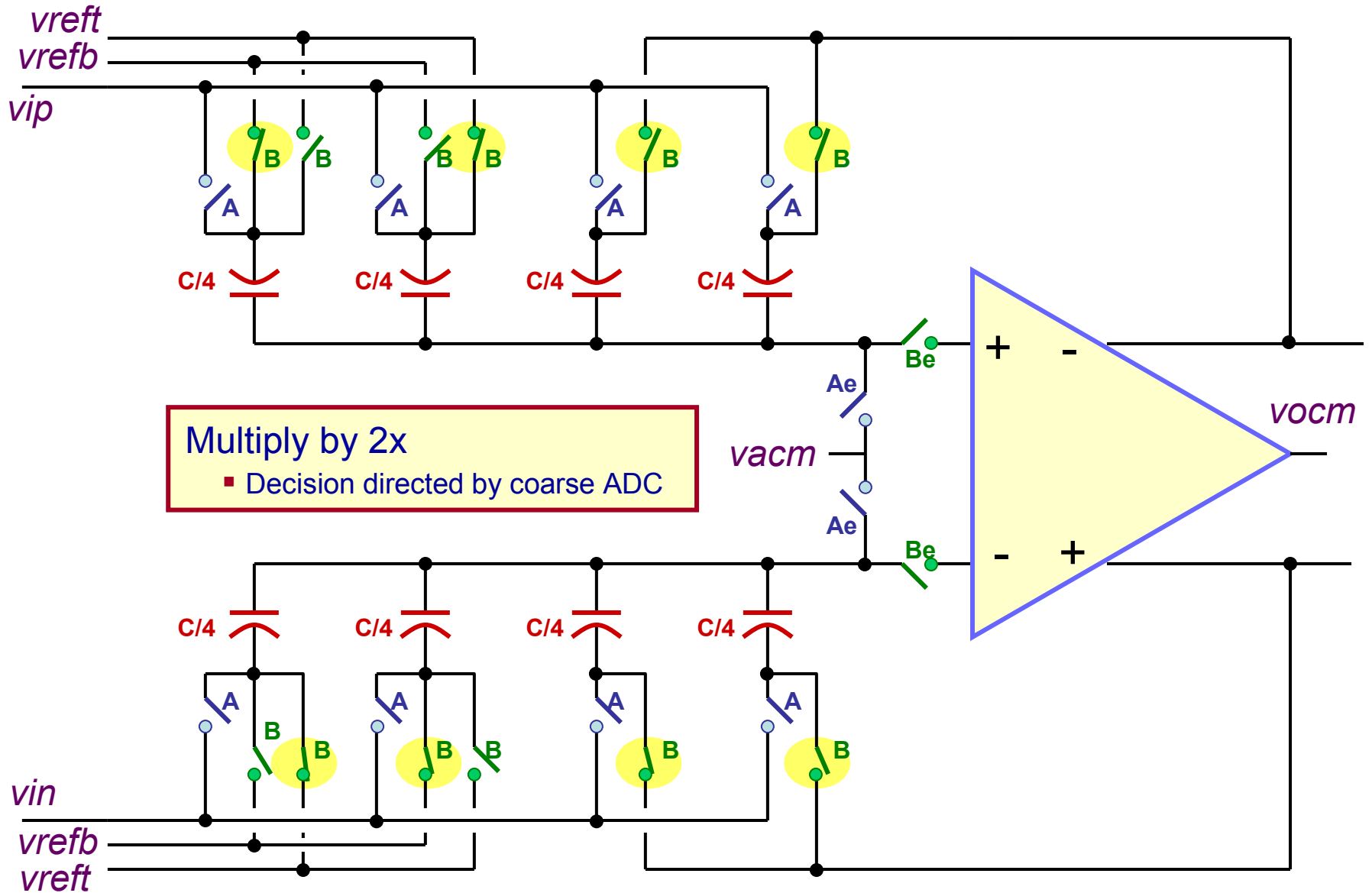


# 1-bit MDAC Stage

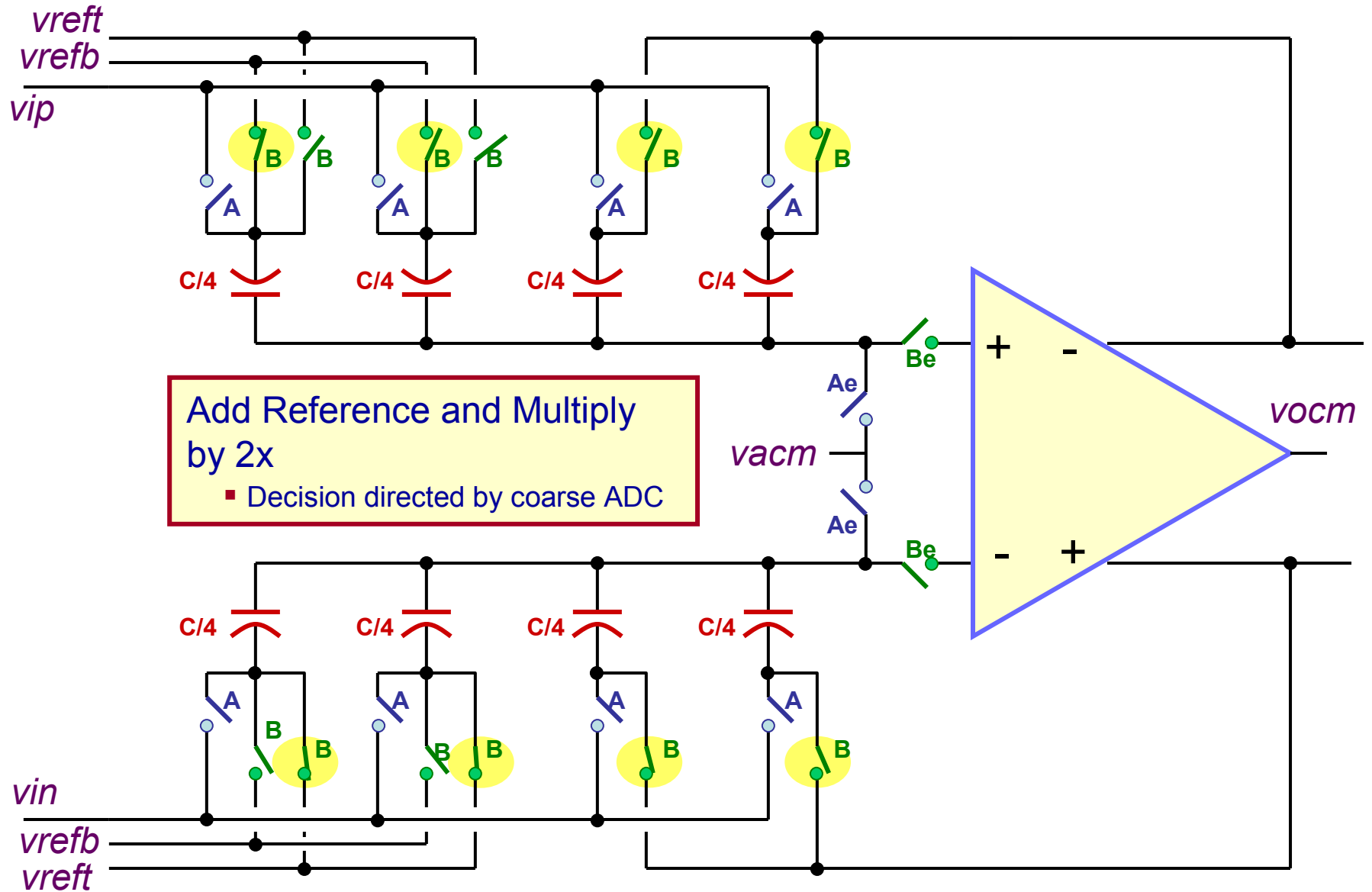





# Opamp Sharing: Adjacent

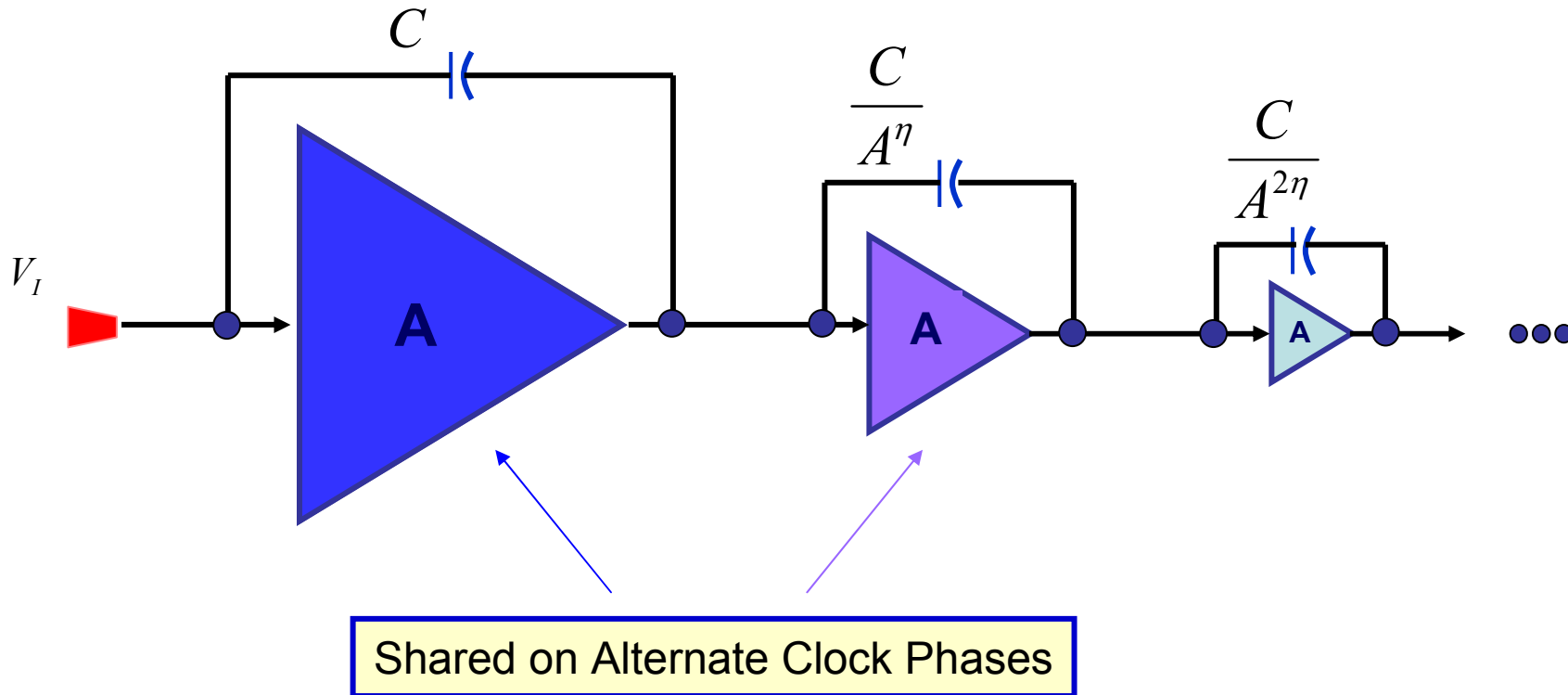

# Opamp Sharing: Ping-Pong

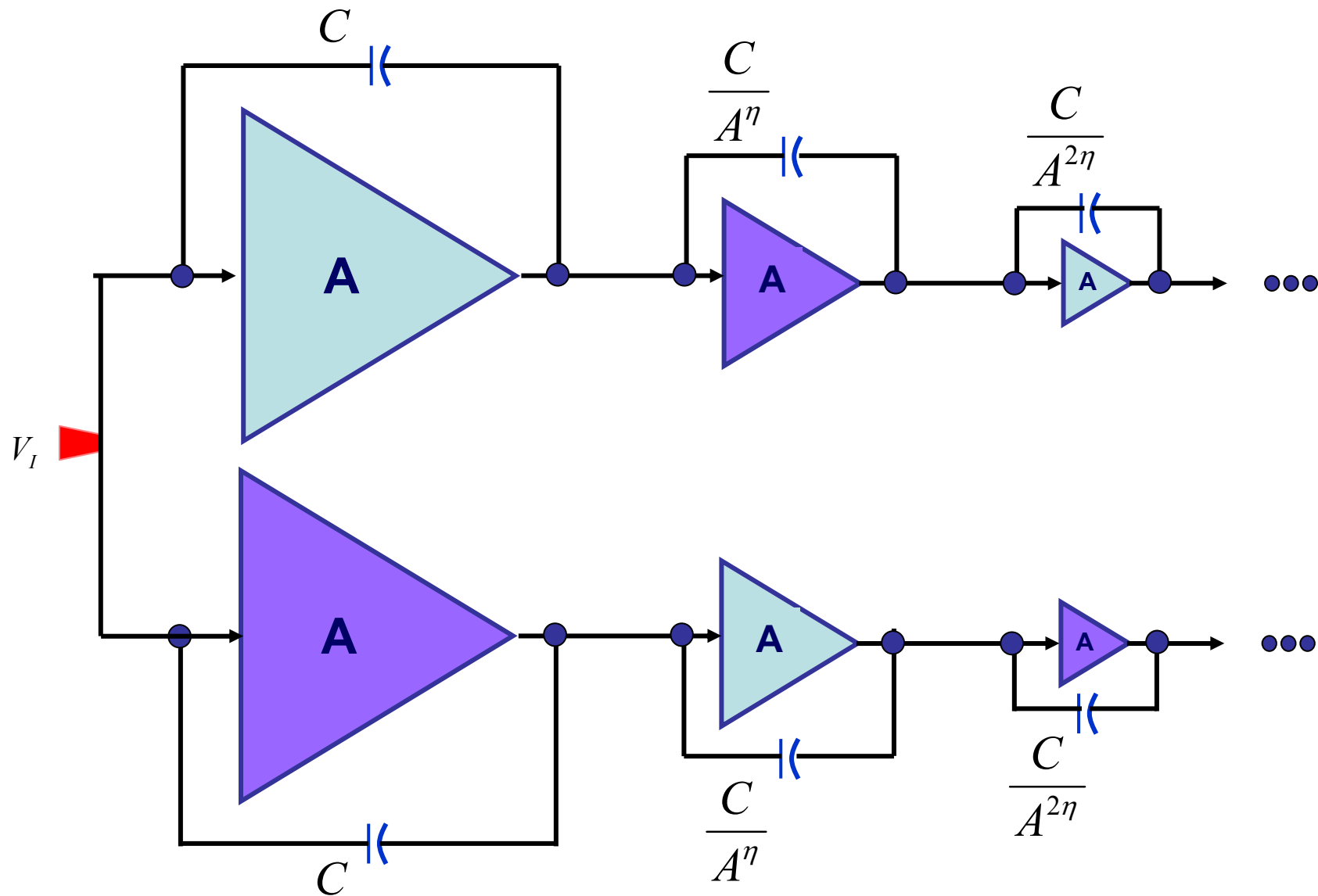

# Opamp Sharing: Ping-Pong

 


All Opamps Shared on Alternate Clock Phases

- Requires dual cap arrays
- Incomplete settling causes signal dependant distortion


# Coarse ADC

R Ladder

 

**Static Power dissipation**

SC Reference Gen, Abo [8]

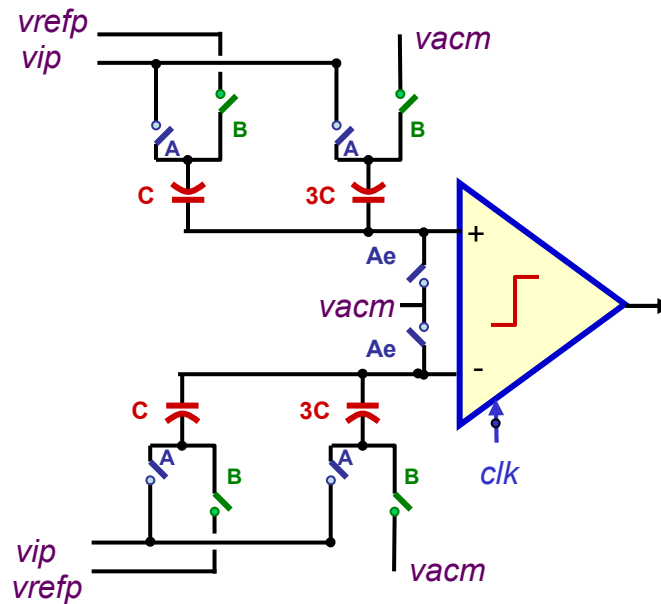


**Adds load to MDAC  
Cap ratios get big beyond 2-3 bits per stage**

Built-in Mismatch



 

[12.3] A 150MS/s 133μW 7b ADC in 90nm Digital CMOS Using a Comparator-Based Asynchronous Binary-Search Sub-ADC  
9:30 AM  
G. Van der Plas, B. Verbruggen



**Lowest power  
Needs calibration**

# Design Issues: Advanced Concepts

- Bootstrapped switch
  - Not needed at 10-bits, but necessary beyond, Abo [8], Hui Pan [9]
- Opamp Sharing – Ping Pong
  - Use dual cap array to utilize opamp at all times, Gupta [10]
  - Be careful for charge sharing (cross-talk, or ISI)
- Adaptive biasing
  - Power dissipation scaled optimally with sample rate, Geelen [11]
- Time Interleaving
  - Poulton [12], Gupta [10]
- Calibration 

*Paradigm shift*

  - Big improvements in performance and huge power reduction
  - Boris Murmann, Ian Galton, Paul Gray, Steve Lewis, Bang Sup Song and more ....

# Advanced Concepts References

**[8] A 1.5-V, 10-bit, 14.3-MS/s CMOS pipeline analog-to-digital converter**

Abo, A.M.; Gray, P.R.  
Solid-State Circuits, IEEE Journal of  
Volume 34, Issue 5, May 1999 Page(s):599 - 606

**[9] A 3.3 V, 12b, 50MSample/s A/D converter in 0.6  $\mu\text{m}$  CMOS with over80 dB SFDR**

Hui Pan Segami, M. Choi, M. Jing Cao Hatori, F. Abidi, A.  
JSSC, vol. 35, issue 12, dec 2000, pp. 1769-1780

**[10] A 1-GS/s 11-bit ADC With 55-dB SNDR, 250-mW Power Realized by a High Bandwidth Scalable Time-Interleaved Architecture**


Gupta, S. K.; Inerfield, M. A.; Wang, J.  
Solid-State Circuits, IEEE Journal of  
Volume 41, Issue 12, Dec. 2006 Page(s):2650 - 2657

**[11] A 90nm CMOS 1.2V 10b Power and Speed Programmable Pipelined ADC with 0.5pJ/Conversion-Step**, G. Geelen, E. Paulus, D. Simanjuntak, H. Pastoor, R. Verlinden  
IEEE ISSCC, Digest of Tech Papers, feb 2006, paper # 12.1


**[12] A 20 GS/s 8 b ADC with a 1 MB memory in 0.18  $\mu\text{m}$  CMOS**

Poulton, K.; Neff, R.; Setterberg, B.; Wuppermann, B.; Kopley, T.; Jewett, R.; Pernillo, J.;  
Tan, C.; Montijo, A. Solid-State Circuits Conference, 2003. Digest of Technical Papers.  
ISSCC. 2003 IEEE International Volume , Issue , 9-13 Feb. 2003 Page(s): 318 - 496 vol.1

# Books

 

 **Data Conversion System Design**  
Behzad Razavi




**CMOS Integrated Analog-to-Digital and Digital-to-Analog Converters**  
Rudy van de Plassche




**CMOS Data Converters for Communications**  
Gustavsson, Wikner and Tan


# Books

 

 **Digitally Assisted Pipeline ADCs**  
Murmann & Boser



 
**Analog Integrated Circuit Design**  
Johns & Martin




**CMOS Analog Circuit Design:**  
Allen & Holberg




# Books

 

 
**CMOS Mixed-Signal Circuit Design**  
R. Jacob Baker



 **The Data Conversion Handbook**  
Walt Kester



 **Analog Design Essentials:**  
Willy Sansen



**Analog Design  
For CMOS VLSI  
System**  
Franco Maloberti



Thank You

Thanks to Steve Lewis [13] for inventing the pipelined ADC and countless others researchers and designers for years of continued improvement

[13] S. H. Lewis and P. R. Gray, "A pipelined 5-Msample/s 9-bit analog-to digital converter," *IEEE J. Solid-State Circuits*, vol. SC-22, pp. 954–961, Mar. 1987.

*ISSCC 2008 Tutorial*

Enjoy The Game



**Patriots 31**



**Giants 17**