


# DPLL Based Clock and Data Recovery

John T. Stonick  
jts@synopsys.com

# Overview


- Focus is on clock recovery
- What is a CDR?
- What is a DPLL based CDR?
- Development of the architecture
- Linear model
- Understanding the operation (making sense of the model)
- Design examples

# Parallel vs Serial Links

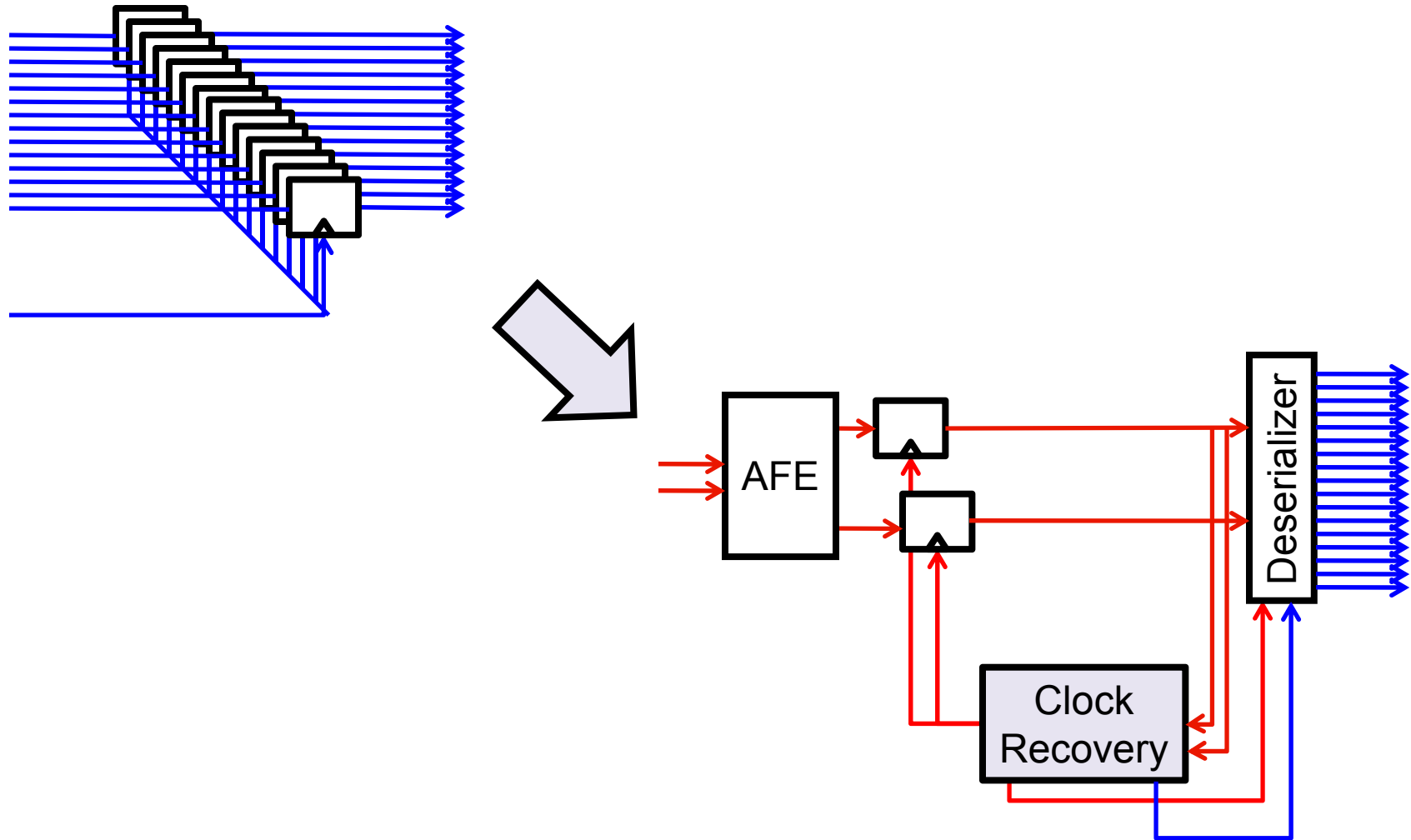

# Clock Recovery

Clock has regular occurrences of edges

 


Data has “missing” edges



- Clock recovery from data edges
  - Nyquist data (101010...) looks like a clock at  $\frac{1}{2}$  data rate
  - Random data has average edge density is .5
    - May go for long periods with no transitions
- CDR's job is to generate a sampling clock synchronous with data from non-uniform set of edges


# Clock Recovery Basics

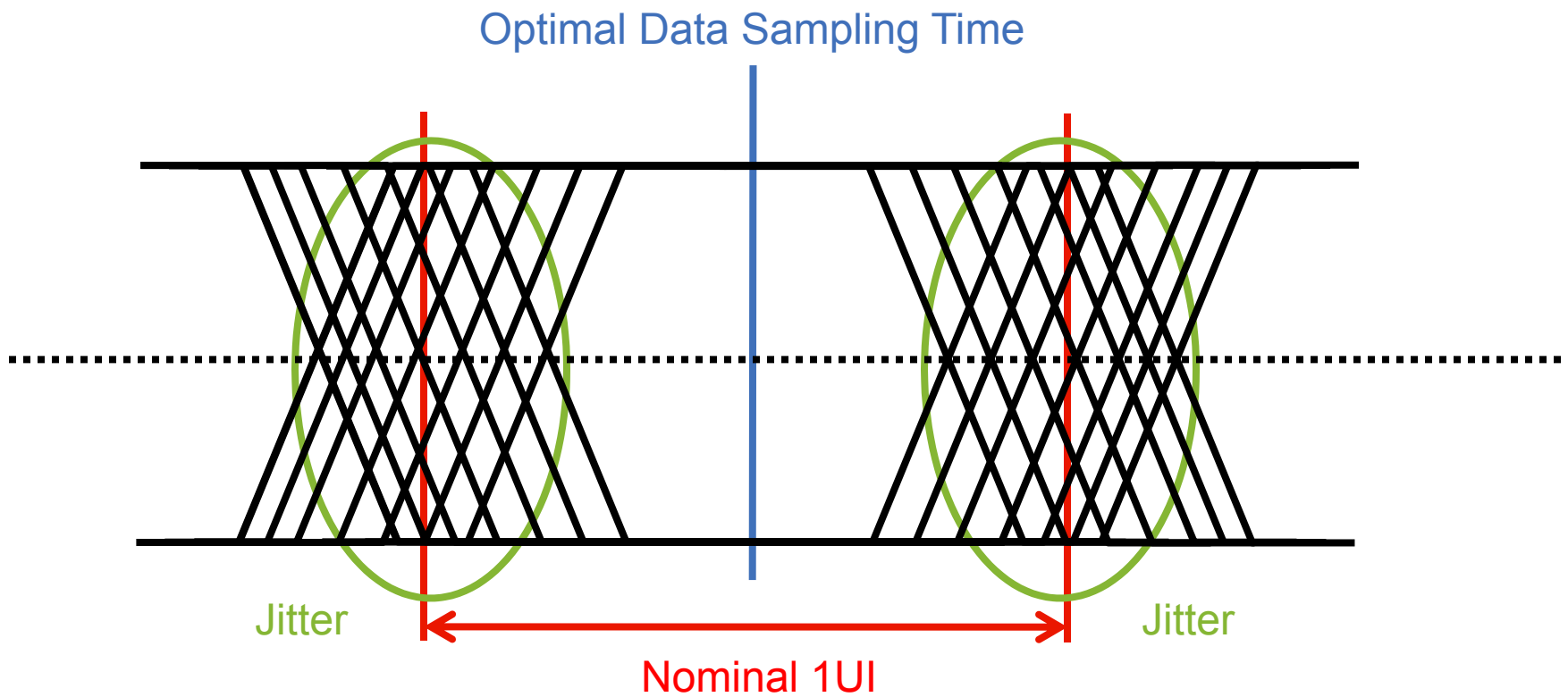

# CDR Types



- Analog
  - PLL based with linear phase detector
  - **PLL based with bang-bang phase detector**
- Digital
  - Oversampling
    - Multiple samples per UI
    - Pick the best sample (farthest from transition)
  - DPLL based
    - **Based on a traditional analog bang bang CDR**
    - Replace analog blocks with digital equivalents
    - Saves power and area, reduces PVT variation and improves testability with respect to analog implementation

# Analog PLL-Based CDR Block Diagram

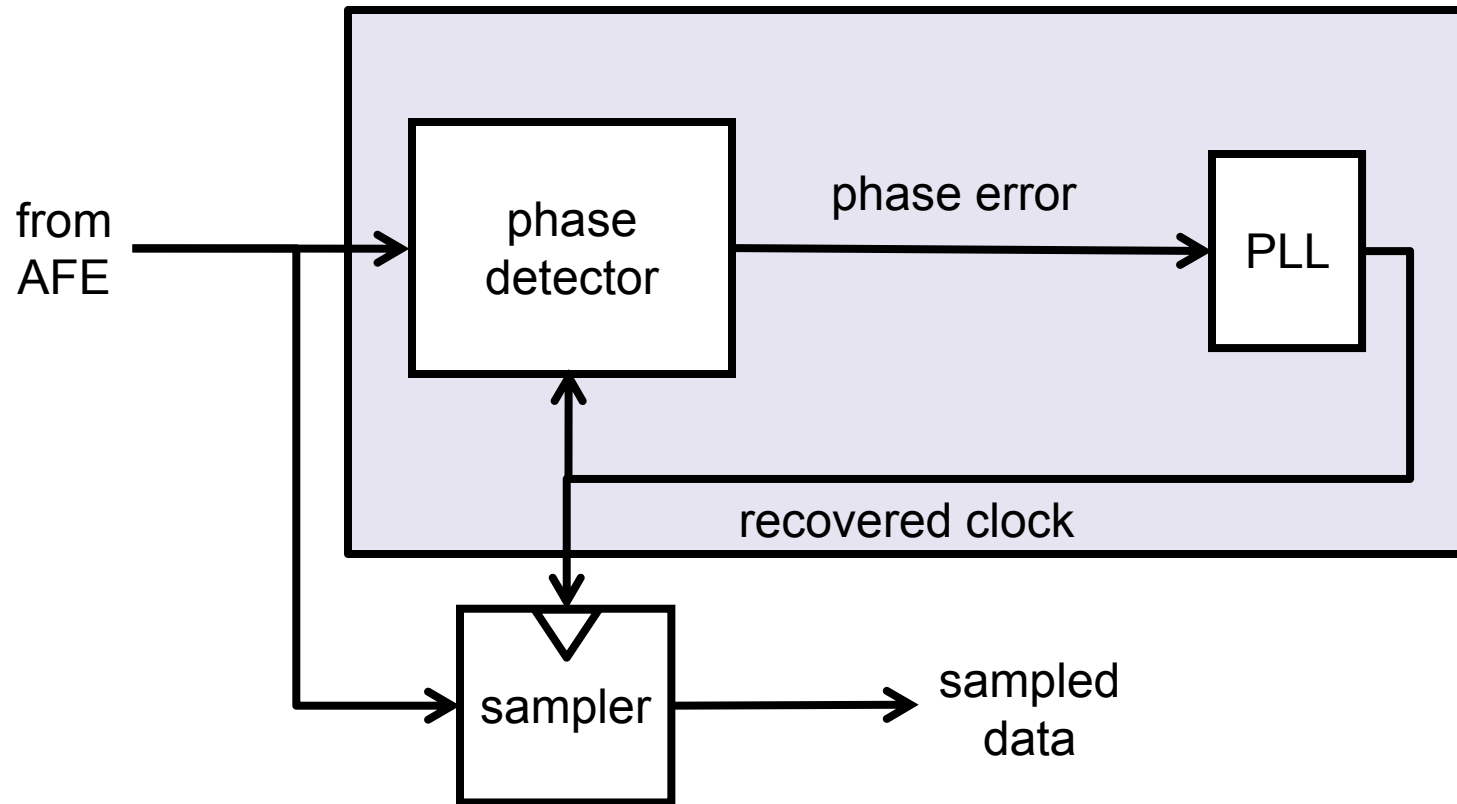

Force recovered clock to be in quadrature with incoming data

# Analog PLL-Based CDR Detail

 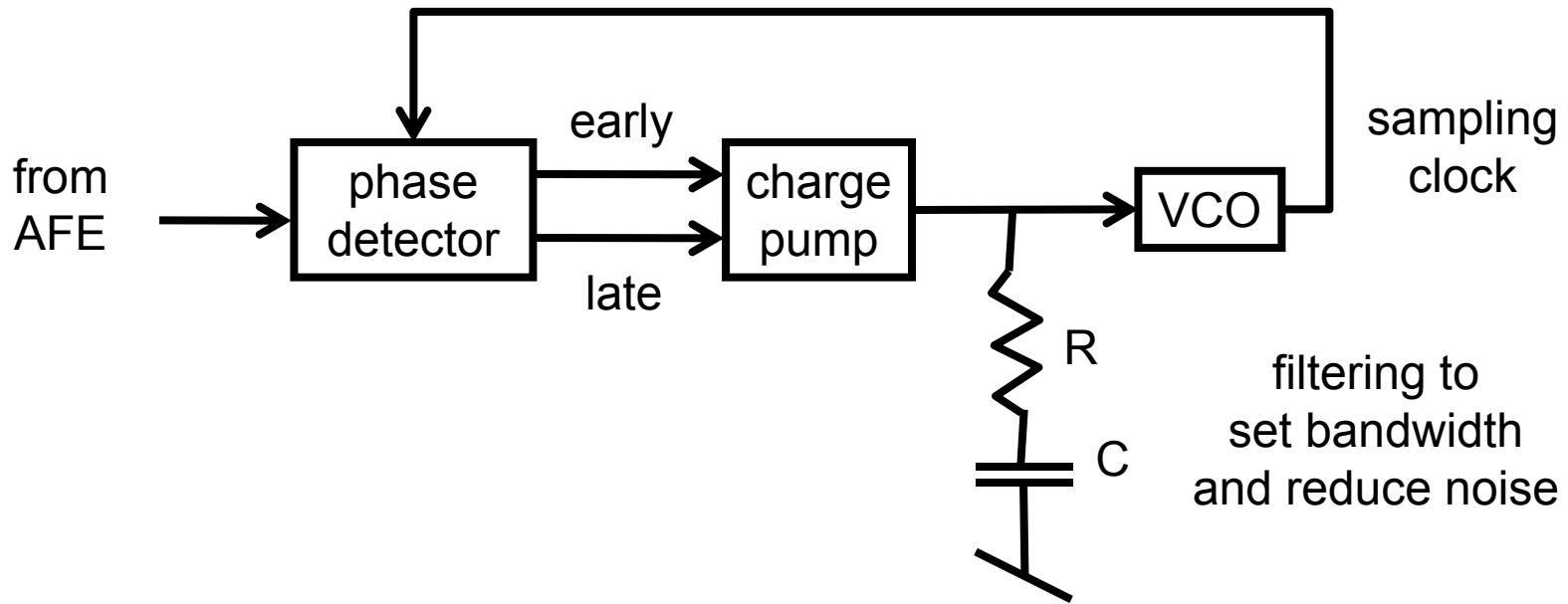




# Phase Detector Types

- Linear (Hogge)
  - Produces a late **and** an early pulse on each transition
  - Late and early pulses are **variable** width. *Difference* in pulse widths *proportional* to phase error
  - Lock condition is late and early pulses of equal width on each clock cycle
  - Difficult to implement without static phase error and only useful in analog implementations
- Bang bang (Alexander)
  - Produces a late **or** an early pulse on each transition
  - Late and early pulses always the **same** width
  - Lock condition is equal average number of early and late pulses (time average to 0)
  - Inherently less problematic than linear PD, usable in DPLL
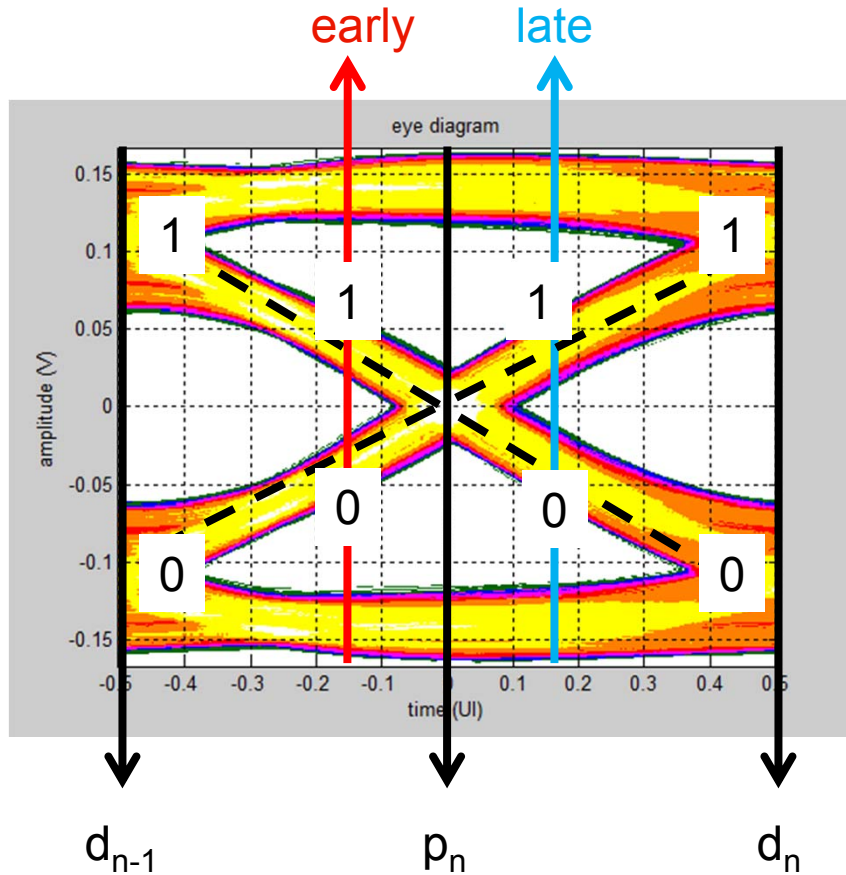
# Digital View of the Bang-Bang Phase Detector





look up table



$d_{n-1}$	$p_n$	$d_n$	phe
0	1	1	late
0	0	1	early
1	1	0	early
1	0	0	late
0	x	0	no trans
1	x	1	no trans

- Output is three levels: (2 bits: early, late, no transition)
- We can take data and phase samples and make phe decisions later

 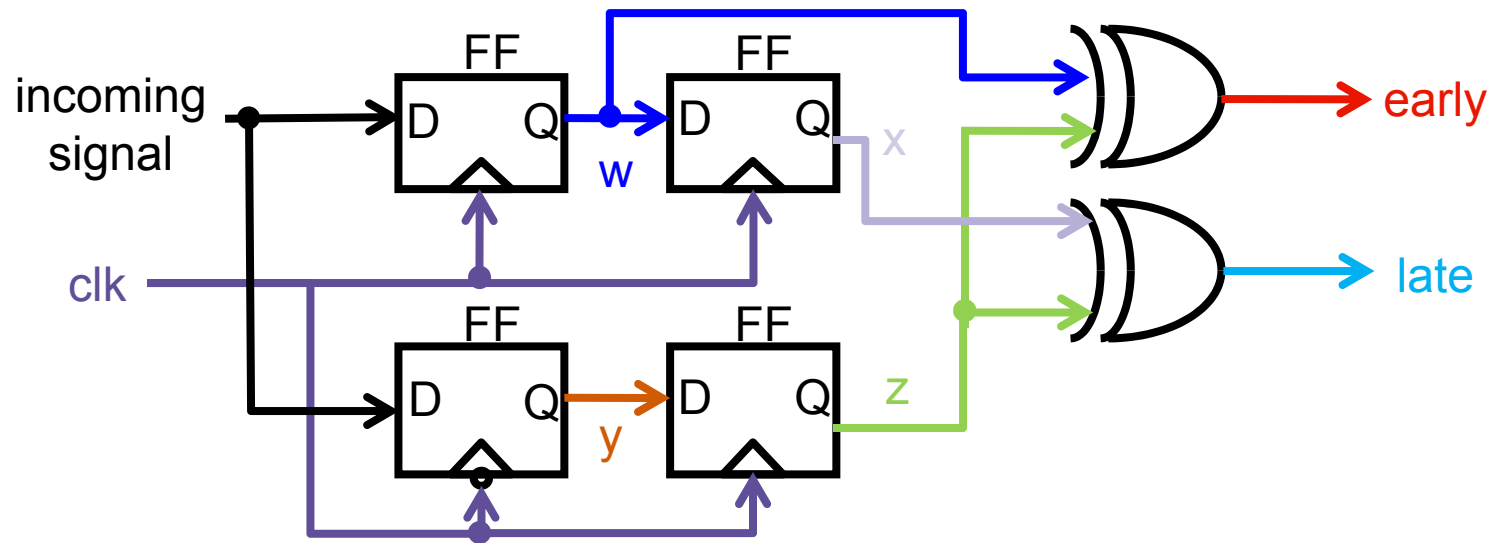
# Bang-Bang (Alexander) Phase Detector (Clock is Early)



# Comparison of Bang-Bang Realizations

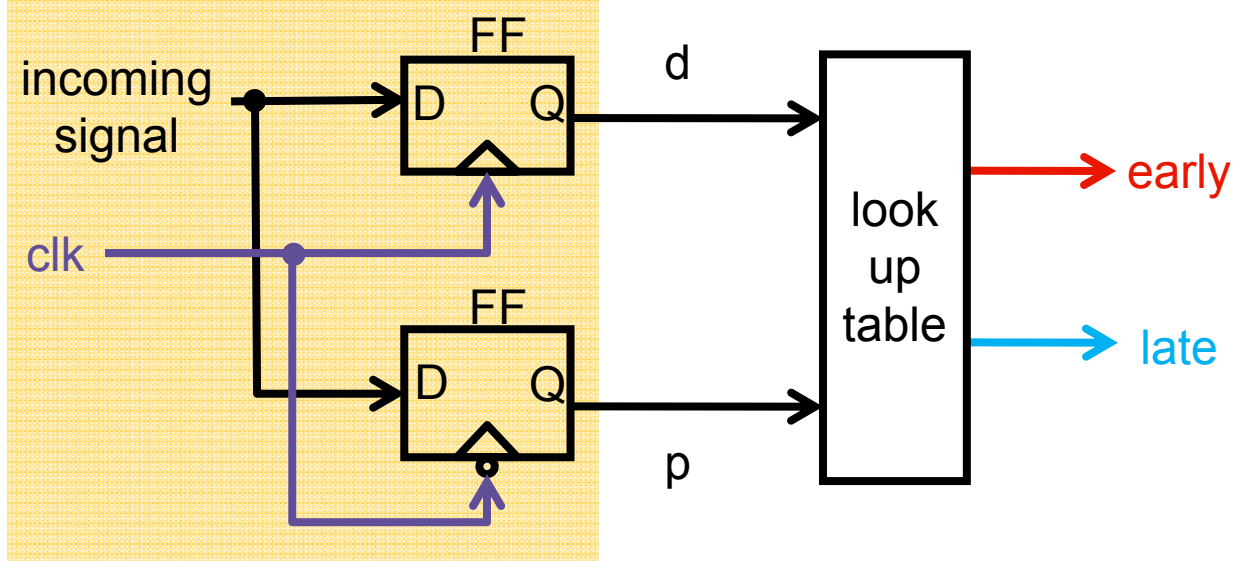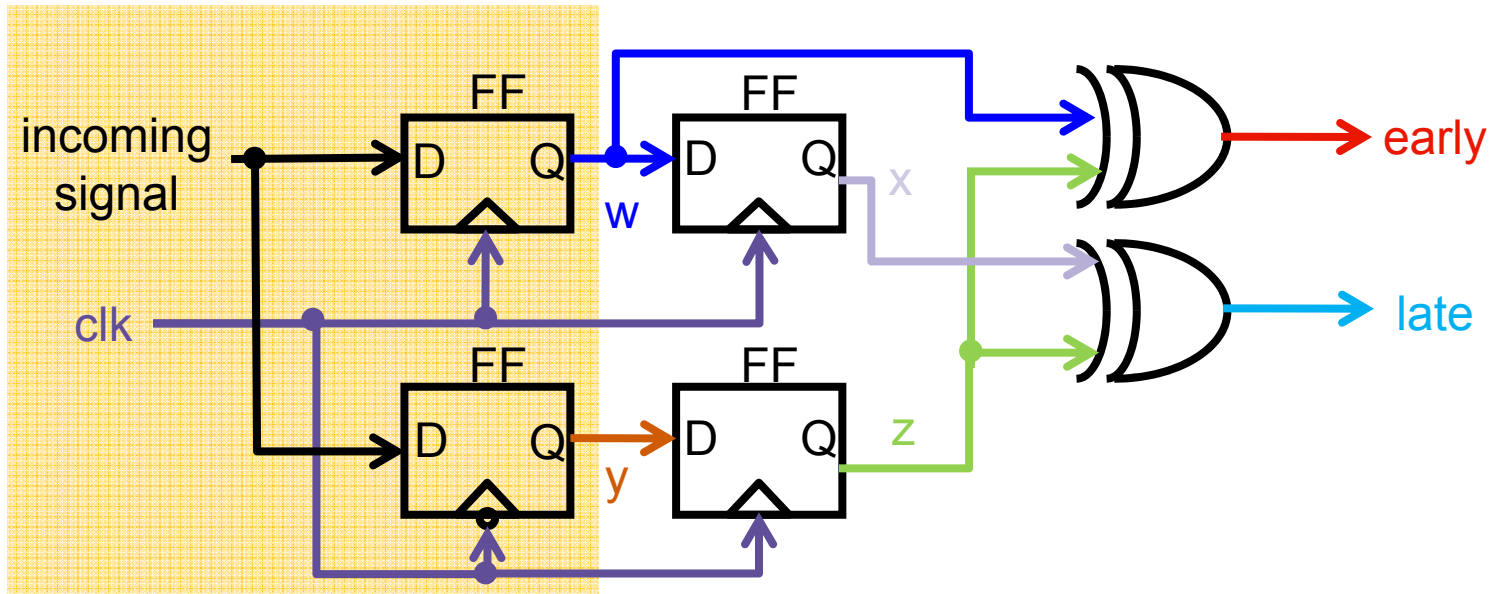

 
# Linearizing the Bang-Bang Phase Detector



1 out of  
phase slicer

0 out of  
phase slicer

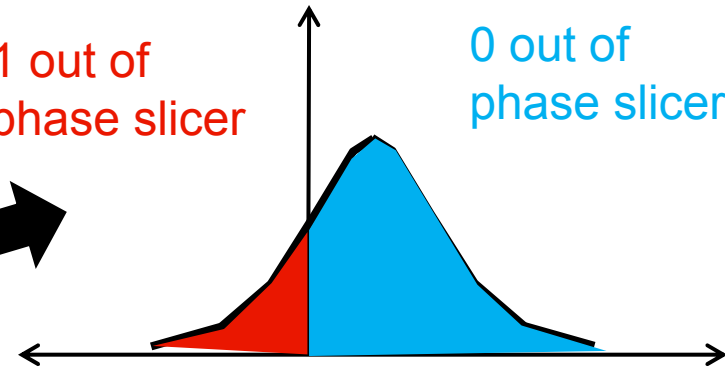

Early probability is area of red  
Late probability is area of blue

Time average value coming out  
of BB PD ( $\mu$ ) with respect to phase  
offset related to gain!

Arbitrarily assign -1 to early and +1  
to late

# Linearizing the Bang-Bang Phase Detector

- $\mu = (1)\Pr(\text{late}|\phi) + (-1)\Pr(\text{early}|\phi)$
- Each phase offset ( $\phi$ ) will have a different mean ( $\mu$ )
  - BB Gain is slope of average BB output,  $\mu$ , versus phase offset,  $\phi$


$$\frac{\partial \mu}{\partial \phi}$$

- BB only produces output for a transition and this de-rates the gain. Transition density = .5 for random data


$$K_{\text{BB}} = \frac{1}{2} \frac{\partial \mu}{\partial \phi}$$

- Need to assume a PDF for jitter to compute  $K_{\text{BB}}$ 
  - Gaussian (RJ dominated) and uniform (DJ dominated)

# Uniform PDF (DJ Dominated)

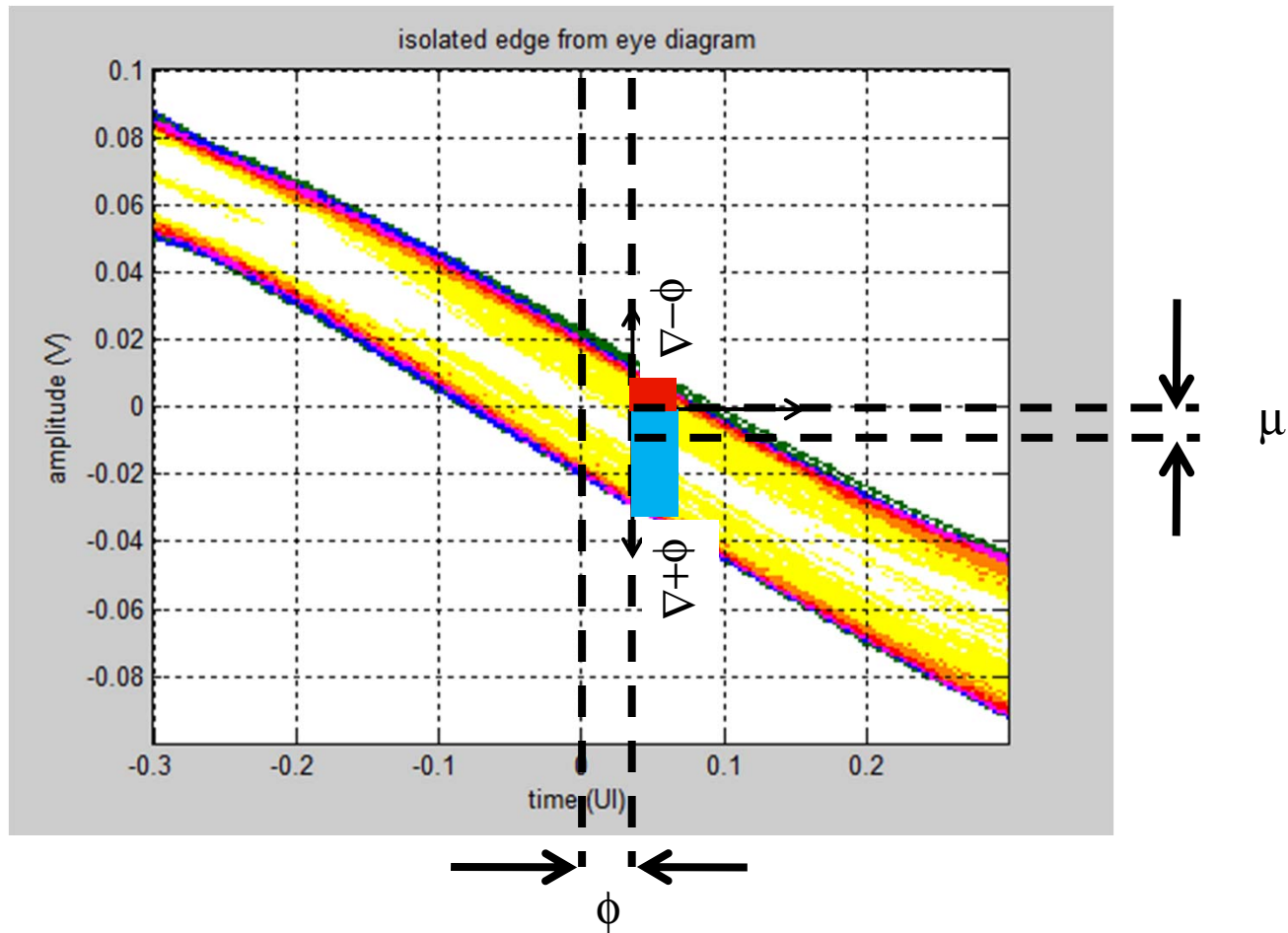

# Pr(late| $\phi$ ) for Uniform PDF

 


$$\sigma^2 = \frac{1}{2\Delta} \int_{-\Delta+\phi}^{\Delta+\phi} x^2 dx - \phi^2 = \frac{\Delta^2}{3} \quad \longrightarrow \quad \Delta = \frac{\sigma}{\sqrt{3}}$$


$$\Pr(\text{late}|\phi) = \frac{1}{2\Delta} [\Delta - (-\phi)] = \frac{\sigma\sqrt{3} + \phi}{2\sigma\sqrt{3}} = \frac{1}{2} \left( 1 + \frac{\phi}{\sigma\sqrt{3}} \right)$$



# Gaussian PDF (RJ Dominated)

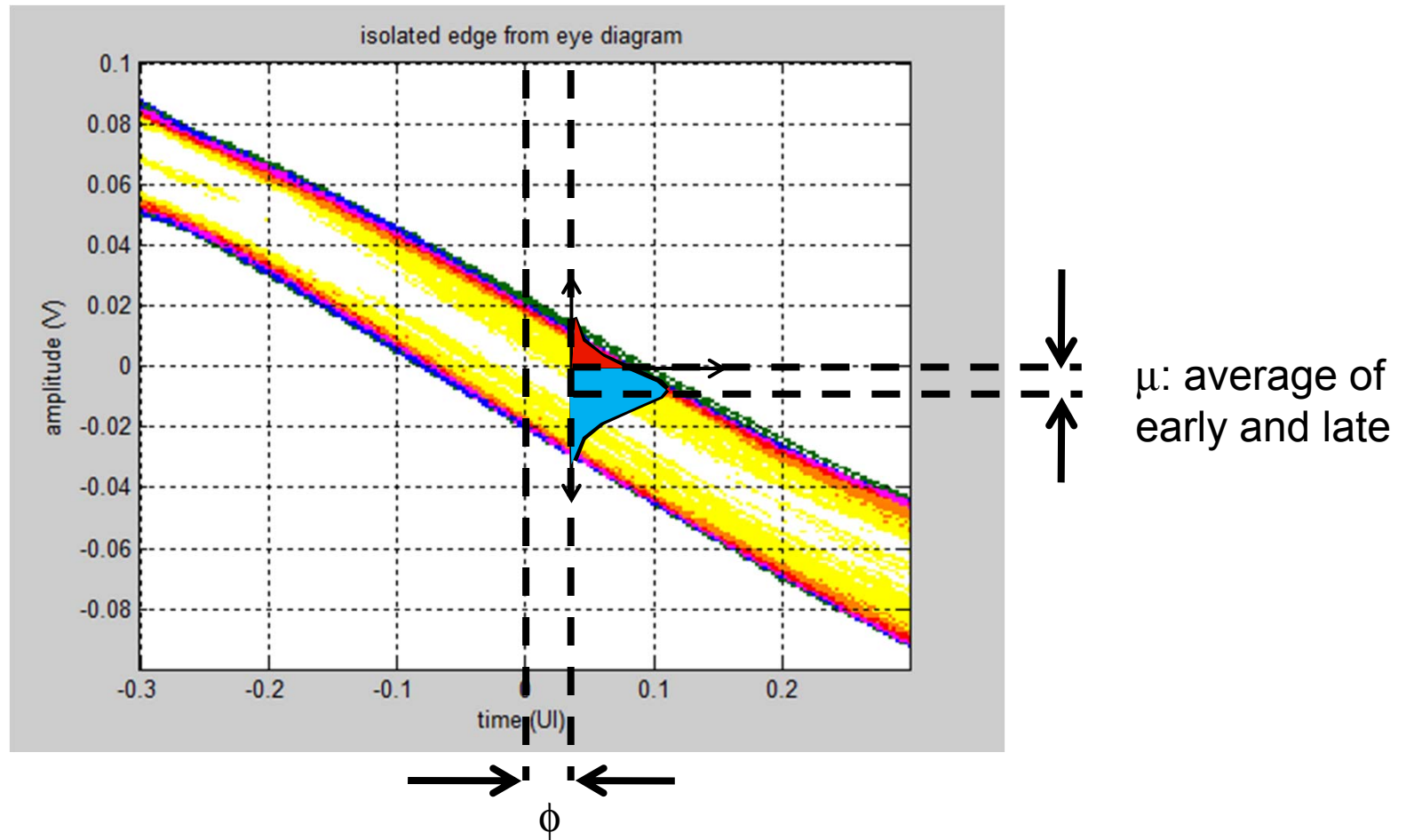

# Pr(late| $\phi$ ) for Gaussian PDF

 

mean is  $-\phi$   
standard deviation is  $\sigma$

$$\Pr(\text{late}|\phi) = \frac{1}{\sigma\sqrt{2\pi}} \int_0^{\infty} e^{-\frac{(x+\phi)^2}{2\sigma^2}} dx$$

$$\Pr(\text{late}|\phi) = \frac{1}{\sqrt{2\pi}} \int_{\frac{\phi}{\sigma}}^{\infty} e^{-\frac{y^2}{2}} dy$$

$$Q(A) = \frac{1}{\sqrt{2\pi}} \int_A^{\infty} e^{-\frac{y^2}{2}} dy$$

$$\Pr(\text{late}|\phi) = Q\left(\frac{\phi}{\sigma}\right) \approx \frac{1}{2} - \frac{\phi}{\sigma\sqrt{2\pi}}$$



# Gain for Bang-Bang Phase Detector

	Uniform	Gaussian
$\text{Pr}(\text{late} \phi)$	$\frac{1}{2} \left( 1 + \frac{\phi}{\sigma\sqrt{3}} \right)$	$\frac{1}{2} - \frac{\phi}{\sigma\sqrt{2\pi}}$
$\mu = 2 * \text{Pr}(\text{late} \phi) - 1$	$\frac{\phi}{\sigma\sqrt{3}}$	$\frac{2\phi}{\sigma\sqrt{2\pi}}$
$K_{\text{BB}} = \frac{1}{2} \frac{\partial \mu}{\partial \phi}$	$\frac{1}{\sigma\sqrt{12}}$	$\frac{1}{\sigma\sqrt{2\pi}}$

BB gain will be somewhere between the two extremes

# Verification for Gaussian Jitter, $\sigma = .1UI$

Zoom in on linear region

 
 


Measured slope: 3.98

calculation:  $\frac{1}{.1\sqrt{2\pi}} = 3.99$

# Verification for Uniform Jitter, $\sigma = .15UI$

Zoom in on linear region

  

Measured slope: 1.89

calculation:  $\frac{1}{.15\sqrt{12}} = 1.92$

# Bang-Bang Self-Noise Term ( $\sigma_{\text{BB}}$ )

- One price we pay for BB PD versus linear PD is the self-noise term
- For small phase errors BB output noise is the full magnitude of the sliced data
  - Average power is the probability of a transition
  - Average transition density is .5,  $\text{Pr}(\text{trans})=.5$
  - $\sigma_{\text{BB}}^2 = \text{Pr}(\text{trans}) = .5$
- To understand impact we can reflect noise back to the input

$$\sigma_{\text{BBin}}^2 = \frac{\sigma_{\text{BB}}^2}{K_{\text{BB}}^2} = \frac{.5}{K_{\text{BB}}^2}$$

# BBPD Self Noise Input Referred

- Lets consider our 2 PDFs

- Uniform,  $K_{\text{BB}} = \frac{1}{\sigma\sqrt{12}}$ ,  $\sigma_{\text{BBin}}^2 = \frac{.5}{K_{\text{PD}}^2} = 6\sigma^2$ ,  $\sigma_{\text{BBin}} = \sqrt{6}\sigma$

- Gaussian,  $K_{\text{BB}} = \frac{1}{\sigma\sqrt{2\pi}}$ ,  $\sigma_{\text{BB}}^2 = \frac{.5}{K_{\text{PD}}^2} = \pi\sigma^2$ ,  $\sigma_{\text{BB}} = \sqrt{\pi}\sigma$

- Input referred jitter from BB PD is proportional to incoming jitter. Assuming they add in power, the increase in jitter is computed to be:

- Uniform:  $\sigma^2 \Rightarrow \sigma^2(1+6)$ ,  $\sigma \Rightarrow \sigma\sqrt{7}$


- Gaussian:  $\sigma^2 \Rightarrow \sigma^2(1+\pi)$ ,  $\sigma \Rightarrow \sigma\sqrt{1+\pi}$

# BBPD Model Summary

- BBPD modeled as a gain plus an additive jitter term
- BBPD gain inversely proportional to incoming jitter
  - More jitter leads to lower gain
  - Clean signals provide highest gain
- BBPD noise reflected to input is proportional to incoming jitter and models the jitter increase versus a linear phase detector



# Analog BB CDR Small Signal Model

 


$$L(s) = \frac{K_{BB} I_{CP} K_{VCO}}{s} \left( R + \frac{1}{sC} \right)$$

# Practical Issues with Bang Bang Phase Detectors

- Loop gain is proportional to the transition density (we derived for long term average)
  - Nyquist data (101010...) has a transition density of 1 (valid 8B10B data)
  - For 8B10B data we can have long term transition density as low as .3
    - For 8B10B coded sustainable long term gain can vary by a factor of 3.33:1
  - For un-coded data, transition density can be almost anything!
  - Later we will look at techniques to mitigate this problem
- Offsets in the phase slicer
  - We have assumed perfect slicing at 0
  - If offset then we are going to make some wrong decisions
  - Study this next
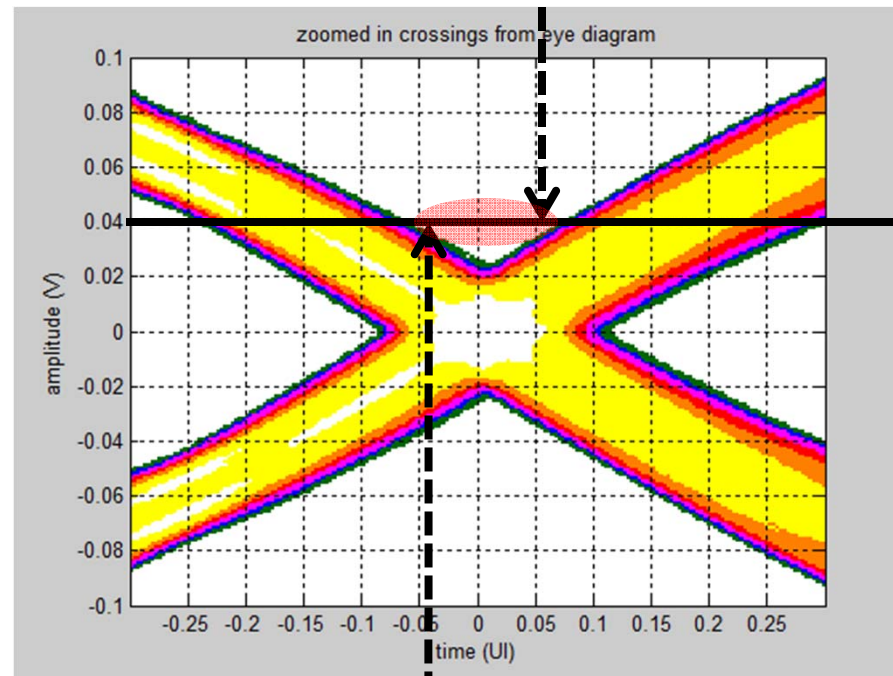
# Offsets in Phase Slicer

Sampling offset is **late**,  $p_n$  always 0, thus **rising** edges always **early**  
**falling** edges always **late**. Averages to zero!




slicer offset

dead zone,  
 $p_n$  always 0  
whether early  
or late!!!

Sampling offset is **early**,  $p$  always 0, but **falling** edges always **late**  
**rising** edges always **early**. Averages to 0!



# Compare Average BB Output

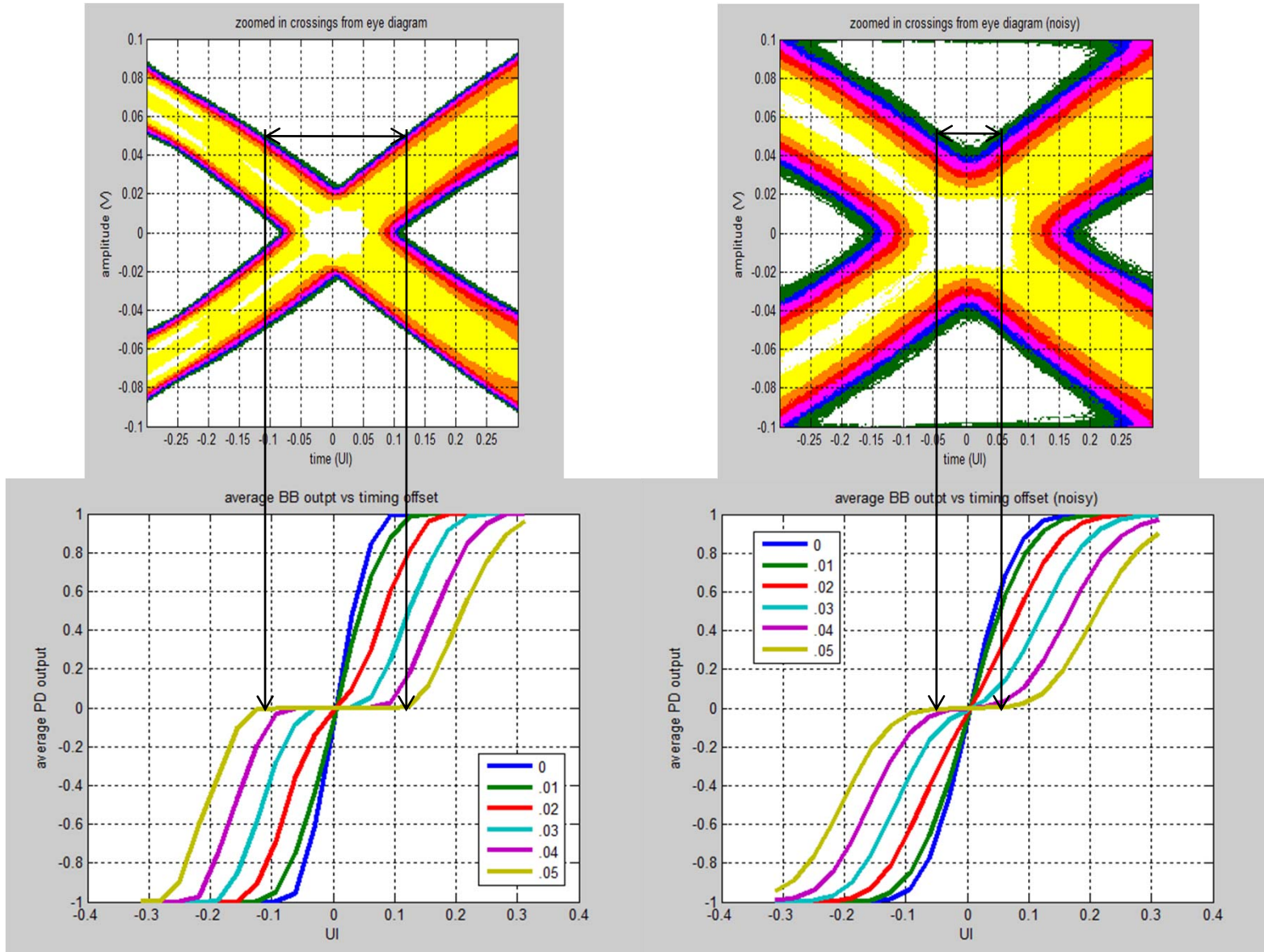


# DPLL Based CDR

- Replace analog blocks in analog BB CDR with digital equivalents
  - BB phase detector stays the same
  - Digital charge pump and loop filter equivalent
  - Digital VCO equivalent
  - Analog block to convert digital to phase
- Derive small signal model and loop gain
- Justify design by comparing digital and analog small signal models

# DPLL Structure

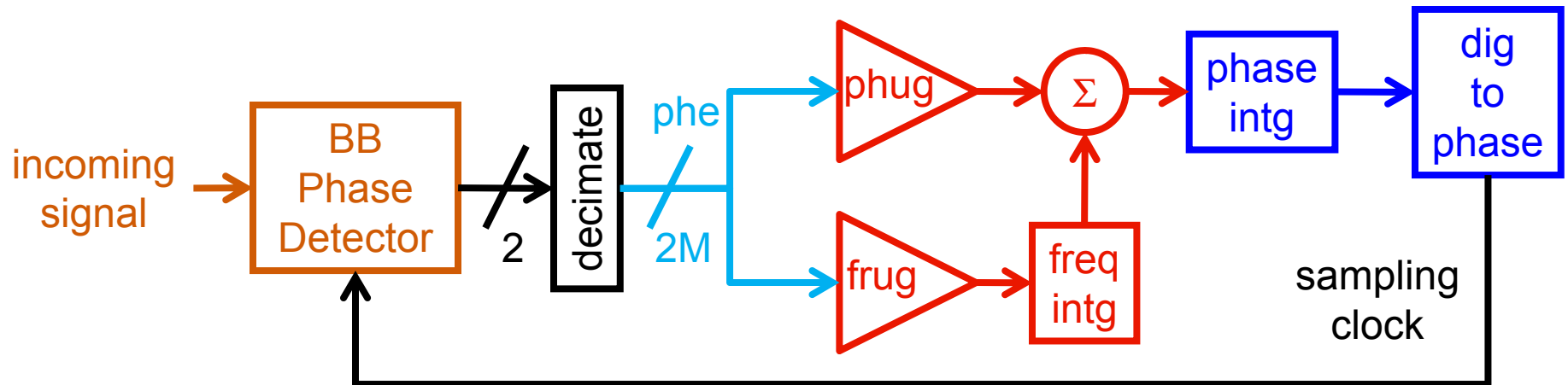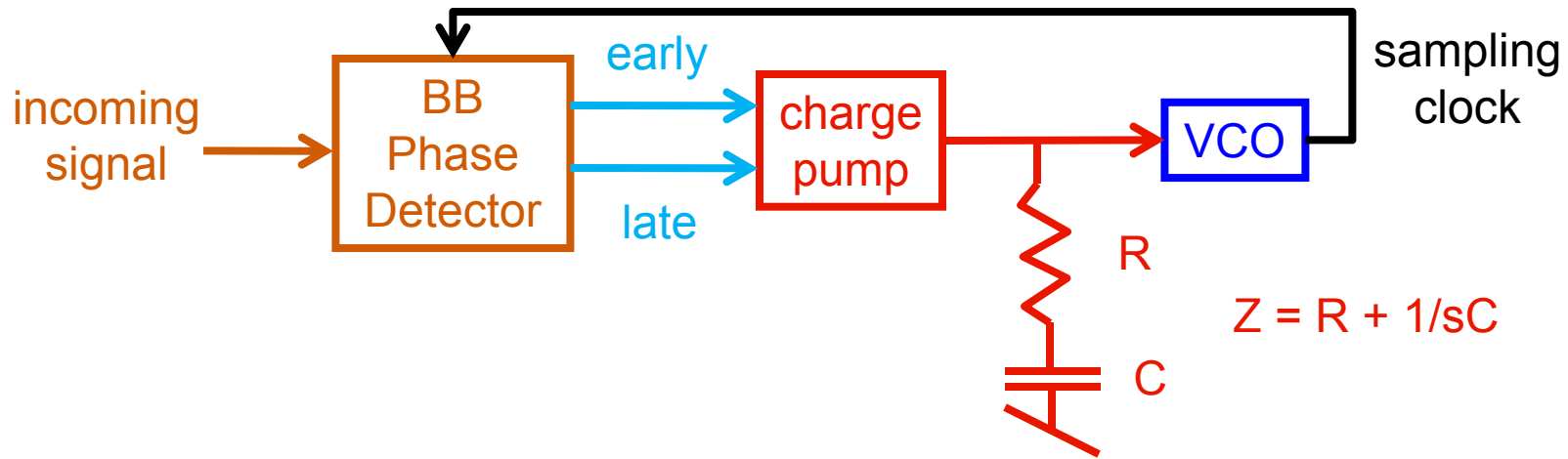

# DPLL CDR Small Signal Model

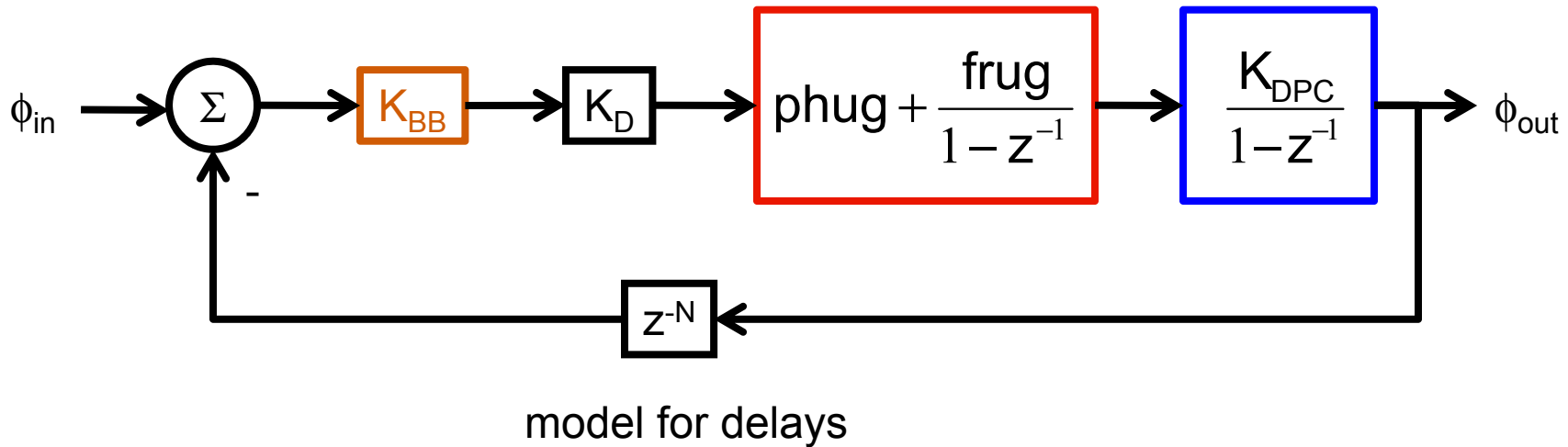

---


$$L(z^{-1}) = \frac{K_{BB} K_D K_{DPC}}{1 - z^{-1}} \left( \text{phug} + \frac{\text{frug}}{1 - z^{-1}} \right) z^{-N}$$

# Loop Gain Comparison

$$L(s) = \frac{K_{BB}K_{VCO}}{s} \left( I_{CP} \cdot R + \frac{I_{CP}}{sC} \right)$$

$$L(z^{-1}) = \frac{K_{BB}K_DK_{DPC}}{1-z^{-1}} \left( \text{phug} + \frac{\text{frug}}{1-z^{-1}} \right) z^{-N}$$

---

$$\text{phug} \sim I_{CP}R$$

$$\text{frug}/(1-z^{-1}) \sim I_{CP}/(sC)$$

$$K_{PDC}/(1-z^{-1}) \sim K_{VCO}/s$$

$$K_{BB} \sim K_{BB}$$

$K_D$  only in DPLL



# DPLL Advantages

- DPLL based CDR derived from tried and true traditional analog BB CDR
- phug acts like an  $I_{CP}R$  **with no PVT variation**
- frug/ $(1-z^{-1})$  acts like a  $I_{CP}/sC$  **with no PVT variation**
- Phase integrator acts like VCO **with no PVT variation**
- DPLL Based CDR acts like an **ideal** analog CDR with **greatly reduced area** since capacitors and resistors replaced with digital gates
- Improved observability and testability


# DPLL Design

- Linear model will provide us with insight in the design process
  - Right now parameters have no physical meaning
  - Parameters of the model need to be defined in terms of how they affect sampling phase
- To gain this understanding we need to walk backwards through the DPLL from the output sampling clock back to the BB PD output
  - Ultimately understand how BB PD output affects sampling phase as it passes through the system
 
# DPLL Structure

$$L(z^{-1}) = \frac{K_{BB}K_DK_{DPC}}{1-z^{-1}} \left( \text{phug} + \frac{\text{frug}}{1-z^{-1}} \right) z^{-N}$$


$K_{DPC} = ?$   
 $\text{phug} = ?$   
 $\text{frug} = ?$   
 $K_D = ?$




# Digital Phase Converter

- Converts digital code from the phase integrator into an edge location with respect to the **local** reference clock
  - Phase Interpolator (PI), phase rotator, DLL, etc
- Design parameter of importance is resolution in bits. For N bits each UI is  $2^N$  steps – discrete steps of **local** reference clock
  - There is quantization error vs analog CDR
  - Average PI will have 4 input (reference) phases and 32 output phase steps



# Phase Interpolator Functional View

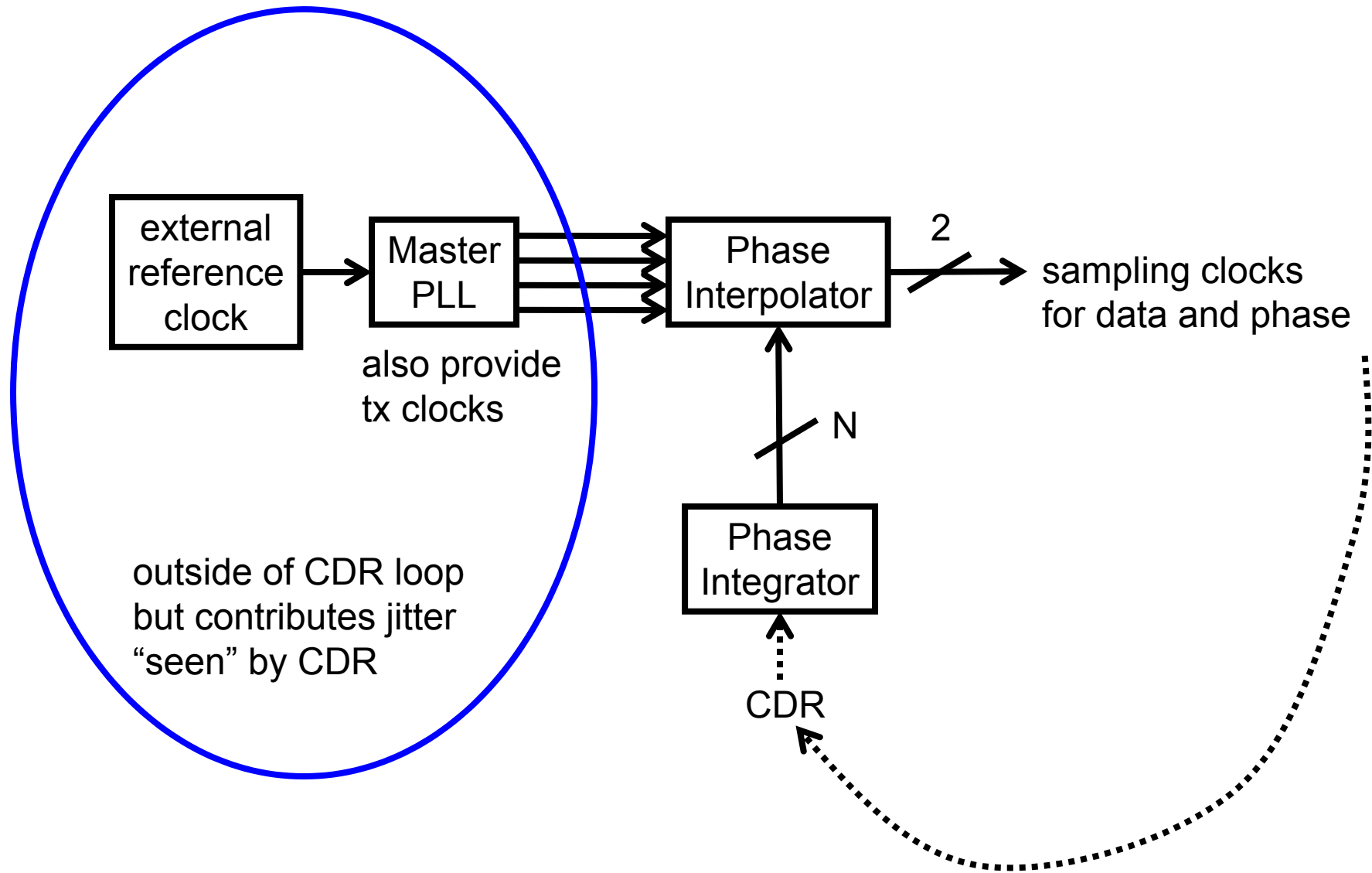

# Phase Interpolator (Rotator)

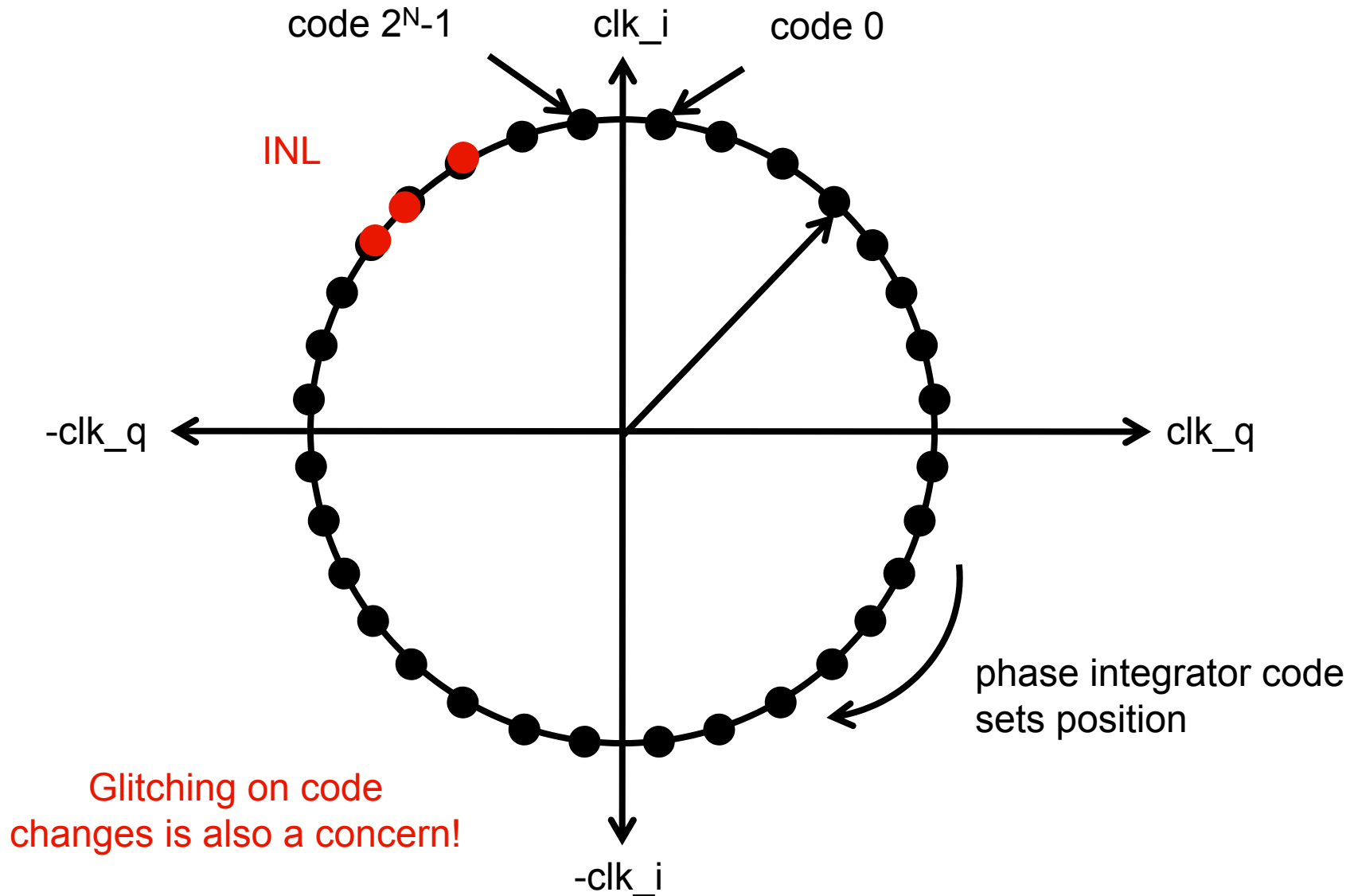
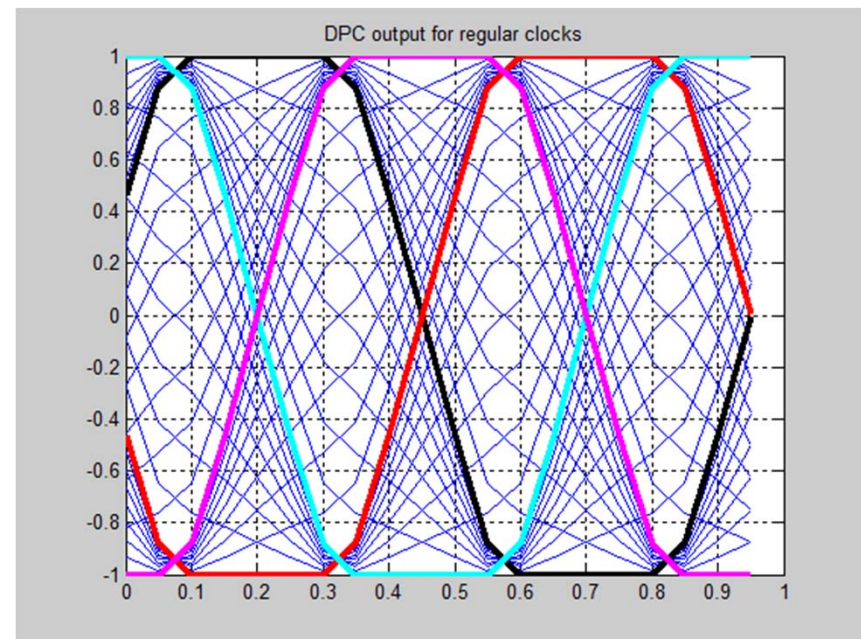 
# Impact of Reference Clock Edges on PI Output




Challenge: Make reference clock edges as triangular shaped across PVT!!!
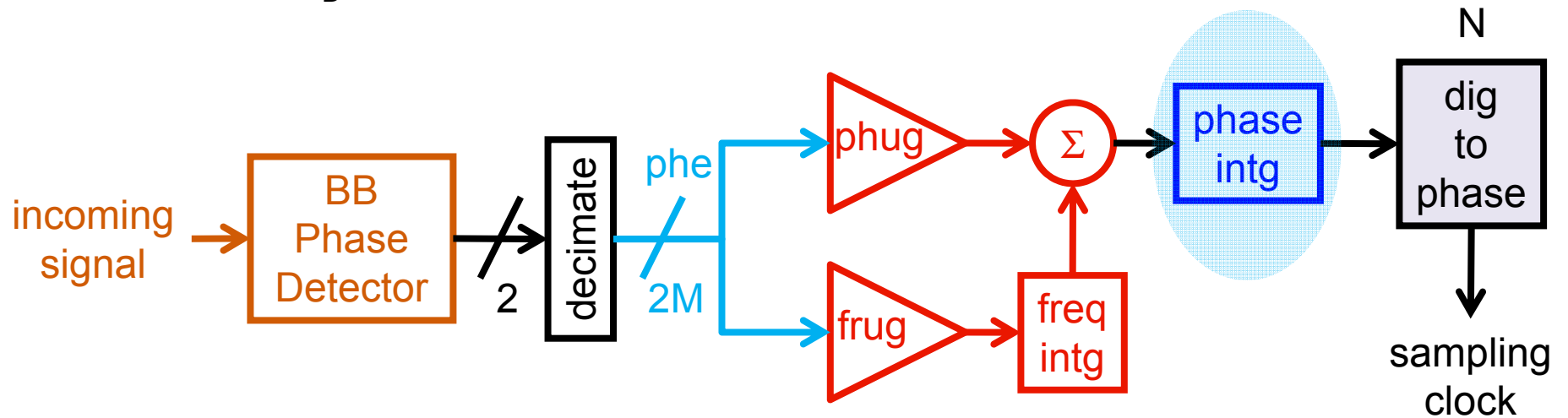
# DPLL Structure

$$L(z^{-1}) = \frac{K_{BB}K_DK_{DPC}}{1-z^{-1}} \left( \text{phug} + \frac{\text{frug}}{1-z^{-1}} \right) z^{-N}$$

$K_{DPC} = ?$   
 $\text{phug} = ?$   
 $\text{frug} = ?$   
 $K_D = ?$






# Phase Integrator

- Digital representation of the sampling phase via DPC
  - Phase integrator is  $N+D_p$  bits - each step in the phase integrator is effectively  $1/2^{(N+D_p)}$  of a UI
  - **Sets the effective resolution for the system**, a value of 1 coming out of BBPD moves phase by  $1/2^{(N+D_p)}$  of a UI
  - $K_{DPC} = 1/2^{(N+D_p)}$  (Model of VCO gain)
- Phase integrator is unsigned (continuous phase rotation in PI)
  - max value is  $2^{(N+D_p)} - 1$ , for 8 bits range is 0 to 255
  - $(2^{(N+D_p)} - 1) + 1 = 0$ , for 8 bits  $255 + 1 = 0$
- If PI has  $2^N$  steps then the top N bits of the phase integrator are attached to the PI
  - The  $D_p$  dither bits of phase integrator are sub-resolution
- Example:  $N=5$ ,  $D_p=2$ 
  - Phase integrator : 7'bxxxxxx
  - Blue bits tied to PI, red bits effectively ignored

# Phase Integrator Example 1

- $N=5$ ,  $D_p=2$ , PI and phase intg both 0, steps of 1 on each clock
  - Clock 0: phase intg = 7'b0000000
  - Clock 1: phase intg = 7'b0000001
  - Clock 2: phase intg = 7'b0000010
  - Clock 3: phase intg = 7'b0000011
  - Clock 4: phase intg = 7'b0000100
    - PI moves after 4 consecutive decisions
    - Effectively reduces max gain by a factor of 4

# Graphical View

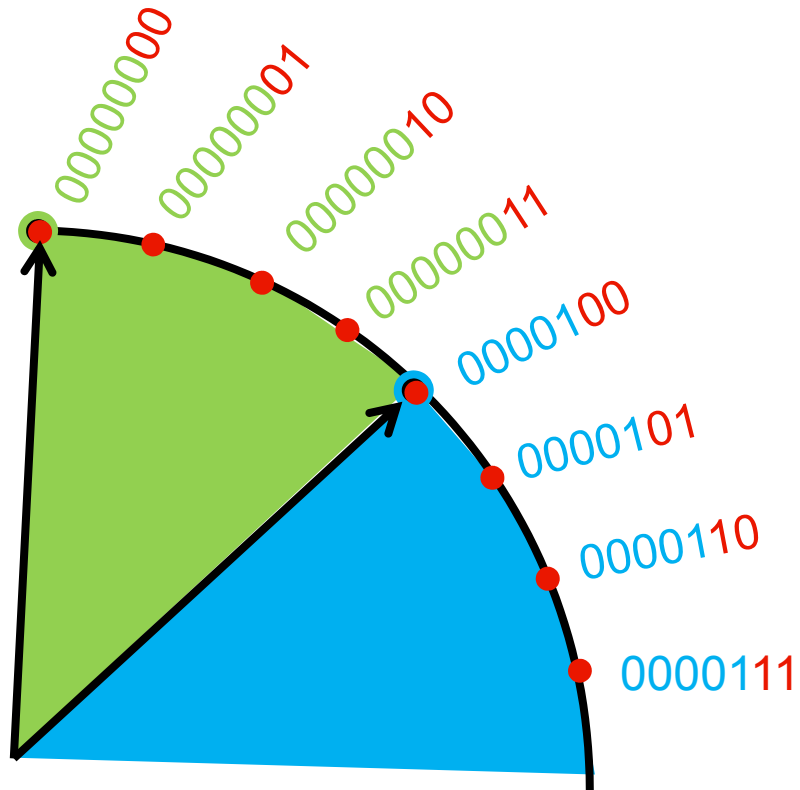


Red dots are the phase integrator values, colored regions are the PI regions with respect to phase integrator values.

# Phase Integrator Example 2

- $N=5$ ,  $D_p=2$ , PI and phase intg both 0, dithering 1 and -1
  - Clock 0: phase intg = 7'b00000000
  - Clock 1: phase intg = 7'b00000001
  - Clock 2: phase intg = 7'b00000000
  - Clock 3: phase intg = 7'b00000001
  - Clock 4: phase intg = 7'b00000000
    - PI did not move
  - If on boundary PI will dither, but probability of that occurring reduced by  $2^{-(D_p-1)}$

# Graphical View

 

Dithering of output phase only occurs at boundaries, within boundaries dithering does not move the output clock

# DPLL Structure


$$L(z^{-1}) = \frac{K_{BB}K_DK_{DPC}}{1-z^{-1}} \left( \text{phug} + \frac{\text{frug}}{1-z^{-1}} \right) z^{-N}$$

$$K_{DPC} = 1/2^{(N+D_p)}$$

$$\text{phug} = ?$$

$$\text{frug} = ?$$

$$K_D = ?$$

 

# Digital Loop Filter

- Filter the phase detector decisions (acts like CPLF)
- Proportional path through phug, integral path through frug
- phug and frug may be time-varying
  - At startup may want higher gain to increase pull-in range at cost of higher jitter
  - May turn on phug first to achieve a crude lock and then turn on frug
- Proportional path controls most of loop dynamics
  - Low latency in this path is extremely important
- Integral path is a slow path to compensate for long term frequency offset

# Proportional Path (phug)

- Compensates for static phase offset with 0 steady state error
  - Same as proportional path in analog CDR
- Adds a +phug, -phug or 0 to phase integrator on each clock cycle
  - phug changes how much we move phase
  - Proportional path can move output phase by up to  $\text{phug}/2^{(N+D_p)}$  of a UI per clock cycle
- phug is an integer value that affects how far phase moves in response to phase error
- phug usually in range of 0,1,2,4 (powers of 2 nice for multiplying digital values (shift))



# Integral Path

- Compensate for a static frequency error with 0 steady state error
- A DC output from the frequency integrator is integrated by phase integrator and turns into a phase ramp
- If far end clock is 100PPM faster than local clock then it is  $1+100/1e6=1.0001$  faster
  - In 10000 of our local clocks the far end will send 10001 bits
  - To keep pace CDR needs to advance 1 extra UI every 10000UI
  - Freq intg should add  $1/10000$ UI to phase integrator every UI
- Frequency integrator is signed!
  - 2's complement arithmetic
  - Sign extended and added to phase integrator
- Frequency integrator saturates

# Frequency Integrator Details

- Frequency integrator is  $M+D_f$  bits with top  $M$  bits sent to phase integrator and  $D_f$  dither bits (fractional bits)
  - A 1 in the top  $M$  bits moves phase  $1/2^{N+D_p}$  UI on each cycle
- Range of top  $M$  bits is  $-2^{M-1}$  to  $2^{M-1}-1$
- Max frequency tracking:
  - If phase integrator is  $N+D_p$  bits then frequency register can move sampling clock by a maximum of  $(2^{M-1}-1)/2^{N+D_p}$  UI per cycle


# Frequency Integrator Example

- If phase integrator is 8 bits ( $1/256$  UI) and frequency integrator output to phase integrator is a 1
  - Phase integrator 0, 1, 2, 3, ....., 254, 255, 0, 1, .....
- Phase integrator moves  $1/256$ UI per UI
  - This is moving phase by  $1/256 * 1e6 = 3906$ PPM
  - Without sub-resolution we would only have a granularity of 3906PPM which is far too coarse
- To reduce granularity we need a way to have frequency integrator sub-resolution seen by phase integrator
  - Sub-resolution in phase integrator thrown on floor
  - Need to use sub resolution from freq intg

# Frequency Integrator Sub-Resolution

- For a 100PPM offset we need to move the phase by 100UI every 1e6 UI (.0001UI per UI)
- Minimum sub-resolution step in an 8-bit phase intg is  $1/256\text{UI}$  (.0039UI)
- If we added 1 to phase integrator every 39 UI we would advance phase an average of  $.0039\text{UI}/39\text{UI} = .0001\text{UI/UI}$
- Dither bits can create a fractional input through **time averaging**

# Sub-Resolution Time Averaging

 

On each cycle take bottom  $D_f$  bits of frequency register as input to an  $D_f$  bit integrator and the output is the carry bit

Acts like a  $D_f$  bit  $\Delta\Sigma$  modulator

Output (carry) is either 0 or 1 – this is an unsigned output

Output is added to top M bits of frequency register in a signed add

# Sub-Resolution Example: $\frac{1}{4}$

- Freq integrator=1/4: 7'b00000\_01 (M=5,  $D_f=2$ )
- M=5'b00000,  $D_f=2$ 'b01,  $\Delta\Sigma$  state=3'b0\_00
  - $\Delta\Sigma$  state = 3'b0\_01, output to phase intg is  $0+0 = 0$
  - $\Delta\Sigma$  state = 3'b0\_10, output to phase intg is  $0+0 = 0$
  - $\Delta\Sigma$  state = 3'b0\_11, output to phase intg is  $0+0 = 0$
  - $\Delta\Sigma$  state = 3'b1\_00, output to phase intg is  $0+1 = 1$
  - $\Delta\Sigma$  state = 3'b0\_01, output to phase intg is  $0+0 = 0$
  - ...
  - Pattern repeats with a 1 being sent every 4<sup>th</sup> cycle =  $\frac{1}{4}$  each cycle
  - Gain of integral path is  $f_{\text{rug}}/2^{D_f}$

# Sub-Resolution Example: $-1/4$

- Freq integrator= $-1/4$ :  $7'b11111\_11$  ( $M=5$ ,  $D_f=2$ )
- $M=5'b11111$ ,  $D_f=2'b11$ ,  $\Delta\Sigma$  state= $3'b0\_00$ 
  - $\Delta\Sigma$  state =  $3'b0\_11$ , output to phase intg is  $-1+0 = -1$
  - $\Delta\Sigma$  state =  $3'b1\_10$ , output to phase intg is  $-1+1 = 0$
  - $\Delta\Sigma$  state =  $3'b1\_01$ , output to phase intg is  $-1+1 = 0$
  - $\Delta\Sigma$  state =  $3'b1\_00$ , output to phase intg is  $-1+1 = 0$
  - $\Delta\Sigma$  state =  $3'b0\_11$ , output to phase intg is  $-1+0 = -1$
  - ...
  - Pattern repeats with a  $-1$  being every 4th cycle =  $-1/4$
  - Unsigned fractional portion is  $+3/4$ , top bits are  $-1$  together they add to  $-1/4$

# Frequency Integrator Summary

- Maximum PPM tracking is  $(2^M-1)/2^{N+D_p}$  UI per cycle
  - For non-SSC usually about +/-1000PPM is adequate
  - For SSC usually about +/-8000PPM is adequate
- Effective resolution is  $1/2^{N+D_p+D_f}$  per cycle
  - A 1 in the frequency register takes  $2^{N+D_p+D_f}$  cycles to move 1 UI
  - In linear model frug value is replaced by  $\text{frug}/2^{D_f}$  (this will change once more when we talk about decimation)
- Maximum slew rate is given by
  - $(\text{frug} \cdot \text{pfe})/2^{N+D_f+D_p}$
  - This is important for SSC tracking
- Dither bits can produce a fraction in the range of:  
 $1/(2^{D_f})$  to  $(2^{D_f} - 1)/2^{D_f}$



# DPLL Structure


$$L(z^{-1}) = \frac{K_{BB} K_D K_{DPC}}{1 - z^{-1}} \left( \text{phug} + \frac{\text{frug}}{1 - z^{-1}} \right) z^{-N}$$

$$K_{DPC} = 1/2^{(N+D_p)}$$

$$\text{phug} = \{0, 1, 2, 4\}$$

$$\text{frug} = \{0, 1, 2, 4\}/2^{D_f}$$

$$K_D = ?$$

 

# Decimation

- Major power consumption in CDR from distributing high speed clocks
- Hard to make frequency and phase integrators run at baud rate
- Save power by slowing down and widening data path
  - Lookup table version of BB PD can be done on slower wider data if desired
  - Decimation for proportional and integral paths do not need to be the same
  - Decimation can be done in two ways: summing or voting
- Decimating by L means frequency register only added once every L UI, reduces integral gain by L thus integral path gain changes to  $\text{frug}/2^{D_f}/L$  in linear model


# Decimation by Summing

- Add  $L$  phase error decisions  $(-1, 0, 1)$  together
  - No loss of information (acts like a pre-add)
  - Loop gain of proportional path is unchanged
  - In DSP this is called boxcar filter
  - Output is in range of  $-L:L$  once every  $L$  UI
  - $2L+1$  possibilities  $\log_2(2L+1)$  bits wide at baud/ $L$
  - Does not change loop sensitivity to transition density
  - **To reduce sensitivity to transition density we need to collapse multiple phase error decisions into a single decision**

# Decimation by Voting


- Voting takes  $L$  samples and then decides either early or late based upon a majority decision (output is -1, 0 or 1)
  - Equivalent to taking the sign of summing decimation
  - Output is 2 bits wide at  $\text{baud}/L$  rate
- The  $-L:L$  range from summing is reduced to  $-1:1$ 
  - Max gain reduced by factor of  $L$
- Reduces dependence on transition density
  - If we are late and we have 1 transition per  $L$  UI or  $L$  transitions per  $L$  UI we get the same output
- We can mix the two techniques and vote over sub-blocks and sum together if desired
- Proportional path loop max loop gain reduced by  $1/L$ 
  - Small signal gain for linear model best derived by a simulation

# Comparison of Decimation

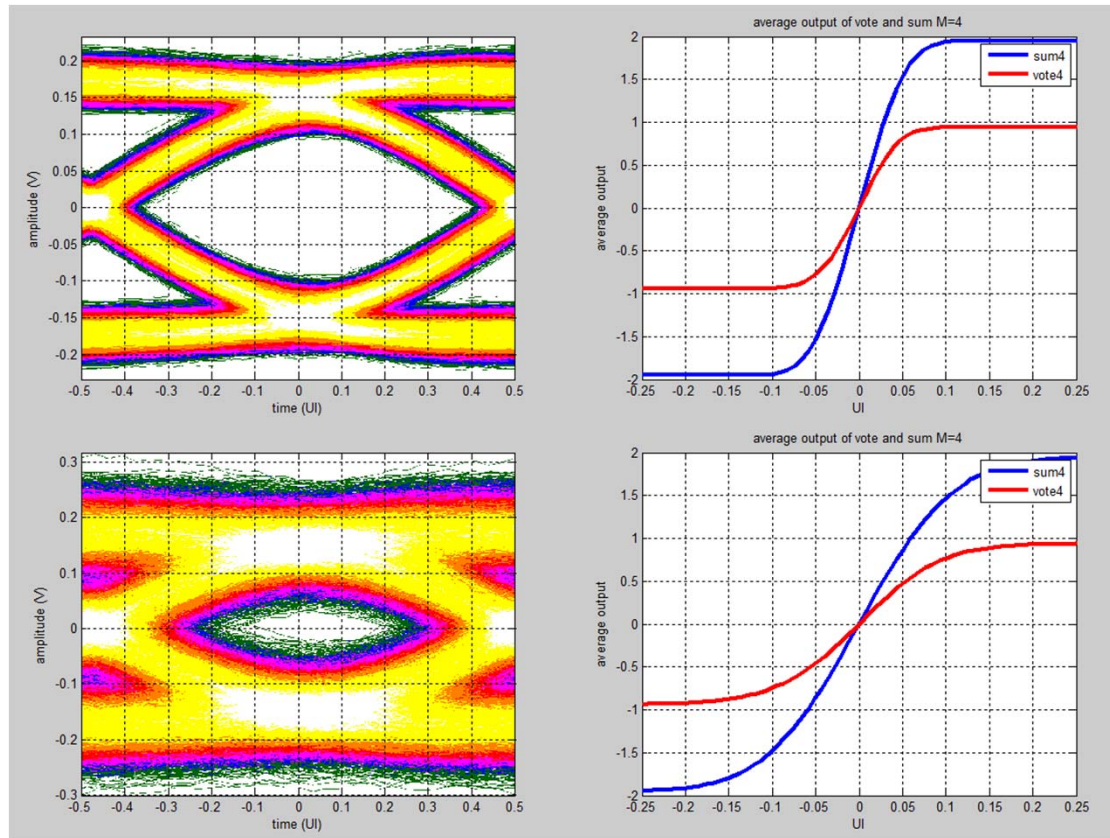

Both slope and maximum gain are reduced  
Rule of thumb: Votingx4 has about  $\frac{1}{2}$  small signal gain of summing x4  
Voting by different decimation factors will have different ratios

# Comparison of Summing Versus Voting

 

# DPLL Structure


$$L(z^{-1}) = \frac{K_{BB}K_DK_{DPC}}{1-z^{-1}} \left( \text{phug} + \frac{\text{frug}}{1-z^{-1}} \right) z^{-N}$$

$$K_{DPC} = 1/2^{(N+D_p)}$$

$$\text{phug} = \{0, 1, 2, 4\}$$

$$\text{frug} = \{0, 1, 2, 4\} / (L * 2^{D_f})$$
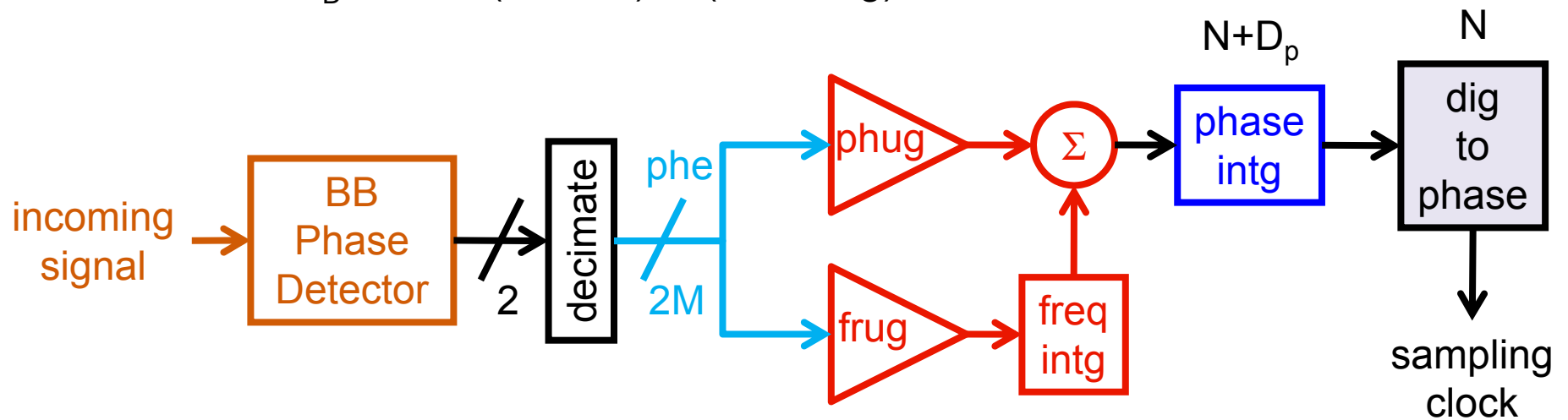
$$K_D = .5 \text{ (vote x4), } 1 \text{ (summing)}$$



# Latency ( $z^{-N}$ )

- A major concern in DPLL based CDRs is the latency of the proportional path
- Latency limits the allowable loop gain and bandwidth
- Excessive latency leads to reduction in stability leads to peaking
- Need to account for all analog delay and digital pipe stages
  - If decimating by  $L$  then each digital pipe stage is  $L UI!$
- Study impact later in design examples



# Summary

- Developed a small signal model of DPLL
- Went through DPLL block by block to understand the detailed operation and impact of loop parameters
- Put it all together and see how we use this knowledge for design

# CDR Example

- Baud rate is 5Gb/s
- $\sim \pm 1000$ PPM tolerance
- Frequency step of  $\sim 10$ PPM
- DPC is 5-bits (32 steps per UI)
  - Dither on a boundary is  $.03125$ UI - acceptable
- Phase integrator has 3 dither bits (8-bits total)
  - $1/256 = .0039$ UI/step is acceptable
- Decimate by voting over 4 decisions
  - CDR clock cycles are 4UI wide
- Assume latency around the loop is 20 UI (this includes delays for analog sections as well)

# Max PPM Tolerance

- 1000 PPM is  $.001\text{UI/UI}$
- CDR clock is  $4\text{UI}$  (cycle is  $4\text{UI}$ )
  - Frequency intg needs to supply  $.004\text{UI/cycle}$
- Phase integrator step is  $1/256 = .0039\text{UI}$ 
  - Freq integrator needs to be able to put in  $\pm 1$  per cycle
- We need 1 signed upper bit to get to  $-1$ 
  - $M=1$  (to represent either a 0 or a  $-1$ )
  - $D_f$  bits will get us very close to  $+1$ :  $(2^{D_f} - 1)/2^{D_f}$

# Min PPM Step Size for $D_f$

- 10PPM resolution means moving sampling phase  $.00004UI/cycle$
- 1 phase integrator step is  $.0039UI/cycle$
- Compute the required number of cycles between dither contribution ( $1$  in  $2^{D_f}$ )
  - $.0039/.00004 =$  one step every  $97.5$  cycles
  - Round up to power of  $2$  yields  $128$  or  $7$  bits
  - $D_f=7$
  - Total frequency integrator width is  $M+D_f = 8$

# Final Frequency Register Results

- $M = 1, D_f = 7$
- Maximum +PPM
  - $(127/128)/256/4 * 1e6 = 972.5\text{PPM}$
- Minimum -PPM
  - $(-1)/256/4 * 1e6 = -976.6\text{PPM}$
- Minimum PPM resolution
  - $.0039/2^7/4UI * 1e6 = 7.6172 \text{ PPM} < 10\text{PPM}$

# Pull-in Range

- Pull-in range is defined by how fast the proportional path can move in PPM
  - $\text{phug}/256/4\text{UI} = \text{phug}/1024 \text{ per UI} = 1/1024\text{UI per UI}$
- This is equal to **976.6PPM if we have a transition every 4 UI**
  - With 8B10B data at least 1 transition every 4UI thus we can achieve ~1000PPM pull-in
  - For uncoded data the pull-in range may be less!!!
- In general we can use larger phug at startup to increase pull-in range !

# DPLL CDR Small Signal Model


$$L(z^{-1}) = \frac{K_{BB} K_D 2^{-(N+D_p)}}{1-z^{-1}} \left( \text{phug} + \frac{\text{frug} \cdot 2^{-D_f} / L}{1-z^{-1}} \right) z^{-N}$$

$$L(z^{-1}) = \frac{13.3 \left( \frac{1}{2} \right) \cdot 2^{-8}}{1-z^{-1}} \left( \text{phug} + \frac{\text{frug} \cdot 2^{-7} / 4}{1-z^{-1}} \right) z^{-N}$$

For analysis assume that input jitter is Gaussian with  $\sigma = .03UI$

$$K_{BB} = \frac{1}{\sigma \sqrt{2\pi}} = \frac{1}{.03 \sqrt{2\pi}} = 13.3$$

# Using the Linear Model

 


$$H(e^{-j\omega}) = \frac{\phi_{\text{samp}}}{\phi_{\text{in}}} = \frac{L(e^{-j\omega})}{1 + L(e^{-j\omega})}$$

$$JT(e^{-j\omega}) = \left( \frac{\phi_{\text{in}}}{\phi_{\text{err}}} \right) \cdot \left( 1 - \frac{12\sigma}{T_{\text{UI}}} \right) = [1 + L(e^{-j\omega})] \cdot \left( 1 - \frac{12\sigma}{T_{\text{UI}}} \right)$$




 
# Transfer Function

$$H(e^{-j\omega}) = \frac{\phi_{\text{samp}}}{\phi_{\text{in}}} = \frac{L(e^{-j\omega})}{1 + L(e^{-j\omega})}$$


  
# Study Peaking as a Function of phug and frug



lower frug looks like right choice,  
really lower integral path gain


Final decision, lower integral path gain by .25

# Integral Path Gain Reduction



- Integral path gain =  $\text{frug}/2^{D_f}/L$ 
  - Either increase  $D_f$  or increase decimation ( $L$ ) for integral path
- Decimate frequency path by 16 instead of 4 (vote x16) decreases integral path by a factor of 4
  - Frequency integrator output only changes every  $16U_I$ , rate at which we can slew integrator reduced
  - Frequency integrator output still added to phase integrator every  $4U_I$  - PPM range not affected
- Frequency integrator was 8 bits at 1.25GHz now it is 8 bits at 312.5MHz
  - Fixed peaking and easier to implement!
- Minimum PPM resolution
  - $.0039/2^7/16 * 1e6 = 1.9043$  PPM
 
# Jitter Tolerance with Reduced Integral Path Gain

$$\text{JT}(e^{-j\omega}) = \left( \frac{\phi_{\text{in}}}{\phi_{\text{err}}} \right) \cdot \left( 1 - \frac{12\sigma}{T_{\text{UI}}} \right) = [1 + L(e^{-j\omega})] \cdot \left( 1 - \frac{12\sigma}{T_{\text{UI}}} \right)$$



# Impact of Latency

  


Latency needs to be controlled, a value of 20 is OK this design. If we can not meet latency then we need to lower gains = lower CDR bandwidth

# Next Step in Design Process

- Linear design provides much insight and a good starting point
- Need to check design based on linear model with a simple time step simulation
  - Start simple (no circuit distortions)
  - As design is refined add simulation complexity
  - Ultimately a very detailed system simulation will need to be run to verify final design
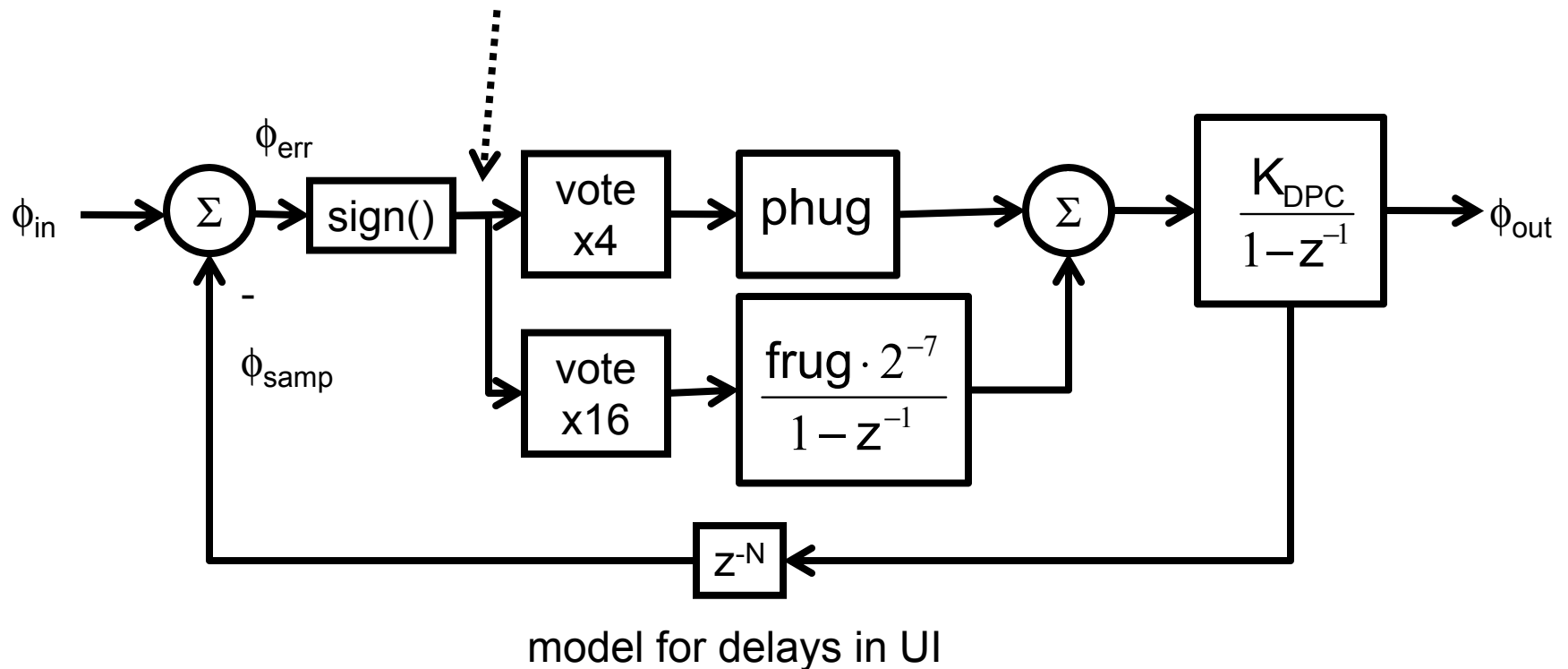
# Simple Time Step Simulator


BB detector output (set every other output to 0 for 50% transition density)






# Time Step Results

actual simulation results

 

 noise in simulation but removed from plot to focus on tracking




input phase noise is Gaussian,  $\sigma=.03$ , white out to 2.5GHz




# Time Step Results, Small Signal SJ (.1Ulp-p @ 1.5MHz)

actual simulation results

 

 
noise in simulation but removed from plot to focus on SJ tracking




SJ of .1Ulp-p at 1.5MHz plus input phase noise of Gaussian,  $\sigma=.03$ , white out to 2.5GHz

# Time Step Results, Larger SJ, (1Ulp-p @ 1.5MHz)

actual simulation results

 

 
noise in simulation but removed from plot to focus on SJ tracking




SJ of 1Ulp-p at 1.5MHz plus input phase noise of Gaussian,  $\sigma=.03$ , white out to 2.5GHz

# Time Step Results, Large Signal SJ, (2UIp-p @ 1.5MHz)

actual simulation results

 


 noise in simulation but removed from plot to focus on SJ tracking



SJ of 2UIp-p at 1.5MHz plus input phase noise of Gaussian,  $\sigma=.03$ , white out to 2.5GHz

# Time Step Results, 500 PPM Offset

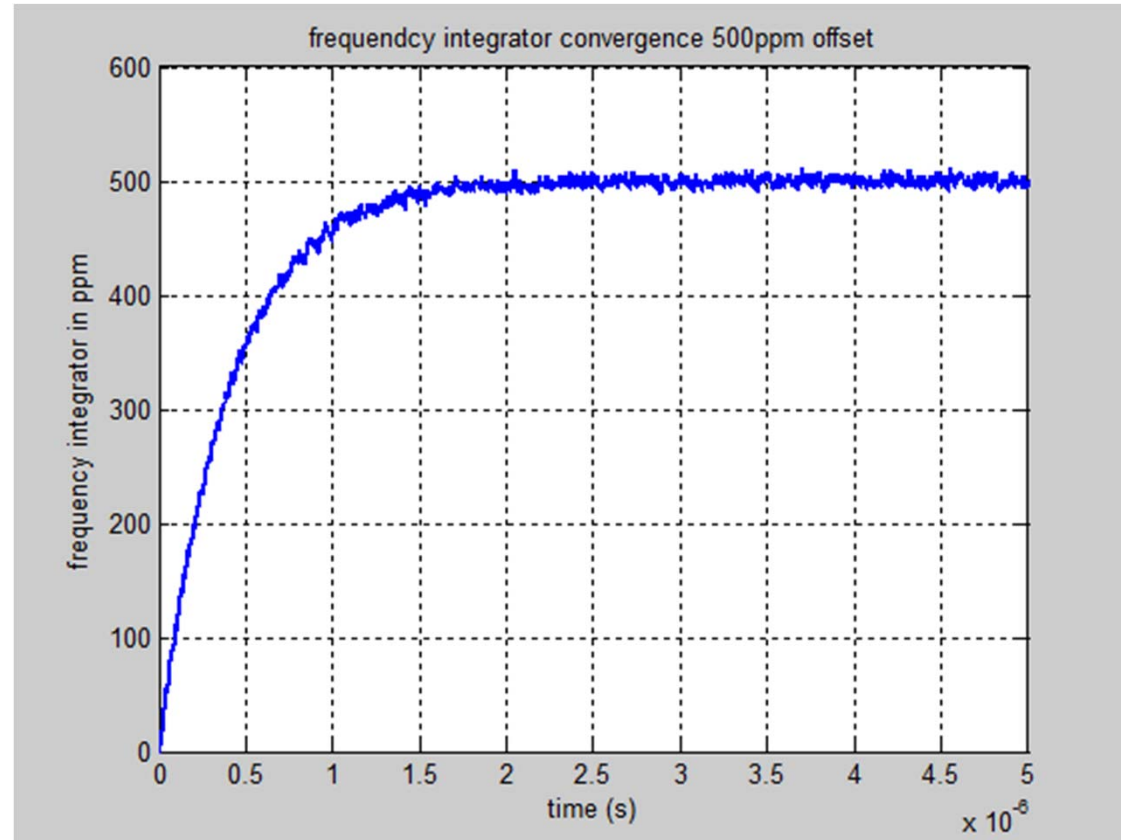

Design performance is reasonable, hold off on JT for next design

# Spread Spectrum Clocking (SSC)

- Asynchronous Spread Spectrum Clocking (SSC)
  - Clock frequency is slewed to reduce EMI
  - Found in USB3, SATA and others
- Greatly increases the PPM tracking range requirement for the CDR
- New criterion: PPM slew rate
  - 2<sup>nd</sup> order DPLL is underdetermined and tracking will be done with a steady state error

# SSC Example

- Add SSC requirements to previous design
- Baud rate is 5Gb/s
- ~ +/-7000PPM tolerance
- Frequency integrator slew rate > 2000PPM/ $\mu$ s
- DPC is 5-bits (32 steps per UI)
  - Dither on a boundary is .03125UI - acceptable
- Phase integrator has 3 dither bits (8-bits total)
  - $1/256 = .0039$
- Decimate phase path by voting over 4 decisions
  - CDR clock cycles are 4UI wide
- Decimate frequency path by voting over 16 decisions
- Assume latency around the loop is 20 UI (this includes delays for analog sections as well)

# Max PPM Tolerance



- 7000 PPM is  $.007\text{UI}/\text{UI}$
- CDR phase integrator runs at  $4\text{UI}$  cycle
  - Frequency intg needs to supply  $.028\text{UI}/\text{cycle}$
- Phase integrator step is  $1/256 = .0039\text{UI}$ 
  - Freq integrator needs to be able to put in  $\pm 7.2$  per cycle (round up to 8)
  - Max PPM is  $8/32/8/4 * 1\text{e}6 = 7812.5\text{PPM} > 7000\text{PPM}$
- We need 1 sign bit and 3 magnitude bits
  - $M=4$
- Previous design had  $D_f$  of 7bits

# PPM Slew Rate

- Want to slew frequency register at  $> 2000\text{PPM}/\mu\text{s}$ 
  - $1\mu\text{s}$  is 5000UI at 5Gb/s, which is 312.5 frequency integrator path CDR clock cycles for frequency integrator with vote x16 decimation ( $312.5\text{cycles} * 16\text{UI}/\text{cycle} = 5000\text{UI}$ )
- Want to slew  $2000\text{PPM}/312.5\text{cycles} = 6.4\text{PPM}/16\text{UI}$  clock cycle
- PPM resolution is 1.9043 PPM from previous analysis
  - Need to shift by at more than 3.36 bits every clock cycle
  - Frequency chasing is under-determined
  - frug = 4 is bare minimum and gives us some margin



  
# Time Step Results for SSC with 2000PPM/ $\mu$ s Triangle Wave



Residual error because tracking a frequency ramp with a 2<sup>nd</sup> order system is underdetermined, static error  $\sim .01UI_{p-p}$

# Jitter Tolerance

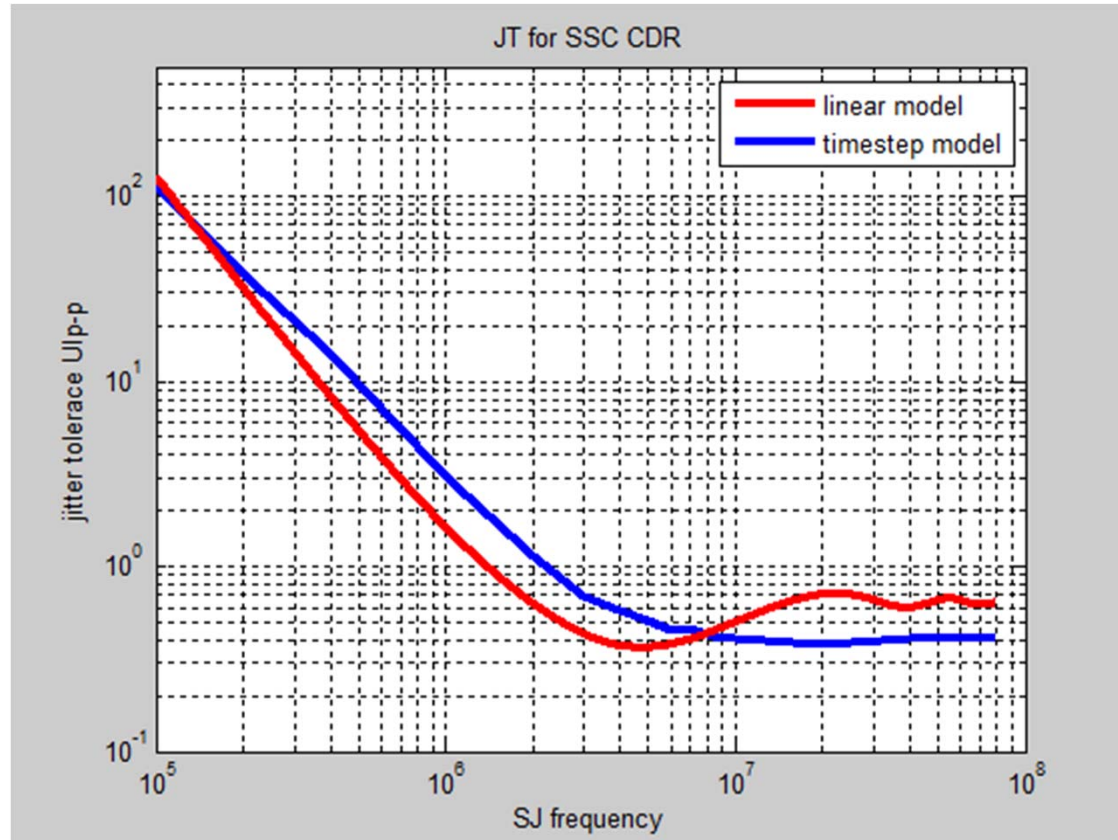

# SSC Design Summary

- Needed to increase  $M$  to allow tracking a larger PPM range
- Needed to increase integral path gain to track a faster PPM ramp
  - Increasing frug allows flexibility
- Same small signal model we started first design with that exhibited peaking - but the time step simulation results look good!
  - Jitter tolerance is a large signal event
  - Linear model is useful as an initial guide but it should not be used for final design decisions

# Conclusion

- DPLL based CDR derived from an analog BB CDR
- BB phase detector modeled and studied
- CDR architecture walked through and linear model developed
- Linear model used to set initial design
- Time step simulations will always need to be done to finalize designs