
Managing offset and flicker noise

Axel Thomsen
axel.thomsen@silabs.com
Silicon Laboratories Inc.
Austin, TX, USA

February 19, 2012

Outline

- Motivation and history
 - Offset and flicker noise background
 - Techniques to manage offset and flicker noise
 - Chopper Stabilization
 - Basic idea
 - Switched capacitor and continuous time implementations
 - Chop artifacts and their removal
 - Second order effects
 - Autozero
 - Basic idea
 - Implementation examples
 - Second order effects
 - Correlated double sampling
 - An extension of Autozero into switched capacitor circuits
 - Conclusion
-

Motivation: High Gain Example

- ❑ 1mV signal, 2 μ V of noise
- ❑ Would like an amplifier with a gain of 1000x
- ❑ 1V signal, 2mV noise,
- ❑ use a 10 bit ADC

BUT –

- ❑ 9mV of opamp offset
- ❑ limits the gain to 100x
- ❑ 900mV of amplified offset, 100mV of amplified signal, 0.2mV of amplified noise
- ❑ Use a 13 bit ADC

The year 1956:HP 150-1800

From www.hparchives.com


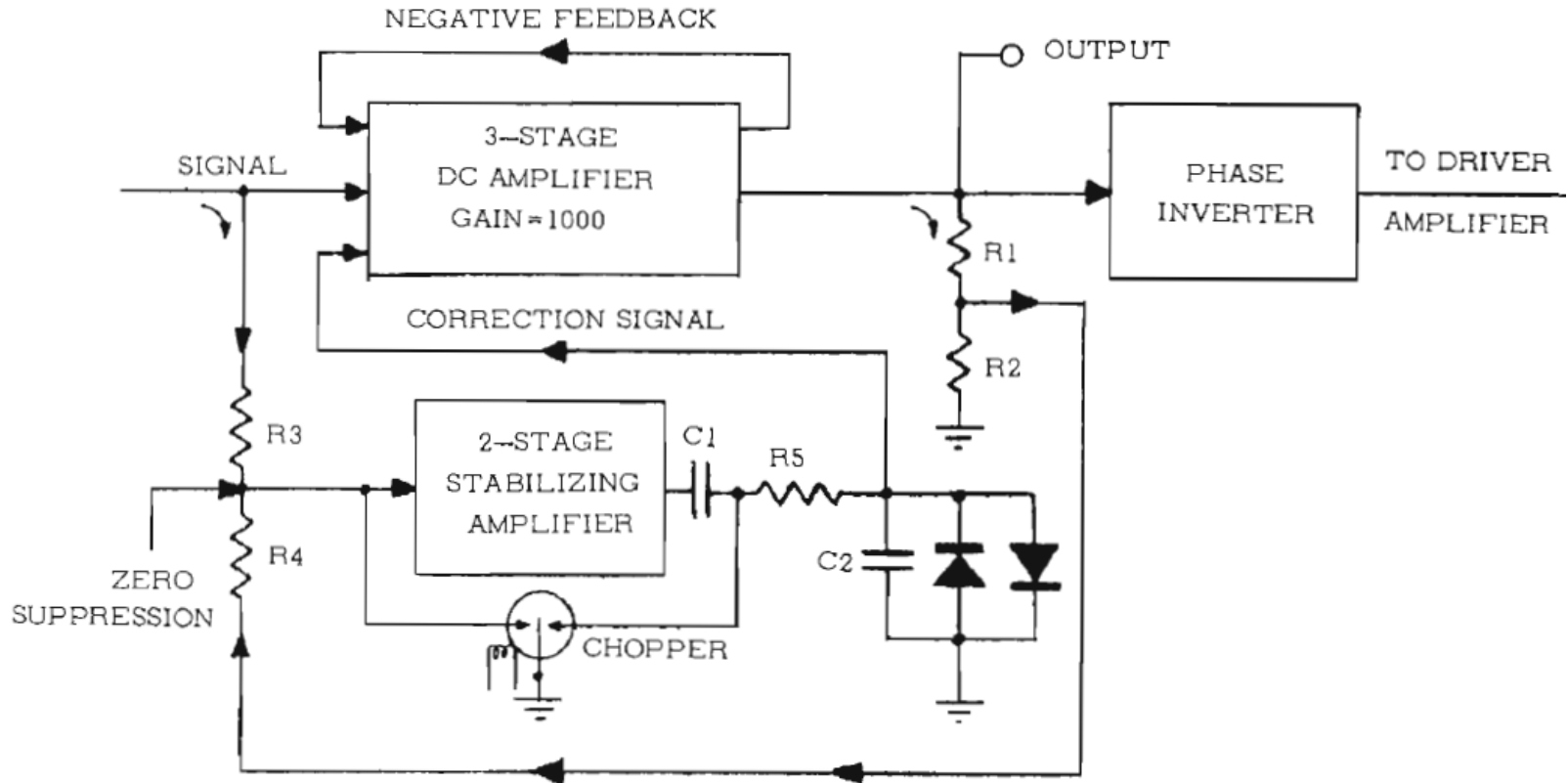


Figure 3. Basic Circuits of the Stabilized DC Preamplifier.

Motivation: Small Signals, Low Noise

 
- Hall Sensor produces μV level signals
- Flicker noise in a FET based opamp can have $100\mu\text{V}_{\text{pp}}$ in 0.1 to 10Hz bandwidth
- Thermal noise in 10Hz can be around $1\mu\text{V}_{\text{pp}}$ in the same band
- Flicker noise buries the signal – can be more than an order of magnitude above the thermal noise level



Typical noise spectrum of a MOSFET

Motivation: Ratiometric Example

 - Bridge transducers – we want to measure $\Delta R/R$



$$\Delta V_1 = V_{ref} * \Delta R / R$$

$$\Delta V_2 = A * \Delta V_1 + v_{os1}$$


$$D = (\Delta V_2 + v_{os2}) / V_{ref}$$

$$D = A * \Delta R / R + (A * v_{os1} + v_{os2}) / V_{ref}$$

If $v_{os1} = 0$ and $v_{os2} = 0$, $D = A \Delta R / R$
 Offset ruins this ratiometric measurement

The bipolar and JFET days

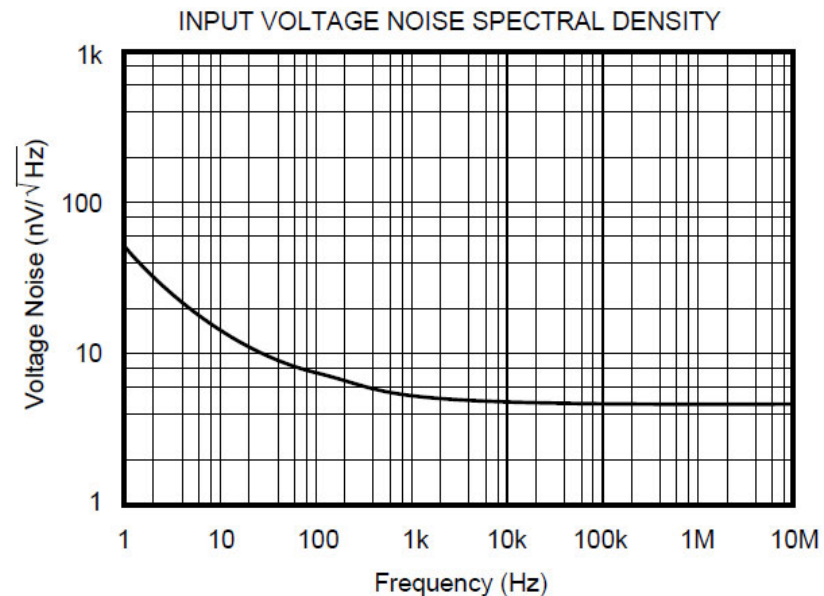
- Good devices from a matching and flicker noise perspective, especially JFETs
- Devices like the OP627 provided excellent DC measurement capability – JFET input
- Offset $< 100\mu\text{V}$,
- offset drift $< 0.8\mu\text{V}/\text{C}$
- $15\text{nV}/\sqrt{\text{Hz}}$ noise density at 10Hz
- Offset and flicker noise are minor problems.



Noise spectrum OP627


Comparison to a MOS opamp

 - MCP6241
- $V_{os}=5\text{mV}$
- $dV_{os}/dT=3\mu\text{V}/\text{C}$
- Noise density at 10Hz 250nV/ $\sqrt{\text{rtHz}}$
- Noise spectrum has significantly higher flicker noise corner



Noise spectrum MCP6241

CMOS device characteristics

 


- $V_{T0} = kT/q(\ln(N_D * N_A / n_i^2) + \ln(N_A / n_i) - Q_b / C_{ox} - Q_{ox} / C_{ox})$
- $V_T = V_{T0} + \gamma * \sqrt{V_{sb} + 2\Phi_F} - \sqrt{2\Phi_F}$
- V_T depends to first order on doping and oxide thickness, both of which have tolerances.
- The larger the area the more consistent the value, the less variation -> inverse proportional to root of gate area

Offset

- Basic Pelgrom model (Pelgrom et al. 1989)
 - $V_{os} = v_{os1} / \sqrt{W * L}$
 - V_{os1} is the standard deviation of a device with 1um gate area
 - Based on characterization from the fab
 - This is the best case
- Offset drift is significant – up to 50% of original offset according to a datasheet survey of uncompensated CMOS opamps
- Additional effects to be considered due to layout
 - Non-identical neighborhoods add to this
 - Specifically distance from active edge
 - Distance from well edge
 - Poly in the neighborhood
 - Active in the neighborhood

Input referred offset example

- Each device has a standard deviation of $\Delta VT = A/\sqrt{Wn \cdot Ln}$
- The mismatch is converted to an output current by multiplying with each device $gm = \sqrt{K' \cdot W/L \cdot I_d}$.
- The output current is converted to an input signal by dividing with the input device $gm_1 = gm_2$ (input referred)
- M1 and M2 and devices 3 and 4 each have identical parameters, M5 contribution gets cancelled through symmetry
- Since these are probabilities they sum as rms.

 

$$V_{os}^2 = V_{os1}^2 + v_{os2}^2 + (v_{os3}^2 + v_{os4}^2) \cdot (g_{m3}/g_{m1})^2$$

$$V_{os}^2 = A^2 \cdot 2 / (W_1 \cdot L_1) + A^2 \cdot 2 / (W_3 \cdot L_3) \cdot K'_n / K'_p \cdot (W_3 / L_3) / (W_1 / L_1)$$

$$V_{os}^2 = A^2 \cdot 2 / (W_1 \cdot L_1) \cdot (1 + K'_n / K'_p \cdot L_1^2 / L_3^2)$$

Example $A = 4 \text{ mV} \cdot \mu\text{m}$, $W = 40 \mu\text{m}$, $L_1 = 0.1 \mu\text{m}$, $L_3 = 0.8 \mu\text{m}$


$K'_p = 200 \mu\text{A}/\text{V}^2$, $K'_n = 800 \mu\text{A}/\text{V}^2$

$$v_{os} = 4 \text{ mV} / 2 \cdot (1 + 1/16) = 2.125 \text{ mV}$$

Flicker noise or 1/f noise

- A simple explanation
 - Surface effect – carrier recombination at surface traps
- Basic textbook model – coarse, does not take into account bias dependency etc.
 - KF and AF are model parameters
 - AF is close to 1
 - $V_n = KF / \sqrt{W * L} / f^{AF}$
- Offset looks like 'static' 1/f noise – whatever works on 1/f noise works for offset, too.

Noise spectrum of MOS device

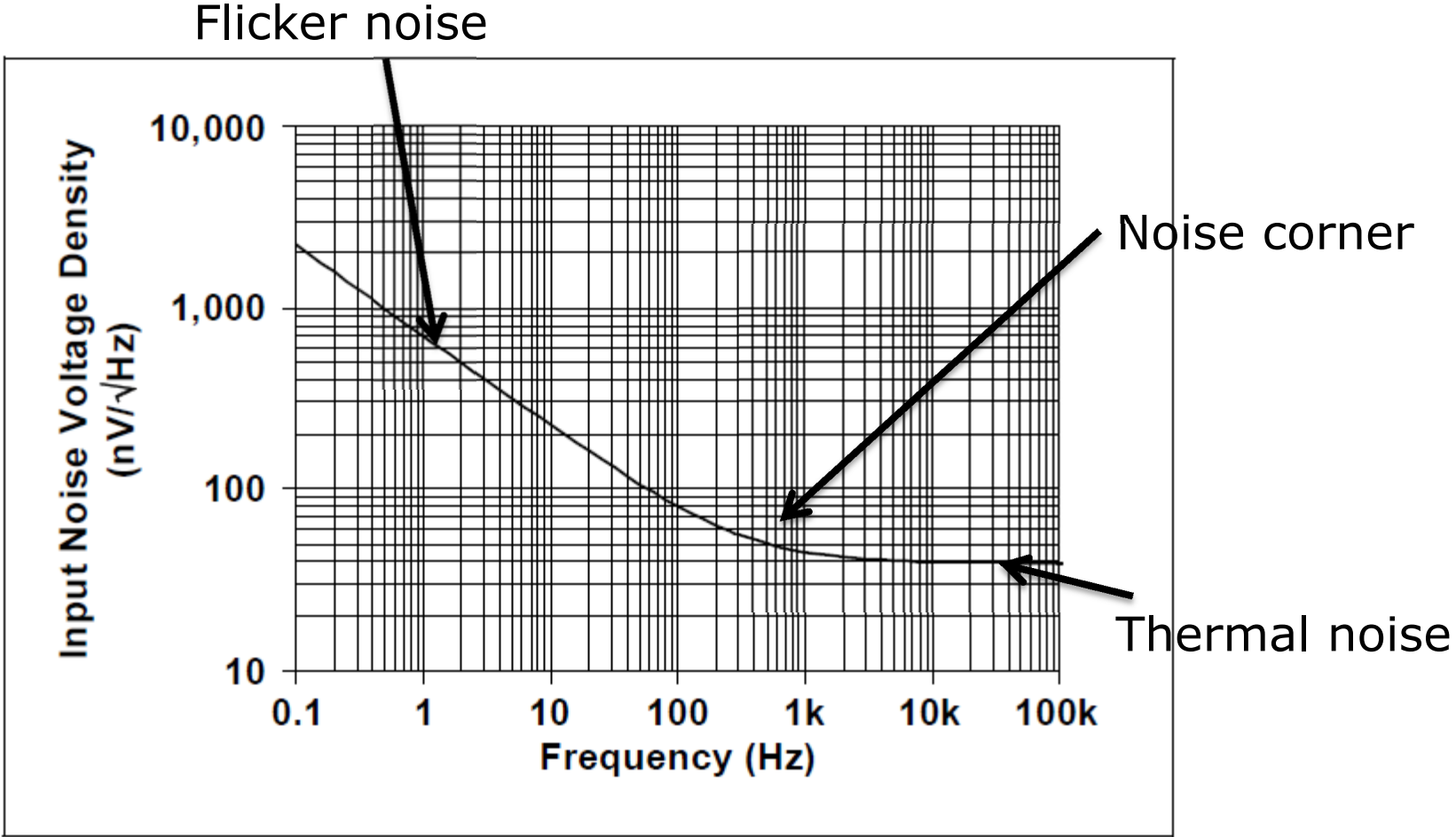

Flicker noise analysis example


Each device has a flicker noise of $V_n = \sqrt{Kf/(W_n * L_n * f^{AF})}$

The voltage noise is converted to an output current by multiplying with each device gm.

The input signal is converted to an output current by multiplying with the input device gm1=gm2

M1 and M2 match, M3 and M4 match, M5 contribution gets cancelled through symmetry

 Since these are noise voltages they sum as rms.




$$V_n^2 = V_{n1}^2 + v_{n2}^2 + (v_{n3}^2 + v_{n4}^2) * (g_{m3}/g_{m1})^2$$

$$V_n^2 = K_{Fp}/f * 2 / (W_1 * L_1) + K'_n / K'_p * K_{Fn} / f * 2 / (W_3 * L_3) * (W_3 / L_3) / (W_1 / L_1)$$

$$V_n^2 = K_{Fp} / f * 2 / (W_1 * L_1) (1 + K'_n / K'_p * K_{Fn} / K_{Fp} * L_1^2 / L_3^2)$$

See Johns/Martin chapter 4

Flicker noise analysis example

 

$$V_n^2 = K_{Fp} / f * 2 / (W_1 * L_1) (1 + K'_n / K'_p * K_{Fn} / K_{Fp} * L_1^2 / L_3^2)$$

Example

$$K_{Fn} = 2e-23$$

$$K_{Fp} = 1e-23$$

$$K'_p = 200 \mu\text{A}/\text{V}^2$$

$$K'_n = 800 \mu\text{A}/\text{V}^2$$

$$W = 40 \mu\text{m}, L_1 = 0.1 \mu\text{m}, L_2 = 0.8 \mu\text{m}, f = 1 \text{Hz}$$

$$V_n^2 = 1e-23 / 2 * (1 + 1/8) = 6.25e-22 \text{V}^2/\text{Hz}$$

$$V_n = 25 \text{pV}/\text{sqrtHz}$$


How to manage offset and flicker noise

- ❑ AC coupling – for example in audio
- ❑ System level planning (e.g. low IF vs. zero IF)
- ❑ Upmodulation of the signal above the flicker noise corner – chopper stabilization
- ❑ One time offset calibration
- ❑ periodic offset calibration – autozero
- ❑ Separation of signal and error through correlated double sampling




Outline

- Motivation and history
 - Offset and flicker noise background
 - Techniques to manage offset and flicker noise
 - Chopper Stabilization
 - Basic idea
 - Switched capacitor and continuous time implementations
 - Chop artifacts and their removal
 - Second order effects
 - Autozero
 - Basic idea
 - Implementation examples
 - Second order effects
 - Correlated double sampling
 - An extension of Autozero into switched capacitor circuits
 - Conclusion
-

Chopper Stabilization

 


Transistor implementation

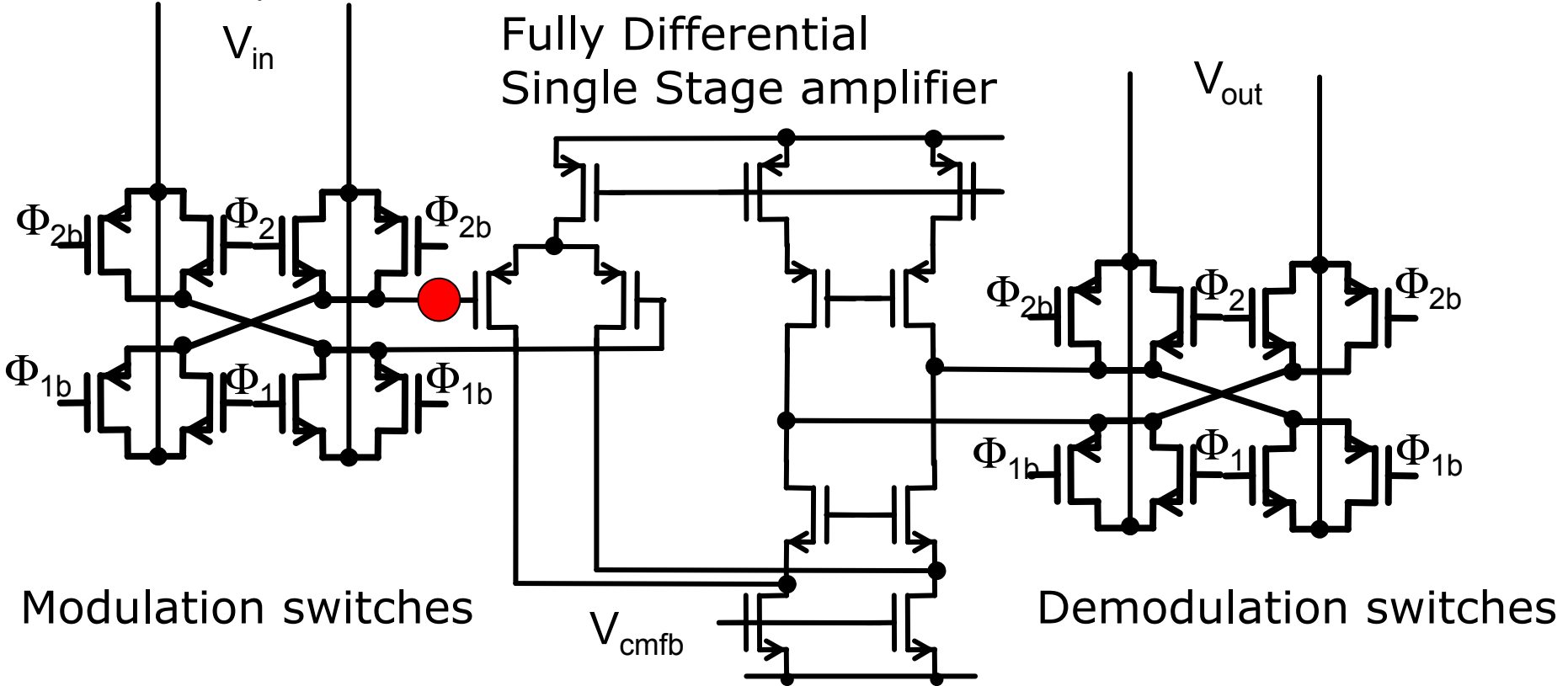  

Chopper amp in SC circuit


2 cycles of charge and dump $V_{out} = (V_{in} - v_{os} + V_{in} + v_{os}) * C_{in} / C_{int}$

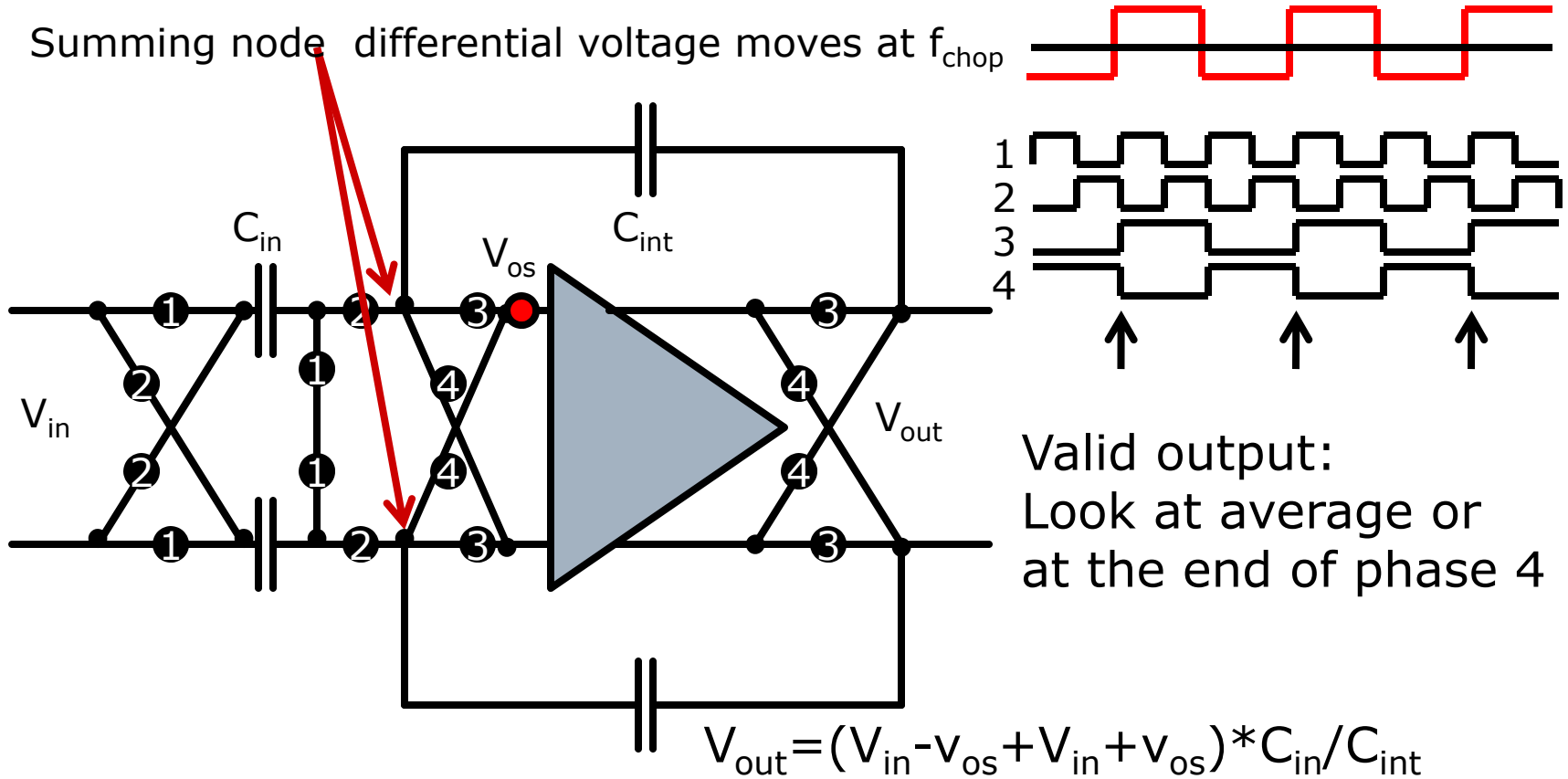Summing node differential voltage moves at f_{chop}



Waveform

Summing
node

 


input
node


output
node

2 stage opamp implementation

 Fully differential, completely symmetric
Chopping of first stage only, no capacitors within chopper




Waveforms (inverting amplifier)

 

Chopper stabilized 2 stage opamp

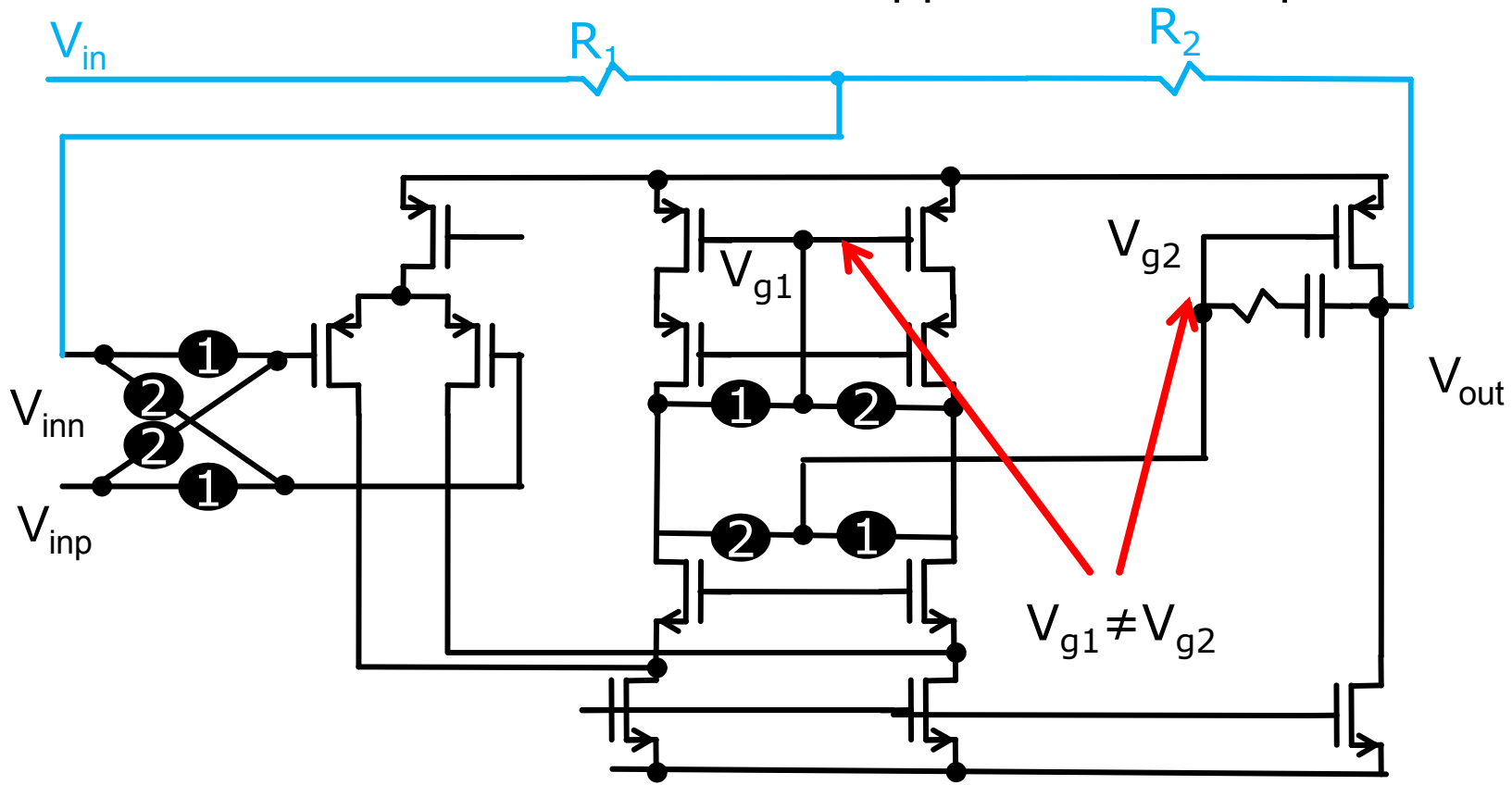
Single ended – not fully symmetric
Danger – systematic offset
Chopper cannot help!




Asymmetry issue – caution!

- Closer look at two stage opamp and limiter of accuracy


input

 


output

 

First stage
output

 

Parasitic switched capacitors

 


C_{p1} and C_{p2} are fundamental, must be taken into account
 C_{p3} and C_{p4} must be avoided

Input current associated with these can affect interfaces
– not suitable for very high impedance sensors


Chop frequency considerations

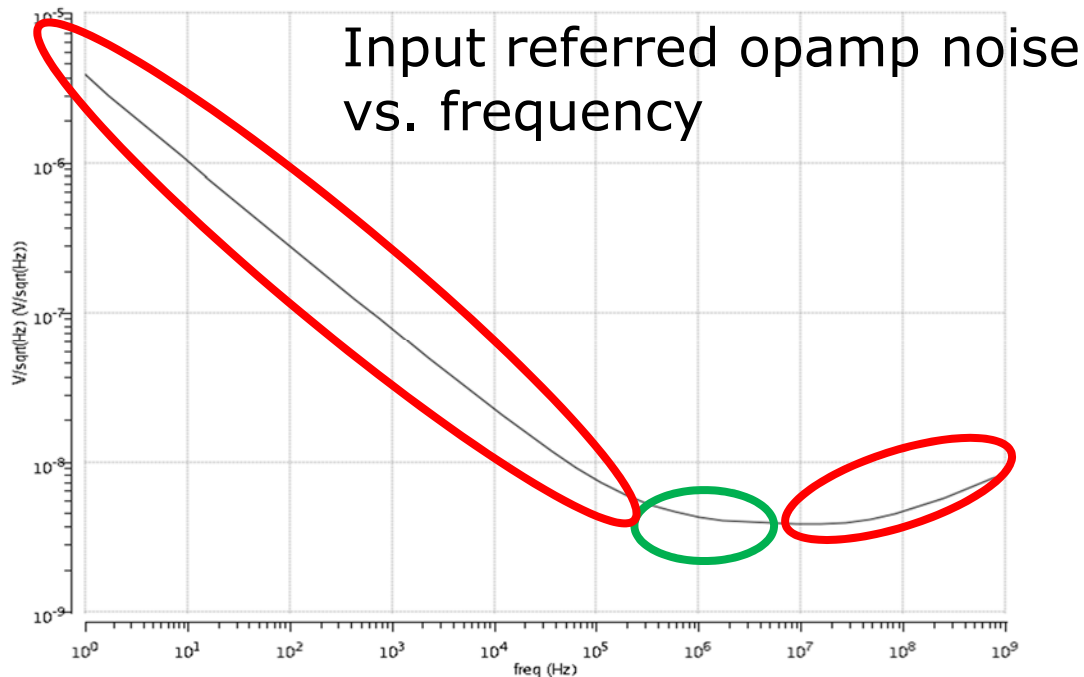- Chop frequency – best above the noise corner
- Keep it low to minimize the switched capacitor effect
- Must be much faster than amplifier bandwidth



Chop artifacts

 
- Imagine an opamp in a gain50x configuration
- $V_{os}=5\text{mV}$, $v_{\text{signalmax}}=5\text{mV}$ @10kHz
- 250mV signal @10kHz plus 250mV square wave at 500kHz – the chopper drives the bandwidth, slew rate specs!



Waveforms of chop artifacts

- Example: offset 5mV, gain of 50


Summing
node

 


output

Eliminate the artifacts

 - Totally different behavior, square wave is absorbed and summing node acts stable!
- Filter removes upmodulated offset inside the opamp





Removal of the chop artifact

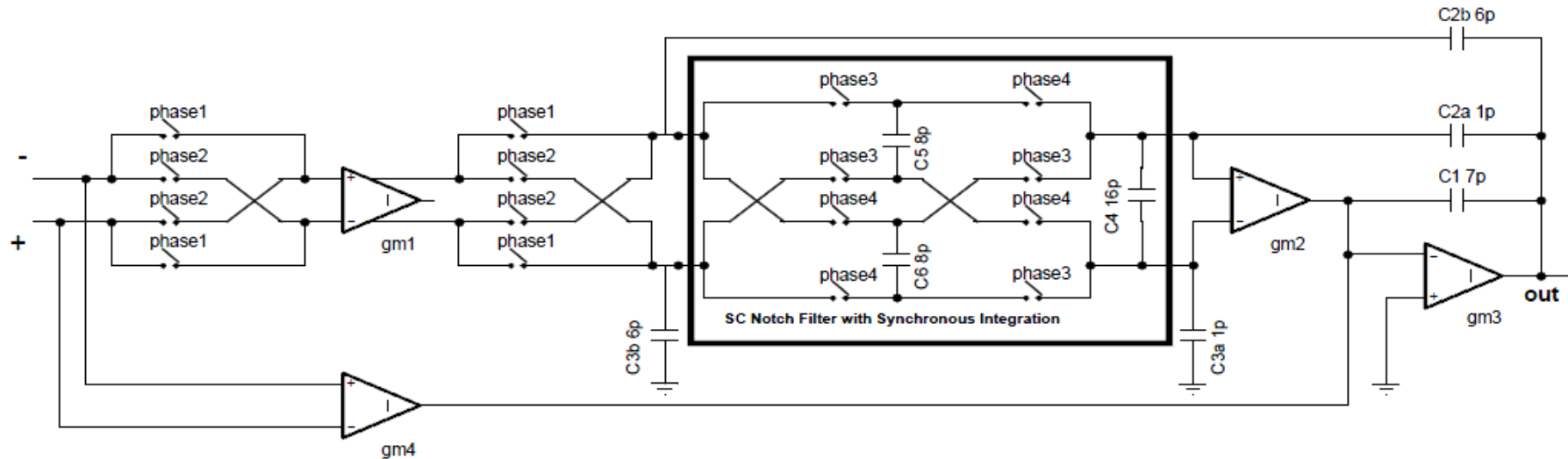

- ❑ Notch filter inserted after chopped stage g_{m1}
- ❑ Switched capacitor filter is synchronous to chop frequency, so notch is very precise
- ❑ Feedforward compensation to maintain stability through g_{m4}


Burt, Zhang, 2006

Switched Capacitor Notch Filter

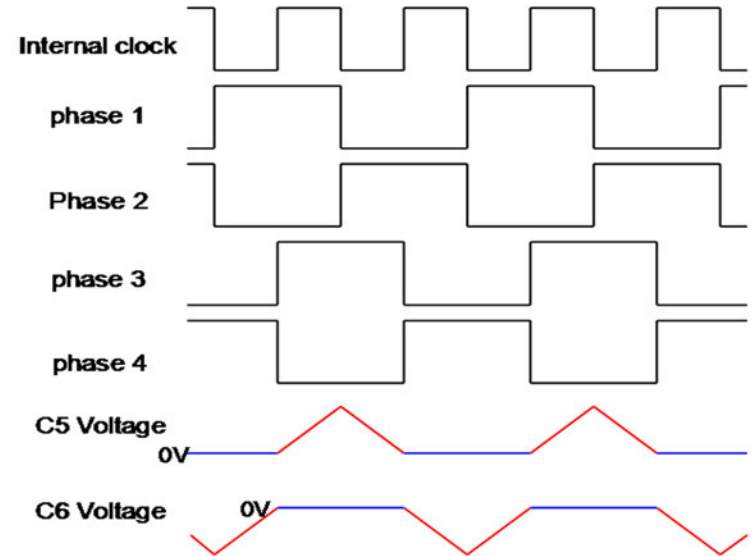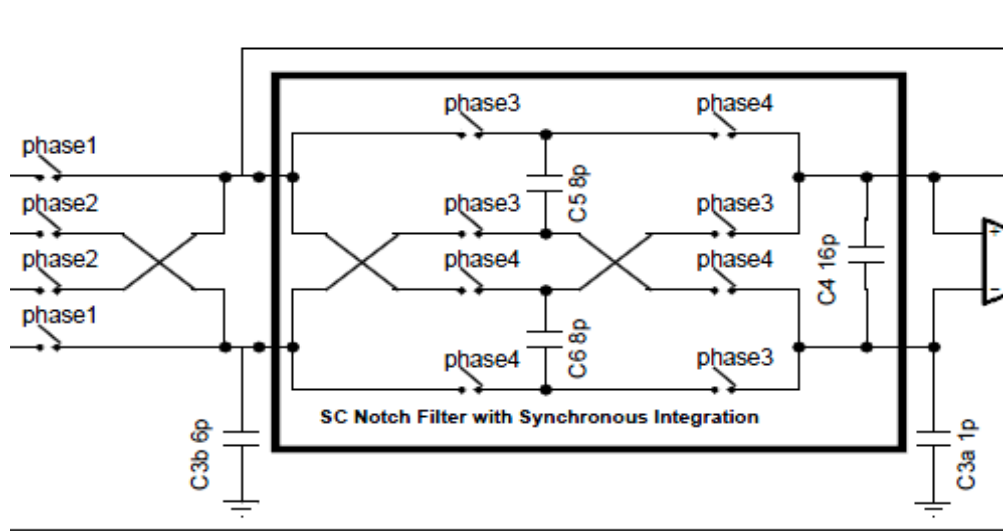

- Phase 3 and 4 are shifted 90° to chop clock
- Integration of two half chop phases on C5 and C6
- Blue waveform drives output stage – no ripple!

Another implementation

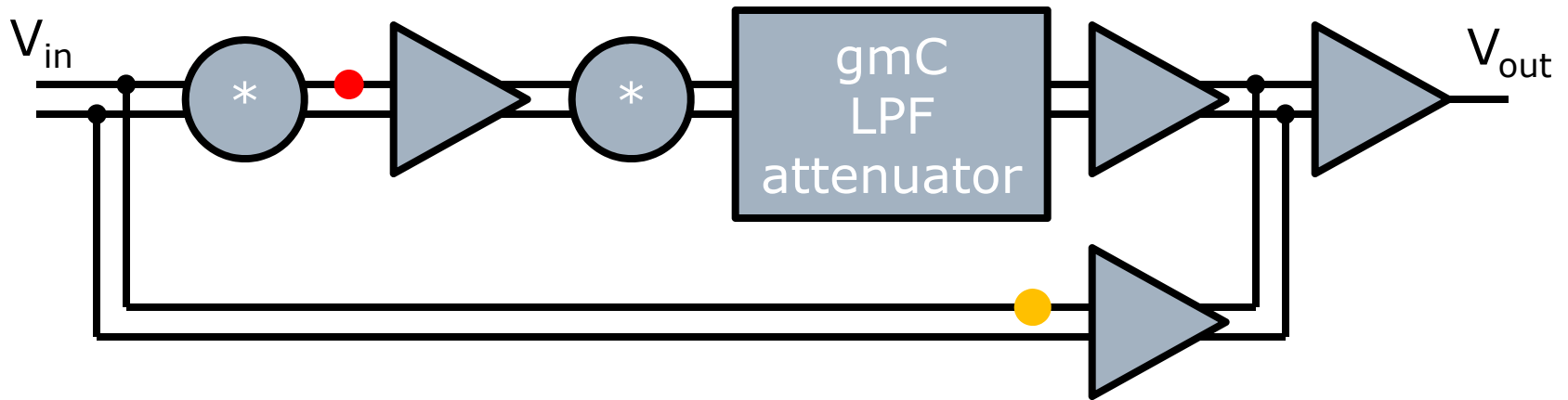


- ❑ Similar idea, 1MHz chop frequency, 3 pole 100kHz filter, 1/64 attenuation, removes upmodulated offset by 96dB
- ❑ Chop artifacts on output are insignificant

Thomsen, 2000


Chopper implementation details

- Current steering at the output

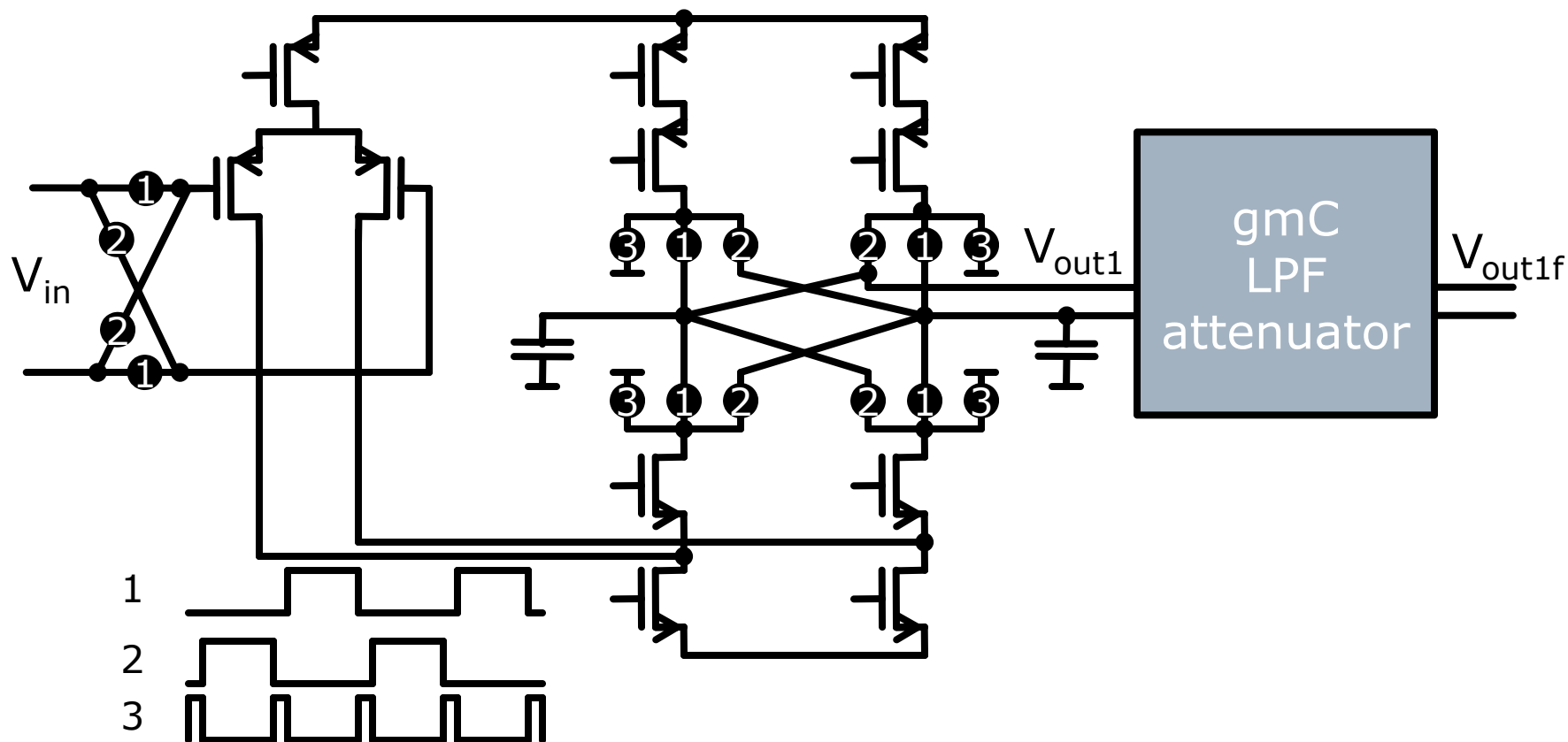

Results for the Cirrus CS3001

 
- Low noise in band
6nV/rtHz
- Flicker noise corner
0.05Hz
- Offset <10 μ V
- Offset drift <50nV/C
- By far exceeds the
OP627 example
from above



Noise spectrum of CS3001


Alternate proposal

 - Signal and offset are still separate in frequency
- Detect the presence of ripple at the output of the opamp
- With another modulation step the amplified ripple can be brought to DC.
- Integration of this error can create a cancellation of the offset
- Still a system without sampling, so no significant noise penalty!



Wu, Makinwa, Huijsing, 2009, 2011

Removal of chop artifacts

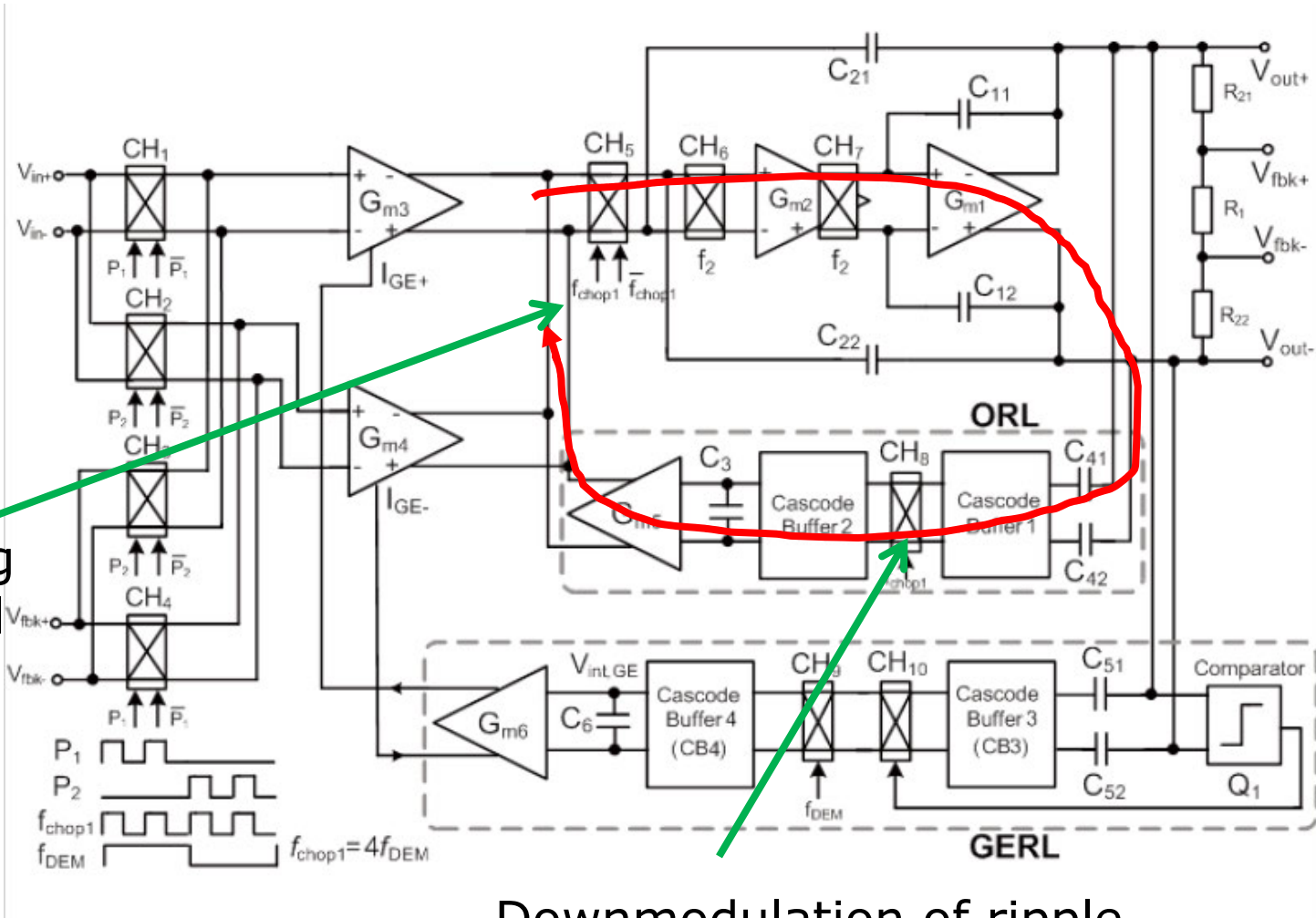

Offset
cancelling
DC signal

Downmodulation of ripple

Noise Analysis: PSS/PNOISE


- Periodic Steady State Analysis followed by PNOISE
 - The simulator finds a repetitive transient waveform (here the chop frequency period)
 - A noise analysis is performed at many timesteps along the way
 - The transfer function and the output noise are calculated as the sum of all these solutions
 - Large signal effects such as modulation and sampling are captured!
 - See cadence Application note in References

Noise Analysis: PSS/PNOISE

- Simulation setup:
 - PSS beat frequency '500kHz', '10' harmonics, 'shooting' method
 - Pnoise '1 to 250kHz', maximum sidebands '10'
 - Output node: amplifier output
 - Noise type 'sources'
 - Input signal grounded for noise measurement

Noise simulation results

Chopper off – noise corner 500kHz

 

Chopper on: no thermal noise increase

List of noise contributors

No chopping – all flicker noise


Device	Param	Noise Contribution	% Of Total
/M122	fn	1.02594e-08	30.24
/M123	fn	1.02547e-08	30.22
/M125	fn	2.3545e-09	6.94
/M124	fn	2.29332e-09	6.76
/M116	fn	2.18637e-09	6.44
/M117	fn	2.13138e-09	6.28
/M118	fn	1.65962e-09	4.89
/M119	fn	1.64596e-09	4.85
/R48	rn	7.03901e-10	2.07
/M120	fn	8.89083e-11	0.26

chopping – thermal noise

/R48	rn	7.74774e-09	63.17
/M116	id	4.4507e-10	3.63
/M117	id	4.45055e-10	3.63
/M122	id	4.00054e-10	3.26
/M123	id	3.99021e-10	3.25
/M122	fn	3.26811e-10	2.66
/M122	fn	3.26735e-10	2.66
/M124	id	3.13567e-10	2.56
/M125	id	3.13498e-10	2.56
/M117	fn	2.53907e-10	2.07

mixed signal implementation?

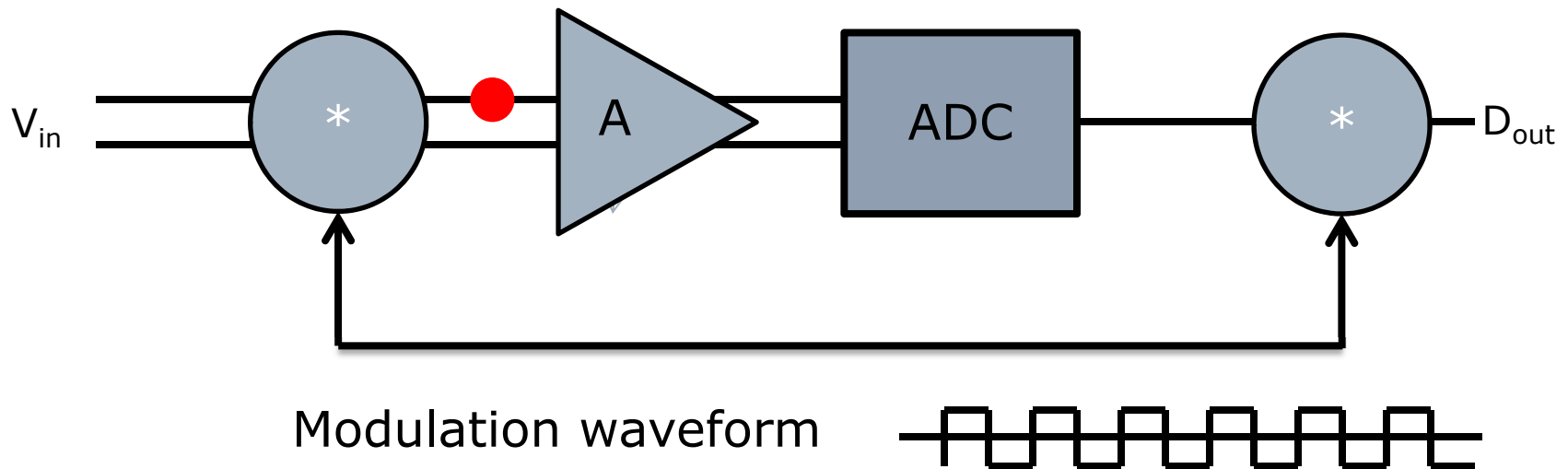- The demodulation can happen in the digital domain
- All bandlimiting effects within the chopper are harmful
- Like to use slow chop frequency – effective offset removal, limited 1/f noise removal



Summary

- ❑ Chopping can greatly improve offset and $1/f$ noise through symmetry
- ❑ No noise penalty
- ❑ In continuous time application, watch or remove the chop artifacts
- ❑ Remaining transients limit accuracy
- ❑ Low risk in a switched cap application
- ❑ Watch out for switched capacitor connections limiting impedance on input and output
- ❑ Watch out for sampling/aliasing of a chopped signal – remove artifacts first

Outline

- Motivation and history
 - Offset and flicker noise background
 - Techniques to manage offset and flicker noise
 - Chopper Stabilization
 - Basic idea
 - Switched capacitor and continuous time implementations
 - Chop artifacts and their removal
 - Second order effects
 - Autozero
 - Basic idea
 - Implementation examples
 - Second order effects
 - Correlated double sampling
 - An extension of Autozero into switched capacitor circuits
 - Conclusion
-


Definition of autozero

- Phase 1: Measure and store offset
 - Circuits are taken 'off line' to calibrate offset
 - Results of calibration are stored digitally or analog

- Phase 2: Measure signal, subtract offset
 - Calibrated circuits used for measurement
 - A means to subtract has to be provided – digitally or analog


Autozero ADC example

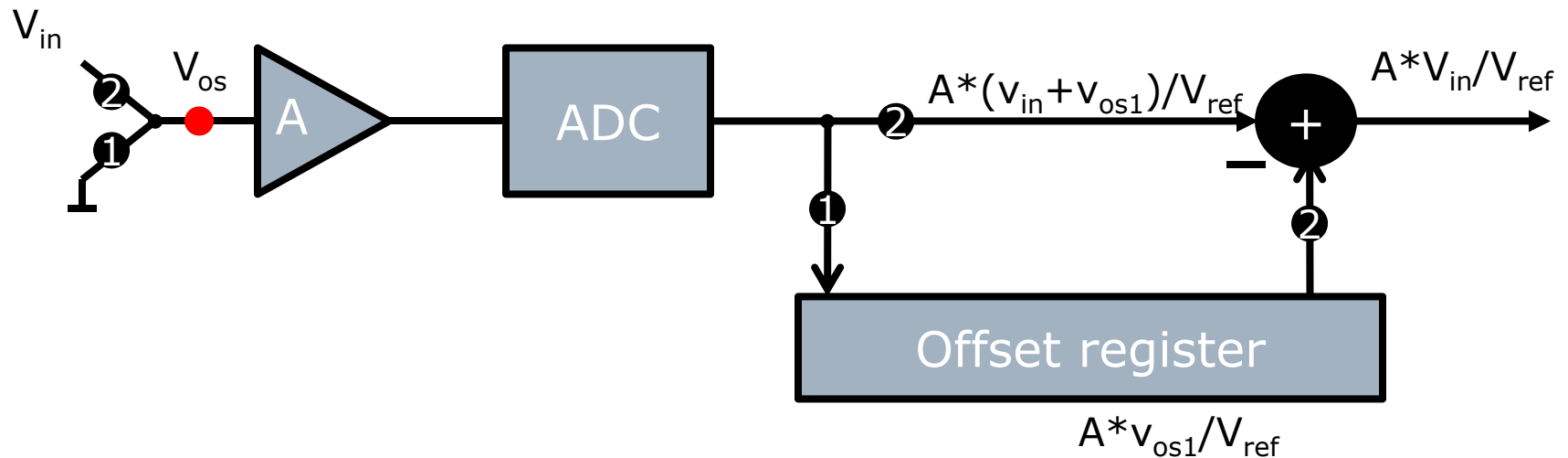- Short the input to ground
- Take a measurement of the error and store it
- Measure the input
- Subtract the offset – result is offset corrected




low gain comparator example

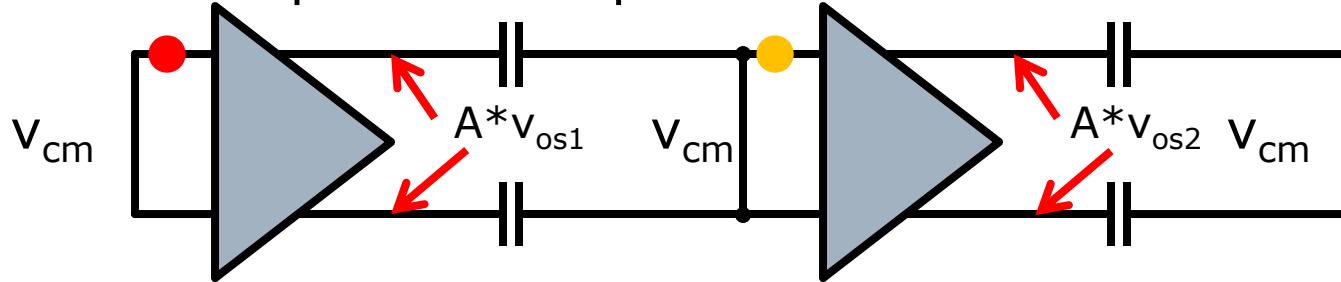- Low gain = gain * offset within output dynamic range
- Auto zero phase: Sample and store error



 
- Operation phase: Amplify signal , subtract error




see Allen/Holberg

high gain opamp example

 - High gain – residual error V_{os}/A is small enough
- Auto zero phase – sample and store offset



 
- Operation phase: Amplify signal , subtract error




see Allen/Holberg

Another opamp example

 
- Autozero phase: measure the offset and store it



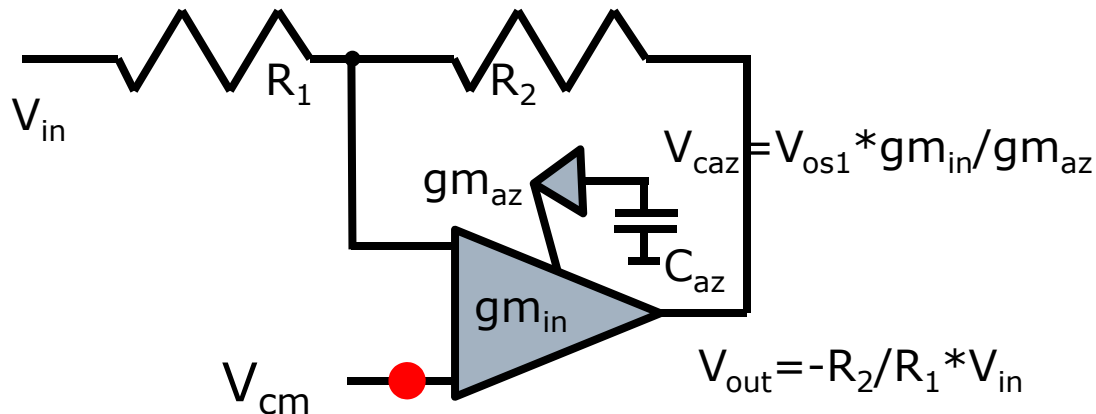- Operation phase: amplify signal and subtract offset




Transistor level example

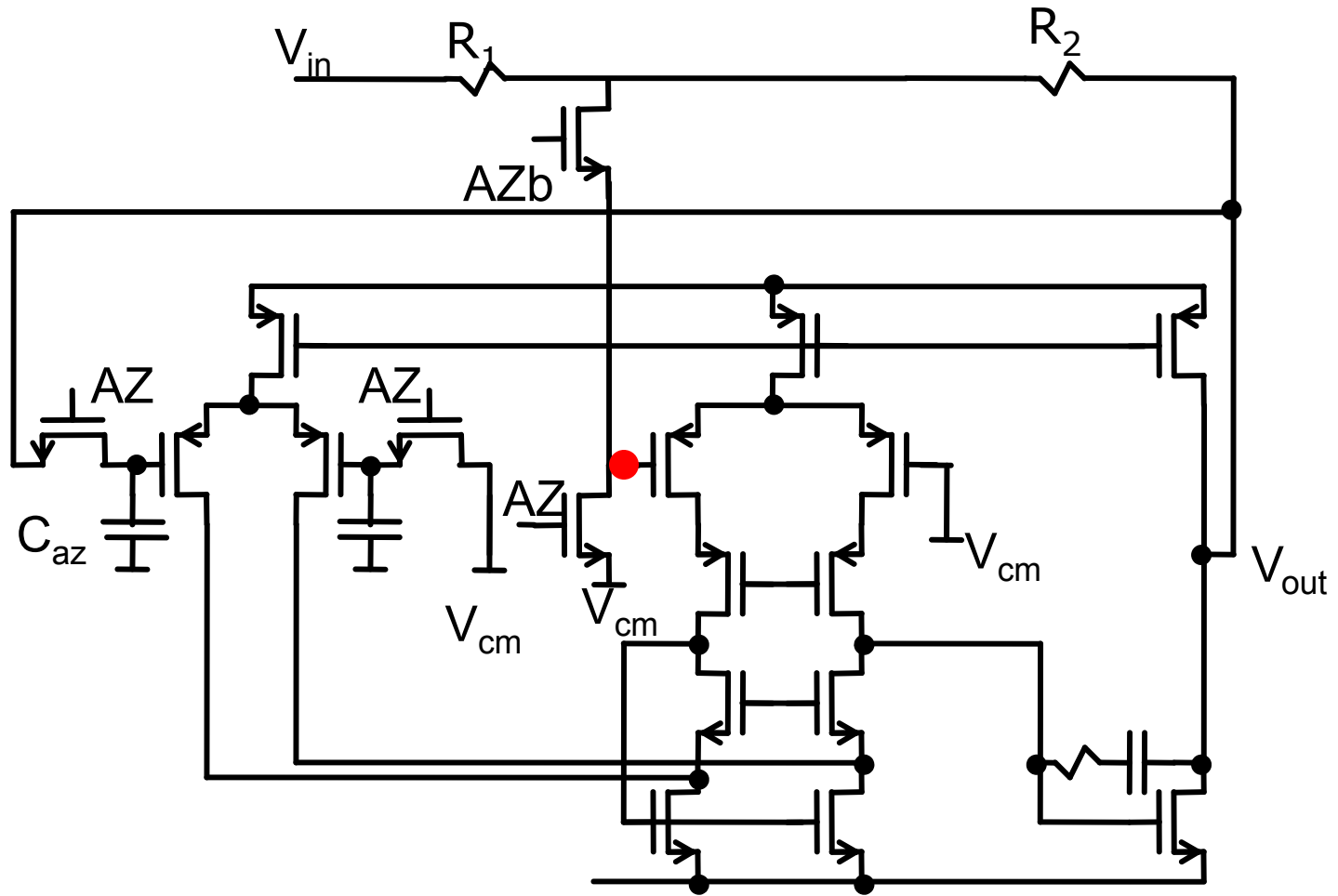


autozero phase

$$V_{az} = V_{os} * gm_{in} / gm_{az}$$

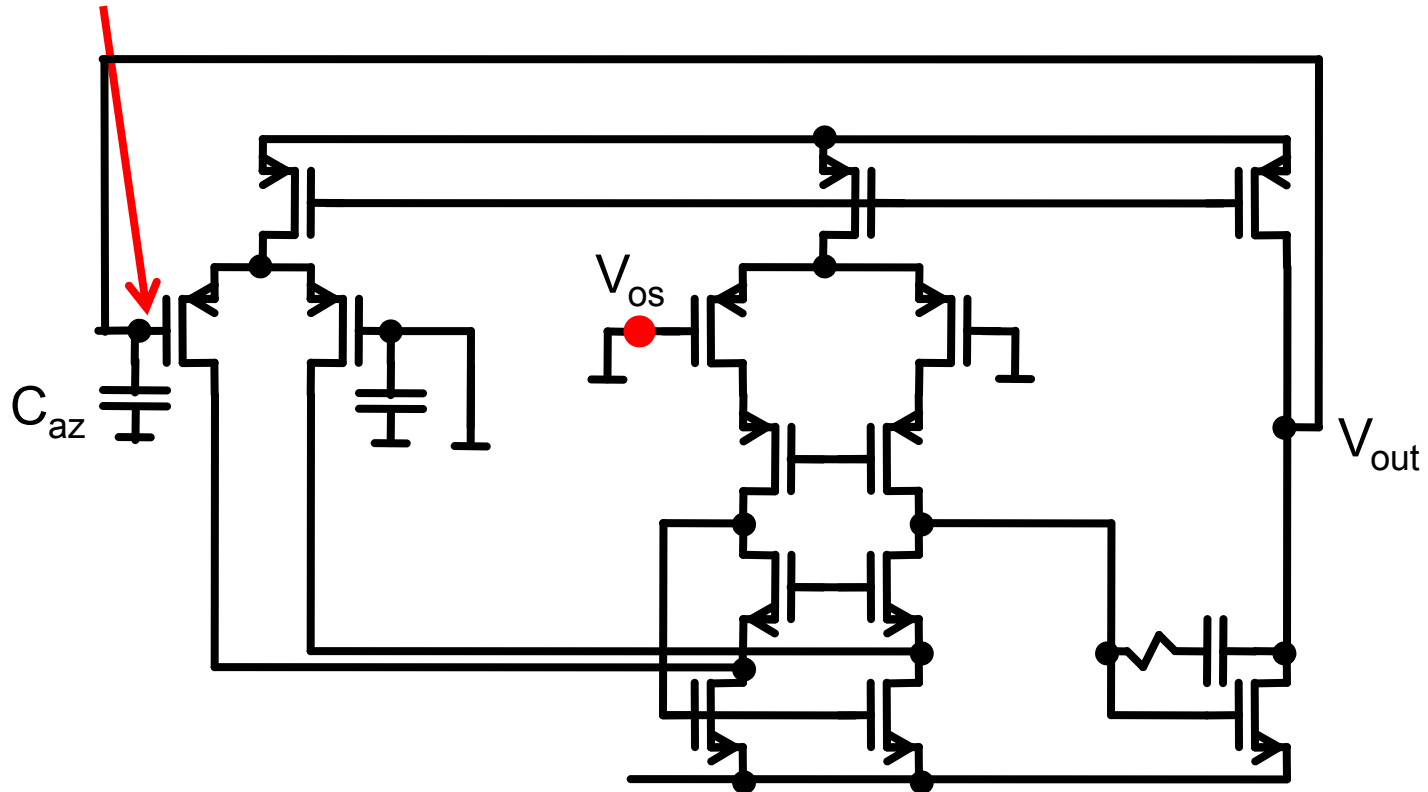


operation phase

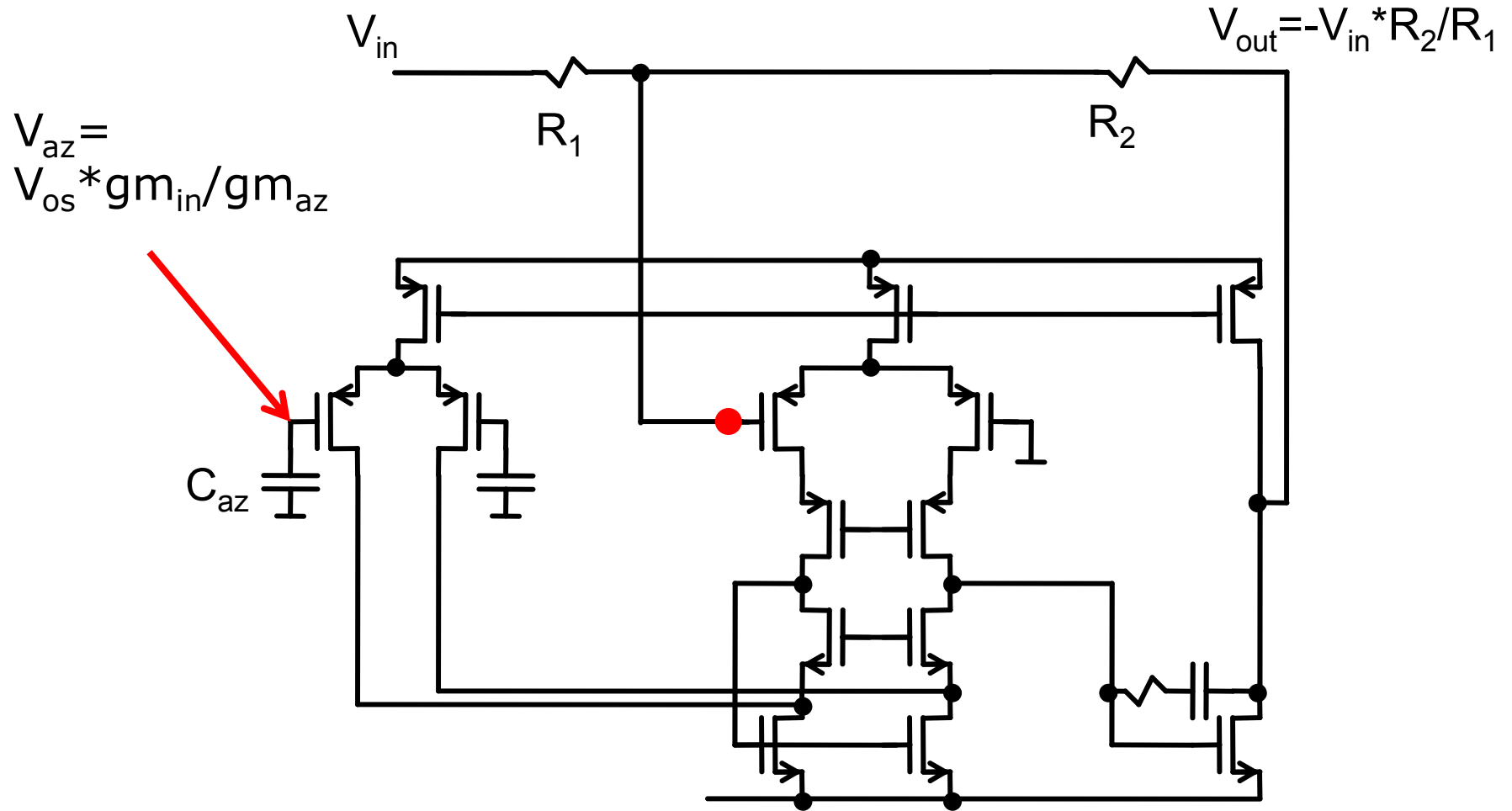

Waveforms


Autozero
nodes

 

input
nodes




output
node
and ideal

 

Error sources

- ❑ Noise penalty - Stored offset has noise, signal measurement has noise. Increases noise voltage by 3dB
- ❑ Autozero phase \neq Operating phase. Switches are in different positions, different currents flow, different glitches may be present. Careful design required.
- ❑ Storage error – digital storage is perfect, Analog storage has errors. Clock feedthrough, charge injection, leakage. Differential implementation helps a lot.


Charge Injection

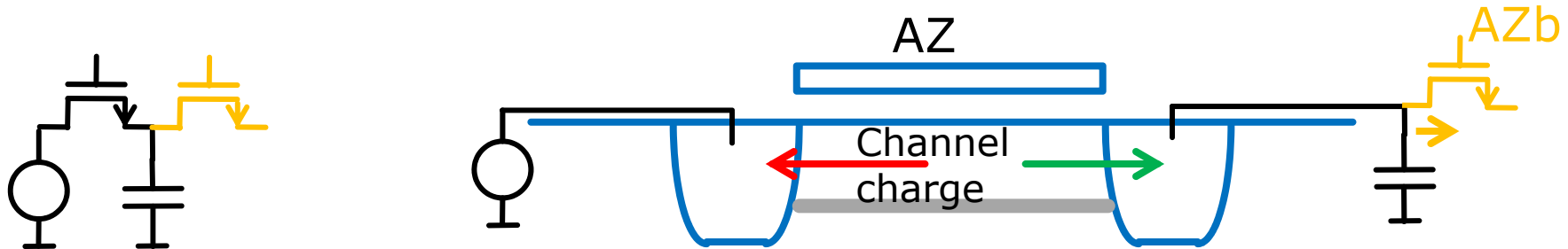

- ❑ Channel charge depends on the gate to channel voltage
- ❑ Charge distribution depends on the impedance seen
- ❑ Charge injection onto the cap can ruin the accuracy of the auto zero operation
- ❑ Differential operation recommended
- ❑ Cancellation techniques are known but are not very robust – see [orange transistor](#)

Eichenburger, Guggenbuhl, 1990

Charge Injection

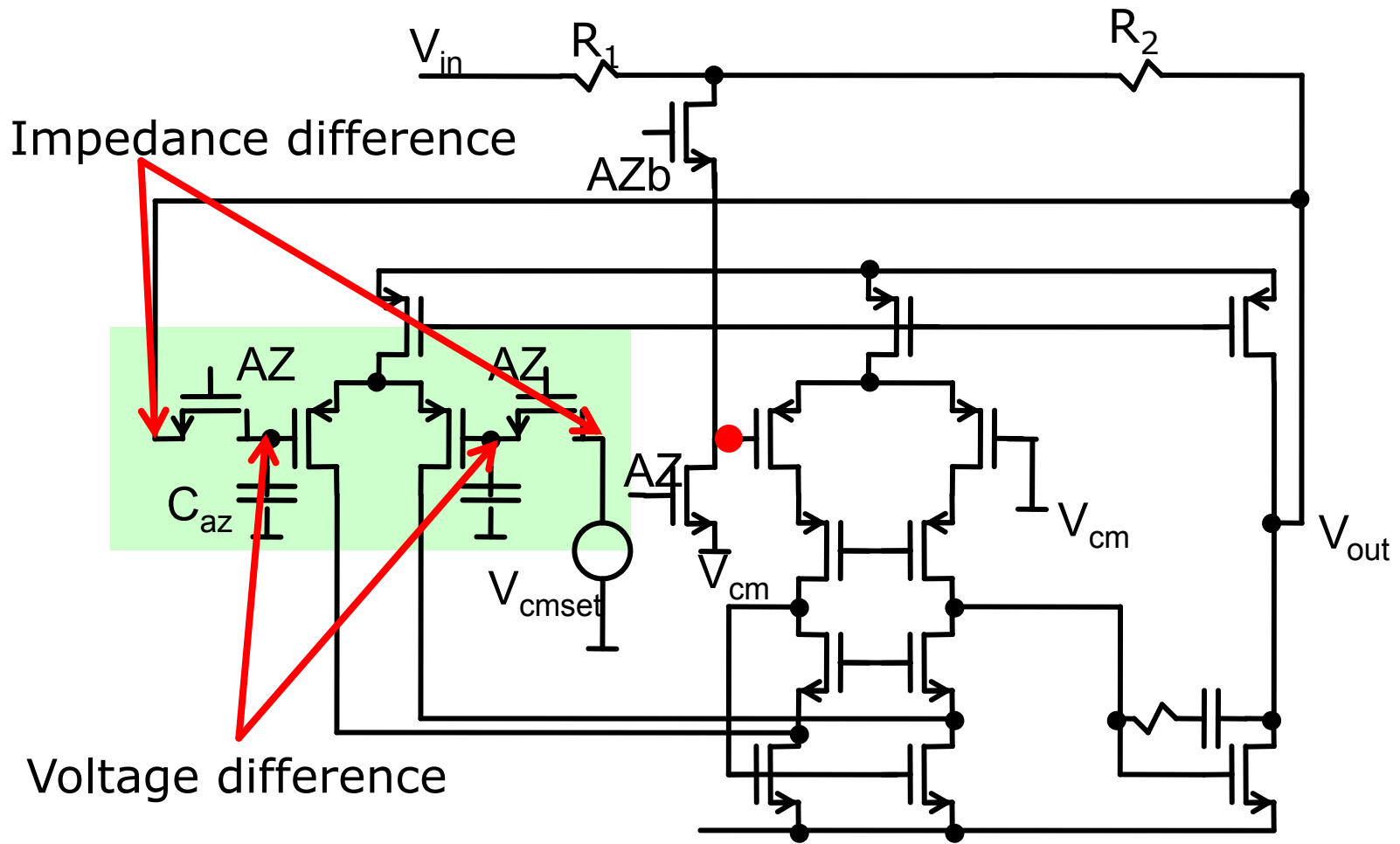


Noise analysis: PSS/PNOISE

- PSS settings
 - Fundamental frequency 500kHz (autozero clock)
 - Harmonics 10 (it pays to vary this, to find sensitivity)
 - Look at the noise spectrum that is sampled, this will indicate where the significant noise is
 - Shooting technique
- PNOISE settings
 - Fundamental frequency 500kHz (autozero clock)
 - Sidebands 10 (similar to harmonics)
 - Look at noise spectrum
 - Look at noise report
 - Integrated noise in the band of interest
 - See that noise contributors are those that you would expect!
- Input grounded, Noise observed at amplifier output

Results of PSS analysis

AZ off: noise corner 500kHz

List of noise contributors

 

Autozero disabled – flicker noise

Device	Param	Noise Contribution	% Of Total
/M186	fn	3.03006e-09	6.24
/M184	fn	2.95966e-09	6.10
/M193	fn	5.29306e-10	1.09
/M188	fn	5.1566e-10	1.06
/M180	fn	5.14673e-10	1.06
/M189	fn	2.72912e-10	0.56
/M191	fn	2.7031e-10	0.56
/M192	fn	2.46558e-10	0.51
/M187	fn	2.28352e-10	0.47
/M179	fn	6.82412e-11	0.14

Autozero enabled – thermal noise

Device	Param	Noise Contribution	% Of Total
/R50	rn	1.33245e-11	6.96
/M189	id	1.06653e-11	5.57
/M191	id	1.03514e-11	5.41
/M184	id	9.74716e-12	5.09
/M186	id	9.2109e-12	4.81
/M157	id	8.92213e-12	4.66
/M161	id	8.65251e-12	4.52
/M68	fn	8.24145e-12	4.31
/M156	id	8.19282e-12	4.28
/M154	id	7.67705e-12	4.01


AZ on: Elevated thermal noise

Autozero considerations

- Requires a reset phase – no processing of the signal part of the time
- Additional circuitry – noise penalty from extra diffpair, noise on cap
 - Minimize g_m of offset cancellation circuits to reduce its extra noise
- Sampling of offset can trap additional noise


Autozero considerations

 - ❑ Careful - Multistage amplifier will add extra noise to sampled offset
- ❑ Use NOISE, PSS and PNOISE analyses to understand the noise impact!




Reducing autozero noise

Case 1: sample offset, sample signal, subtract – noise penalty 3dB

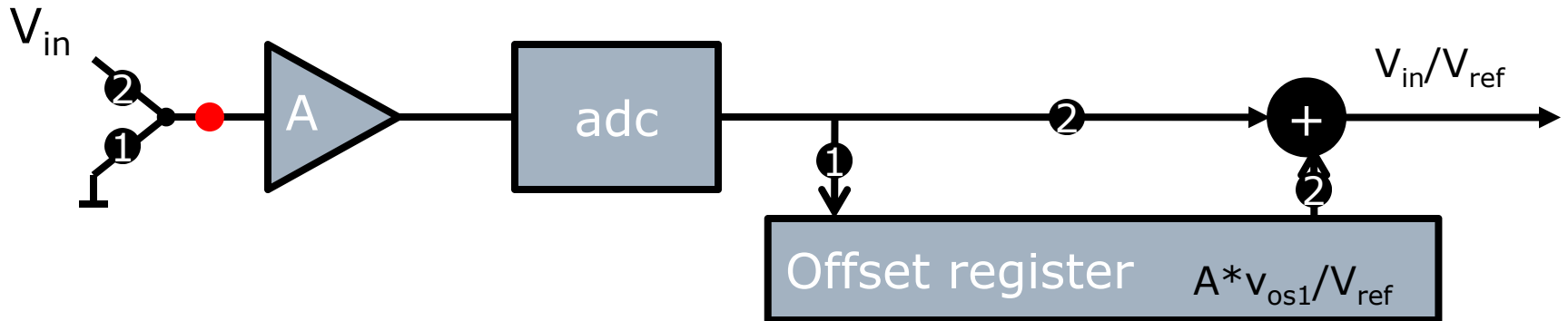


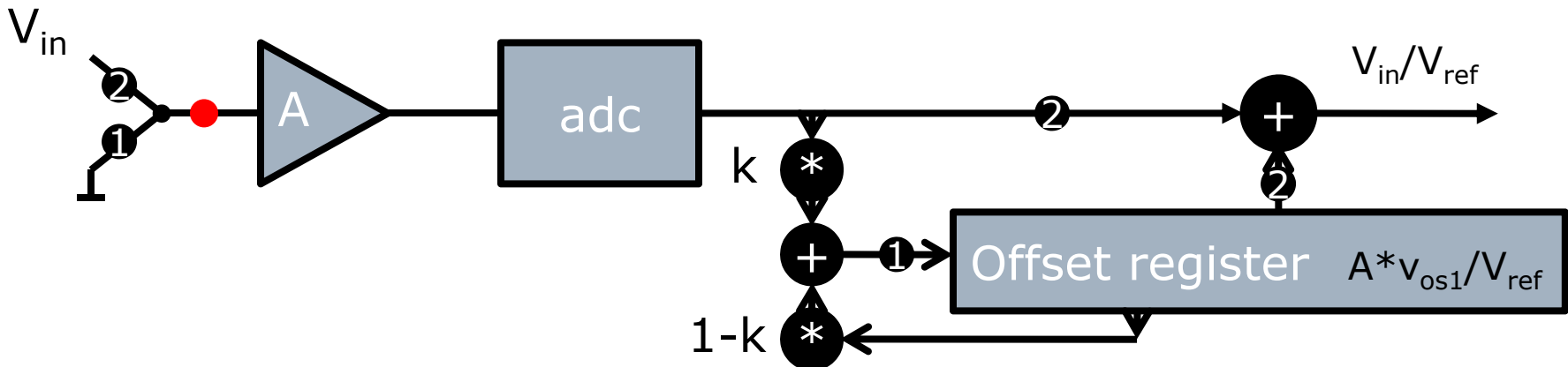Case 2: sample offset, integrate/average with previous samples sample signal, subtract – noise penalty reduced, bandwidth reduced




Analog implementation

 - Autozero phase: measure the offset and store it



 - Operation phase: amplify signal and subtract offset



$C_{az1} \gg C_{az2}$
 Implementing a
 low pass filter
 (leaky integrator)

Reduced bandwidth and noise

- Don't measure instantaneous offset, but average the most recent offset measurements.
- Reduces the cancellation bandwidth
- Reduces the noise – can make it a much less significant noise source
 - No averaging 3dB noise penalty
 - 4 times averaging, 1dB noise penalty
 - 32 times averaging 0.1dB noise penalty
 - ...unless we are starting to lose flicker noise cancellation.


Waveforms

Az nodes


Output first stage

Output second stage

summing node

 


AZ in a continuous time opamp 2

 

- Autozero 'reset time limitation' overcome by sample and hold of auto-zero voltage
- Phase 1 samples offset of A2 on C_{az2}
- Phase 2 refreshes A1 offset stored on C_{az1}

Performance data AZ-opamp

 - ADI AD8628
- Offset $< 1\mu\text{V}$
- Offset drift $2\text{nV}/\text{C}$
- Noise floor $22\text{nV}/\sqrt{\text{Hz}}$



Autozero summary

- ❑ Sampled system
- ❑ Sampling has noise and aliasing issues
- ❑ Devices are taken 'offline' to calibrate – amplifier is not continuously available
- ❑ Storage of offset required
- ❑ Storage is perfect in digital
- ❑ Analog storage is imperfect. Charge injection is the biggest issue, modern processes also present leakage challenges


Outline

- Motivation and history
 - Offset and flicker noise background
 - Techniques to manage offset and flicker noise
 - Chopper Stabilization
 - Basic idea
 - Switched capacitor and continuous time implementations
 - Chop artifacts and their removal
 - Second order effects
 - Autozero
 - Basic idea
 - Implementation examples
 - Second order effects
 - Correlated double sampling
 - An extension of Autozero into switched capacitor circuits
 - Conclusion
-



Correlated Double Sampling

- Switched capacitor Sampling systems
- Extension of Autozero technique into the world of switched capacitors
- Capacitors are already present, introduce switch phasing to take advantage and store offset voltage
- Take advantage of finite gain error storage

Offset compensated SC amplifier

 

  
- Phase 1 similar to autozero – stores offset on the caps
- C_1 and C_2 serve both as offset storage and gain elements
- Inverting input always sits at V_{os}




Gregorian, 1981

Waveforms


Summing node

 


Opamp output

 



Input node

 

CDS for gain error correction

 

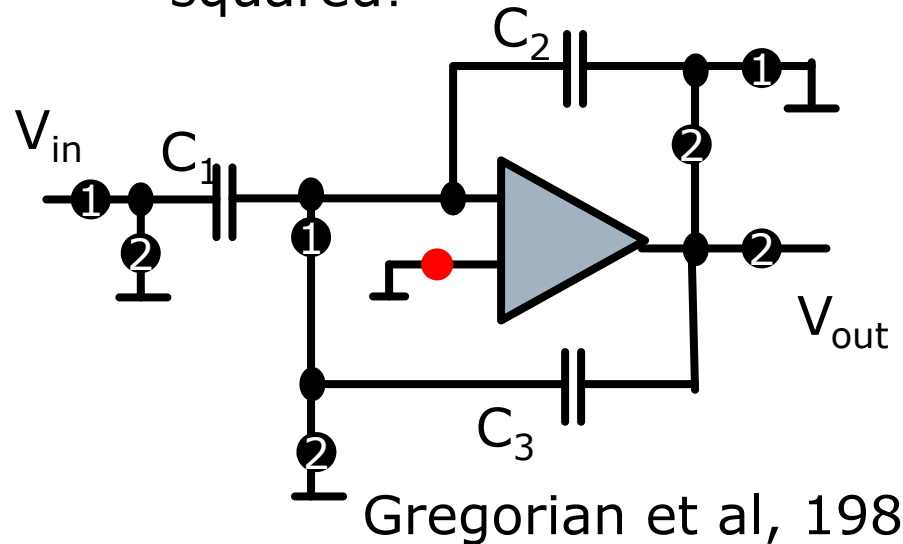 - The addition of capacitor C_3 keeps the output of the opamp at $V_{out_old} + V_A$
- $V_A = V_{os} + V_{out_old}/A$ where A is the gain of the opamp
- Acts like we have gain squared!



Gregorian et al, 1984

Error sources in CDS

- Charge injection – fully differential implementations are preferred
- Sometimes a noise penalty – little noise penalty in first example, noise penalty for storing charge on C3
- Ability to take out gain error related problems if V_{out} does not change much from cycle to cycle.

CDS summary

- Look for opportunities to store offset on exiting capacitors in switched capacitor circuits
- Taking the Autozero idea and applying it in circuits that already have capacitive charge transfer.
- Ability to store and subtract gain error related offset voltage can be added – very attractive in modern technologies where gain is hard to come by.

Comparison

Chopper Stabilization	Autozero	Correlated double sampling
Modulation, no sampling	Sampled system	Sampled system
No noise penalty, best noise performance	Increased noise	Increased noise
Output cannot be sampled easily		Also compensates for gain error
Accuracy limited by transients, best offset	Accuracy limited by sampling process	Accuracy limited by sampling process
Recommended for continuous time applications	Applicable in many discrete time systems	Suitable for switched capacitor systems

Conclusion

- Good low frequency and DC performance has a lot of value in applications such as sensor interfaces
- Although MOS devices have poor matching and flicker noise, several techniques are available to improve this performance
- Noise, power, and area penalties are manageable
- Modern simulation tools can fully support this
- The resulting noise and offset performance can be world class

Papers to see

- 21.8 KU Leuven Chopping and dynamic element matching for low offset and high gain accuracy
- 21.9 TU Delft chopper amplifier across isolation barrier
- 21.10 Analog Devices chopper amplifier across isolation barrier

References

- www.hparchives.com HP 150-1800
- Ti.com OP627
- Microchip.com MCP5241
- Cirrus.com CS3001
- Analog.com AD8628
- C. C. Enz, G. C. Temes, Circuit techniques for reducing the effects of op-amp imperfections: autozeroing, correlated double sampling, and chopper stabilization, Proceedings of the IEEE, 1996, Volume 84, Issue 11, pp.1584-1614
- D. Johns, K. Martin, Analog Integrated Circuit Design, Wiley, 1997. Chapter 4 Noise Analysis
- Allen, Holberg, CMOS Analog Circuit Design, Oxford, 1989
- R. Gregorian, "High Resolution Switched capacitor D/A converter, Microelectron. J.no 12, pp. 10-13, 1981
- K. Haug, G.C. Temes, K. Martin, Improved Offset Compensation Schemes for switched capacitor circuits, Proc IEEE Int Symp Circ Syst, 1984, pp. 1054-1057
- C. Eichenburger, W. Guggenbuhl, On charge injection in analog MOS switches and dummy switch compensation techniques, IEEE Trans. on Circuits & Systems, vol. 37, no. 2, Feb. 1990, p. 256-264.
- M. J. M. Pelgrom, A.C. J. Duinmaijer, A. P. G. Welbers, Matching Properties of MOS Transistors, IEEE JSSC, vol. 24, no. 5, Oct. 1989, pp. 1433-1439
- Simulating Switched-Capacitor Filters with SpectreRF Application Note, Verison 5.0, June 2003, http://www.cdnusers.org/community/virtuoso/resources/spectreRF_scfiltersAN.pdf

References

- A. Bilotti, G. Monreal, Chopper-stabilized amplifiers with a track-and-hold signal demodulator, IEEE Trans. On Circuits & Systems-I, vol. 46, April 1999, p. 490-495.
- A. Thomsen, DC measurement IC with 130nVpp noise in 10Hz, Digest of ISSCC 2000, pp.334-335.
- K.A.A. Makinwa, J.H.Huijsing, A smart CMOS wind sensor,"Digest of ISSCC 2002, pp.432-433.
- A. Bakker, J.H.Huijsing, Low-offset, low-noise 3.5mW CMOS spinning-current Hall-effect sensor with integrated chopper amplifier, Proc. of Eurosensors XIII, Sept 1999, pp.1045-1048.
- C. Hagleitner et al., N-well based CMOS calorimetric sensors, Proc. of MEMS 2000, pp. 96-101.
- C.C. Enz et al., A CMOS chopper amplifier, IEEE JSSC, vol.22, pp.335-342, June 1987.
- C. Menolfi, Q.Huang, A fully integrated CMOS instrumentation amplifier with submicrovolt offset," IEEE JSSC, vol. 34, March 1999, pp.415-420.
- A. Bakker et al., A CMOS nested chopper instrumentation amplifier with 100nV offset, IEEE JSSC, vol. 35, no. 12, 2000, pp. 1877 -1883.
- C. Menolfi, Q. Huang, "A low-noise CMOS instrumentation amplifier for thermoelectric infrared detectors," IEEE JSSC, vol. 32, no. 7, July 1997, pp.968 -976.
- A. Bakker, "High-accuracy CMOS smart temperature sensors," Kluwer Academic Publishers, Boston, 2000.
- C. Menolfi, Q.Huang, "A 200nV 6.5 nV/ $\sqrt{\text{Hz}}$ noise PSD 5.6kHz chopper instrumentation amplifier," Digest of ISSCC 2001, pp. 362-363.
- R. Burt, J. Zhang, A Micropower Chopper-Stabilized Operational Amplifier using a SC Notch Filter with Synchronous Integration inside the Continuous-Time Signal Path, ISSCC 2006, paper 19.6, pp

References

- A Chopper Current-Feedback Instrumentation Amplifier with a 1mHz 1/f Noise Corner and an AC-Coupled Ripple Reduction Loop R. Wu, K. A. A. Makinwa, J. H. Huijsing, ISSCC2009 paper 19.1 .
- A 140dB-CMRR Current-Feedback Instrumentation Amplifier Employing Ping-Pong Auto-Zeroing and Chopping M. A. Pertijs, W. J. Kindt, ISSCC2009 paper 19.2
- A 1.05V 1.6mW 0.45°C 3 σ -Resolution $\Delta\Sigma$ -Based Temperature Sensor with Parasitic-Resistance Compensation in 32nm CMOS Y. Li, H. Lakdawala, A. Raychowdhury, G. Taylor, K. Soumyanath, ISSCC, 2009 paper 20.1
- A Micropower Chopper-Correlated Double-Sampling Amplifier with 2 μ V Standard Deviation Offset and 37nV/ $\sqrt{\text{Hz}}$ Input Noise Density M. Belloni¹, E. Bonizzoni, A. Fornasari, F. Maloberti, ISSCC 2010, paper 4.2
- 4.4 A 21nV/ $\sqrt{\text{Hz}}$ Chopper-Stabilized Multipath Current-Feedback Instrumentation Amplifier with 2 μ V Offset Q. Fan, J. H. Huijsing, K. A. Makinwa, ISSCC 2010, paper 4.4
- A 5.9nV/ $\sqrt{\text{Hz}}$ chopper operational amplifier with 0.78 μ V maximum offset and 28.3nV/ $^{\circ}\text{C}$ offset drift, Y. Kusuda, ISSCC 2011 paper 13.4
- A current-Feedback instrumentation amplifier with a Gain error Reduction loop and 0.06% untrimmed Gain error R. Wu, J. H. Huijsing, K. A. Makinwa Delft University of Technology, Delft, The Netherlands ISSCC 20011 paper 13.5
- 13.6 a 6.7nv/ $\sqrt{\text{hz}}$ Sub-mhz-1/f-corner 14b analog-to-digital interface for Rail-to-Rail precision voltage Sensing C. D. Ezekwe, J. P. Vanderhaegen, X. Xing, G. K. Balachandran, ISSCC 2011 paper 13.6
- A Current-Feedback Instrumentation Amplifier with 5 μ V Offset for Bidirectional High-Side Current-Sensing J. Witte, J. Huijsing, K. Makinwa, ISSCC 2008, paper 3.5