

Simulation Techniques in Data Converter Design


Shanthi Pavan

Indian Institute of Technology, Madras


Outline

- Overview of selected Nyquist ADCs
- Creating and interpreting ADC spectra
- Oversampling ADCs
 - Simulation techniques
 - Use of RF analyses in oversampling converter designs
- Concluding Remarks
- References

Data Conversion in our World

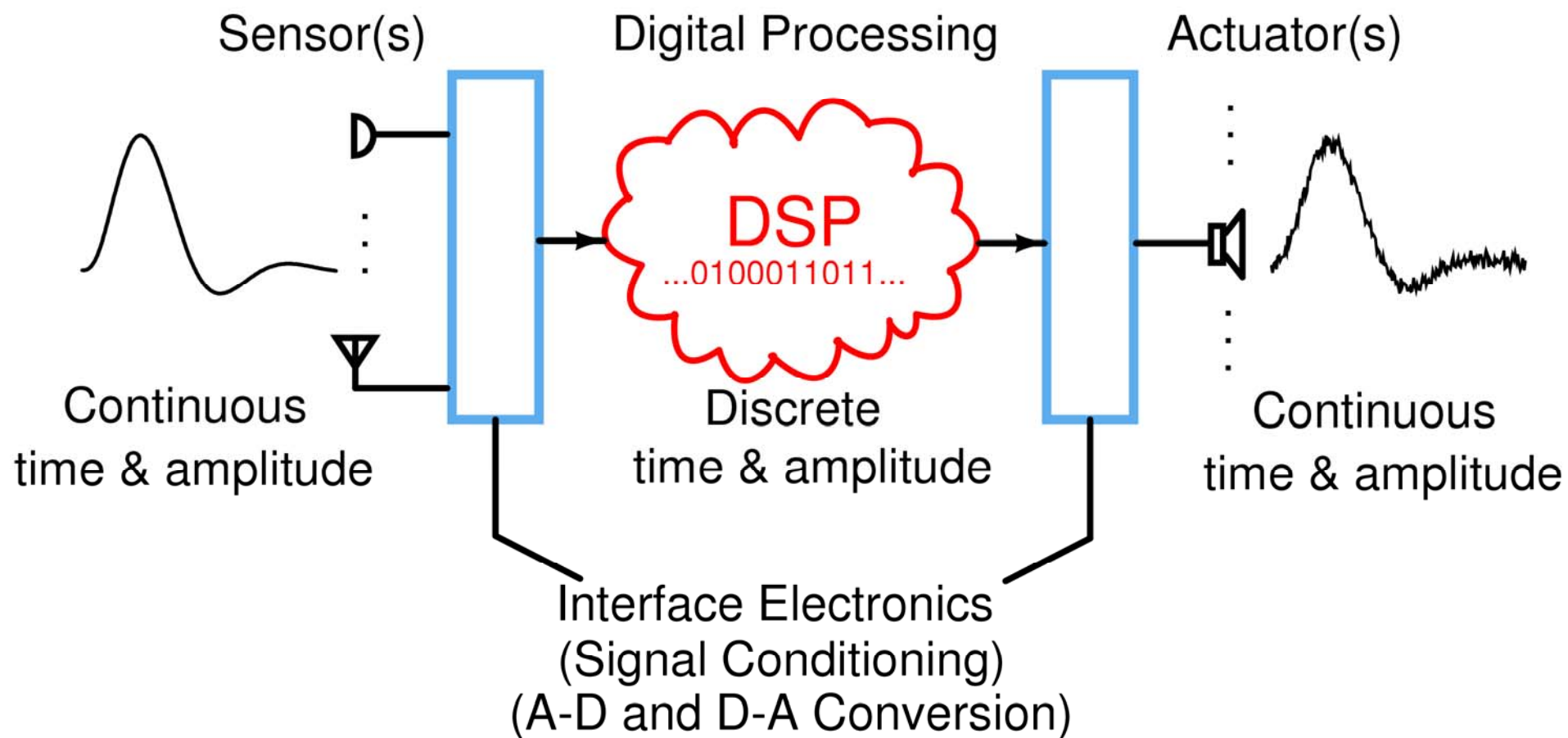

The A/D Conversion Process

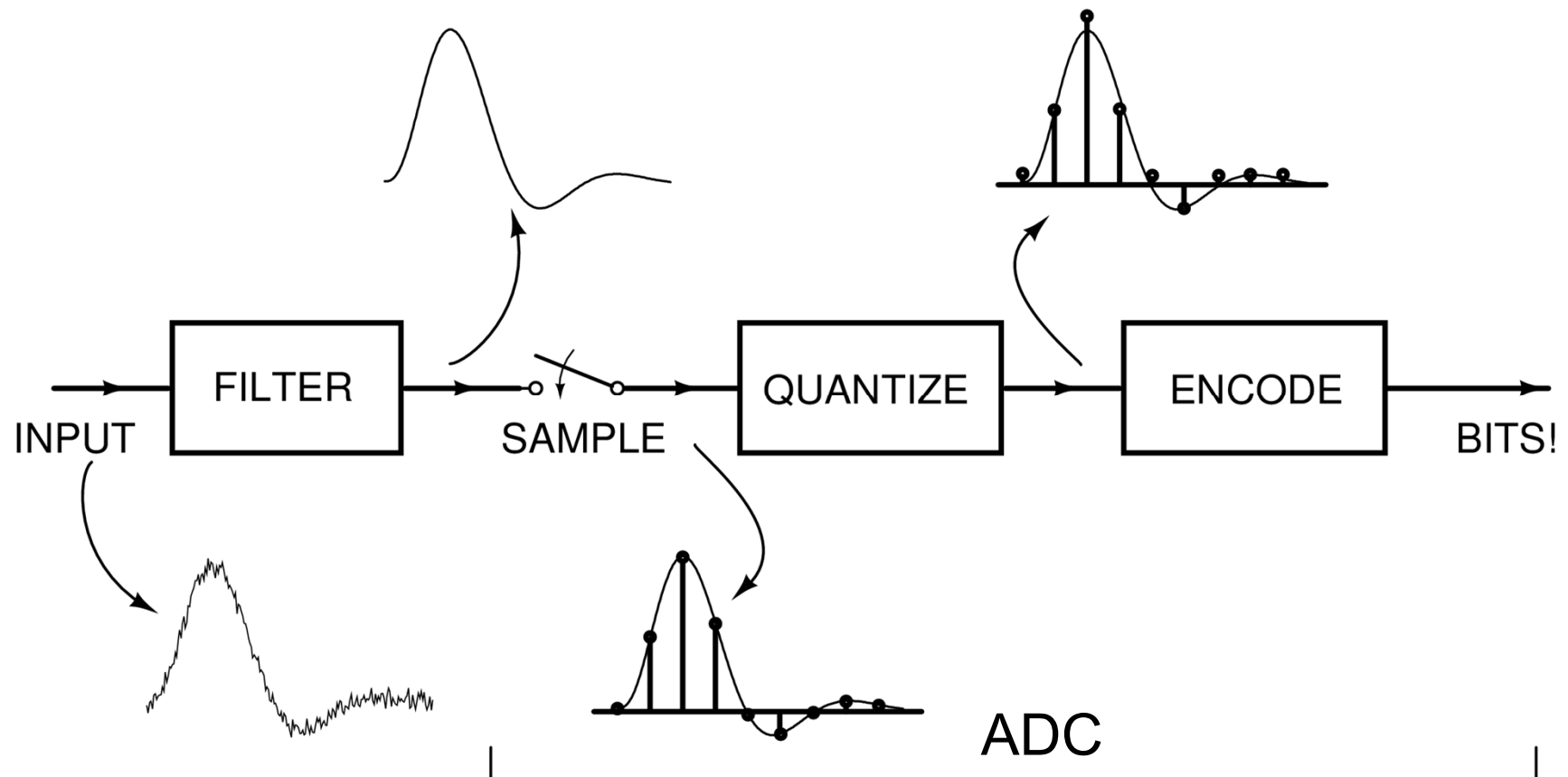

Simulation Strategies

- ADCs and DACs are complex mixed signal systems
- Can be simulated at several levels
 - ADC Functional Behavior
 - Models at the block level
 - Models at the circuit level
 - Mix and match

Simulation Strategies

- Functional behavior
 - Full chip or SoC functionality simulation
 - Second order effects not important/needed
- Block level models
 - Architectural exploration
 - What-if scenarios
 - Rapid estimates of mismatch effects
- Mix and match
 - Behavioral + transistor level
 - Helps isolate problems during debug

Simulation Strategies

- Functional behavior
 - Full chip or SoC functionality simulation
 - Second order effects not important/needed
- Behavioral
 - Always run the full layout extracted design at the transistor level –
 - What you did not model bites you most of the time
 - Rapid estimates of mismatch effects
- Mix and match
 - Behavioral + transistor level
 - Helps isolate problems during debug



ADC Architectures

- Nyquist Rate
 - Flash
 - Folding
 - Two step
 - Pipeline and Algorithmic
 - Successive Approximation (SAR)
- Oversampling ($\Sigma\Delta$) ADCs
 - Discrete-time $\Sigma\Delta$
 - Continuous-time $\Sigma\Delta$

DAC Architectures

- Nyquist Rate
 - Current Steering
 - Resistor String
 - Algorithmic
- Oversampling ($\Sigma\Delta$) DACs
- Not covered in this tutorial

ADC Operations : Sampling

  


Quantizer Basics


$$v_{out} = v_{in} + q_e$$

Assumptions

 uniform in $\left[-\frac{\Delta}{2}, \frac{\Delta}{2}\right]$
 uncorrelated with v_{in}
 spectrally white




Offset Error

 


Benign when relative accuracy is desired
- Cancelled digitally

Gain Error

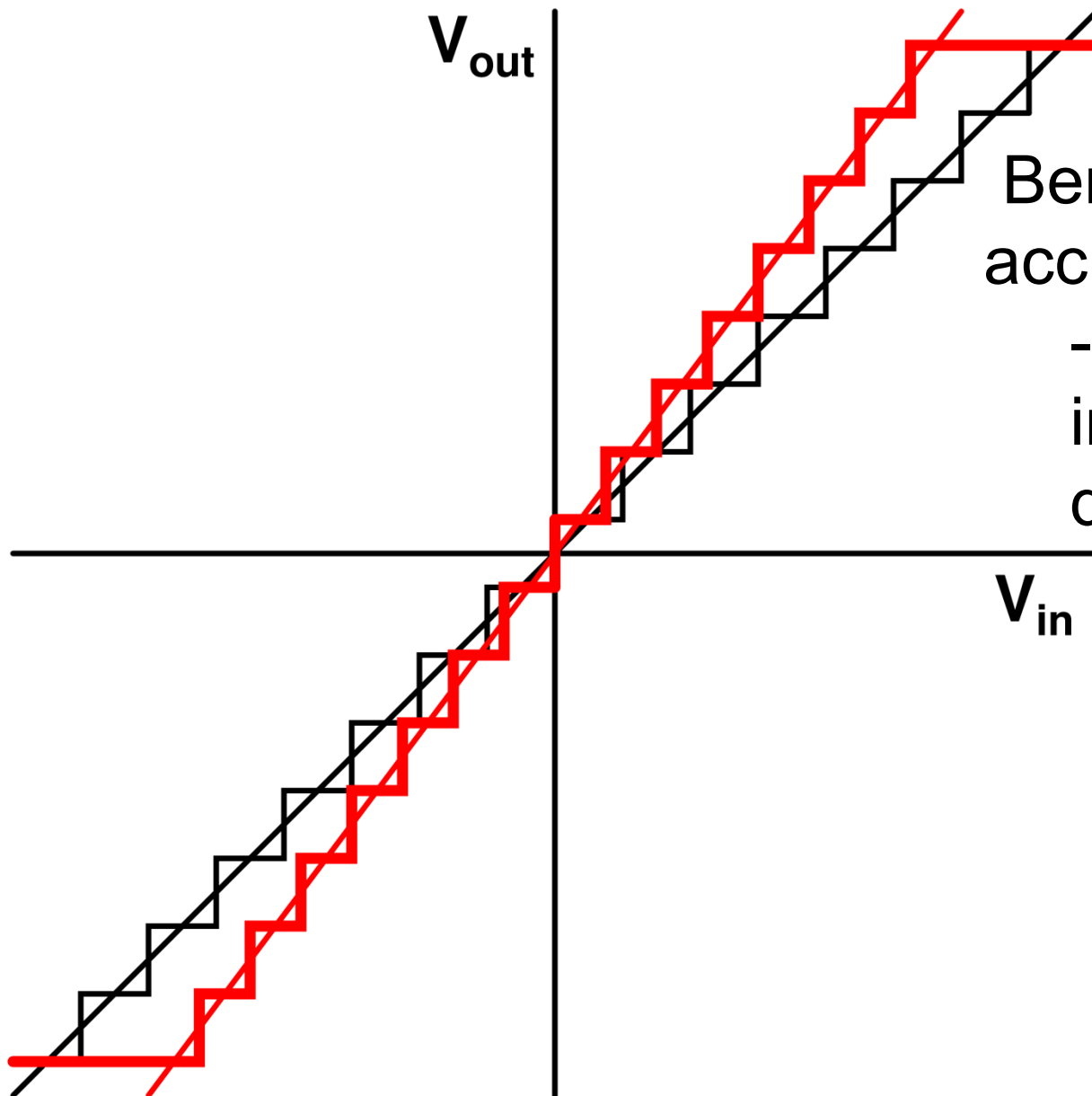

Benign when relative accuracy is desired
- Correct using AGC in the analog/digital domains

Differential Nonlinearity (DNL)

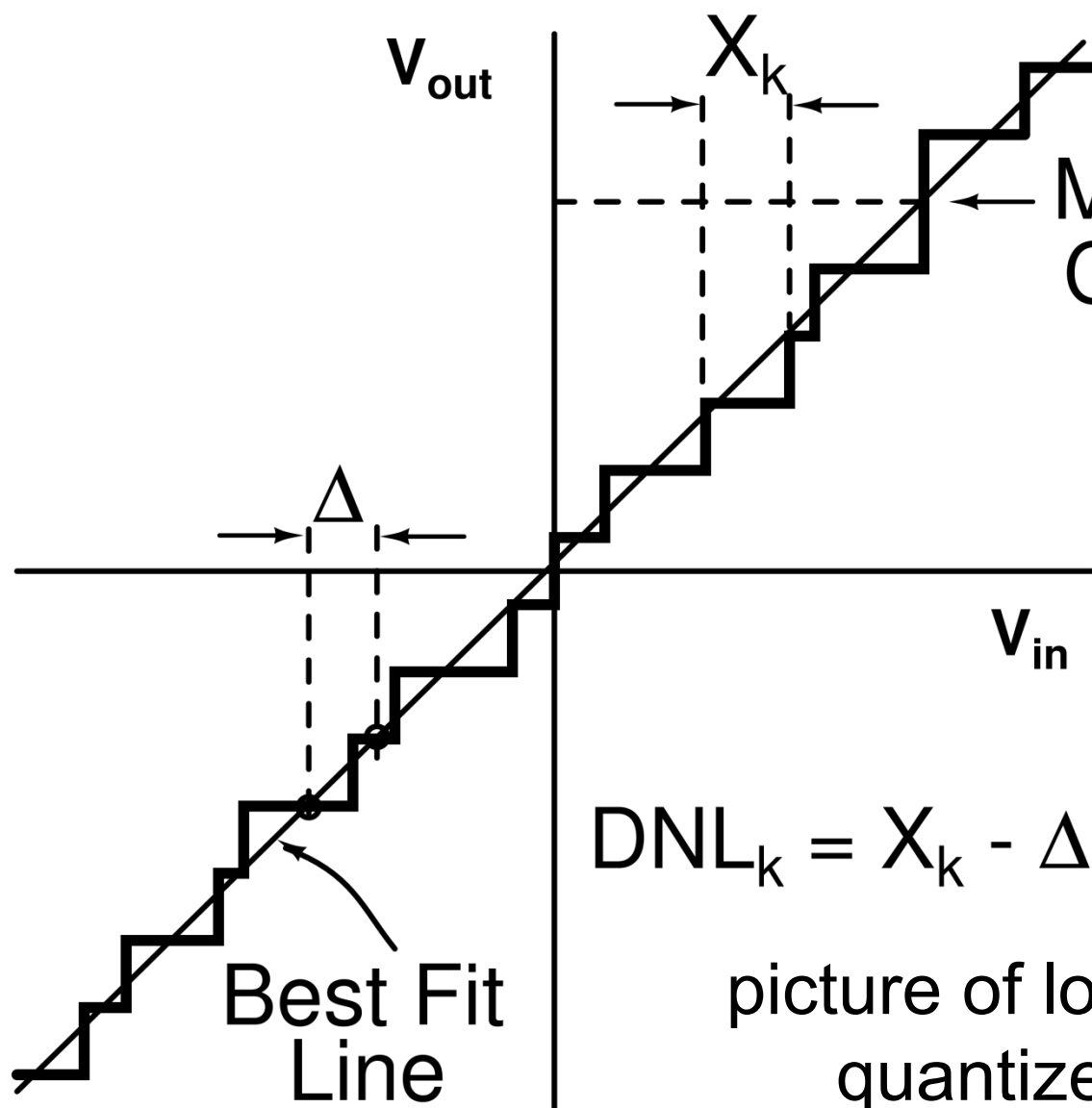


Nonmonotonicity
& missing codes

Monotonic if
 $|DNL| < \Delta$

picture of local variations in
quantizer thresholds

Integral Nonlinearity (INL)

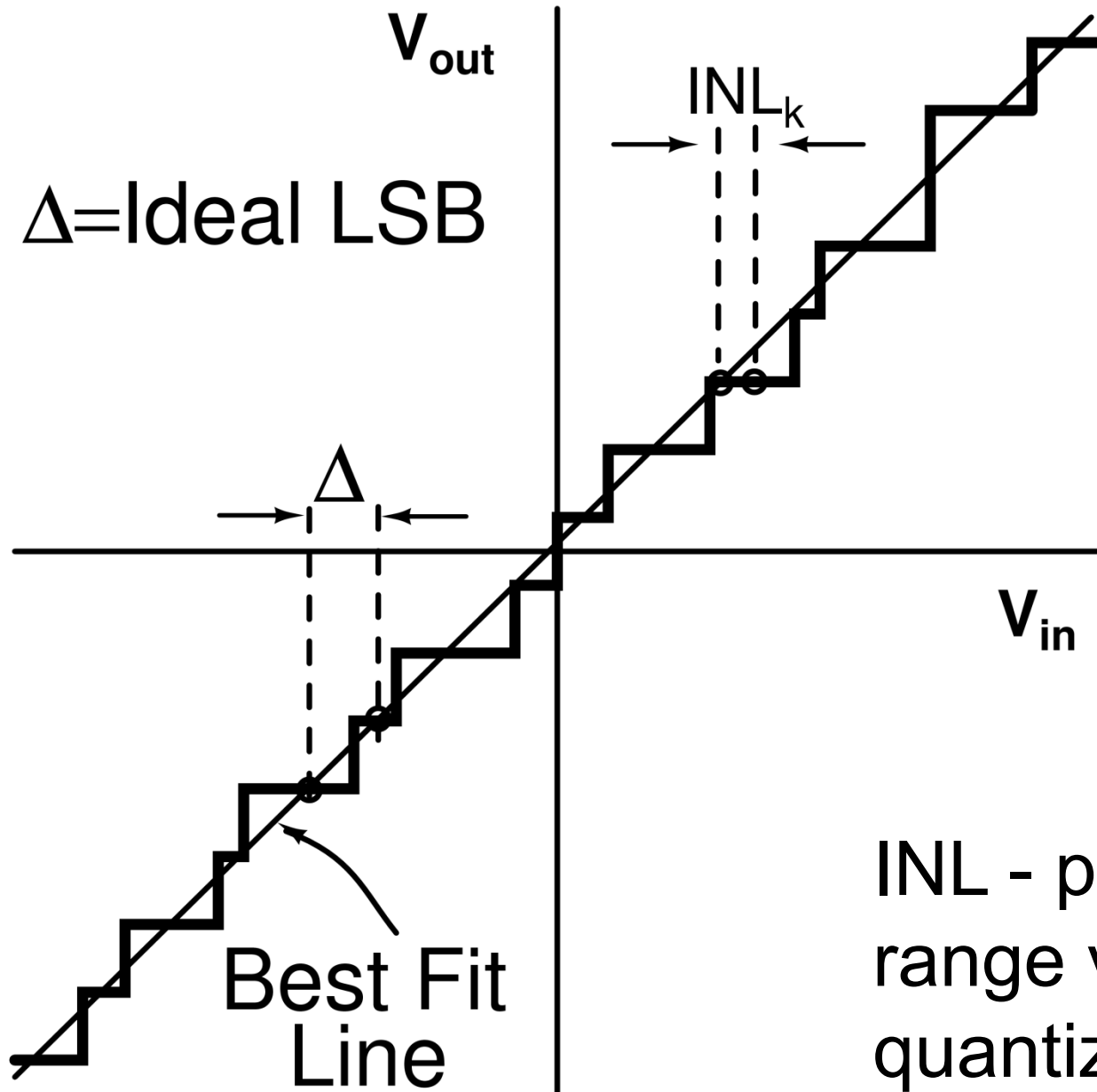


INL - picture of long range variations in quantizer thresholds

Dynamic Performance Metrics

- Peak Signal to Noise Ratio (SNR) of an ideal quantizer
 - $-(6N + 1.76)$ dB for a full scale sine wave
 - $1/2$ the step size means $1/4$ the noise power
- Signal to Noise + Distortion Ratio (SNDR)
 - Signal to everything else
- Effective Number of Bits (ENOB)


$$\text{ENOB} = \frac{\text{SNDR} - 1.76}{6.02}$$

Spurious Free Dynamic Range

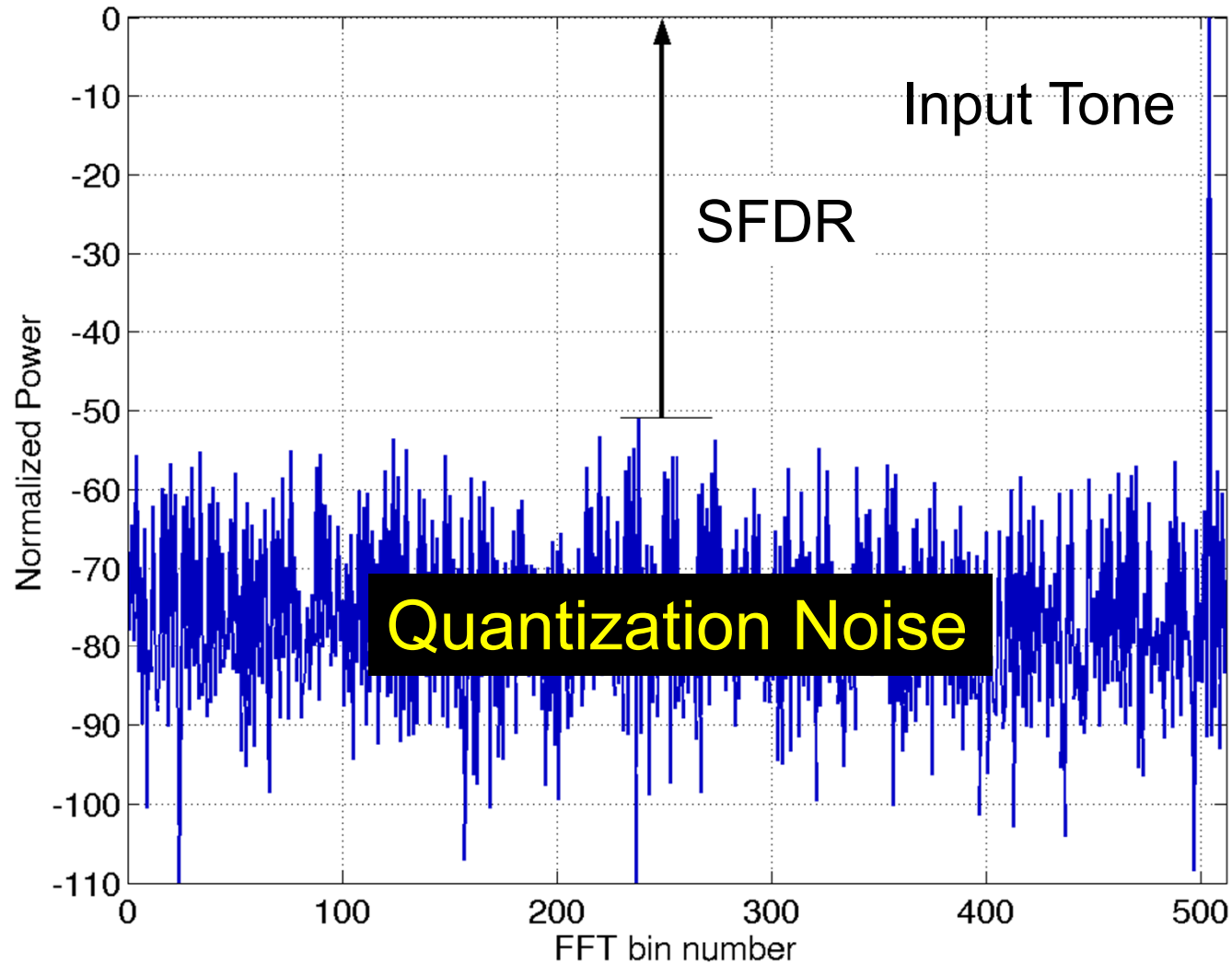


Flash A/D Conversion

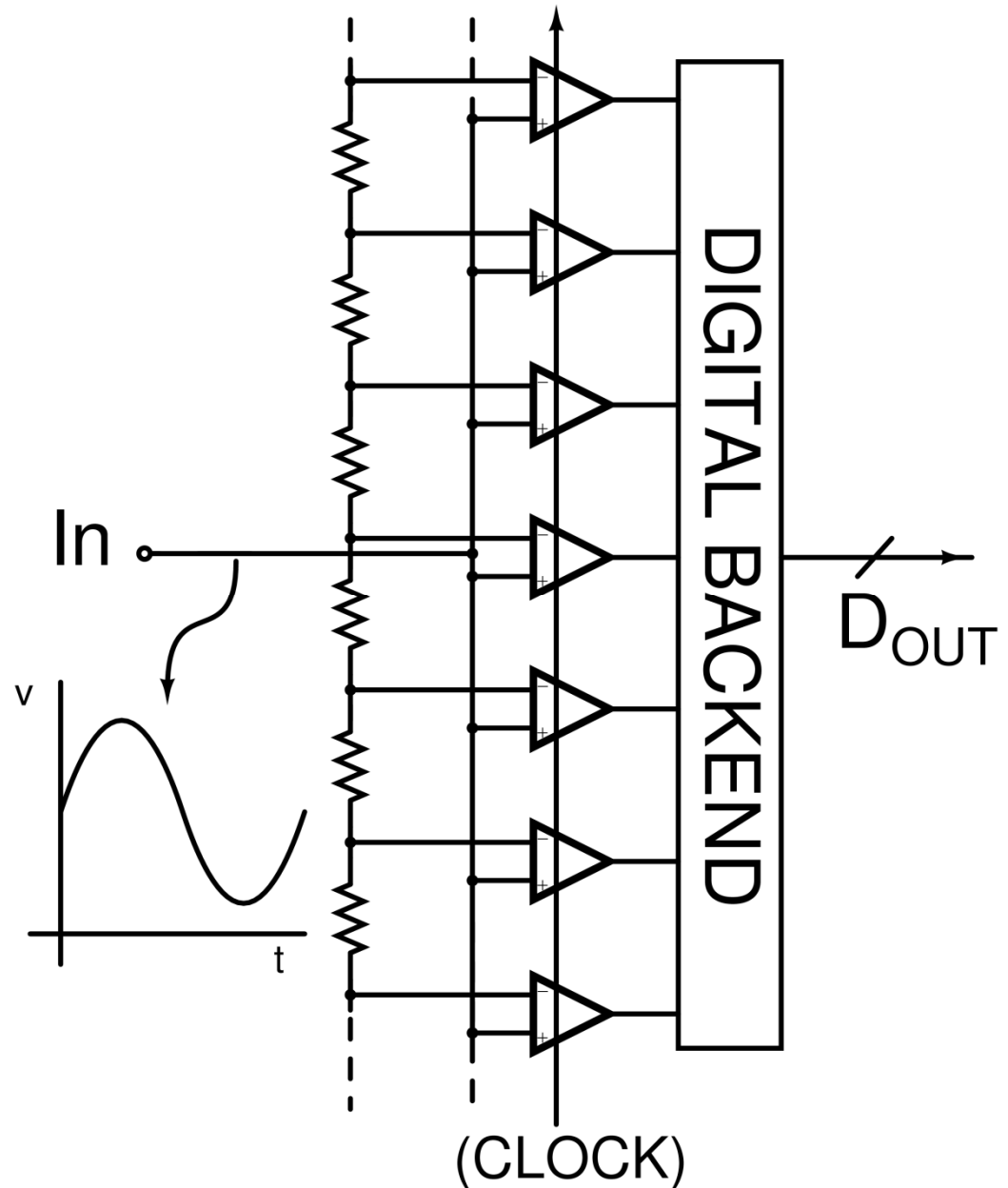- (+) Parallel technique
→ Low latency
- (+) References
– resistor ladder
- (-) Complexity - $O(2^N)$
- (-) Excessive power
and area for $N > 6$





Flash ADCs : Clock skew

 


Practical Flash ADC

 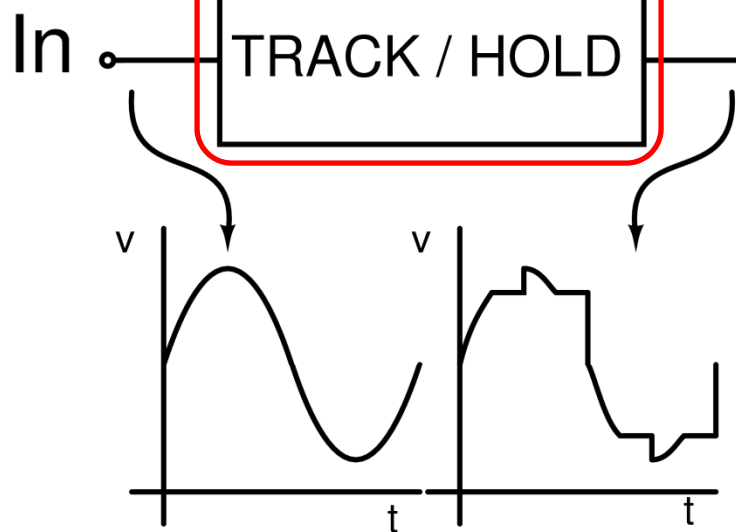Good dynamic performance & benign input impedance



Backend Logic

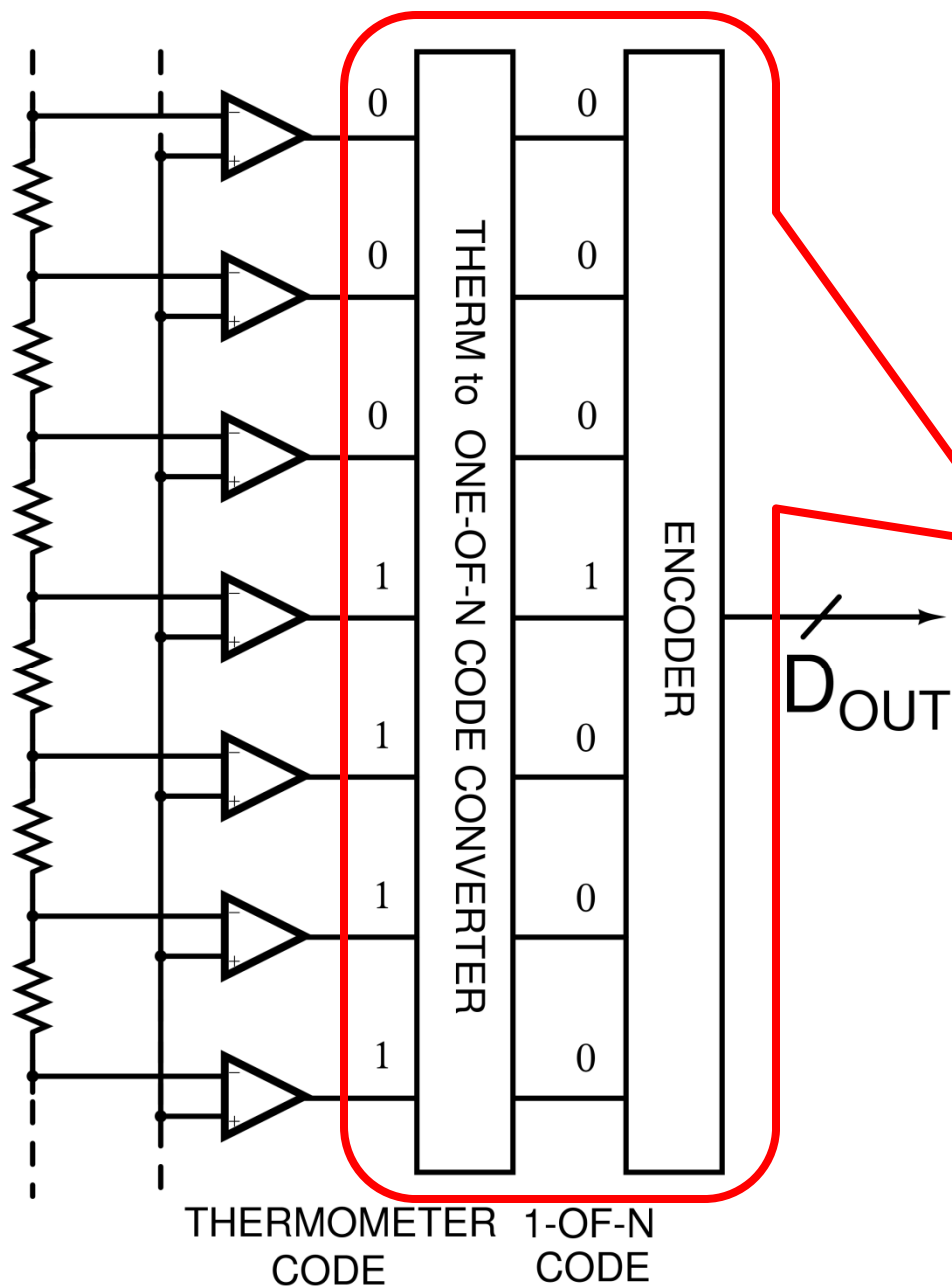


Ideal candidates for abstraction during the design phase

“Flash ADC Family” Design Steps

- Comparator design
 - Should have sufficiently low static and dynamic offset
 - Must regenerate sufficiently fast
- Track and Hold design
 - Tricky and depends on comparator architecture
- Back end logic


Flash ADC Simulations

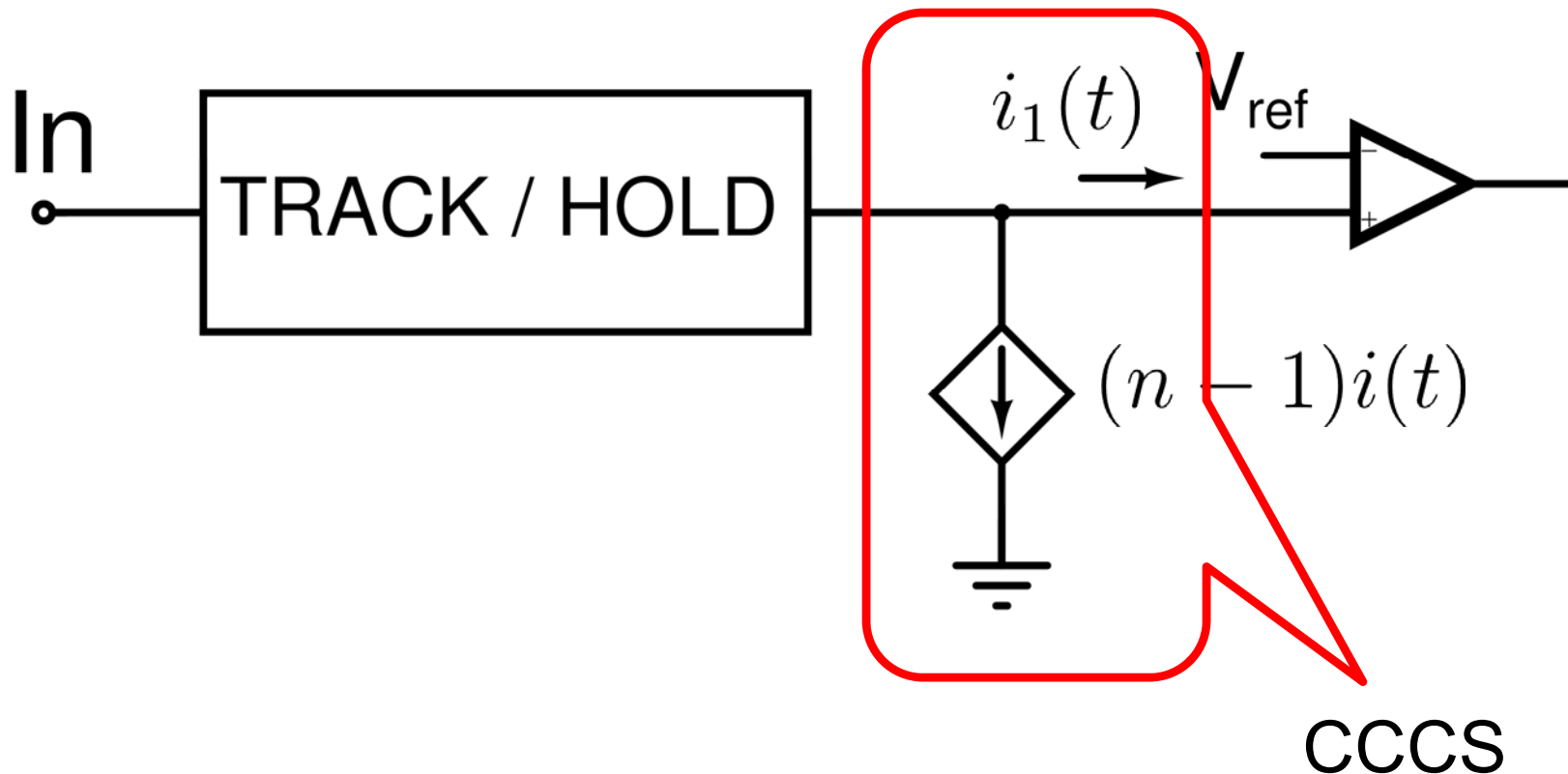

- **CCCS** emulates the load of n comparators
 - with only one comparator instantiation
- Convenient during design iteration

Flash ADC Simulations

 Drives comparator array
 Simulating T/H with
 all comparators @ device level
 → time consuming




Back end logic
 → behavioral

Two Step Flash ADC

- Motivation:
 - Reduce number of comparators in a flash ADC
- Idea:
 - In a flash ADC, only comparators “near” the input give useful information
 - Use a coarse ADC to estimate where the signal is, then use a fine ADC placed “around” the coarse estimate for better accuracy

Two Step Flash ADC

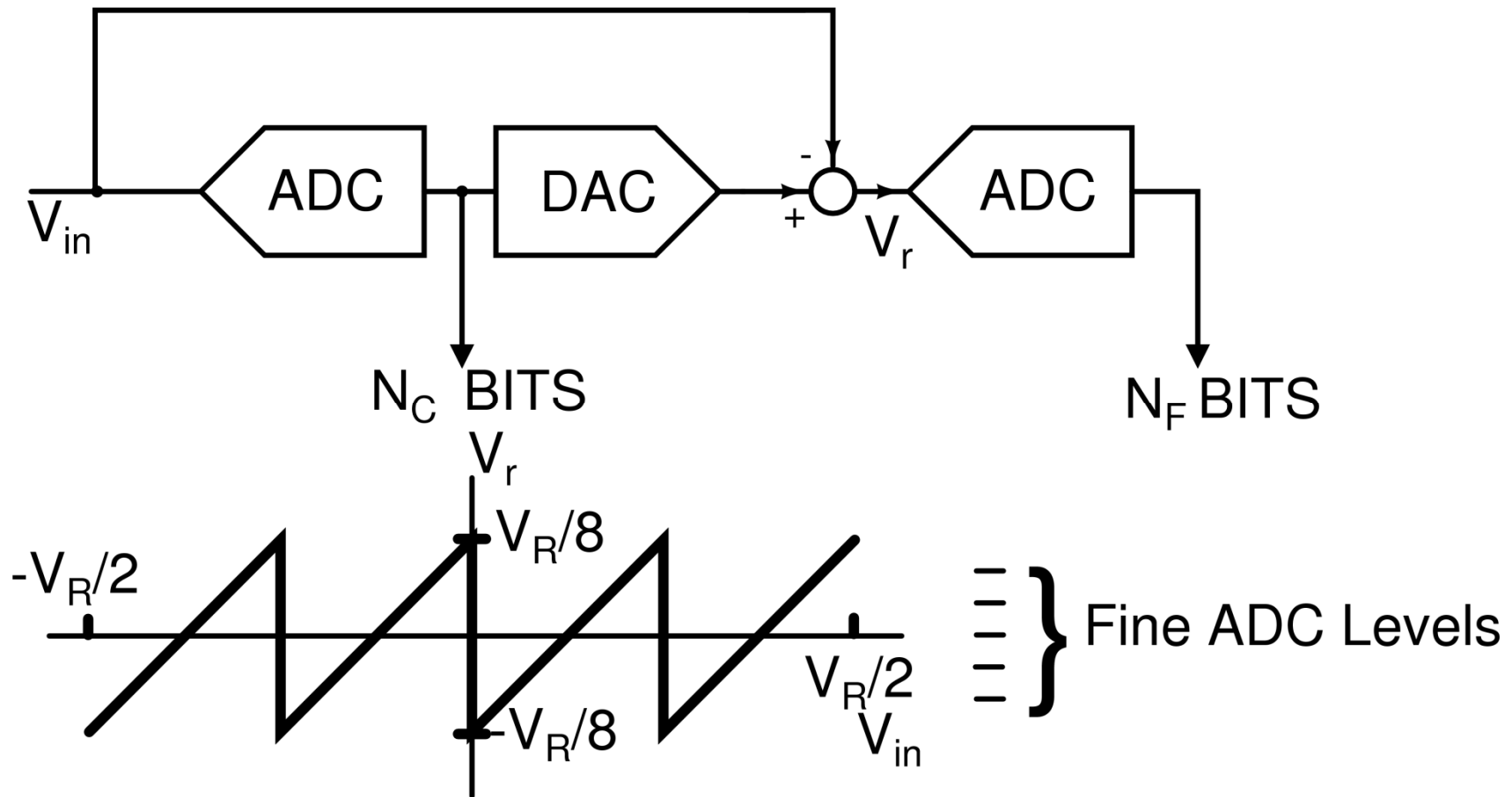


Number of comparators : $(2^{N_c} + 2^{N_f} - 2)$

Resolution $N_c + N_f$ bits


ADCs & DAC must be good to $(N_c + N_f)$ bits

Improved Two Step Flash ADCs

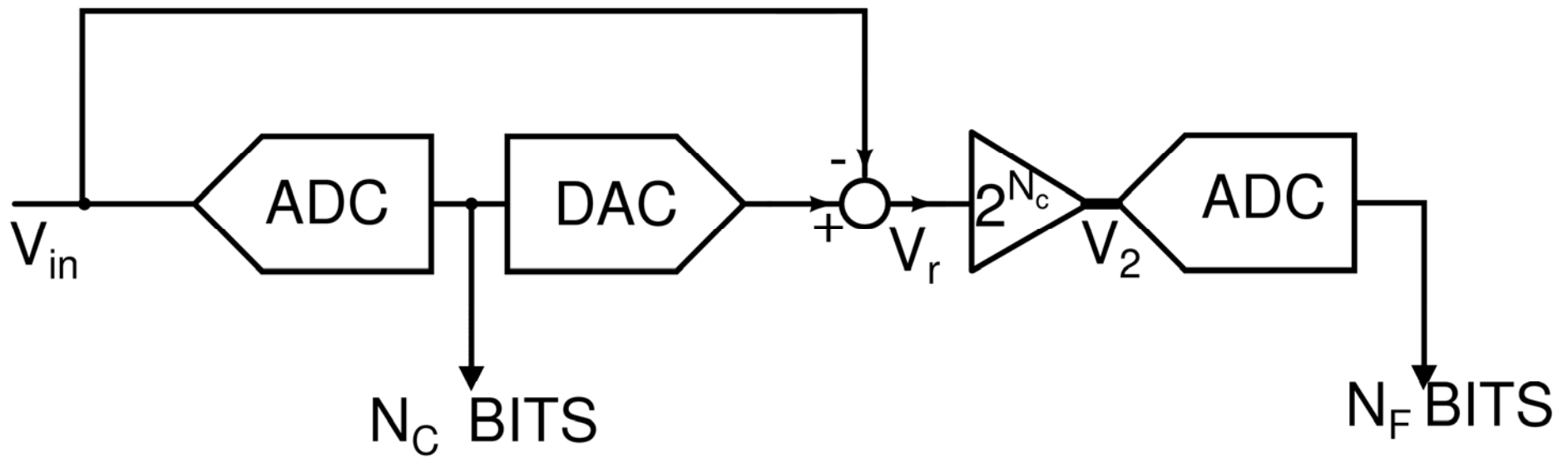
- The fine ADC operates on a small input
 - Offset requirements for the fine ADC can be relaxed if the input signal swing was larger
 - Amplify the input to the fine ADC



Pipeline ADC Principle

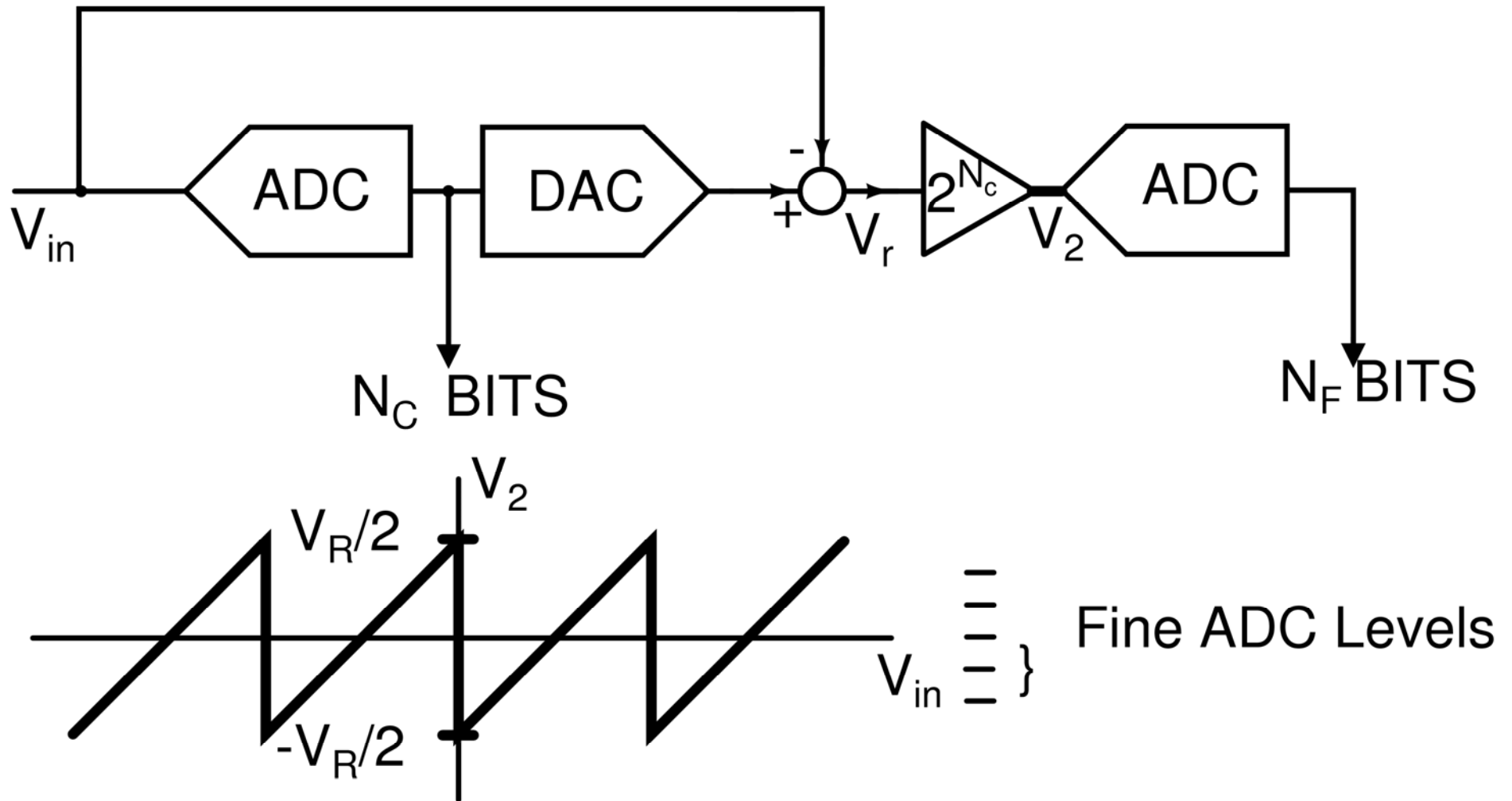

Pipeline ADC Principle

 


- Recursive implementation of the fine ADC
- Each stage implemented using switched capacitor techniques
- State of the art pipelines based on sophisticated digital correction and calibration algorithms

Pipeline ADC Design Flow

- High level design exploration at the behavioral level
 - Bits per stage
 - Opamp gain, linearity and bandwidth requirements
 - Capacitor matching studies
 - Digital calibration algorithms
- Stage Design
 - Opamp
 - Coarse ADC & DAC



Example Pipeline ADC Stage

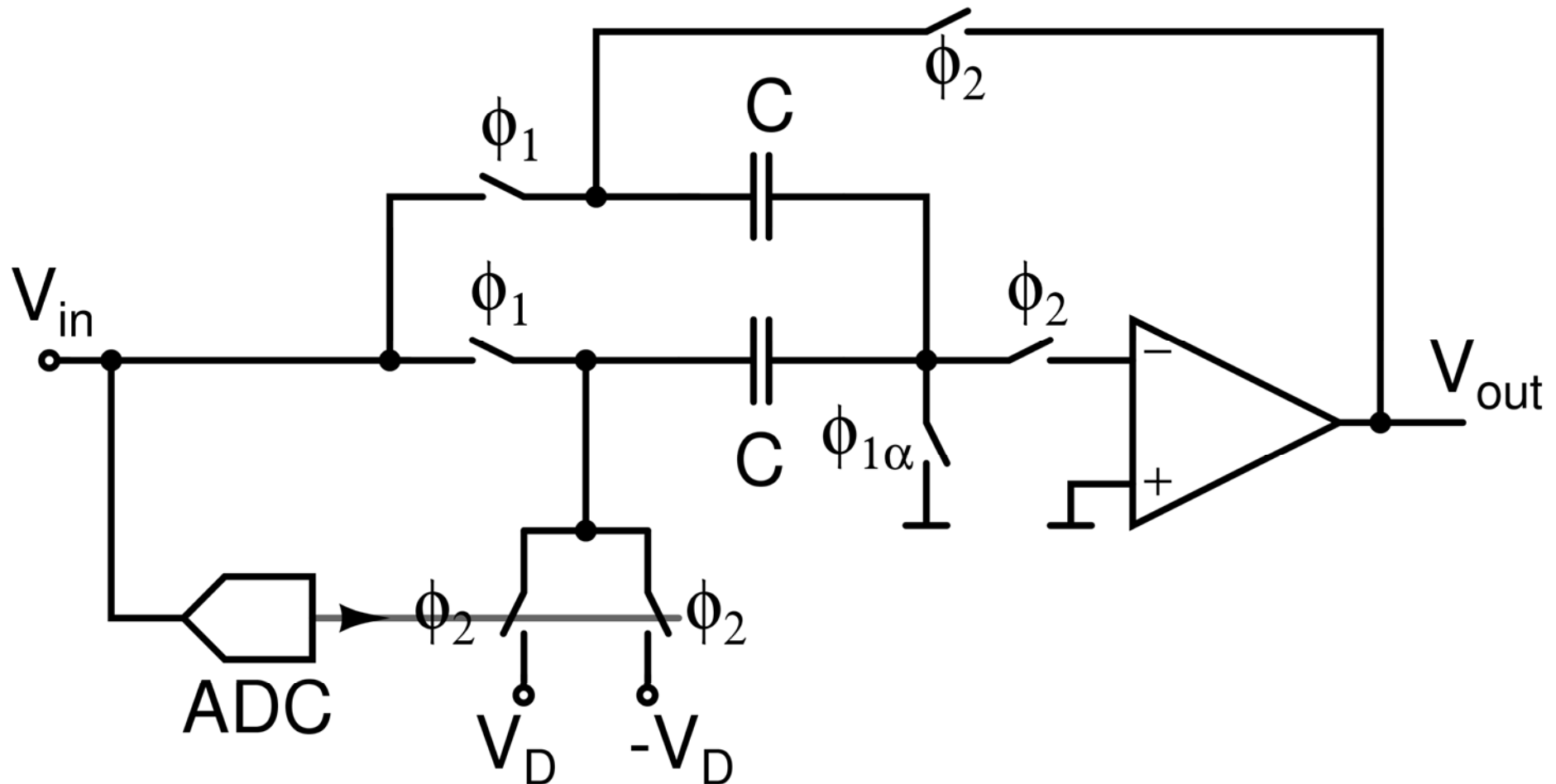

DAC, Subtraction and Amplifier using
one switched capacitor stage : SPICE it carefully

Spectral Analysis in ADC Design

ADC Simulation: Black Box Testing

 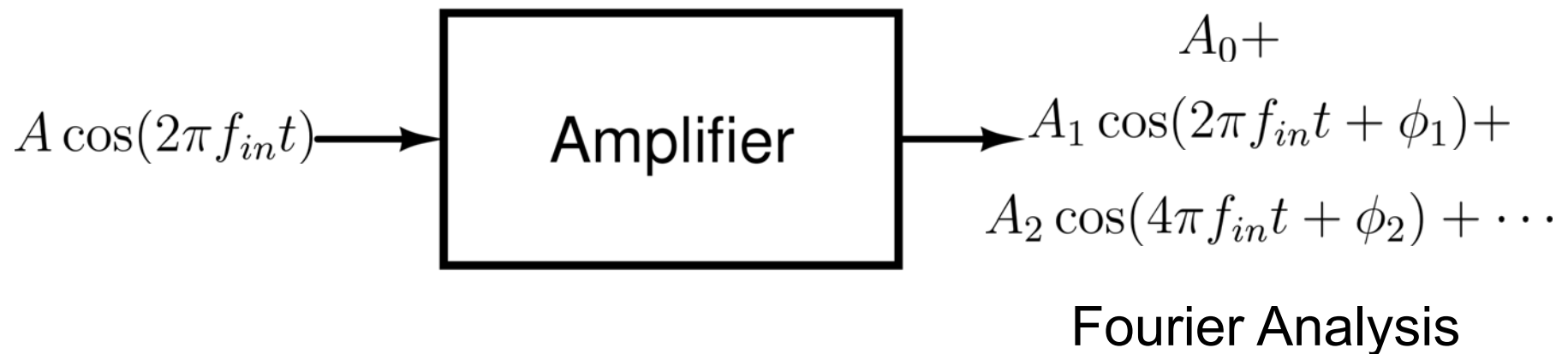

Basics

A discrete-time signal is periodic with period P if

$$s[n] = s[n + P]$$

It can be expanded into the *discrete* Fourier Series

$$s[n] = \sum_{k=0}^{k=P-1} A_k \cos \left[2\pi \frac{k}{P} n + \phi_k \right]$$

A discrete-time periodic signal with period P has only P coefficients in its Fourier expansion

A_k, ϕ_k can be rapidly computed using the FFT

Basics


$$s[n] = \sum_{k=0}^{k=P-1} A_k \cos \left[2\pi \frac{k}{P} n + \phi_k \right]$$

$s(t)$ sampled at f_s

Jargon

P is the FFT record length
 $\frac{f_s}{P}$ is the FFT bin width

Choice of f_{in}

 


$$A \cos \left[2\pi \frac{f_{in}}{f_s} n \right] = A \cos \left[2\pi \frac{f_{in}}{f_s} (n + P) \right] = A \cos \left[2\pi \frac{f_{in}}{f_s} n + 2\pi \frac{f_{in}}{f_s} P \right]$$

$$\text{periodic only if } \frac{f_{in}}{f_s} = \frac{m}{P}$$

Input and sampling frequencies must be rationally related

Choice of f_{in}

 

$$A \cos \left[2\pi \frac{f_{in}}{f_s} n \right] = A \cos \left[2\pi \frac{f_{in}}{f_s} (n + P) \right] = A \cos \left[2\pi \frac{f_{in}}{f_s} n + 2\pi f_{in} \frac{P}{f_s} \right]$$

$$\text{only if } \frac{P}{f_s} = \frac{m}{f_{in}}$$


Integral number of input cycles in the length of a record

$$\frac{f_{in}}{f_s} = \frac{m}{P} \quad \text{Is any } \frac{m}{P} \text{ good?}$$

Choice of f_{in}

Example : choose $\frac{f_{in}}{f_s} = \frac{m}{P} = \frac{1}{4}$

Very bad quantizer !

 


$$\cos \left[2\pi \frac{f_s}{4} \frac{n}{f_s} \right] = \cos \left[\frac{\pi}{2} n \right] = 1, 0, -1, 0 \dots \quad 1, 0, -1, 0 \dots = \cos \left[\frac{\pi}{2} n \right]$$

Predicts zero distortion !

Why ?

Choice of f_{in}

 

For a wrongly chosen m , multiple harmonics alias to the same frequencies after sampling

If $f_{in} = f_s/4$ all odd harmonics alias to $f_s/4$

Moral : Choose f_{in} so that its significant harmonics do not alias to the same locations

Choice of f_{in}

- (f_{in} / f_s) must be rational (m/P)
- *Choose m and P to be relatively prime*
- Convenient for FFT : choose $P = 2^Q$

$$f_{in} = \frac{m}{2^Q} f_s$$

Jargon : Input tone “lies on a bin”


Example : Choice of f_{in}

- 6-bit ADC sampling rate (f_s) = 1 GS/s
- Want to test around 250 MHz
- Choose record length = 1024

$$f_{in} = \frac{253}{1024} f_s = 247.0703125 \text{ MHz}$$

- Do not round off !

Test Setup for a Nyquist ADC

 


ADC input and clock source must be synchronous

- What happens when f_{in} & f_s are not rationally related ? (a.k.a f_{in} is “not on a bin”)


Aside

- What are the implications of computing the FFT of an P point sequence ?
- You assume that the sequence is **one period** of a periodic discrete-time sequence with period P
- You are computing the coefficients of the discrete Fourier series of this periodic sequence

FFT Leakage

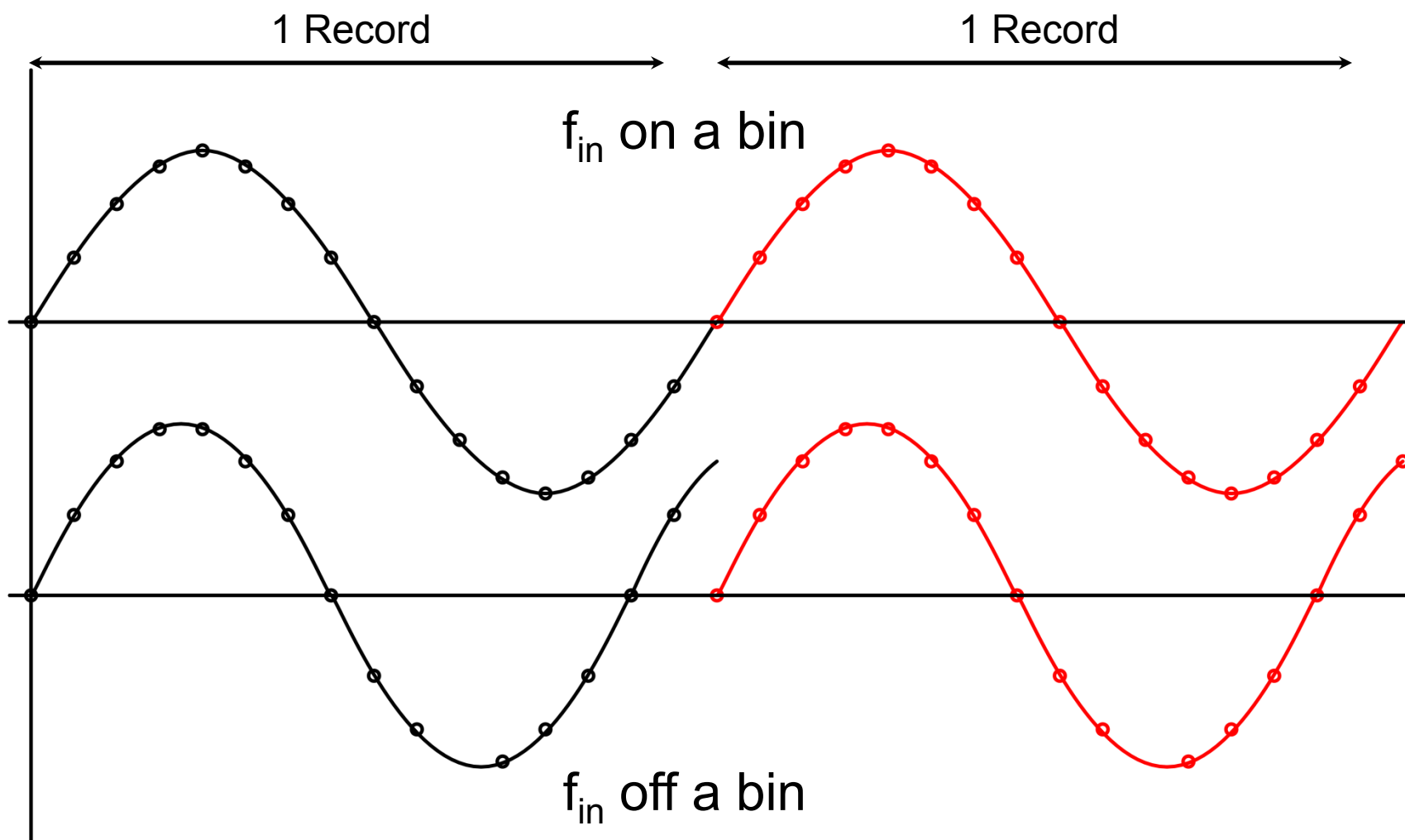


FFT Leakage

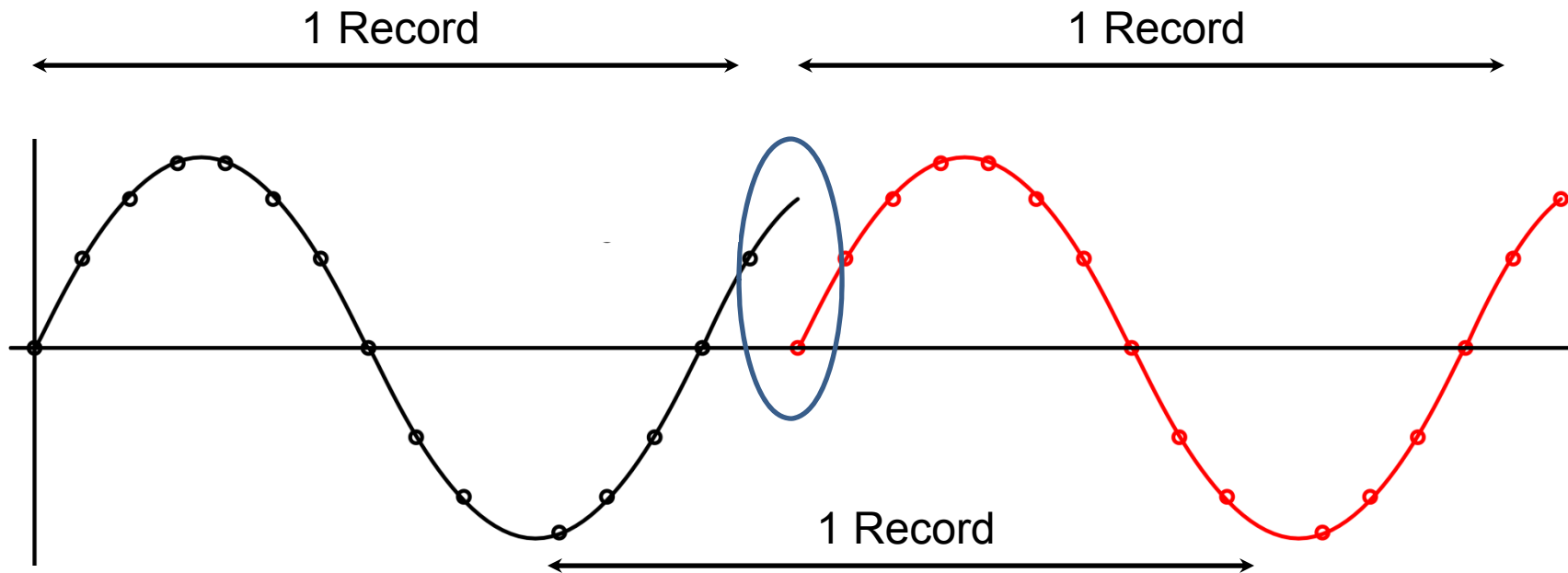


Jump here – impulse – lots of spectral energy everywhere
Called FFT “leakage”

FFT Leakage

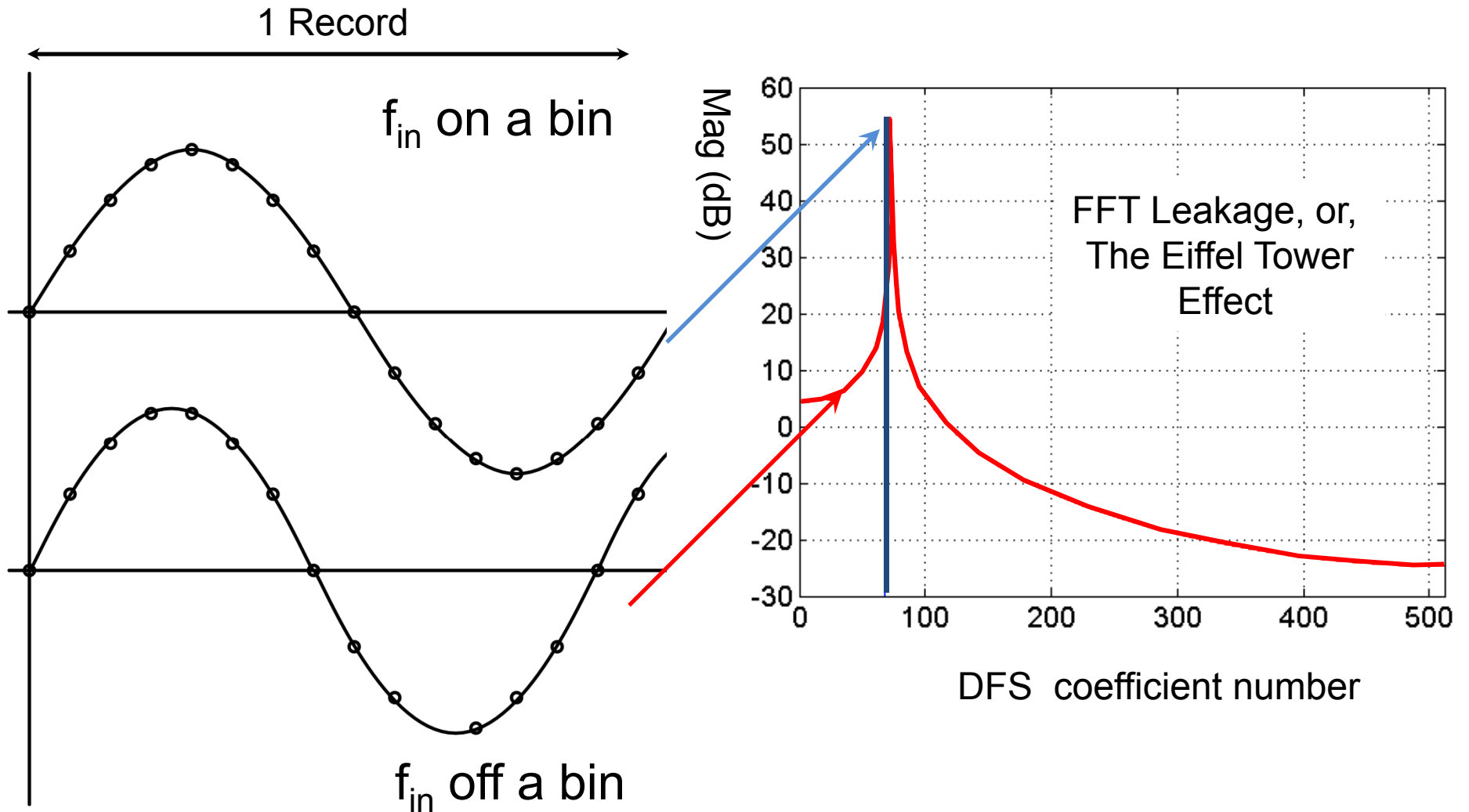


Why is Leakage Problematic ?

No leakage

 


Why is Leakage Problematic ?

with leakage

 


FFT Leakage : Solution

 



Basic Idea :

Data at the ends of the record are problematic
→ Pay less attention to the ends of the record

Windowing

 


Leakage : A spectral view

  


$$S[\omega] = \frac{1}{2} (\delta(\omega - \omega_0) + \delta(\omega + \omega_0))$$


Leakage : A spectral view

 

Leakage : A spectral view

 


Leakage : A spectral view

 


Discrete Fourier Series is obtained by sampling the Discrete Fourier Transform


Leakage : with windowing

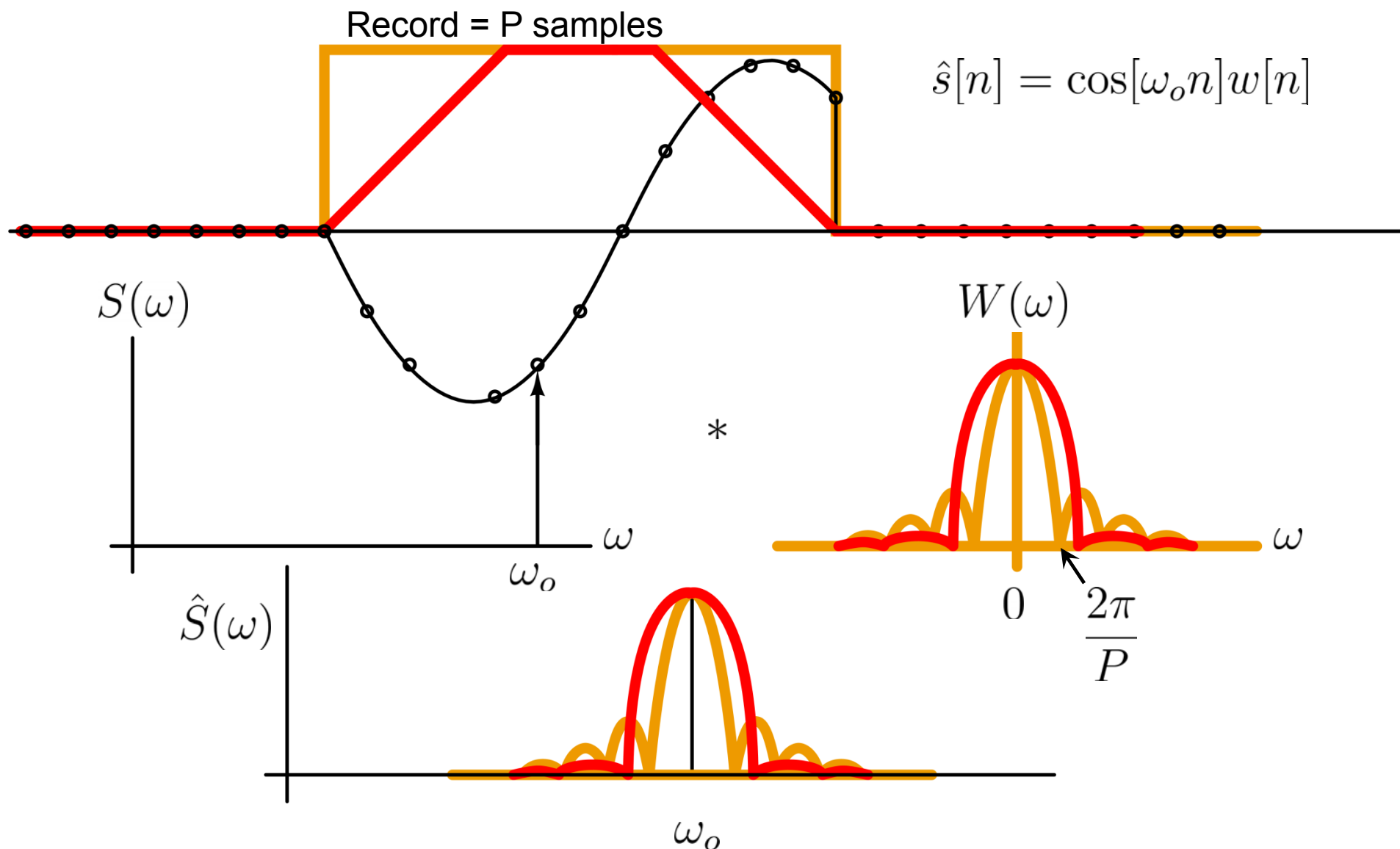

Windowing

 


Commonly used windows

 

Rectangular


Hann

Blackman-Harris

 

Trade off between main lobe width and side lobe suppression

PSD & FFT

 


$$PSD = \frac{1}{N} \sum_{k=1}^N |FFT_k|^2$$

Simulation of $\Delta\Sigma$ ADCs

- Stiff
 - Low frequency input, high frequency clock
- No “one-to-one” correspondence between input and output
 - Debug is not trivial
- Computing SNDR
 - More involved than the Nyquist case
- Simulating device noise
 - Computationally expensive

Delta Sigma ADCs

 


Basic Idea

Embed a coarse quantizer in a negative feedback loop

$L(z)$ has high gain @ low frequency

$\Rightarrow v \approx u$ @ low frequency

Oversampling Converters

 

$$V(z) = \frac{L(z)}{1 + L(z)} U(z) + \frac{1}{1 + L(z)} E(z)$$

Signal Transfer
Function
STF

Noise Transfer
Function
NTF

Oversampling Converters

$$V(z) = \frac{L(z)}{1 + L(z)} U(z) + \frac{1}{1 + L(z)} E(z)$$

Signal Transfer
Function

STF

$$L(z) \rightarrow \infty \text{ as } z = e^{j\omega} \rightarrow 1$$

$$STF(z) \rightarrow 1 \text{ and } NTF(z) \rightarrow 0$$

Noise Transfer
Function

NTF

Quantization Noise is high pass filtered
 \Rightarrow High inband SNR

Oversampling Converters

$$V(z) = \frac{L(z)}{1 + L(z)}U(z) + \boxed{\frac{1}{1 + L(z)}}E(z)$$


Noise Transfer
Function
NTF

Choosing an appropriate $L(z)$ is the
first step in the design


Too little gain : Not enough noise suppression

Gain is too high : Loop becomes unstable


NTF = High Pass Filter Design

 

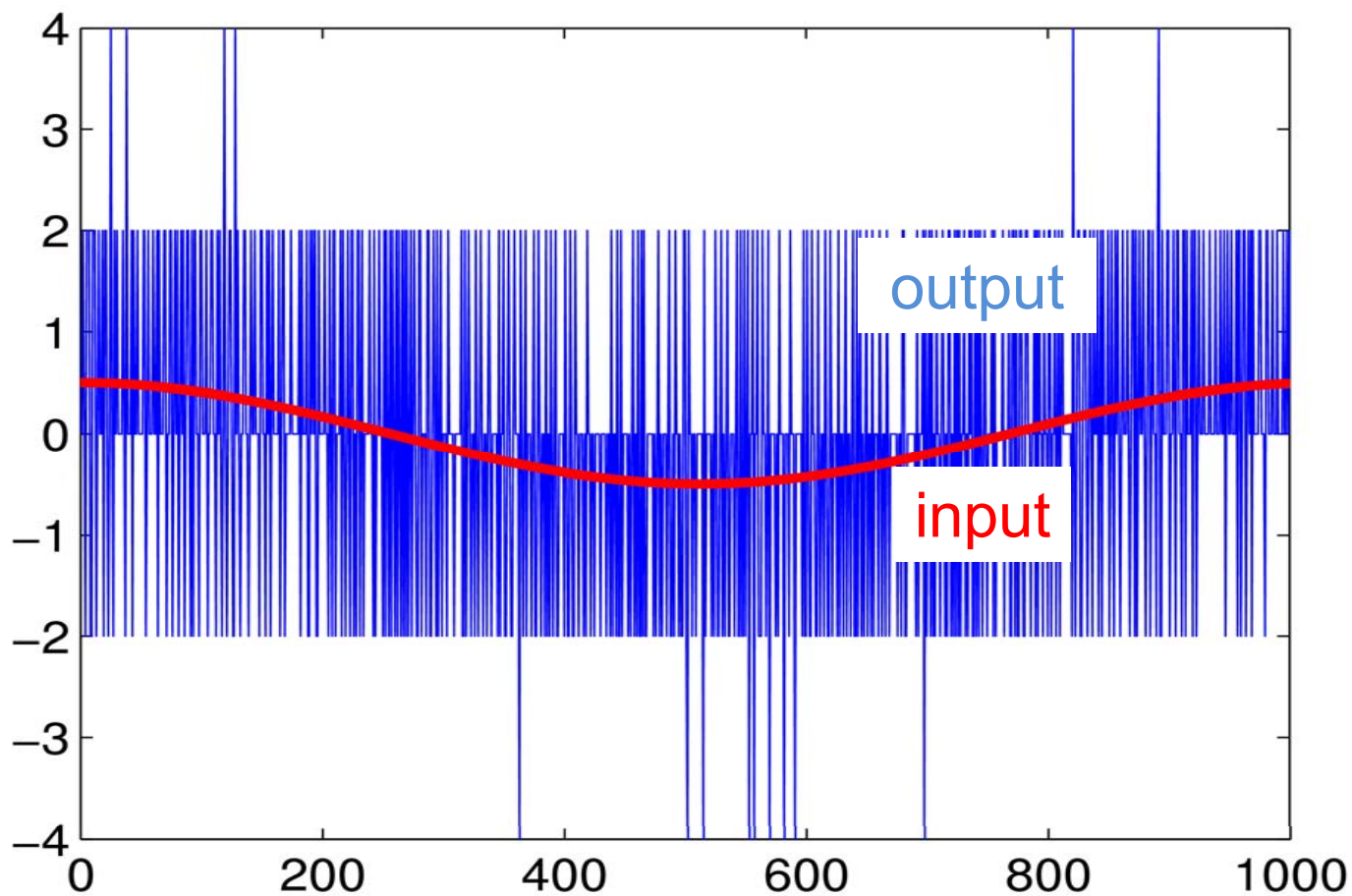Example $\Delta\Sigma$ Converter Waveforms




 Example $\Delta\Sigma$ Converter Spectrum



Signal Dependent Stability


$$V(z) = STF(z) U + NTF(z) E$$

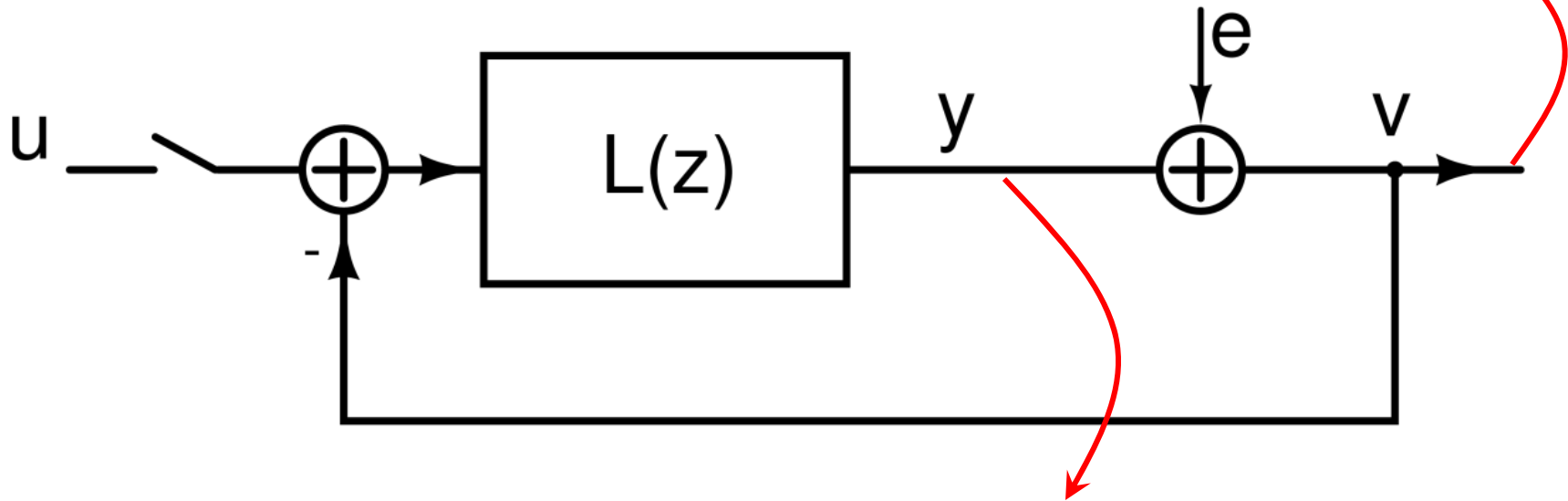

$$Y(z) = STF(z) U + (NTF(z) - 1) E$$

$$\approx U + (NTF(z) - 1) E$$

Stability

 

$$Y(z) \approx U + (NTF(z) - 1) E$$

Shaped Quantization Noise

$u \rightarrow$ close to quantizer saturation limits

- Shaped noise saturates the quantizer $\rightarrow e$ increases
- This saturates the quantizer more $\rightarrow e$ increases even more
- ... until y becomes unbounded \rightarrow modulator becomes unstable



Stability

- Signal dependent stability to be **expected**


$$\frac{\text{Stable Input Range}}{\text{Quantizer Range}} = \text{Maximum Stable Amplitude (MSA)}$$

- MSA depends on
 - NTF
 - Number of quantizer levels
 - Input frequency

DAC Nonidealities

 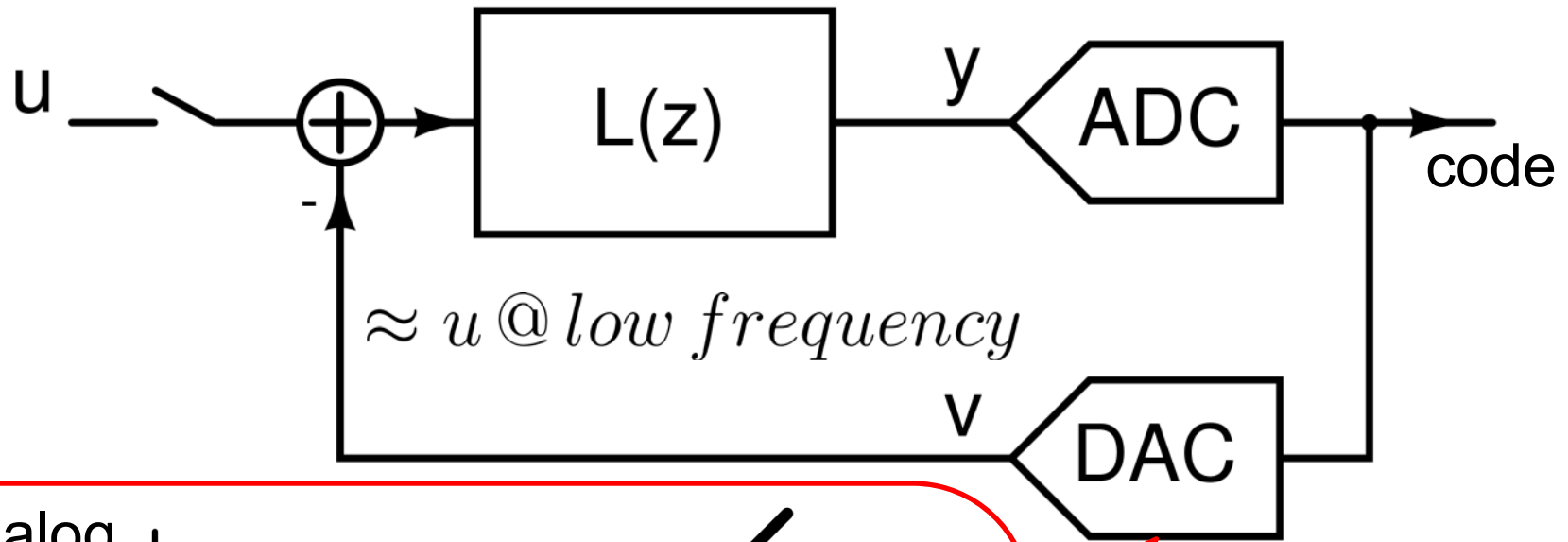


DAC Nonidealities

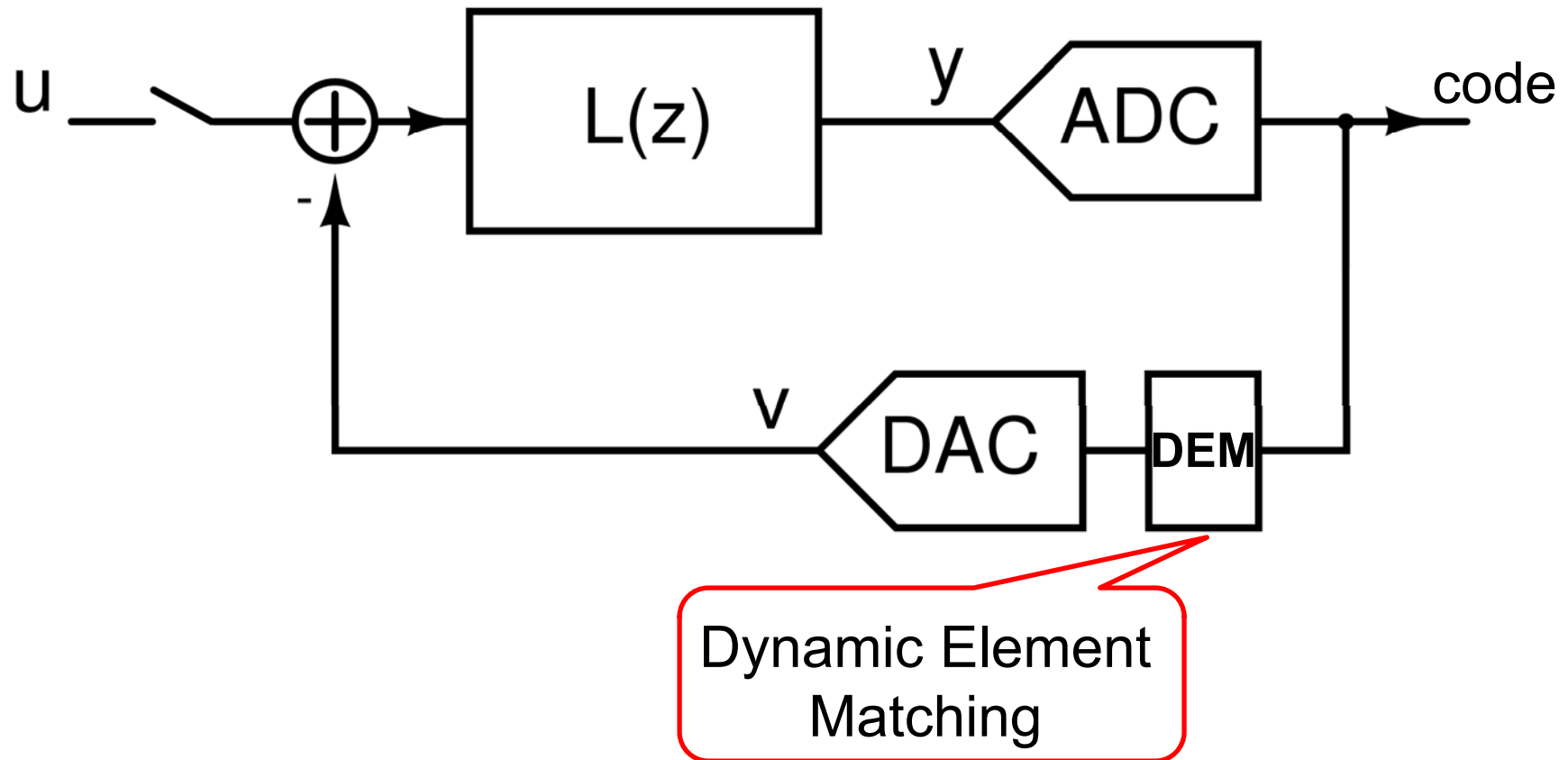

DEM : Magically shapes mismatch noise out of the signal band


Generic Single Loop DT-DSM

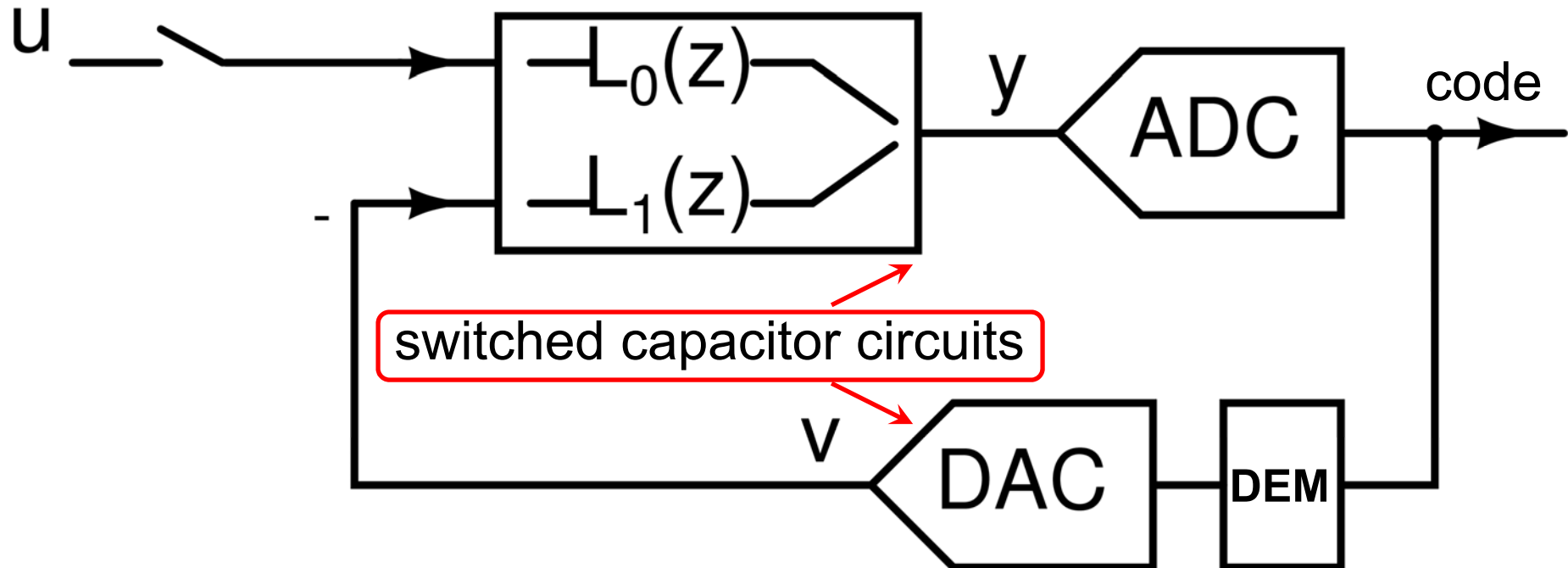

$$NTF(z) = \frac{1}{1 + L_1(z)}$$


$$STF(z) = \frac{L_0(z)}{1 + L_1(z)}$$

Generic Single Loop CT-DSM

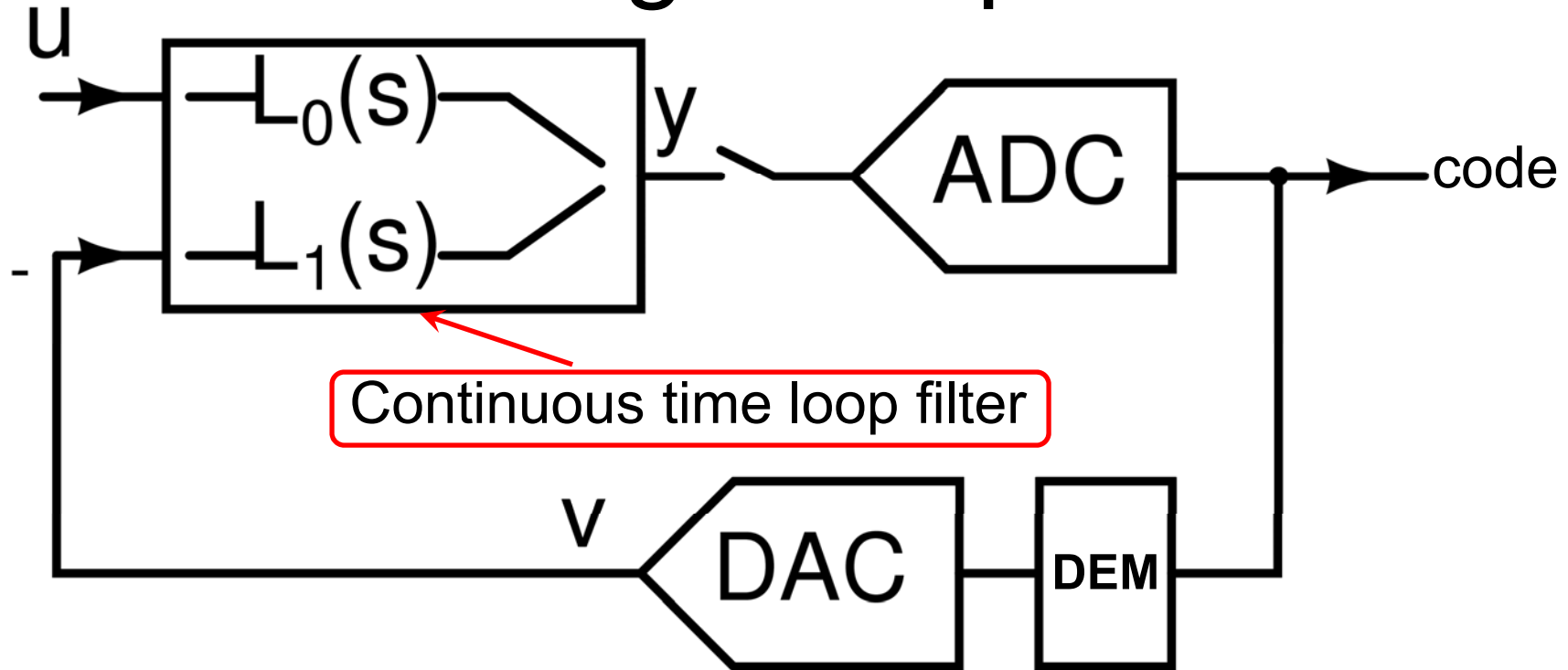

- Input sampled at the loop filter output
 - Implicit anti-aliasing if the loop filter is time invariant
- Resistive input impedance \rightarrow easy to drive
- Reduced slew requirements of opamps


Linear Models : DT & CT DSMs

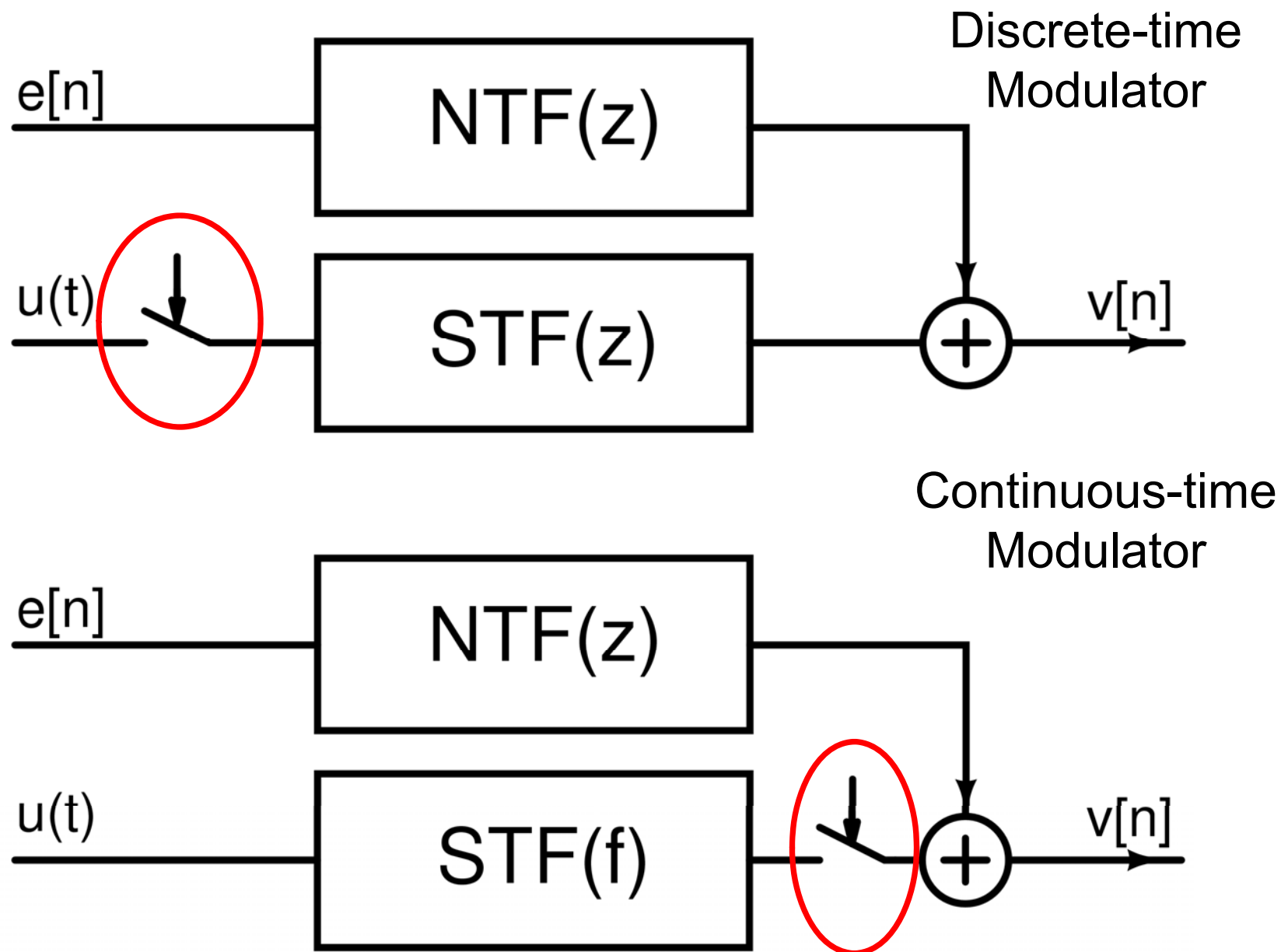


$\Delta\Sigma$ ADC : Design Flow

- Choose OSR, quantizer levels, NTF and architecture
 - Determine MSA (use simulation)
- Determine component values
- Design building blocks
 - Loop filter, ADC, DAC, DEM logic


Building Block Design - DT

 

 
Loop Filter :
Gain, Unity gain freq.
Parasitic poles




Comparator :
Offset, Delay

 




Building Block Design - CT

 

 Loop Filter :
Gain, Unity gain freq.
Parasitic poles




Comparator :
Offset, Delay

 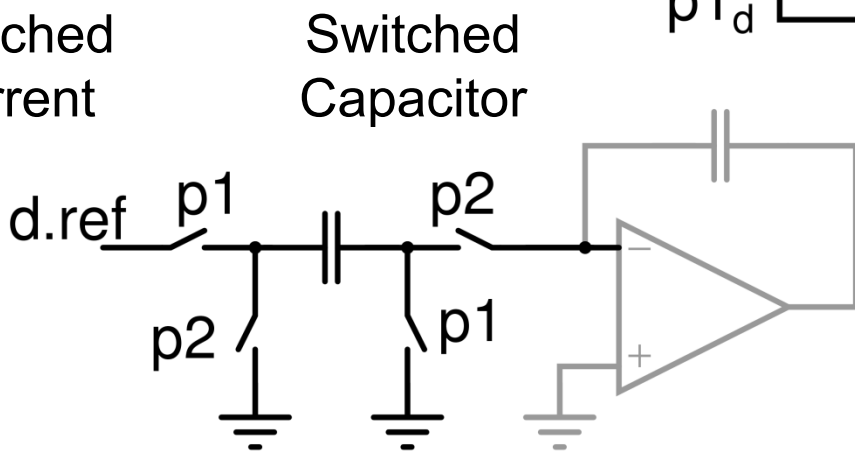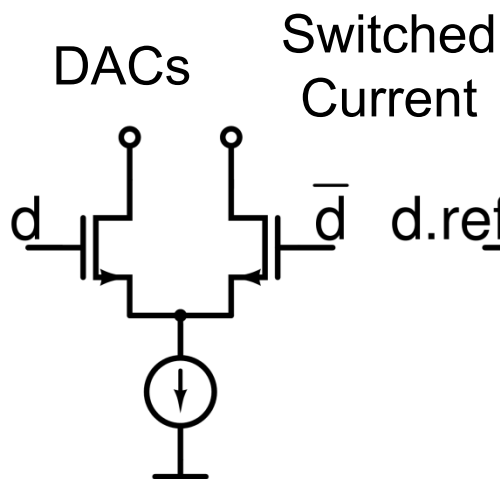

High Level Design Aids

- $\Delta\Sigma$ Toolbox for MATLAB
 - Richard Schreier of Analog Devices
- Neat set of routines that enable high level design and rapid simulation
 - Find SN(D)R, MSA for a given NTF
 - Simulate a DT modulator given loop filter description in state space form

$\Delta\Sigma$ Toolbox for MATLAB

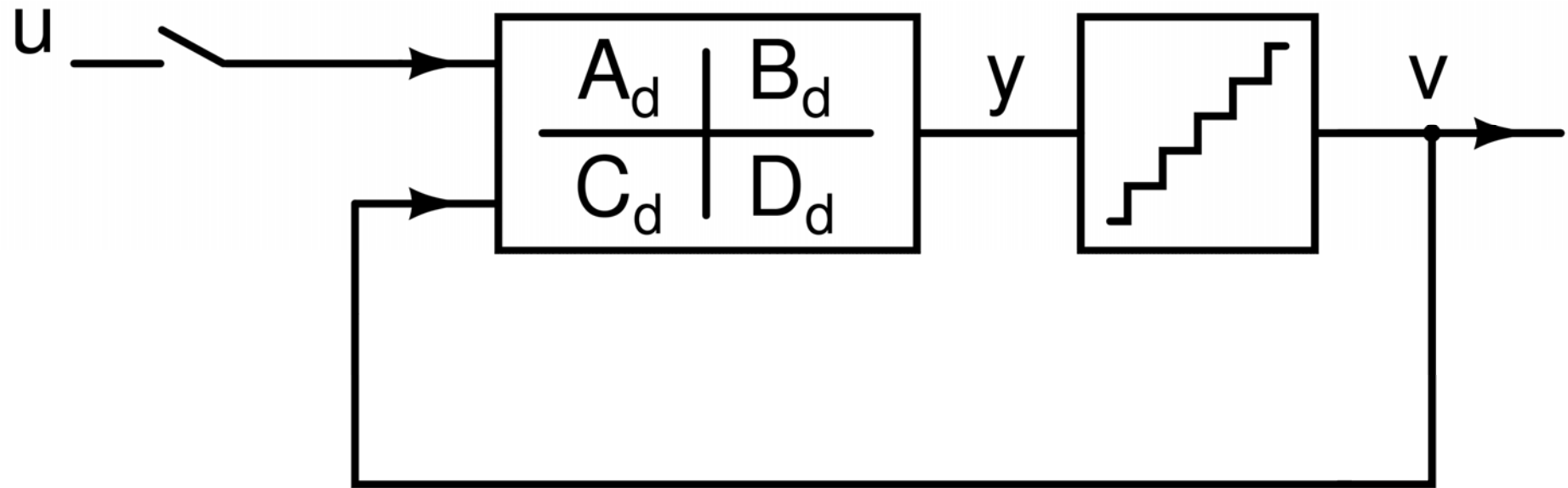

- Support for multiple inputs/quantizers
- Can be combined with the power of MATLAB to design/simulate CTDSMs as well

$\Delta\Sigma$ Toolbox for MATLAB

- All linear effects can be modeled with the tool box
 - Finite gain and parasitic poles in the loop filter
 - Excess loop delay
- With minor modifications
 - Flash ADC offsets
- Great design and educational value
- Highly recommended !


Circuit Simulation Strategies

- Keep one block real – all others behavioral
 - e.g. loop filter real but Verilog-A ADC, DAC, DEM
 - Isolates “gross” problems
- Two blocks real – others Verilog-A
 - Enables debug of “interface” issues
- **MUST** run the complete design at the transistor level
 - Many problems are often subtle and only show up at this level


$\Delta\Sigma$ ADC : Simulations

- Inband SNDR
 - How to calculate this ?
 - How long should I simulate ?
- Realized NTF
 - As opposed to intended NTF
- Realized STF
 - Especially in CT modulators
- Device Noise

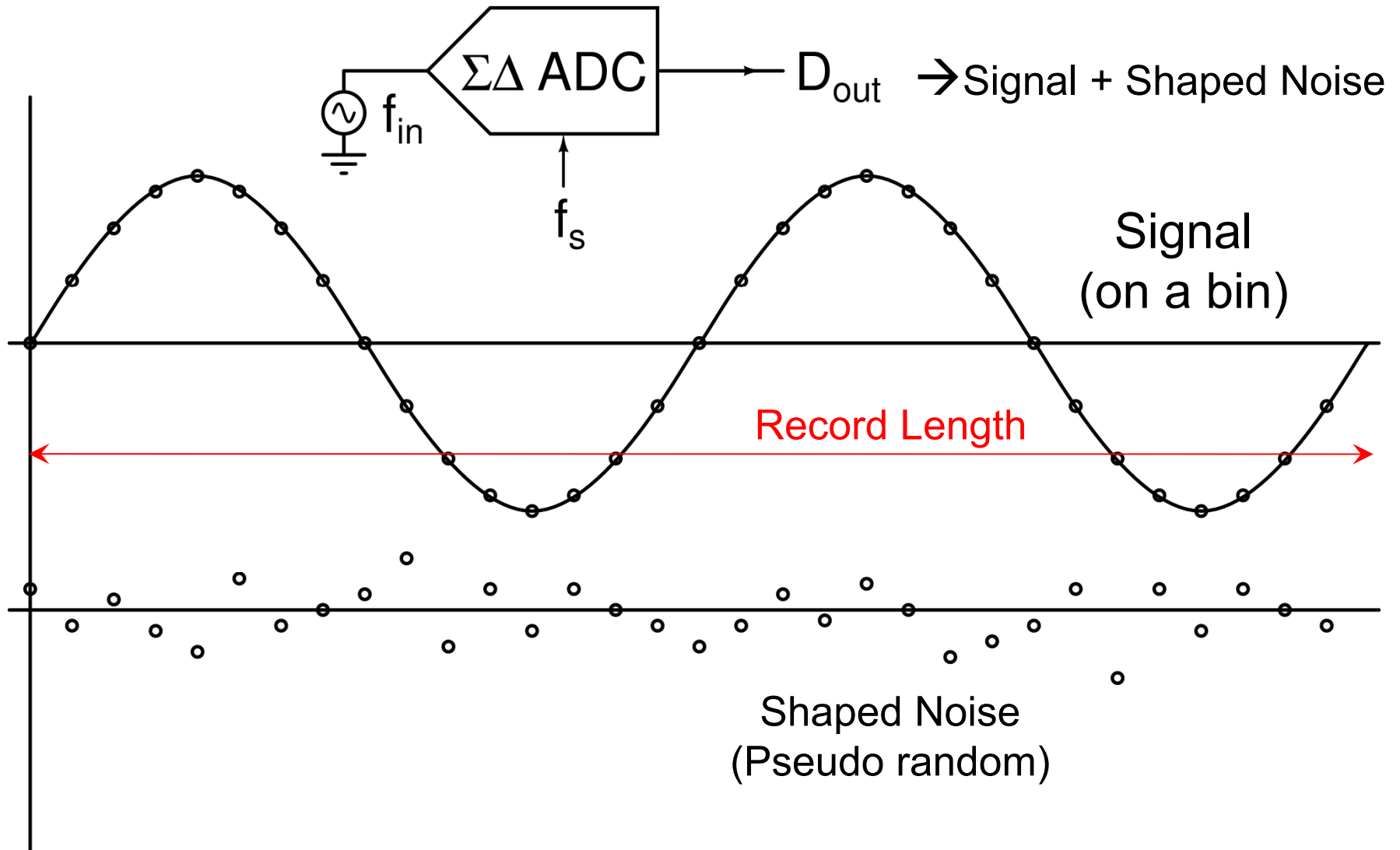
Simulating Inband SNDR in $\Sigma\Delta$ ADCs



Simulating SNDR

 

$\Sigma\Delta$ Example Spectra

 

Moral : Must window data even if
input tone lies on a bin

How many samples do I need ?

- Record Length = Number of FFT bins = N
- Number of bins in the signal band : $\frac{N}{2OSR}$
- Input signal + 2 harmonics (Hann): 9 bins
- DC Offset : 2 bins

Estimating noise from $(\frac{N}{2OSR} - 11) \approx 15$ bins

$\Rightarrow N \approx 52 OSR$ samples


Thumbrule : Choose N to be **atleast** $64 OSR$

$\Delta\Sigma$ ADC : Simulations

- Inband SNDR
 - How to calculate this ?
 - How long should I simulate ?
- Realized NTF
 - As opposed to intended NTF
- Realized STF
 - Especially in CT modulators
- Device Noise

What NTF do I have ?

 - NTF is the all important loop parameter
 - Deviates too much from the designed \rightarrow trouble
- NTF \rightarrow easy to determine MSA using high level model




$$V(z) \approx U(z) + NTF(z)E(z)$$

$$PSD(v) = PSD(u) + |NTF|^2 PSD(e)$$


Output PSD

$$PSD(v) = PSD(u) + |NTF|^2 PSD(e)$$

 


Estimating NTF

 - Eyeballing the PSD \rightarrow misleading




$$V(z) = STF U(z) + NTF \{V(z) - Y(z)\} \text{ exactly}$$

 “Error” is in thinking of this
as white noise





Estimated NTF

 

Another Example

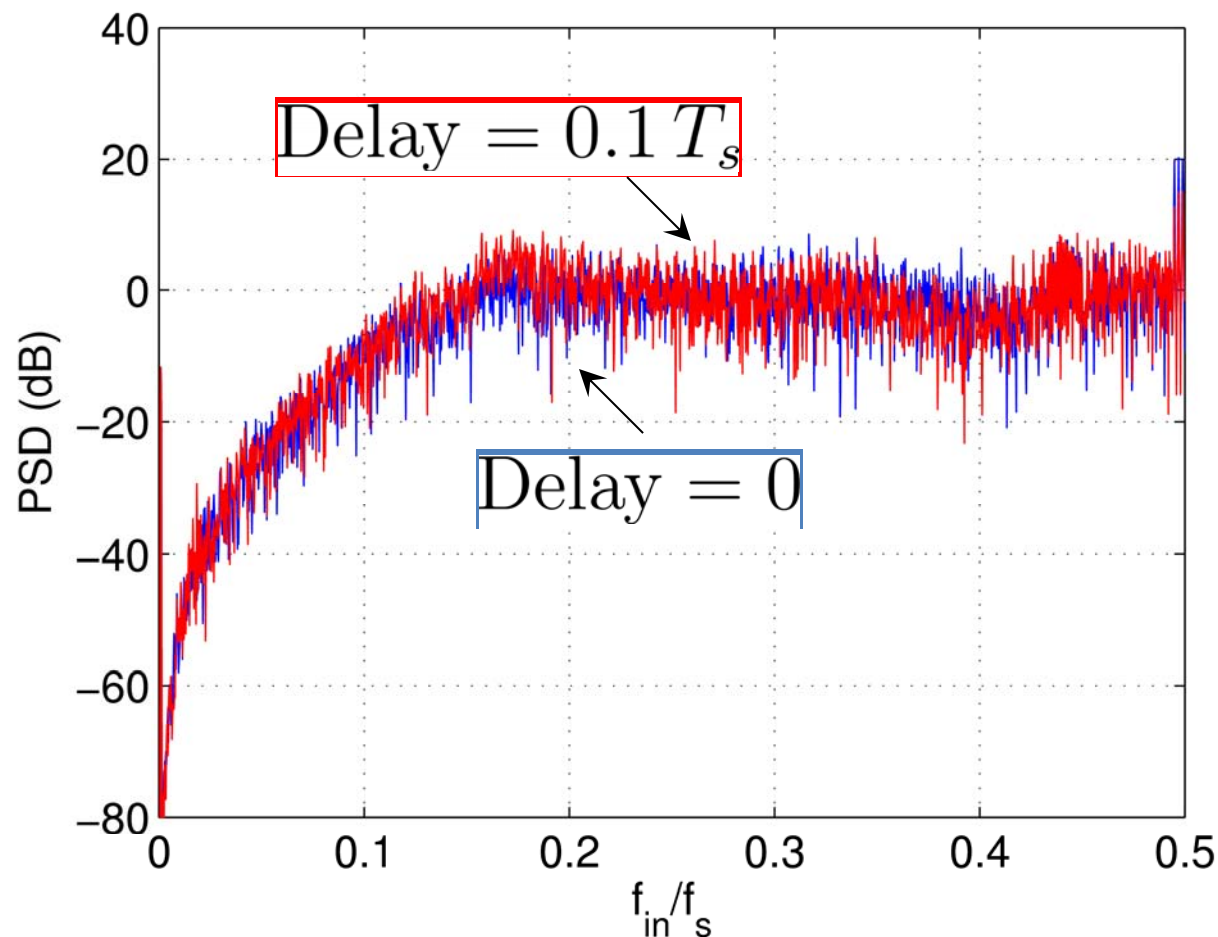- Two second order single bit CTDSMs
 - Nominal NTF = $(1 - z^{-1})^2$
 - One with unintended feedback delay of $0.1T_s$



 

$\Delta\Sigma$ ADC : Simulations

- Inband SNDR
 - How to calculate this ?
 - How long should I simulate ?
- Realized NTF
 - As opposed to intended NTF
- Realized STF
 - Especially in CT modulators
- Device Noise

RF Analyses in ADC Designs ?

- Typical RF designer's arsenal
 - Periodic Steady State (PSS)
 - Periodic AC (PAC)
 - Periodic Transfer Function (PXF)
 - Periodic Noise (Pnoise)
- Why/where are they relevant in ADC design ?


RF Analyses in ADC Designs ?

- PSS, PAC, PXF, Pnoise
 - Pertain to systems described by linear differential equations with periodically time varying coefficients
 - Linear networks with periodic switching
- Why are they important ?
 - All ADCs aim to be Linear Periodically Time Varying (LPTV) (if quantization noise is zero)


LPTV Systems

- Time domain analysis time consuming
 - Especially with noise
- Frequency domain analysis of LPTV systems
 - Yields certain kinds of insight
 - Now supported by several commercial simulators
 - Powerful and fast analysis tool
 - Helps to know “what is going on” behind these methods


Linear Time Invariant

 

Linear Time Variant

 

LTV System

 


$$y(t) = \int_0^{\infty} h(t, t - \tau)x(t - \tau)d\tau$$

$$x(t) = e^{j\omega t}$$

$$\begin{aligned}
 y(t) &= \int_0^{\infty} h(t, t - \tau)e^{j\omega(t-\tau)}d\tau \\
 &= e^{j\omega t} \int_0^{\infty} h(t, t - \tau)e^{-j\omega\tau}d\tau \\
 &= e^{j\omega t} \underbrace{H(j\omega; t)}
 \end{aligned}$$

Time Dependent
Frequency Response

L-Periodically-TV Systems

 

LPTV Systems

$$H(j\omega; t) = \int_0^{\infty} h(t, t - \tau) e^{-j\omega\tau} d\tau$$

$$\begin{aligned} H(j\omega; t + T_s) &= \int_0^{\infty} h(t + T_s, t + T_s - \tau) e^{-j\omega\tau} d\tau \\ &= \int_0^{\infty} h(t, t - \tau) e^{-j\omega\tau} d\tau = H(j\omega; t) \end{aligned}$$


$$H(j\omega; t + T_s) = H(j\omega; t) = \sum_{l=-\infty}^{l=\infty} H_l(j\omega) e^{jl\omega_s t}$$

$$\text{Input : } x(t) = e^{j\omega t}$$

$$y(t) = \sum_{l=-\infty}^{l=\infty} H_l(j\omega) e^{j(\omega + l\omega_s)t}$$

$$y(t) = \sum_{l=-\infty}^{l=\infty} H_l(j\omega) e^{j(\omega + l\omega_s)t}$$

sideband

 


Input at ω causes components at $\omega \pm (0, 1, 2, \dots)\omega_s$

Periodic AC Analysis yields $H_l(j\omega)$ for any desired l

PAC Analysis

Periodic XF Analysis

 

Output at ω due to components at $\omega \pm (0, 1, 2, \dots)\omega_s$

Periodic XF Analysis yields $H_l(j\omega)$ for any desired l

┌──────────┐
PXF Analysis

Noise in LPTV Systems

- Frequency translation is an inherent property of LPTV systems
- Same applies to noise


Noise at ω due to components at $\omega \pm (0, 1, 2, \dots)\omega_s$

PNoise finds noise accounting for freq translation

$\Delta\Sigma$ ADC : Simulations

- Inband SNDR
 - How to calculate this ?
 - How long should I simulate ?
- Realized NTF
 - As opposed to intended NTF
- Realized STF
 - Especially in CT modulators
- Device Noise

Linear Model : CT DSMs

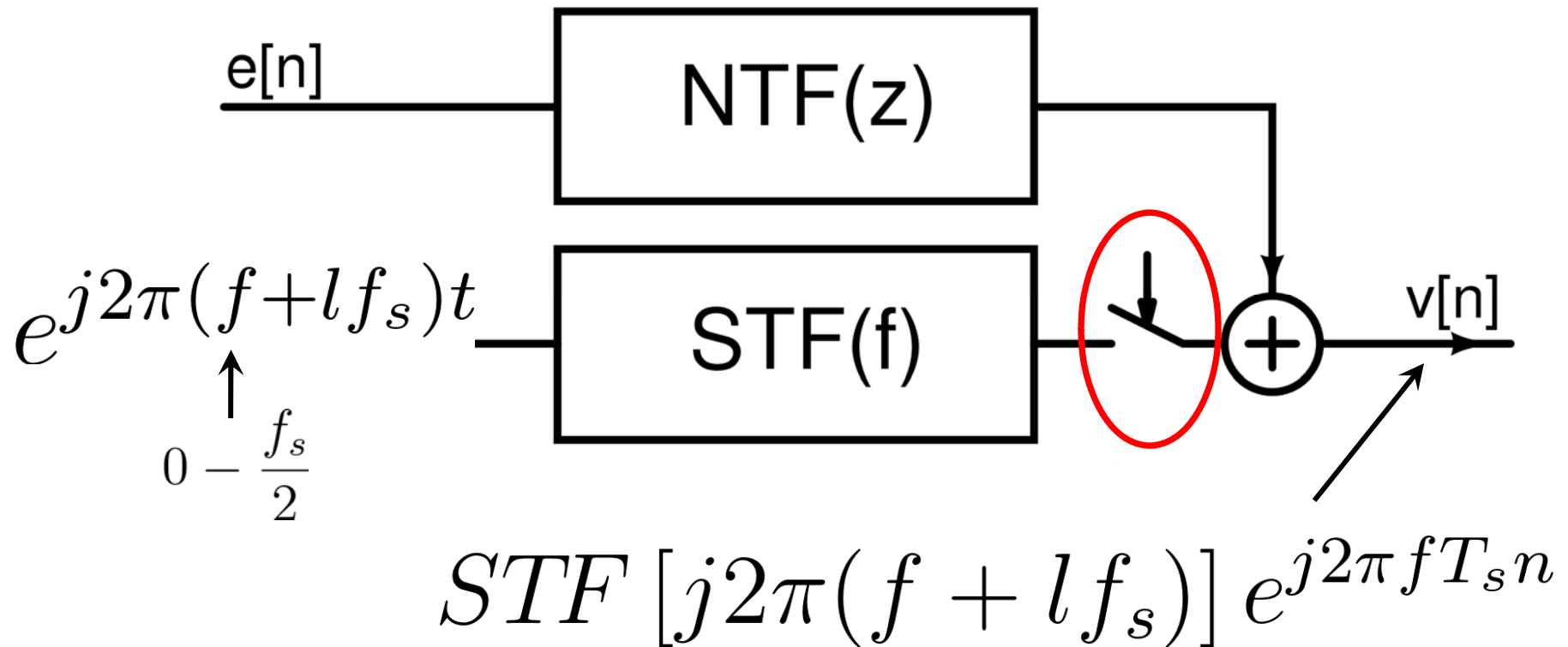

Determining the STF

At least two ways of doing this

- **A** : Put in a sinewave, run the modulator, measure the strength of the output sinewave, repeat for another frequency
 - Takes very long, if high resolution of frequency is needed
 - Amplitude of the tone has to be carefully chosen
 - The “true” STF, accounting for the quantizer gain

Determining the STF

- **B: Periodic Transfer Function (PXF) analysis**
 - Replace quantizer by a sampler
 - The system is LPTV
 - Run PSS/PXF
 - Yields the STF assuming unity quantizer gain

Periodic XF Analysis

PSS Beat Frequency (Hz)

Sweeptype Sweep is currently absolute

Output Frequency Sweep Range (Hz)

Start-Stop

Sweep Type

Linear Step Size Number of Steps

Add Specific Points

Sidebands

Maximum sideband

When using shooting engine, default value is 7.

Output

voltage Positive Output Node

probe Negative Output Node

Specialized Analyses

Sampled Sine Step

Signal	Threshold	Crossing Direction
<input type="radio"/> probe <input type="text" value="/clk"/> <input type="button" value="Select"/>	<input type="text" value="1"/>	<input checked="" type="radio"/> rise <input type="radio"/> fall
<input checked="" type="radio"/> voltage <input type="text" value="/gnd"/> <input type="button" value="Select"/>		

Sampled Optional Parameters:

Maximum Sample Sample Delay

Additional Timepoints

Sampling Rate


$$0 - f_s/2$$

To find STF in the range

$$\pm \left(\left[0 - \frac{f_s}{2} \right] + \{0, 1\} f_s \right)$$

Only the output samples at clock rising edge are relevant

STF from PXF Analysis

 


$\Delta\Sigma$ ADC : Simulations

- Inband SNDR
 - How to calculate this ?
 - How long should I simulate ?
- Realized NTF
 - As opposed to intended NTF
- Realized STF
 - Especially in CT modulators
- **Device Noise**

Transient Noise Analysis

- Conceptually straightforward


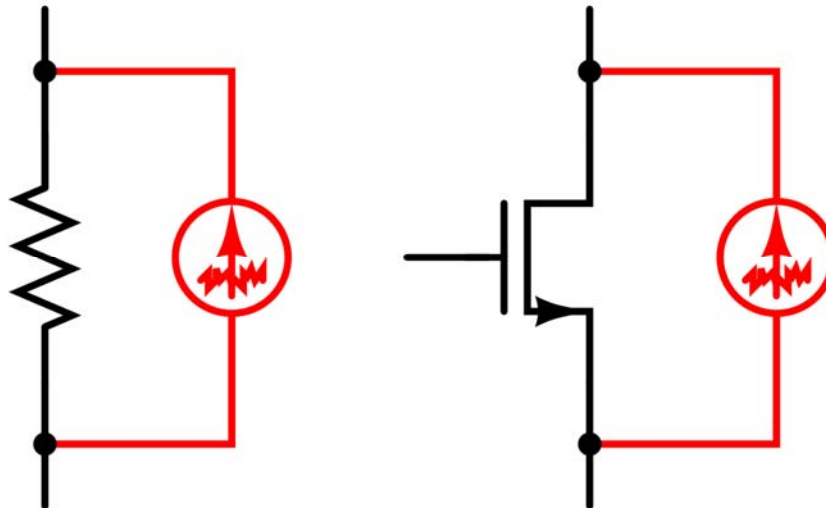


- Noise currents added in parallel with device currents
 - Spectral density can be bias dependent


Transient Noise Analysis

- Noise updated at every simulation step
 - White and colored noise can be modeled
- Results need careful interpretation
- Very expensive with respect to simulation time
 - Can run many instances simultaneously
 - Use only as needed


Generating White Noise

  


Generating White Noise

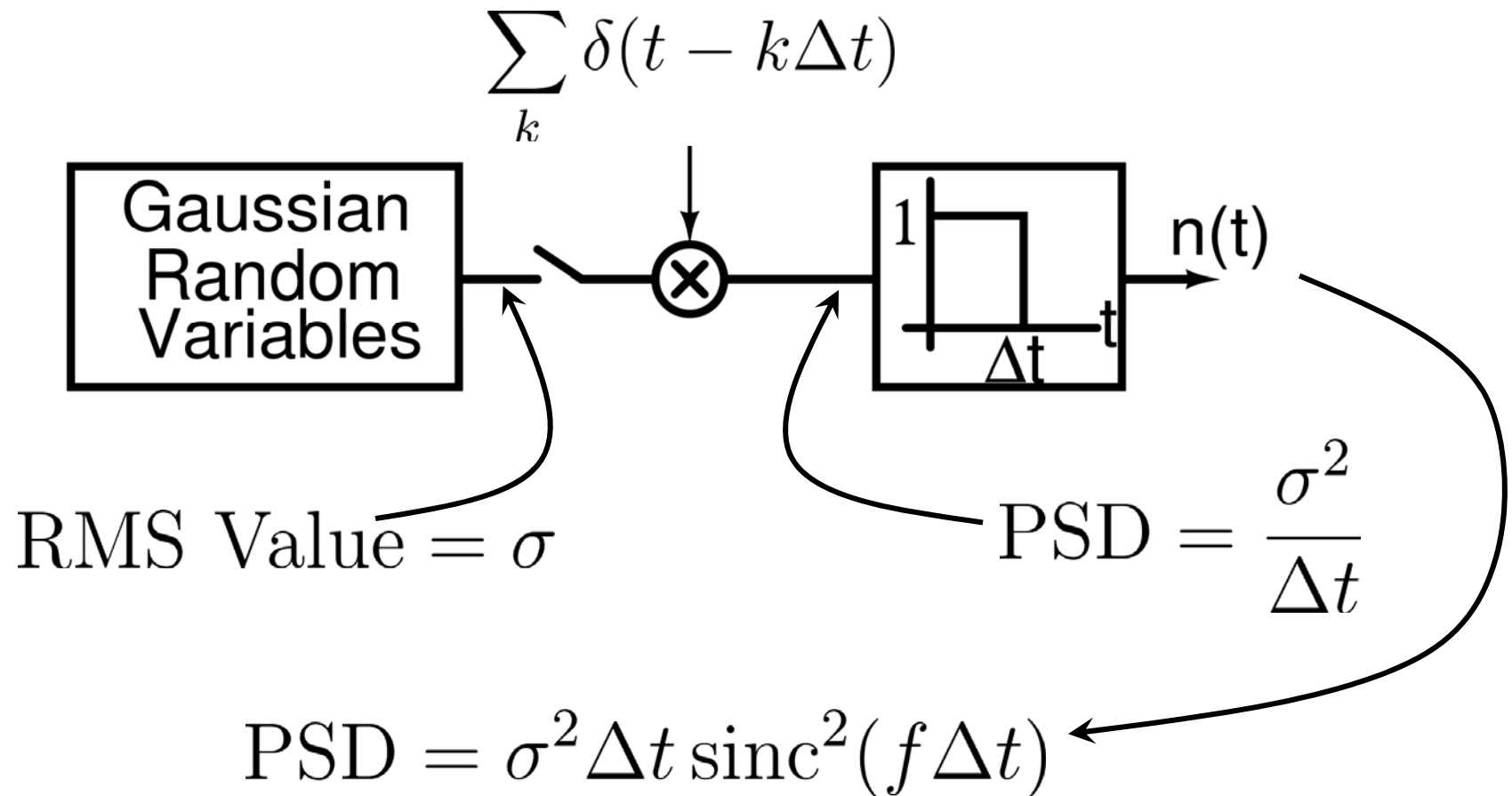

Generating White Noise

 



Simple Example

 

Scales noise voltages and currents by 100


Choosing Analyses -- Virtuoso® Analog Desig...
 OK Cancel Defaults Apply Help
 Analysis tran dc ac noise
 xf sens dcmatch stb
 pz sp envlp pss
 pac pstb pnoise pxf
 psp qpss qpac qpnoise
 qpxf qpss hb hbac
 hbnoise measure
 Transient Analysis
 Stop Time 200m
 Accuracy Defaults (empreset)
 conservative moderate liberal
 Transient Noise
 Noise Fmax 1e6
 Noise Fmin 1
 Noise Seed 1
 Noise Scale 100
 Noise Tmin
 Noise Update step fmax
 Multiple Runs
 Number of Runs 100
 Noise Contribution on off
 Instance List [] Select Clear
 Dynamic Parameter
 Enabled Options...

Simple Example

  

```
[P, f] = pwelch(0.01*vn,rectwin(Nfft),0,Nfft,fs)
```

Second Order CTDSM Example

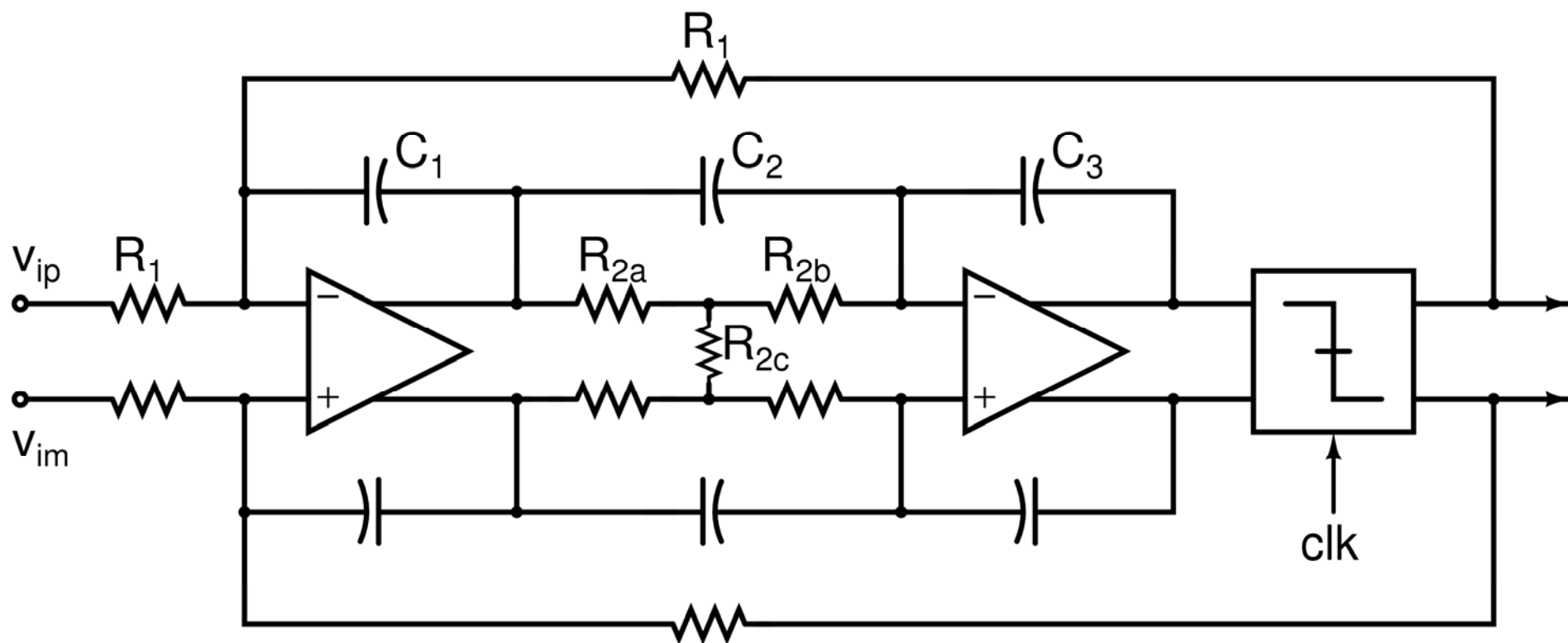

400 kHz sampling rate


Not amenable to periodic noise analysis

Delta Sigma Modulator Noise


- In-band noise dominated by thermal and 1-by-f noise
- Quantization noise should be made lower by at least 12-15 dB
- Virtually all noise should come from the loop filter

Opamp Schematic

Comparator and Clock Waveforms

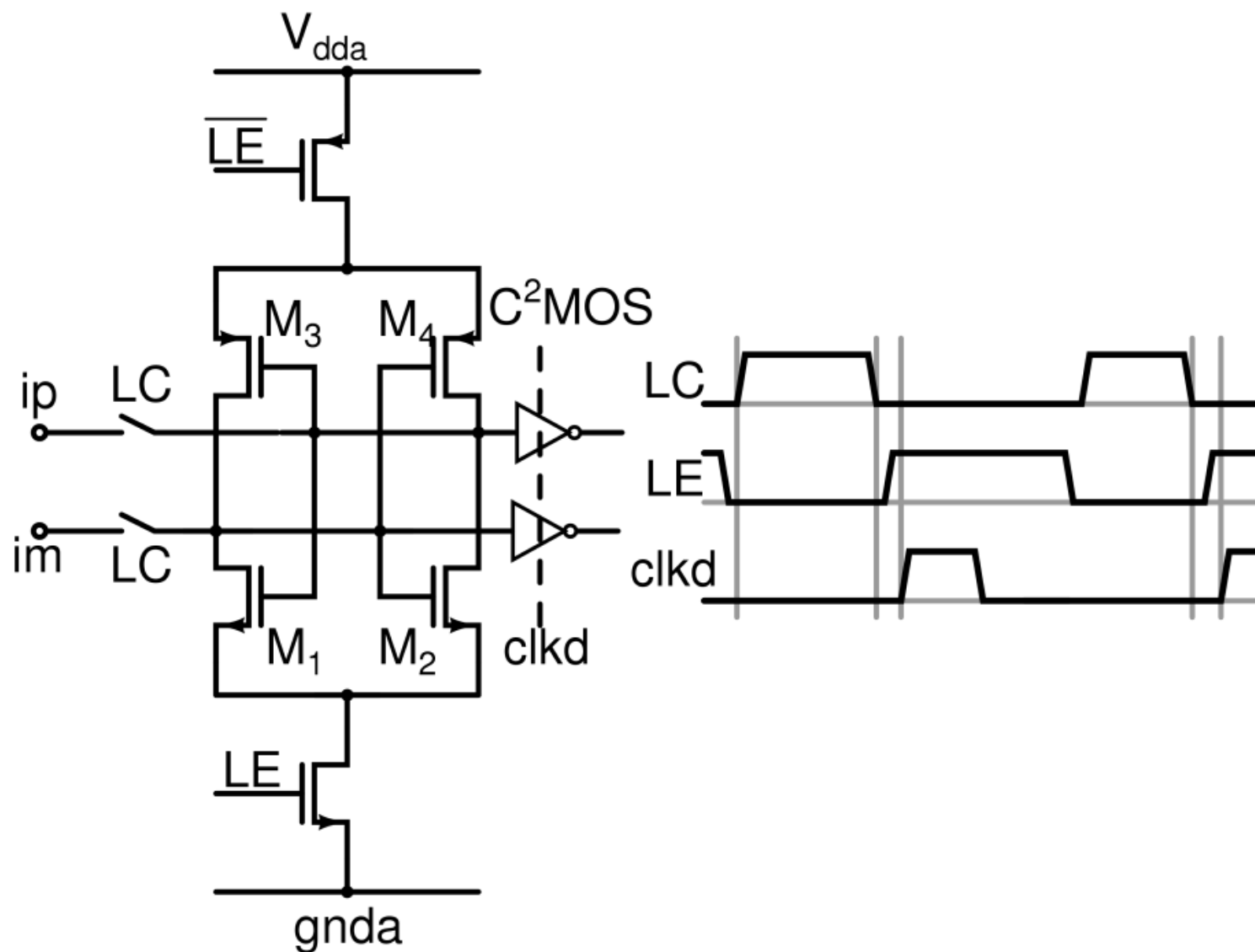


Delta Sigma Example

 

$\Delta\Sigma$ Noise Quick Simulation

- Transient noise
 - Computationally expensive
- Periodic Noise is very fast
 - Delta Sigma ADCs do not lend themselves easily to periodic noise analysis (PNOISE)
 - PSS difficulties due to the quantizer

CTDSM : Using PNoise

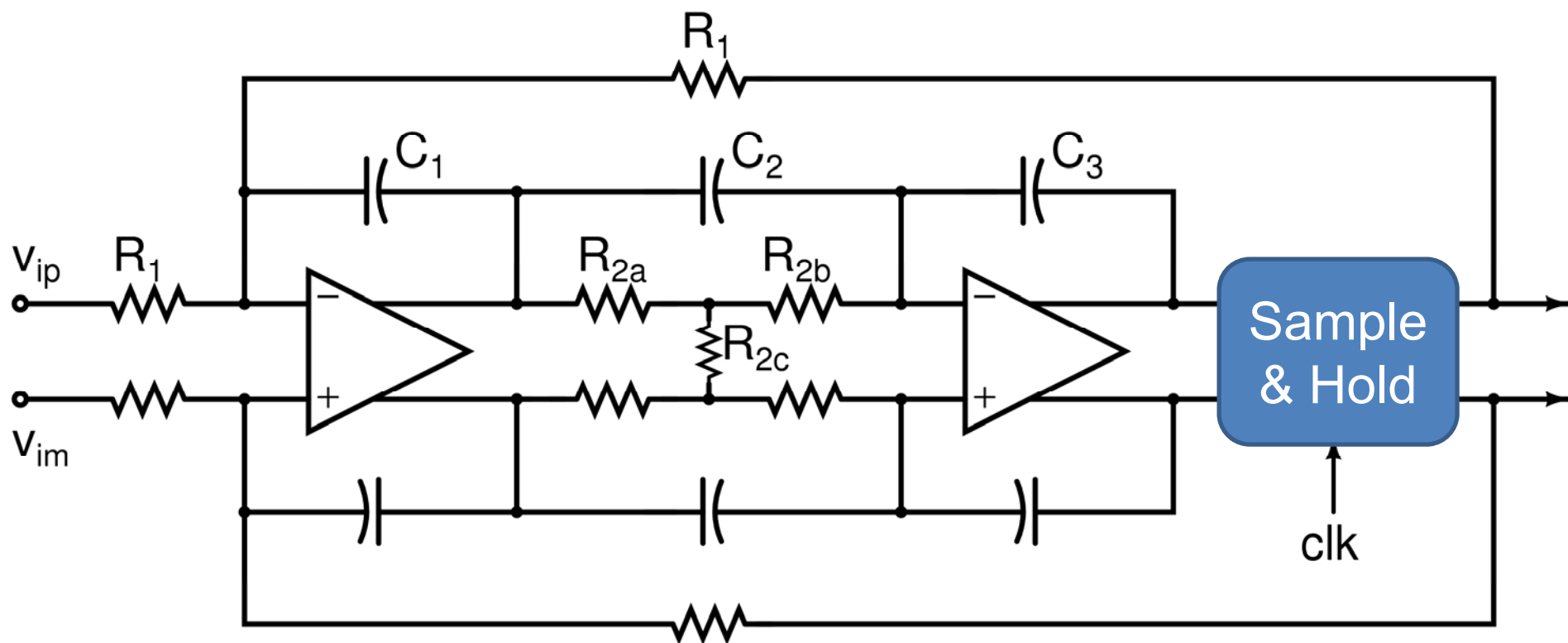

Replace comparator with Sample & Hold
CTDSM becomes LPTV

Pnoise Setup


The screenshot shows the 'Periodic Noise Analysis' dialog box. Key settings are highlighted with red circles and arrows:

- PSS Beat Frequency (Hz):** Set to 400K. An arrow points to the text 'LPTV fundamental frequency'.
- Sweep is currently absolute:** A checkbox that is checked, circled in red.
- Maximum sideband:** Set to 10. An arrow points to the text 'Aliases noise from 10 sidebands'.

Other visible settings include:

- Multiple pnoise:**
- Sweeptype:** default
- Output Frequency Sweep Range (Hz):** Start: 1, Stop: 1e4
- Sweep Type:** Logarithmic
- Points Per Decade:** 11
- Number of Steps:** (unchecked)
- Add Specific Points:**
- Sidebands:** Maximum sideband: 10. Note: When using shooting engine, default value is 7.
- Output:** voltage
- Positive Output Node:** /op
- Negative Output Node:** /om
- Input Source:** voltage
- Input Voltage Source:** /v2
- Reference Side-Band:** $|f(in)| = |f(out) + \text{refsideband} * \text{fund}|$
- Enter in field:** (empty)

Delta Sigma Example with PNoise

 

Summary

- Data Converter Overview
 - Simulation in Flash and Pipeline ADCs
- Spectral analysis in ADCs
 - Windowing
- Simulation Techniques for $\Delta\Sigma$ ADCs
 - In-band SNR estimation
 - Determining NTF
- Use of RF analyses in data converter simulations
 - STF and Noise simulations

Closing Remarks

- Every ADC/DAC architecture
 - own design **and simulation** challenges
- Analysis and design iteration
 - behavioral models/simulation
- Design debug
 - mixture of tx level and macromodels
- Innovation
 - e.g : exploit RF analyses of commercial tools to reduce simulation times

References

- General Data Converter Reading
 - M. Gustavsson, J. Wikner & N. Tan, “CMOS Data Converters for Communications”, *Springer*
 - R. Jacob Baker, “CMOS : Mixed Signal Circuit Design”, *IEEE Press*
- Flash and Pipeline ADCs
 - R.van de Plassche : “CMOS Integrated Analog-to-Digital and Digital-to-Analog Converters”, *Springer*
- Delta Sigma Data Converters
 - R.Schreier, S.Norsworthy and G.Temes, “Delta-Sigma Data Converters : Theory, Design and Simulation”, *IEEE Press*
 - R.Schreier and G.Temes, “Understanding Delta-Sigma Data Converters”, *Wiley*
 - J.Cherry, “Theory, Practice, and Fundamental Performance Limits of High-Speed Data Conversion Using Continuous-Time Delta-Sigma Modulators”, PhD Dissertation <http://www.dissonance.com>

References

- RF analyses background
 - K.Kundert, “Introduction to RF Simulation and its Applications”, *IEEE Journal of Solid State Circuits*, Sept 1999.
- Verilog-A Macromodels
 - White papers at <http://www.designers-guide.org>
- Macromodeling Tools
 - MATLAB and Simulink
 - The Schreier Delta-Sigma Toolbox
 - CPPSim <http://cppsim.com>