

---

# ADC-Based Serial Links: Design and Analysis




Samuel Palermo  
[spalermo@tamu.edu](mailto:spalermo@tamu.edu)  
Analog & Mixed-Signal Center  
Texas A&M University

# We Need More Data Bandwidth

## Human-driven traffic growth



Hi definition video conference

 


[Cisco Global Cloud Index 2016]



## Machine-driven traffic growth



Cloud service, big data, IoT

 



Enterprise service

 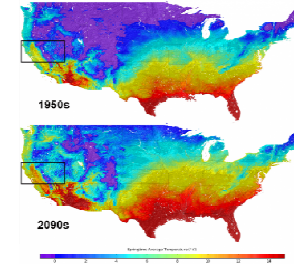

Supercomputer

# Electrical Channel Bandwidth Limitations


## 56Gb/s Legacy Backplane Channel

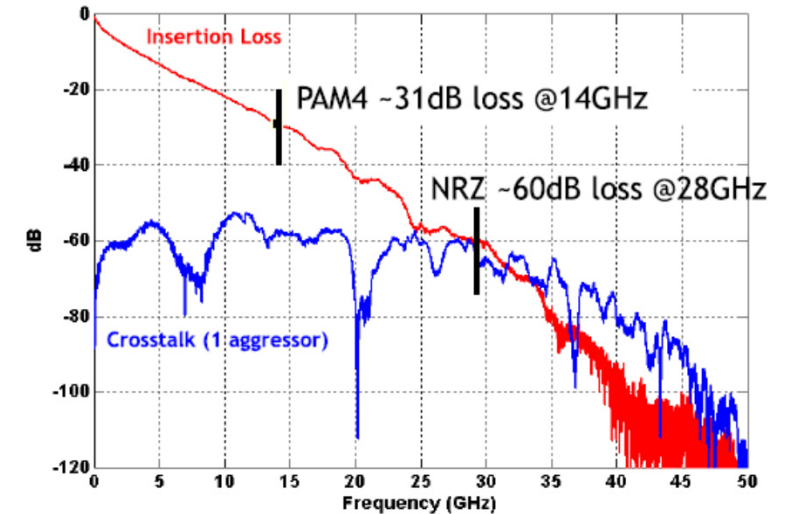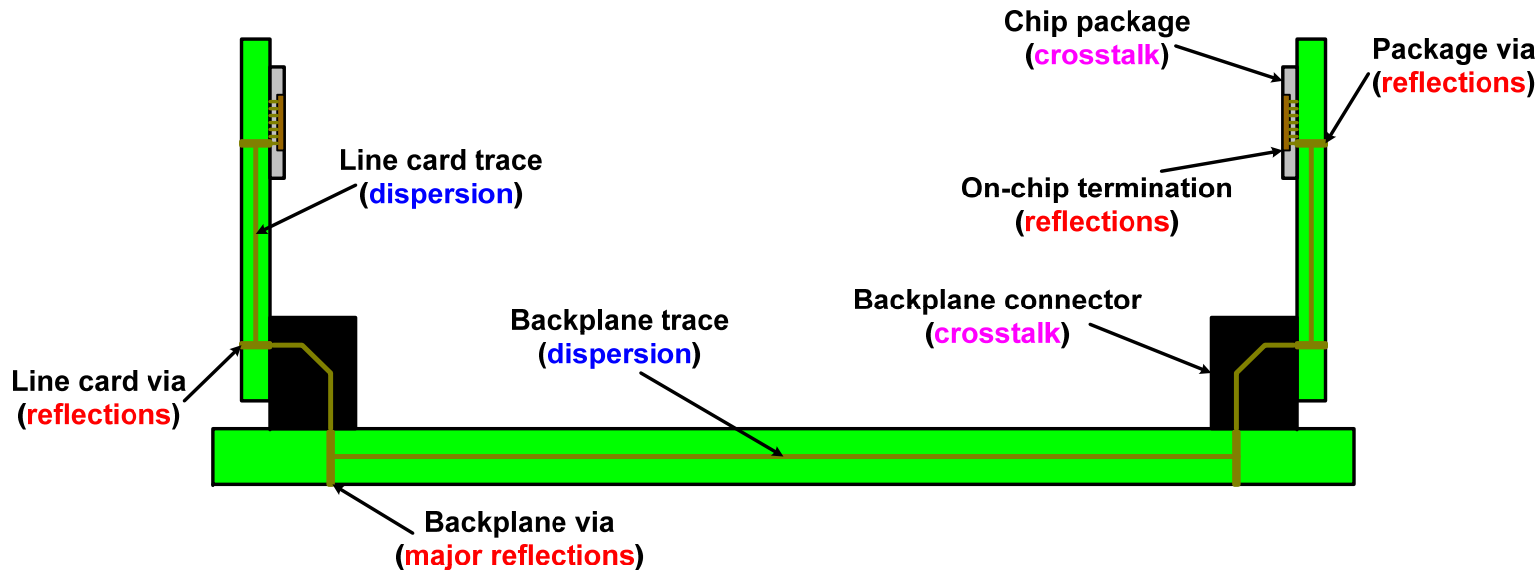


[Frans JSSC 2017]

- Electrical channel bandwidth has not scaled to match I/O bandwidth demands and the CMOS technology speed
- Motivates more spectrally-efficient modulation schemes (PAM4)

## PAM4 Eye Diagram

 

# ADC-Based Receiver Front Ends

 

- ❑ ADC-based receivers perform ISI cancellation in digital domain, allowing for flexible advanced equalization and symbol detection
- ❑ Well suited for more spectrally-efficient modulation schemes (PAM4)
- ❑ Benefit from improved area and power with CMOS scaling
- ❑ Power dissipation of both the ADC and digital equalizer is a major issue

# Outline


---

- ADC Resolution Requirements & Topologies
- Key ADC Circuits
- ADC Calibration Techniques
- Digital Equalization
- Analog Front-End
- Conclusion

# ADC Resolution Requirements


- The required ADC resolution is a function of
  - Channel loss
  - Amount of TX and RX front-end analog equalization
  - Modulation scheme
  - Required BER (FEC) →
  
- Quantization noise must be accurately modeled to select the necessary ADC resolution

## Impact of FEC on RX Front-End Raw BER

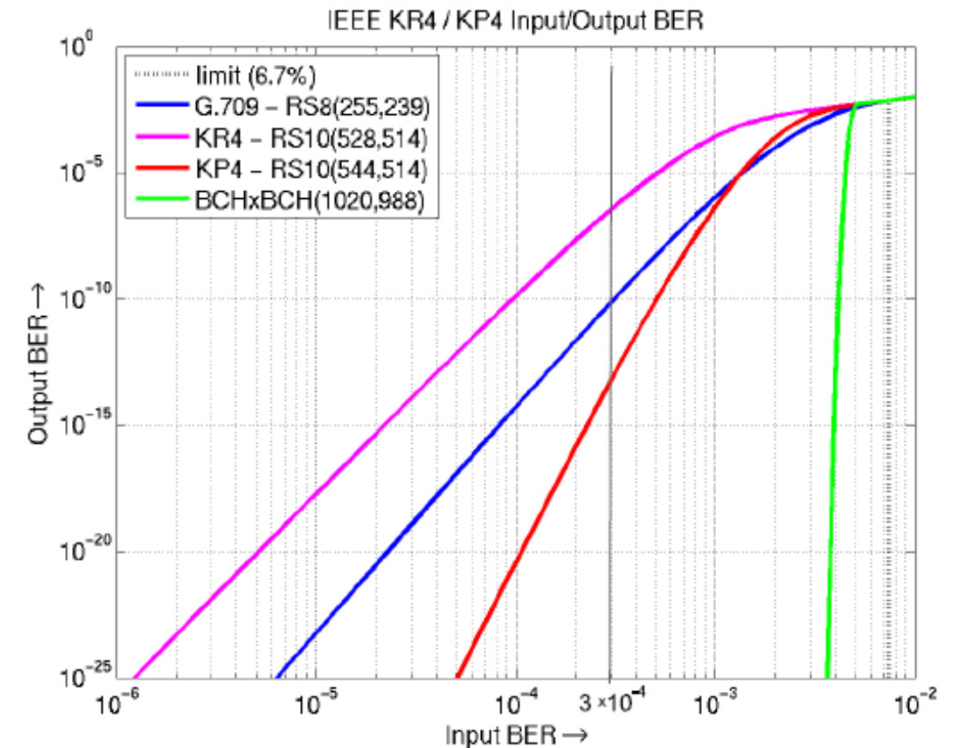

[Frans JSSC 2017]




# Quantization Distortion Modeling

 

- Quantization noise is shaped by RX-side digital FFE
- Allows for direct convolution w/ other noise/distortion PDFs
  - Assuming small INL/DNL and front-end non-linearity



# 56Gb/s PAM4 Example

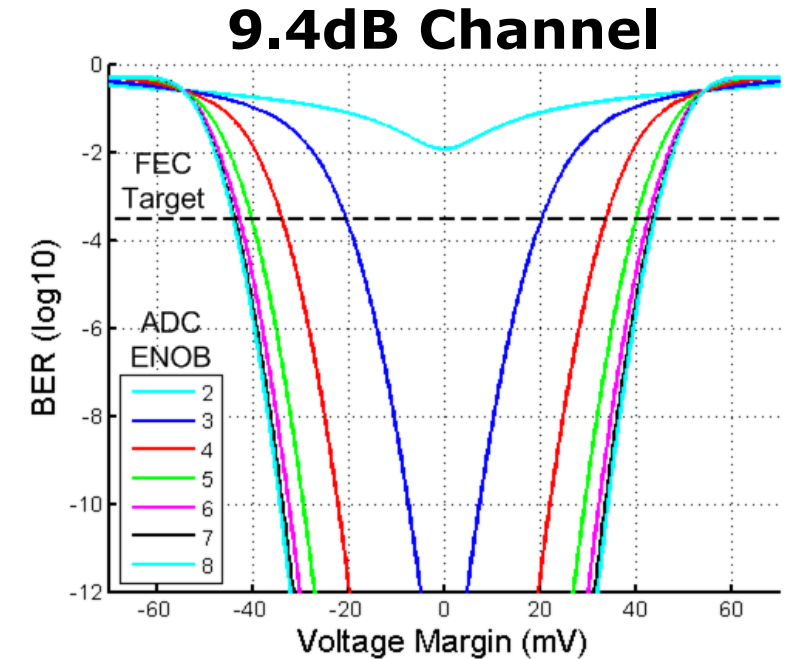  

- High-loss channel requires 3-4b ENOB for FEC BER ( $3e-4$ ) and  $>5b$  ENOB to achieve a  $1e-12$  raw BER
- Low-loss channel can achieve  $1e-12$  raw BER with only 3b ENOB
- Motivates configurable resolution ADCs

## Key Simulator Settings

- 3-tap TX w/ 1Vpp swing
- CTLE/AGC FE w/ 7.4dB peaking and 16GHz BW
- 400mV ADC FSR
- Digital 14-tap FFE & 1-tap DFE
- $3mV_{rms}$  ADC input noise
- $RJ=300fs_{rms}$
- No TI effects (more later)



# Recent ADC-Based XCVR/RX




Specification	Frans JSSC'17	Gopalakrishnan ISSCC'16	Cui ISSCC'16	Rylov ISSCC'16	Shafik JSSC'16	Zhang JSSC'15
Data Rate (Gb/s)	56	56	32	25	10	11.5
Modulation	PAM4	PAM4	PAM4	PAM2	PAM2	PAM2
ADC Sample Rate (GS/s)	28	28	16	25	10	11.5
ADC Structure	<b>Asynchronous SAR</b>	<b>Synchronous SAR w/ Redundancy</b>	<b>Asynchronous SAR w/ Redundancy</b>	<b>Flash</b>	<b>Asynchronous SAR</b>	<b>Rectifying Flash</b>
ADC Resolution (bit)	<b>8</b>	<b>7</b>	<b>8</b>	<b>5</b>	<b>6</b>	<b>6</b>
ADC ENOB at Nyquist (bit)	<b>4.9</b>	<b>4.9</b>	<b>5.85</b>	<b>3.8</b>	<b>3.9</b>	<b>4.6</b>
ADC TI Factor	32	32	32	4	32	4
TX Swing ( $V_{ppd}$ )	1.2	1.4	NA	NA	NA	NA
TX FFE Taps	3	3	NA	NA	NA	NA
RX FE Equalization	CTLE w/ 7dB Peaking	CTLE w/ 8dB Peaking	CTLE w/ 7dB Peaking	CTLE	Embedded 3-tap FFE in ADC	CTLE w/ 6dB Peaking
RX Digital FFE Taps	<b>24</b>	<b>Multiple</b>	<b>NA</b>	<b>8</b>	<b>4</b>	<b>Multiple</b>
RX Digital DFE Taps	<b>1</b>	<b>1</b>	<b>NA</b>	<b>8</b>	<b>3</b>	<b>Multiple</b>
Max Channel Loss (dB)	-31	-35	-32	-40	-36.4	-34
TX Power (mW)	140	NA	NA	NA	NA	NA
ADC/FE Power (mW)	370	NA	320	310	79	195
DSP Power (mW)	NA	NA	NA	143	10	NA
Clocking Power (mW)	40	NA	NA	NA	NA	NA
Area (mm <sup>2</sup> )	2.8	30.87	0.89	0.39	0.81	0.82
Technology	16nm FinFET	28nm	28nm	32nm SOI	65nm	40nm

# Some Observations

---


- PAM2 systems are generally implementing 5-6b ADCs and achieving close to 4-4.5b ENOB at Nyquist
  - A mixture of flash and SAR architectures are utilized
- PAM2 digital equalization enables robust implementation of RX-side FFE and multiple DFE taps
- PAM4 systems are generally implementing 7-8b ADCs and achieving close to 5-6b ENOB at Nyquist
  - SAR architectures are well suited for this resolution
- PAM4 digital equalization employs large tap count FFEs to effectively cancel residual ISI, but few DFE taps due to complexity

# Common ADC Topologies

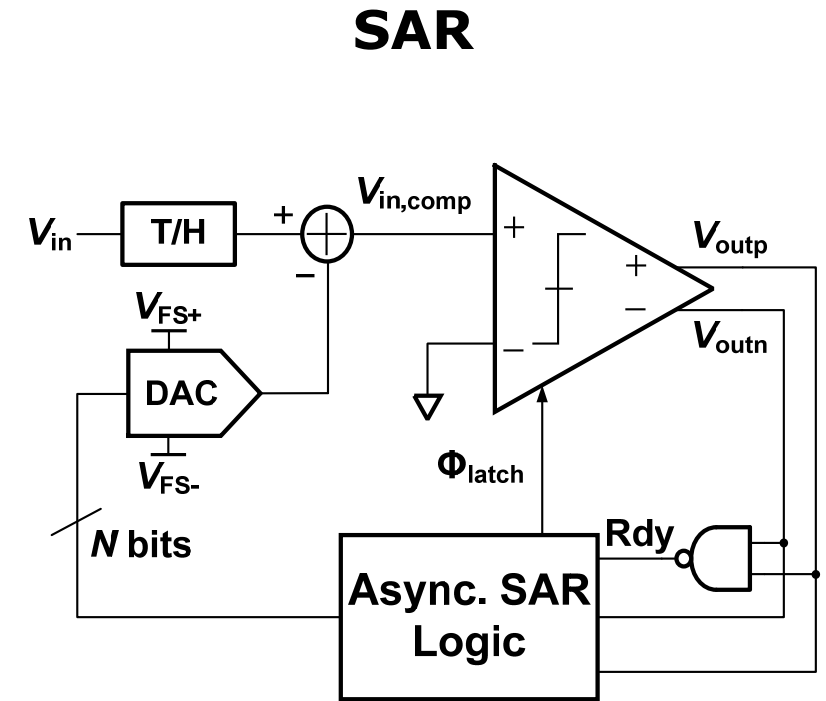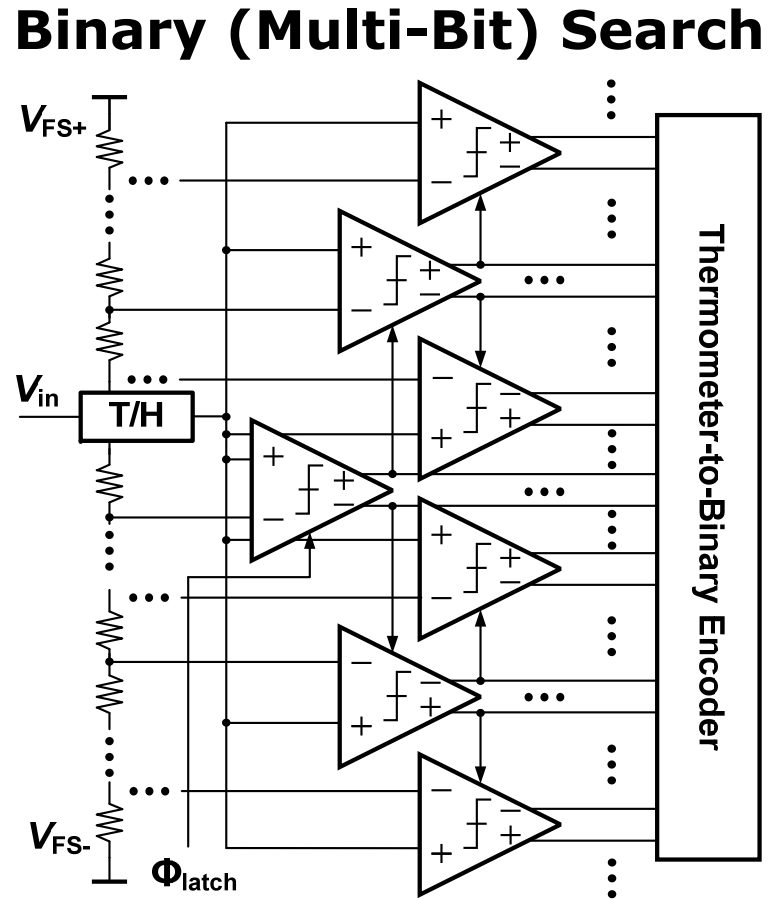 

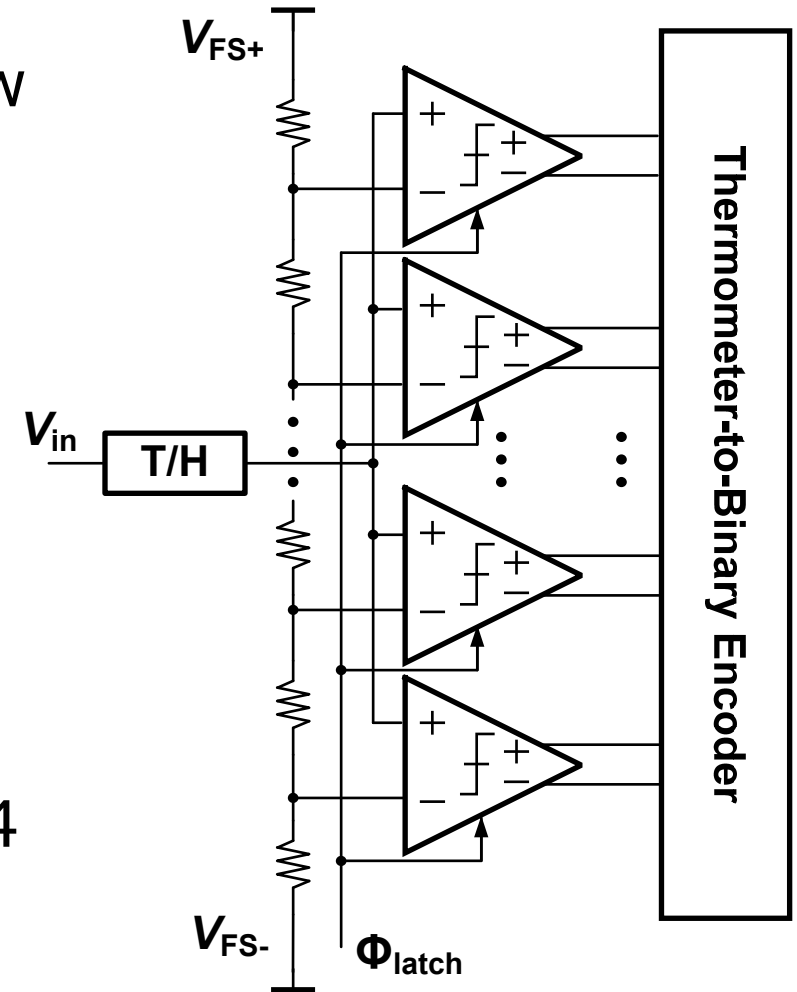
# Flash ADC

- ❑ Comparators at each reference level allow for simultaneous parallel conversion
- ❑ Single cycle operation allows for high speeds
  - Typical interleave factors of 4-8
- ❑ Main downside is large comparator count
  - Rectifying flash architectures can reduce this
- ❑ Flash ADC is a reasonable choice for PAM2, but resolution is a bit low for PAM4



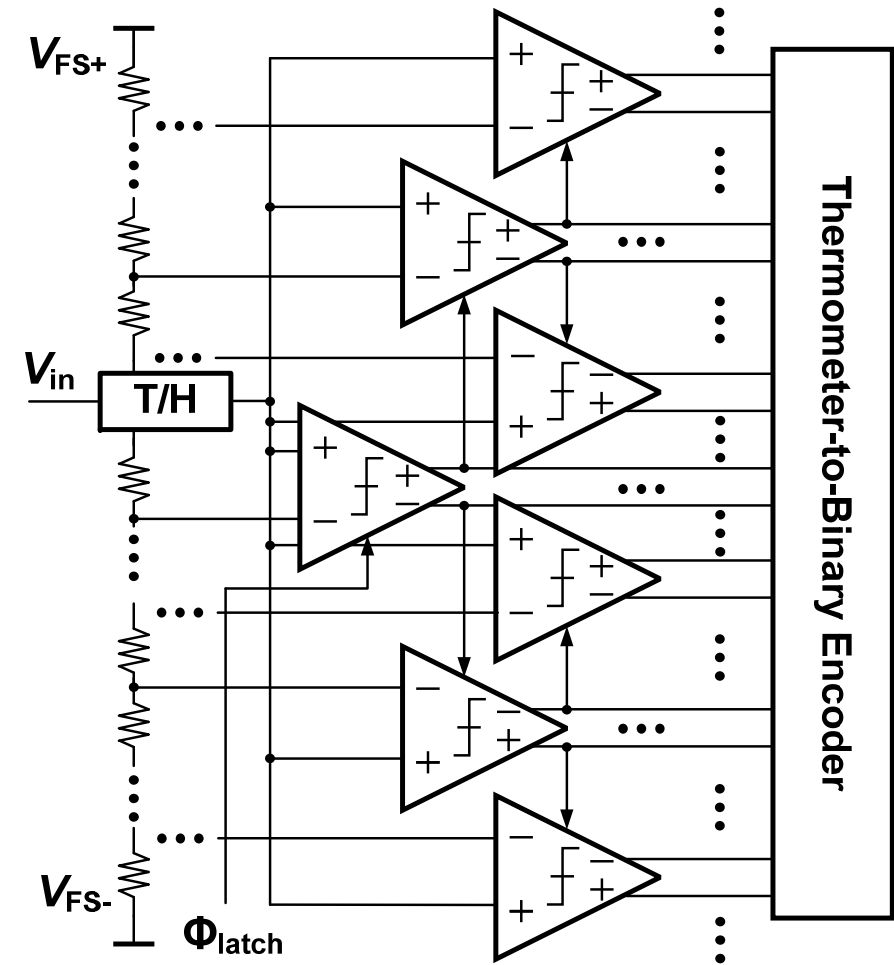
# Binary (Multi-Bit) Search ADC

- ❑ Binary (multi-bit) search ADCs combine desirable properties of flash & SAR ADCs
- ❑ Efficient binary search algorithm allows only necessary comparator evaluation
- ❑ Avoids the DAC settling and logic delay present in SAR ADCs, but slower than flash due to serial comparator evaluation
- ❑ Good choice for PAM2 applications, area may be a bit high for PAM4 applications



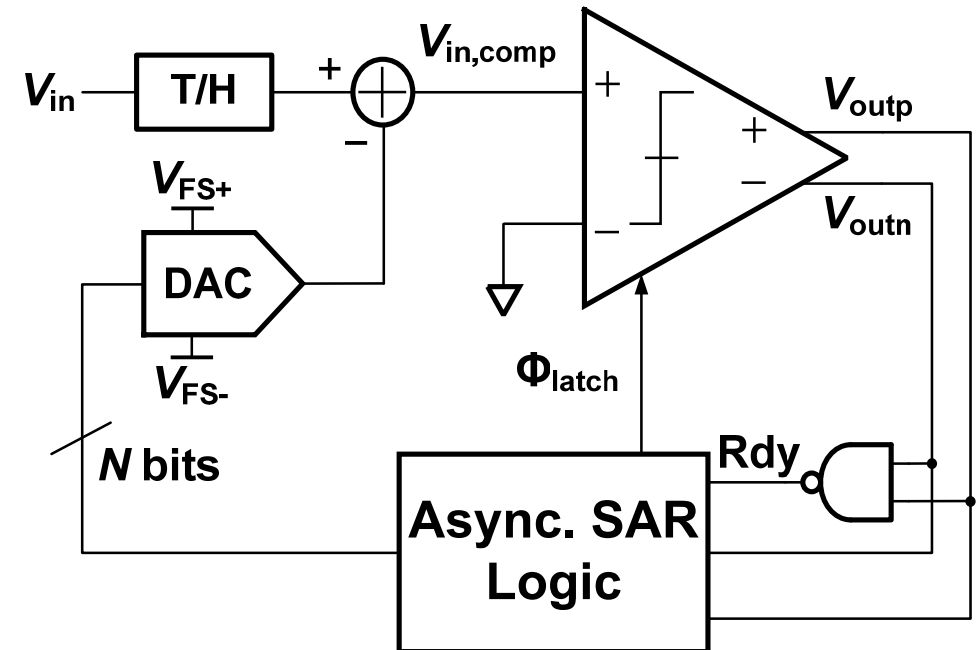
# SAR ADC

- ❑ Performs a binary search conversion over multiple clock cycles
- ❑ Simplest implementations only require one comparator per unit ADC
- ❑ Slower unit ADC relative to flash/binary search
  - Typical interleave factors of 32-64
- ❑ Excellent choice for 6-8b resolution to support both PAM2 and PAM4
- ❑ The dominant architecture for PAM4 ADC-based receivers


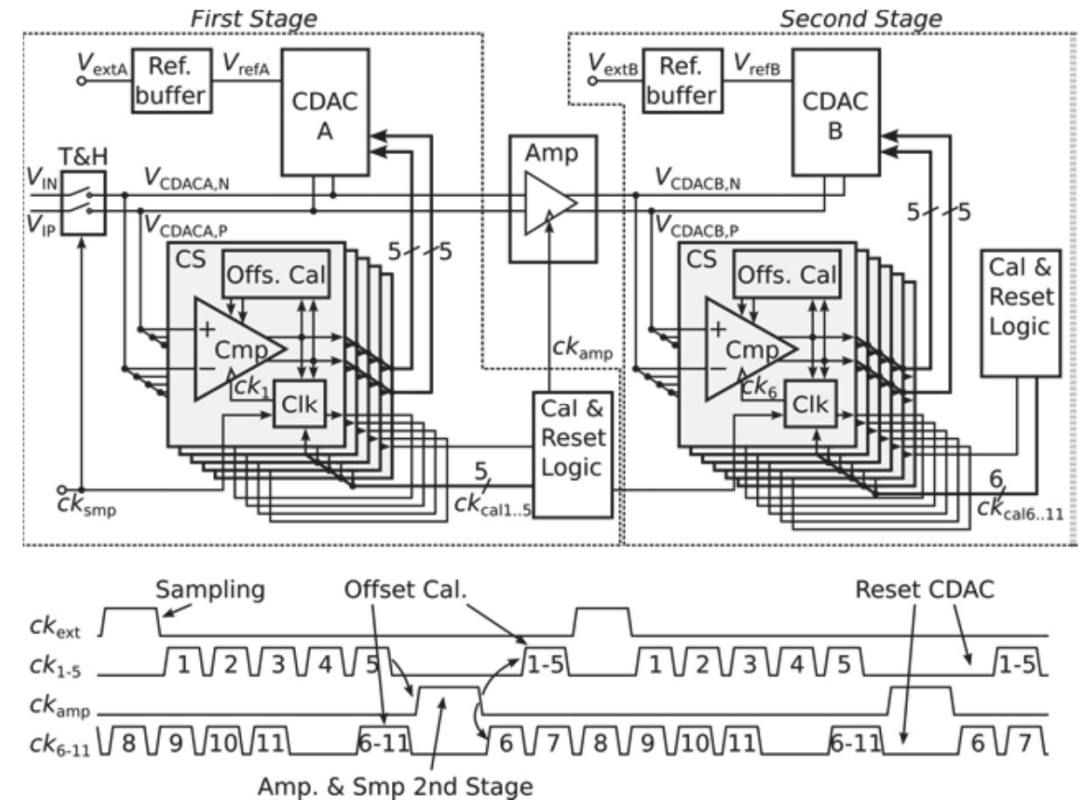
# Pipeline SAR ADC

- Looking forward, pipeline SAR architectures are attractive in order to further push sample rates (100+Gb/s)
- Pipelining allows for higher sample rate and fewer unit ADCs
- Inter-stage gain block can reduce impact of comparator noise to allow for higher resolution




[Kull ISSCC 2017]



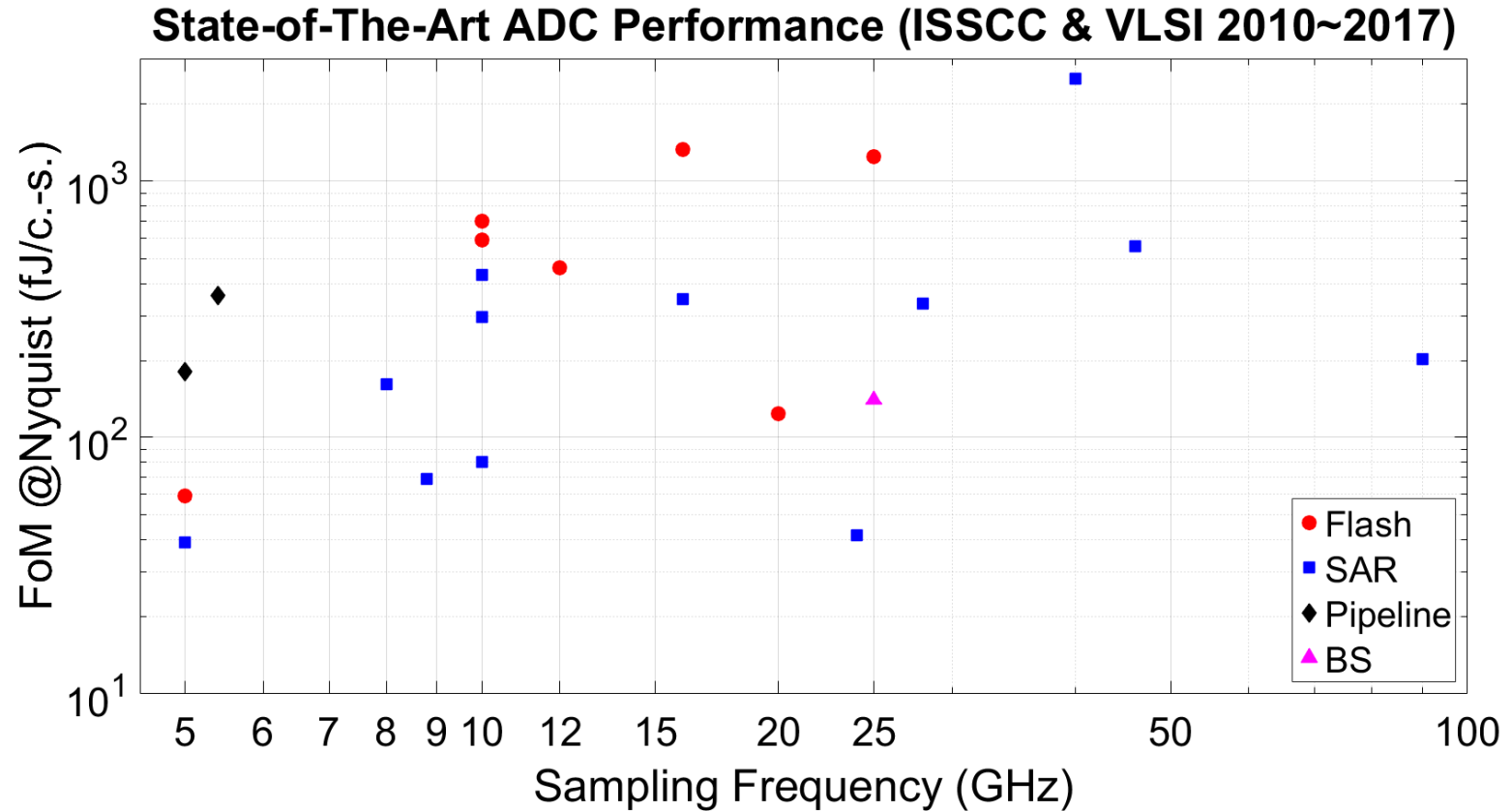
# State-of-the-Art ADC Performance

$$FoM = \frac{Power}{2^{ENOB} \cdot f_s}$$



- SAR is the most popular architecture and provides best power efficiency for >10GS/s 6~8b ADC design

# Time-Interleaved ADCs

 


- ❑ Wireline ADCs are time-interleaved to achieve high sample rates
- ❑ As the SAR ADC is the dominant wireline ADC architecture, we will walk through it's key circuits

# Outline

---



- ADC Resolution Requirements & Topologies
- Key ADC Circuits
- ADC Calibration Techniques
- Digital Equalization
- Analog Front-End
- Conclusion

# Time-Interleaved ADCs

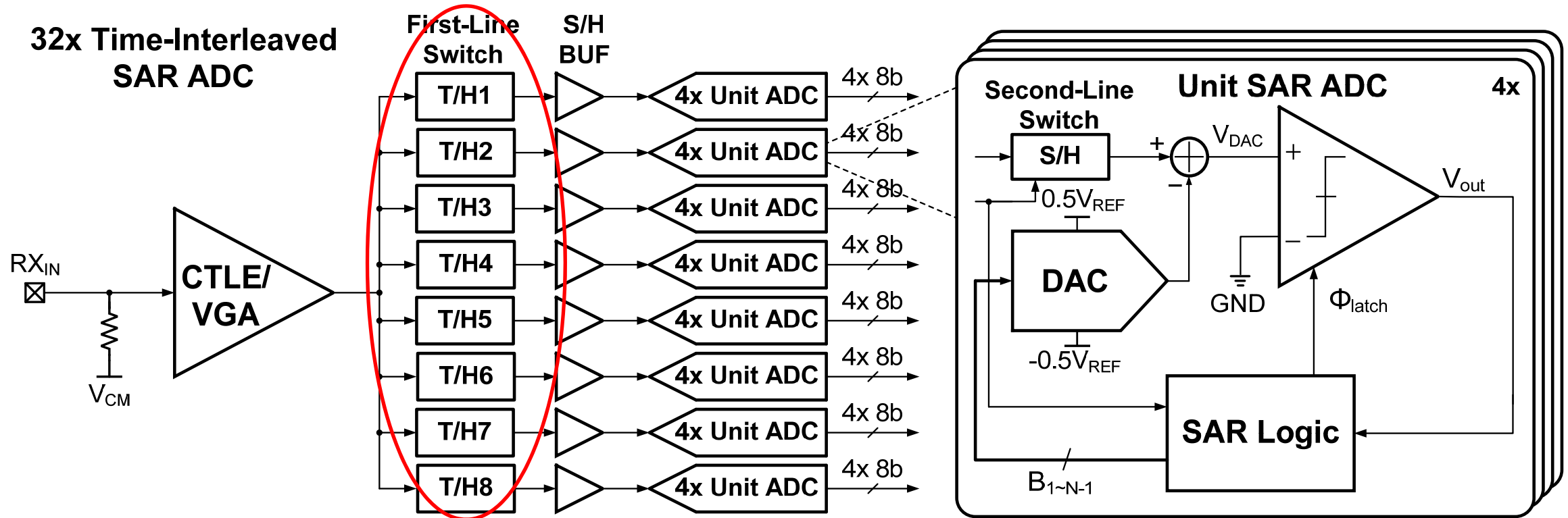

- Because we can only generate a relatively small number of low-jitter, low-skew clock phases (4-16), input sampling is performed in 2 stages
- The input T/H must track and sample (hold) the full-bandwidth input signal for further sampling to the unit ADCs

# Input T/H

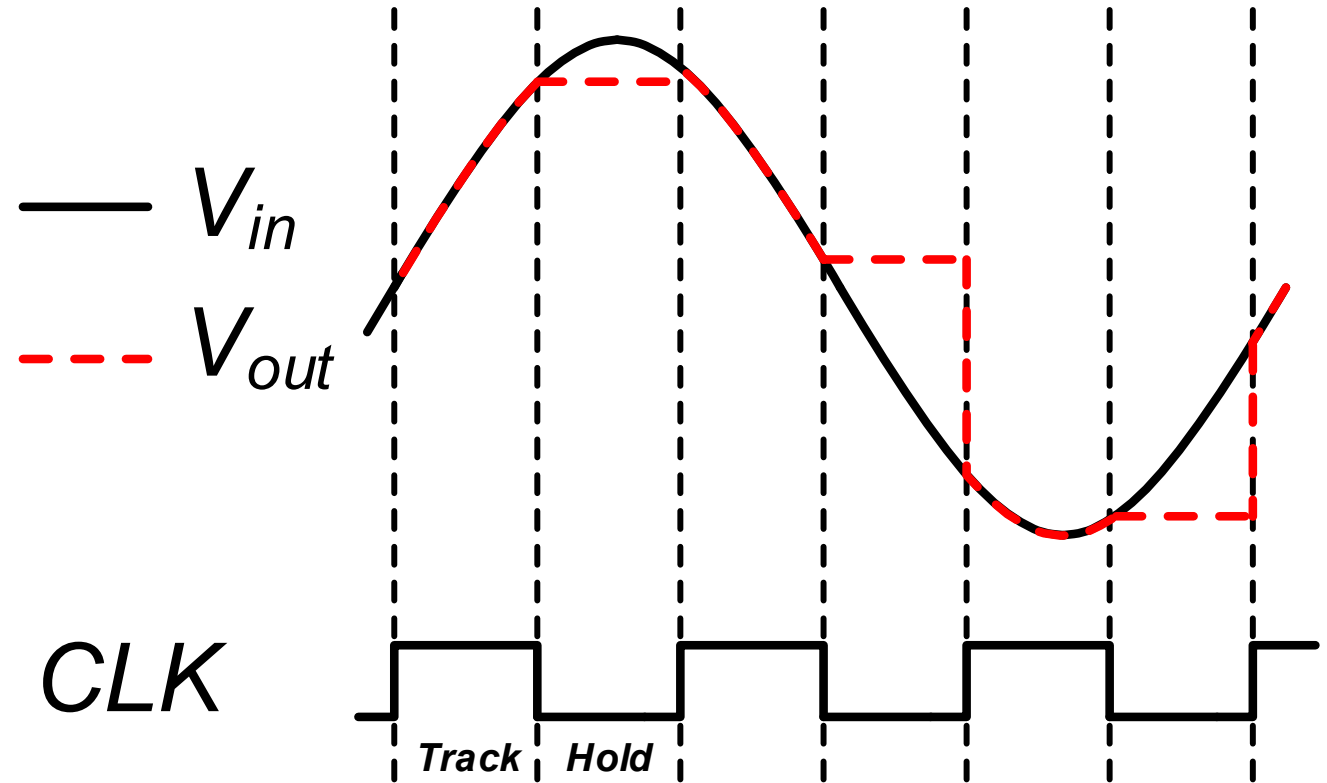 

## Issues


- On-resistance
- Signal-dependent hold instant
- Hold-mode input feedthrough

# Signal-Dependent On-Resistance & Sample Point

During track-mode, the MOS operates in triode

$$I_D = \mu C_{OX} \frac{W}{L} \left( V_{GS} - V_{TH} - \frac{V_{DS}}{2} \right) V_{DS}$$

$$R_{ON} \cong \left[ \frac{dI_D(\text{triode})}{dV_{DS}} \Big|_{V_{DS} \rightarrow 0} \right]^{-1} = \frac{1}{\mu C_{OX} \frac{W}{L} (V_{CLK} - V_{IN} - V_{TH})}$$

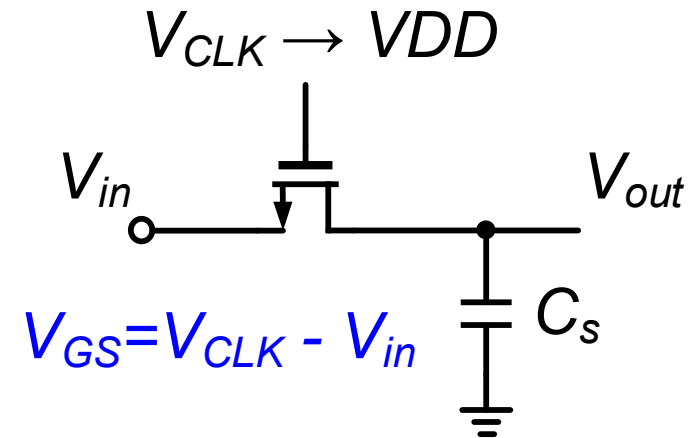

**Track - Mode**

## □ Issues


- $R_{ON}$  is modulated by  $V_{IN} \rightarrow$  Distortion
- Signal dependent hold instant, occurs when  $V_{CLK} = V_{IN} + V_{TH}$

# Signal-Dependent On-Resistance & Sample Point

The signal is sampled when

$$V_{CLK} = V_{IN} + V_{TH}$$


- The sampling clock fall time should be much faster than the maximum  $dV_{IN}/dt$  to minimize the sampling point mismatch

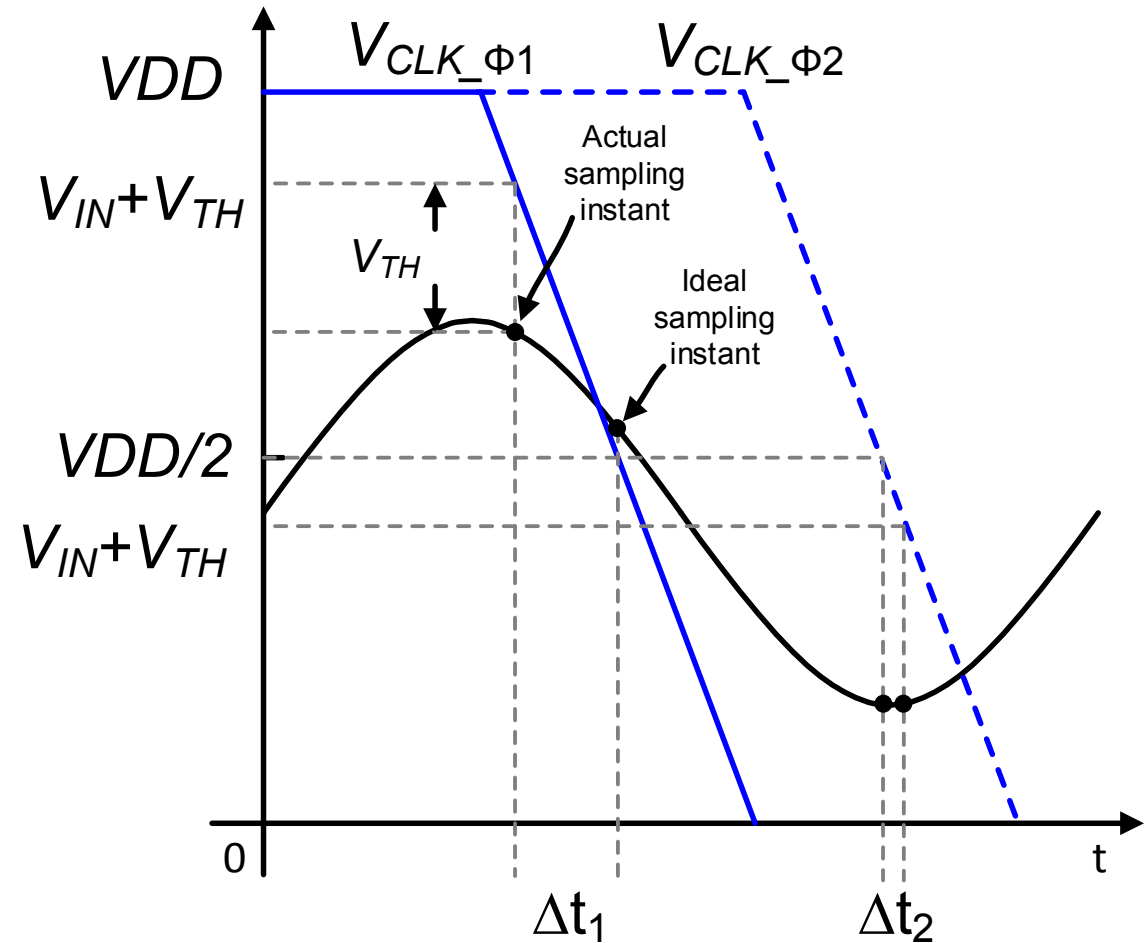

[Razavi 1995]




# Bootstrapped Switch

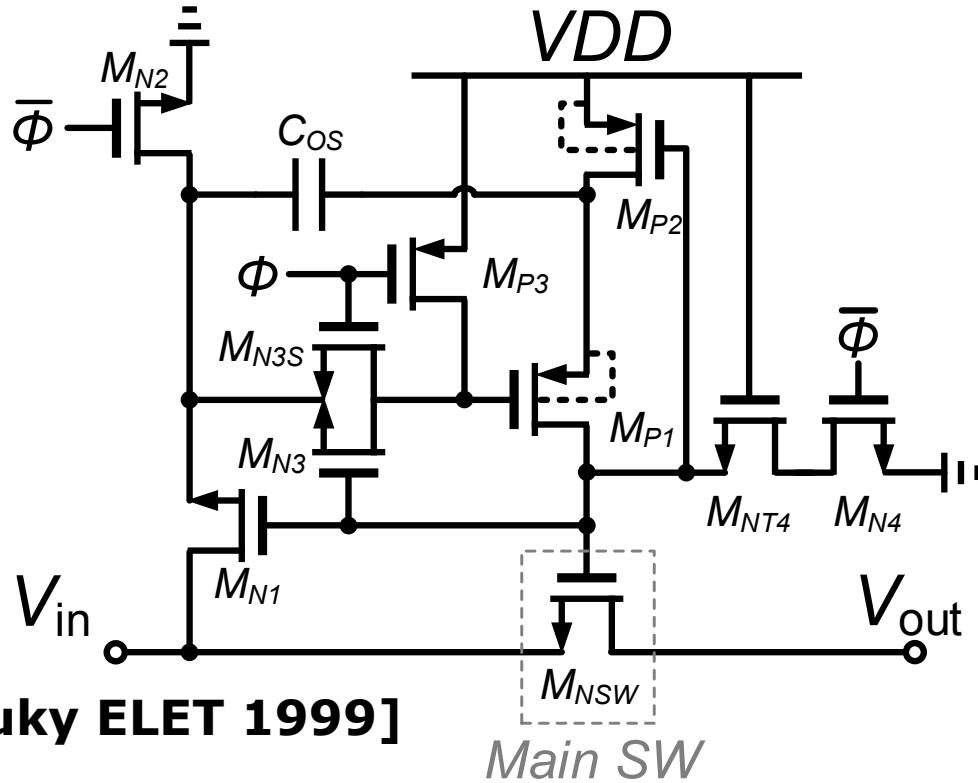


[Dessouky ELET 1999]

Main SW

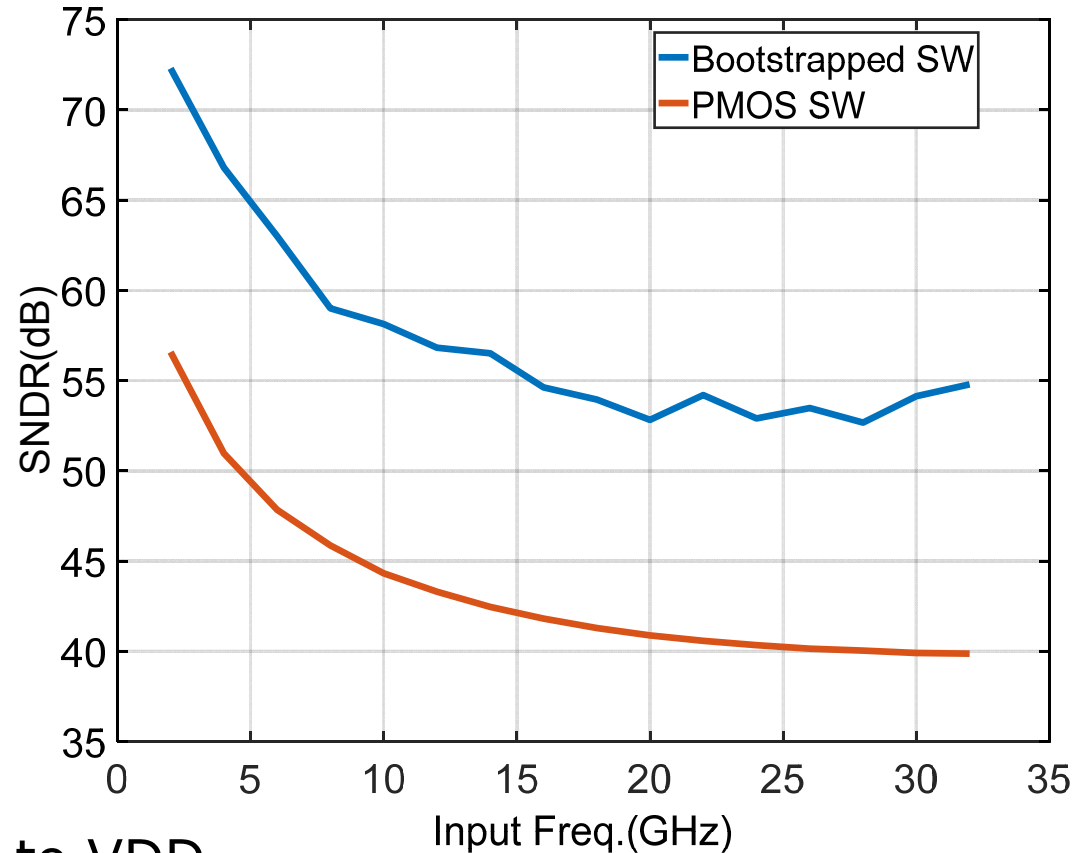


- $\Phi = 0$ , switch off and  $C_{OS}$  is precharged to  $V_{DD}$
- $\Phi = 1$ , main switch is on with constant  $V_{GS} = V_{DD}$  and, to first order, both  $R_{on}$  and sampling instant are signal independent

# Hold-Mode Feedthrough

 


- High-pass feedthrough paths when switch ideally open

$$\frac{V_{OUT}}{V_{IN}} = \frac{C_{gd}R \cdot s}{(C_{gs} + C_{gd})R \cdot s + 1} \Bigg|_{C_s \gg C_{gs,gd}}$$

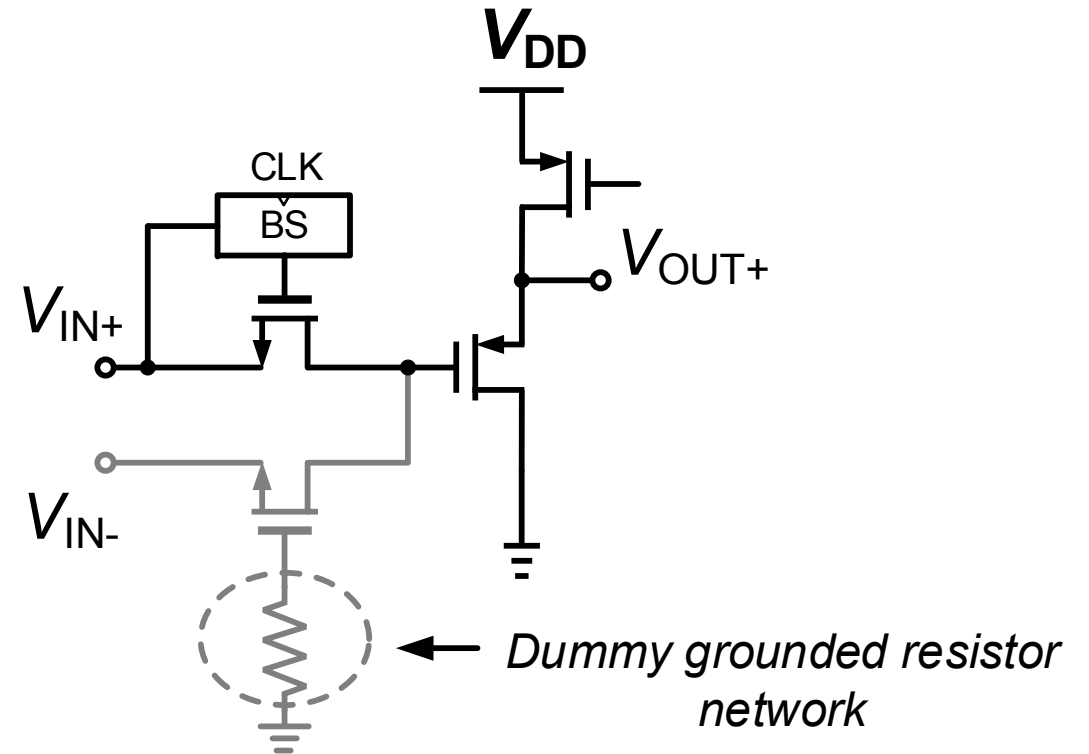


- Using a dummy path to generate an opposite feedthrough for cancellation
- Make sure to place a proper impedance on the dummy transistor gate

# How Much Track Time?

 
 
$$v(t) = \underbrace{-\frac{A \cos(\phi - \theta)}{\sqrt{1 + R^2 C^2 \omega^2}} \cdot e^{-\frac{t}{RC}}}_{\text{Initial Transient Response}} + \underbrace{\frac{A \cos(\omega t + \phi - \theta)}{\sqrt{1 + R^2 C^2 \omega^2}}}_{\text{Steady-State Response}} - \underbrace{v_{in}(0) \cdot e^{-\frac{t}{RC}}}_{\text{Worst-Case Natural Response}}$$






$$\tan \theta = RC\omega, v_{in}(0) = -A$$

$$v_{in} = -A \cos(\omega t + \phi)$$


□ The initial transient response (yellow) goes to zero quickly with proper  $N=t/RC$

# How Much Track Time?

   


- ❑ The initial transient response error can be ignored by an 8 bit system when  $N > 7$
- ❑ It is unrealistic to lower the steady-state error by dramatically decreasing RC
  - Often compensated by digital equalizer
  - $N=12$  gives  $\sim 0.7x$  attenuation with a Nyquist input and a common 8-way first-line interleave factor
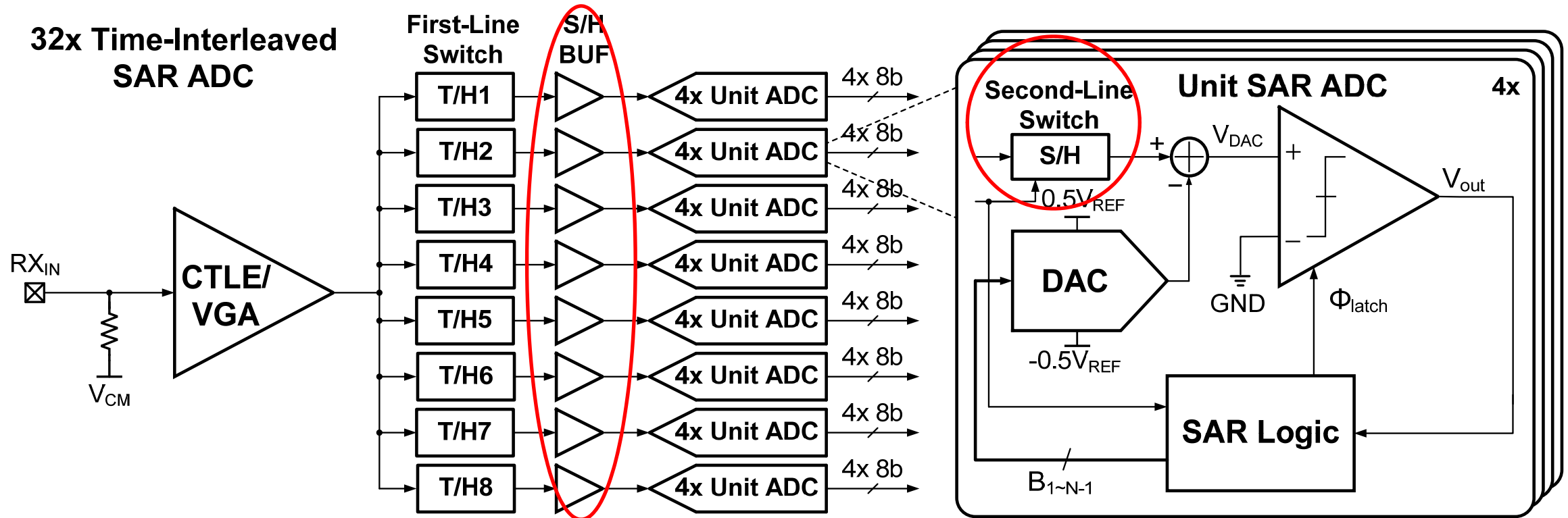
# Time-Interleaved SAR ADC: S/H Buffer & Second-Line Switch



- ❑ Active buffer isolates ADC loading from the bootstrap switch
- ❑ Second-line switch (S/H) output should settle with  $\epsilon < \text{LSB}/2$
- ❑ As this settling is a function of both the buffer bandwidth and switch time constant, let's consider them together

# S/H Buffer & Second-Line Switch

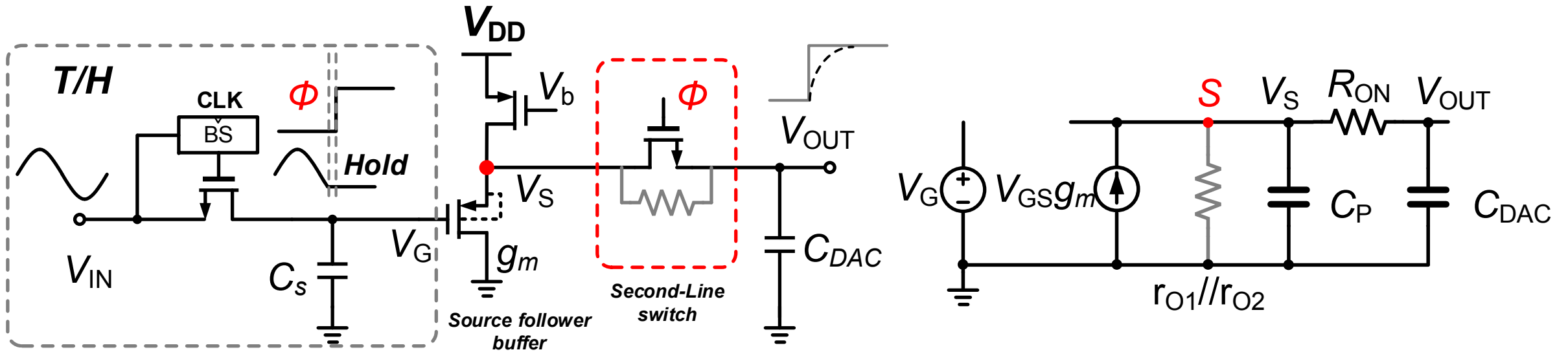

$$C_P \frac{dV_S}{dt} - g_m \cdot V_{GS} + \frac{V_S - V_{OUT}}{R_{ON}} = 0$$

$$V_S = R_{ON} \cdot C_{DAC} \cdot \frac{dV_{OUT}}{dt} + V_{OUT}$$

$$BW \cdot 2\pi = \frac{g_m}{C_P}$$

$$k = \frac{C_P}{C_{DAC}} = 2$$


$$\tau = R_{ON} \cdot C_{DAC} \quad V_{OUT}(0) = 0$$

$$V_S(0) = 1 - \max(|V_G(t) - V_S(t)|)$$

**worst initial condition**

- The settling time of  $V_{OUT}$  is related both to the buffer BW and switch  $\tau$
- The worst case is when  $V_{OUT}$  settles from '0' to max amplitude with a Nyquist input
- Note that  $C_P$  can be larger than  $C_{DAC}$  due to long routing from buffer to unit-ADCs


 
# S/H Buffer & Second-Line Switch: 64GS/s Example



- ❑ For  $\tau=6.25$ , the source follower BW should be larger than 35GHz for 8 bits
- ❑ A smaller  $BW=32\text{GHz}$  allows lower source follower power, but need smaller  $\tau \approx 5$  ps



 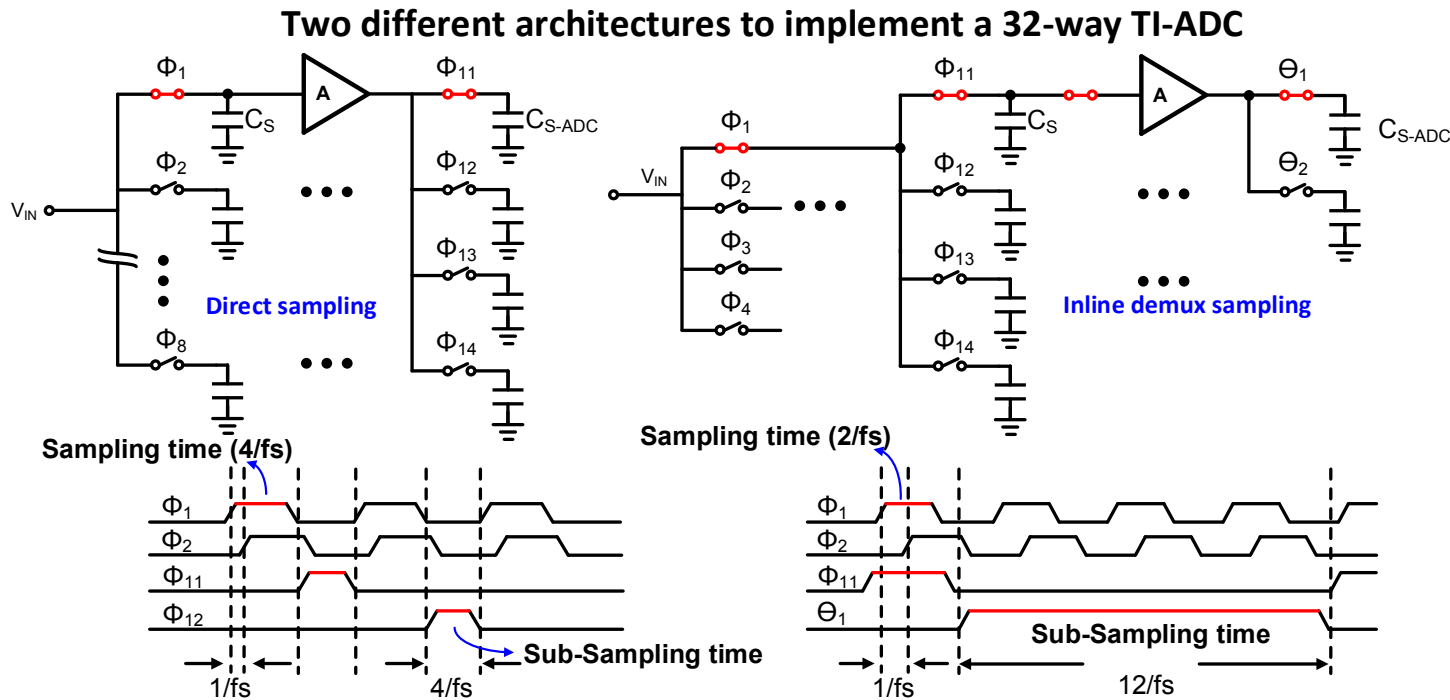
# Time-Interleaving Sampling Architectures




- Direct sampling has better BW due to the shortest path from  $V_{IN}$  to the  $C_{DAC}$ . But the sub-sampling time (second-line SW hold time) is just  $4/f_s$  (50% duty cycle).
- Serialized SW ( $\phi_1, \phi_{11}$ ) lowers the BW of the inline demux arch, but allows for an increased hold time and a relaxed buffer design
  - Note, this often requires a higher sampling clock, which also decreases sampling time

# Time-Interleaved SAR ADC: Unit ADC

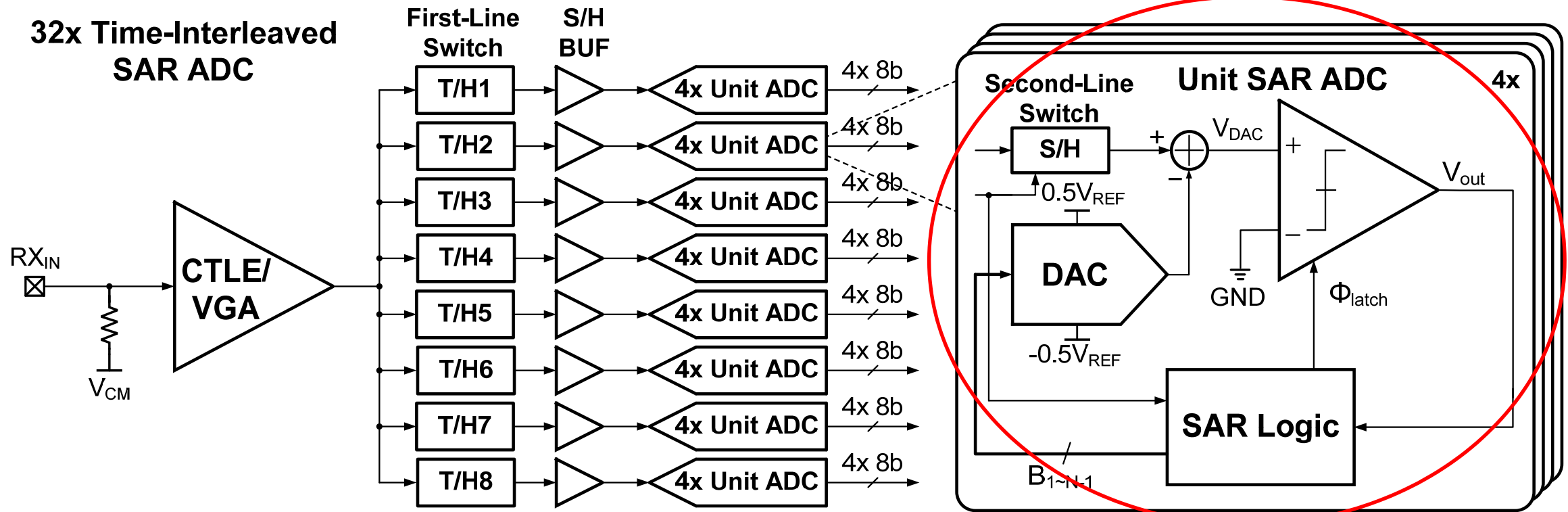

- ❑ Unit SAR ADC speed sets the interleave factor
- ❑ It's noise and linearity limit the achievable ADC ENOB
- ❑ Mismatches between the unit ADCs (and the preceding individual T/Hs and S/H buffers) will need to be calibrated


# Unit SAR ADC: Critical Timing Path

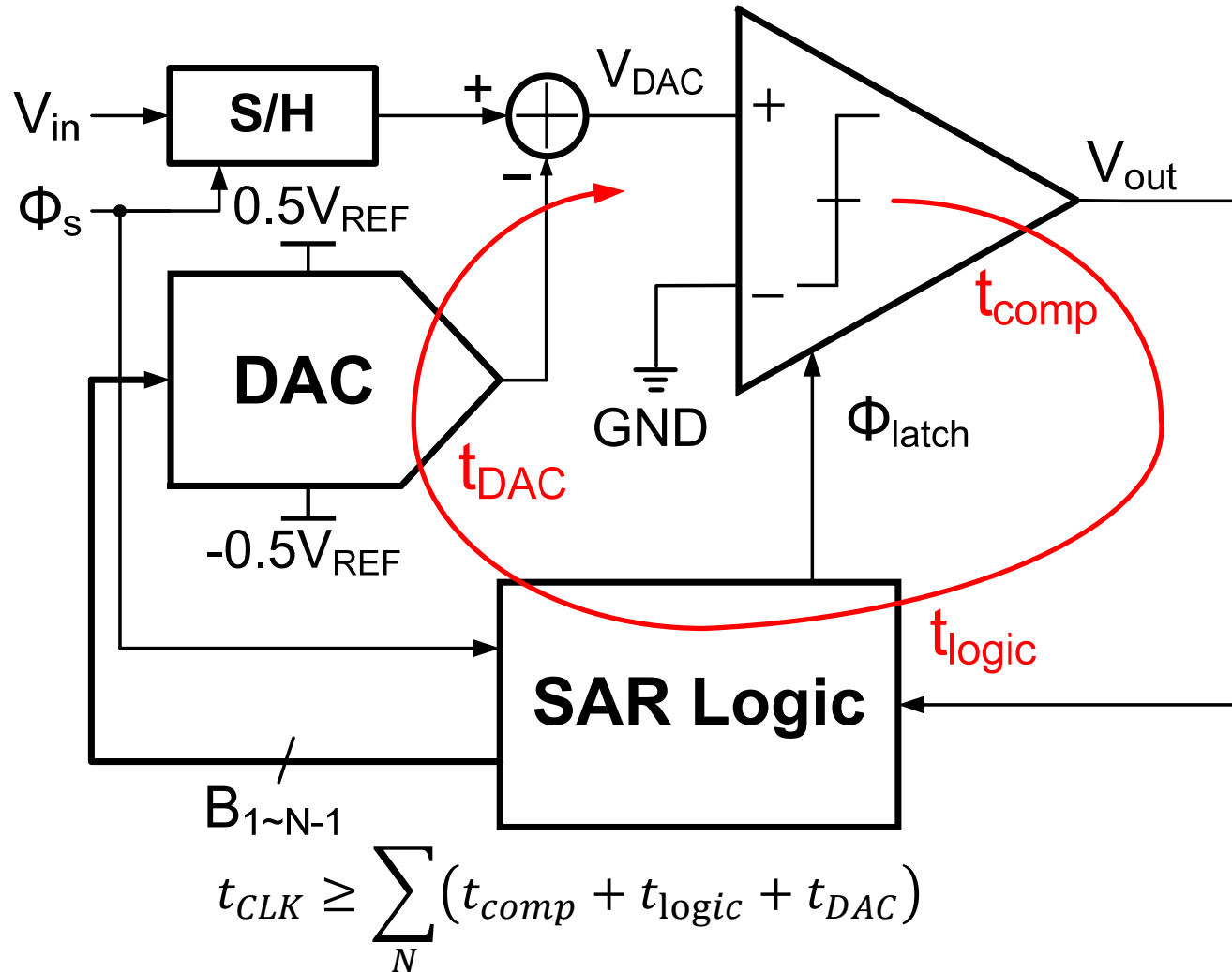

- SAR ADC consists of S/H, DAC, comparator and SAR logic
- The conversion speed of SAR ADCs depends on the delay from comparator, logic and DAC in the critical timing path
- Various techniques to reduce the delay for faster SAR ADC speed

# Unit SAR ADC: Advanced Techniques

## Asynchronous SAR operation

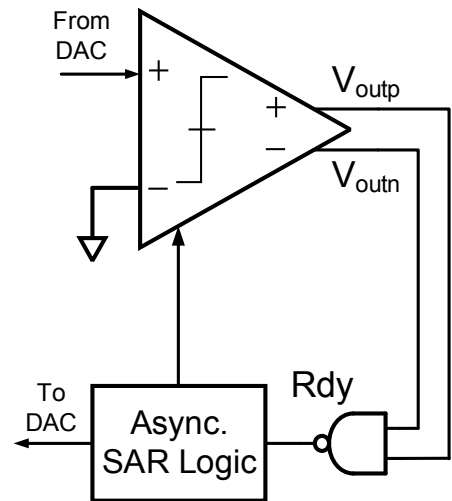


$$\sum_{i=0}^{N-1} \ln\left(\frac{V_{FS}}{V_{DAC}(i)}\right)$$

**[Chen JSSC 2006]**

$$t_{CLK} \geq \sum_N (t_{comp} + t_{logic} + t_{DAC})$$


## Multi-bit/stage conversion

 

$$N' = \left\lceil \frac{N}{M} \right\rceil$$


for M-bit/stage  
**[Cao JSSC 2009]**

## Loop-unrolled SAR

 


**[Jiang JSSC 2012]**

## Redundant SAR algorithm (trade-off N)

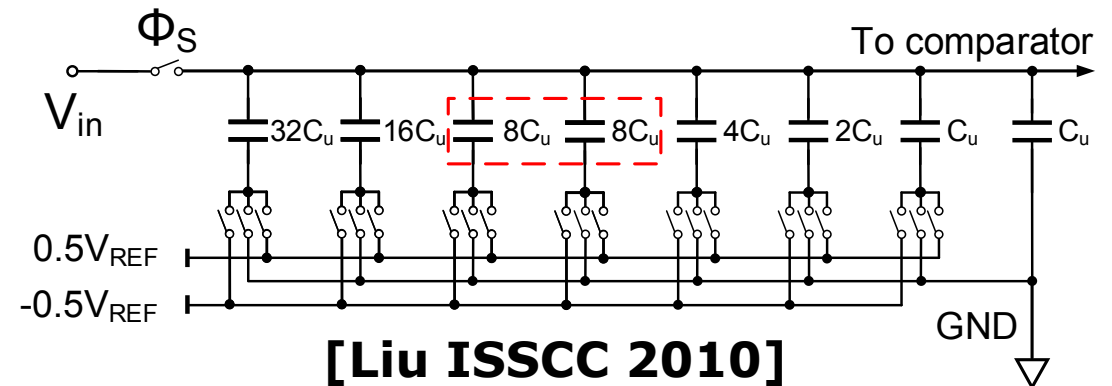


**[Liu ISSCC 2010]**

# DAC

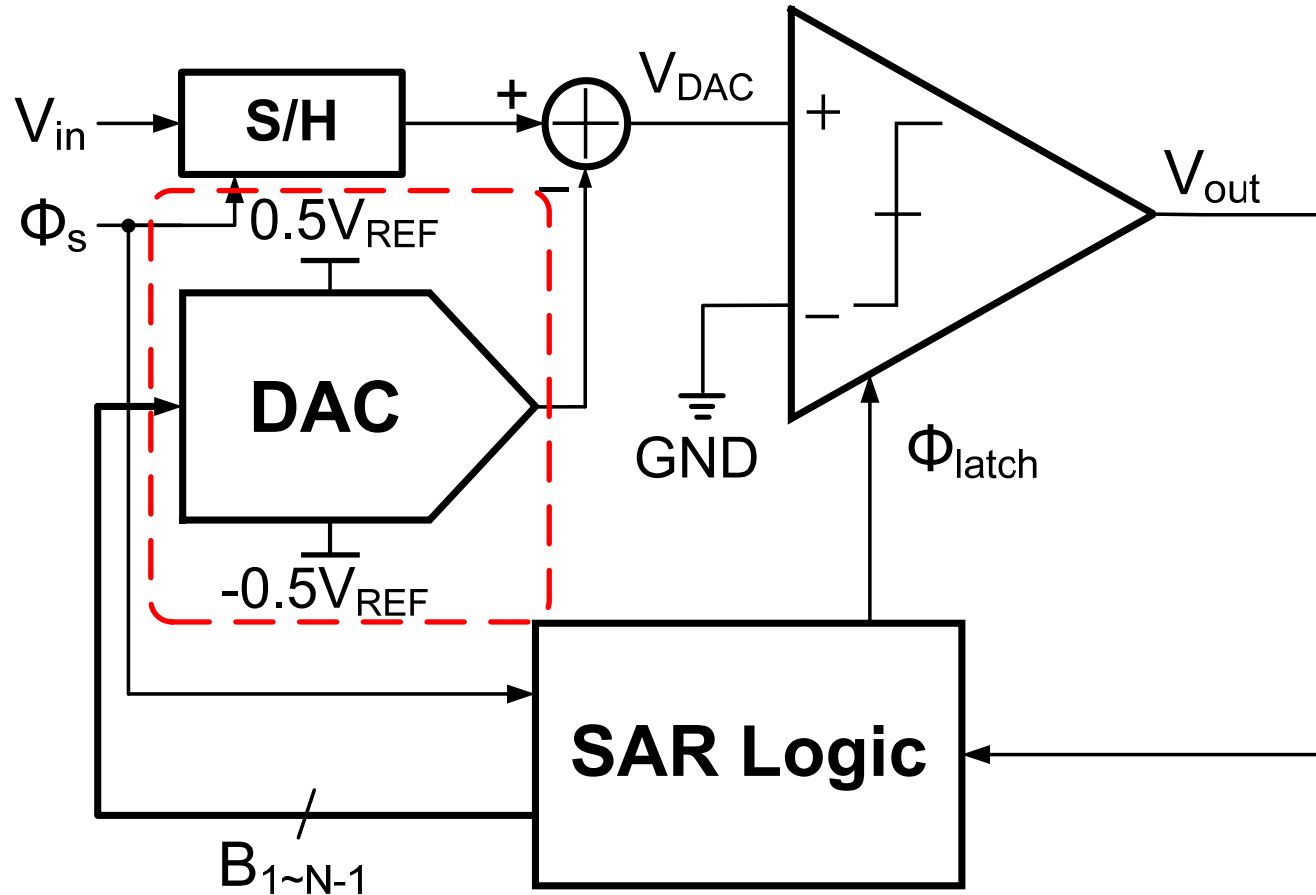


- DAC generates residue signals by subtracting binary weighted reference from input
- Capacitive DAC is the most popular DAC structure due to low power consumption


# DAC Implementation

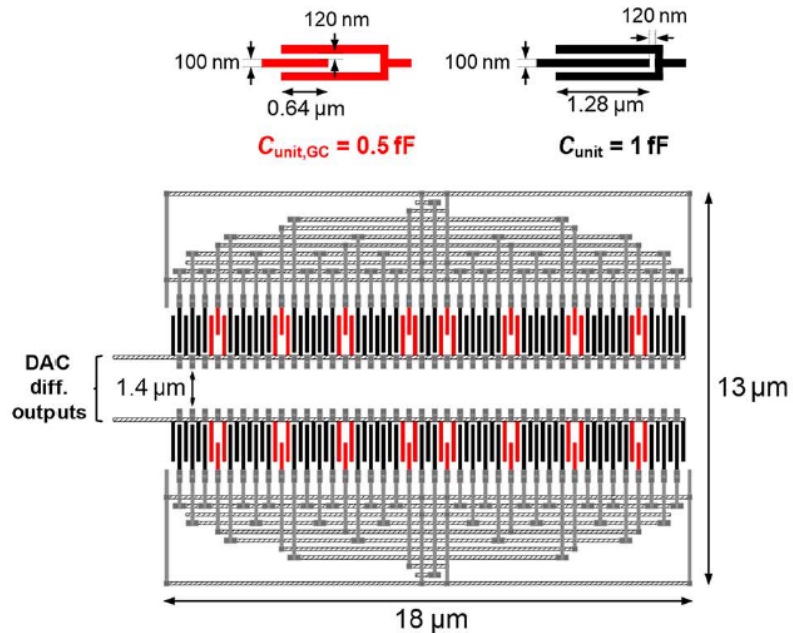

**Worst case error w/ cap mismatch**

 


**[Shafik JSSC 2016]**

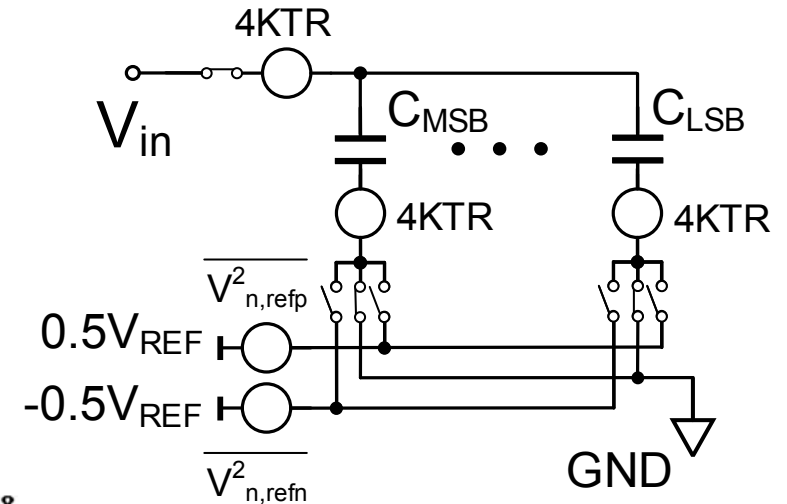

- ❑ Minimize cap size for medium resolution SAR (6~8bit)
- ❑ Minimum unit cap size limited by matching requirement and  $KT/C$  noise (noise usually dominated by front-end and comparator)


# Comparator

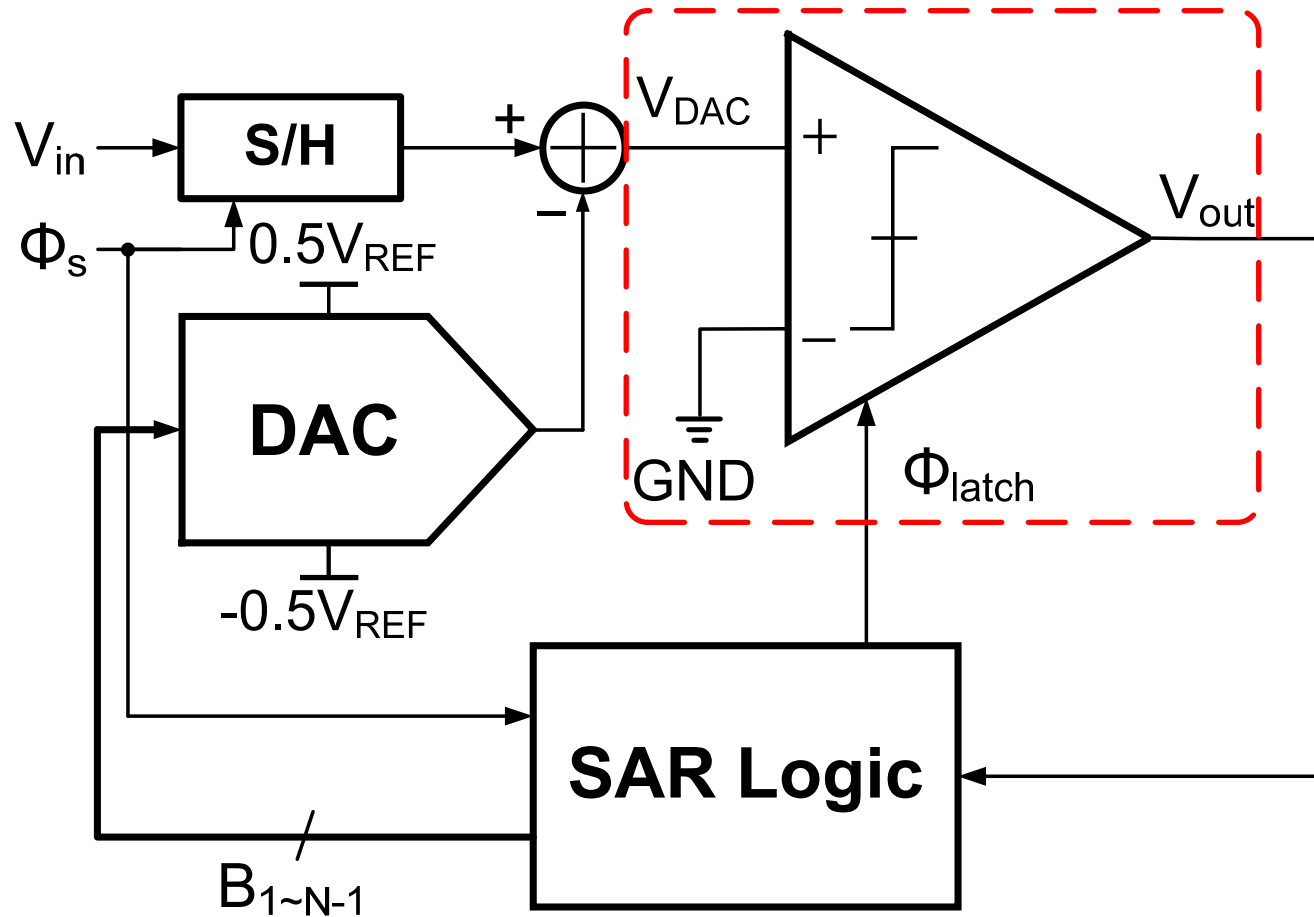

- Comparator makes decision on the DAC signal and generates binary search codes for SAR logic and DAC




# Dynamic Comparator

 


## □ Dynamic latch specs

- Noise
- Offset
- Metastability


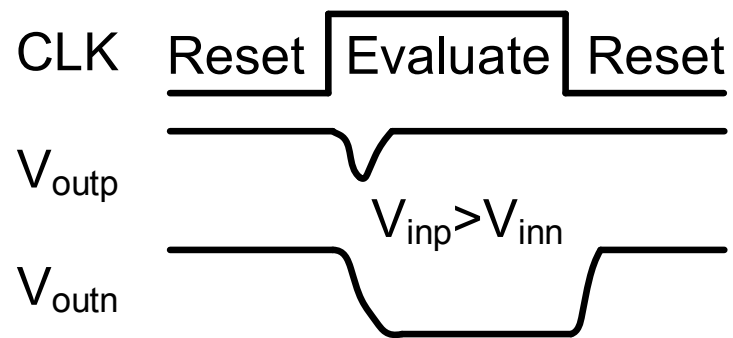


# Comparator Noise

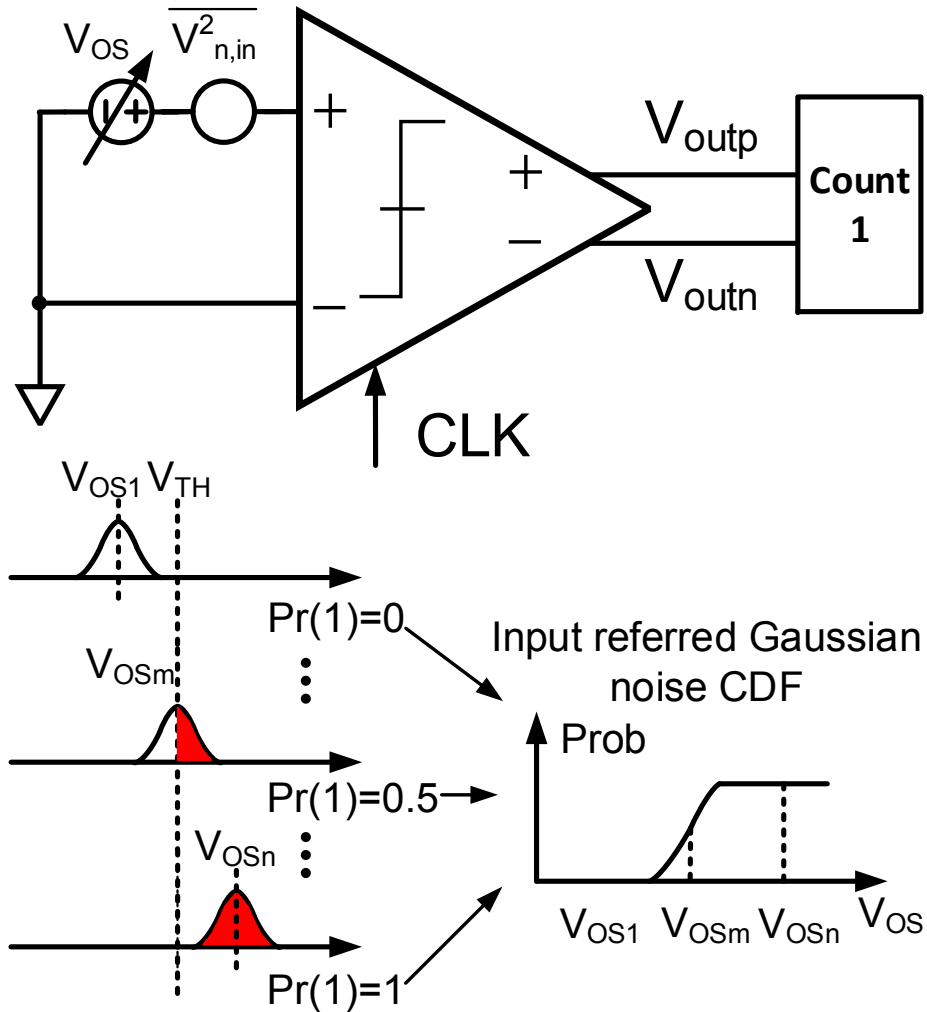

- Device noise causes random decisions even with zero input signal
- Noise variance can be found by fitting output to a Gaussian CDF as the input is swept and transient noise is enabled
- Noise can also be simulated with PSS+PAC+PNOISE, but requires post processing to find ISF from sideband transfer function [Kim TCAS-I 2009]

# Comparator Offset

  


- The input referred offset is primarily a function of  $V_{th}$  mismatch and a weaker function of  $\beta$  (mobility) mismatch

$$\sigma_{V_t} = \frac{A_{V_t}}{\sqrt{WL}}, \quad \sigma_{\Delta\beta/\beta} = \frac{A_{\beta}}{\sqrt{WL}}$$

- To reduce input offset 2x, we need to increase area 4x
- Not practical due to excessive area and power consumption
- Offset correction necessary to efficiently achieve good sensitivity



# Comparator Metastability

 

$$t_{samp} \sim \frac{C_{out} V_{THP}}{I_D}$$

+



$t_{comp}/\tau_{comp}$

  

$$t_{reg} \sim \ln\left(\frac{V_{DD}}{V_{in}}\right)$$

- Comparator evaluation is exponentially proportional to input voltage
- Probability of metastability error depends on ADC architecture



# Synchronous SAR Logic

 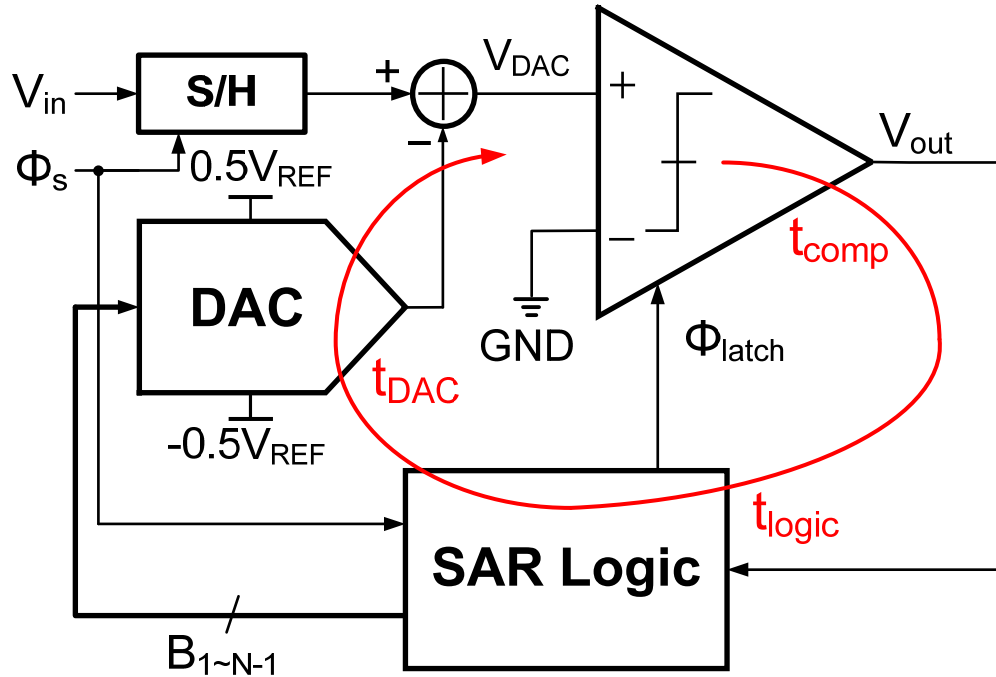

- ❑ Need an internal clk at  $N+1$  times sampling frequency
- ❑ Maximum frequency limited by worst case stage delay

$$f_s = \frac{1}{(N+1) \max_i (t_{comp,i} + t_{logic,i} + t_{DAC,i})}$$



# Asynchronous SAR Logic

 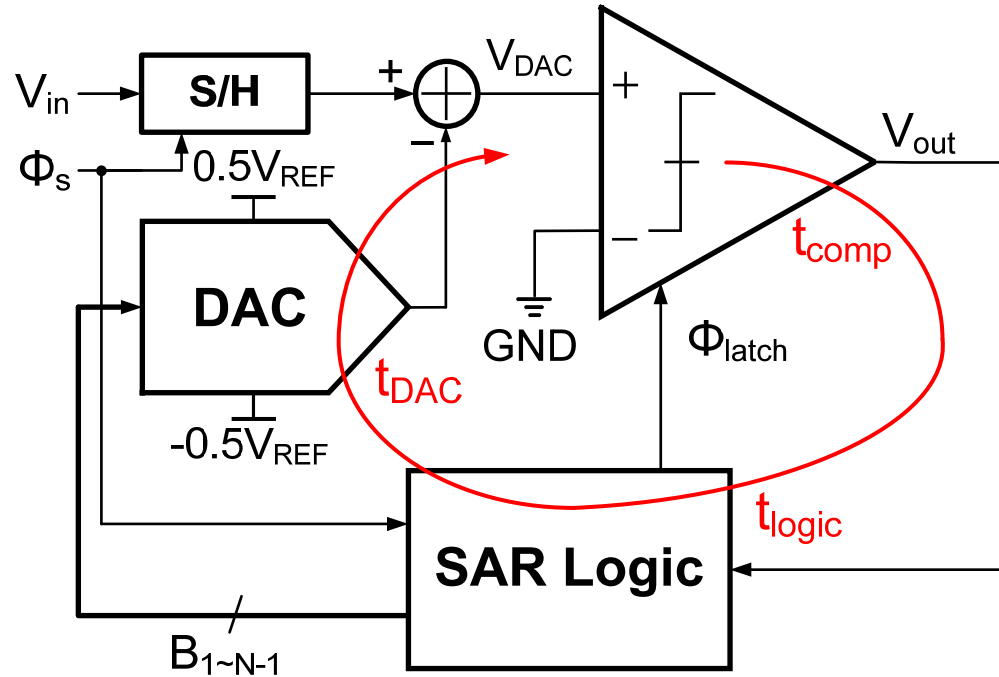

- ❑ Comparator triggered in a ripple fashion, no need for  $(N+1)fs$
- ❑ Maximum frequency speeded up by reducing the non-worst-case stage delay

$$f_s = \frac{1}{T_{Track} + \sum_{i=1}^N (t_{comp,i} + t_{logic,i} + t_{DAC,i})}$$

# Metastability Error Rate

  

- ❑ Metastability error rate can be improved with a faster comparator
- ❑ Metastability error could be propagated through digital FFE and impact RX BER performance even if it meets the ADC SNDR specification


# Outline

---

- ADC Resolution Requirements & Topologies
- Key ADC Circuits
- ADC Calibration Techniques
- Digital Equalization
- Analog Front-End
- Conclusion





# Time-Interleaving Errors

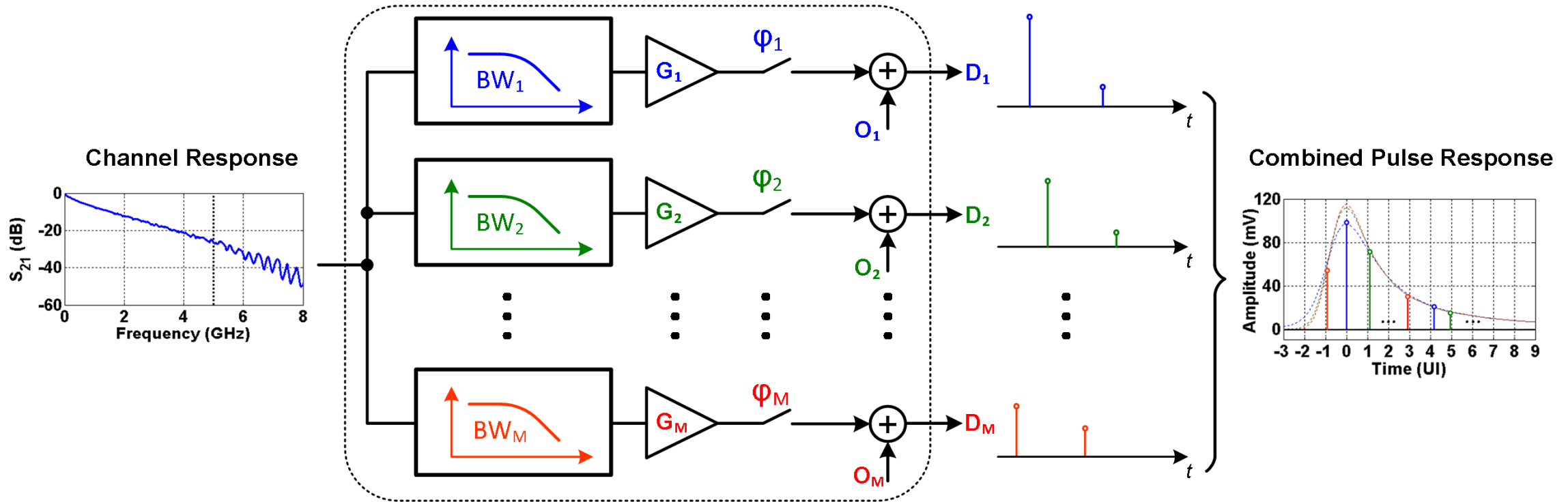

- ❑ Mismatches between time-interleaving channels degrade performance
- ❑ Modelled as an effective pulse response from each time-interleaved ADC channel, including offset, gain, bandwidth, and skew effects
- ❑ Both analog and digital calibration techniques are employed to correct these issues



# Offset Errors

 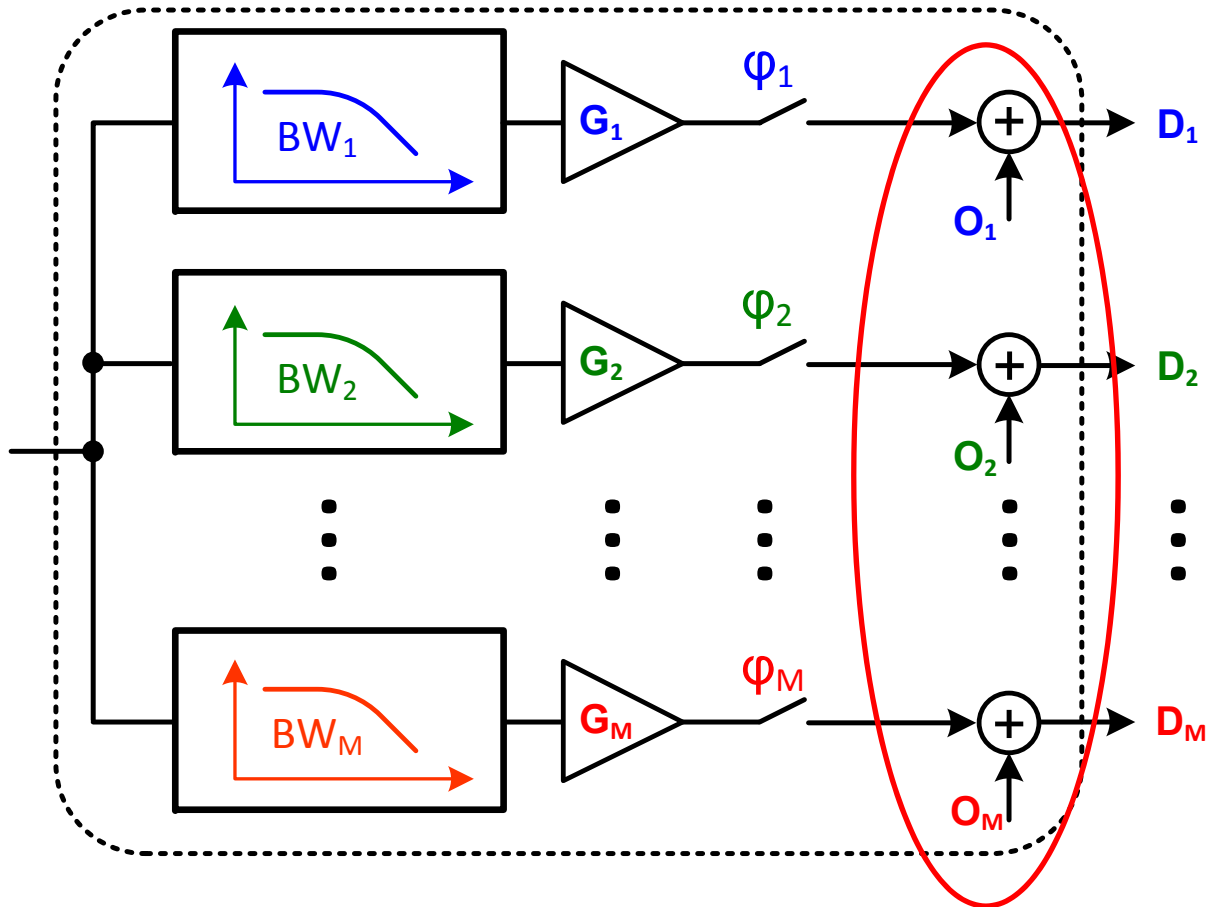

□ Caused by device mismatches in T/Hs, DACs, and comparators
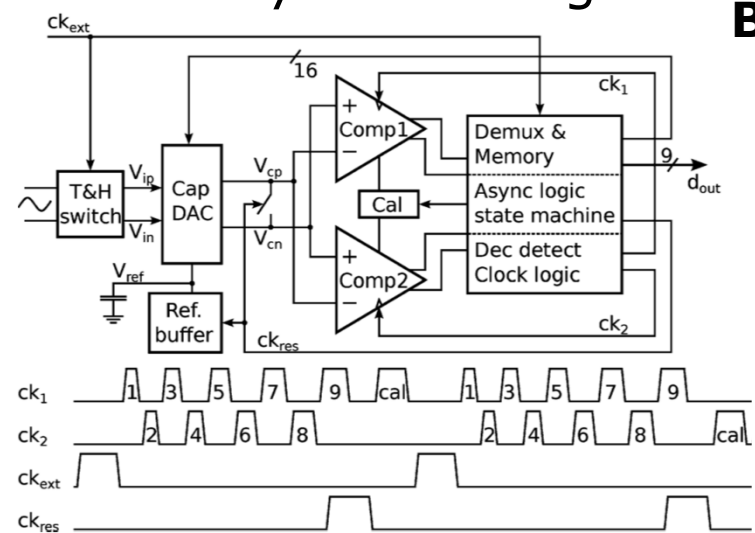 
# Offset Error Correction



- Most commonly corrected in the analog domain in the comparators
  - Current-mode/Capacitive DACs
  - Parallel diff pair driven by ref voltage
- Common foreground calibration scheme involves shorting inputs and adjusting offset DACs until 50% output 1/0
- Background calibration includes monitoring the average digital output or adding extra ADC correction cycles
- Can also be corrected in the digital domain with the loss of some dynamic range



**Background Offset Calibration w/ Extra SAR Cycle**

**[Kull JSSC 2013]**

# Gain Errors

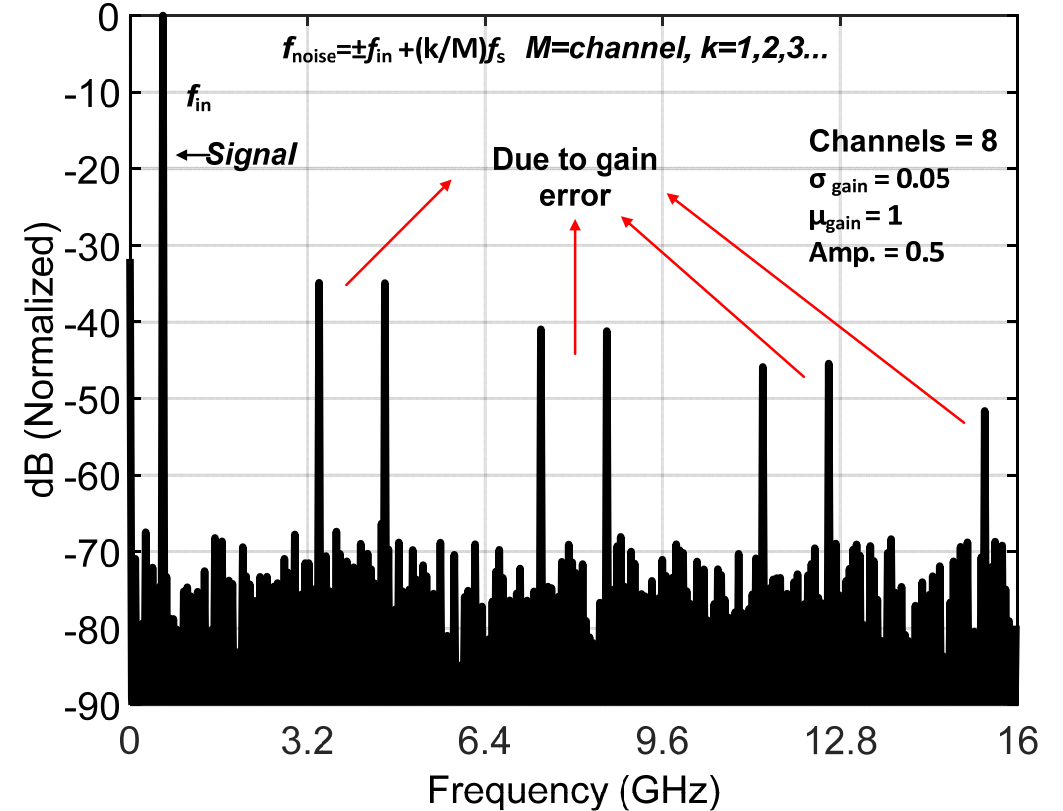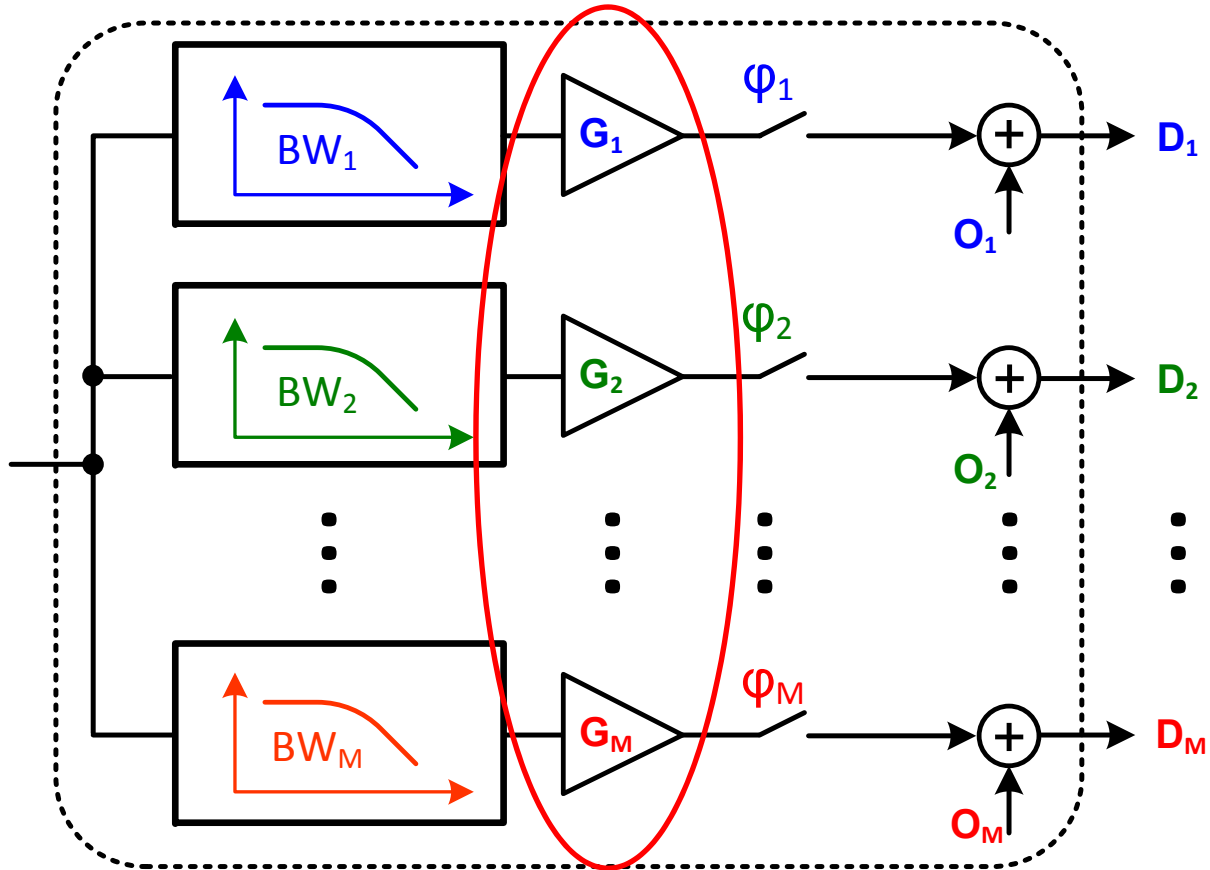


□ Caused by device mismatches in T/Hs, DACs, and comparators

# Gain Error Correction


- Effective background calibration involves digitally monitoring the ADC peak output and correcting it to match the FSR
- Flash ADC
  - Adjustment of comparator thresholds
  - Programmable gain amplifier in sub-ADC
- SAR ADC
  - Adjusting capacitive DAC reference voltage
  - Introducing additional programmable capacitors
- Further fine gain calibration can also be implemented in the DSP

## Programmable Gain Amplifier

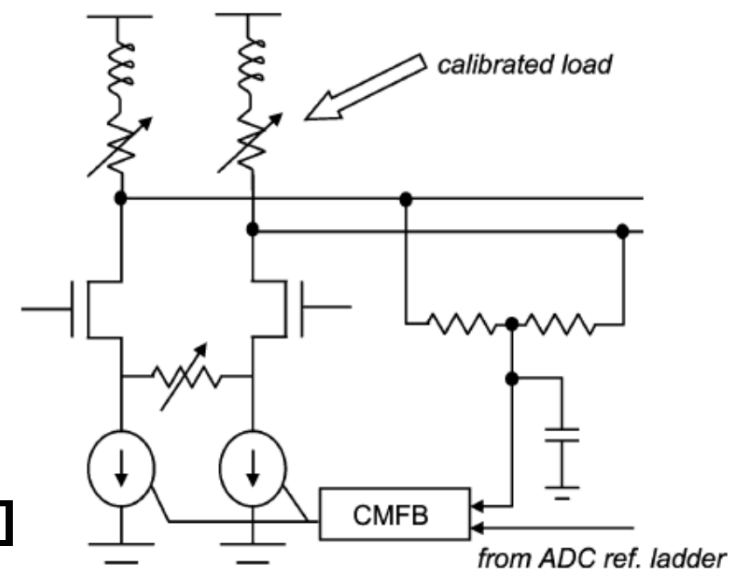



[Cao JSSC 2010]
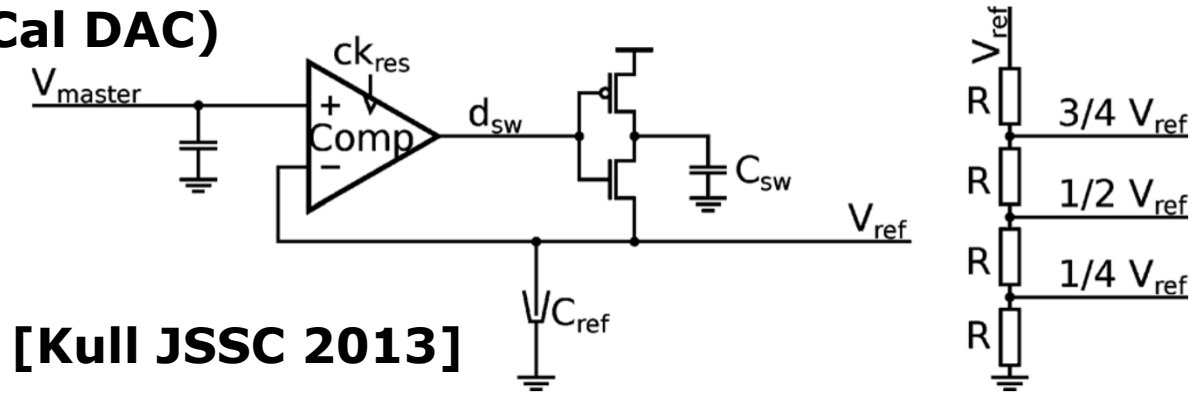
## Unit SAR DAC Programmable Reference (From Gain Cal DAC)



[Kull JSSC 2013]

# Bandwidth Errors

 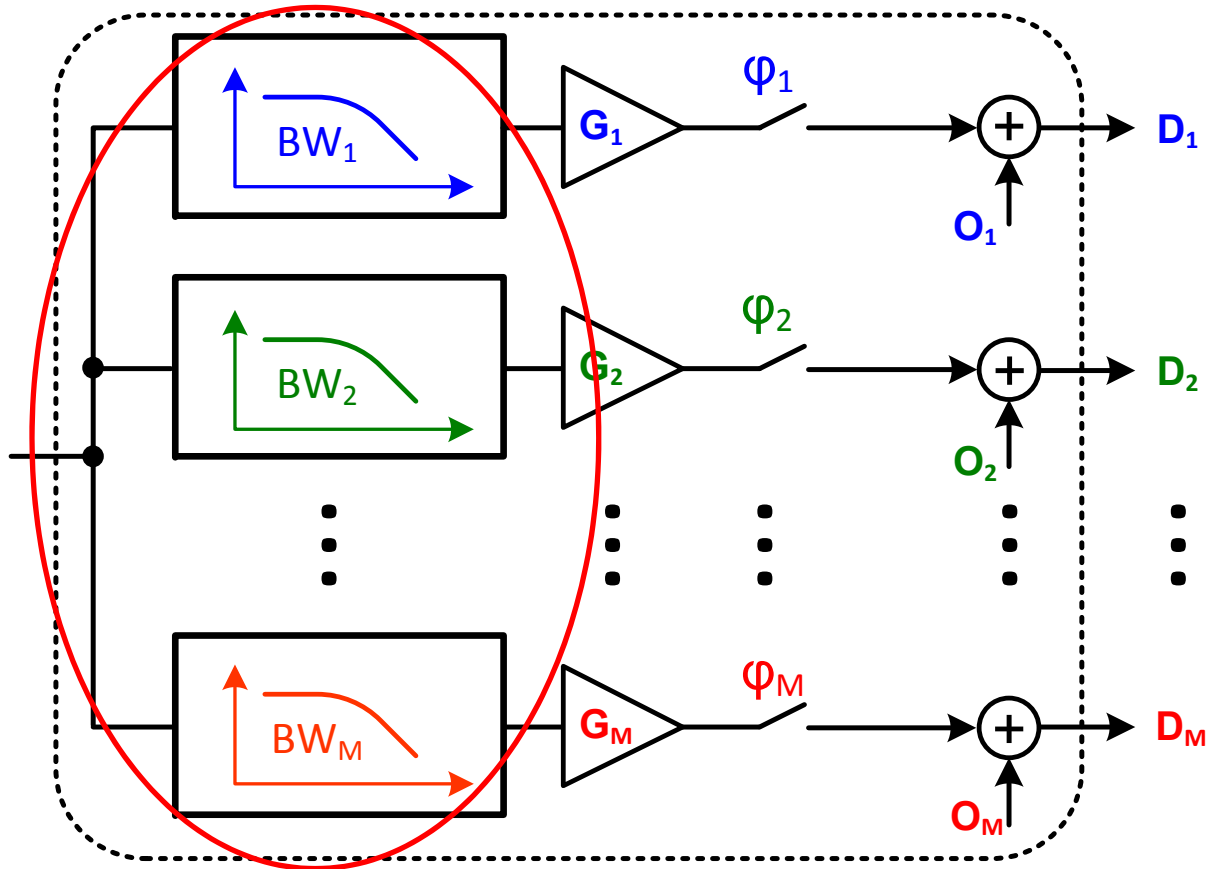


- ❑ Caused by layout asymmetries and device mismatches in T/Hs, DACs, and comparators


# Bandwidth Error Correction

- Simply design the signal path with sufficient bandwidth such that any variations don't translate into major differences in the pulse response

- Shunt peaking PGAs


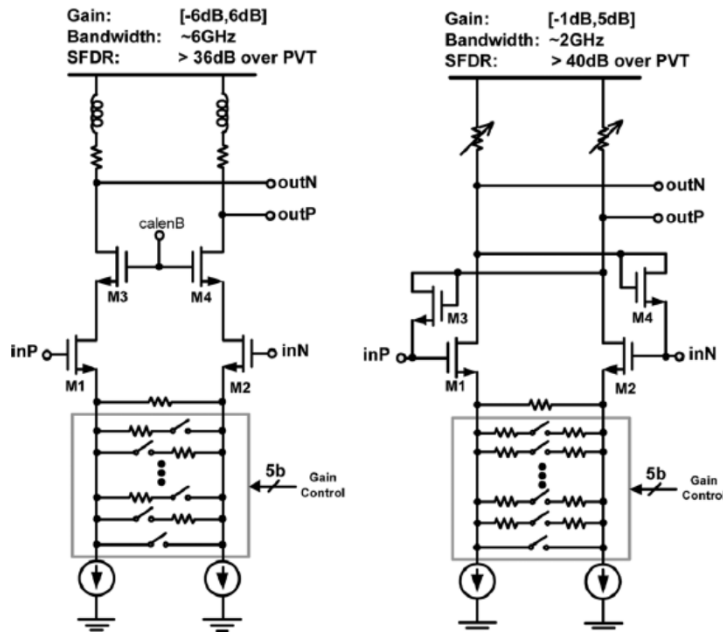


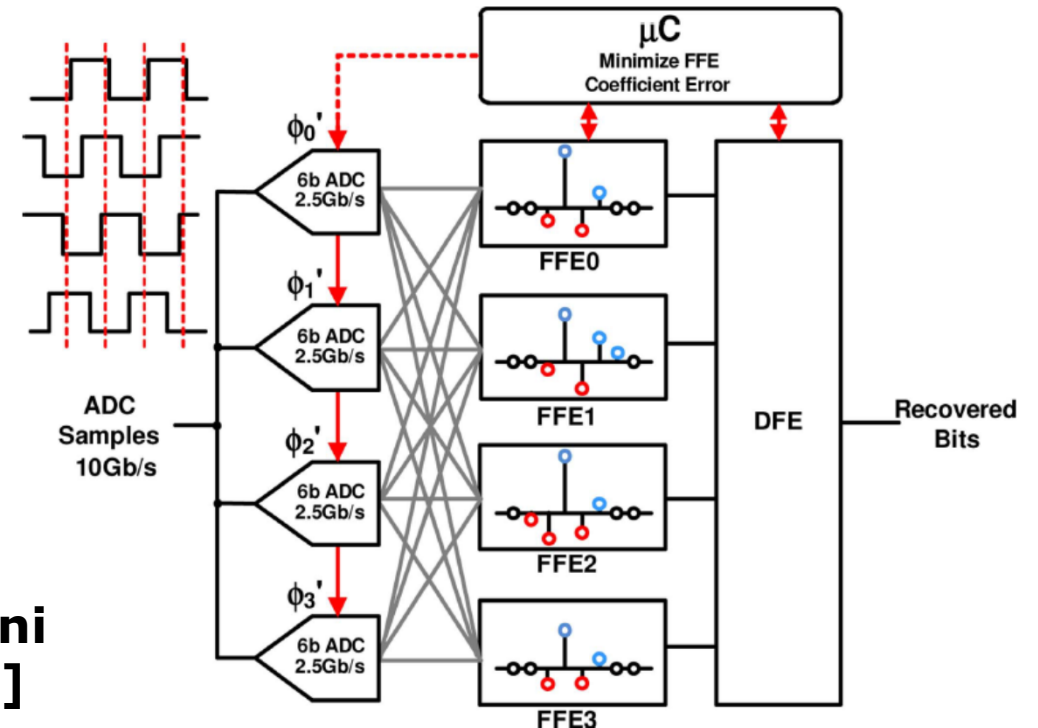- Digital domain compensation treats each sub-ADC as a unique channel
  - Per-slice independent adaptation of FFE and DFE taps



[Varzaghani  
JSSC 2013]

# Skew Errors

 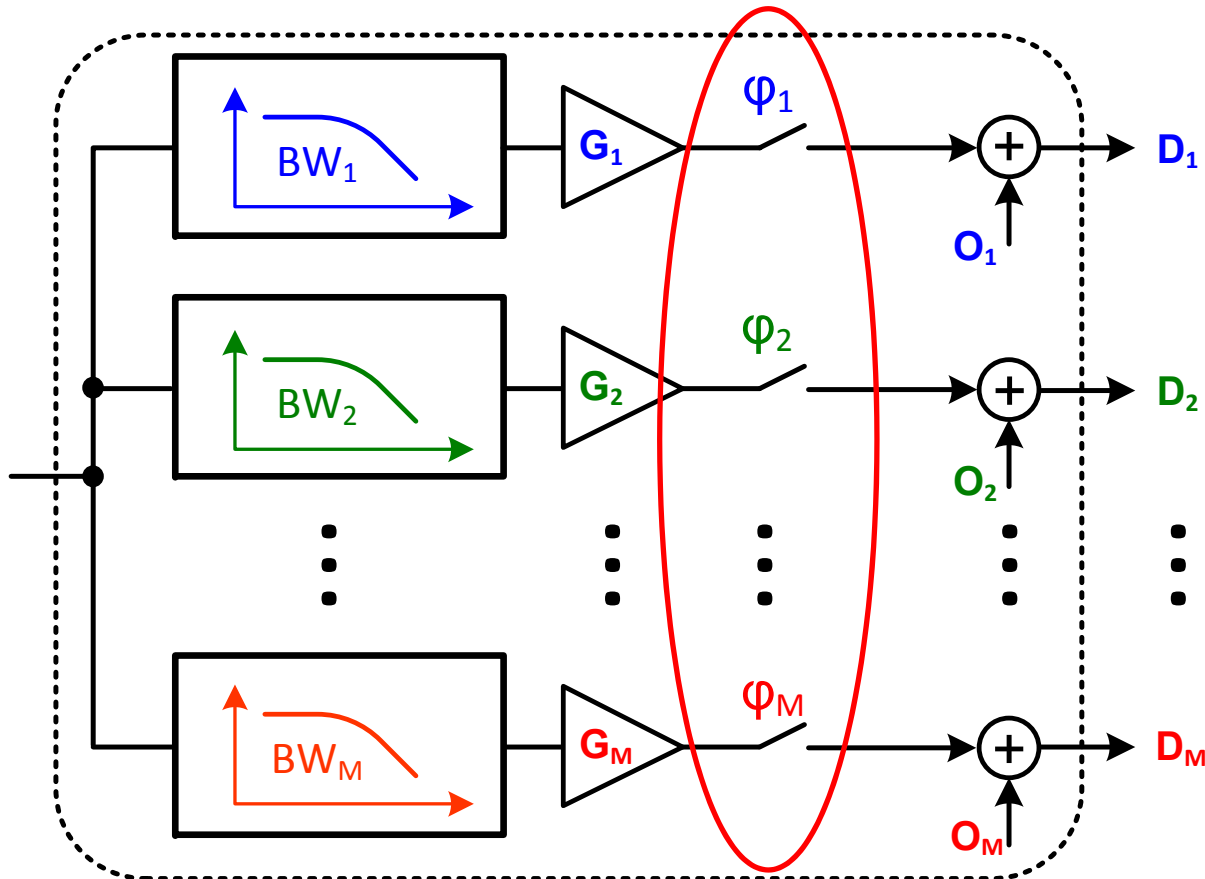


□ Caused by device mismatches and layout asymmetries in the multi-phase clock generation and distribution to the input track-and-holds


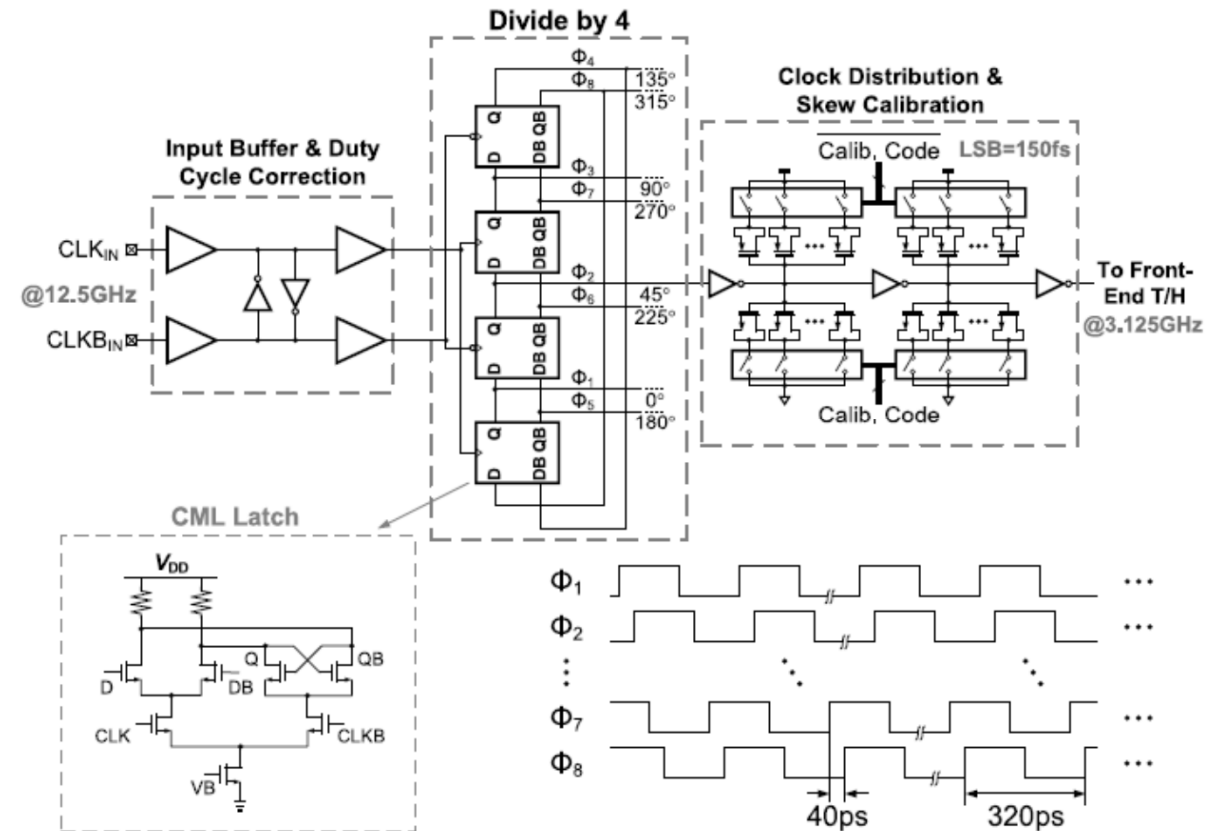
# Skew Error Correction

- Calibrated with per-phase digitally-adjustable delay cells in the clock distribution buffers or phase interpolators with independent phase offset codes
- Similar to bandwidth errors, skew errors will cause each sub-ADC to generate a pulse response with a slightly different ISI characteristic
- Efficient approach to detect skew errors is to monitor the differences in the converged tap coefficients of a per-slice adaptive equalizer



[Cai JSSC 2017]


# Outline

---


- ADC Resolution Requirements & Topologies
- Key ADC Circuits
- ADC Calibration Techniques
- Digital Equalization
- Analog Front-End
- Conclusion
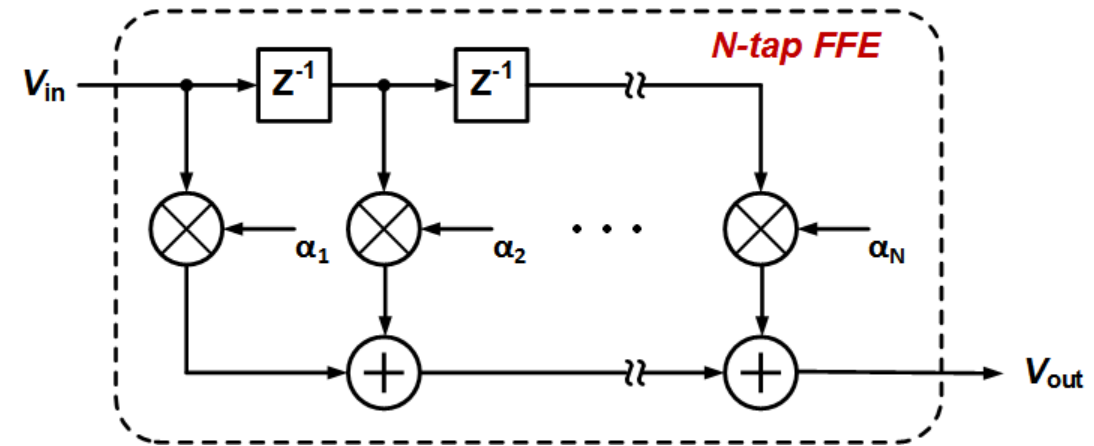
# Feed-Forward Equalizer

- Symbol by symbol linear equalizer
- Parallel implementation often matches or exceeds the ADC time-interleaving factor
- Timing constraints can be easily met through pipelining
- FFE power efficiency can be improved through several techniques such as
  - Power supply scaling
  - Employing CSD representation for taps
  - Tapering coefficient range for taps far from main tap
- FFE architecture is independent of modulation format




 **Energy efficiency of an 8-tap FFE vs supply level [Toifl ESSCIRC 2014]**


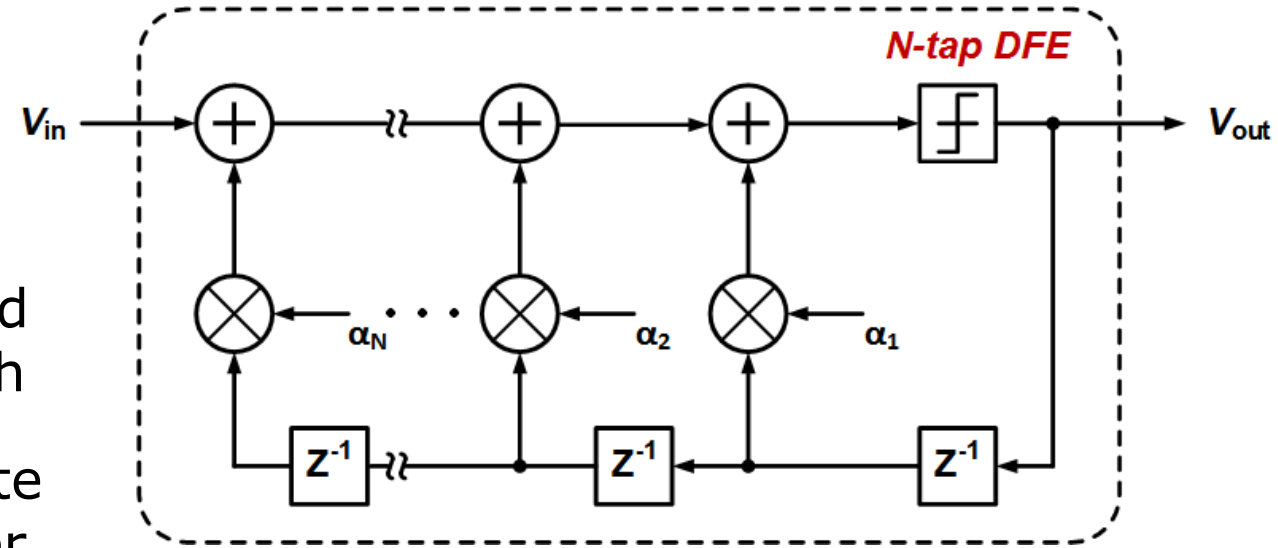
# Decision Feedback Equalizer

- Non-linear equalizer that cancels post-cursor ISI
- Conceptual full rate implementation has all the summers, 1 multiplier and 1 comparator in the 1-UI critical path
- Loop critical path delay in the full rate implementation is significantly longer than the iteration bound  
(1\*(summer + multiplier + slicer) / 1UI)




$$\text{Iteration Bound} = \text{Max} \left( \frac{\text{Total Logic Delay}}{\text{Total Loop Time}} \right) \text{ over all loops}$$

- DFE often implemented to have the same number of parallel slices as the preceding FFE
  - Does this effectively solve the critical path issue?

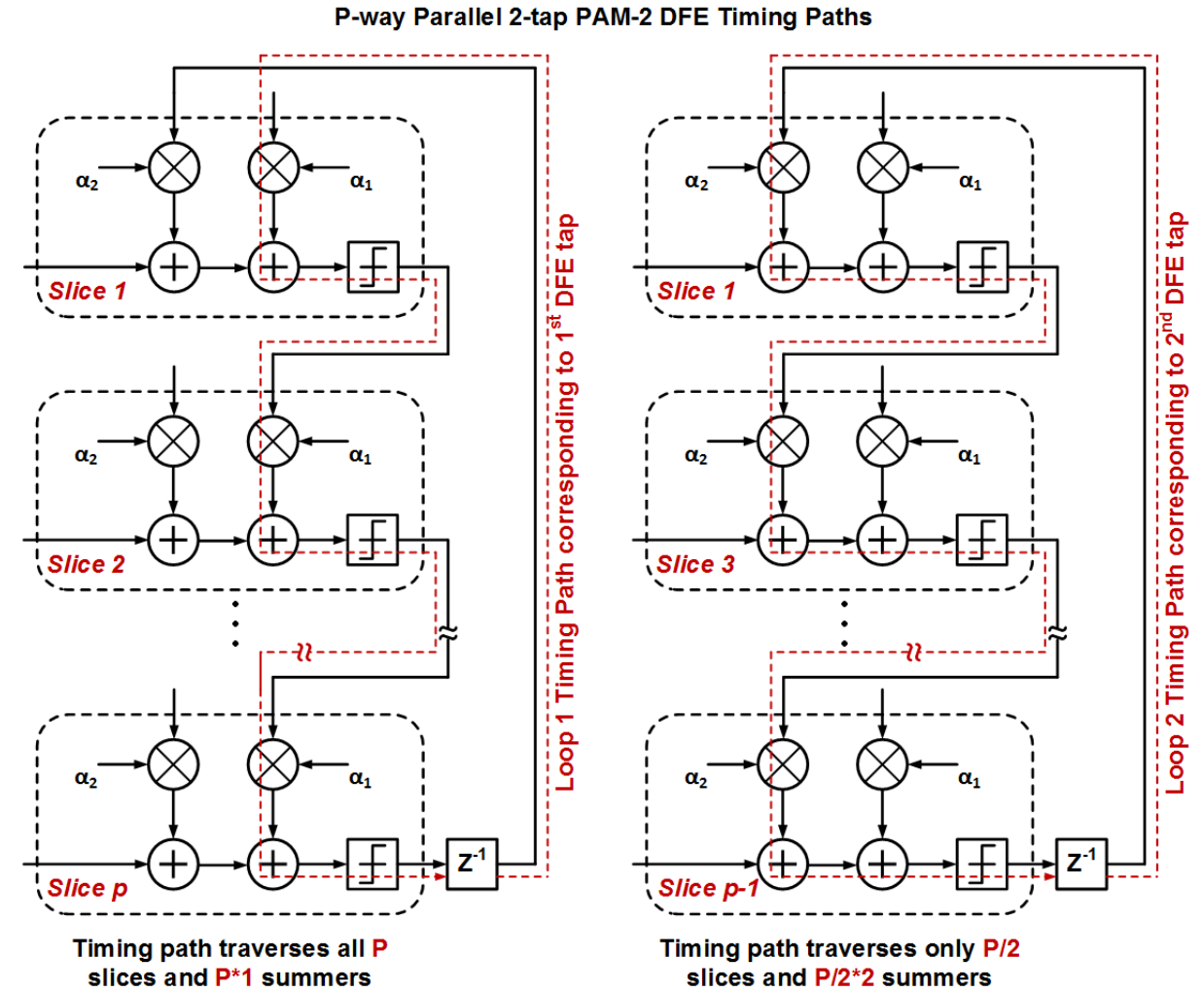
# Parallel Slice Decision Feedback Equalizer

- DFEs are implemented with  $P$  parallel slices operating with a clock period of  $P$  UIs
- This still results in a maximum of  $P$  adders in the timing paths for the timing loops
- Even though the clock period increases by a factor of  $P$ , the logic delay also effectively increases by the same  $P$  factor
- While the parallel implementation brings the loop critical path period much closer to the iteration bound, advanced techniques are necessary to operate at high data rates



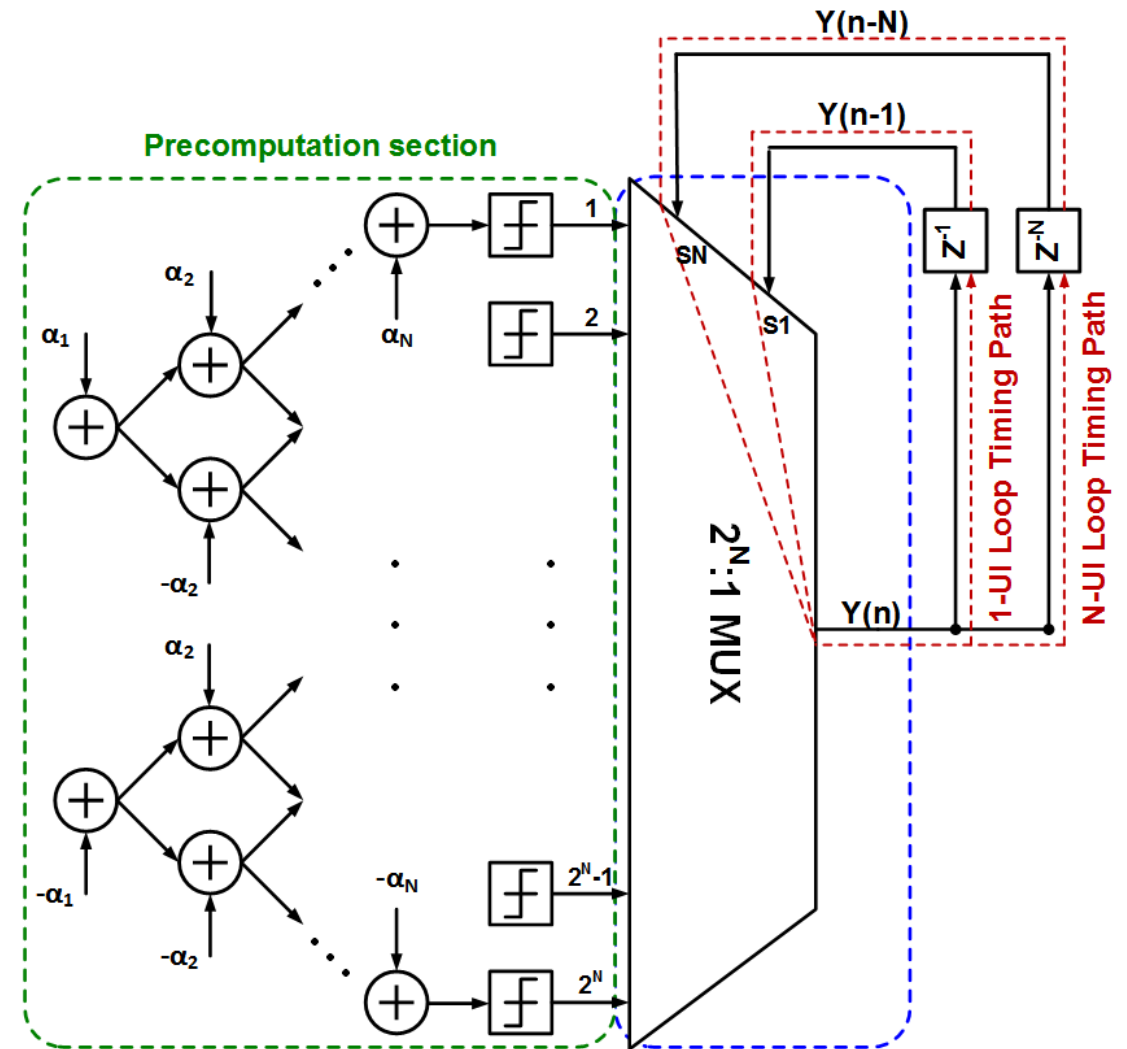
# Loop-Unrolled DFE

- Loop-unrolling involves precomputing all the possible decisions for the current symbol using all possible decisions for the preceding decisions that are part of the DFE
- Results in  $2^N$  precomputed decisions for PAM-2 and  $4^N$  precomputed decisions for PAM-4
- The **adder is removed from the loop critical path** as the precomputations can be pipelined
- The loop critical path primarily contains 2:1 muxes for PAM-2 and 4:1 muxes for PAM-4




# Example: PAM-4 2-tap Loop Unrolled DFE

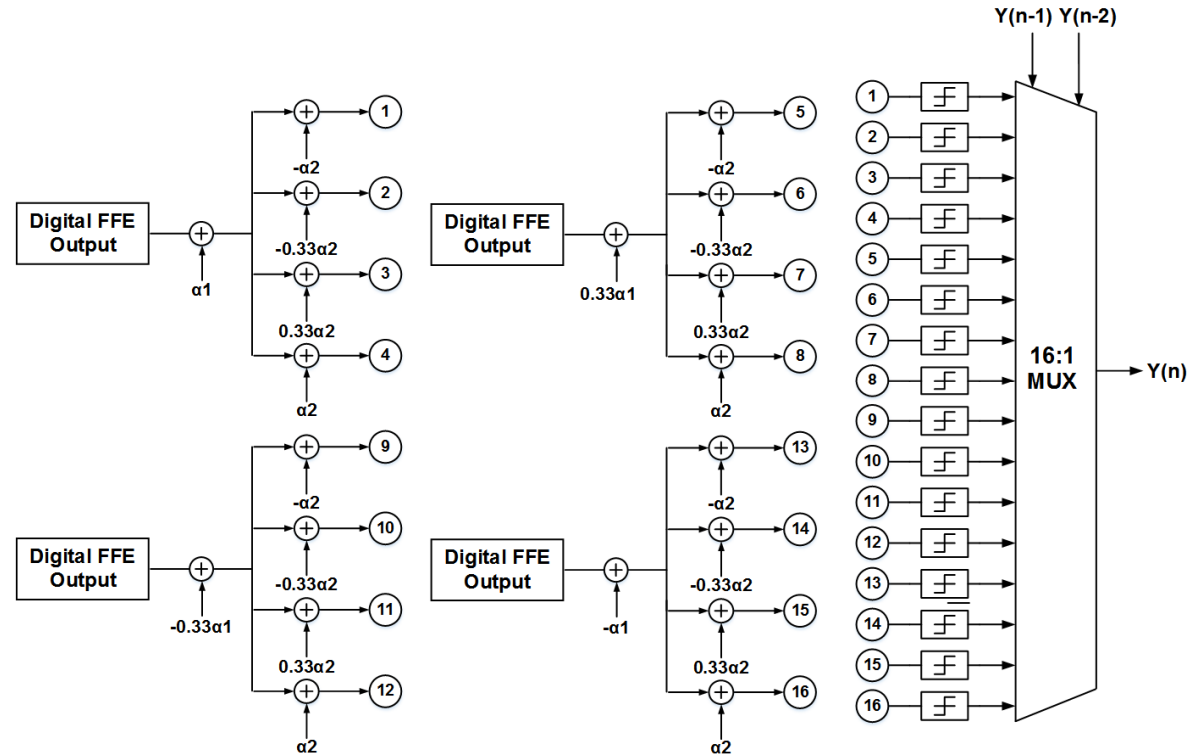

- ❑  $4^2 = 16$  decisions are precomputed with a 2-tap loop-unrolled DFE
- ❑ The output of the summers is sliced and fed into a 16:1 mux
- ❑ Select lines to the multiplexers come from the two **immediately preceding** decisions that have been made
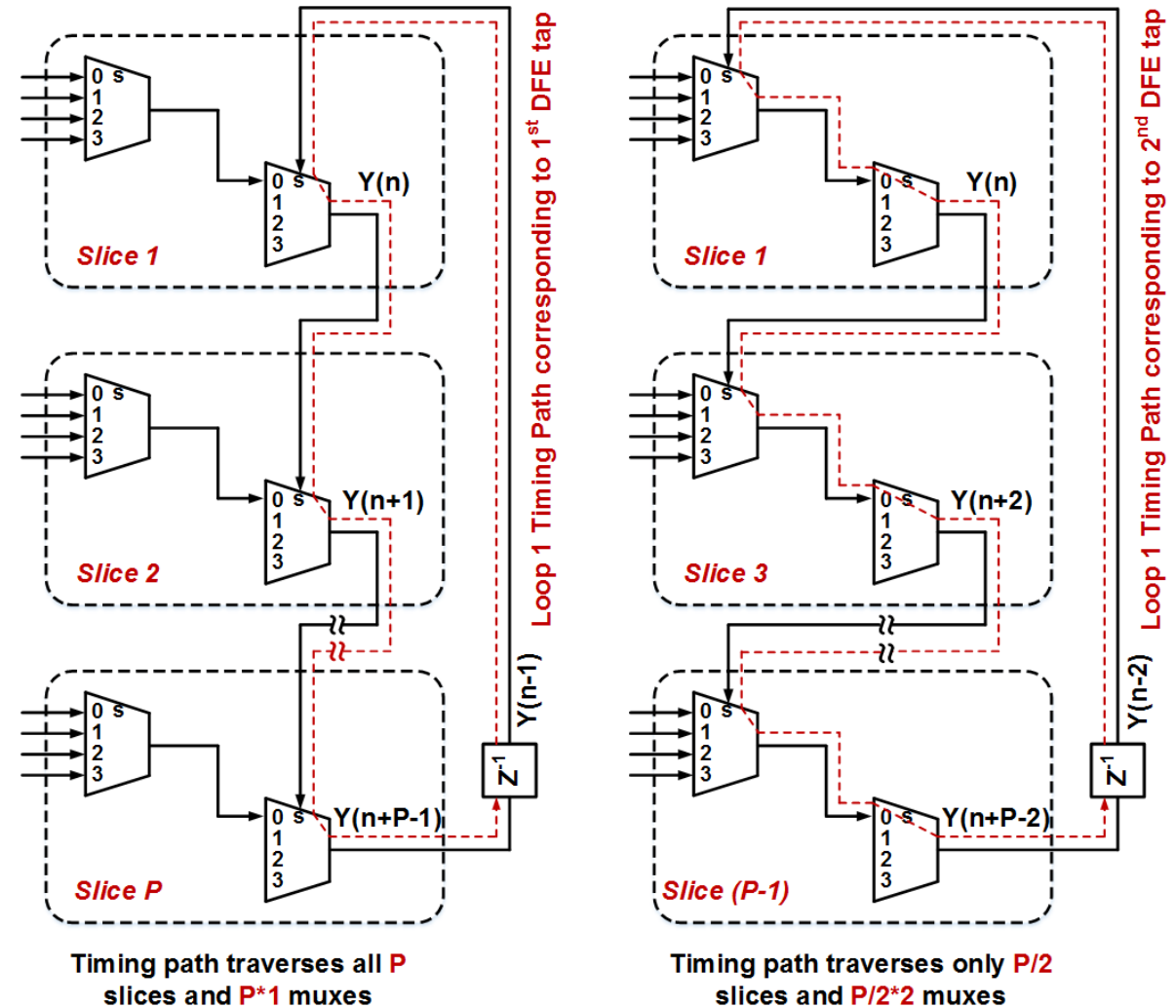
# Example: Timing Paths for PAM-4 2-tap Loop-Unrolled DFE

- Assuming  $P$  is even, each timing loop goes through  $P$  4:1 muxes
- The total loop critical path is  $P$  4:1 muxes, 1 Clk  $\rightarrow$  Q delay, 1 setup time delay and routing delay
- For the  $N^{\text{th}}$  tap of the DFE, the timing loop contains  $(1 + \lfloor \frac{P-1}{N} \rfloor) * N$  4:1 muxes
- For high data rates, further techniques to reduce the number of muxes in the loop critical path becomes necessary






# Look-Ahead Multiplexer Loops

- Look-ahead architecture reduces the number of muxes in the loop critical path

- A mux loop is described by

- $Y_n = A_n Y'_{n-1} + B_n Y_{n-1} \dots (1)$  and

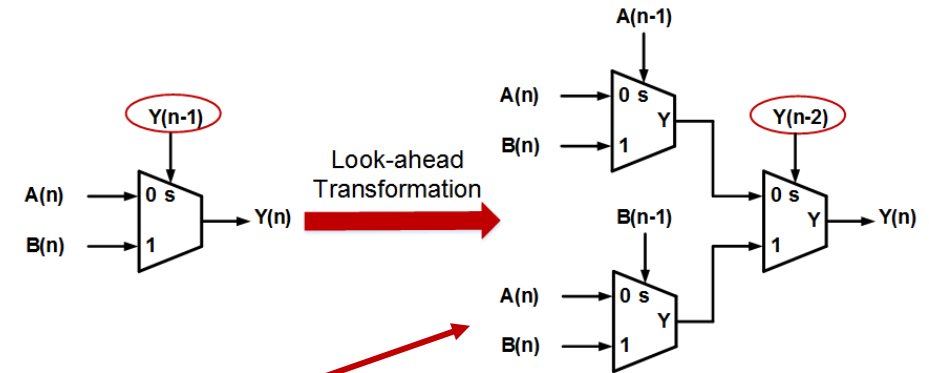- $Y_{n-1} = A_{n-1} Y'_{n-2} + B_{n-1} Y_{n-2} \dots (2)$



- Substituting (2) in (1)


- $Y_n = (A_n A'_{n-1} + B_n A_{n-1}) Y'_{n-2} + (A_n B'_{n-1} + B_n B_{n-1}) Y_{n-2} \dots (3)$  **[Parhi TVLSI 2005]**

- In (3)  $Y_n$ 's dependency on  $Y_{n-1}$  has been removed! (Iteration bound halved)

# Look-Ahead Multiplexer Loops

- The look-ahead multiplexor loop comes at the cost of extra muxes
- The feed forward section can be pipelined but the feedback section cannot be
- In case of PAM-2 N tap DFE, with LF way look-ahead the number of 2:1 muxes need is:  $2^N(LF - 1) + \sum_{i=1}^N 2^{N-i}$

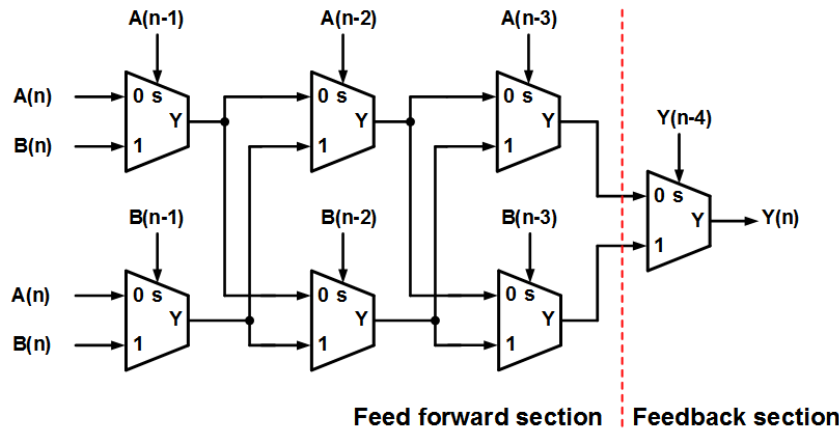
**1-tap PAM-2 4-way look-ahead mux architecture**



- In the case of PAM-4, the number of 2:1 muxes needed is:


$$(4^N(LF - 1) + \sum_{i=1}^N 4^{N-i}) * 2 * 3$$

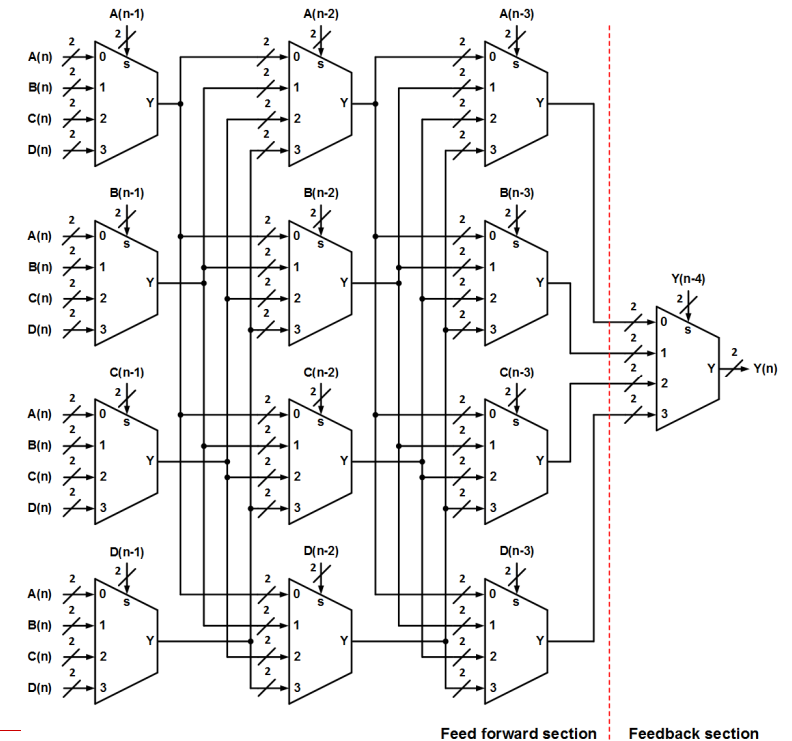**1-tap PAM-4 4-way look-ahead mux architecture**


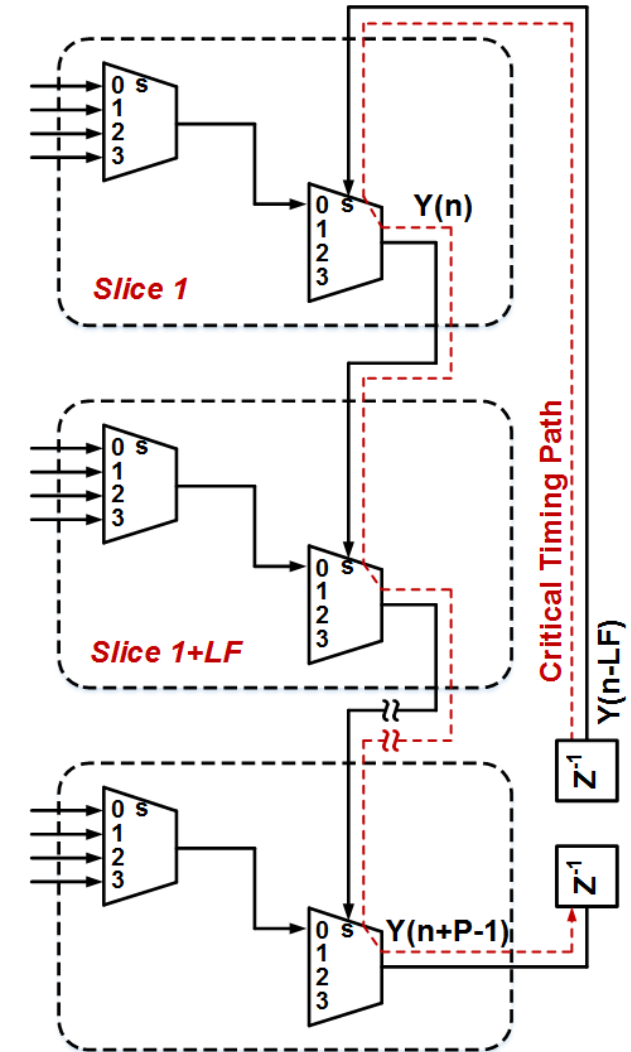
# Example: PAM-4 Look-Ahead Loop Timing Path

- Select lines of the mux come from decisions made **LF-UIs** ago where LF is the look-ahead factor
- Input lines of the mux are fed from a bank of look-ahead muxes which can be pipelined
- Critical path for Nth DFE tap consists of 1 Clk->Q delay,  $(1 + \left\lfloor \frac{P-1}{LF+N-1} \right\rfloor) * N$  4:1 muxes, 1 setup time and routing delay
  - Approximately divided by the look-ahead factor



# Maximum Achievable Data Rate



□ For P-parallel path, N-tap DFE if Td is the 4:1 mux delay

□ DFE timing constraint with no look-ahead must satisfy



$$P * UI = \left(1 + \left\lfloor \frac{P-1}{N} \right\rfloor\right) * N * (Td) + \text{clock uncertainty} + 1 \text{ Clk} \rightarrow Q \text{ delay} + \text{setup time}$$

□ With look-ahead factor LF the constraint is
  
$$P * UI = \left(1 + \left\lfloor \frac{P-1}{LF + N - 1} \right\rfloor\right) * N * (Td) + \text{clock uncertainty} + 1 \text{ Clk} \rightarrow Q \text{ delay} + \text{setup time}$$



# Complexity

  

- The 2:1 mux count for different number of DFE taps employing the minimum possible look-ahead factor necessary for that tap number shows the dramatic increase in going from 1 to 3 taps of DFE

# Digital DFE Take-Aways

---


- PAM-4 system unit delay element is a 4:1 mux, as opposed to 2:1 mux for NRZ
  - At the same baud rate makes timing closure much harder than NRZ
  
- Loop-unrolling and look-ahead techniques can significantly reduce the critical path delay and enable high data rates
  
- High data rates come at the cost of huge complexity
  - Grows as power of 4 for PAM-4 systems

# Outline

---

- ADC Resolution Requirements & Topologies
- Key ADC Circuits
- ADC Calibration Techniques
- Digital Equalization
- Analog Front-End
- Conclusion


# Analog Front-End (AFE)

 


- ❑ Provides CTLE equalization to partially compensate for channel loss
- ❑ Variable gain amplifier (VGA) stages sets the ADC input to match the FSR for different channel and equalization configurations



 
# AFE Impact on ADC Resolution & Digital FFE Taps



TX=3-tap, RX=14-tap FFE & 1-tap DFE

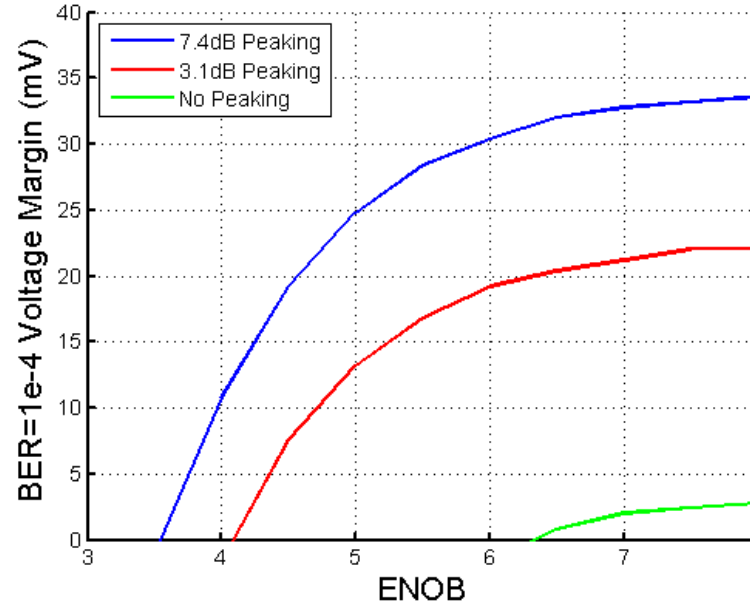

6b ENOB

 


- CTLE peaking allows reduction in digital FFE tap count and strength
- This reduces quantization noise amplification and allows for a lower ENOB



## Key Simulator Settings

- 3-tap TX w/ 1Vpp swing
- 400mV ADC FSR
- $3\text{mV}_{\text{rms}}$  ADC input noise
- $\text{RJ}=300\text{fs}_{\text{rms}}$
- No TI effects

# AFE Bandwidth

 

TX=3-tap, RX=14-tap FFE & 1-tap DFE

 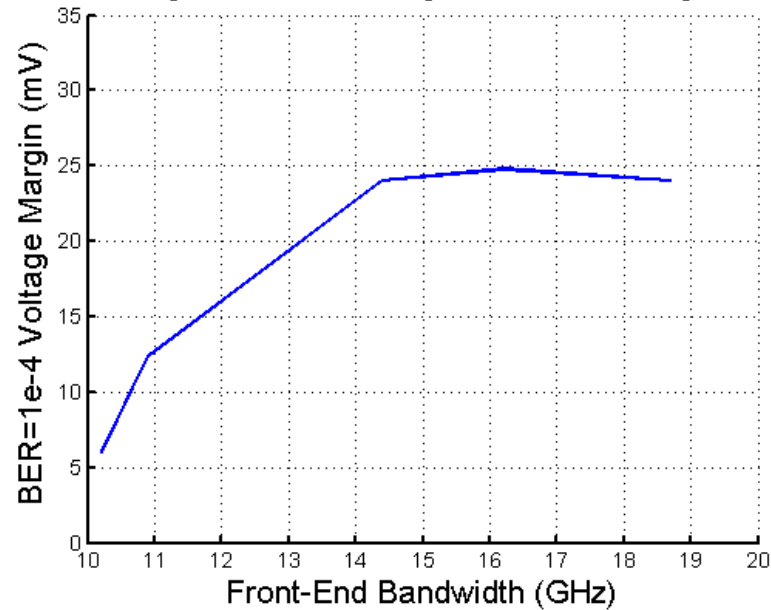


- ❑ Additional ISI is introduced if the AFE bandwidth drops below Nyquist
- ❑ This can be partially compensated with additional digital FFE taps

## Key Simulator Settings

- 3-tap TX w/ 1Vpp swing
- 5b ENOB
- 400mV ADC FSR
- 3mV<sub>rms</sub> ADC input noise
- RJ=300fs<sub>rms</sub>
- No TI effects

# AFE Linearity

 


- ❑ AFE compressive non-linearity degrades performance
- ❑ Setting the AFE 1dB compression voltage to  $>1.25X$  ADC FSR allows for minimal impact
- ❑ Severe degradation as the 1dB compression falls below the ADC FSR

## Key Simulator Settings

- 3-tap TX w/ 1Vpp swing
- CTLE/AGC FE w/ 7.4dB peaking and 16GHz BW
- 400mV ADC FSR
- Digital 14-tap FFE & 1-tap DFE
- $3\text{mV}_{\text{rms}}$  ADC input noise
- $\text{RJ}=300\text{fs}_{\text{rms}}$
- No TI effects
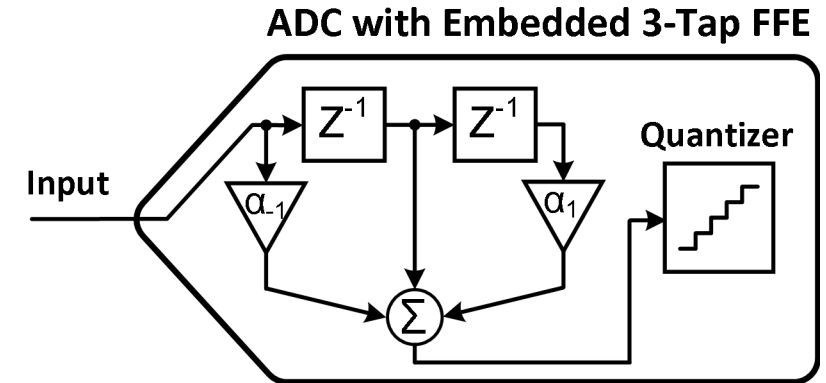
# Embedded FFE in ADC


- Partial analog equalization in the form of an FFE filter can be efficiently embedded inside a SAR ADC
- Translates into reduced power and complexity in both the ADC and the digital equalizer




## Key Simulator Settings

- Same 56Gb/s PAM4 over the 37dB channel
- 3-tap TX w/ 1Vpp swing
- CTLE/AGC FE w/ 7.4dB peaking and 16GHz BW
- 400mV ADC FSR
- Digital 1-tap DFE
- 3mV<sub>rms</sub> ADC input noise
- RJ=300fs<sub>rms</sub>
- No TI effects (more later)



**TX=3-tap, RX=14-tap FFE & 1-tap DFE**

 

**5b ENOB**

 

# Unit SAR ADC with Embedded FFE


 
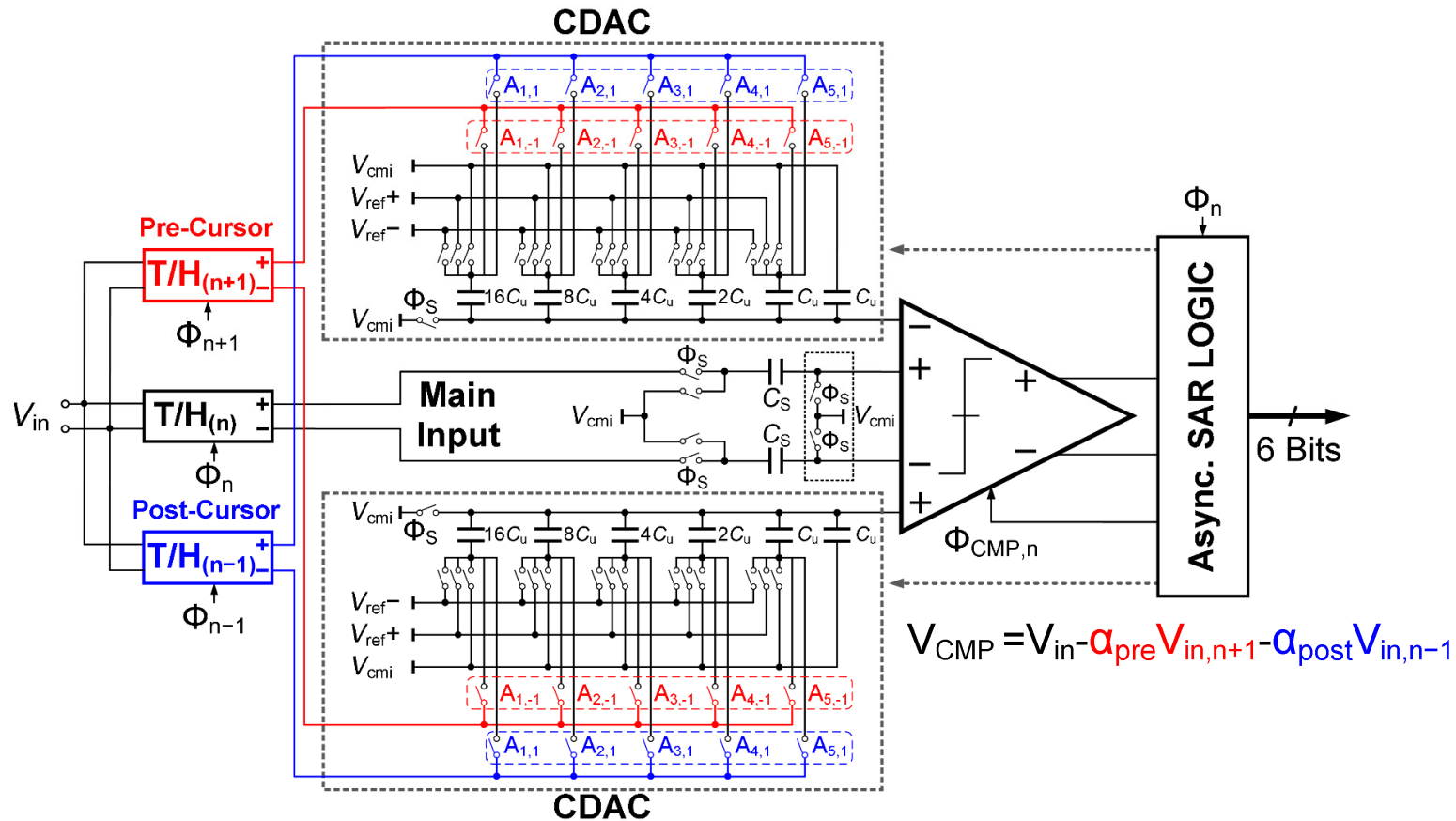


Both pre- and post-cursor taps have  $\sim 33$  LSB range and  $\sim 1.1$  LSB resolution

- ❑ 3-tap FFE efficiently embedded in the SAR CDAC
- ❑ Main trade-off is increased T/H loading (3X)


  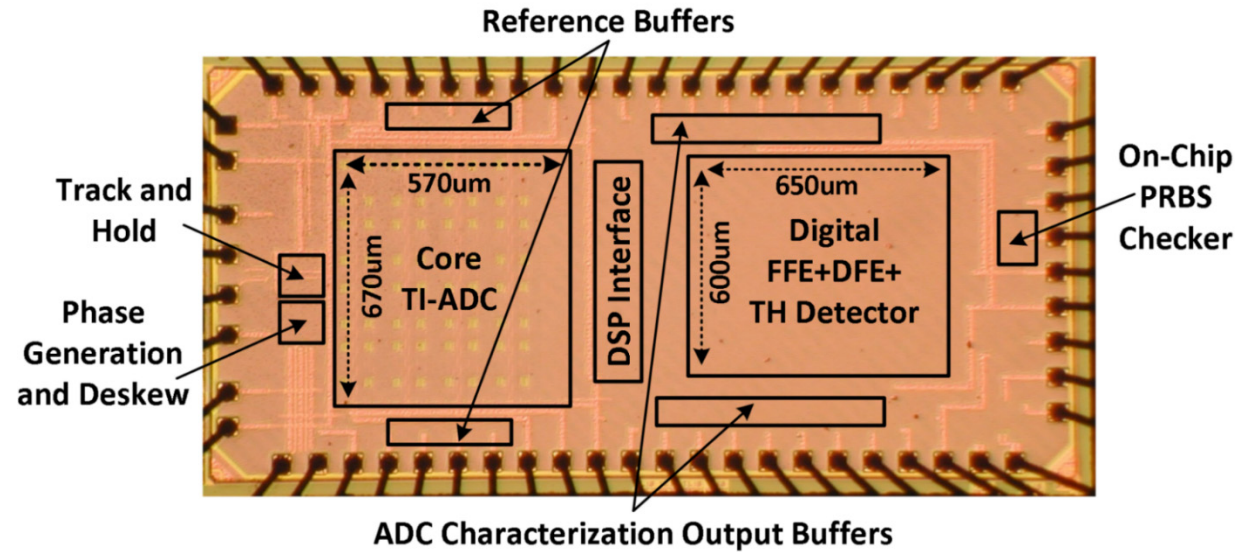
# 10Gb/s NRZ ADC-Based RX 65nm CMOS Prototype



- ❑ 10GS/s 32-way interleaved SAR ADC with embedded 3-tap FFE
- ❑ Digital 4-tap FFE and 3-tap loop-unrolled DFE
- ❑ Embedded equalization alone is sufficient for the two lowest-loss (21, 25dB) channels
- ❑ Additional digital equalization is necessary for the two highest-loss (32, 36dB) channels

# Conclusion

---

- CMOS ADC-based receivers enable powerful digital equalization and symbol detection techniques for high data rate operation over electrical and optical wireline channels
- Time-interleaved ADCs are implemented to achieve the high effective sample rates
  - Calibration is necessary to compensate for channel mismatches
- Digital equalization allows for straight-forward implementation of large-tap digital FFEs, but PAM4 DFEs suffer from large complexity
- Analog front-end (CTLE & VGA) is critical to reduce ADC resolution requirements and match the input signal to ADC FSR
  - Must be designed with sufficient bandwidth and linearity

# Acknowledgement

---

- My graduate students Shengchang Cai, Shiva Kiran, and Yuanming Zhu for assistance in slide preparation
- Intel, Semiconductor Research Corporation, and National Science Foundation for funding support



# Suggested Papers at ISSCC 2018

---

- 6.4: A Fully Adaptive 19-to-56Gb/s PAM-4 Wireline Transceiver with a Configurable ADC in 16nm FinFET
- 6.5: A 64Gb/s PAM-4 Transceiver Utilizing an Adaptive Threshold ADC in 16nm FinFET
- 22.1: A 24-to-72GS/s 8b Time-Interleaved SAR ADC with 2.0-to-3.3pJ/conversion and  $>30$ dB SNDR at Nyquist in 14nm CMOS FinFET

# References

---

## Motivation

- [Cisco Global Cloud Index 2016] (2016). *Cisco Global Cloud Index: Forecast and Methodology*, 2015–2020. [Online]. Available: <http://www.cisco.com>.

## Recent ADC-Based XCVR/RX

- [Frans JSSC 2017] Y. Frans *et al.*, "A 56-Gb/s PAM4 Wireline Transceiver Using a 32-Way Time-Interleaved SAR ADC in 16-nm FinFET," *IEEE JSSC*, vol. 52, no. 4, pp. 1101-1110, Apr. 2017.
- [Gopalakrishnan ISSCC 2016] K. Gopalakrishnan *et al.*, "A 40/50/100Gb/s PAM-4 ethernet transceiver in 28nm CMOS," in *ISSCC Dig. Tech. Papers*, pp. 62-63, Feb. 2016.
- [Cui ISSCC 2016] D. Cui *et al.*, "A 320mW 32Gb/s 8b ADC-based PAM-4 analog front-end with programmable gain control and analog peaking in 28nm CMOS," in *ISSCC Dig. Tech. Papers*, pp. 58-59, Feb. 2016.
- [Rylov ISSCC 2016] S. Rylov *et al.*, "A 25Gb/s ADC-based serial line receiver in 32nm CMOS SOI," in *ISSCC Dig. Tech. Papers*, pp. 56-57, Feb. 2016.

# References

---

## Recent ADC-Based XCVR/RX (cont.)

- [Shafik JSSC 2016] A. Shafik *et al.*, "A 10Gb/s hybrid ADC-based receiver with embedded analog and per-symbol dynamically-enabled digital equalization," *IEEE JSSC*, vol. 51, no. 3, pp. 671–685, Mar. 2016.
- [Zhang JSSC 2015] B. Zhang *et al.*, "A 40nm CMOS 195mW/55mW dual-path receiver AFE for multi-standard 8.5-11.5 Gb/s serial links," *IEEE JSSC*, vol. 50, no. 2, pp. 426–439, Feb. 2015.
- [Cao JSSC 2010] J. Cao *et al.*, "A 500 mW ADC-based CMOS AFE with digital calibration for 10 Gb/s serial links over KR-backplane and multimode fiber," *IEEE JSSC*, vol. 45, no. 6, pp. 1172–1185, Jun. 2010.
- [Varzaghani JSSC 2013] A. Varzaghani *et al.*, "A 10.3-GS/s, 6-Bit flash ADC for 10G ethernet applications," *IEEE JSSC*, vol. 48, no. 12, pp. 3038-3048, Dec. 2013.

# References

---

## High-Speed ADCs

- [Kull ISSCC 2017] L. Kull *et al.*, "A 10b 1.5GS/s Pipelined-SAR ADC with Background Second-Stage Common-Mode Regulation and Offset Calibration in 14nm CMOS FinFET," in *ISSCC Dig. Tech. Papers*, pp. 474-475, Feb. 2017.
- [Kull JSSC 2016] L. Kull *et al.*, "Implementation of low-power 6–8b 30–90GS/s time-interleaved ADCs with optimized input bandwidth in 32 nm CMOS," *IEEE JSSC*, vol. 51, no. 3, pp. 636–648, Mar. 2016.
- [Chen JSSC 2006] S. Chen *et al.*, "A 6-bit 600-MS/s 5.3-mW Asynchronous ADC in 0.13-um CMOS," *IEEE JSSC*, vol. 41, no. 12, pp. 2669-2680, Dec. 2006.
- [Jiang JSSC 2012] T. Jiang *et al.*, "A Single-Channel, 1.25-GS/s, 6-bit, 6.08-mW Asynchronous Successive-Approximation ADC With Improved Feedback Delay in 40-nm CMOS," *IEEE JSSC*, vol. 47, no. 10, pp. 2444-2452, Oct. 2012.
- [Cao JSSC 2009] Z. Cao *et al.*, "A 32 mW 1.25 GS/s 6b 2b/Step SAR ADC in 0.13 um CMOS," *IEEE JSSC*, vol. 44, no. 3, pp. 862-873, Mar. 2009.
- [Liu ISSCC 2010] C. Liu *et al.*, "A 10b 100MS/s 1.13mW SAR ADC with Binary-Scaled Error Compensation," in *IEEE ISSCC Dig. Tech. Papers*, 2010, pp. 386–387.

# References

---

## High-Speed ADCs (cont.)

- [Kull JSSC 2013] L. Kull *et al.*, "A 3.1 mW 8b 1.2 GS/s Single-Channel Asynchronous SAR ADC With Alternate Comparators for Enhanced Speed in 32 nm Digital SOI CMOS," *IEEE JSSC*, vol. 48, no. 12, pp. 3049-3058, Dec. 2013.
- [Cai JSSC 2017] S. Cai *et al.*, "A 25GS/s 6b TI binary search ADC with soft-decision selection in 65nm CMOS," in *Proc. IEEE Symp. VLSI Circuits*, pp. C158-C159, June 2015.

## ADC Fundamentals & Key Circuits

- [Razavi 1995] B. Razavi, *Principles of Data Conversion System Design*, Wiley-IEEE Press, 1995.
- [Dessouky ELET 1999] M. Dessouky and A. Kaiser, "Input switch configuration suitable for rail-to-rail operation of switched op amp circuits," in *Electronics Letters*, vol. 35, no. 1, pp. 8-10, 7 Jan 1999.
- [Kim TCAS-I 2009] J. Kim *et al.*, "Simulation and Analysis of Random Decision Errors in Clocked Comparators," *IEEE TCAS-I: Reg. Papers*, vol. 56, no. 8, pp. 1844-1857, Aug. 2009.

# References

---

## Digital Equalization

- [Toifl ESSCIRC 2014] T. Toifl *et al.*, "A 3.5pJ/bit 8-tap-Feed-Forward 8-tap-Decision Feedback Digital Equalizer for 16Gb/s I/Os," *ESSCIRC*, pp. 455-458, Sept. 2014.
- [Parhi TVLSI 2005] K. K. Parhi, "Design of Multigigabit Multiplexer-Loop-Based Decision Feedback Equalizers," *IEEE TVLSI*, vol. 13, no. 4, pp. 489-493, Apr. 2005.