

---

# **Analog Building Blocks of DC-DC Converters**

Bernhard Wicht  
Institute of Microelectronic Systems  
Leibniz University Hannover, Germany  
bernhard.wicht@uni-hannover.de

February 16, 2020

# Outline

---


- Introduction
- Power Transistors
- Gate Drivers
- Level Shifters
- Control Loop
- System Design

# Outline

---


- Introduction
- Power Transistors
- Gate Drivers
- Level Shifters
- Control Loop
- System Design

# DC-DC Conversion

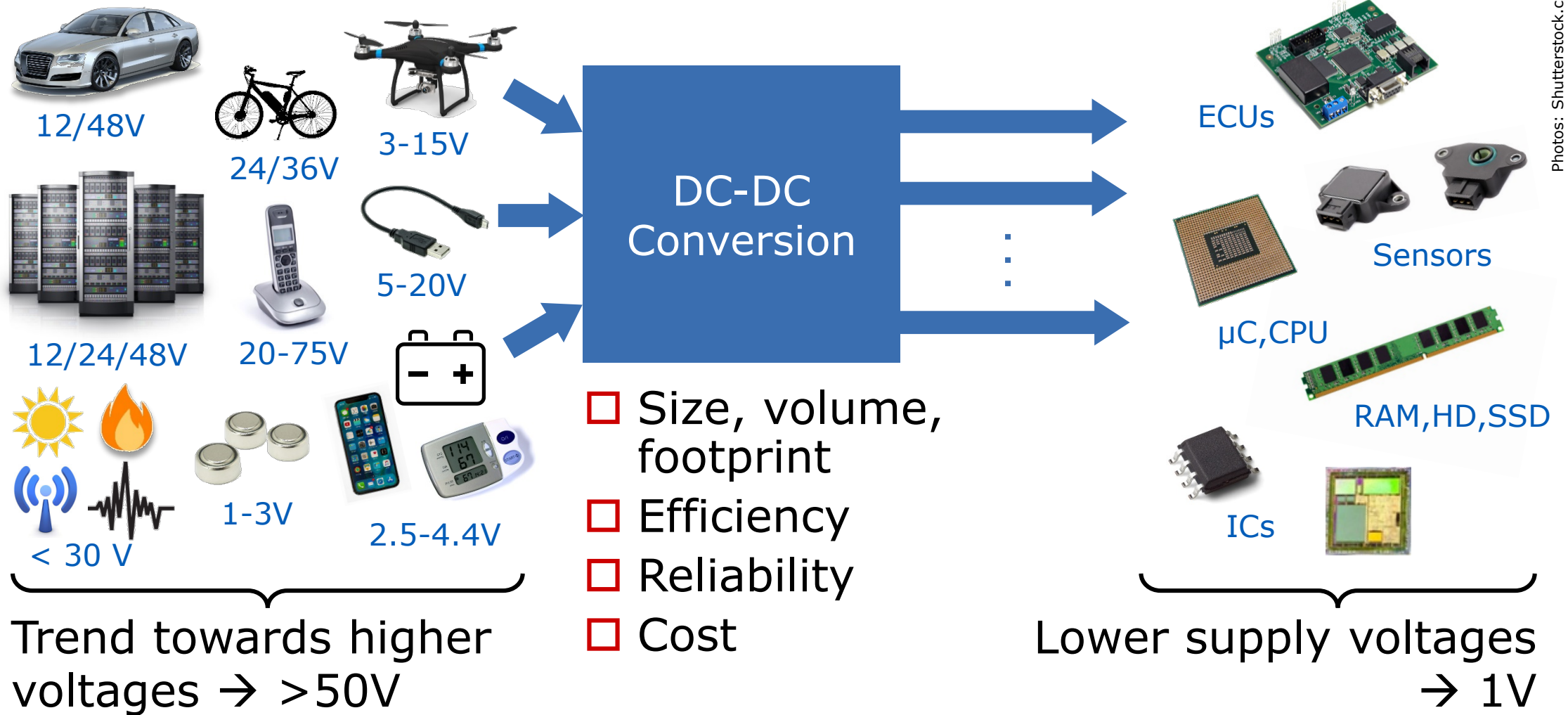

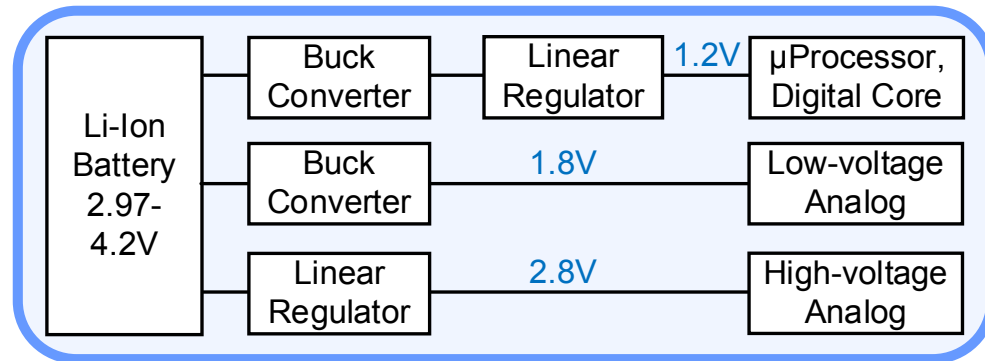
# Power Management Systems

Part of complex ICs or separate power management units: Multiple DC-DC converters to supply  $\mu$ Cs, MPUs, DSPs, analog & mixed-signal circuits



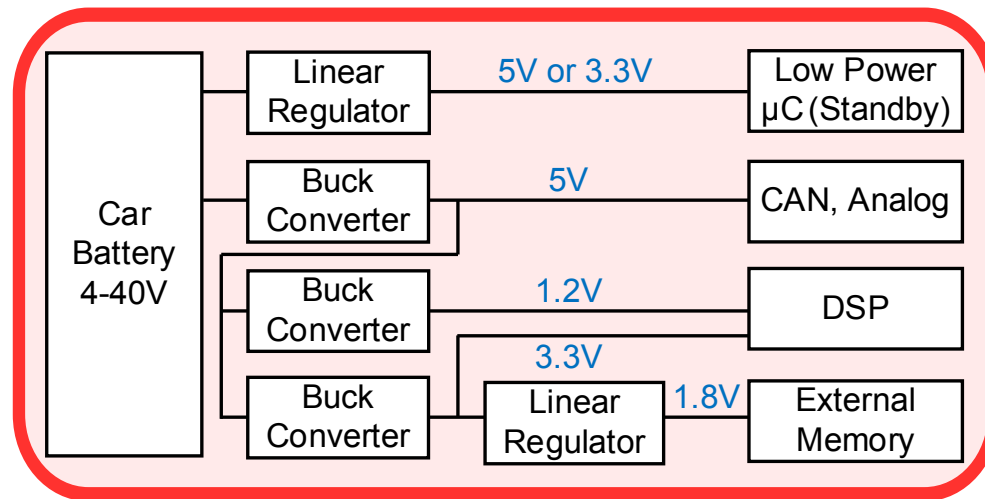Handheld devices, PDAs, consumer products:  
 $V_{in} \sim 4V$ , moderate conversion ratios




Automotive / Industrial, server applications:  
 $V_{in} > 10 - 60V$ , larger conversion ratios
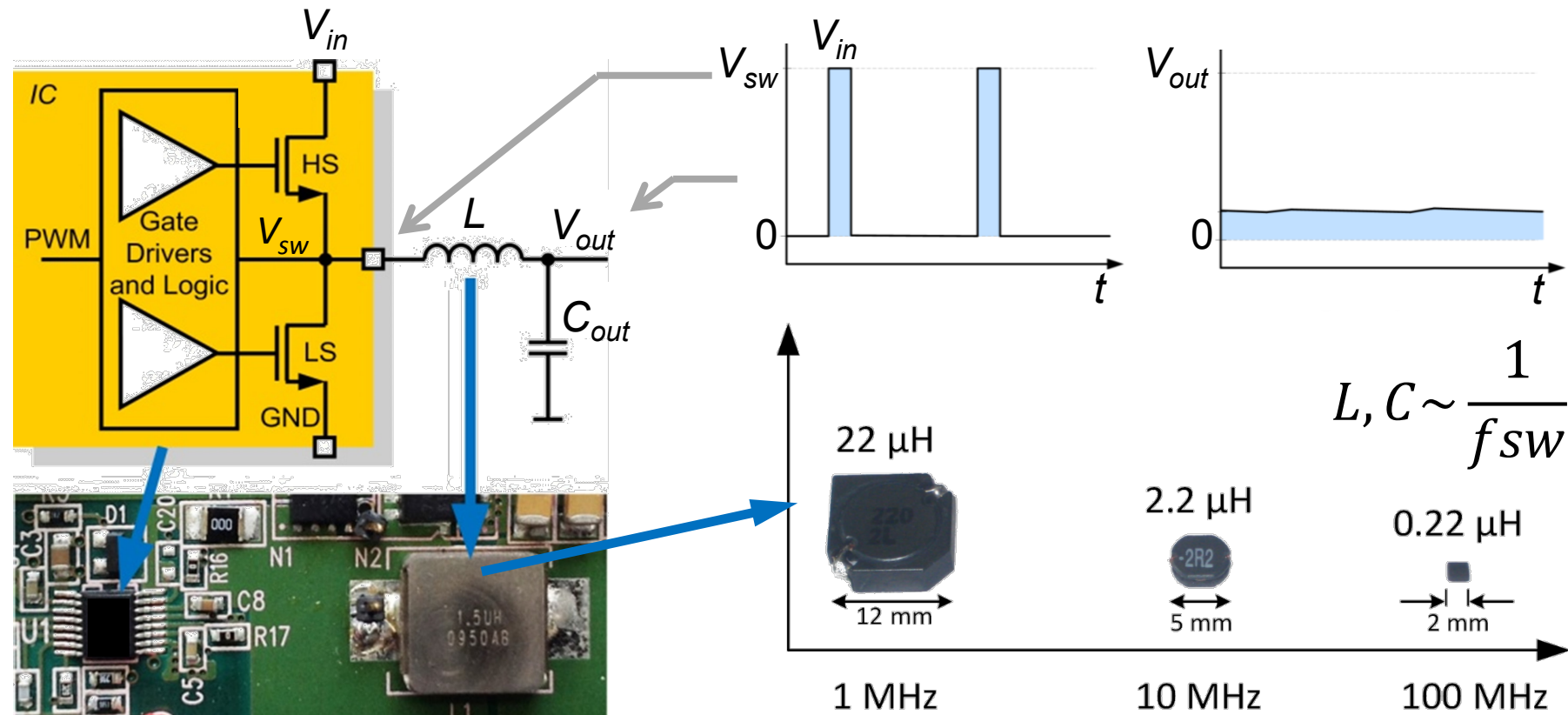
# DC-DC Conversion Fundamentals



Pulse-width modulation: Much higher efficiency than a linear regulator (LDO)

Challenges: Increasing switching losses, EMC, parasitic coupling



# Analog Building Blocks in DC-DC Converters

## Example: DC-DC Buck Converter

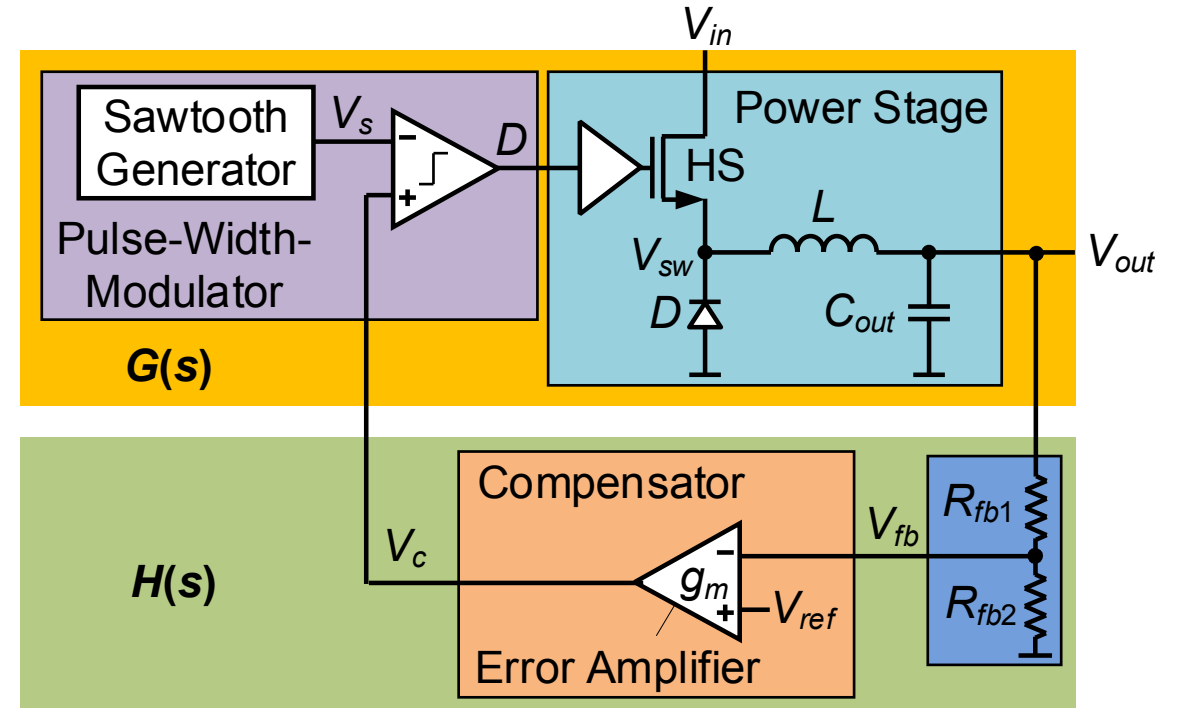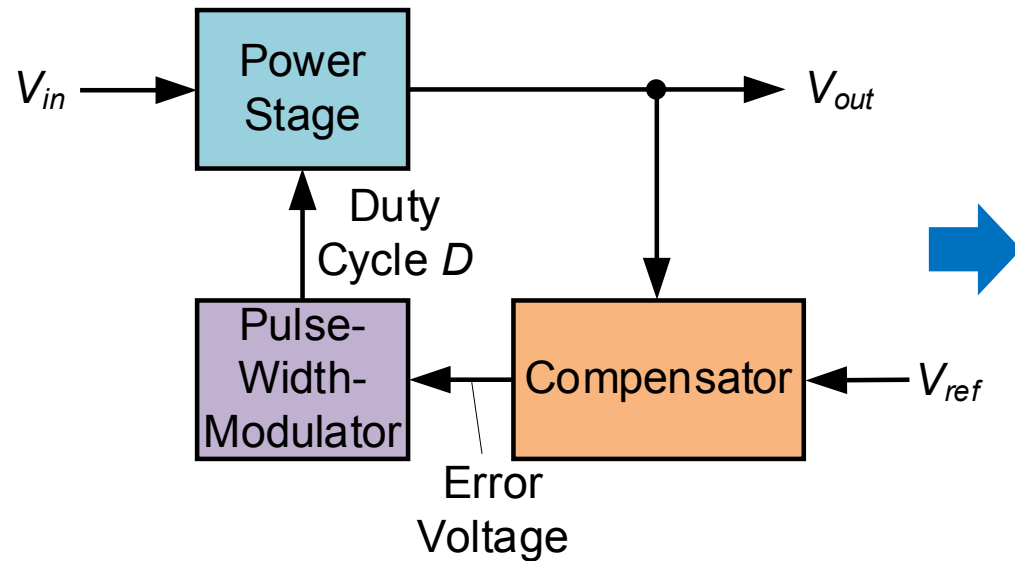


### Blocks of Interest:

- ❑ Power stage: switch, gate driver, level shifter
- ❑ Error amplifier and control loop components
- ❑ Current sensing
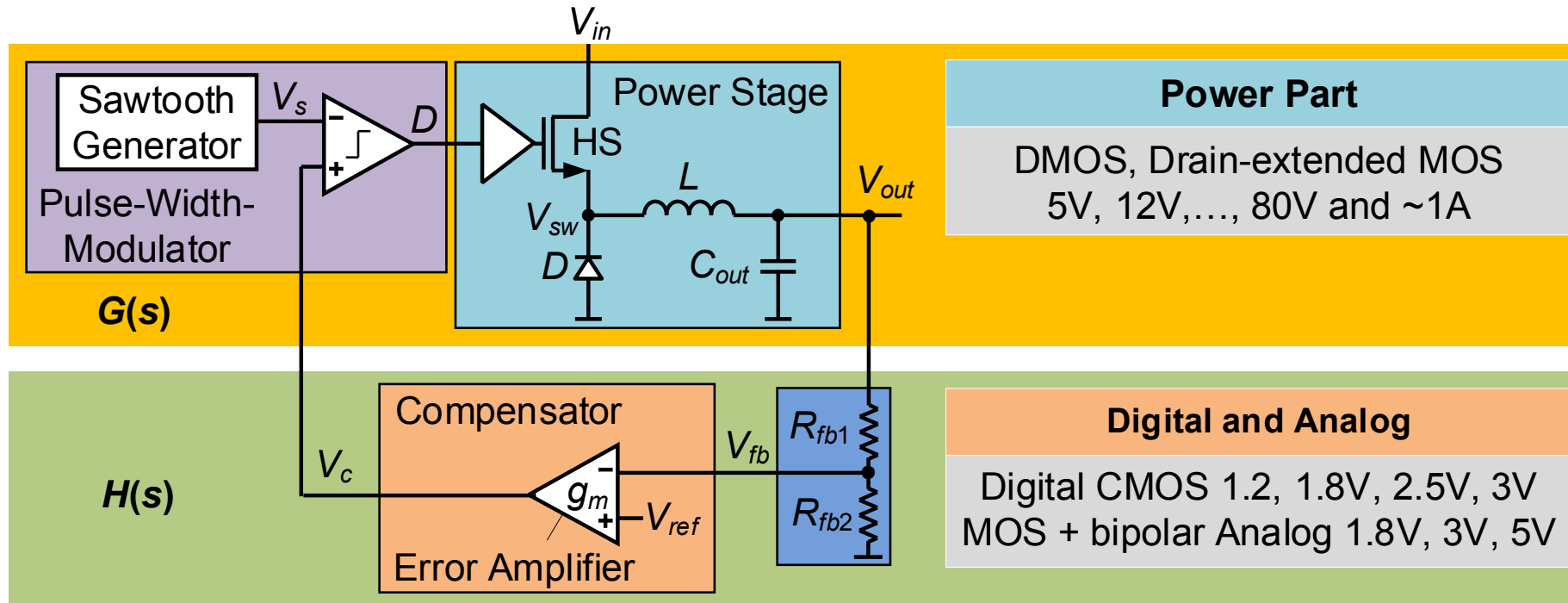
# Technology Options / Devices

- ❑ Various HV, LV transistors
- ❑ Buried layer or trench isolation
- ❑ Zener diodes, Schottky and power diodes
- ❑ OTP memory, EEPROM, flash memory






# Outline

---


- Introduction
- Power Transistors
- Gate Drivers
- Level Shifters
- Control Loop
- System Design

# Power Switch Configurations


Low-Side

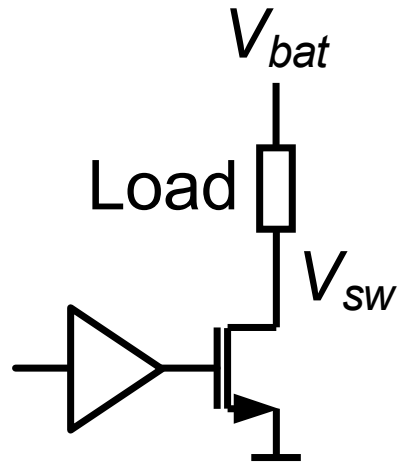


High-Side

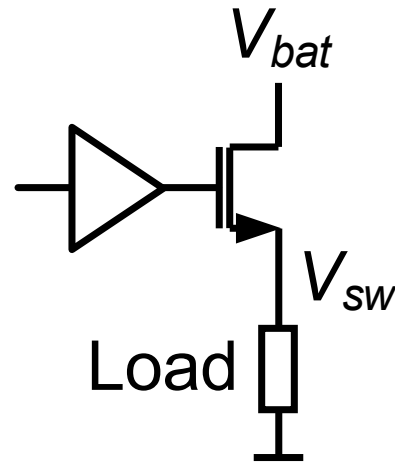

Half-Bridge

 


Full-Bridge (H-Bridge)

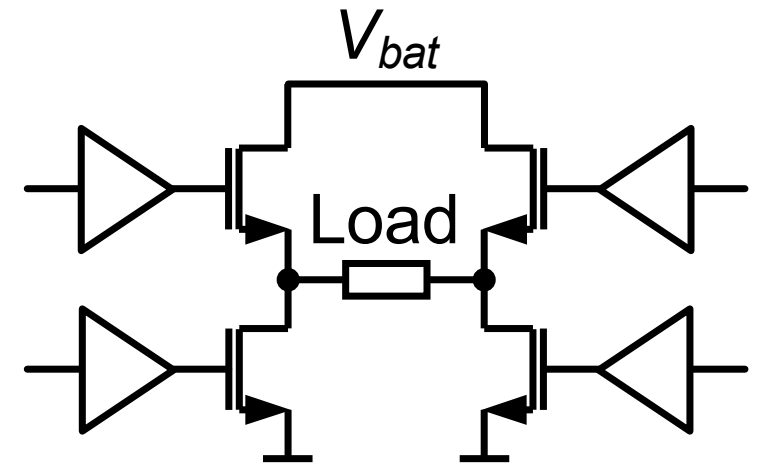

- ❑ Transistors can be on-chip (integrated) or discrete (external)
- ❑ On-chip: Any transistor can be used as a power device, if voltage ratings are suitable
- ❑ High-power and high-voltage applications prefer n-type transistors due to lower on-resistance  $R_{DSon}$

 
# Power Transistors

Discrete power FET  
(external component)



On-resistance  $\sim 10 \dots 100 \text{ m}\Omega$   
Drain currents  $> 1 \dots 10 \text{ A}$


 
Integrated power FET in CMOS  
and BCD technologies



On-resistance  $< 1 \Omega$   
Drain currents  $< 1 \dots 2 \text{ A}$   
FET types for  $> 60 \text{ V}$  available

# Transistor Switching Behavior and Losses

Inductive loads: Four phases

 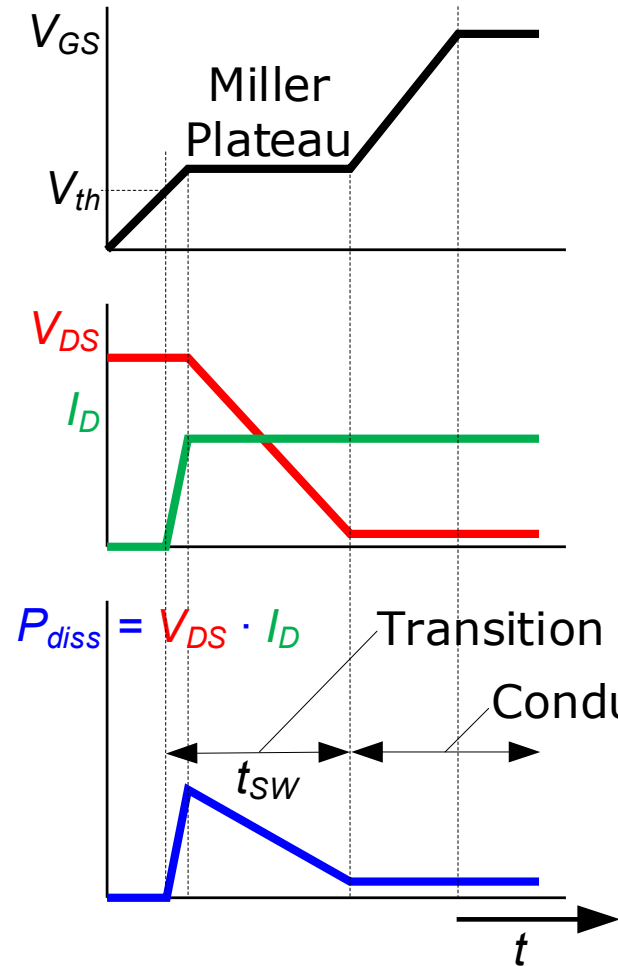

Example:

$$\begin{aligned}
 V_{GS} &= 8\text{V} \\
 V_{th} &= 2\text{V} \\
 I_D &= 0.5\text{A} \\
 R_{DSon} &= 0.5\Omega \\
 V_{DS} &= 12\text{V} \\
 t_{sw} &= 100\text{ns} \\
 f_s &= 500\text{kHz}
 \end{aligned}$$


Transition Losses:  
 $0.5 V_{DS} I_D f_s t_{sw} = 150\text{mW}$

Conduction Losses:  
 $I_D^2 R_{DSon} = 125\text{mW}$



+ gate driver losses (→ see section on gate drivers)
 
# Power MOSFET: DMOS


DMOS = Double Diffused MOS (lateral oder vertical)



  - ❑ Combines low  $R_{DSon}$  ( $< 1\Omega$ ,  $> 1-2A$ ) with large  $V_{DSmax}$  (...100V)
- ❑ Source and gate isolated from substrate  
→ negative voltages possible
- ❑ Parasitic diodes at drain-source and drain-substrate
  - have to be taken care of
  - can be utilized as free-wheeling or power diode
- ❑ Layout: Multiple fingers in parallel (unit transistors)




# Body Diode in Standard CMOS Devices

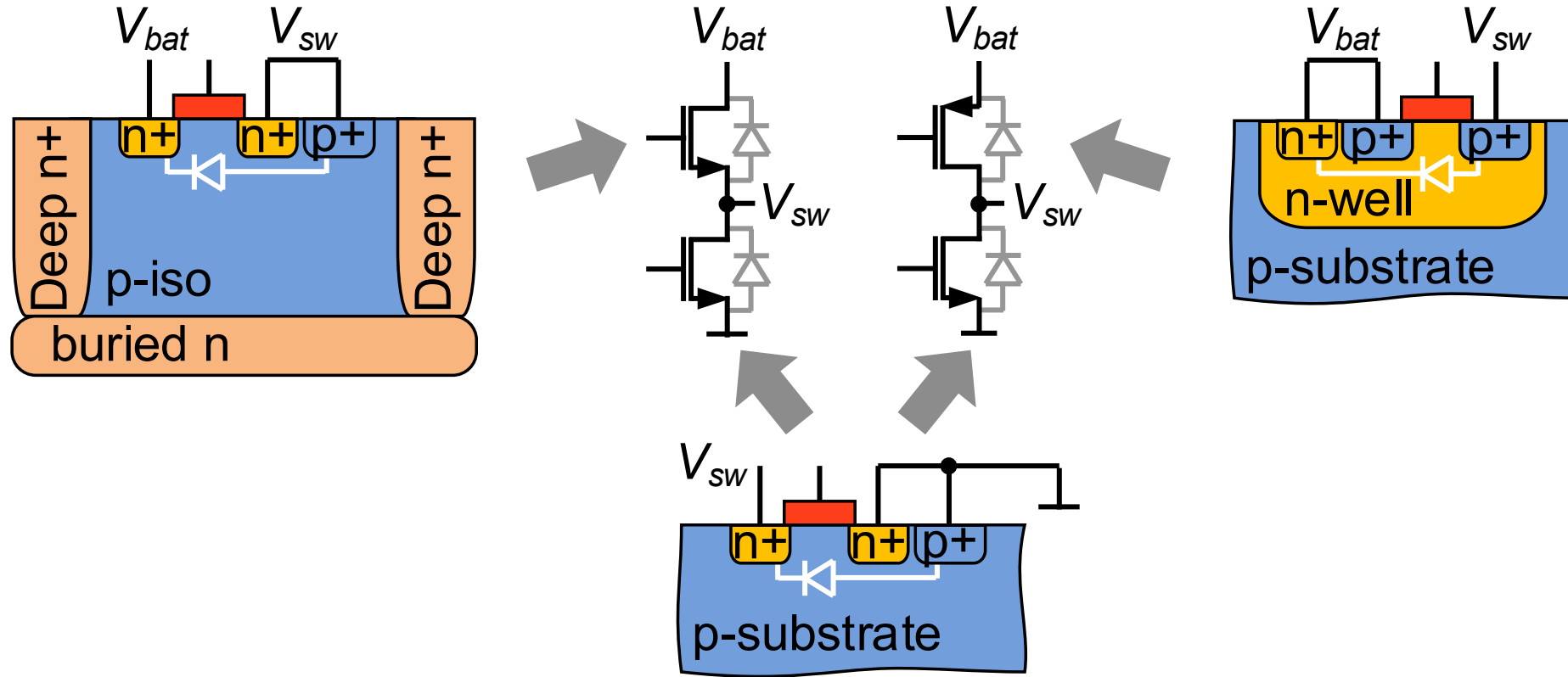

- Body diode: always present and associated with a parasitic bipolar structure
- Inductive switching: losses due to  $V_F$  and reverse recovery
- Risk of back-supply (diode conducts even if switch is off)

 
# Parasitic Effects

For  $V_D < 0$  substrate currents through parasitic npn:




- ❑ Disturbance of other circuits blocks
- ❑ Debiasing, latch-up

Guardring (GR):

 

- ❑ GR around power transistor
- ❑ Nearly zero disturbance at sensitive circuits
- ❑ GR around every drain which goes to an IC Pin
- ❑ Drawback: Layout area / cost

# Isolation of Circuit Blocks

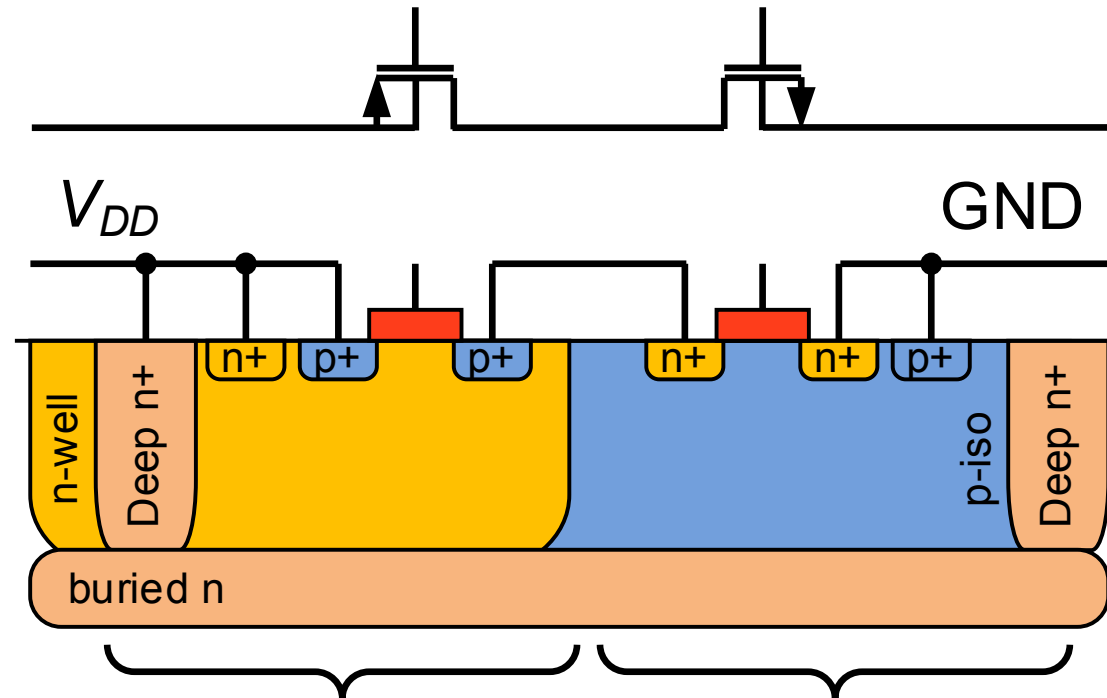


Common isolation of all p-/n-channel devices

- ❑ Rule: Isolate every (sensitive) circuit block (if possible)
- ❑ Shielding against substrate noise coupling
- ❑ Similar to guardring with full "incapsulation"


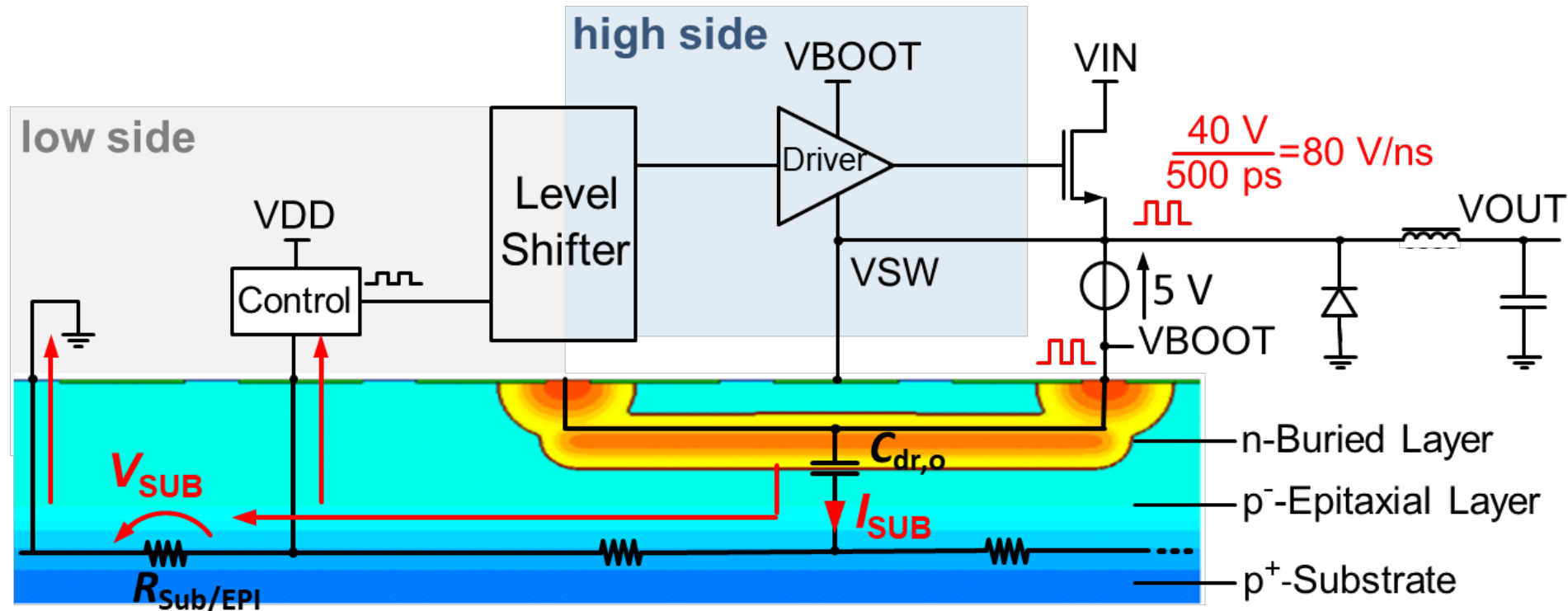
# Substrate Coupling


Voltage slopes  $> 10\text{V/ns}$  cause capacitive charging currents ( $\sim 100\text{mA}$ ) during transition  $\rightarrow$  substrate debiasing  $> 4\text{V}$   $\rightarrow$  malfunction of analog and digital




Back-side metallization reduces coupling by  $\sim 100\%$ , conducting trench by  $\sim 90\%$  (if available), p-Guardring is less efficient but readily available
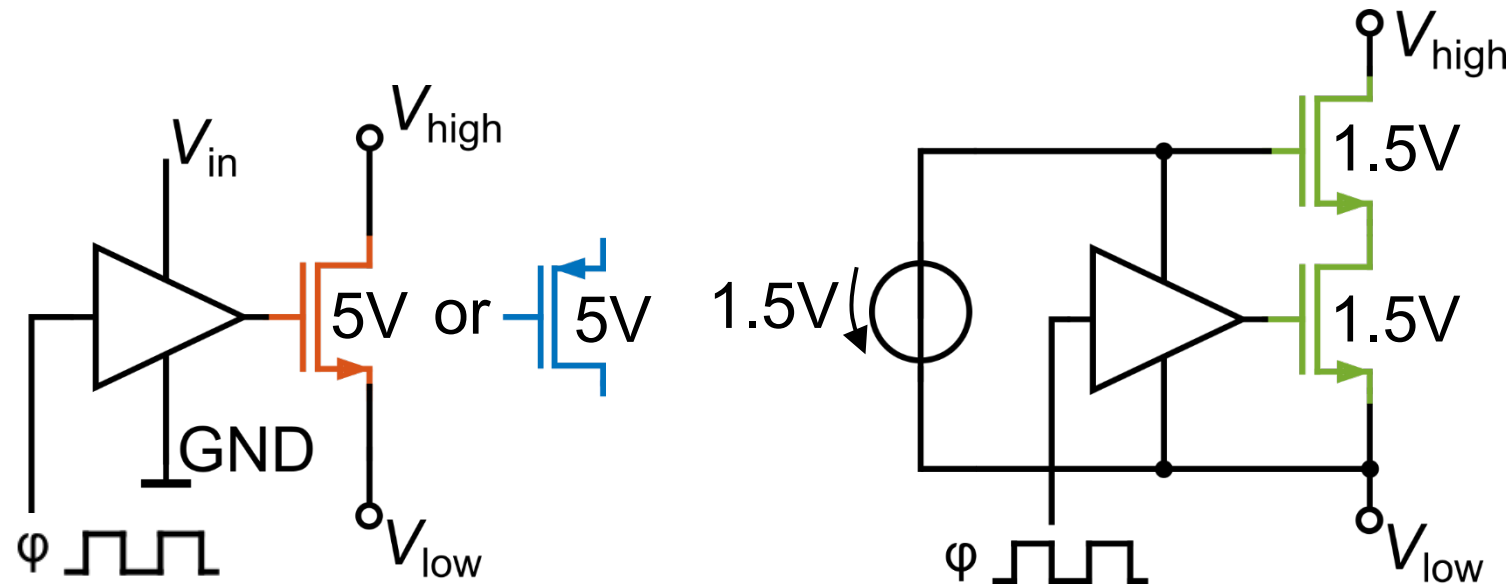
# Switch Stacking

Replace HV devices by stacked LV switches  
→ significant switching loss and area reduction




Renz, ISSCC 2019

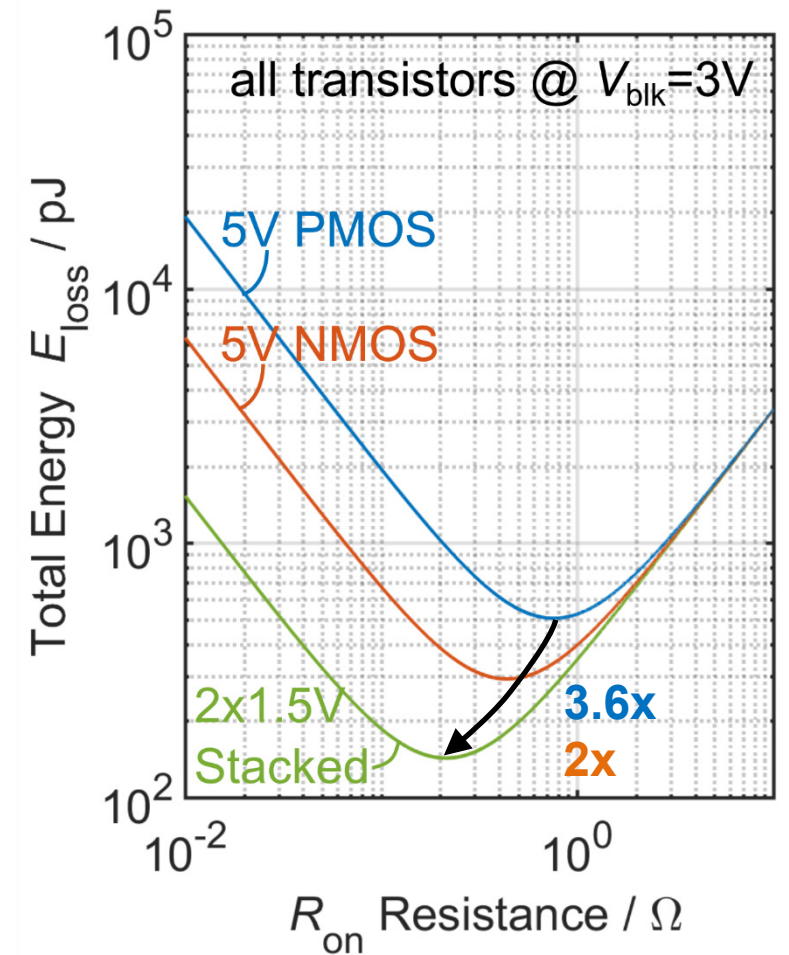


# Useful Configurations

## Back-to-back

 


Prevents back-supply into battery or  $V_{in}$  of LDO or HS switch (but 4x area!)

## Voltage Limitation

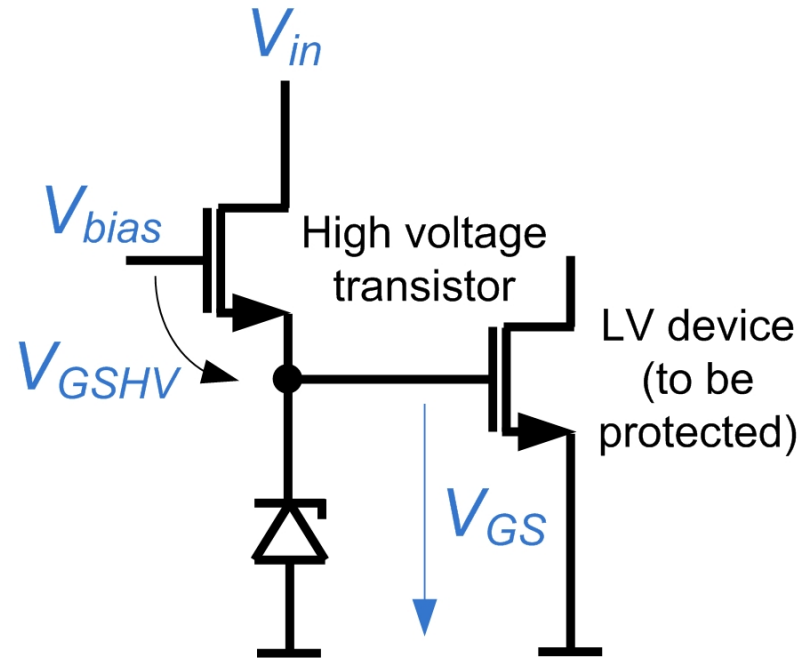

DMOS as cascode to keep  $V_{GS}$  or  $V_{DS}$  of LV devices within max. ratings


## Active Zener

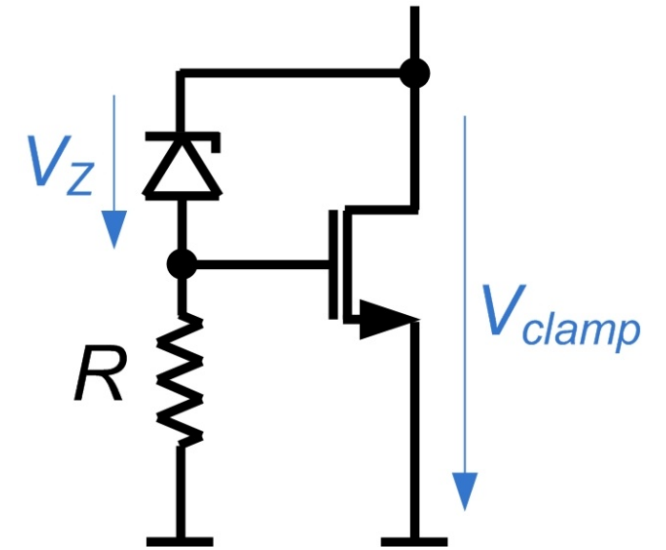

Clamp with large current capability  
 $V_{clamp} = V_Z + V_{GS}$
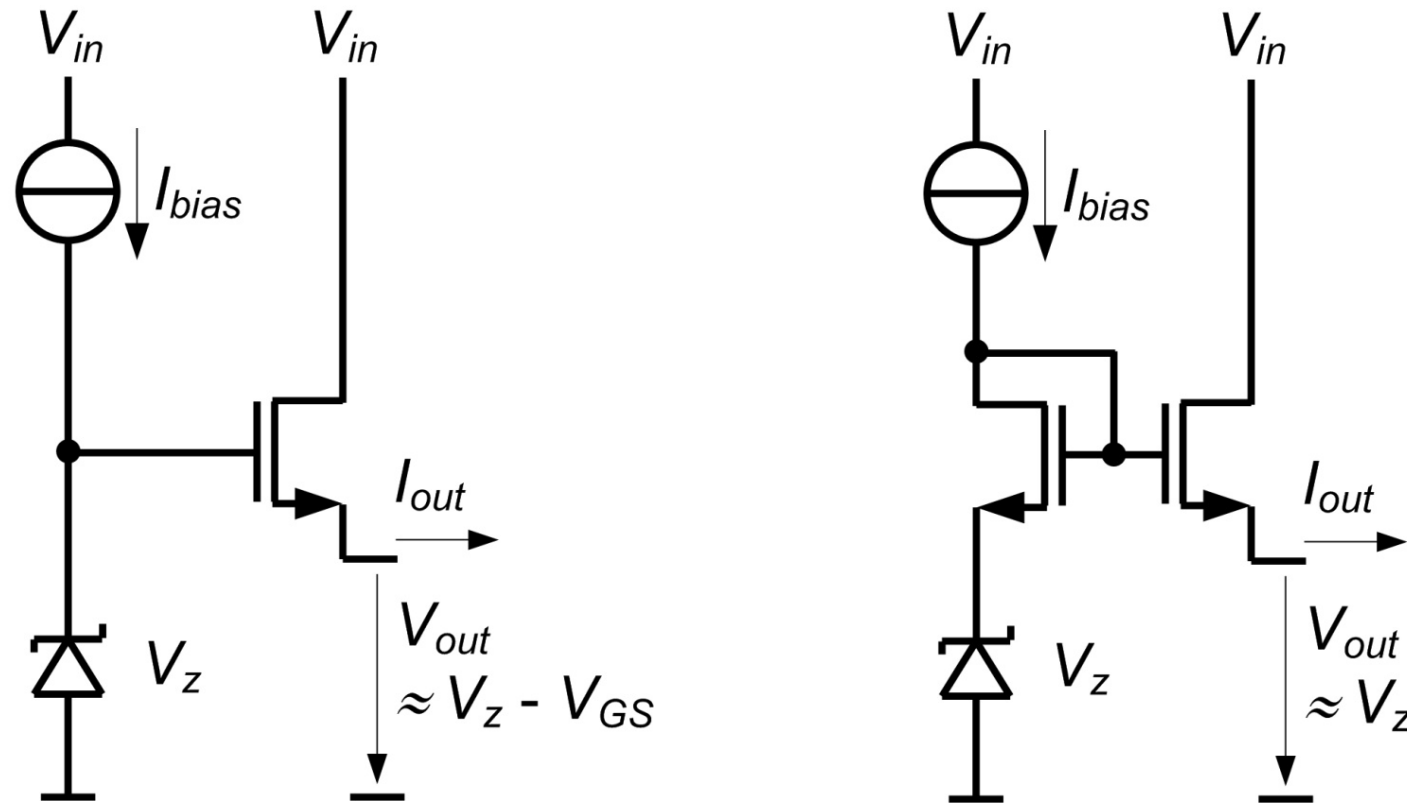
# Shunt Regulator

Alternative to linear regulator, often as a coarse supply for a noncritical digital block, analog standby or as a pre-regulator



“Open loop” → fast, but not very precise

---

# Interim Q&A Session

Please ask questions that you feel is essential to follow the rest of this tutorial

# Outline


---

- Introduction
- Power Transistors
- Gate Drivers
- Level Shifters
- Control Loop
- System Design
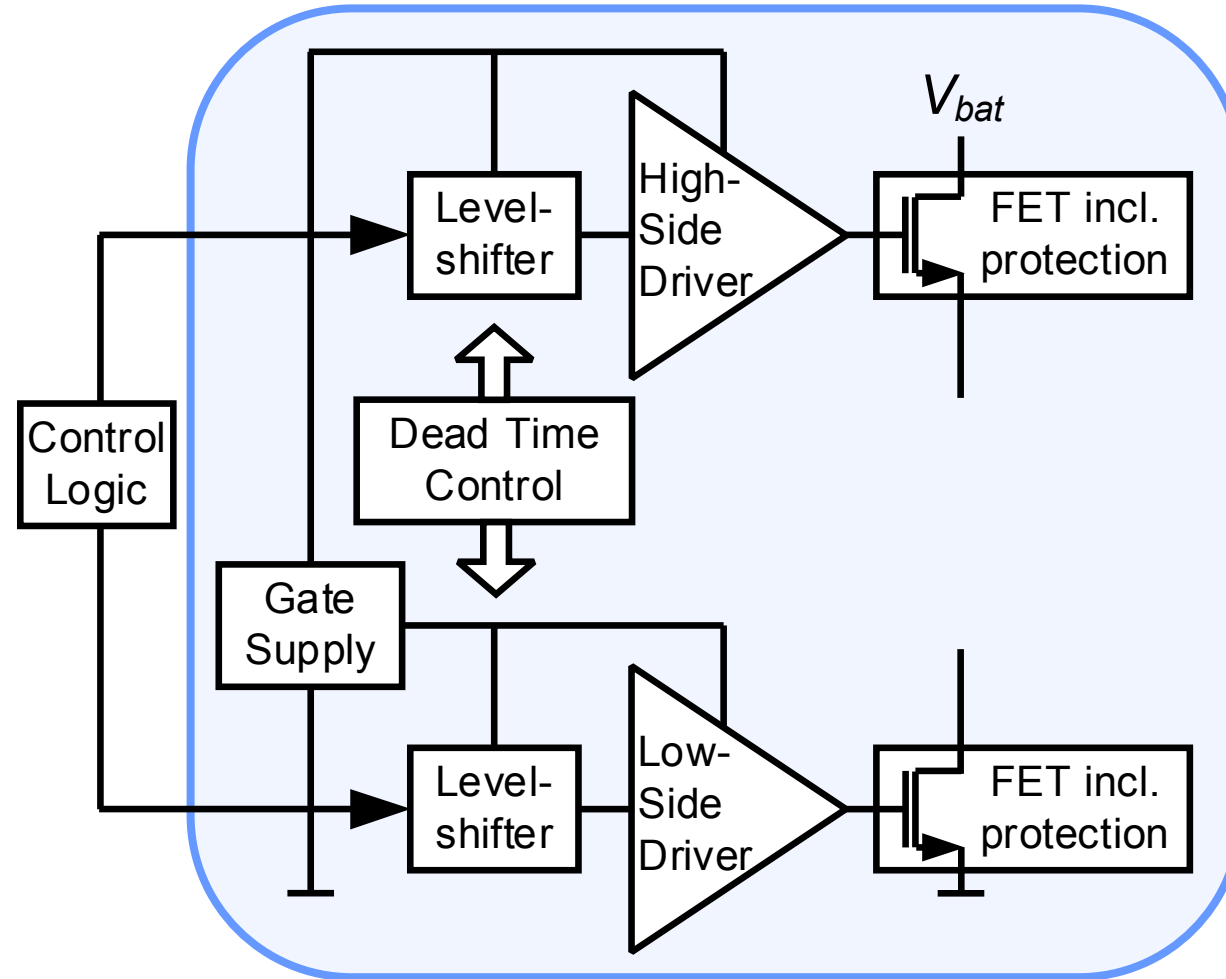
# Gate Driver Block Diagram and Circuits


Main circuit blocks:

- Power FET (n/p-type)
- Protection
- LS / HS driver
- Level shifter
- Gate supply
- Dead time control (only for bridges)


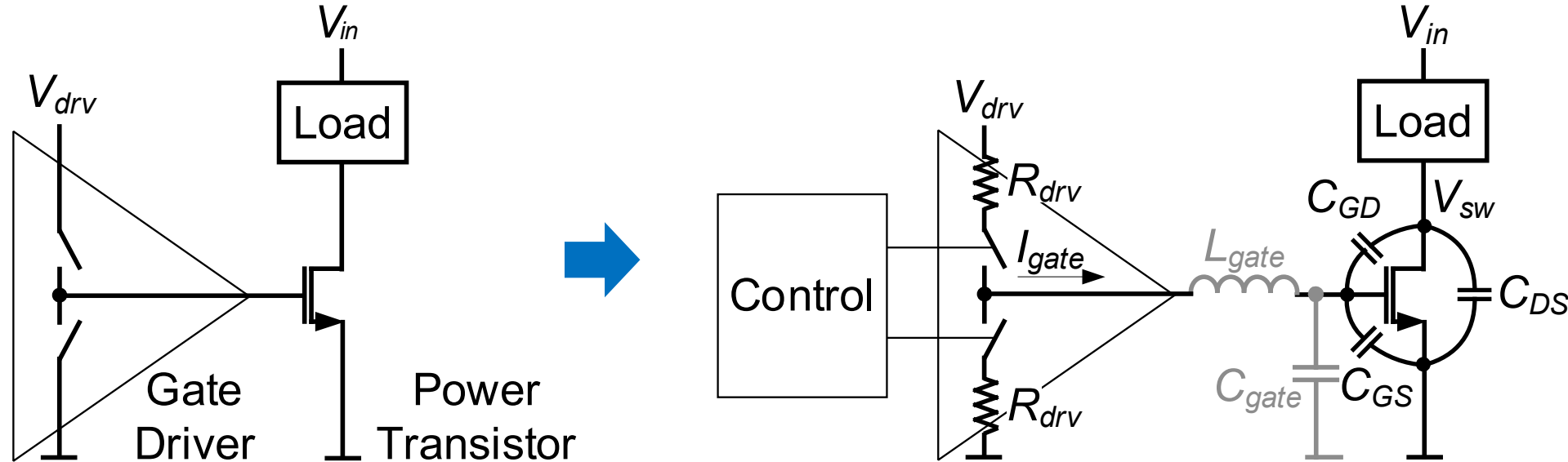
# Gate Driver Fundamentals, Key Parameters

Function: Turn-on/off power switch with sufficient gate overdrive (voltage) and appropriate driving capability (current over time)




- $V_{drv}$  defines the gate-source voltage of the power transistor **5V**
- Gate driver sink / source resistance  $R_{drv}$  (at given  $I_{gate}$ ) **1Ω**
- Sink / source peak current  $I_{peak}$  **1A**
- Parasitic  $L_{gate}$ : speed ↓, dv/dt triggered turn-on, max.  $V_{GS}$






# Low-Side Driver

Circuit structure:

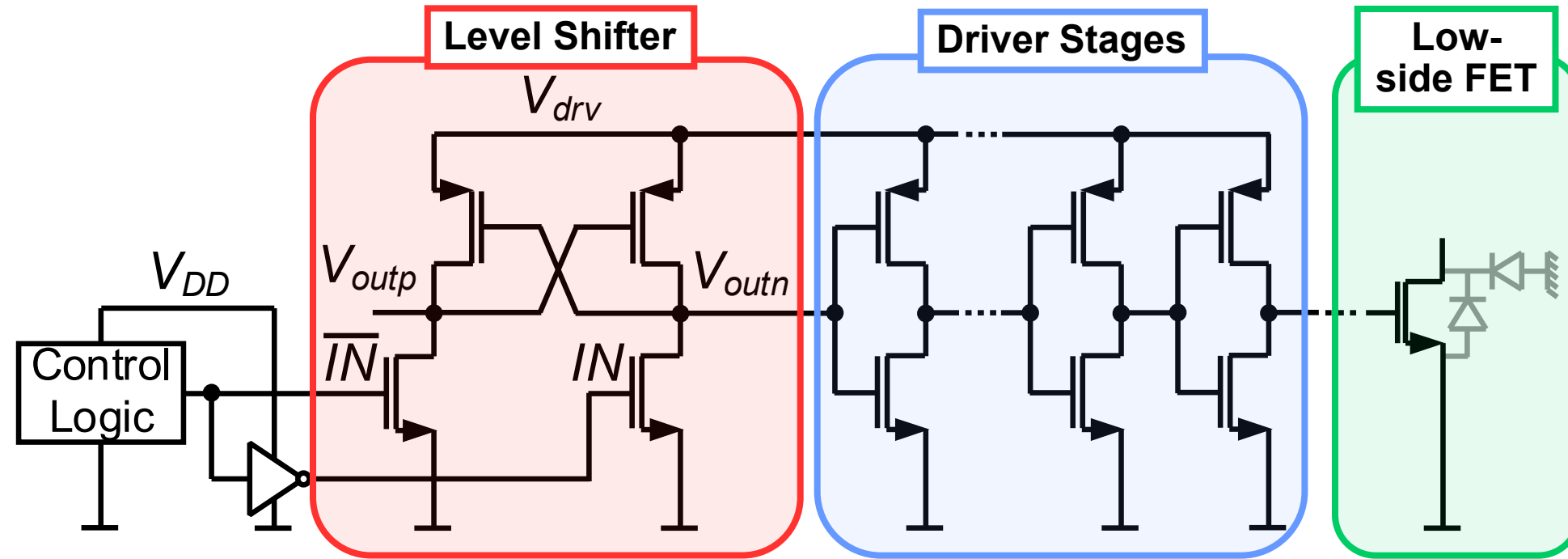

- Level shifter followed by driver stage(s) (CMOS inverter)
- Single driver stage if small power FET (low  $C_{gate}$ )
- Cascaded driver stages if large power FET (large  $C_{gate}$ )

# Example: Integrated Half-Bridge Driver

 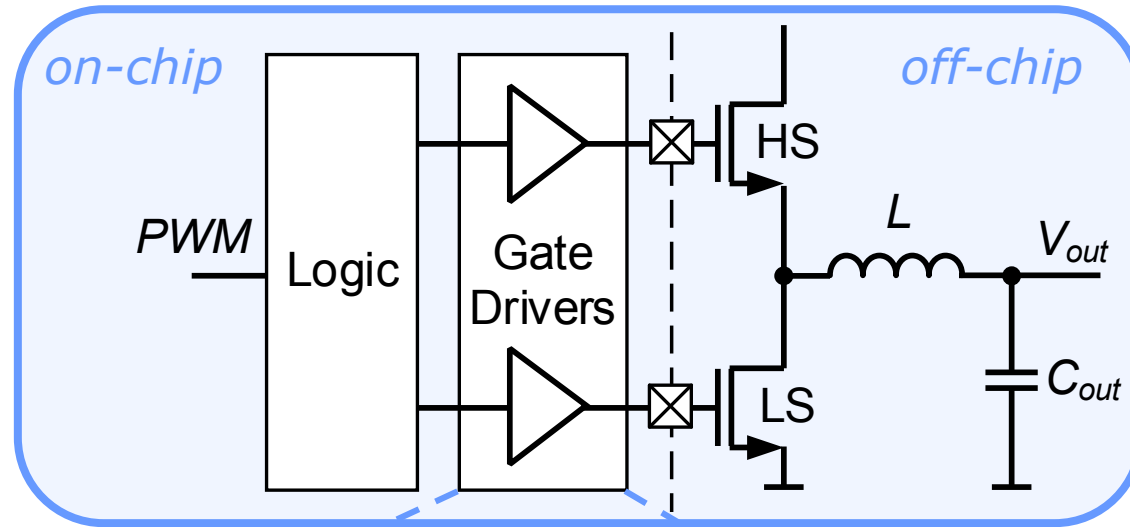 

Driver resistance:  $3\Omega$   
 Driver peak current: 1.5A


Optimization:  $n$  stages, each increasing in driver strength ( $W/L$ ) by factor  $\alpha$

# Cascaded Driver Stages

Different design goals depending on application needs:

- ❑ Design for minimum delay
- ❑ Design for minimum power (correlates with die area)
- ❑ Always: Ensure  $dv/dt$  immunity  $\rightarrow$  adjust  $R_{drv}$  by W/L of last driver stage



Single inverter:

 
  
# Cascaded Driver: Optimization for Speed

Speed optimization:  $n$  stages, each increasing in driver strength ( $W/L$ ) by  $\alpha$

$$t_{direct} = t_{apd} \frac{C_L}{C_G} \quad \Rightarrow \quad t_{cascade} = n t_{apd} \frac{\alpha^{x+1} C_G}{\alpha^x C_G} = n \alpha t_{apd} \quad \Rightarrow \quad \frac{t_{cascade}}{t_{direct}} = \frac{\ln C_L / C_G}{C_L / C_G} \cdot \frac{\alpha}{\ln \alpha}$$



Practical trade-off speed vs. area, power:

Choose  $\alpha = 3 \dots 6$  ( $\gg$  Euler's number  $e$ )  $\rightarrow$  calculate  $n$

Example:  $C_L = 300\text{pF}$ ,  $C_G = 30\text{fF}$ ,  $t_{apd} = 1\text{ns}$

$\rightarrow t_{direct} = 10\mu\text{s}$ ,  $t_{cascade,min} = 25\text{ns}$  ( $\alpha = e$ ,  $n = 9$ ),  $t_{cascade} = 32\text{ns}$  ( $\alpha = 6.3$ ,  $n = 5$ )

# Optimization for Power Efficiency and Area


Optimization for speed does not result in minimum driver power loss:

- ❑ Too many stages: Increasing driver losses  $E_{driver}$
- ❑ Too few stages: Increasing power FET switching losses  $E_{sw}$  due to larger rise/fall times

Options:


- ❑ Fixed-taper buffer  
[Villar, ISCAS 2005]
- ❑ Combination of fixed-taper and variable-taper buffers  
[Vemuru, JSSC Sept. 1991]

 Rule: Fewer stages  $n \rightarrow$  correlates to larger scaling factors  $\alpha \rightarrow 6...>10$



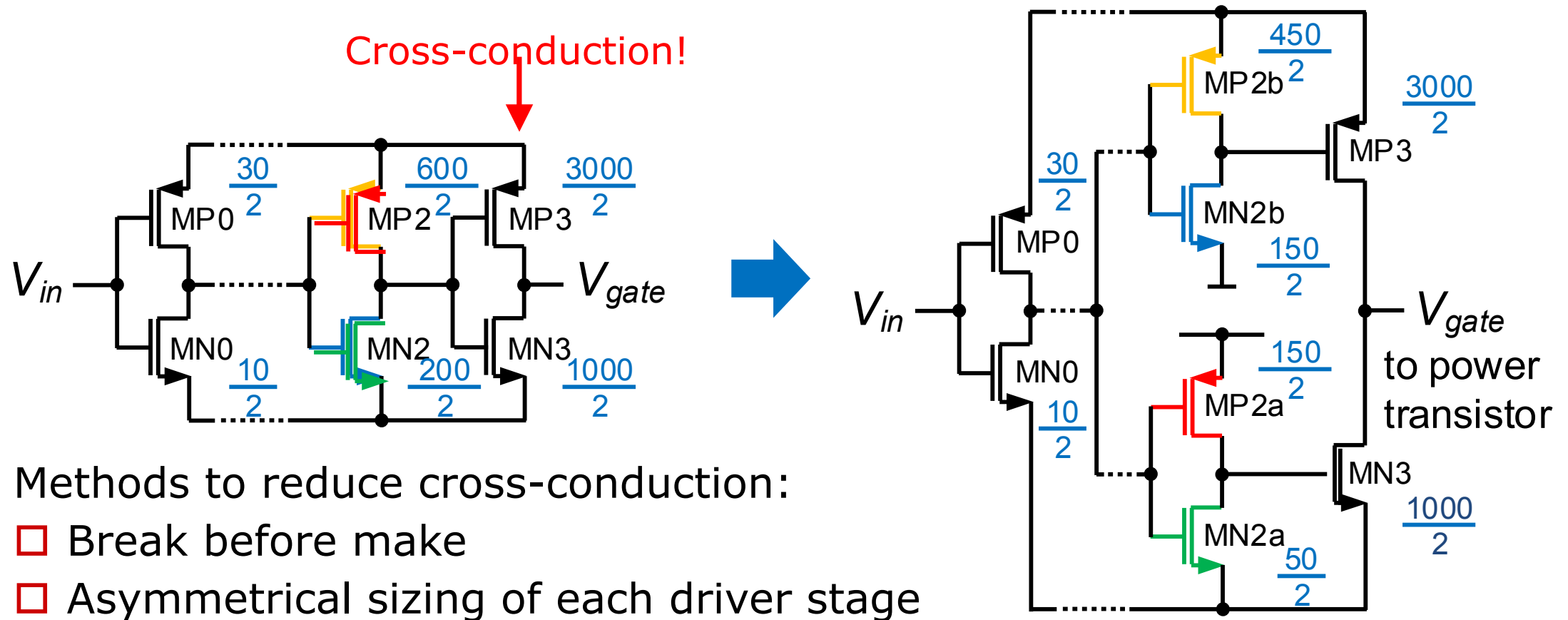
# Optimization for Power Efficiency: Last Stage

Further power reduction by eliminating cross-conduction in last driver stage  
 → separate branches for pull-up / down path → no area penalty



# Reduction of Cross-conduction in Last Stage


## Break before Make

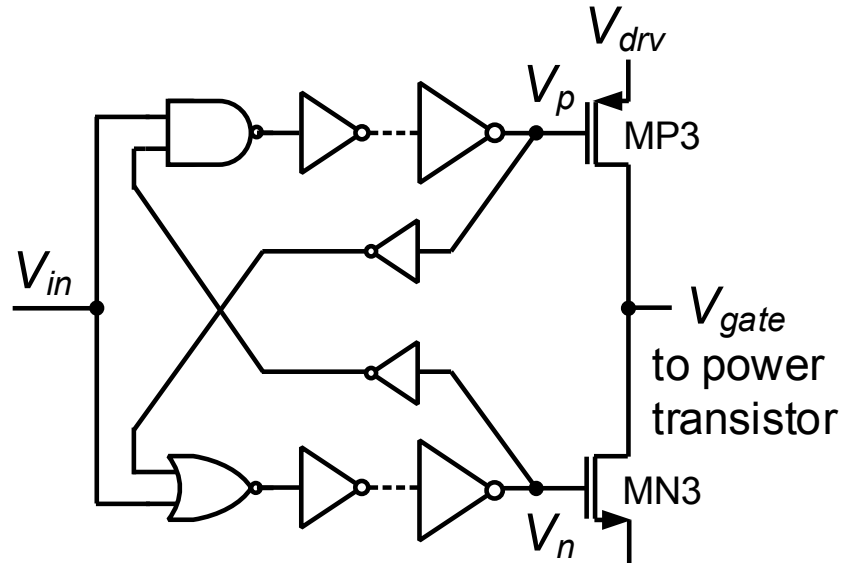

## Drawback:

- Large delay (switching signal propagates 2x through buffer)
- Delay margin required to cope with process variations

## Asymmetrical Driver Sizing

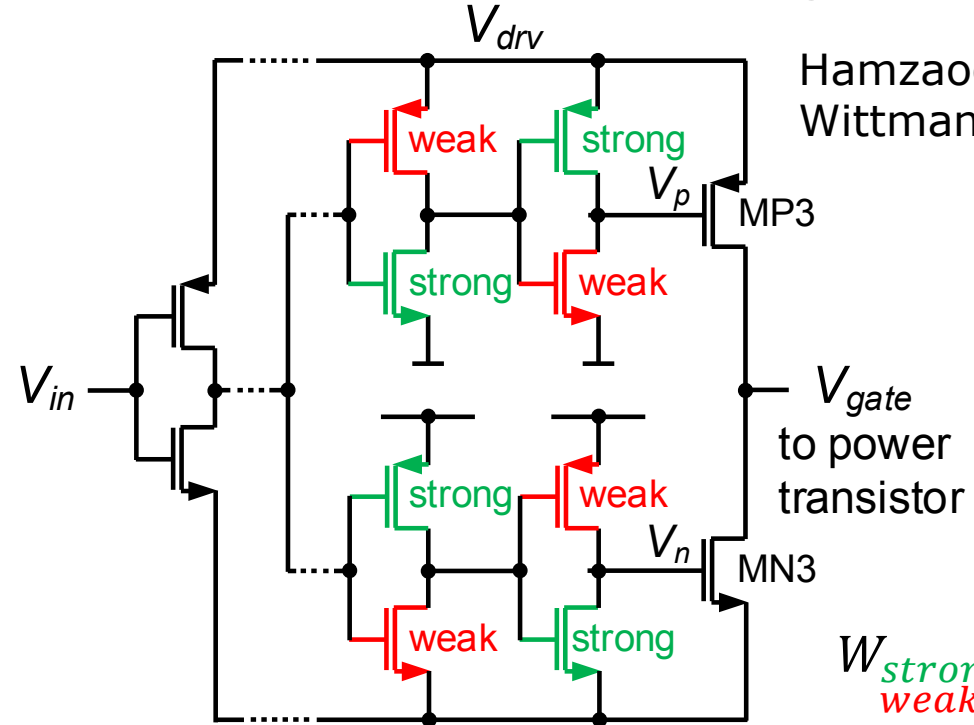

Hamzaoglu TCAS II Oct. 2001  
Wittmann JSSC July 2018


$$W_{\text{strong}}^{\text{weak}} = W \left( 1 \pm \frac{AF}{100\%} \right)$$

Adjust width  $W$  found for optimum speed or losses by asymmetry factor  $AF = 20\text{-}30\%$ :


- Fast Turn-off of MN3, slow turn-on MP3 and in pre-stages

# High-Side Driver

Type 1 Floating Driver

 

Type 2 Referred to ground

 


- n-type power switch: Overdrive needed  $\rightarrow V_{high} = V_{bat} + V_{GS}$
- $V_{high}$  from charge pump, bootstrapping or boost converter



# High-Side Driver


Example for floating driver (Type 1)

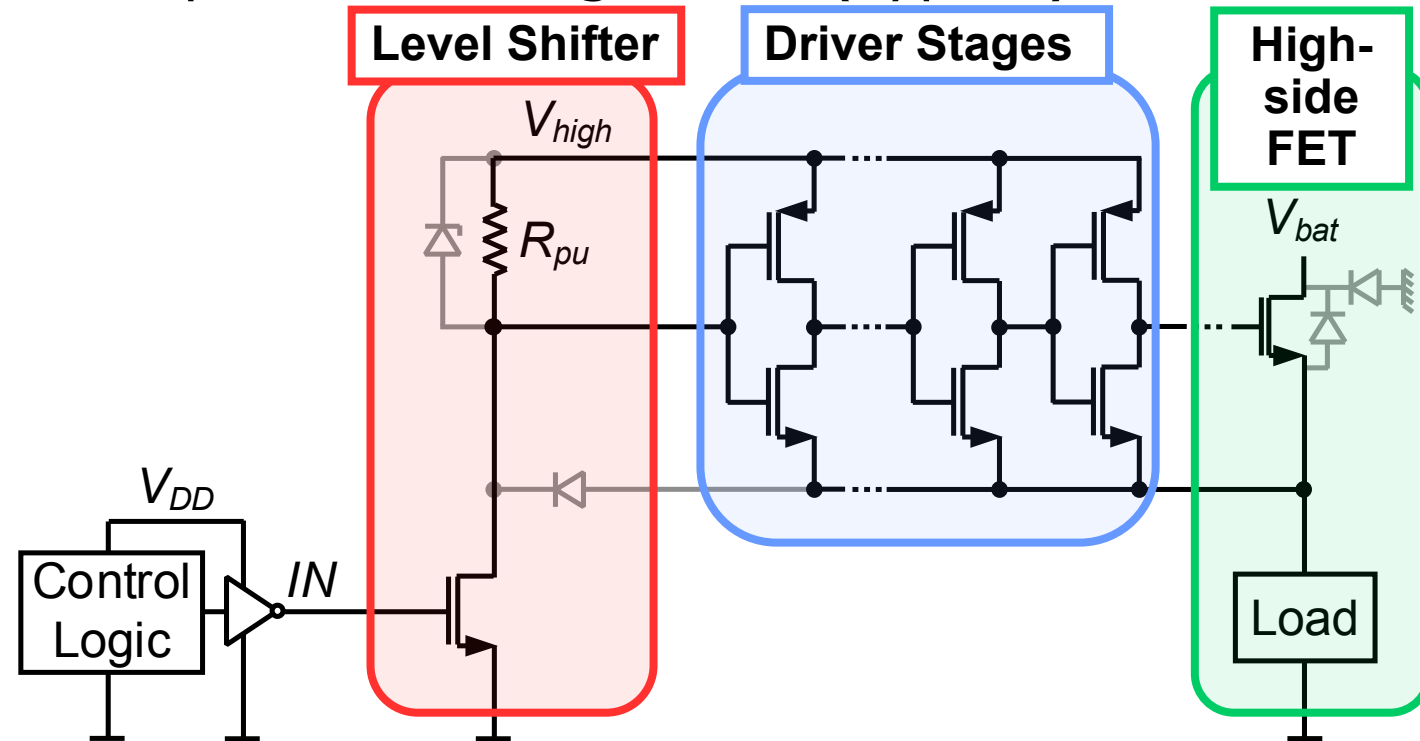

- ❑ Driver stage: Low voltage transistors even for large  $V_{bat}$
- ❑  $R_{pu}$ : Tradeoff between speed and DC current (typ.  $100\text{k}\Omega$ )
- ❑ Diode(s) to clamp voltage across  $R_{pu}$  and limit  $V_{GS}$  for driver
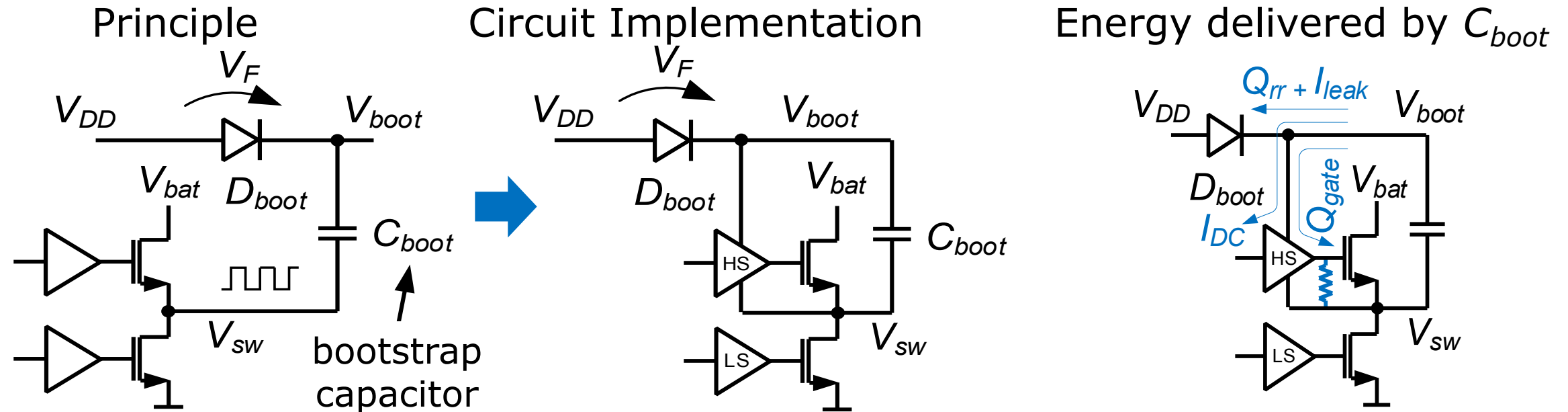
# High-Side Gate Supply: Bootstrapping



Similar to charge pump with oscillator replaced by half-bridge (power stage)



- $C_{boot}$  supplies high-side driver  $\rightarrow V_{boot} = V_{bat} + V_{DD} - V_F$
- $C_{boot}$  gets recharged if high-side is off (low-side on,  $V_{SW} = 0V$ ) from  $V_{DD}$  through bootstrapping diode  $D_{boot}$
- Sizing:  $C_{boot} \geq (Q_{gate} + Q_{rr} + I_{boot} / f_{sw}) / \Delta V_{boot}$

Example:  
 $Q_{gate} = 10nC, Q_{rr} = 1nC,$   
 $I_{boot} = 500\mu A, \Delta V_{boot} =$   
 $0.1V @ f_{sw} = 500kHz$   
 $\rightarrow C_{boot} \geq 120nF$


# Power Stage Dead Time Control

 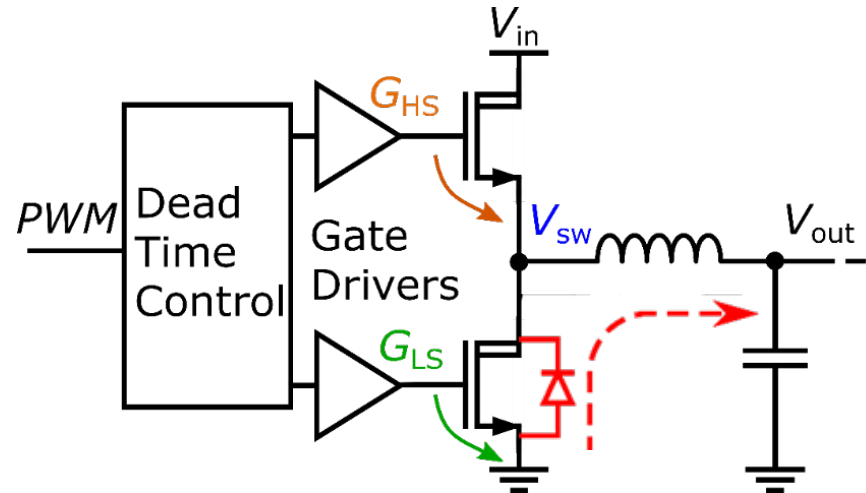

- Turn off one FET → then turn on other FET with dead time in between
- To avoid cross-conduction (damage!) and minimize losses
  - Cross-currents, body-diode ( $V_F$ ,  $Q_{rr}$ ), zero-voltage switching, >25% loss reduction
- Optimum dead time dependent depends on operating point ( $V_{in}$ , load,...)
  - Constant delay (with trimming)
  - Adaptive delay: Sensing of off-state → then turn on other FET
  - Predictive delay: Cycle-by-cycle control, complex


# Dead Time Control Concepts (1)

## Constant Delay (two examples)

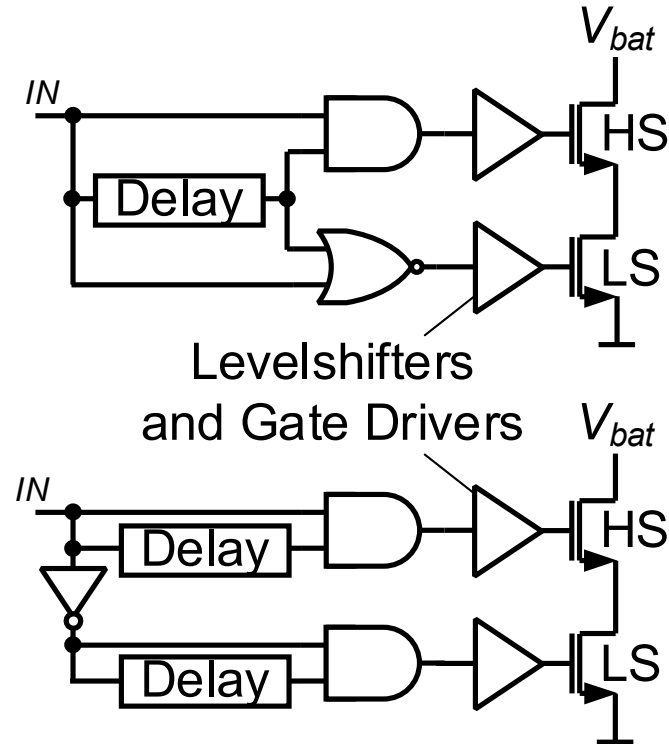

- ❑ Worst case margin  $\rightarrow$  large  $t_{dead}$
- ❑ delay trimming  $\rightarrow$  length of inverter chain



## Adaptive Dead Time Control

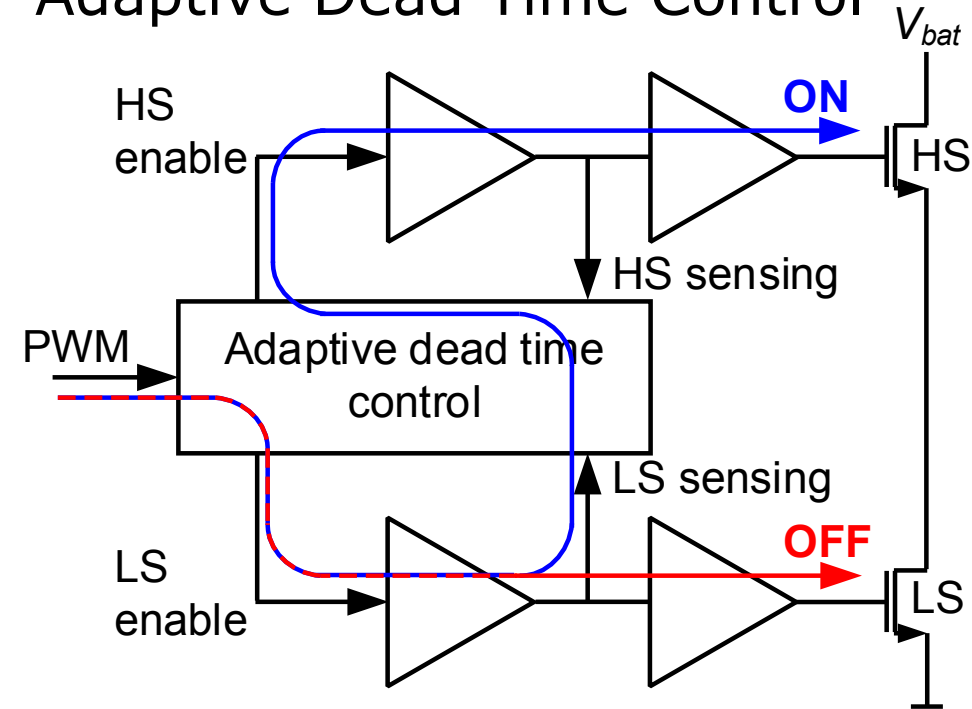

- ❑ Off-state detection at cascaded drivers allows shorter  $t_{dead}$
- ❑ LS sensing: Simple inverter  
HS sensing: Down-level shifter
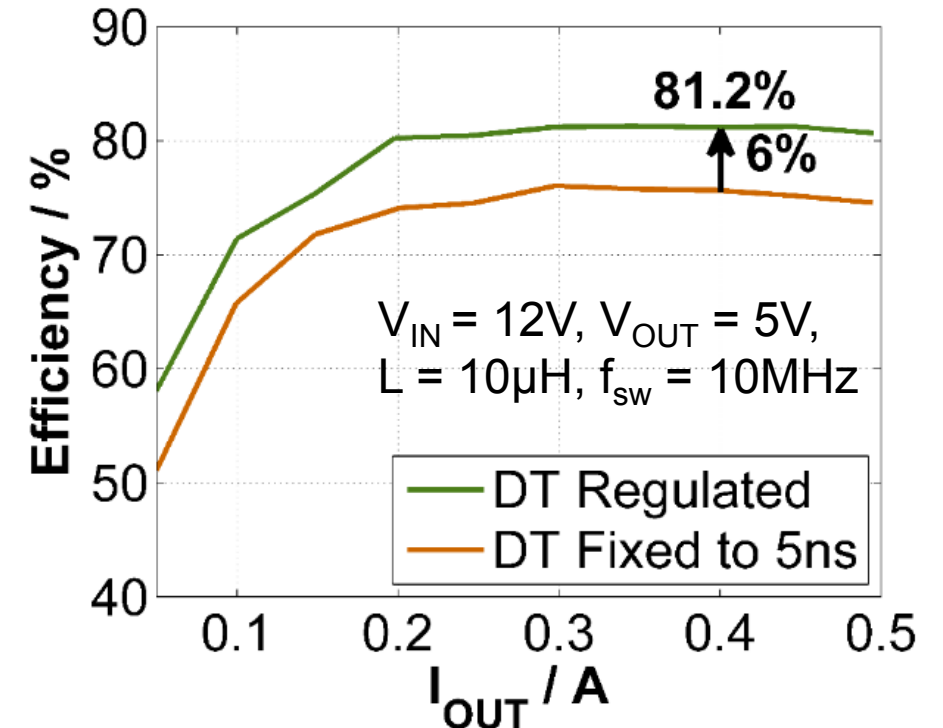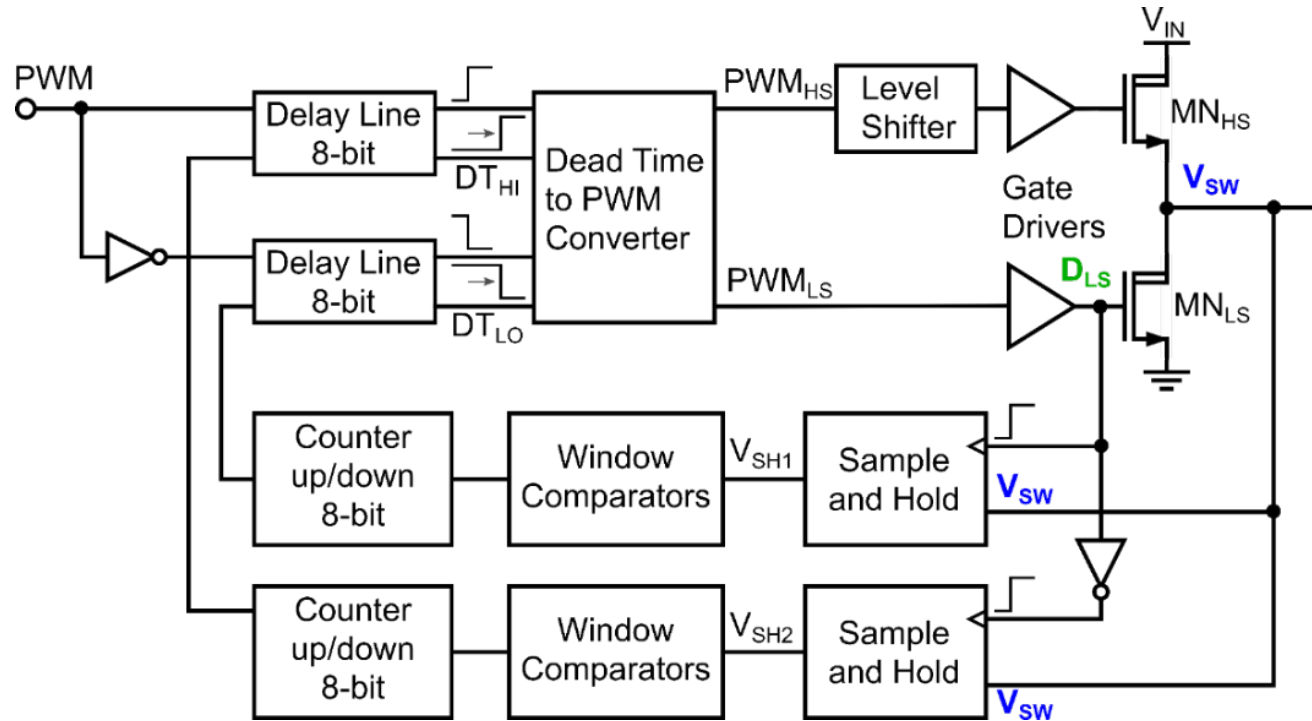
# Dead Time Control Concepts (2)

Predictive mixed-signal dead time control [Wittmann JSSC July 2016]:



- ❑ 10MHz buck converter, 125ps dead time resolution by inverter delay line
- ❑ Low-side turn-on if  $V_{SW} \sim 0V$ , sensed by S&H, no body diode conduction
- ❑ Loss reduction of up to 30%  $\rightarrow$  6% higher efficiency at 10 MHz

# Outline


---

- Introduction
- Power Transistors
- Gate Drivers
- Level Shifters
- Control Loop
- System Design

# Basic Level Shifter Configurations


Signal transmission from low side (control) to high side (power stage)

Resistor-based Level Shifter

 


- DC current
- + Simple, small
- + Default state

Cross-coupled Level Shifter

 

- + No DC current
- Slow and large area
- No default state




High-voltage version with cascodes

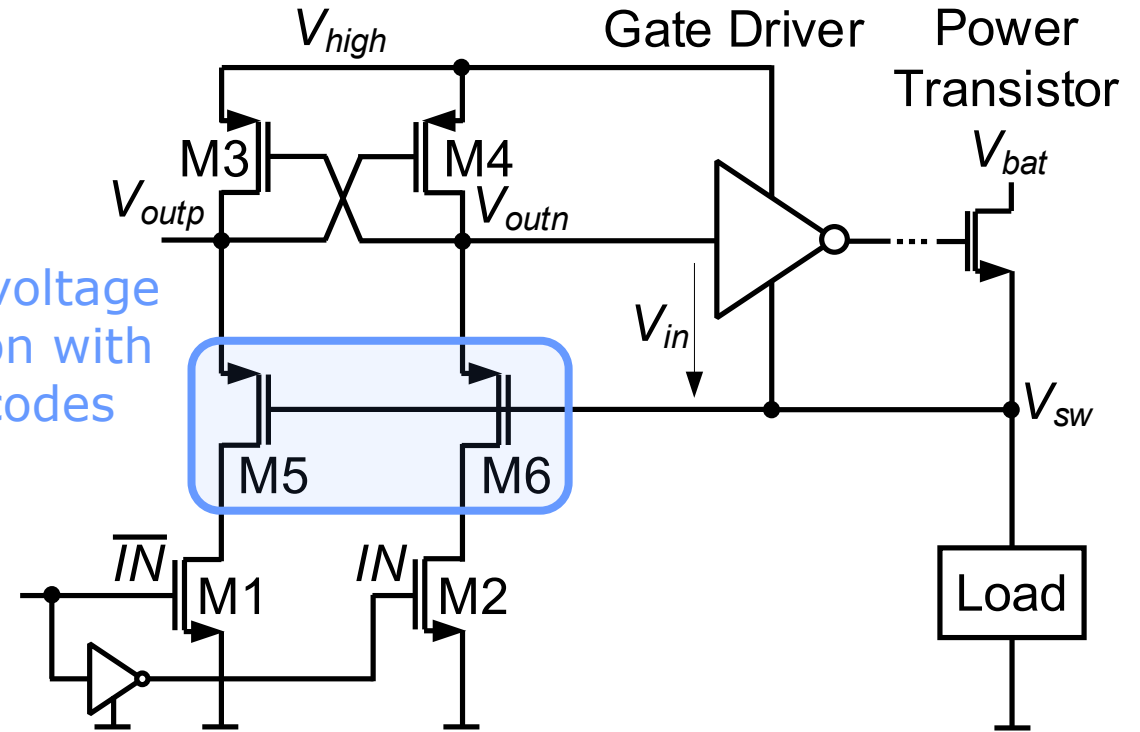

- Drawback:  $V_{in} \neq V_{sw}$   
 → weak '0' level at gate driver input → cross-currents!

# Cross-coupled Level Shifter with Full HS Swing

Moghe, JSSC Feb. 2011

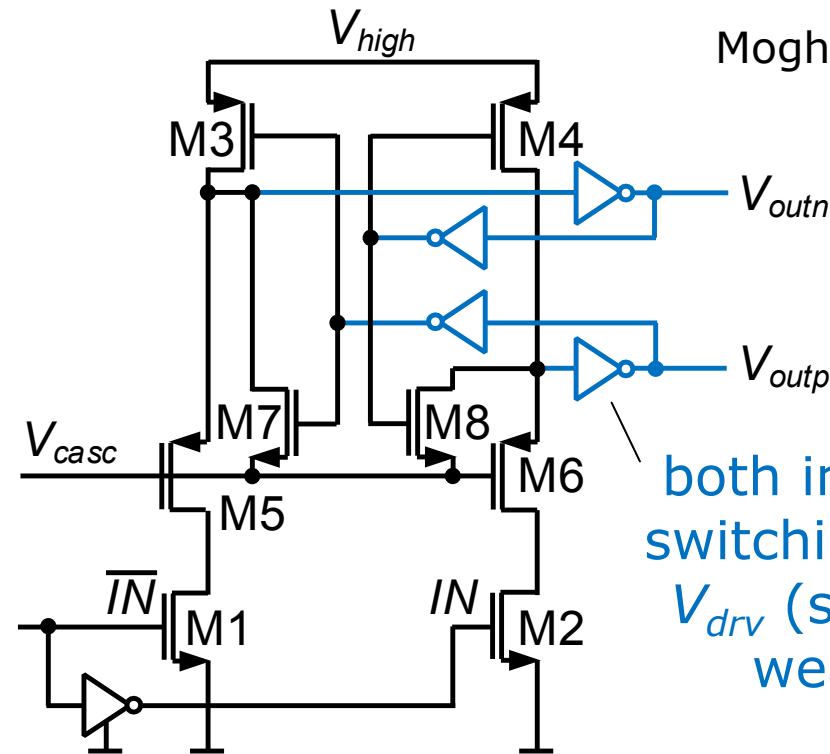  

both inverters with switching point near  $V_{drv}$  (strong pmos, weak nmos)

$V_{SG}$  of cascodes M5, M6 prevents logic '0' level at driver input  
 → full high-side swing achieved by bypass devices M7, M8

Inverters increase loop gain  
 → faster switching and reduced power consumption → M7, M8 can become minimum size




# Sizing of the Cross-coupled Level Shifter (1)

M1 (M2) needs to be strong enough to pull drain of M3 (M4) below  $V_{drv}$  by one  $V_{th}$   $\rightarrow$   $W/L$  follows from condition  $I_1 = I_3 (= I_5)$

$$\left(\frac{W_1}{L_1}\right) / \left(\frac{W_3}{L_3}\right) = 2 \frac{\mu_{op} (V_{drv} - V_{th}) V_{sdx}}{\mu_{on} (V_{DDL} - V_{th})^2}$$

$$V_{th} = V_{thn} = |V_{thp}|$$

 

Design guideline:

1. Use minimum  $L$  and  $V_{sdx} \geq V_{th}$  (higher  $V_{sdx}$  gives higher speed)
2. Choose min.  $W_1$ ,  $W_3$  (and  $W_5$ ) that fulfill sizing equation(s)
3. Increase  $W_1$ ,  $W_3$  (and  $W_5$ ) concurrently to enhance speed
4.  $W_1$  may be set even larger to faster charge parasitic cap at drain of M1, M3

Example:  $\mu_{op}/\mu_{on} = 1/3$ ,  $V_{drv} = 12V$ ,  $V_{DDL} = 3.3V$ ,  $V_{th} = 0.8V \rightarrow$  Width ratio M1 to M3 =  $0.96 \sim 1$

Moghe JSSC Feb. 2011




# Outline

---

- Introduction
- Power Transistors
- Gate Drivers
- Level Shifters
- Control Loop
- System Design
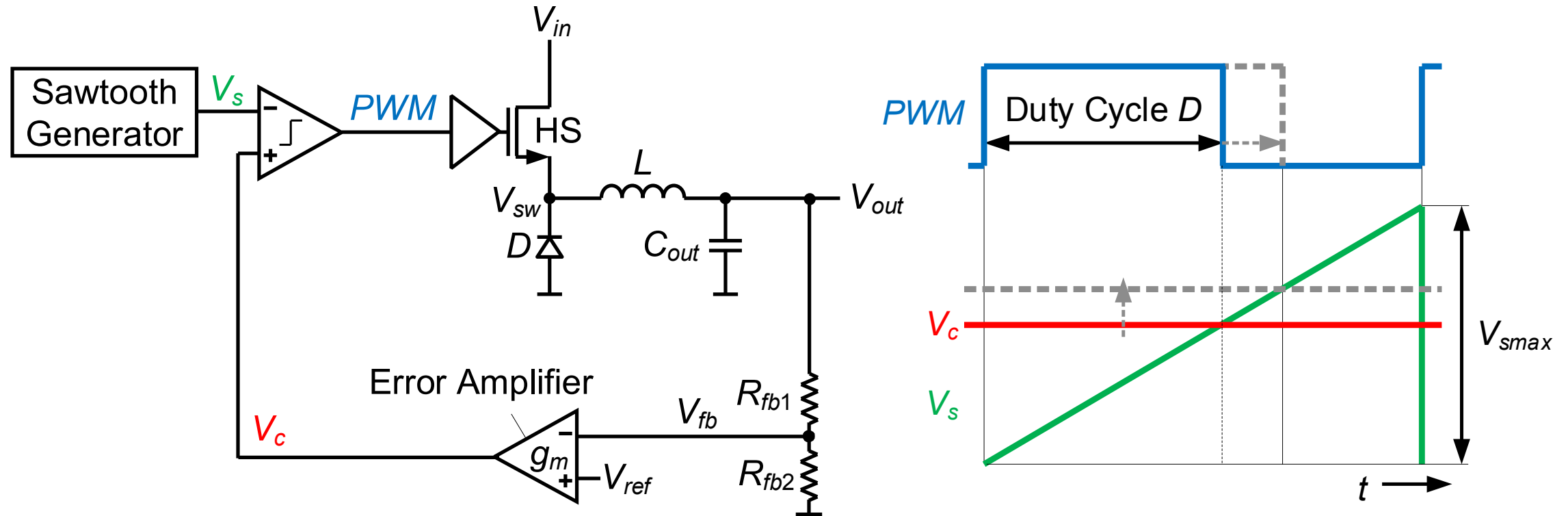
# Regulation Schemes: Voltage Mode Control





Two-pole plant transfer function: Change in  $D$  has  $L-C_{out}$  time constant  
→ relatively slow, complex loop stabilization

# Error Amplifier

Influence on line / load regulation, transient response, etc.


Widely used:  
symmetrical OTA, cascode OTA

 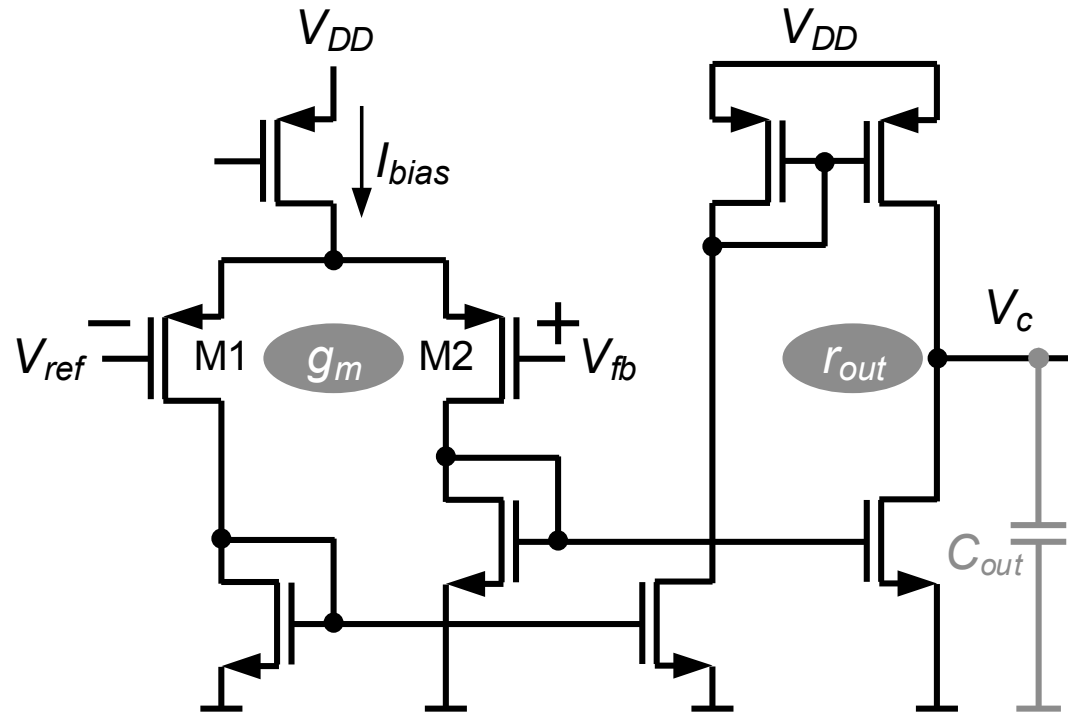Loop compensation  
requires well controlled  
 $G_m = g_m$  of input pair


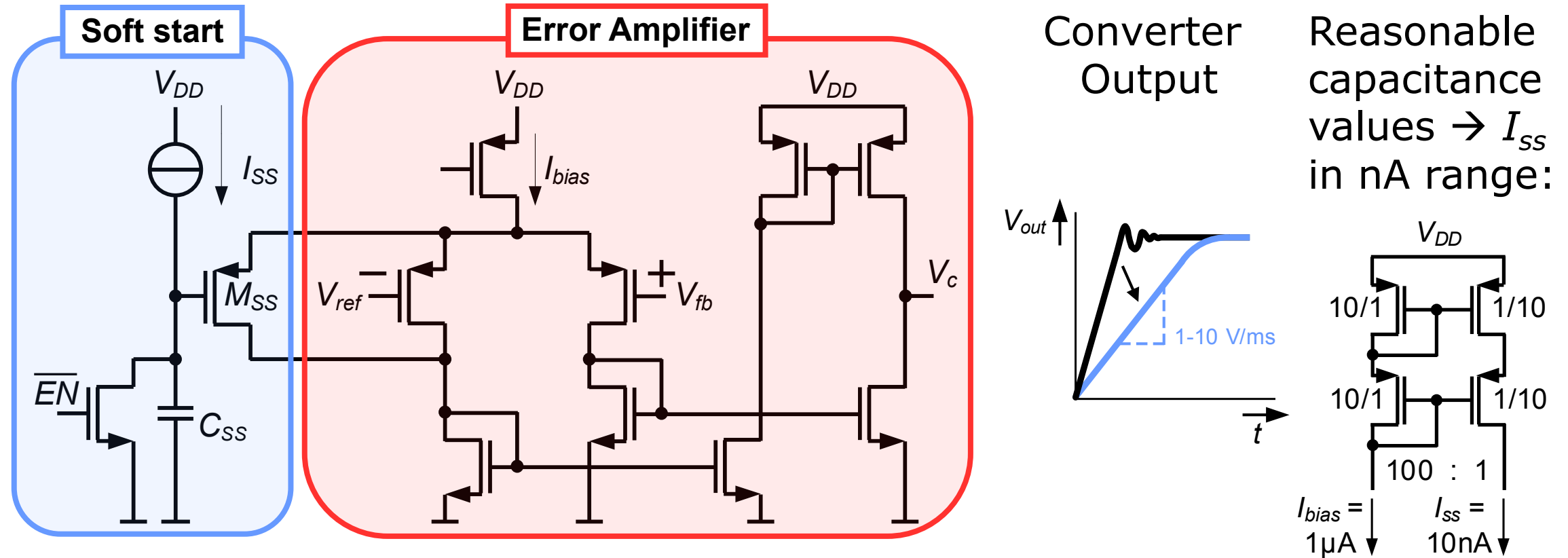
# Soft Start

To prevent inrush currents at start-up: Soft start input at error amplifier replaces fixed reference by slowly increasing ramp of  $\sim 1-10$  V/ms







Example: Slope = 2V/ms,  $C_{SS} = 5\text{pF} \rightarrow I_{SS} = 2\text{V/ms} \cdot 5\text{pF} = 10\text{nA}$

   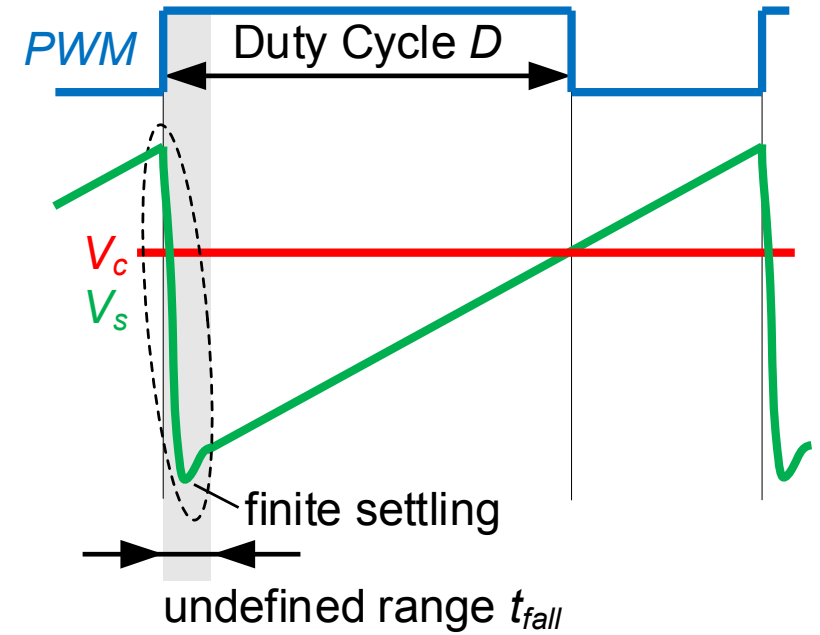
# Sawtooth Generator

Settling time of falling edge limits duty cycle and switching frequency

Preferred solution: Integrator with fast and precise refresh, saw tooth bias level easily controlled by  $V_{ref}$ , can be combined with time-interleaved approach (two integrators)



# Control Loop Analysis and Stability

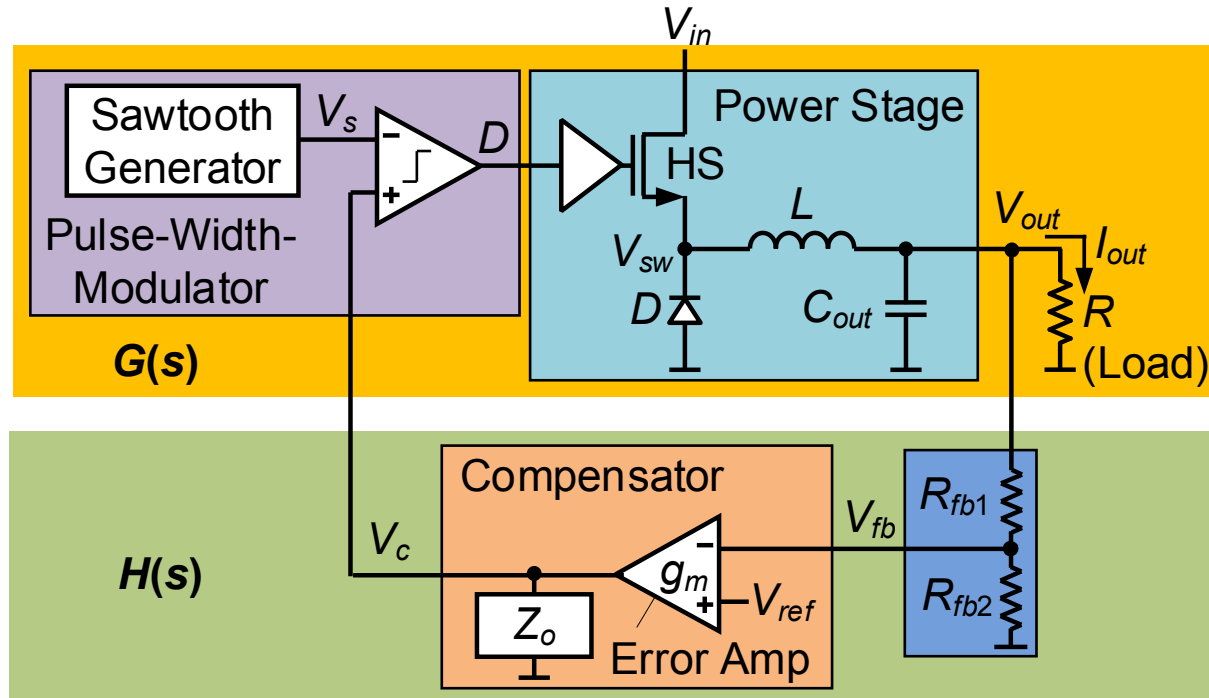

$$\alpha = \frac{R_{fb2}}{R_{fb1} + R_{fb2}}$$

Closed loop transfer function:  $\frac{V_{out}}{V_{ref}} = \frac{1}{\alpha} \frac{G(s)H(s)}{1 + G(s)H(s)} \sim \frac{1}{\alpha}$

→ Loop gain:  $\frac{V_{fb}}{V_{ref}} = G(s)H(s)$



Modulator (plant) transfer function:  $G(s) = \frac{D}{V_c} \frac{V_{out}}{D} = \frac{1}{V_{smax}} V_{in} \frac{1}{1 + \frac{sL}{R} + s^2 LC_{out}}$  → double pole

Frequency compensation through  $H(s)$  by inserting zeros (and poles) →  $Z_o(s)$



# Frequency Compensation

 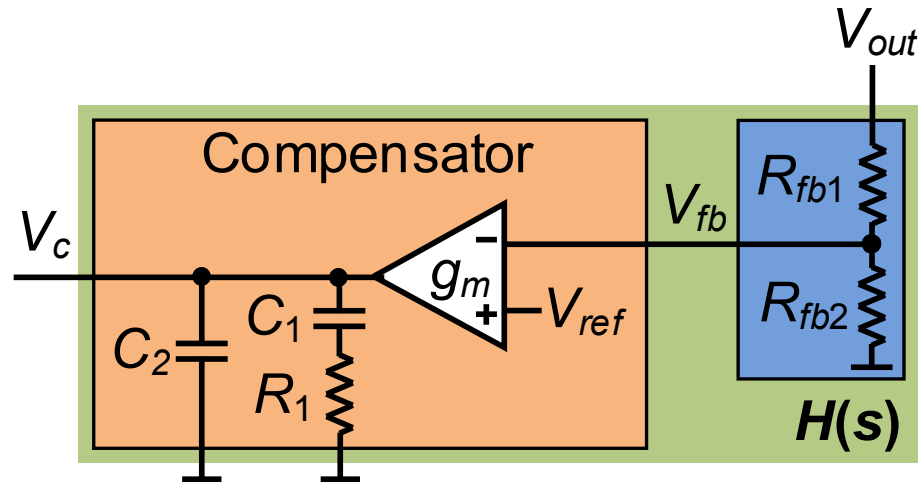Example: Type II compensation  $\rightarrow H(s) =$  two poles, one zero



$$H(s) = \frac{V_c}{V_{out}} = - \frac{R_{fb2}}{R_{fb1} + R_{fb2}} \underbrace{\frac{g_m}{sC_1}}_{\text{Integrator (pole at } f = 0)} \underbrace{\frac{(1 + sR_1C_1)}{(1 + sR_1C_2)}}_{\text{Pole } f_p \text{ Zero } f_z}$$



Integrator (pole at  $f = 0$ ) Pole  $f_p$  Zero  $f_z$

Example:  $f_z = 10\text{kHz}$ ,  $f_p = 87\text{kHz}$   
 $\rightarrow R_1 = 4\text{k}\Omega$ ,  $C_1 = 3.9\text{nF}$ ,  $C_2 = 457\text{pF}$



$\rightarrow$  On-chip integration by means of capacitance multiplier

# Cap Multiplier: Fully Integrated Compensation



Voltage mode  
(Miller effect):

  

Current mode:

  

Rincon-Mora, JSSC Jan. 2000

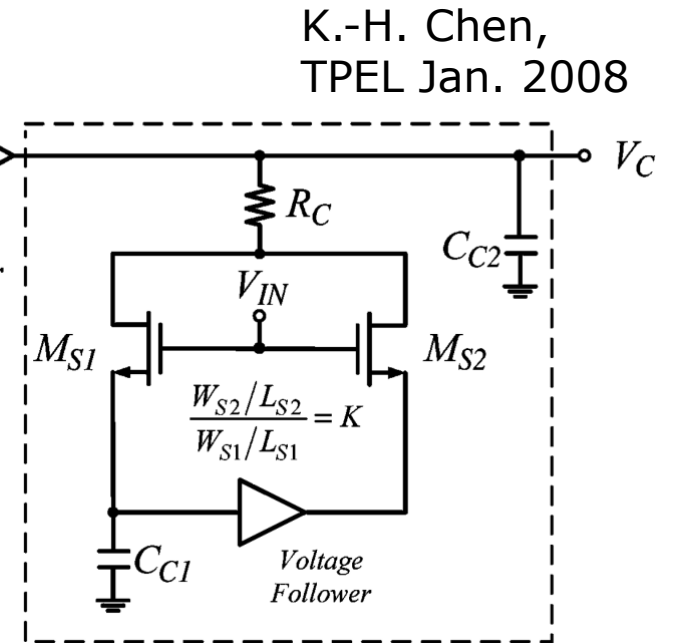
 


Type II example:  $R_{MS1} = 4k\Omega$ ,  $R_{MS2} = 80k\Omega$   
 $C_{C1} = 200pF$  "equal" to  $4nF \rightarrow 20x$  smaller

- ❑ Area efficient on-chip implementation of large capacitors
- ❑ Additional advantage: Can be adaptive  $\rightarrow$  adjust phase margin for fast transient response

 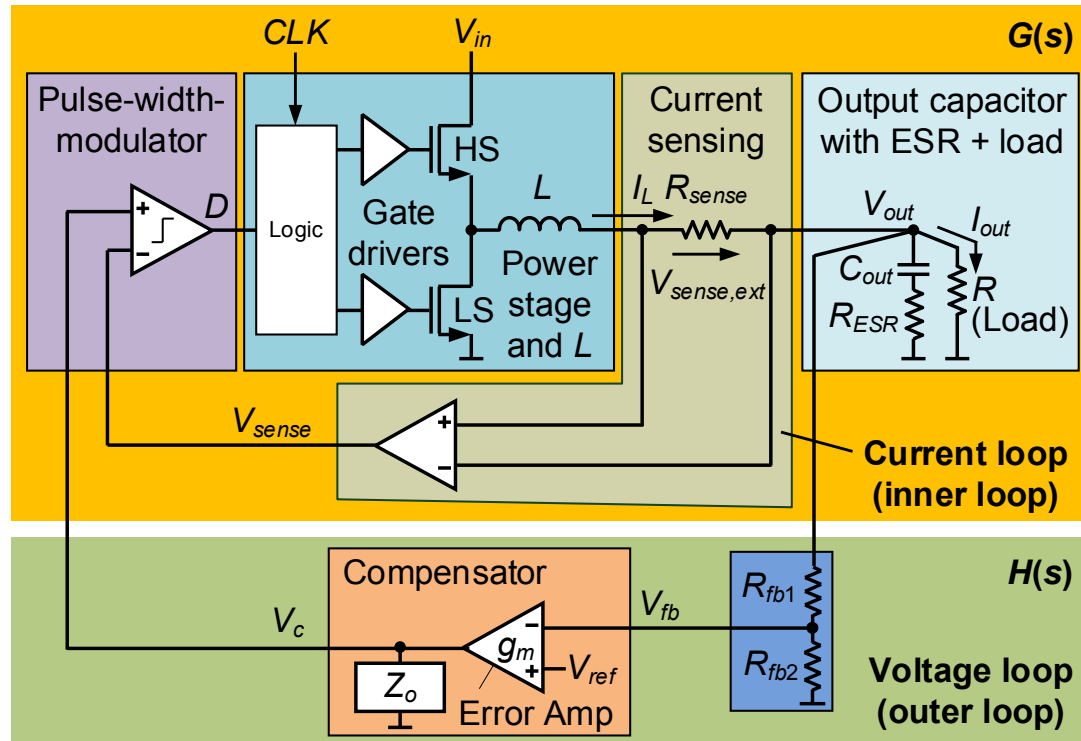
# Regulation Schemes: Current Mode Control

$V_c$  is compared to a ramp voltage  $V_{sense}$  derived from the inductor current  $I_L$ , forming a second, inner control loop




- ❑ Excellent line transient response  $\rightarrow V_{out}$  independent of  $V_{in}$
- ❑ Inherent  $I_L$  current limit (by limiting  $V_c$ )
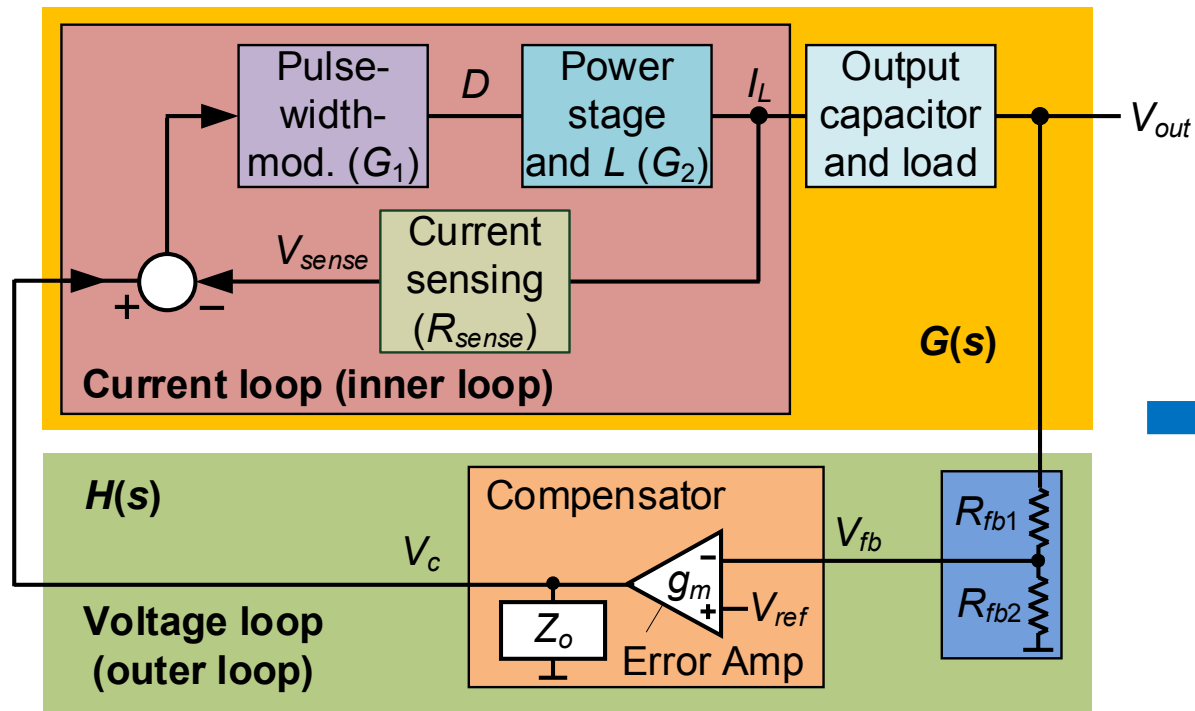
# Control Loop Analysis Current Mode Control



Current loop transfer function:
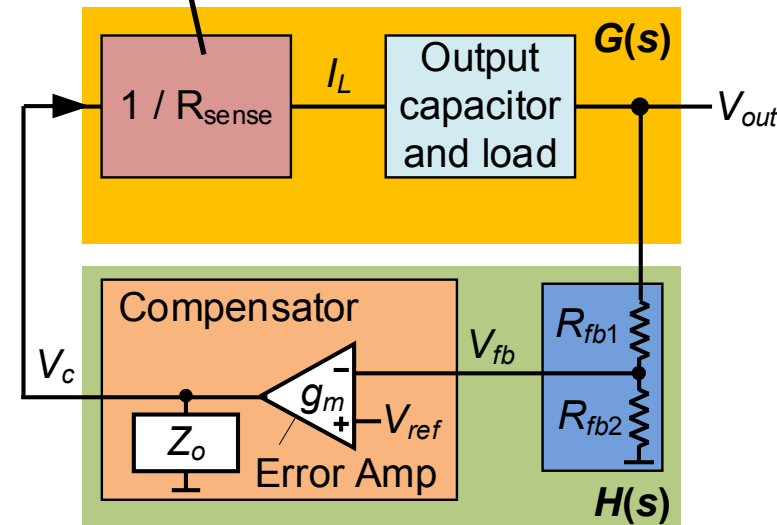
$$\frac{I_L}{V_c} = \frac{G_1 G_2}{1 + G_1 G_2 R_{sense}} \sim \frac{1}{R_{sense}}$$



Modulator (plant) transfer function:  $G(s) \sim \frac{1}{R_{sense}} \frac{1 + sR_{ESD}C_{out}}{1 + sRC_{out}}$


→ 1st order system: much easier stabilization

# Current Mode: Subharmonic Oscillations


Unconditional instability above 50% duty cycle (step-down)

→ perturbation  $\Delta I_L$  of inductor current leads to subharmonic oscillations at  $f_{sw}/2$


$D < 50\%$  (stable)

 

$D > 50\%$  (unstable)

 


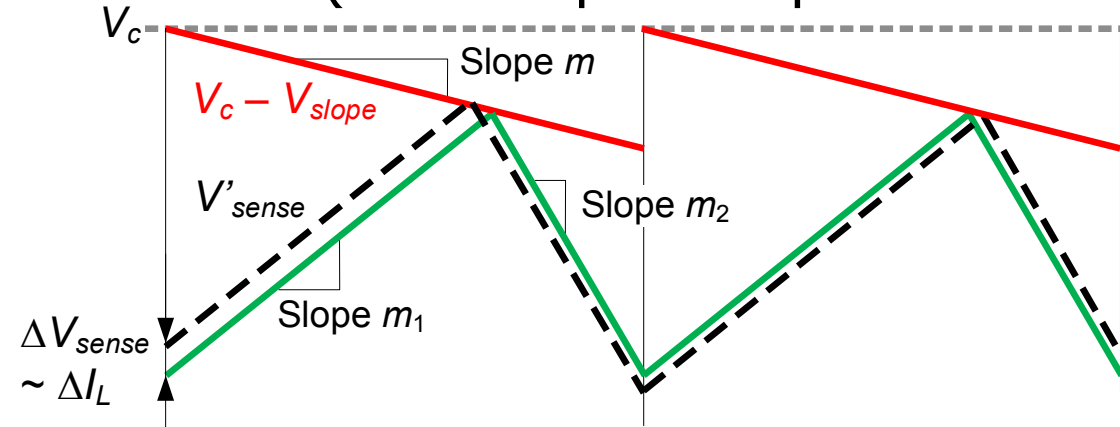
$D > 50\%$  (with slope compensation → stable)



→ stable if  $m > \frac{m_2}{2}$

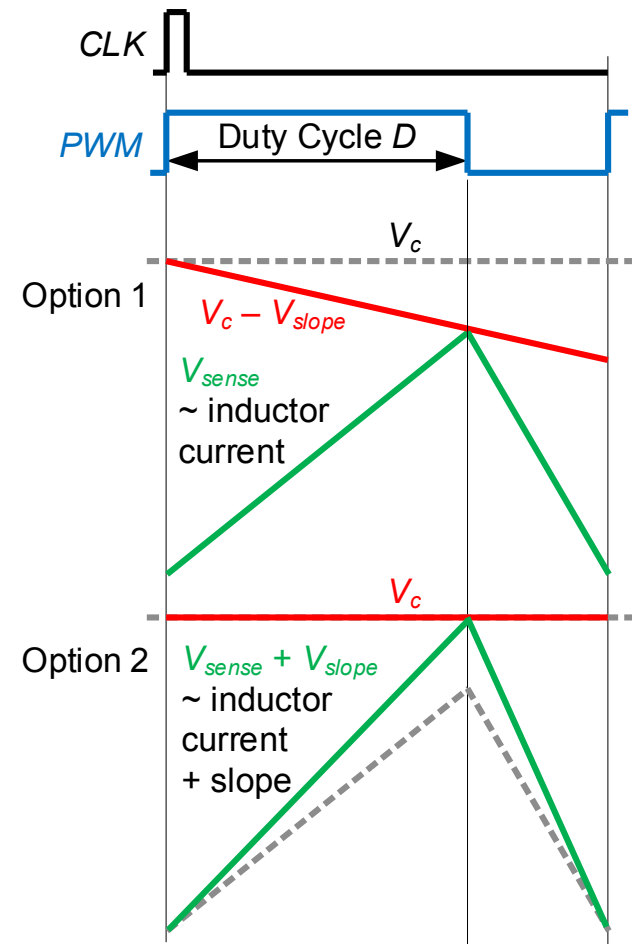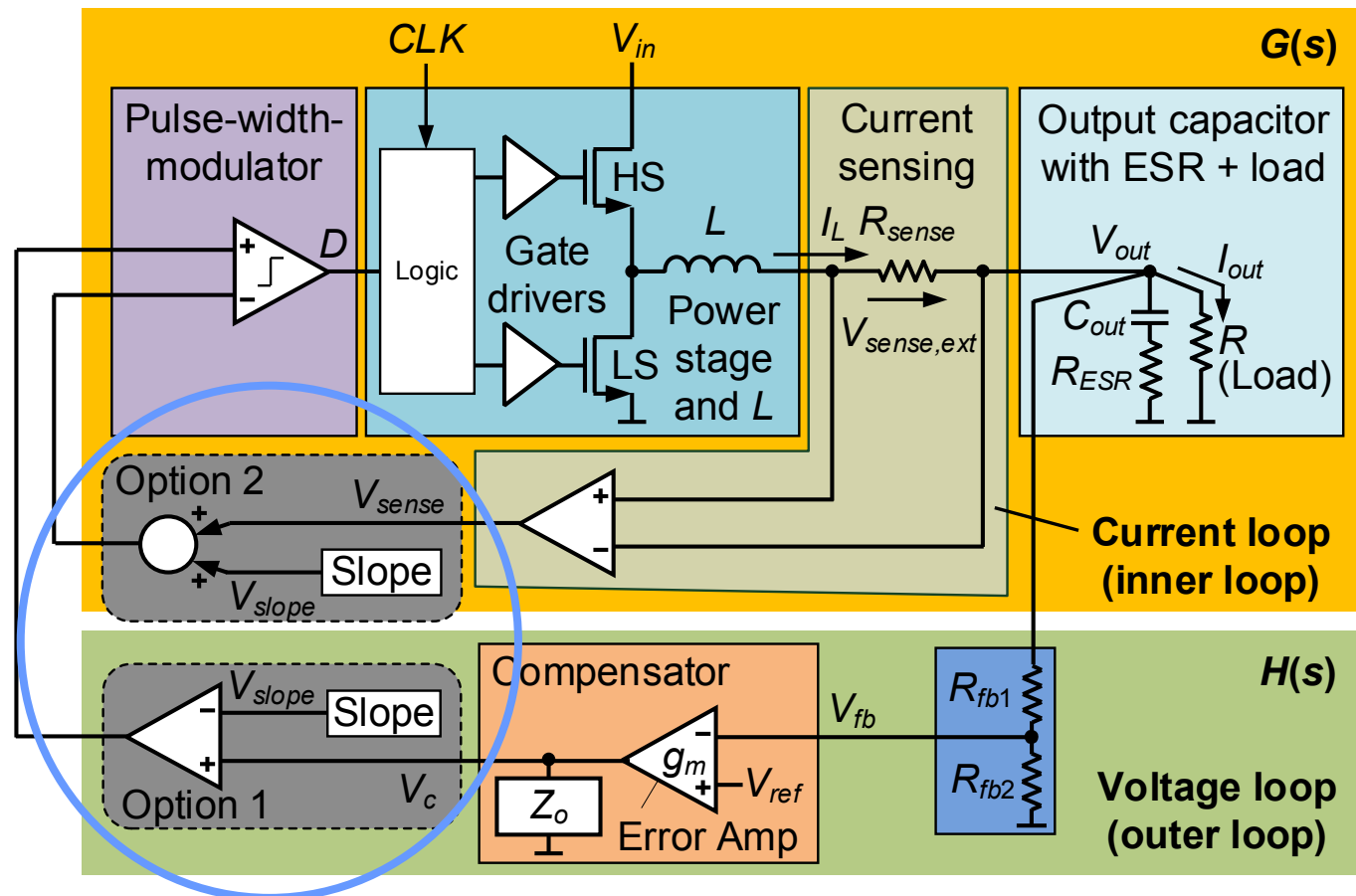
# Current Mode Control with Slope Compensation

$(V_c - V_{slope})$  gets compared to a ramp voltage  $V_{sense}$  derived from the inductor current  $\rightarrow$  two implementation options


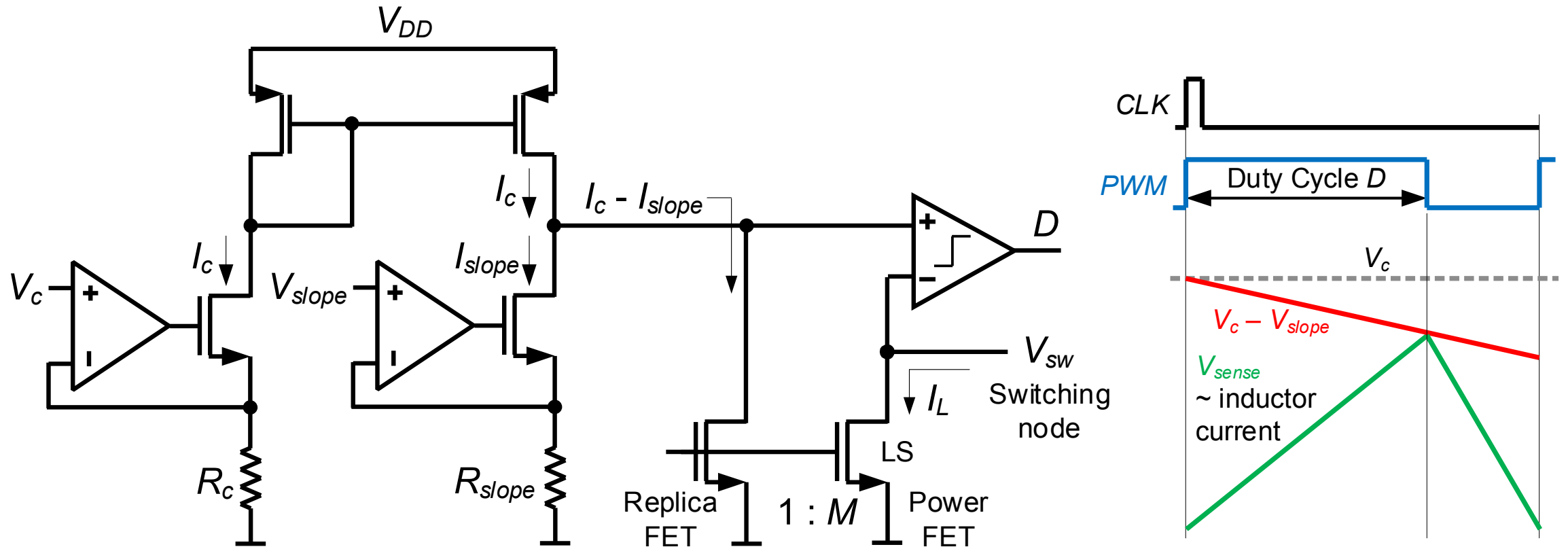
# Slope Compensation: Circuit Design (1)


Option 1: Difference ( $V_c - V_{slope}$ ) is generated in the current domain, fed into replica FET and compared to voltage across power FET =  $V_{sense} = V_{sw} = R_{DSon} \cdot I_L$



Concept can also be implemented on high-side FET (more complex)



# Slope Compensation: Circuit Design (2)

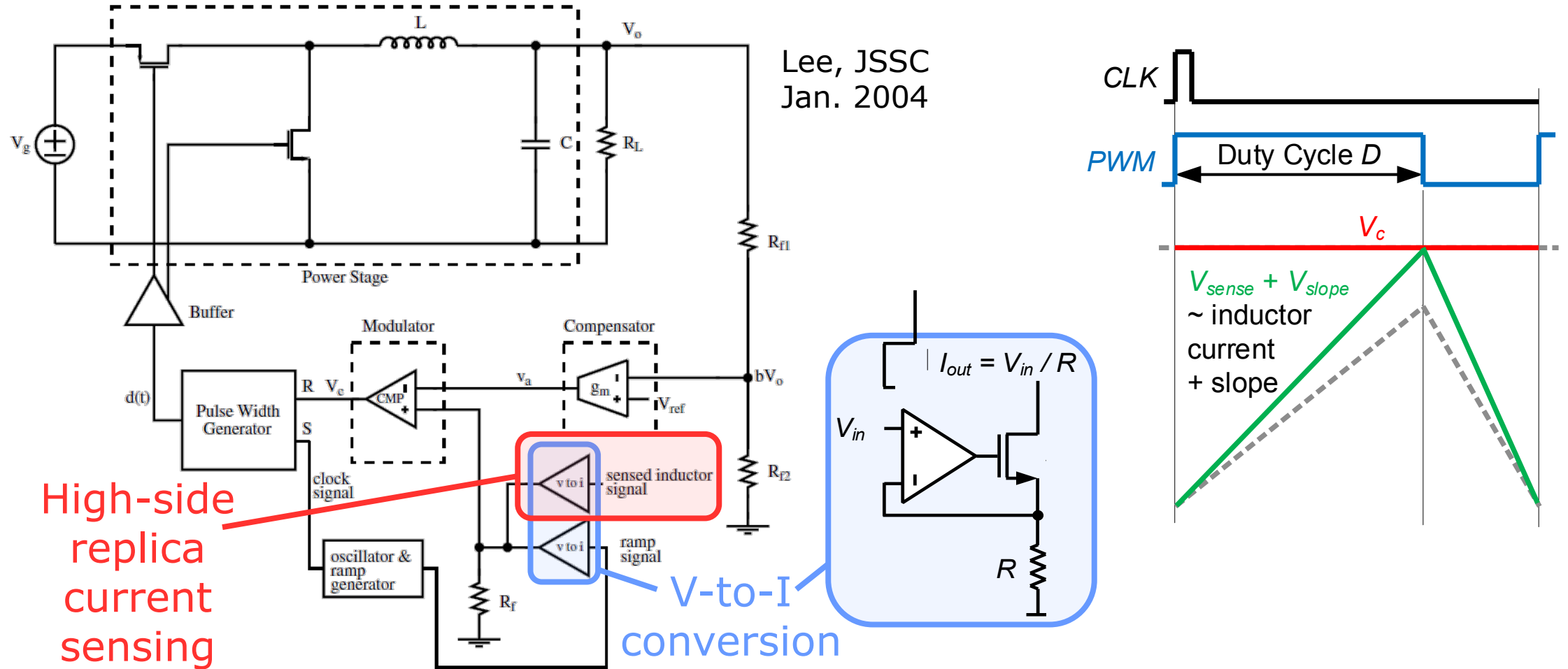Example for Option 2 with replica current sensing and slope compensation





# Current Sensing

 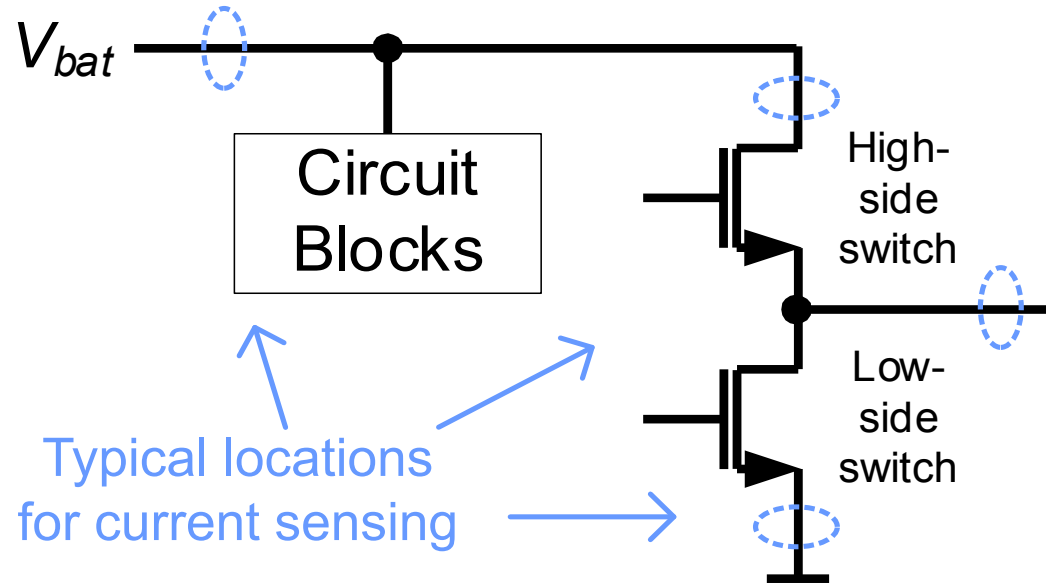

## □ Open loop:


- Over-current detection → turn-off power FET
- Continuous current measurement

## □ Closed loop:

- Current limit
- Current controlled DC-DC conversion


# Current Sensing Concepts and Circuits (1)

$R_{DS}$  Sensing

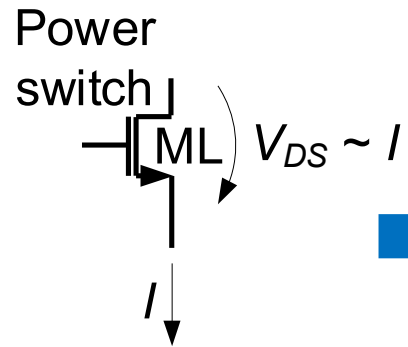


+ Lossless  
- Accuracy

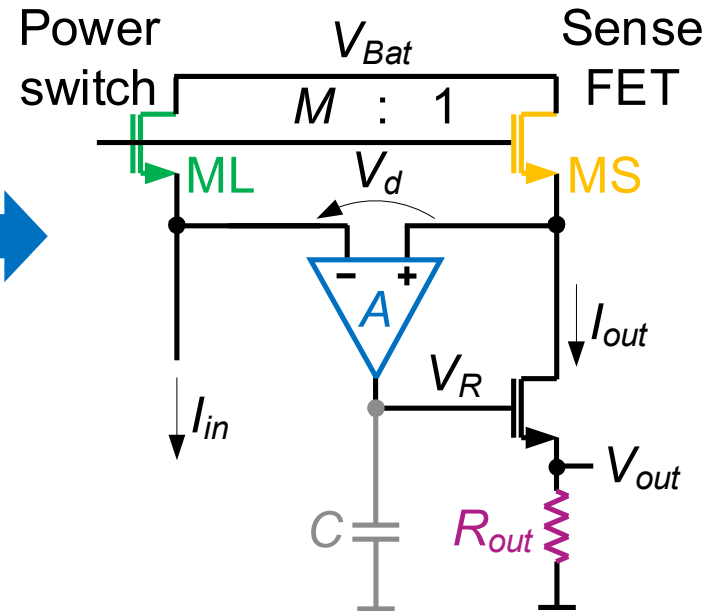Replica Sensing: Sense FET + Sense Amplifier



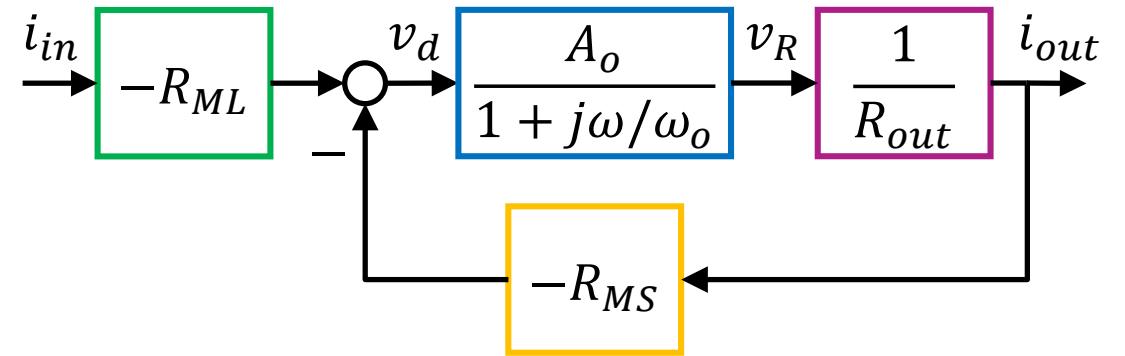+ Lossless  
+ Good accuracy  
- Complexity



$$i_{out} = v_d A / R_{out} \quad (1)$$


$$v_d = -i_{in} R_{ML} + i_{out} R_{MS} \quad (2)$$

$$(2) \rightarrow (1): \frac{i_{out}}{i_{in}} = \frac{A R_{ML} / R_{out}}{1 + A R_{MS} / R_{out}} \approx \frac{R_{ML}}{R_{MS}} = \frac{1}{M}$$

Loop Gain:  $GBW = \underbrace{A_o \omega_o}_{GBW(A)} R_{MS} / R_{out}$  (slow!)

# Current Sensing Concepts and Circuits (2)
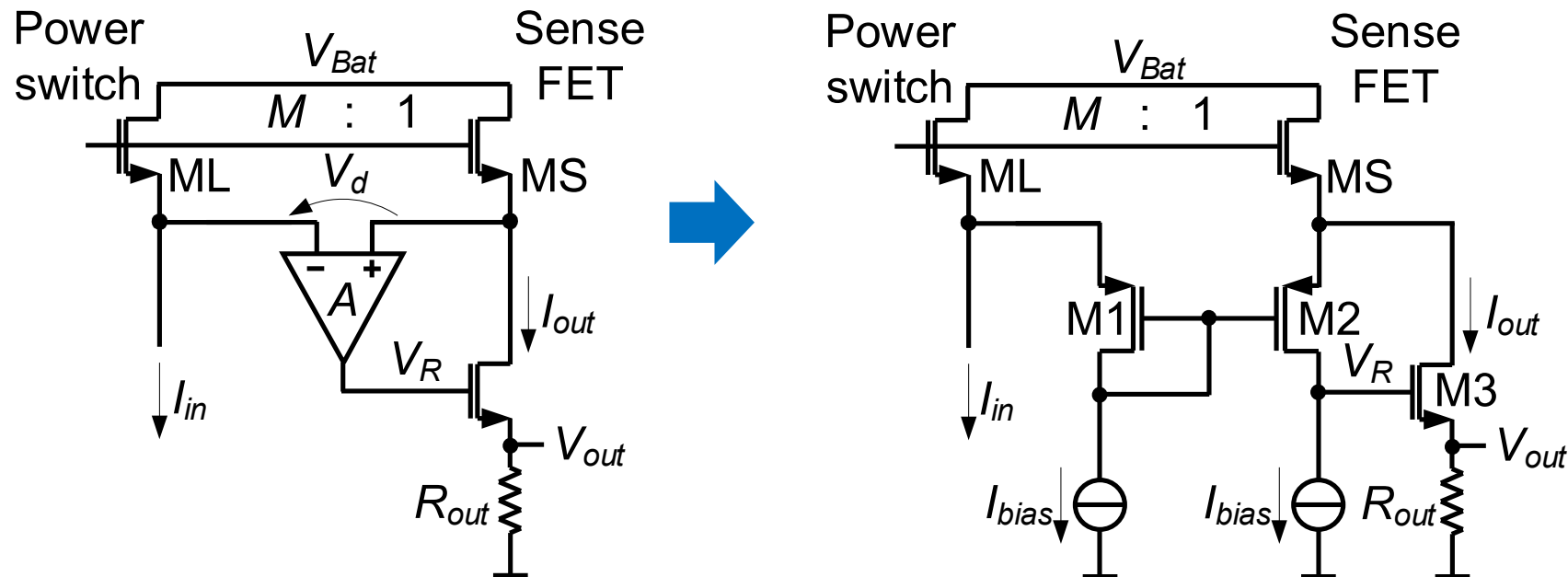
## Sense FET + Sense Amplifier: Practical implementation




- ❑ Accuracy: Mismatch ( $M$ , amp offset), variation of  $R_{out}$  (trimming), loop gain
- ❑ Lower input current limited:  $I_{in} \geq MI_{bias}$
- ❑ Finite  $I_{bias}$  causes a DC error:

$$R_{ML}(I_{in} + I_{bias}) = R_{MS}(I_{out} + I_{bias}) \rightarrow I_{in} = M(I_{out} + I_{bias}) \approx MI_{out} \text{ for } I_{bias} \ll I_{out}$$
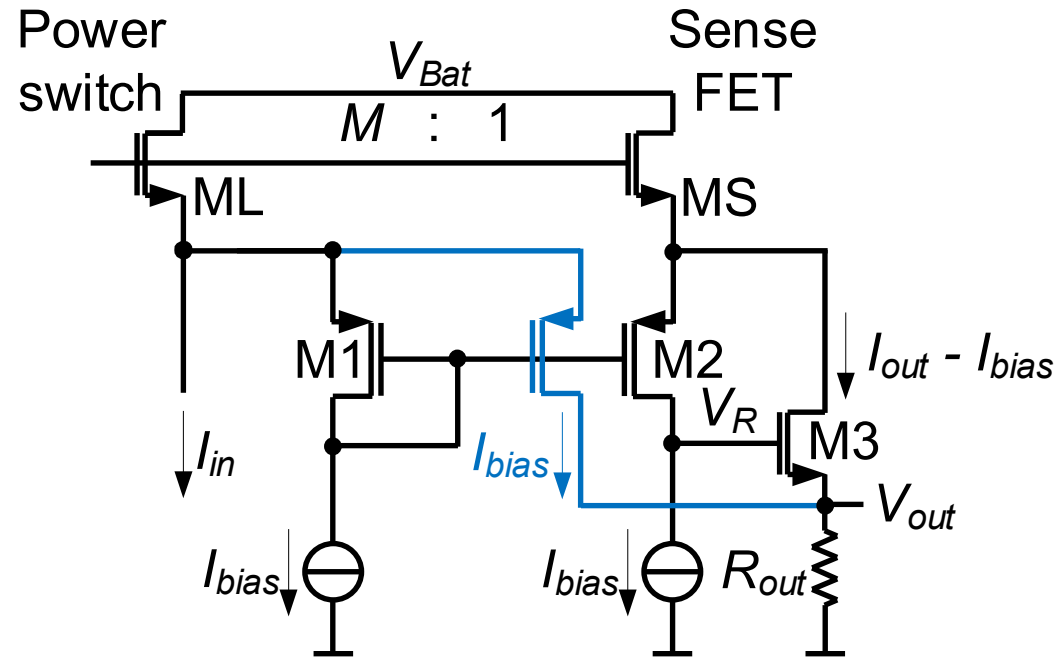
# Current Sensing Concepts and Circuits (3)


Sense FET + Sense Amplifier:  $I_{bias}$  compensation



□ With  $I_{bias}$  compensation:

$$R_{ML}I_{in} = R_{MS}(I_{out} - I_{bias} + I_{bias}) \Rightarrow I_{out} = I_{in}/M$$

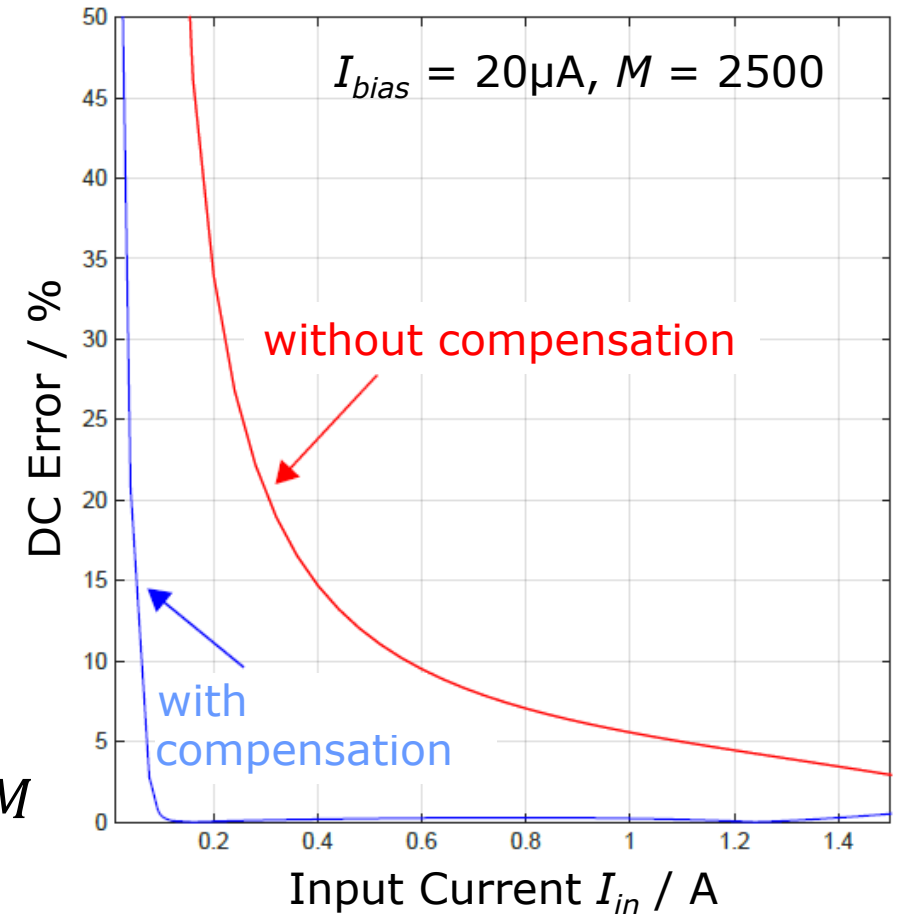□ Input current limit remains:  $I_{in} \geq MI_{bias}$




# Outline

---

- Introduction
- Power Transistors
- Gate Drivers
- Level Shifters
- Control Loop
- System Design
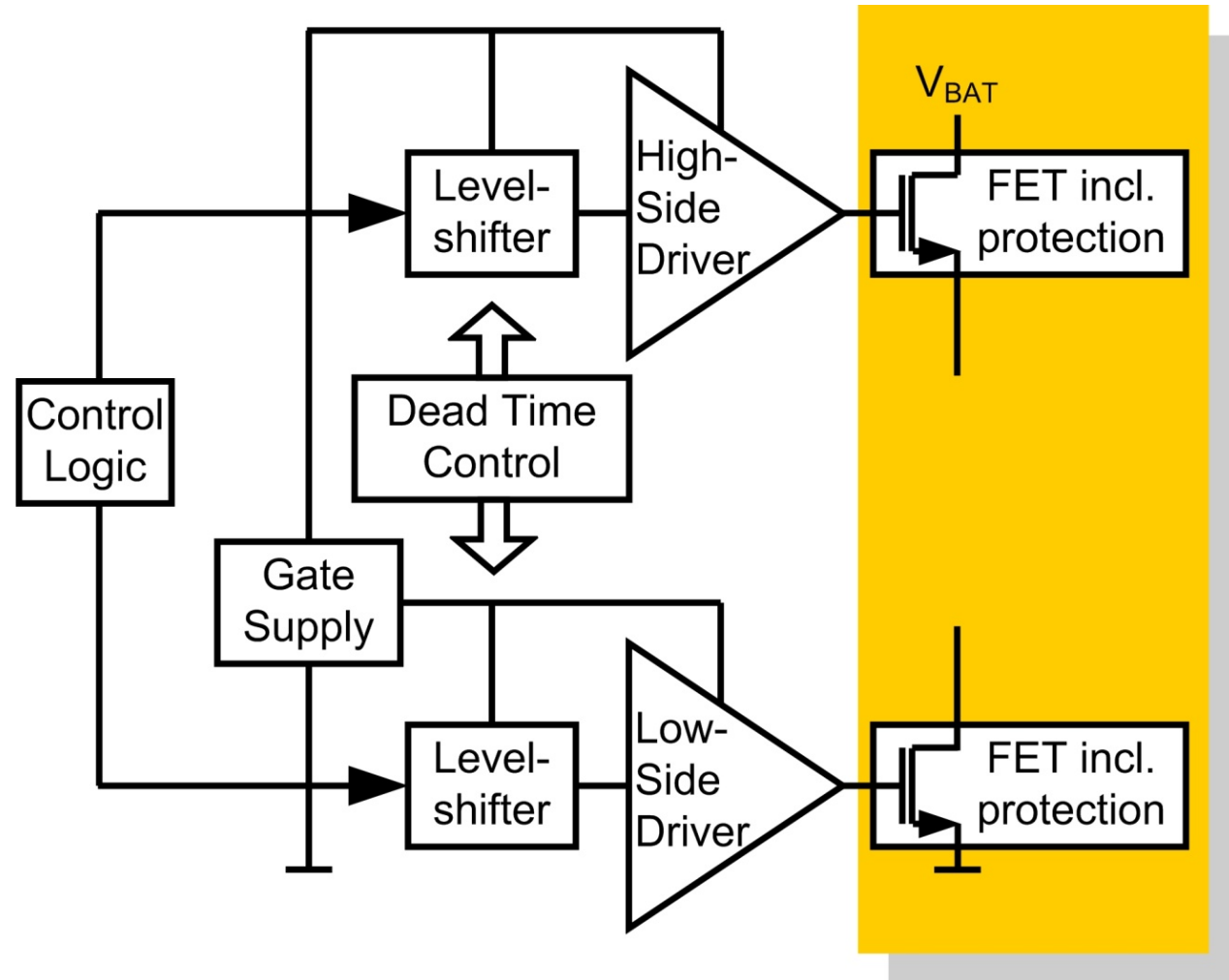
# Protection and Diagnostics


- ❑ Thermal protection
- ❑ Over-voltage (VDS)
- ❑ Over-current
- ❑ Short-to-ground
- ❑ Short-to-battery
- ❑ Open load
- ❑ Under-voltage (UVLO)




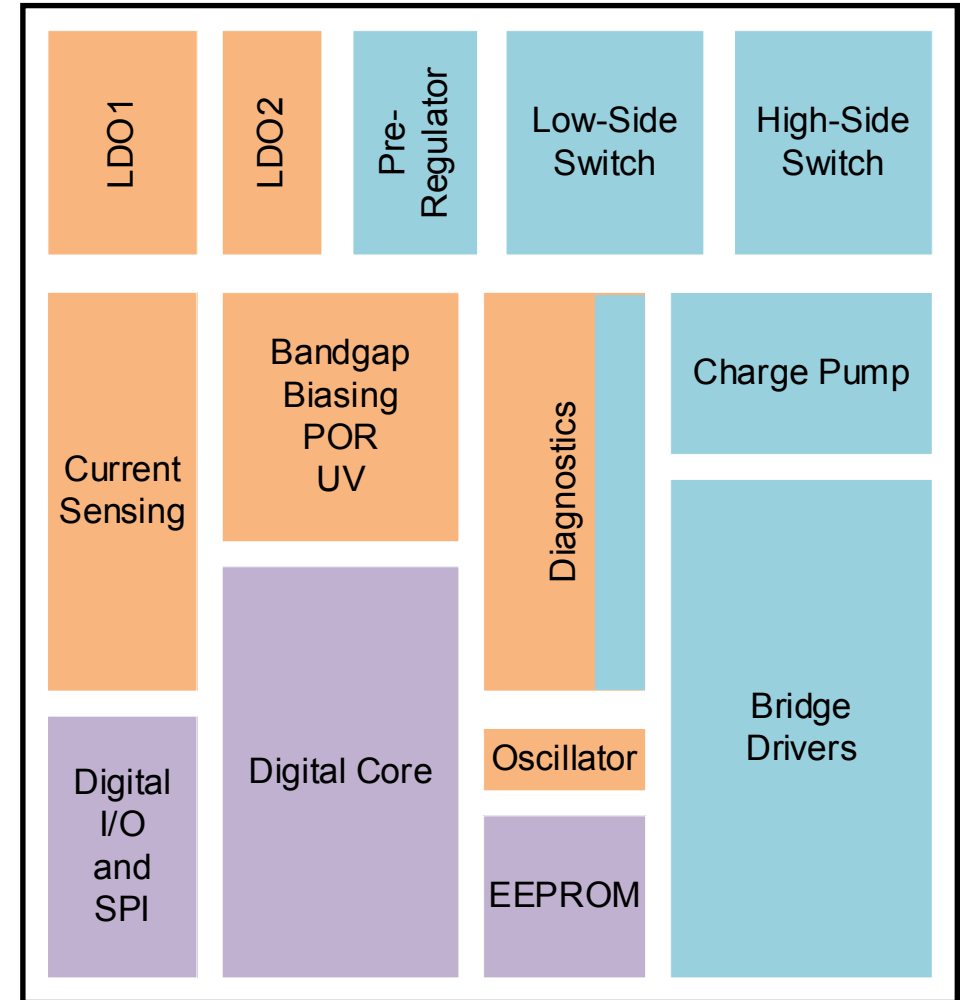
# Floorplan


- ❑ Rule: Separate high-voltage and low-voltage domains
- ❑ Reason: HV-Isolation = Spacing = Chip Area = Cost
- ❑ IC level copper metallization
- ❑ Thermal analysis
- ❑ Mechanical stress: avoid corners / edges for sensitive blocks (bandgap)





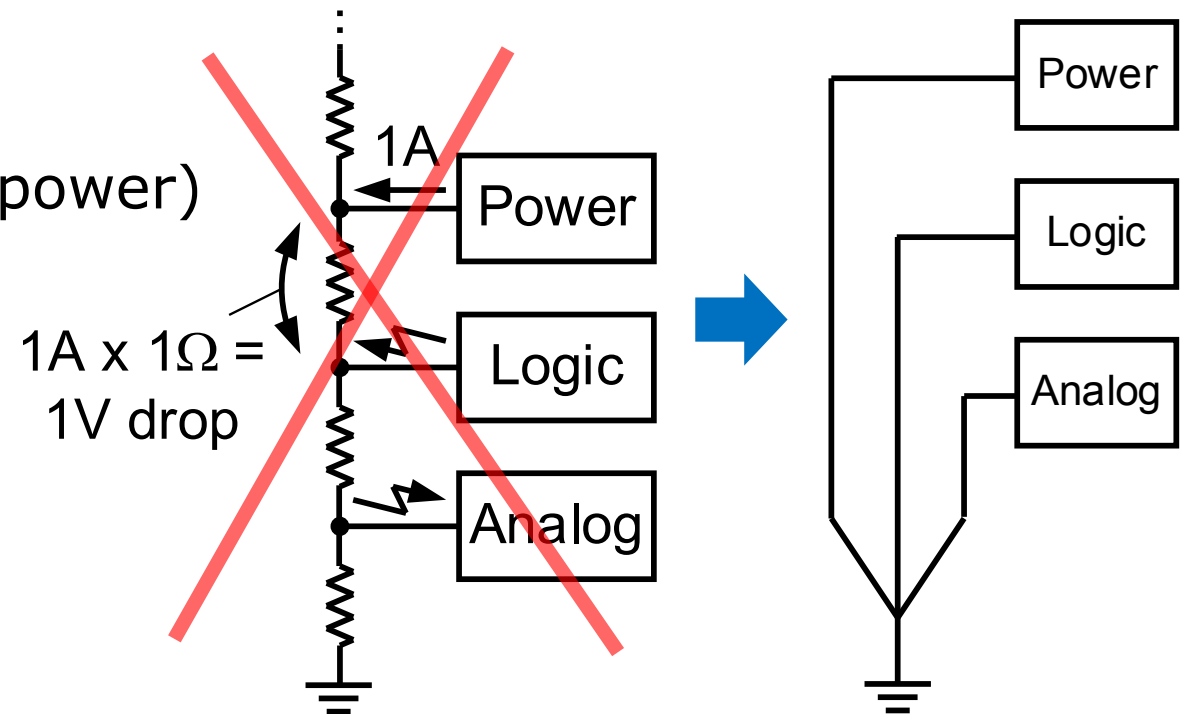
# Pinout, Grounding and Supply Guidelines


- ❑ Supply and ground pins adjacent, bypass-C placed here close to pins
- ❑ Short bond wires for power pins and fast signals ( $R \downarrow$ ,  $L \downarrow$ )  $\rightarrow$  close to the middle of one side of the die, vice versa: corner pins for quiet signals
- ❑ Use separate bond pads for each domain or at least apply star connections, consider double / tripple-bond
- ❑ IC-Level wiring in groups:
  - Noisy lines (digital, switching power)
  - Supply lines (high current)
  - Sensitive lines (analog)


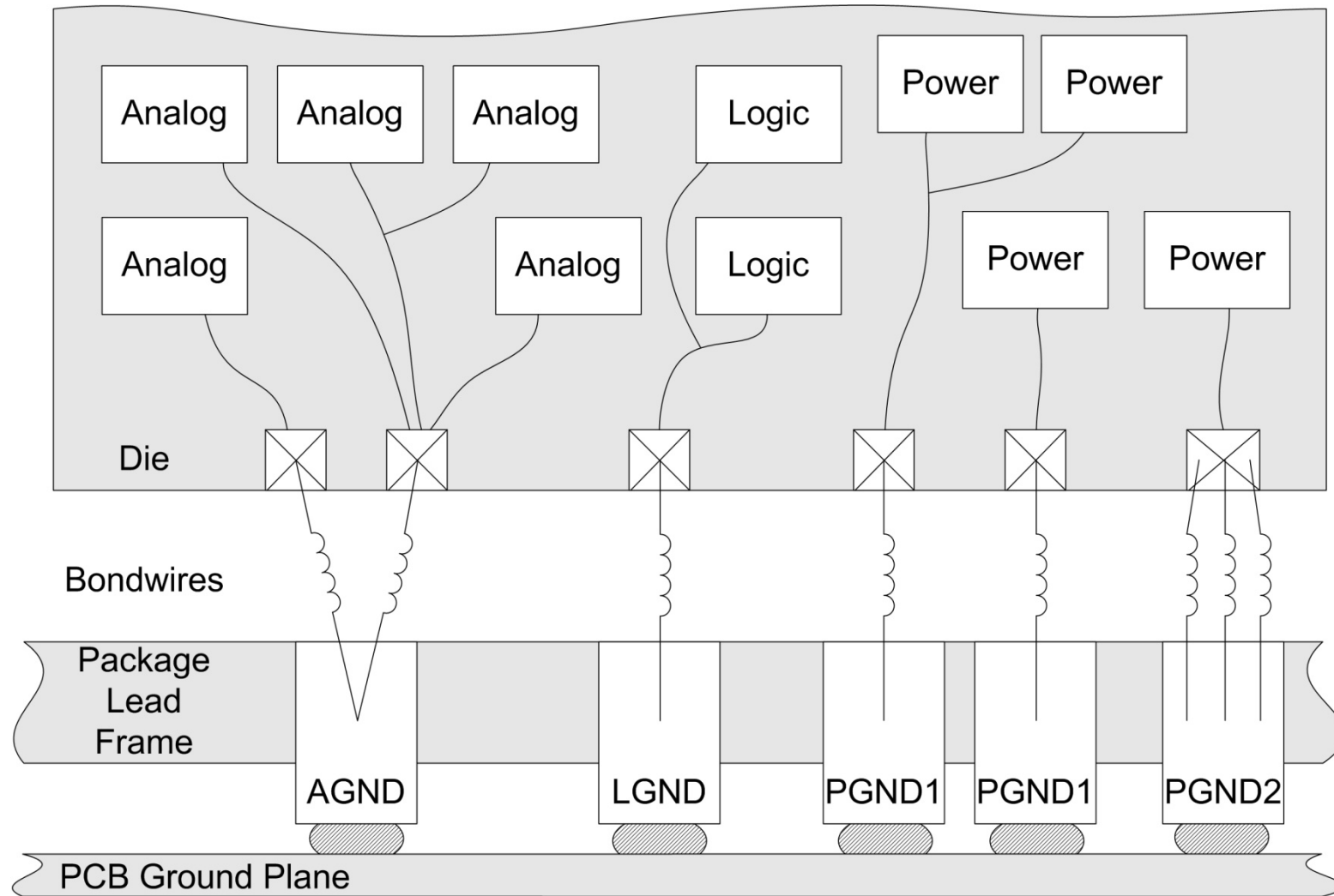
# Pinout, Grounding and Supply Guidelines



# Conclusion

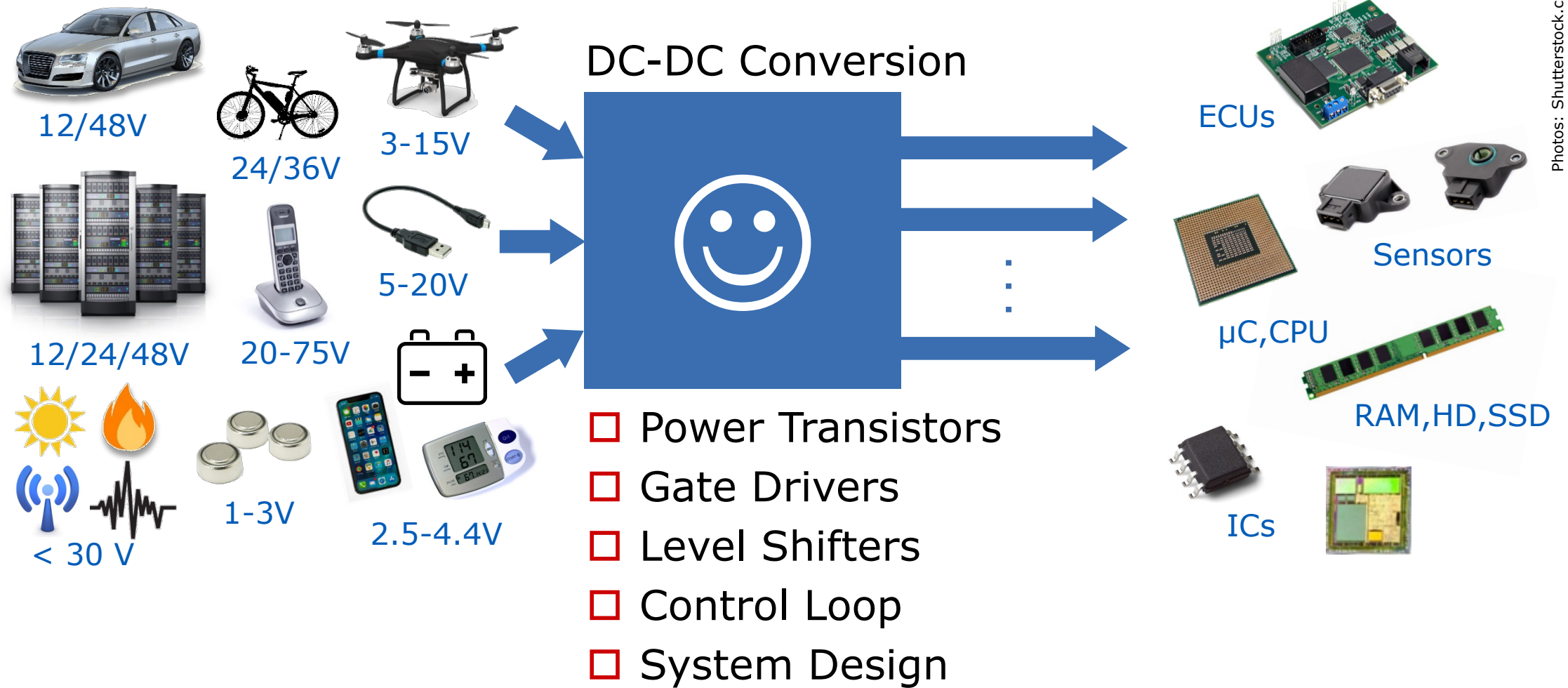

Photos: Shutterstock.com

# Papers to See This Year

---

## Session 11 "DC-DC Converters" Relevant Papers:

- 11.2: Resonant SC converter with on-chip L-C, level shifter, switch stacking
- 11.3: One-Step 325V-to-3.3–10V DC-DC, bootstrap gate supply
- 11.4: 48 – 80V input 2MHz GaN DC-DC, current sensing (DCR)
- 11.7: Buck-boost DC-DC, 2.5-5V input, adaptive dead time

## Session 18 "GaN & Isolated Power Conversion" Relevant Papers:

- 18.2: 400V Offline monolithic GaN IC with control loop
- 18.6: 60A, 48V-to-1V DC-DC, dynamic level shifter

## Session 32 "Power Management Techniques" Relevant Papers:

- 32.2: Piezoelectric Energy Harvesting IC

# References (1)

---

- J. Wittmann et al., "MHz-Converter Design for High Conversion Ratio, " ISPSD 2013
- T. Efland et al., "Bipolar Issues in Advanced Power BiCMOS," BIPOLAR/BiCMOS Circuits and Technology Meeting, 2000
- J. Wittmann et al., "Substrate Coupling in Fast-Switching Integrated Power Stages," ISPSD 2015
- P. Renz et al., "A Fully Integrated 85%-Peak-Efficiency Hybrid Multi-Ratio Resonant DCDC Converter with 3.0-4.5V Input and 500 $\mu$ A-120mA Load Range," ISSCC 2019
- B. Serneels et al., "A high-voltage output driver in a 2.5-V 0.25-um CMOS technology," JSSC, March 2005
- A. Annema et al., "5.5-V I/O in a 2.5-V 0.25-um CMOS technology," JSSC, March 2001
- S. Herzer et al., "Capacitive-coupled Current Sensing and Auto-ranging Slope Compensation for Current Mode SMPS with Wide Supply and Frequency Range", ESSCIRC 2009, pp. 140 – 143
- R. Jaeger, Comments on "An optimized output stage for MOS integrated circuits," JSSC, March 1975
- N. Li et al., "CMOS tapered buffer", IEEE JSSC, April 1990
- G. Villar et al., "Energy optimization of tapered buffers for CMOS on-chip switching power converters," ISCAS 2005
- S. Vemuru et al., "Variable-Taper CMOS Buffer," JSSC, Sept. 1991, pp.1265-1269
- S. Hamzaoglu, "Split-path skewed (SPS) CMOS buffer...", IEEE TCAS II, Oct 2001
- J. Wittmann et al., "An 18V Input 10MHz Buck Converter with 125 ps Mixed-Signal Dead Time Control," JSSC, July 2016
- J. Wittmann, "Integrated High-Vin Multi-MHz Converters", Springer 2020

# References (2)

---

- A. Barner et al., "A 10 MHz, 48-to-5V Synchronous Converter with Dead Time Enabled 125 ps Resolution Zero-Voltage Switching," APEC 2016
- Moghe et al., "Nanosecond Delay Floating High Voltage Level Shifters ...," JSSC, Feb. 2011
- N. Mohan et al., "Power Electronics Converters, Applications, and Design" 3rd ed. New York: Wiley, 2003
- Gabriel A. Rincon-Mora, "Active Capacitor Multiplier in Miller-Compensated Circuits," JSSC, January 2000
- K.-H. Chen et al., "Bidirectional Current-Mode Capacitor Multipliers for On-Chip Compensation," IEEE TPEL, pp.180-188, Jan. 2008
- R. Ridley, "A more accurate current mode control model" Ridley Engineering Inc., 2001
- C. F. Lee et al., "A Monolithic Current-Mode CMOS DC-DC Converter With On-Chip Current-Sensing Technique," JSSC, January 2004
- W.H. Ki, "Current sensing technique," U.S. Patent 5,757,174, May 26, 1998.
- D. Ma et al., "A 1.8V Singleinductor Dual-output...," VLSI Symp. Circ., June 2001
- H. Y. H. Lam et al., "Loop Gain Analysis and ...," ISCAS 2004
- P. Renz et al., "A 40V Current Sensing Circuit with Fast on/off Transition ...," MWCAS 2016