

---

# Fundamentals of Fully-Integrated Voltage Regulators

Yan Lu  
University of Macau, Macao, China  
[yanlu@um.edu.mo](mailto:yanlu@um.edu.mo)

Live Q&A Session: Feb. 13, 2021, 8:00-8:20 am, PST

# Yan Lu 路延


---



- Education
  - South China University of Technology, Guangzhou, BEng, MSc, '06 & '09
  - Hong Kong University of Science and Technology, Hong Kong, PhD, '13
- Experiences
  - Associate Professor, University of Macau, Macao, June 2020–
  - Assistant Professor, University of Macau, Macao, 2014–2020
  - Visiting Scholar, University of Twente, the Netherlands, 2013 Spring
- Research Interests
  - Fully-integrated voltage regulators
  - Wireless power transfer circuits and systems
- Awards
  - ISSCC 2017 Takuo Sugano Award for Outstanding Far-East Paper
  - IEEE Circuits and Systems Society Outstanding Young Author Award 2017
  - IEEE Solid-State Circuits Society Pre-doctoral Achievement Award 2013-14
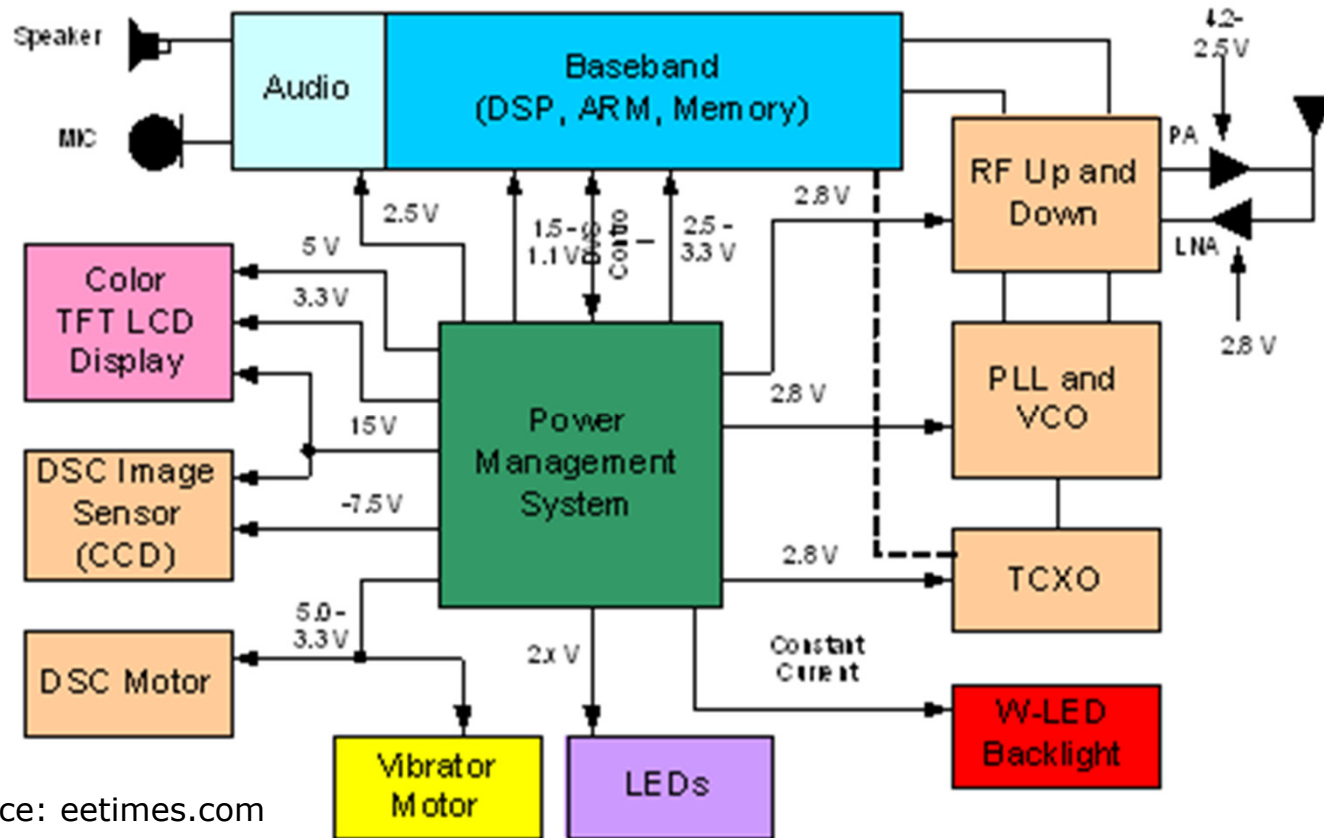
# What does power management do?

- “Cook” the (battery/line) energy for the customers (like processors).



# Outline

---

- Introduction
- Basic Power Stage Selections
  - Linear Low-Dropout (LDO) Regulator
  - Switched-Capacitor Converter
  - Switched-Inductor Converter
- Control Loop Designs
  - PID Control
  - Hysteretic Control
- Advanced Topologies and Techniques
  - Resonant Switched-Capacitor Operation
  - Multiple Interleaving Phase
  - Switched-Capacitor-Inductor Hybrid Topologies
  - Distributed Integrated Voltage Regulators
- Summary


# Outline

---

- Introduction
- Basic Power Stage Selections
  - Linear Low-Dropout (LDO) Regulator
  - Switched-Capacitor Converter
  - Switched-Inductor Converter
- Control Loop Designs
  - PID Control
  - Hysteretic Control
- Advanced Topologies and Techniques
  - Resonant Switched-Capacitor Operation
  - Multiple Interleaving Phase
  - Switched-Capacitor-Inductor Hybrid Topologies
  - Distributed Integrated Voltage Regulators
- Summary

# Fully Integrated Voltage Regulator (FIVR)

---


 


Source: Lion Semi

- Compact size, reduce number of pads, faster transient response, reduce IR drop, fine-grained voltage domains.
  
# Dynamic Voltage and Frequency Scaling (DVFS)


- Decrease  $V_{DD}$  and  $F_{CLK}$  when the CPU is idle.
- Increase  $V_{DD}$  and  $F_{CLK}$  when the CPU needs high performance.
- Transition time is also considered as wasting power.
- **Fast-DVS can significantly save power.**



Source: W. Kim, Harvard

# Fine-Grained Power Domains (Granular power)


---

 

- Energy-efficient computing.
- Granular power needs FIVRs with small area and fast response.




# FIVR Candidates

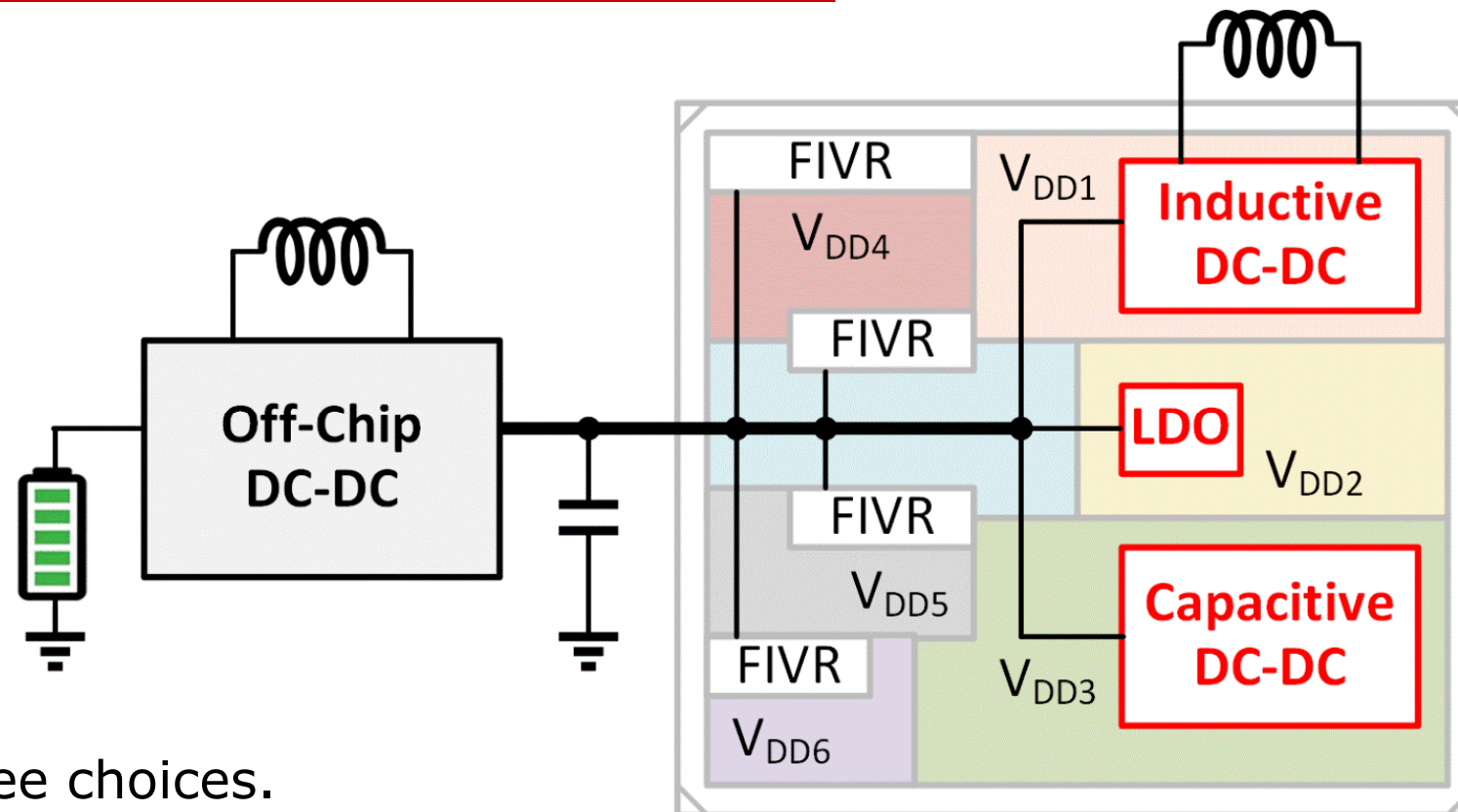

- Basically three choices.
  - Low dropout (LDO) regulator
  - Switched-capacitor (capacitive) DC-DC converter
  - Switched-inductor (inductive) DC-DC converter

# What we will cover in this tutorial.

---

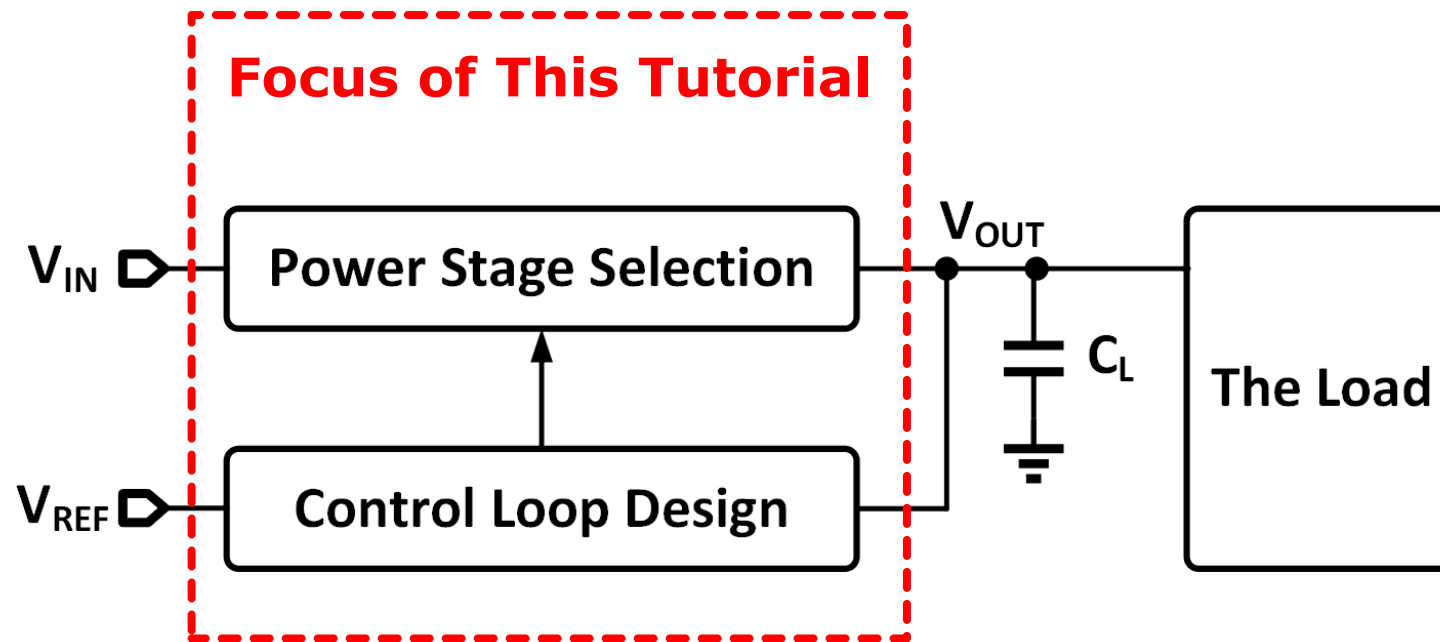

Power stage selection + Control loop design  
for fully-integrated voltage regulator (FIVR)

# Outline


---

- Introduction
- Basic Power Stage Selections
  - Linear Low-Dropout (LDO) Regulator
  - Switched-Capacitor Converter
  - Switched-Inductor Converter
- Control Loop Designs
  - PID Control
  - Hysteretic Control
- Advanced Topologies and Techniques
  - Resonant Switched-Capacitor Operation
  - Multiple Interleaving Phase
  - Switched-Capacitor-Inductor Hybrid Topologies
  - Distributed Integrated Voltage Regulators
- Summary



# LDO Characteristics


---

 

**LDO Regulator**

- ❑ Power transistor operates in linear or saturation region, acts as a tunable resistor.
- ❑ Low efficiency. Efficiency  $\approx V_{OUT}/V_{IN}$ .
- ❑ Single pole power stage, easy to control.
- ❑ No energy storage components (C or L), tiny.
- ❑ Fast transient response.
- ❑ No switching activity (analog control), no ripple.

 
# Output Impedances of the PMOS and NMOS LDOs



$$z_{oP} = r_{dsP} \parallel \frac{1}{sC_L} \parallel \frac{1}{A(s) \cdot g_{mP}}$$

$$z_{oP} = \frac{r_{dsP}}{1 + s \cdot r_{dsP} C_L + A(s) \cdot g_{mP} r_{dsP}}$$
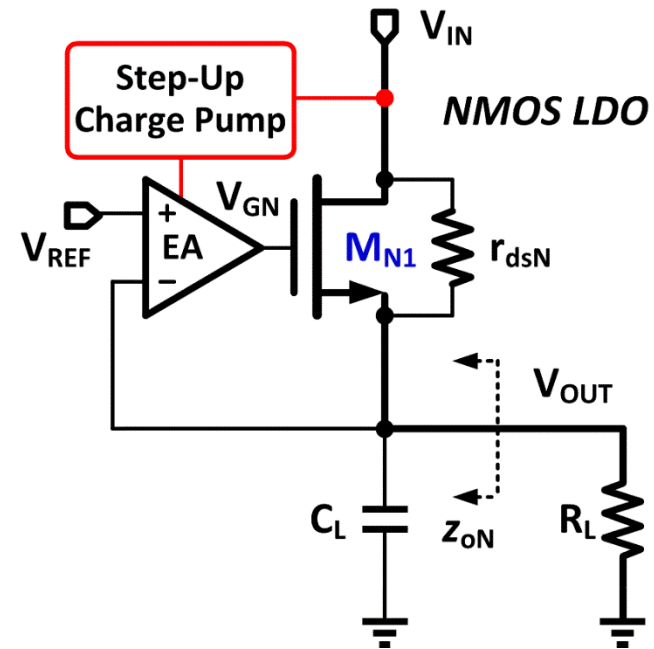
$$z_{oP, LF} \approx 1/A(s) \cdot g_{mP} \quad z_{oP, HF} \approx 1/sC_L$$




$$z_{oN} = r_{dsN} \parallel \frac{1}{sC_L} \parallel \frac{1}{(1 + A(s)) \cdot g_{mN}}$$


$$z_{oN} = \frac{r_{dsN}}{1 + s \cdot r_{dsN} C_L + (1 + A(s)) \cdot g_{mN} r_{dsN}}$$

$$z_{oN, LF} \approx 1/A(s) \cdot g_{mN} \quad z_{oN, HF} \approx 1/(sC_L + g_{mN})$$


# Analogue of Charge Pump

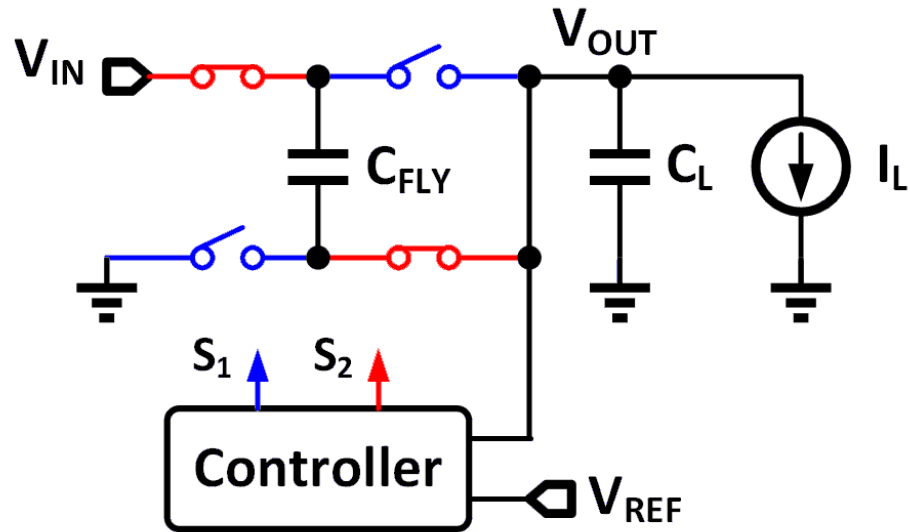

 - Fly capacitor is the cup or bottle.
- The bucket is  $C_L$ .
- The load drain current from  $C_L$ .
- In fast switching, switch is the bottleneck.




# Transfer Charge Between Capacitors

 

- To transfer charge between capacitors, the dissipation on the resistor (switch) is irrelevant to the resistance!


 
# Charge Redistribution Loss (Hard Charging)



$$C_1V_1 + C_2V_2 = (C_1 + C_2)V$$

$$V = \frac{C_1V_1 + C_2V_2}{C_1 + C_2}$$

$$E_{Cap} = \frac{1}{2}CV^2$$

$$E_{Initial} = \frac{1}{2}C_1V_1^2 + \frac{1}{2}C_2V_2^2$$

$$E_{Final} = \frac{1}{2}(C_1 + C_2)V^2$$

$$E_{Loss} = E_{Initial} - E_{Final} = \frac{1}{2} \left( \frac{C_1C_2}{C_1 + C_2} \right) (V_1 - V_2)^2$$

## Assume

$$C_1 = C_2 = C$$

$$\Delta V = 0.5(V_1 - V_2)$$



## We have

$$E_{Loss} = E_{Initial} - E_{Final}$$

$$= C\Delta V^2$$

**$E_{Loss}$  is proportional to  $\Delta V^2$ .**

# Charge Redistribution Loss

  

$$E_{Loss} = \frac{1}{2} \left( \frac{C_1 C_2}{C_1 + C_2} \right) (V_1 - V_2)^2 = \frac{1}{2} C_2 (V_1 - V_2)^2$$

$$C_1 \rightarrow \infty \quad = \frac{1}{2} (V_1 - V_2) \Delta Q_{IN}$$

Assume  $C_1 \gg C_2$ , then,  $V_1$  barely changes and  $C_1$  can be considered as a voltage source.

A current source is connected to  $C_2$  as a load, and  $V_1$  refreshes  $C_2$  periodically.

$$E_{Loss} = \frac{1}{2} (V_1 - V_2) \Delta Q_{IN}$$

$$E_{Load} = \frac{V_1 + V_2}{2} \Delta Q_{OUT}$$


$\Delta Q_{IN} = \Delta Q_{OUT}$  In steady-state

$$\eta = \frac{E_{Load}}{E_{Loss} + E_{Load}}$$


$$= \frac{(V_1 + V_2)/2}{V_1} = \frac{V_{2,AVG}}{V_1}$$

# Linear-VCR Topologies and Fibonacci Topology

## □ Dickson

 


## □ Ladder

 


$V_{CR} = (N+1)V_{IN}$ , N: no. of flying capacitors

## □ Series-Parallel

 

 
## □ Fibonacci ( $V_{CR} = 2, 3, 5, 8, \dots$ )



 
# SC Topology Comparisons

- Series-Parallel (SP)
  - Using the capacitors more efficiently.
  - Large switch resistances in the series state.
  - Suitable for capacitor limited case, like in FIVR.
  
- Cockcroft-Walton (Dickson) and Ladder
  - Perform better at fast switching frequency.
  - Smaller equivalent capacitance compared to SP.
  - Suitable for solution with large capacitance.
  
- Fibonacci
  - Not good in both capacitor and switch usage.
  - Suitable for scenarios with limited number of discrete capacitors.



[M. D. Seeman, TPEL, 2008]


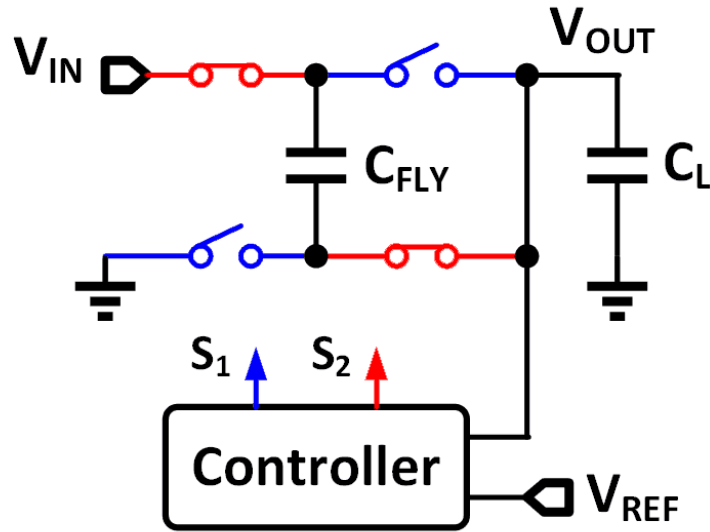
# Switched-Capacitor (SC) Converter Characteristics



## Capacitive DC-DC

- ❑ SC network acts as a tunable resistor, low efficiency.
- ❑  $V_{OUT} = VCR \times V_{IN} - I_{OUT} \times T / \alpha C_{FLY}$ , where  $\alpha$  is a topology related factor.
- ❑ Efficiency can be improved by having a proper voltage conversion ratio (VCR).
- ❑ More capacitors and switches for more VCRs.
- ❑ Single pole power stage, easy to control.
- ❑ Performances of both switches and capacitors improve with advanced processes, easy to integrate.
- ❑ Easy for multi-interleaving phase operation, reducing input and output ripples.


# Operation of a Buck Converter

  

## Inductive DC-DC

- $V_{OUT} = D \times V_{IN}$ , where  $D$  is duty cycle of the switch  $S_1$ .
- $V_{OUT}$  is an averaged value of  $V_X$ .
- $I_{OUT}$  is an averaged value of  $I_{L1}$ .
- LC is a 2<sup>nd</sup>-order filter.
 
# Switching-Mode Buck Converter Characteristics




## Inductive DC-DC

- Energy transfer between L and C is ideally lossless, theoretically high efficiency.
- But, its efficiency heavily depends on the inductor Q.
- Inductor Q is limited by physical constrains.
- Inductor has intrinsically larger DCR than a capacitor, difficult to integrate.
- Switching noises can be large.
- High switching frequency ( $F_{SW}$ ) for smaller passives, but with high switching losses.
- The LC filter forms a two-pole power stage, needs more complex compensation.






# Advanced Power Stage Choices

 


**LDO Regulator**

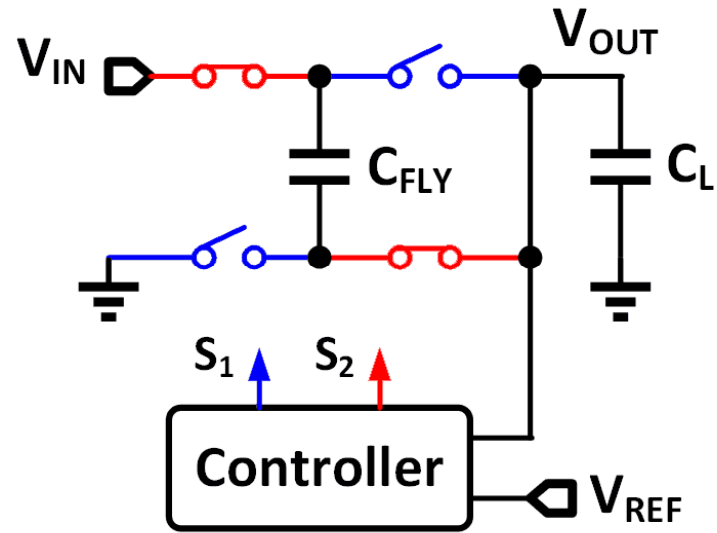

 **Capacitive DC-DC**

**More caps and switches  
for more voltage  
conversion ratios.**



**Inductive DC-DC**

**More caps and switches  
for hybrid operation with  
a smaller inductor.**







**Switched-Capacitor-Inductor  
Hybrid Topology!**

# Outline


---

- Introduction
- Basic Power Stage Selections
  - Linear Low-Dropout (LDO) Regulator
  - Switched-Capacitor Converter
  - Switched-Inductor Converter
- Control Loop Designs
  - PID Control
  - Hysteretic Control
- Advanced Topologies and Techniques
  - Resonant Switched-Capacitor Operation
  - Multiple Interleaving Phase
  - Switched-Capacitor-Inductor Hybrid Topologies
  - Distributed Integrated Voltage Regulators
- Summary
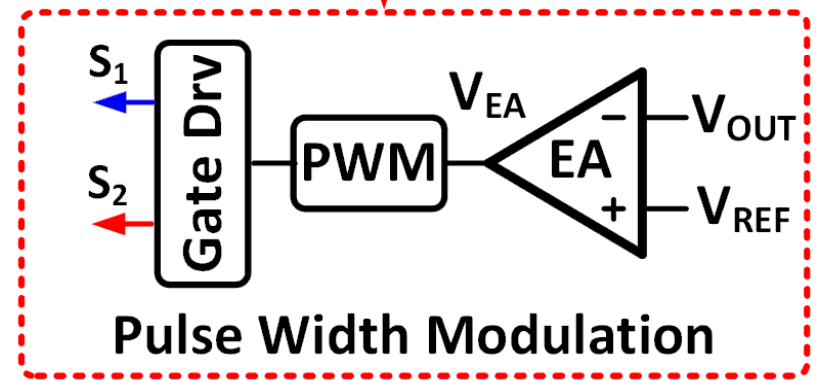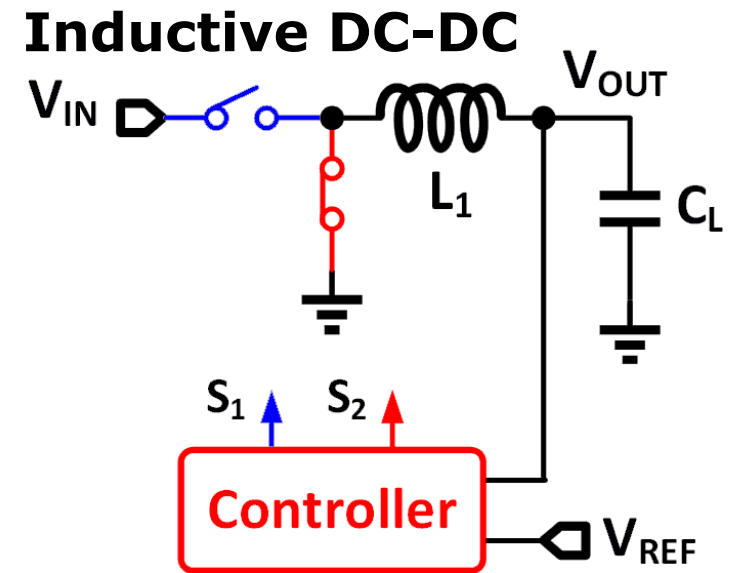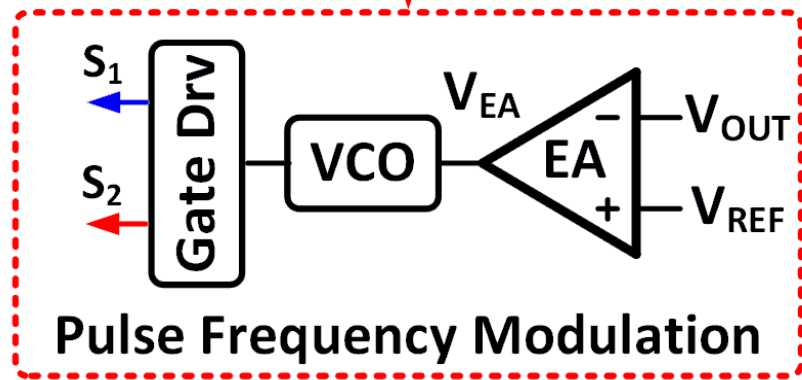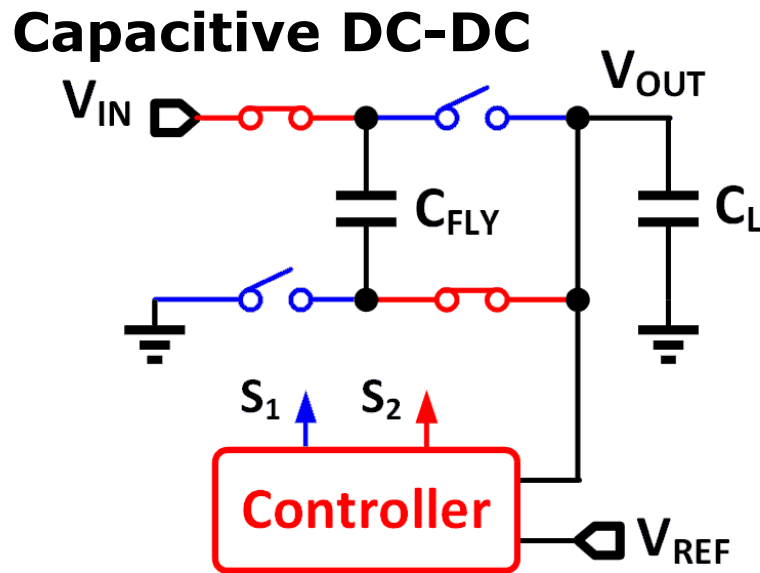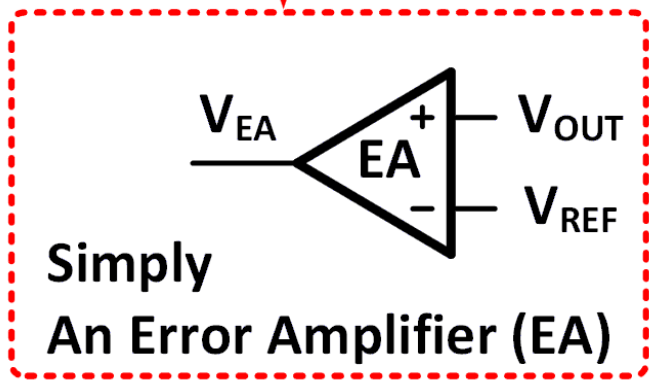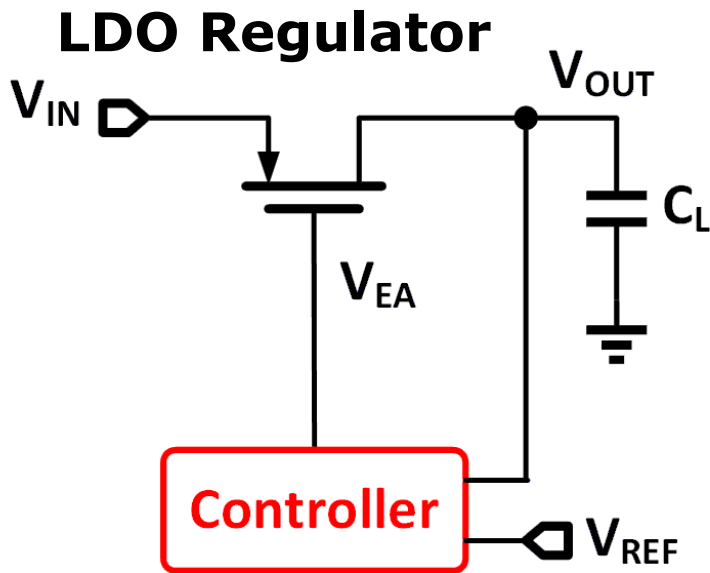
# Basic Control Strategy for Each Selection


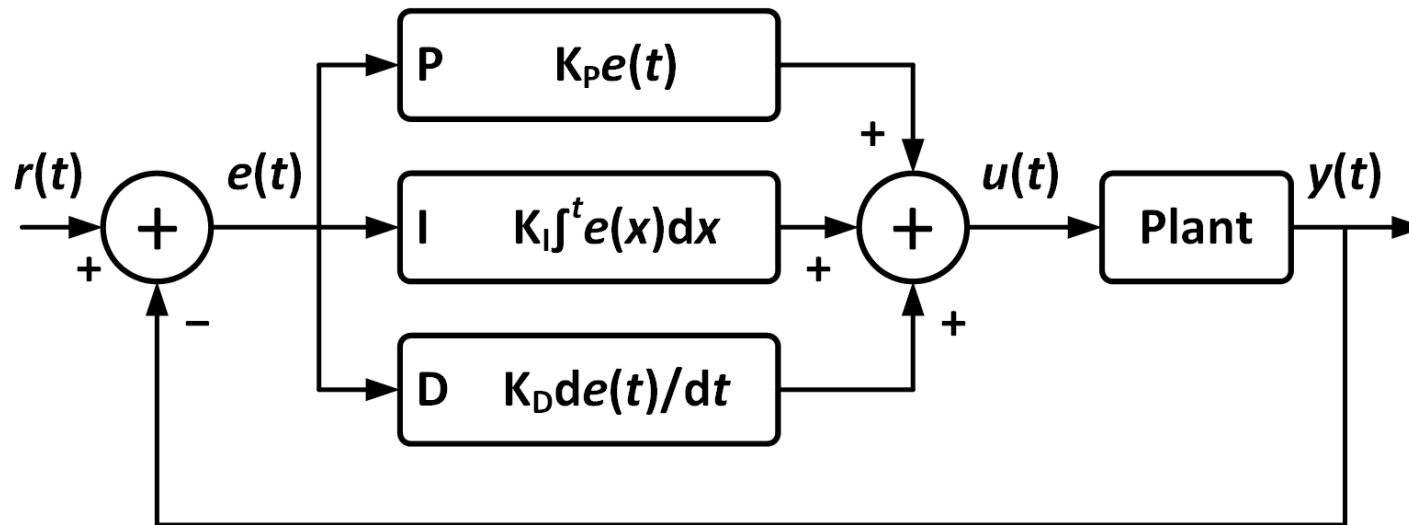
# Proportional-Integral-Derivative (PID) Control




**The plant is the power stage that being controlled.**

$$u(t) = K_P e(t) + K_I \int_0^t e(x) dx + K_D de(t)/dt$$


- The P path output is proportional to the **current** error.
- The I path integrates the **past** information.
- The D path predicts the **future** based on the rate of change.
 
# Bode Plots of PID Control Paths for an LDO




- The I path is a low pass filter.
- The P path may have poles beyond the frequency of interest.
- The D path processes high freq. (HF) signal, so is vulnerable to HF noise.
 
# Load Transient Responses with PI or PID Controls




# LDO with Proportional (P) Control

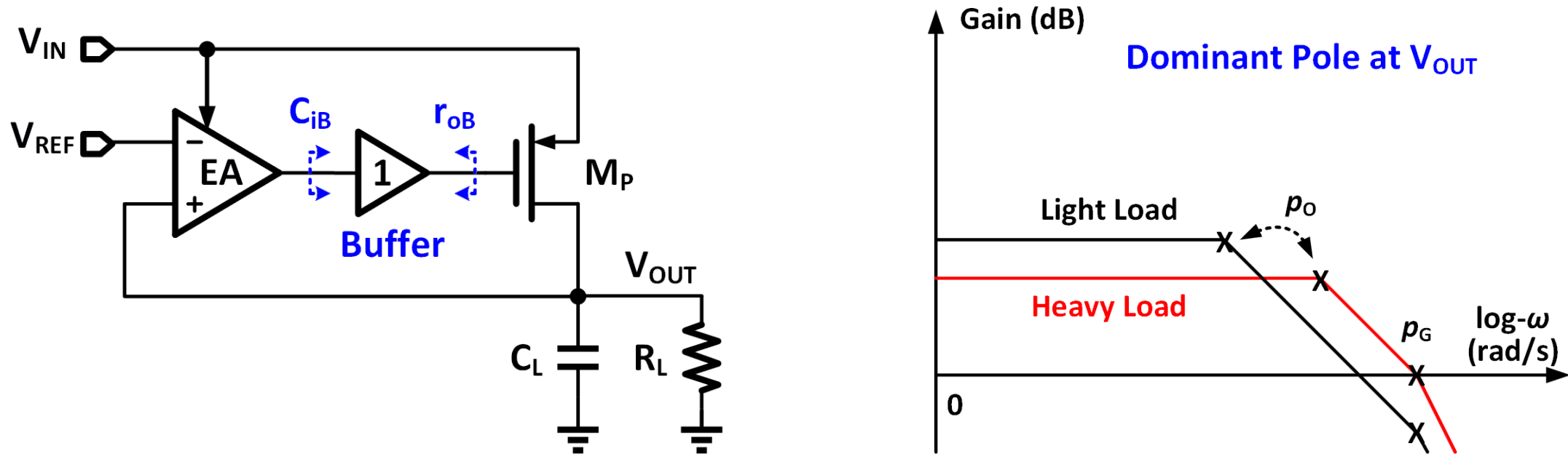

- ❑ Output pole dominant.
- ❑ Push internal poles to HF with buffer.
- ❑ Output current is proportional to the  $V_{OUT}$  error.
- ❑ **Fast, but poor accuracy.**



# Example: LDO with Small-Gain Stages

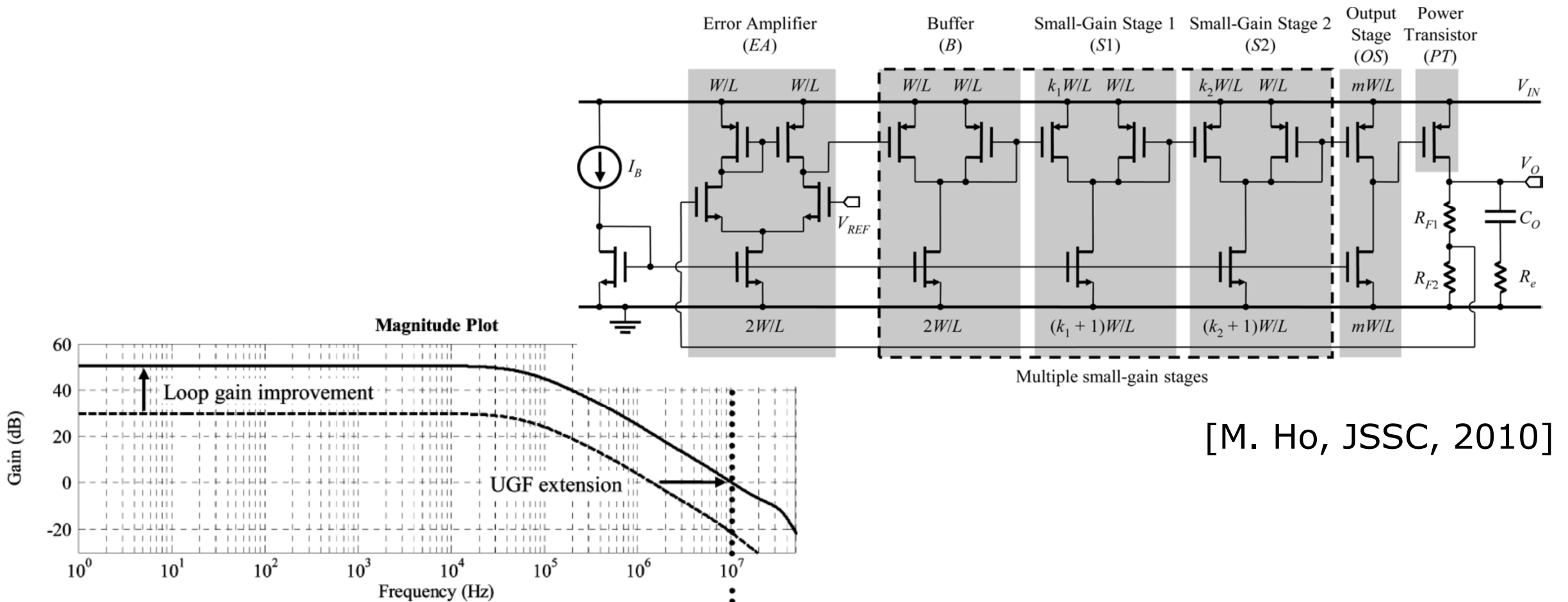

- Increase the loop gain with multiple small-gain stages, advanced P control.





# Integral (I) Control

  

- ❑ Internal pole dominant.
- ❑  $V_{OUT}$  error is integrated on an internal capacitor.
- ❑ Miller compensation lowers the dominant pole freq. with smaller capacitor.
- ❑ **Low power, accurate, but slow.**

 
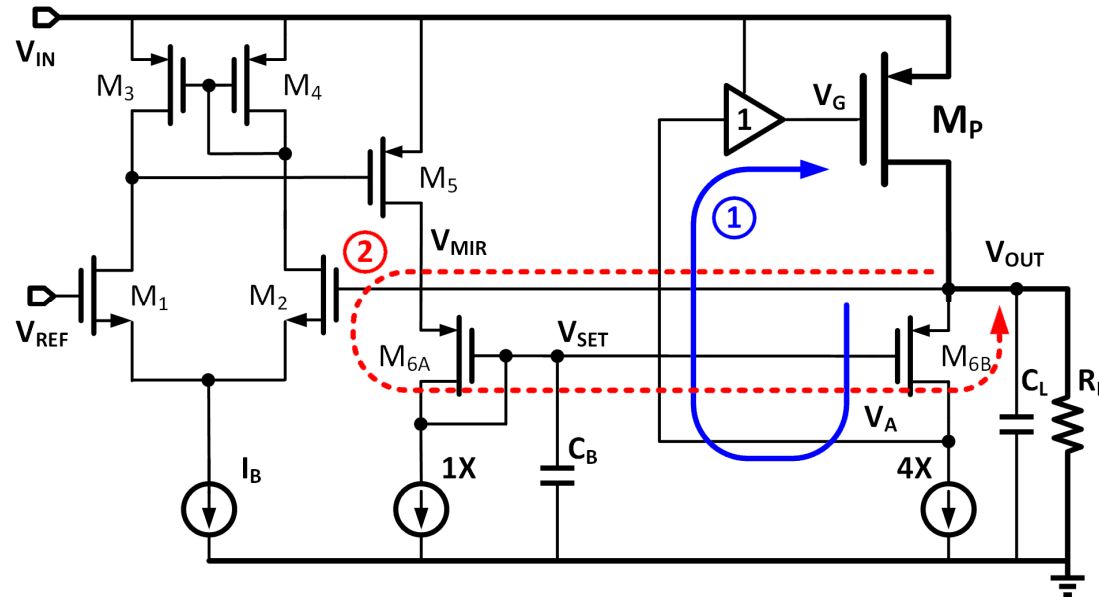
# Example: LDO with Dual-Loop (PI) Control



- ❑ Realize PI control with one fast (P) loop and one slow (I) loop.
- ❑ The flipped-voltage follower (FVF) forms the P path.
- ❑  $C_B$  is an integrator.



[Y. Lu, ISSCC, 2014]

# Derivative (D) Control

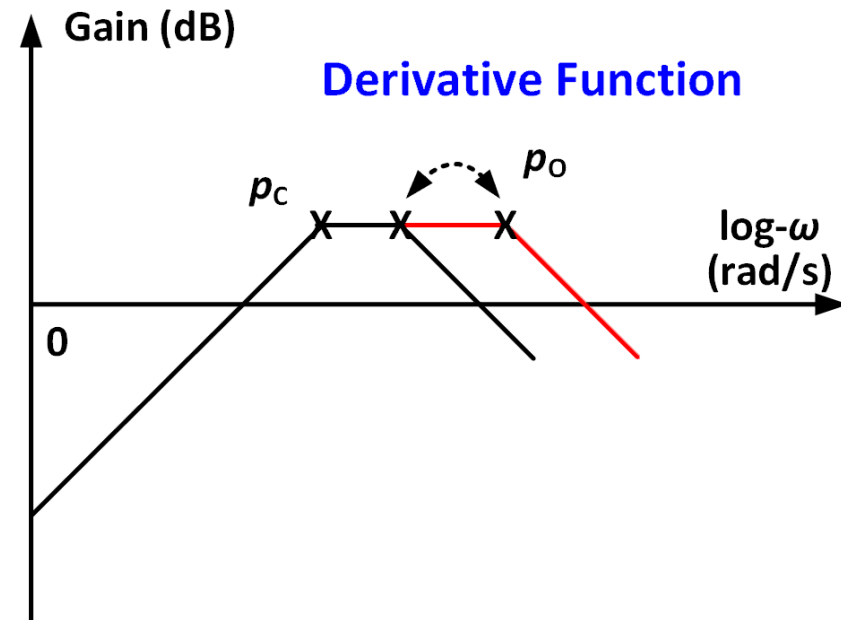 

- A derivative path is a high-pass path, contributes a zero.
- The high frequency (HF) path is vulnerable to HF noise.
- Needs HF poles to attenuate the HF noise, then becomes a band-pass path.


# Example: LDO with a Differentiator

 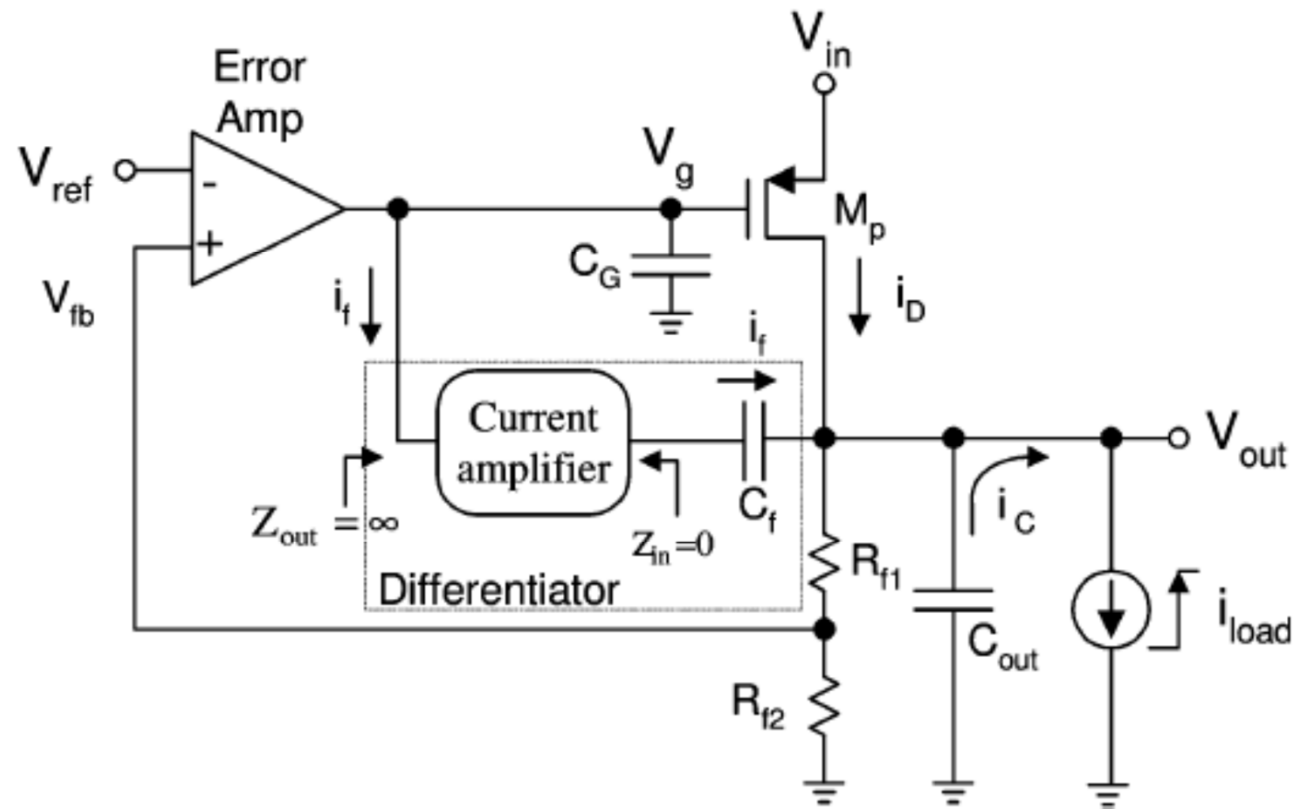

[R. J. Milliken, TCAS-I, 2007]


- $C_f$  senses the slope of  $V_{OUT}$  changes.
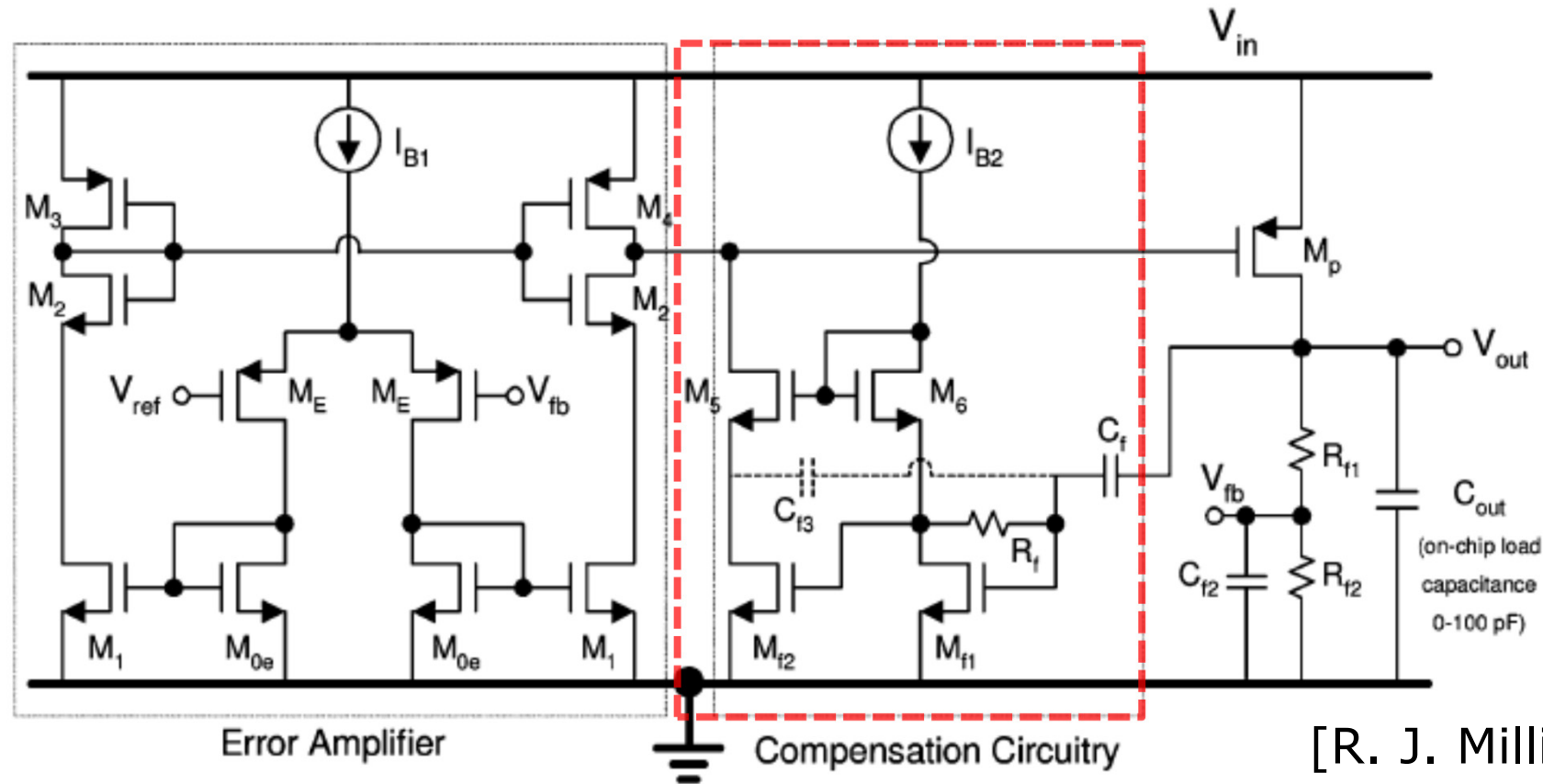
# Transistor-Level Schematic of the LDO with Differentiator



- $R_f$  transforms the  $C_f$  transient current into a voltage, helps to lower the differentiator's input impedance, pushing the added pole to higher frequency.

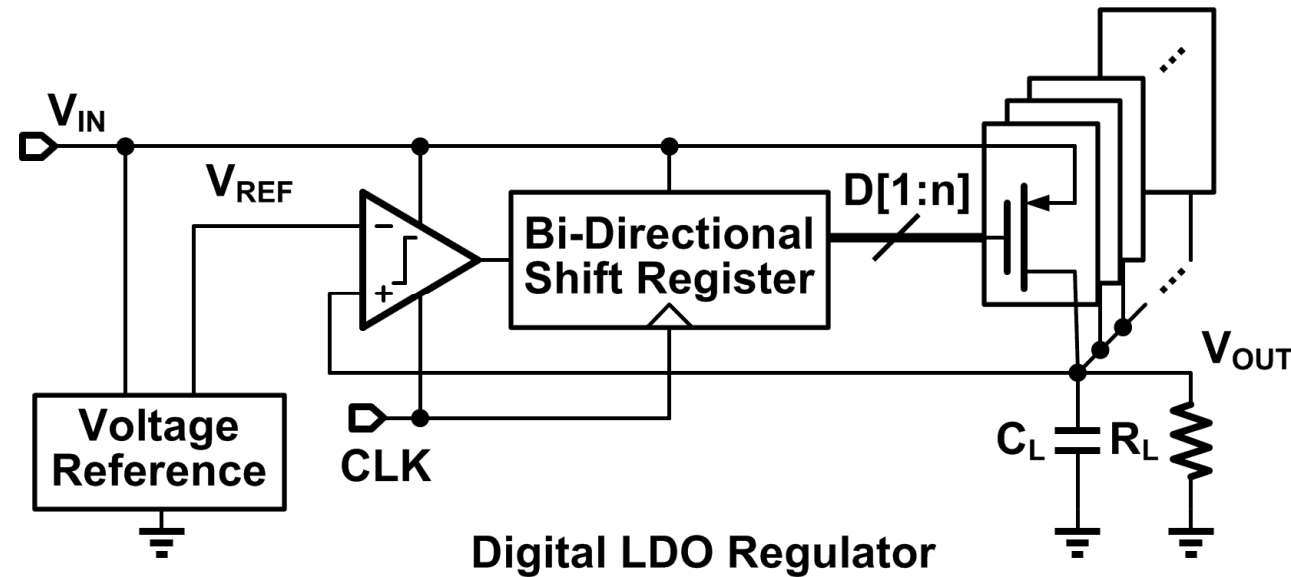
# Digital Low Dropout Regulator (Digital LDO)



- ✓ Low voltage operation ( $<0.6\text{V}$ )
- ✓ Benefit from process scaling
- ✓ Easy cooperation with digital loads
- x Not energy-efficient for the power-speed tradeoff
- x Limit cycle oscillation (LCO)

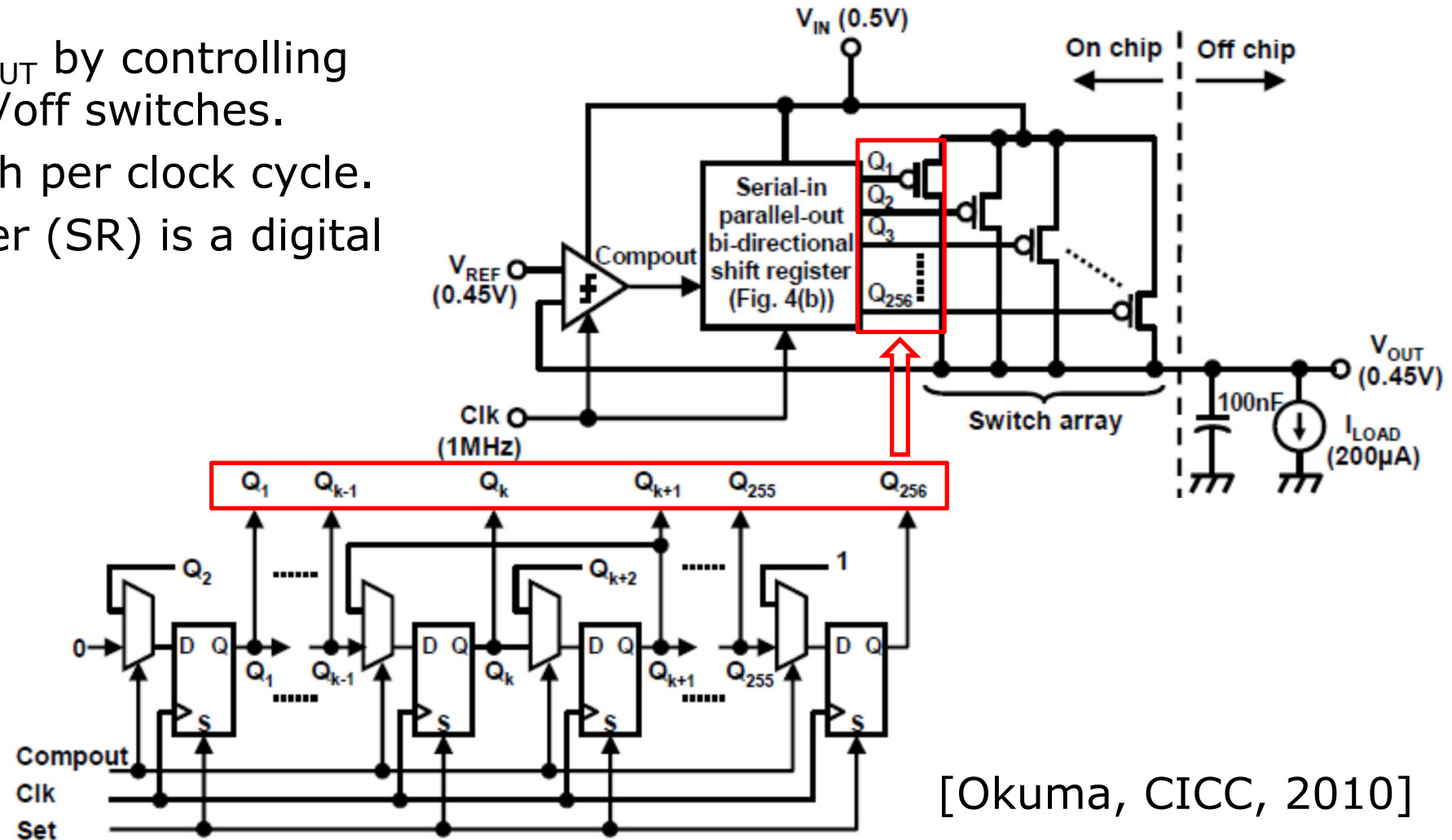
# Shifter-Register-Based Digital LDO (I Control)

- Regulating the  $V_{OUT}$  by controlling the number of on/off switches.
- Change one switch per clock cycle.
- The shifter register (SR) is a digital integrator.



[Okuma, CICC, 2010]

# Example: DLDO with PI Control

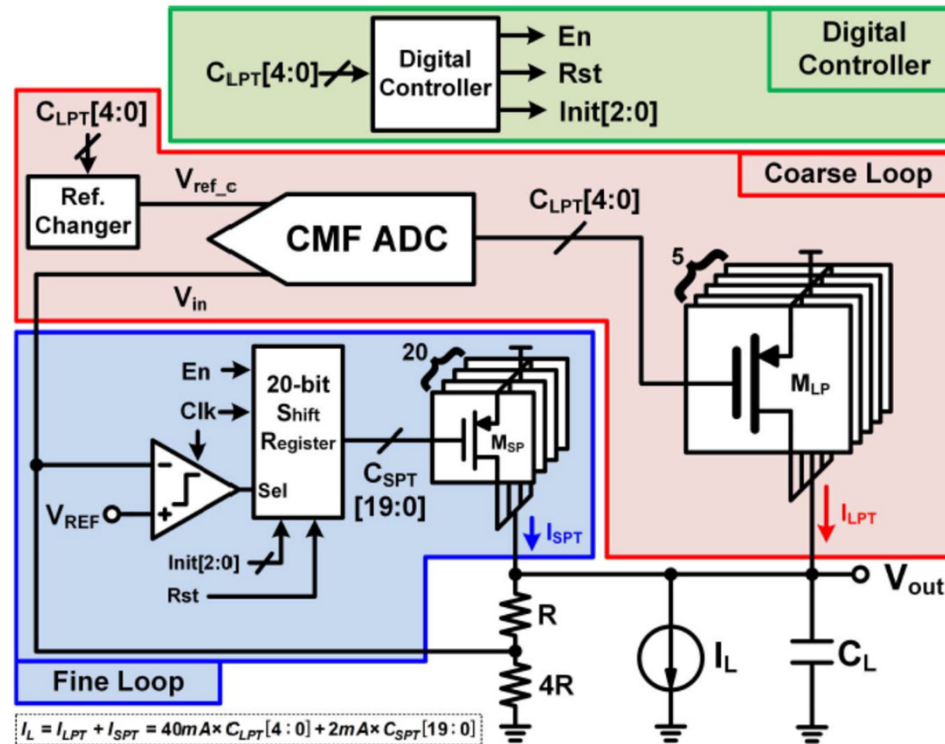


[Y.-J. Lee, ISSCC, 2016]

[Y.-J. Lee, JSSC, 2017]

- Shift-register based loop for fine tuning (I control).
- Flash-ADC based loop for coarse tuning (P control).
- Reference changer compensates the  $V_{OUT}$  error that comes from the P control.





# Example: DLDO with PI Control

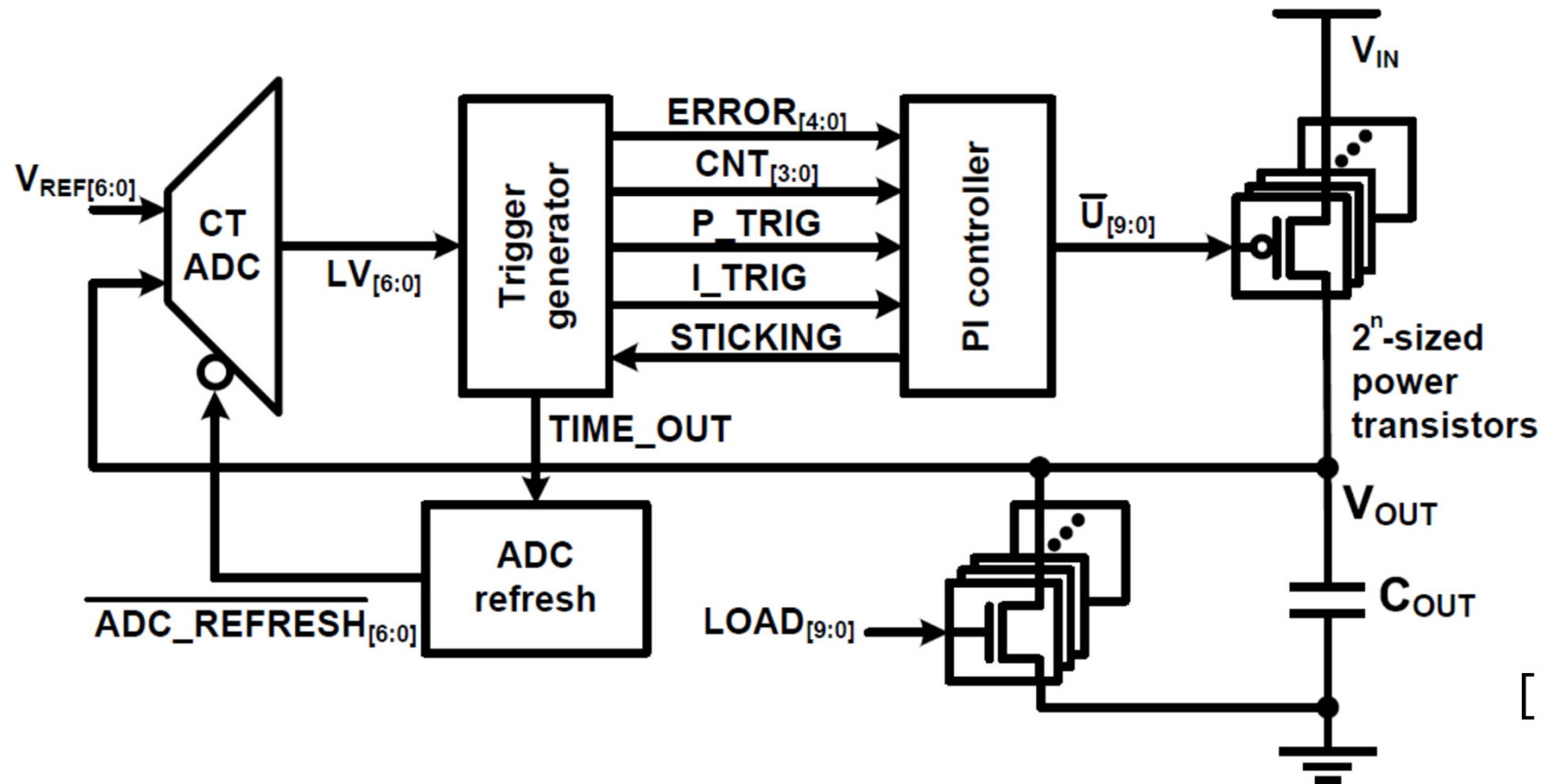

[D. Kim, ISSCC, 2016]  
[D. Kim, JSSC, 2017]

- Continuous-time ADC: 7-bit thermometer-coded.



# Example: DLDO with PID Control

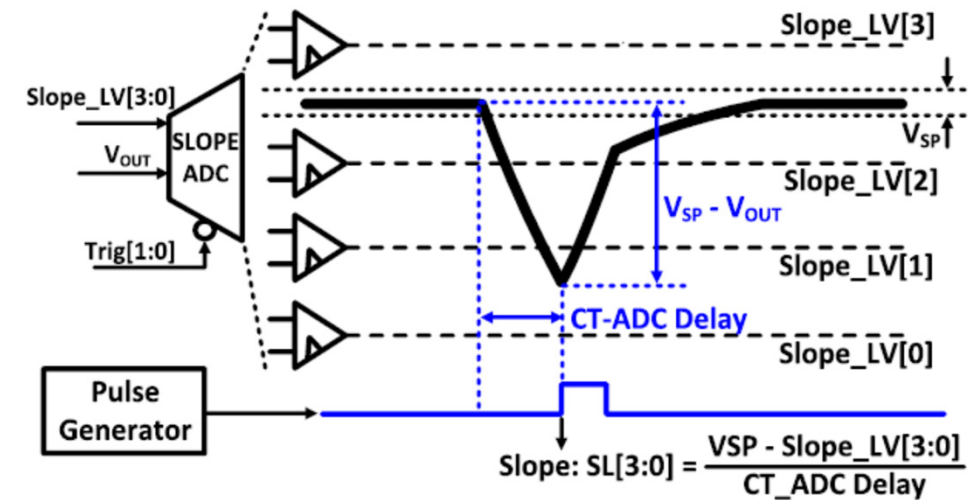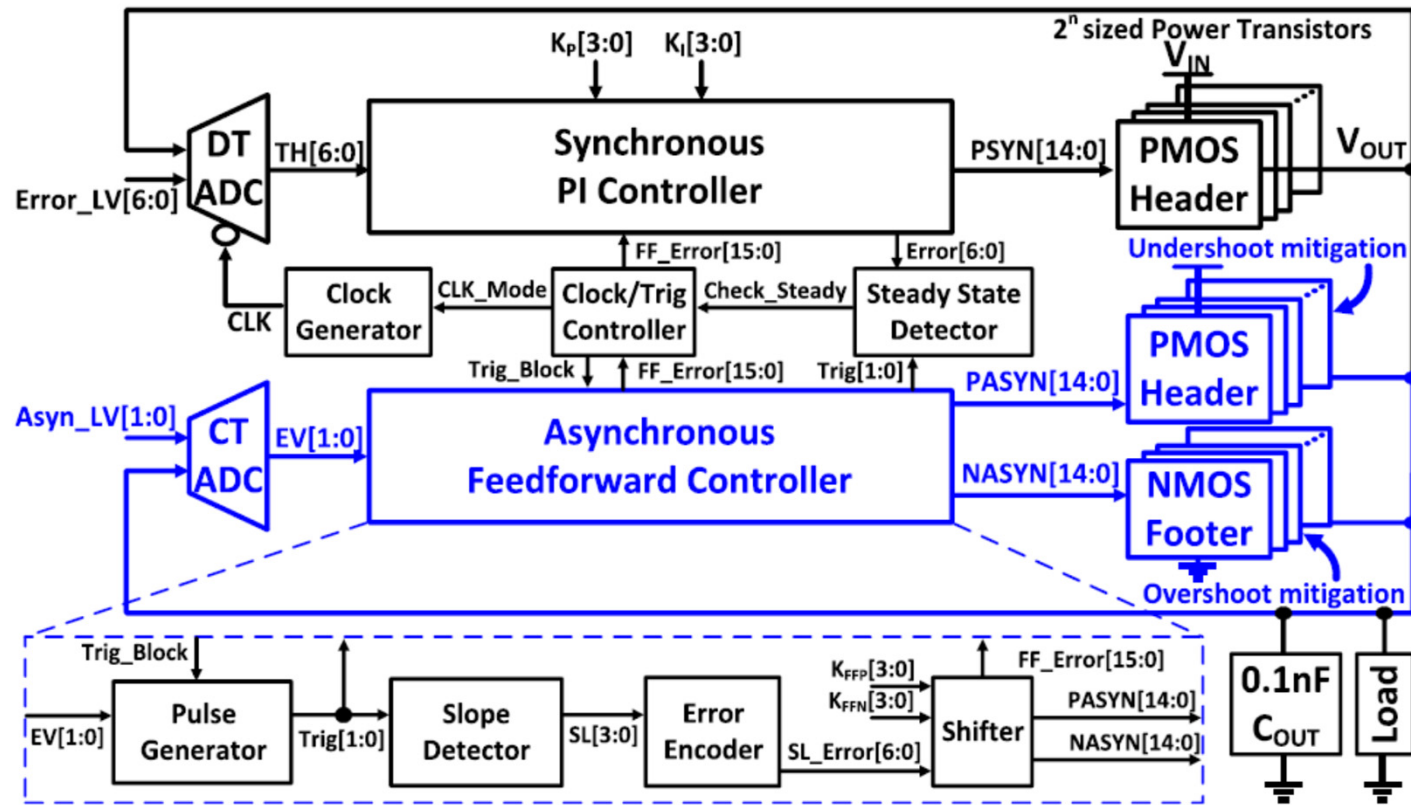

[S. J. Kim, SSC-L, 2018]

- ❑ Asynchronous slope detection (D).
- ❑ Synchronous PI control.



# Control Loops: Analog, Digital, Hybrid

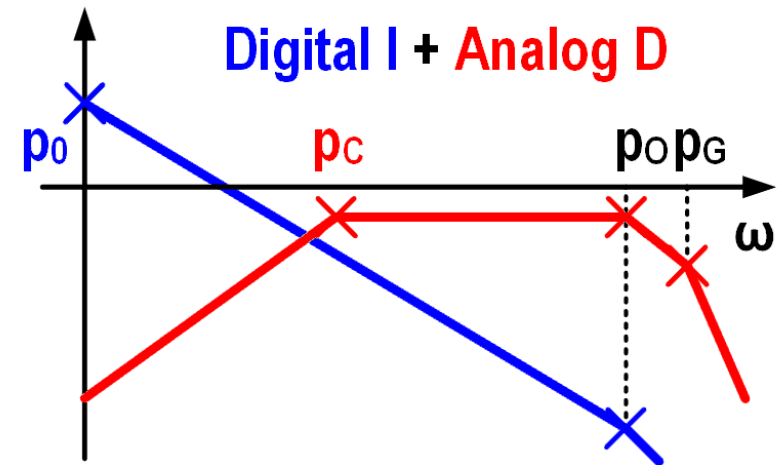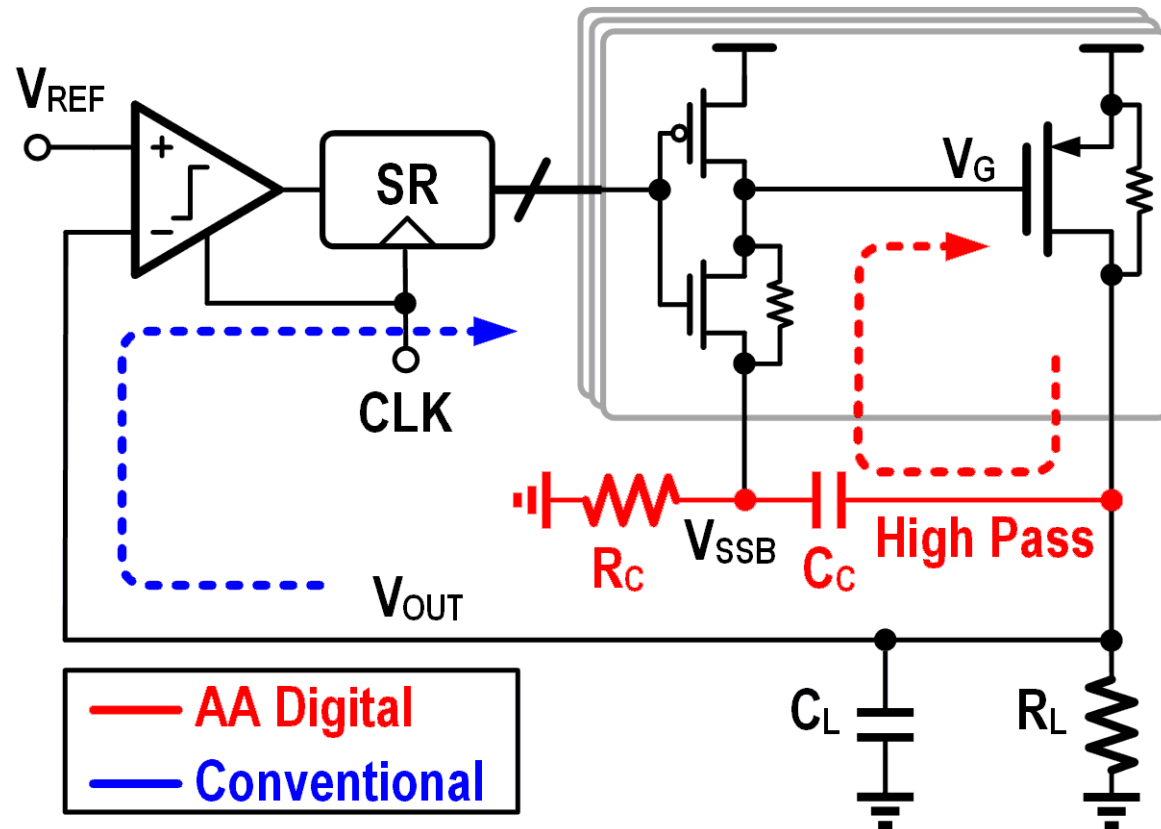

[M. Huang, ISSCC 2017]  
[M. Huang, JSSC 2018]

- Using a high pass analog path to assist the slow digital loop.


# Analog-Assisted (AA) NMOS Digital LDO

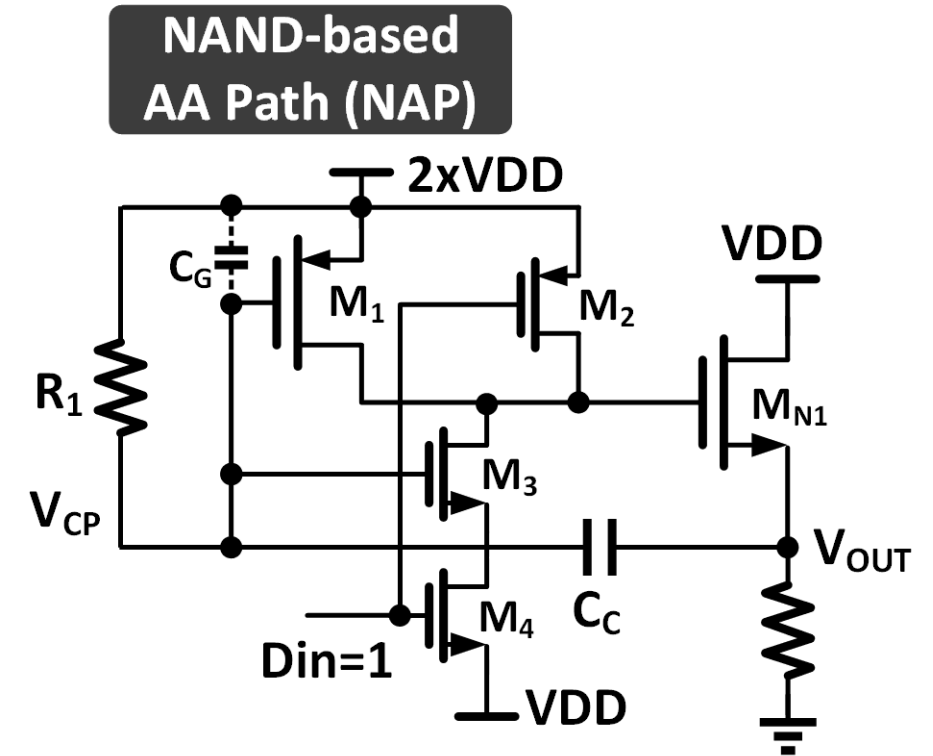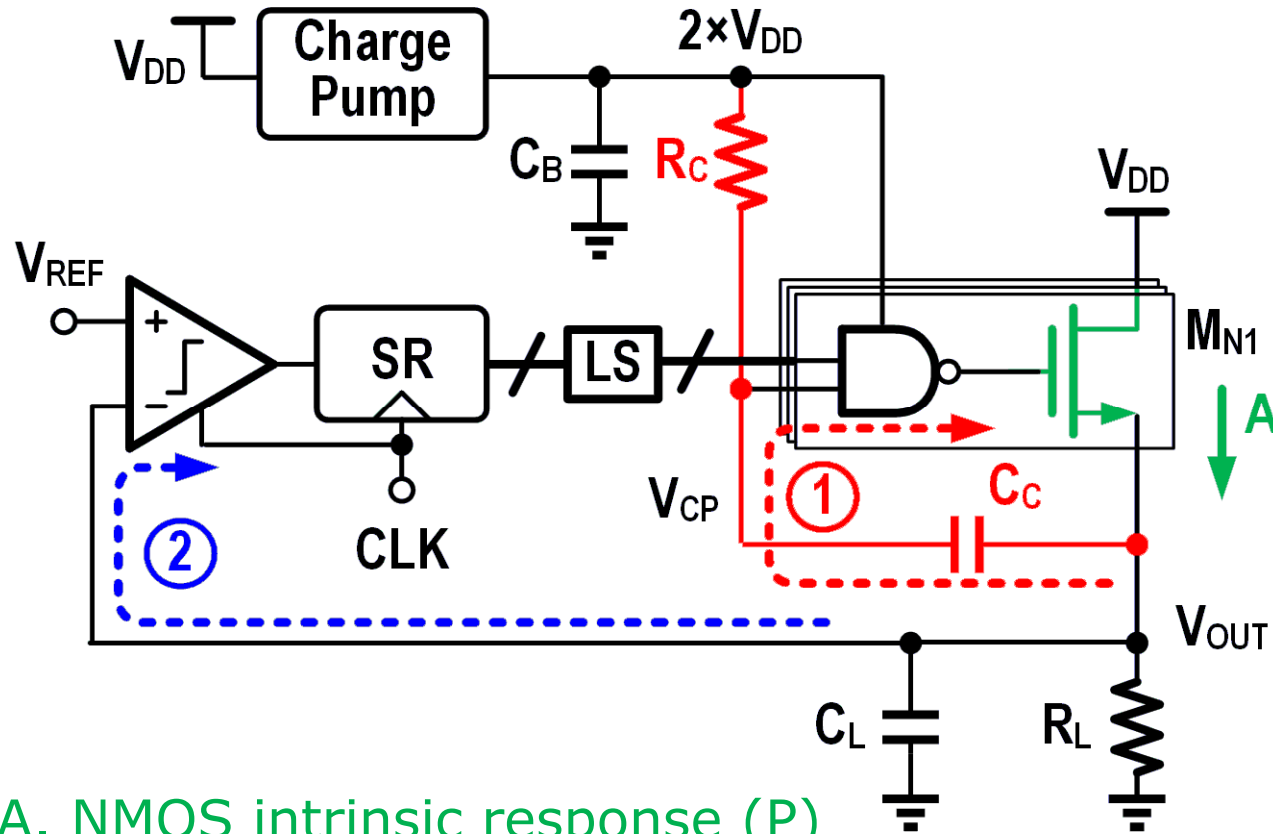

- A. NMOS intrinsic response (P)
- 1. NAND-based AA path (D)
- 2. Digital control loop (I)

[X. Ma, ISSCC 2018]

# Example: Analog-Digital Hybrid LDO

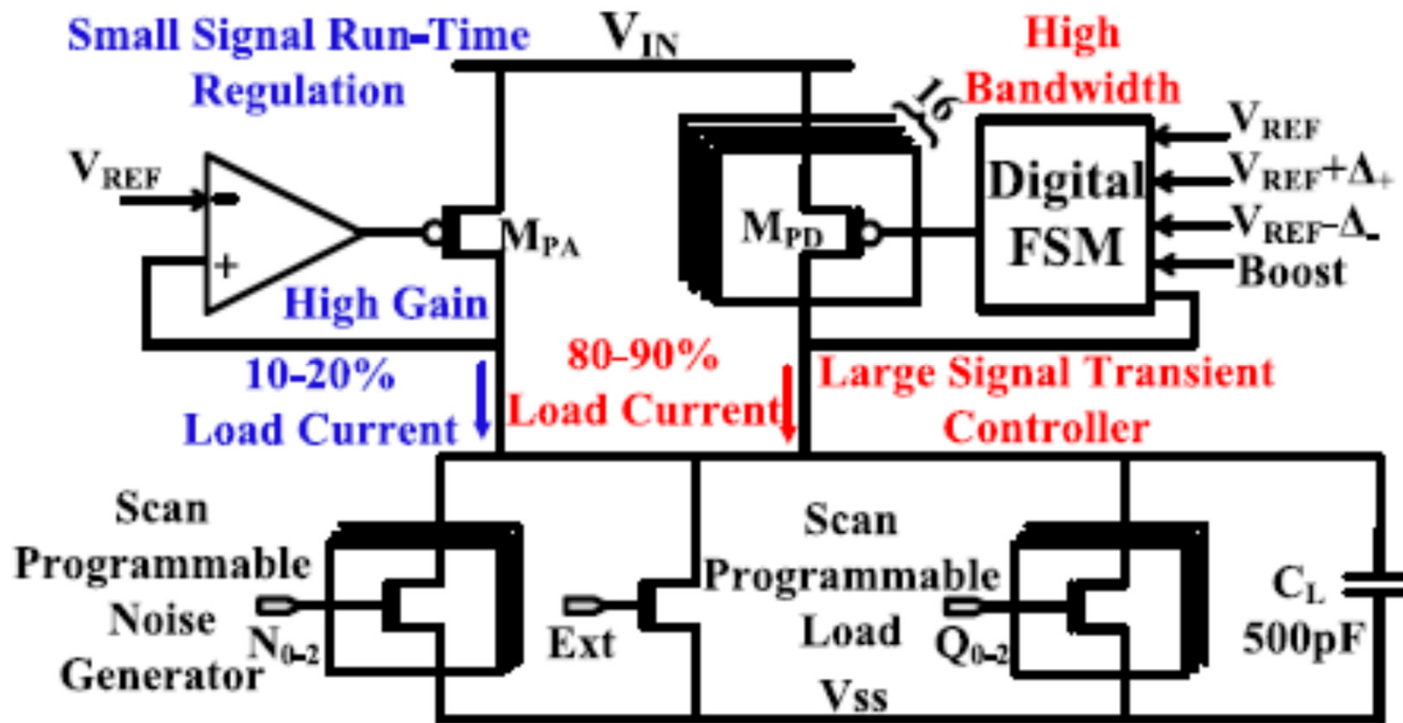



[S. B. Nasir, ESSCIRC, 2016]  
[S. B. Nasir, JSSC, 2018]

- Small-signal analog.
- Large-signal digital.

# Example Summary of LDO Control Techniques

Category	Publications	Techniques
<b>Analog P</b>	Ho, JSSC 2010	Small-gain stages
<b>Analog PI</b>	Lu, TCAS-I 2015	Dual-loop with fast FVF
<b>Analog PID</b>	Milliken, TCAS-I 2007	Differentiator
<b>Digital I</b>	Okuma, CICC 2010	Shift-register based
<b>Digital PI</b>	Lee, ISSCC 2016 Kim, ISSCC 2016	Flash ADC with reference changer Multi-bit ADC and digital PI
<b>Digital PID</b>	Kim, SSC-L 2018	Slope detector
<b>Digital I + Analog P</b>	Nasir JSSC 2018 Huang, CICC 2019	Small-signal analog Fast and adaptive analog
<b>Digital I + Analog D</b>	Huang, ISSCC 2017	Analog-assisted (AA) digital
<b>Digital I + Analog PD</b>	Ma, ISSCC 2018	NAND-based AA NMOS LDO
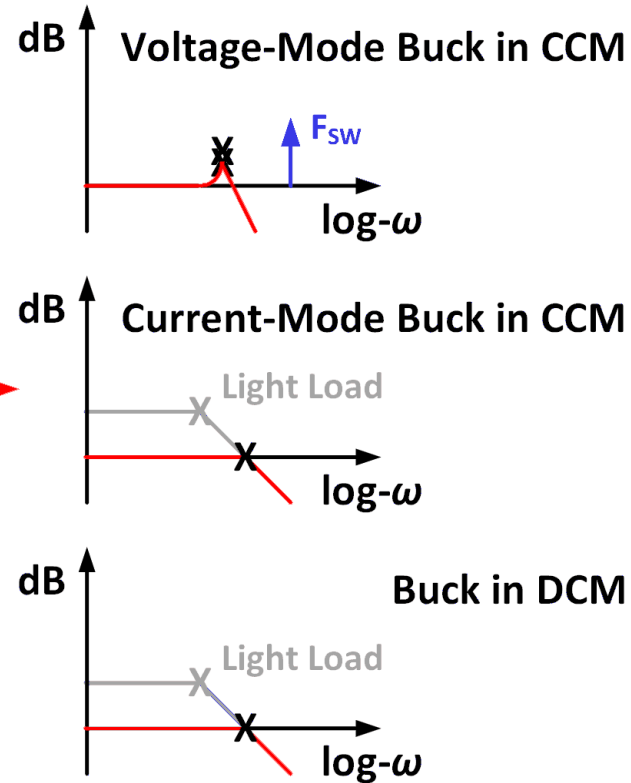 
# Bode Plots of PID Control for Buck Converter





- The LC filter in continuous-conduction mode (CCM) has a pair of complex poles.
- Current-mode control uses the inductor current information, complex pole pair turns into two separated real poles, one related to  $R_L$ .
- Discontinuous-conduction mode (DCM) operation only has a small inductor, of which the dynamics occur at HF, above or just below  $F_{sw}$ .

# Loop Compensation for Buck Converter

 
 
## □ Type-I: I Control

- Simple, slow.
- Need large compensation cap.
- Unity-gain freq. (UGF) limited to  $\sim 10x < F_{RES,LC}$ .



  
## □ Type-II: PI Control

- 1 zero compensates 1 pole.
- Used for current mode or DCM.
- Not for voltage mode CCM.



 
## □ Type-III: PID Control

- 2 zeros compensate complex pole pair.
- For voltage mode, extend the UGF  $> F_{RES,LC}$ .





# Hysteretic Control (Bang-Bang Control)

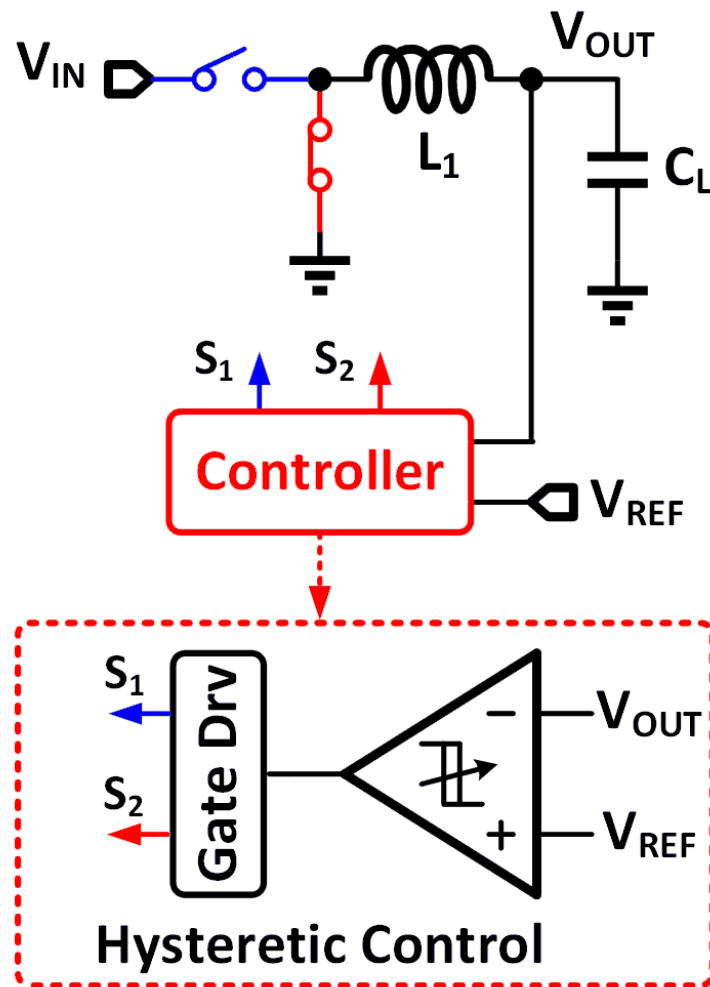

- Replace the compensator and PWM generator with simply a hysteresis comparator. React immediately when  $V_{OUT} < V_{REF} - \Delta$ , or  $> V_{REF} + \Delta$ .
- Pros:
  - Extremely simple, and extremely fast.
  - Low quiescent current.
- Cons:
  - $F_{SW}$  varies with  $V_{IN}$  and  $I_{OUT}$ , EMI issue.
- Solutions:
  - Adaptive hysteresis window tuning.
  - Constant on-time control,  $D = T_{ON}/T = V_{OUT}/V_{IN}$ .

# Outline


---

- Introduction
- Basic Power Stage Selections
  - Linear Low-Dropout (LDO) Regulator
  - Switched-Capacitor Converter
  - Switched-Inductor Converter
- Control Loop Designs
  - PID Control
  - Hysteretic Control
- Advanced Topologies and Techniques
  - Resonant Switched-Capacitor Operation
  - Multiple Interleaving Phase
  - Switched-Capacitor-Inductor Hybrid Topologies
  - Distributed Integrated Voltage Regulators
- Summary

# Root-Mean-Square (RMS) Current


## □ Sinusoidal current

■  $I_{RMS,S} = I_{AVG} \times 1.11$

 


## □ Triangular current

■  $I_{RMS,T} = I_{AVG} \times 1.155$

 

## □ Duty-cycled (D) current

■  $I_{RMS,D} = I_{AVG} / D^{1/2}$

 


## □ Conduction loss = $I_{RMS}^2 R$


■  $1.11^2 = 1.232$  (Sinusoidal)

■  $1.155^2 = 1.334$  (Triangular)


■  $1.414^2 = 2$  (Pulse D=0.5)

 
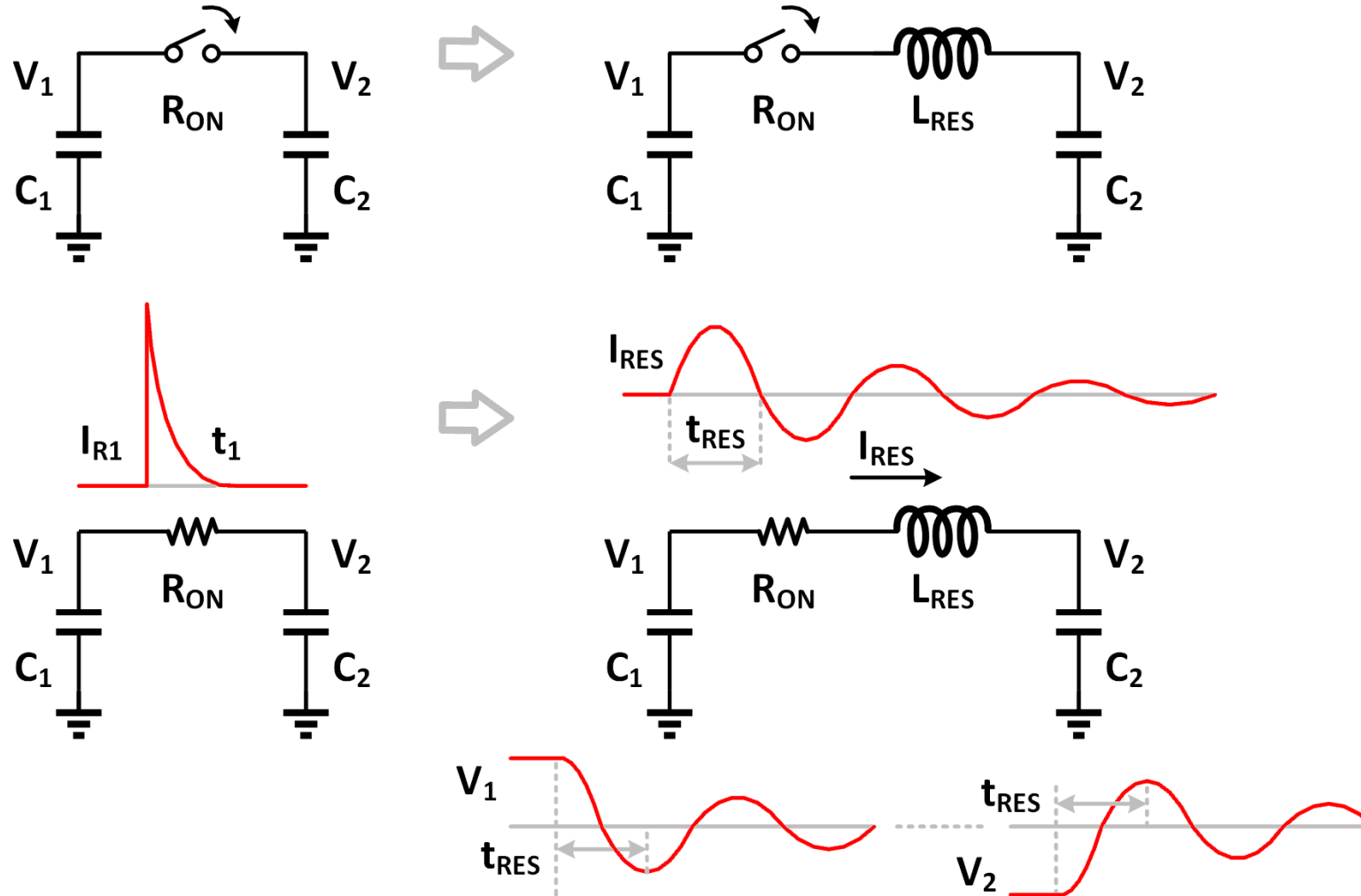
# Charge Redistribution with a Resonant Inductor



 
# Charge Redistribution with a Resonant Inductor



- No hard charging and no loss in the ideal resonant case.
- Soft charging.

# Resonant SC (ReSC) Converter


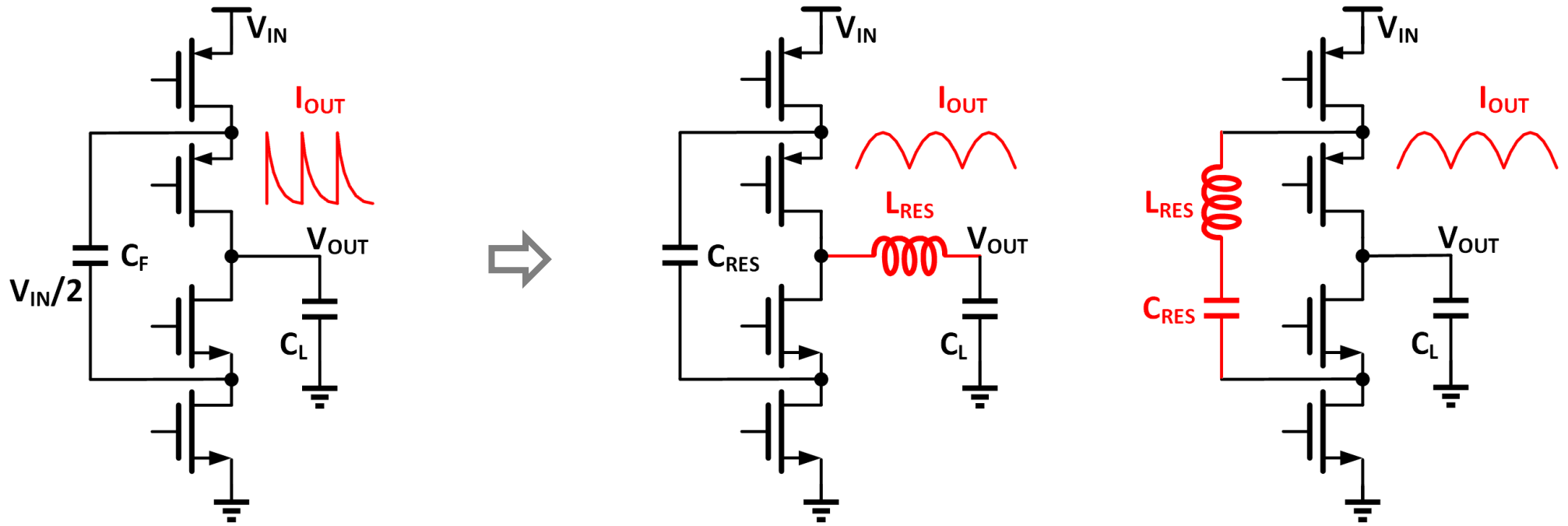


- ❑ 2:1 SC Converter
- ❑ Hard charging

- ❑ 2:1 Resonant SC Converters
- ❑ Soft charging



# Output Impedance of a Resonant SC Converter

[K. Kesarwani, ISSCC, 2014]

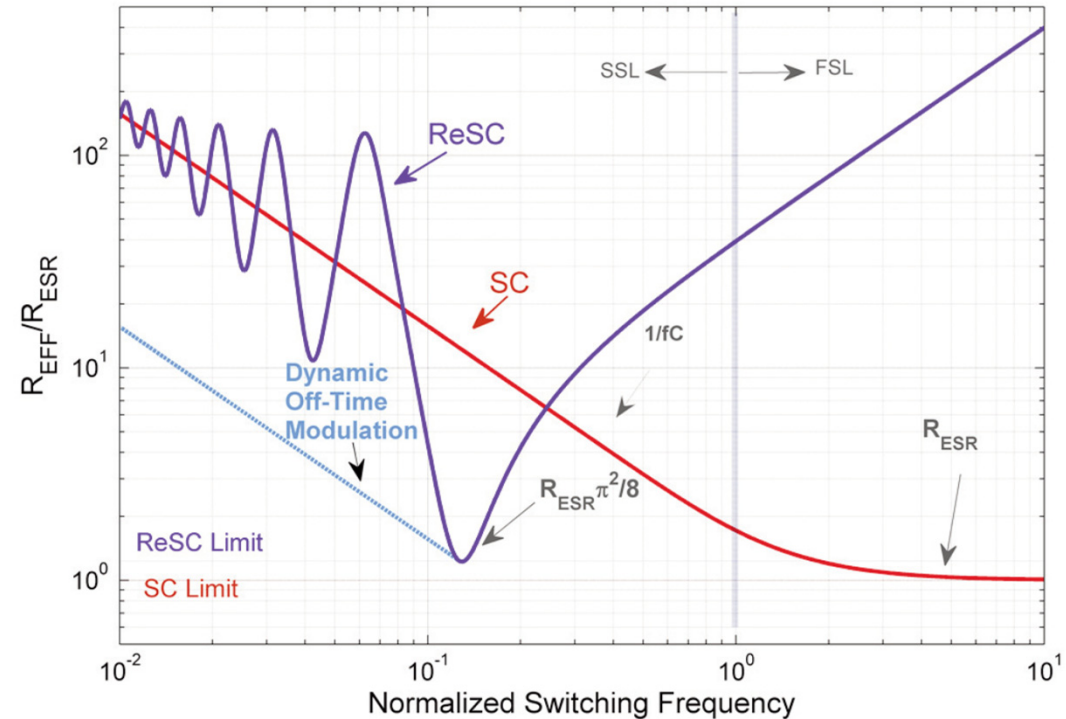 

- ReSC converter achieves the same  $R_{OUT}$  as SC converter at much lower  $F_{SW}$ .
- Resonant operation allows  $C_{RES}$  to have much larger  $\Delta V$ , compared to  $C_F$  in SC.
- But, the maximum output capability is limited by  $L_{RES}$ .

# Ripple Effect

 
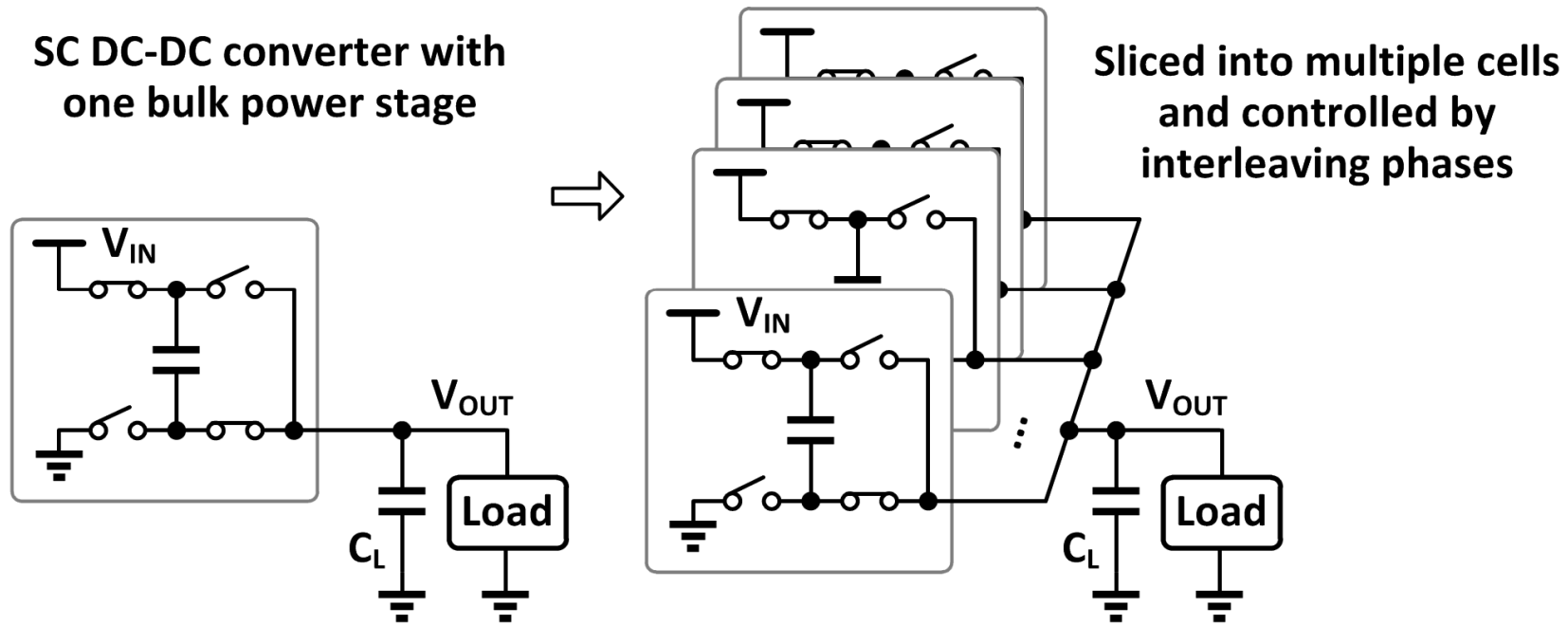


- Any voltage higher than  $V_{OUT,MIN}$  is wasted.


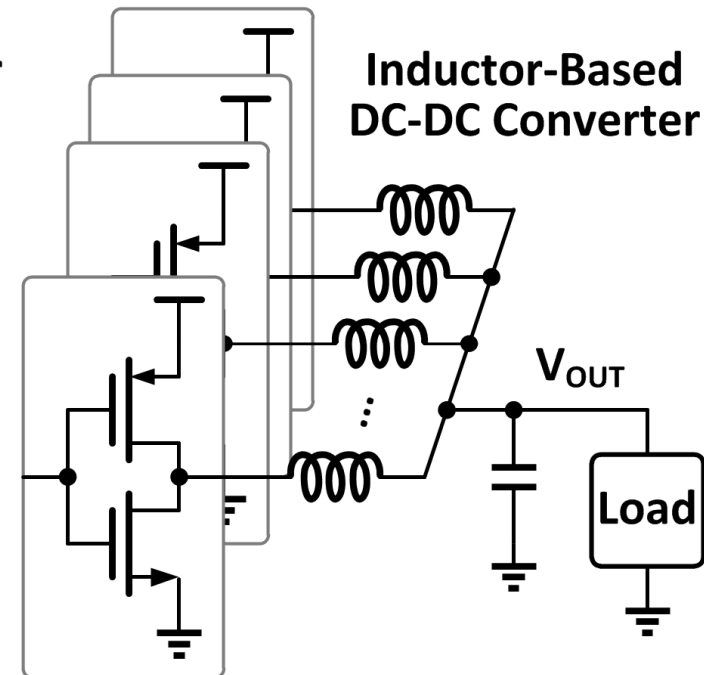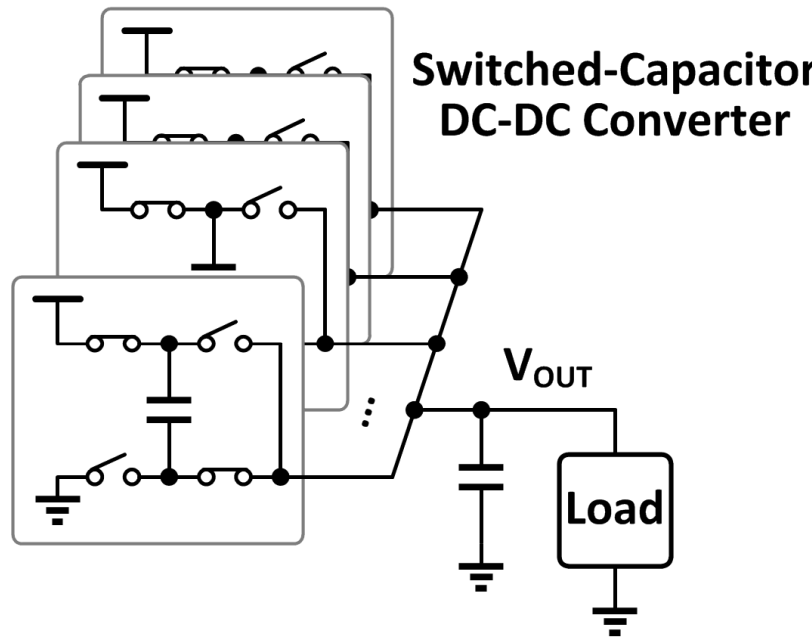
# Multiphase-Interleaving DC-DC Converters


- Reduce output voltage and input current ripples.



- ✓ Fully-on-chip, multi-phase
- x Efficiency (like linear regulator)
- ✓ First-order power stage (Potential for fast control loop)

- x One  $L$  for each phase
- Efficiency (ideally 100%, but need high  $Q$ )
- $LC$  second-order filter (Complex compensator)
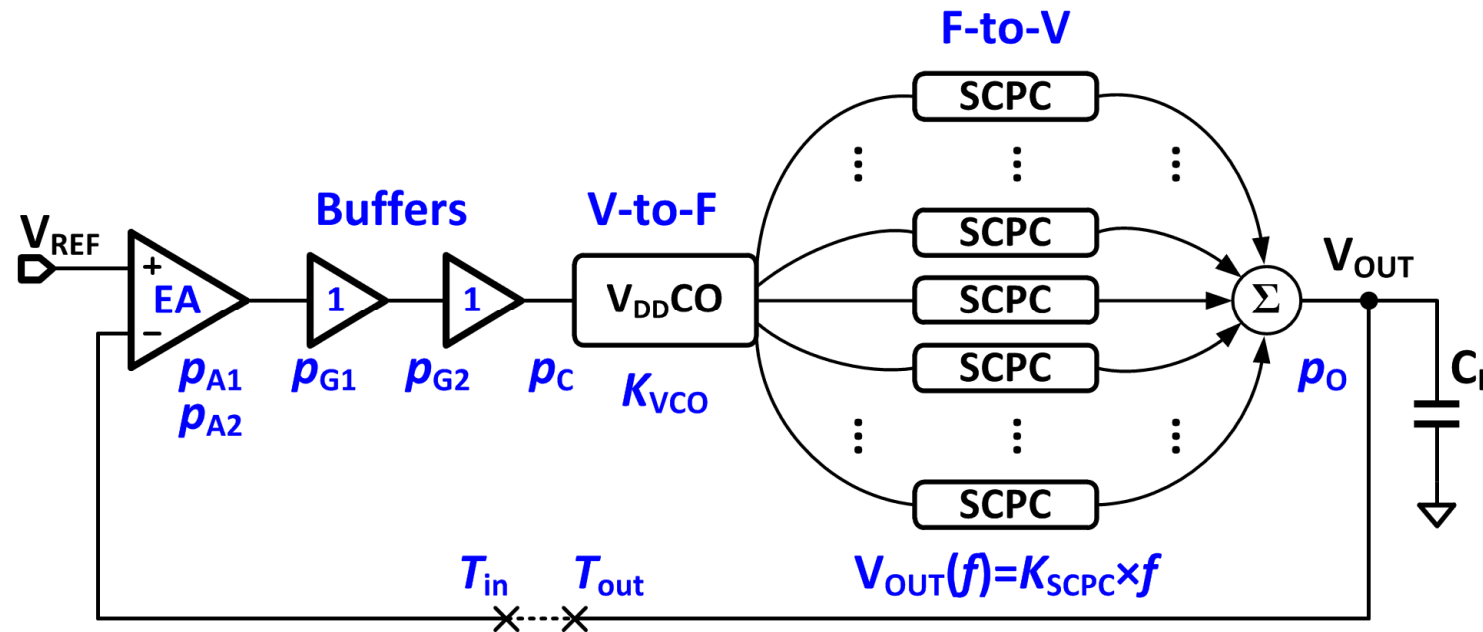
# Extending the Loop Bandwidth Beyond $F_{SW}$




- The control loop bandwidth can be extended beyond  $F_{SW}$  with multi-interleaving phase operation.

[Y. Lu, ISSCC, 2015]  
[Y. Lu, JSSC, 2017]

\*SCPC: Switched-Capacitor Power Converter


# Non-Ideal Effects of the Fully-Integrated SC

---

 

- Parasitic loss
  - Parasitic capacitor of the on-chip capacitors is about 5% of the main capacitor.
  - High density capacitor helps.
  - Topology dependent.


# Parasitic Insensitive Topology

 


[J. Jiang, ISSCC, 2015]

CAP	Sum $\Phi_1$	Sum $\Phi_2$	Voltage Swing	Sub $\Phi_1$	Sub $\Phi_2$	Voltage Swing
$C_{p1(+)}$	$V_{IN}$	$1/3V_{IN}$	$2/3V_{IN}$	$1/3V_{IN}$	$2/3V_{IN}$	$1/3V_{IN}$
$C_{p1(-)}$	$2/3V_{IN}$	GND	$2/3V_{IN}$	GND	$1/3V_{IN}$	$1/3V_{IN}$
$C_{p2(+)}$	$2/3V_{IN}$	$1/3V_{IN}$	$1/3V_{IN}$	$V_{IN}$	$2/3V_{IN}$	$1/3V_{IN}$
$C_{p2(-)}$	$1/3V_{IN}$	GND	$1/3V_{IN}$	$1/3V_{IN}$	GND	$1/3V_{IN}$

# Parasitic Insensitive Topology

 


[J. Jiang, ISSCC, 2015]

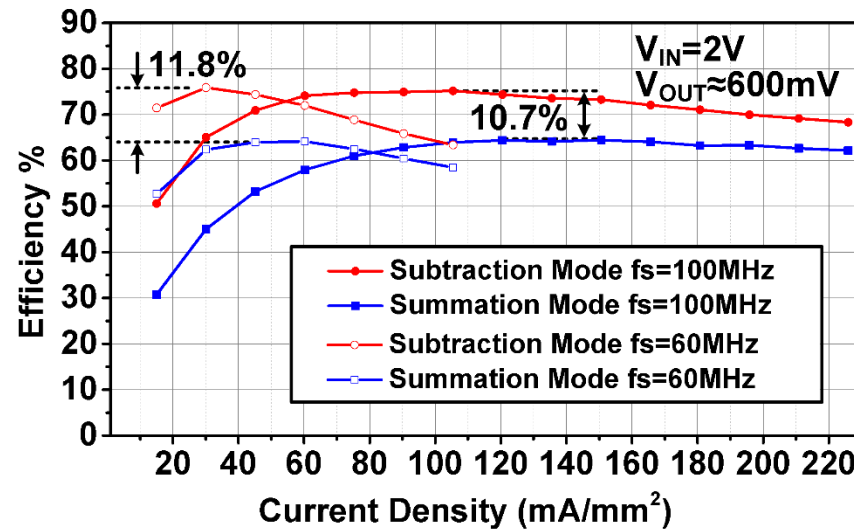

 
# Subtraction-Mode SC

- Modified series-parallel topology.
- Subtraction-mode SC converters with parasitic loss reduction.
- Different capacitor voltages on each  $C_{FLY}$ .



[J. Jiang, TPEL, 2020]

# Parasitic Reduction Techniques (1/3)

 


- Use a large resistor R1 to bias the N-well, making the N-well “floating”.
- Then, parasitic cap is dominated by  $C_w$  ( $\ll C_c$ ).


[H.-P. Le, ISSCC 2013]

# Parasitic Reduction Techniques (2/3)

## P-type MOS Capacitor

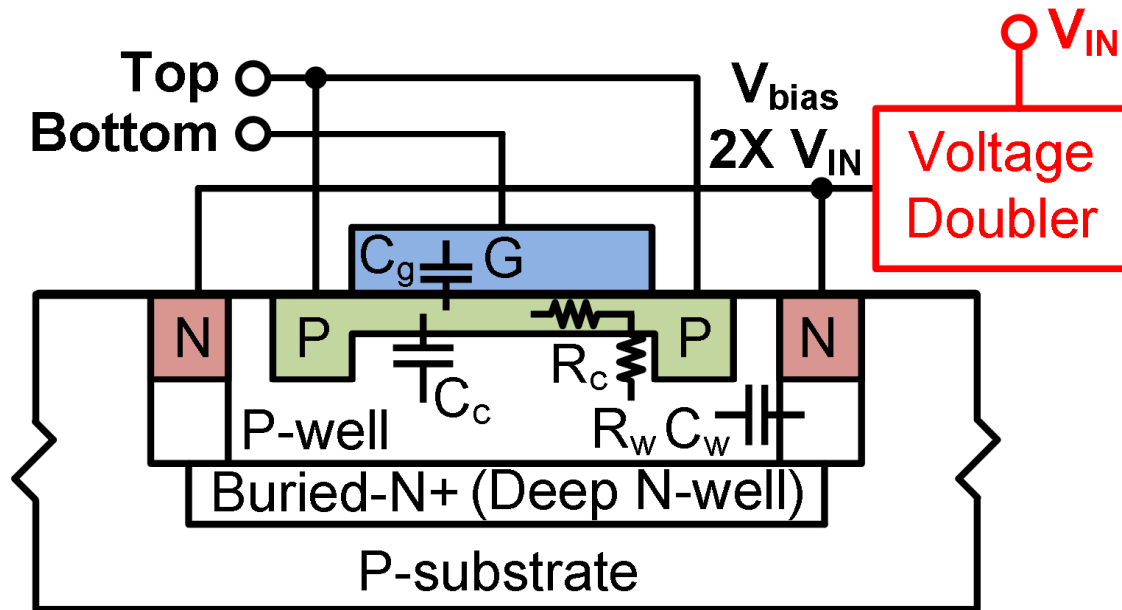

## Equivalent Circuit

 


- $C_w$ : Reduced by on-chip voltage doubler.

[J. Jiang, ISSCC, 2015]



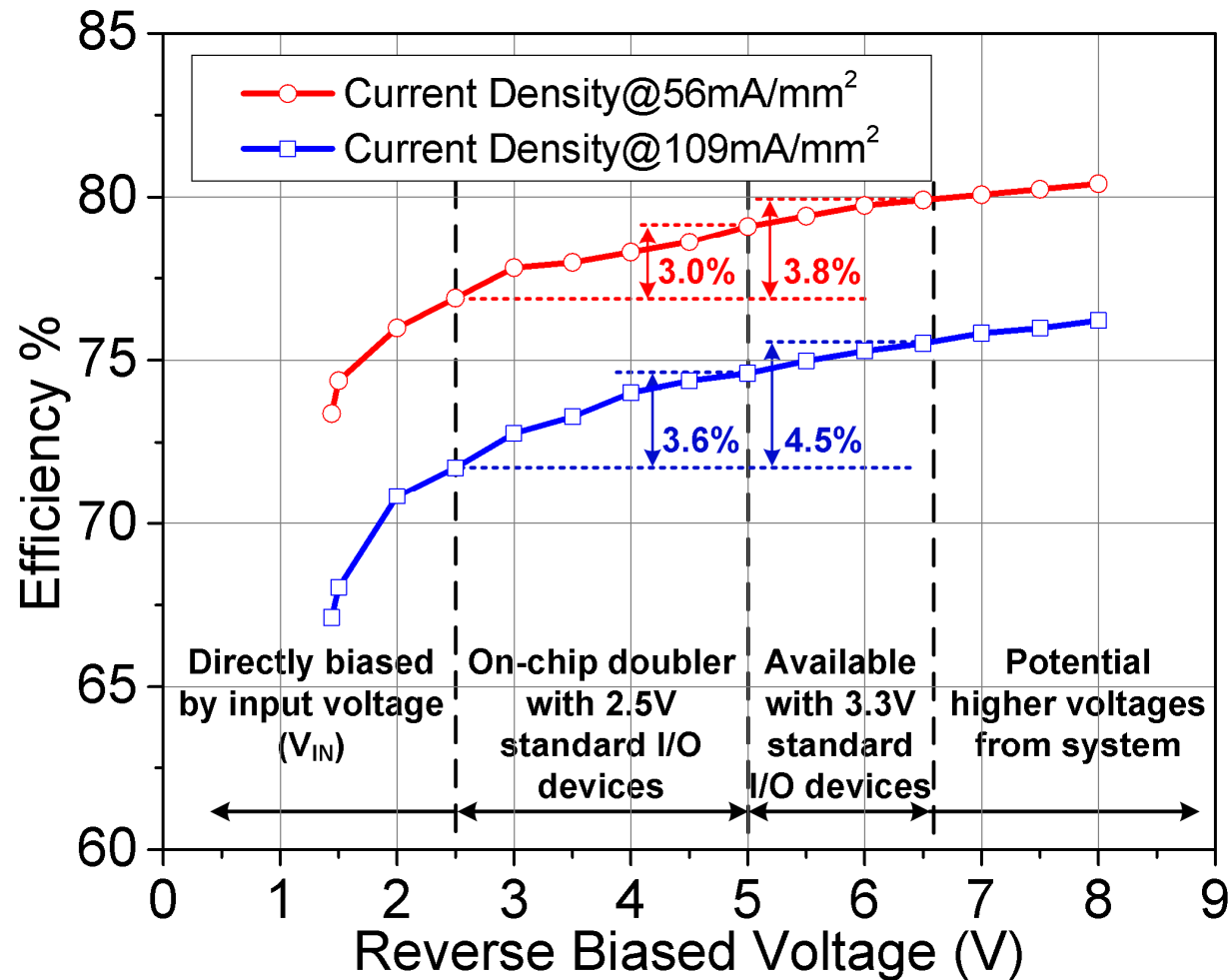
# Efficiency Improvements with Reverse Bias Voltage



- >3% efficiency improvement for reverse bias voltage changes from 2.5V to 5V.
- Another >3% improvement for voltage changes from 5V to 6.6V.

[J. Jiang, ISSCC, 2015]

# Parasitic Reduction Techniques (3/3)

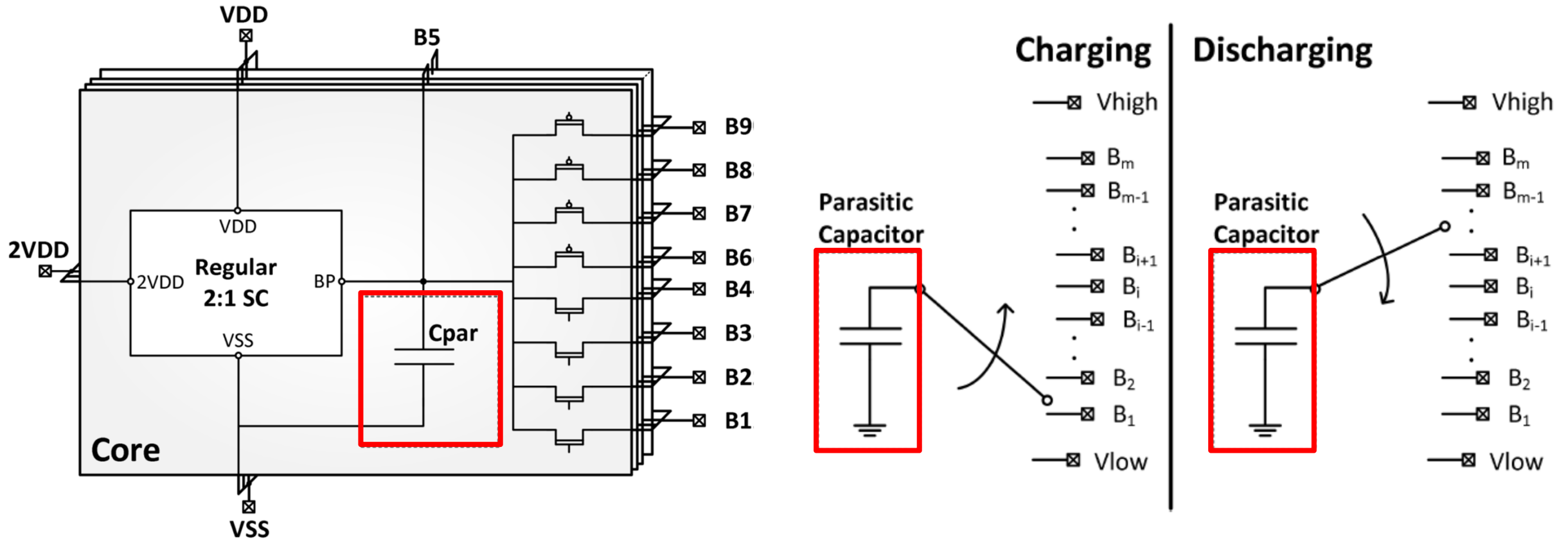

□ Recycle parasitic charge between multiple phases.


[N. Butzen, JSSC 2017]

# Fully-Integrated SC Converter Considerations

---

- For efficiency
  - More VCR means high efficiencies across a wide input/output range.
  - Choose parasitic-insensitive conversion topologies.
  - Use parasitic reduction circuit techniques.
  
- For output accuracy and efficiency
  - Pulse-frequency modulation (PFM)
  - Adaptive switch size for optimum efficiency and smaller ripple.
  - Tuning the gate-drive voltage of the switches

# Multi-Level Hybrid DC-DC Converter

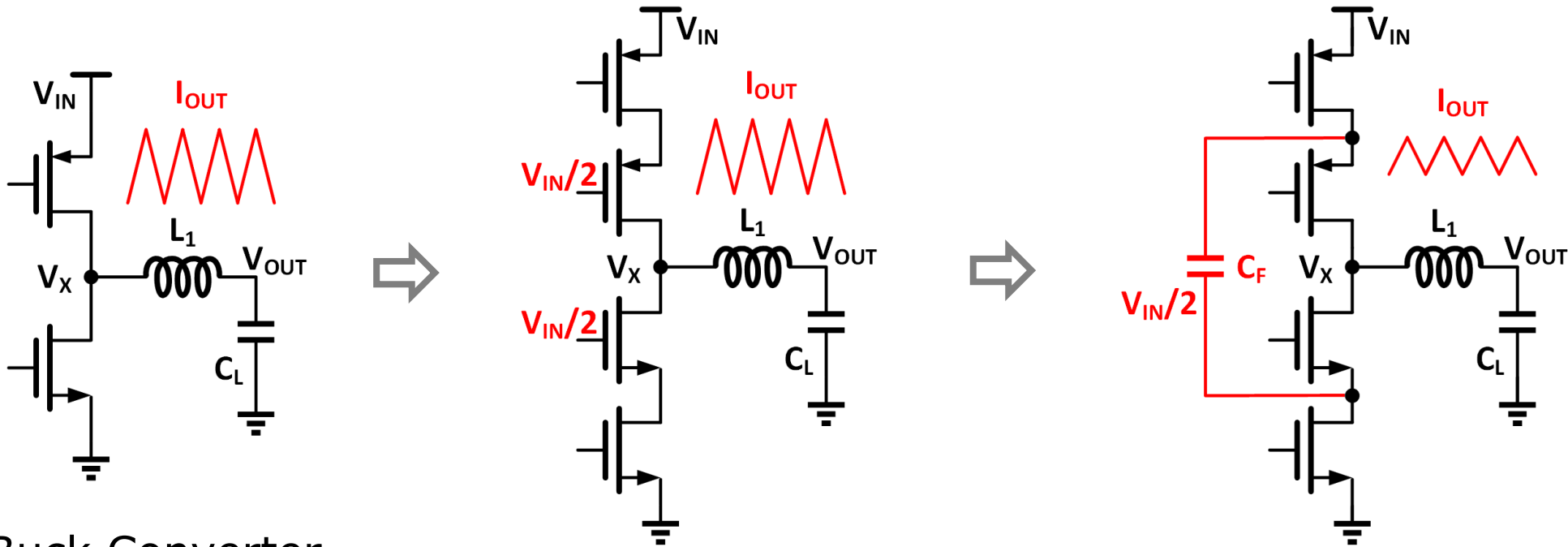

□ Buck Converter

□ Buck with Stacked Switches


□ Use low-voltage devices for less switching losses

□ 3-Level Buck


□ Smaller voltage swing on  $V_X$

□ Smaller  $\Delta I_L$

# Integrated Inductors

 

Cross-sectional View

 


Bottom View



Top View

- On-chip magnetic inductor
- 1.5nH,  $Q \approx 3.8$  @100MHz

[H. K. Krishnamurthy, ISSCC 2017]

 


  - In-package air-core inductor
  - 2.5nH,  $Q \approx 7.8$  @70MHz
- [C. Schaef, ISSCC 2019]




- On-chip coupled LC resonator
  - 7.7nH @47.5MHz
- [P. H. McLaughlin, ISSCC 2020]

# Distributed FIVR

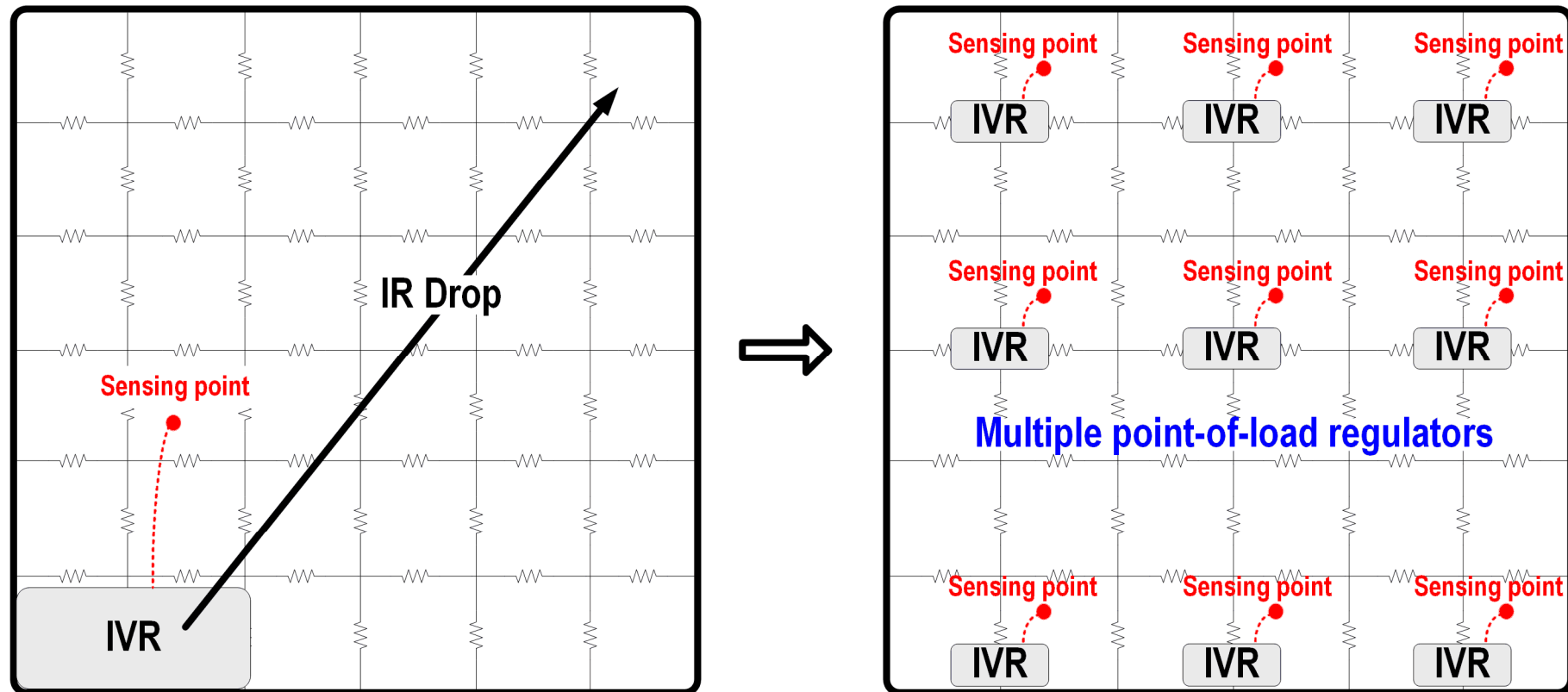


- ❑ Reducing the IR drop across a large area chip ( $>1\text{mm}$ ).
- ❑ Improving the droop during transient response.


# Distributed FIVR Examples

 

 - Global + Distributed local
  - Switching linear regulator
- [M. E. Perez, CICC, 2019]



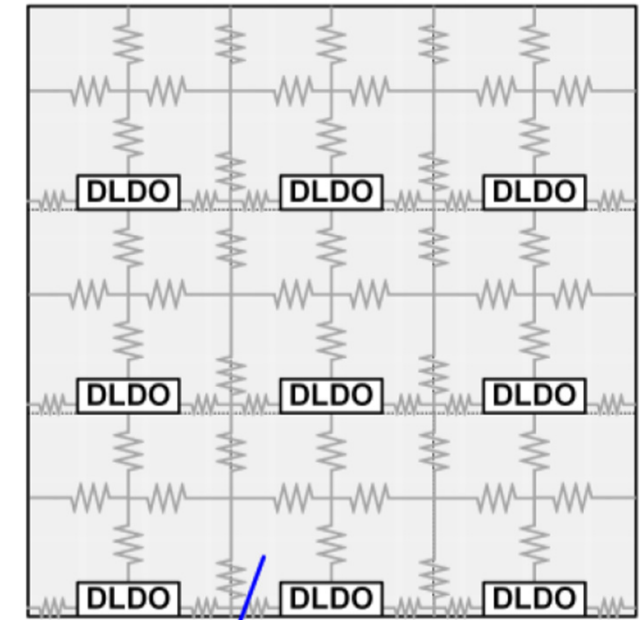- Neighboring cooperation
  - Analog-assisted DLDO
- [Y. Lu, ISSCC, 2018]



Single Supply Voltage in Shared Power Grid

- Each works independently
  - Synthesizable DLDO
- [S. Bang, ISSCC, 2020]

# Outline

---

- Introduction
- Basic Power Stage Selections
  - Linear Low-Dropout (LDO) Regulator
  - Switched-Capacitor Converter
  - Switched-Inductor Converter
- Control Loop Designs
  - PID Control
  - Hysteretic Control
- Advanced Topologies and Techniques
  - Resonant Switched-Capacitor Operation
  - Multiple Interleaving Phase
  - Switched-Capacitor-Inductor Hybrid Topologies
  - Distributed Integrated Voltage Regulators
- Summary





# Summary

---

- For power stage selection between LDO, SC, and Buck converters, and their control strategies.
  - LDO and SC converter have a single pole power stage.
  - Buck converter in CCM has a complex pole-pair, needs two zeros (PID, Type-III) to cancel out the pole-pair, extending the bandwidth beyond the LC  $F_{RES}$ .
  - Buck converter in DCM, or with current-mode control, can ignore the pole associated with the power inductor, being like a single pole power stage.
  - Hysteretic control is extremely fast, but has a varying  $F_{SW}$ .
  - Multiple-interleaving-phase power stage helps to extend the loop bandwidth.
- For full integration:
  - LDO is fast, tiny, and hot.
  - SC converter is friendly to process scaling, suffers from parasitic losses.
  - Inductor-based DC-DC needs a good inductor (a luxury for FIVR).
  - Switched-capacitor-inductor hybrid topologies alleviate the burden on inductor.
  - System-in-package solutions provide high Q passives.

# Knowledge Required for PMIC

---

- Analog IC
- Digital IC
- Power Electronics
- Power Device
- Magnetics/Electromagnetics
- Control theory
  
- A multi-disciplinary area.**

# Papers to See This Year

---

- **Session 17 “DC-DC Converters”** Relevant Papers:
- **17.1** A Two-Stage Cascaded Hybrid Switched Capacitor DC-DC Converter With 96.9% Peak Efficiency Tolerating 0.6V/ $\mu$ s Input Slew Rate during Startup
- **17.3** A 1.25GHz Fully Integrated DC-DC Converter Using Electromagnetically Coupled Class-D LC Oscillators
- **17.4** Peak-Current-Controlled Ganged Integrated High-Frequency Buck Voltage Regulators in 22nm CMOS for Robust Cross-Tile Current Sharing
- **17.5** A 98.2%-Efficiency Reciprocal Direct Charge Recycling Inductor-First DC-DC Converter

# References (1/3)

---

- W. Kim, M. S. Gupta, G. Wei, and D. Brooks, "System level analysis of fast, per-core DVFS using on-chip switching regulators," in *IEEE 14th International Symposium on High Performance Computer Architecture*, Feb. 2008, pp. 123–134.
- W. Kim, D. Brooks, and G.-Y. Wei, "A Fully-Integrated 3-Level DC-DC Converter for Nanosecond-Scale DVFS," *IEEE J. Solid-State Circuits*, vol. 47, no. 1, pp. 206–219, Jan. 2012.
- Y. Lu, W.-H. Ki, and C. Patrick Yue, "An NMOS-LDO Regulated Switched-Capacitor DC-DC Converter With Fast-Response Adaptive-Phase Digital Control," *IEEE Trans. Power Electron.*, vol. 31, no. 2, pp. 1294–1303, Feb. 2016.
- W.-H. Ki, F. Su, and C. Tsui, "Charge redistribution loss consideration in optimal charge pump design," in *IEEE International Symposium on Circuits and Systems (ISCAS)*, May 2005, pp. 1895–1898 Vol. 2.
- M. D. Seeman and S. R. Sanders, "Analysis and Optimization of Switched-Capacitor DC #x2013;DC Converters," *IEEE Trans. Power Electron.*, vol. 23, no. 2, pp. 841–851, Mar. 2008.
- Y. Lu, M. Huang, R. P. Martins, "PID Control Considerations for Analog-Digital Hybrid Low-Dropout Regulators (Invited Paper)," in *Proc. IEEE EDSSC*, Jun. 2019.
- M. Al-Shyoukh, H. Lee, and R. Perez, "A Transient-Enhanced Low-Quiescent Current Low-Dropout Regulator With Buffer Impedance Attenuation," *IEEE J. Solid-State Circuits*, vol. 42, no. 8, pp. 1732–1742, Aug. 2007.
- M. Ho, K. N. Leung, and K.-L. Mak, "A low-power fast-transient 90-nm low-dropout regulator with multiple small-gain stages," *IEEE J. Solid-State Circuits*, vol. 45, no. 11, pp. 2466–2475, Nov. 2010.
- Y. Lu et al., "A Fully-Integrated Low-Dropout Regulator With Full-Spectrum Power Supply Rejection," *IEEE Trans. Circuits Syst. I, Reg. Papers*, vol. 62, no. 3, pp. 707–716, Mar. 2015.
- R. J. Milliken, J. Silva-Martinez, and E. Sanchez-Sinencio, "Full On-Chip CMOS Low-Dropout Voltage Regulator," *IEEE Trans. Circuits Syst. I, Reg. Papers*, vol. 54, no. 9, pp. 1879–1890, Sep. 2007.
- Y. Okuma et al., "0.5-V input digital LDO with 98.7% current efficiency and 2.7- $\mu$ A quiescent current in 65nm CMOS," in *Proc. IEEE CICC*, Sep. 2010, pp. 1–4.
- Y. J. Lee et al., "A 200-mA digital low drop-out regulator with coarse-fine dual loop in mobile application processor," *IEEE J. Solid-State Circuits*, vol. 52, no. 1, pp. 64–76, Jan. 2017.

# References (2/3)

---

- D. Kim and M. Seok, "A fully integrated digital low-dropout regulator based on event-driven explicit time-coding architecture," *IEEE J. Solid-State Circuits*, vol. 52, no. 11, pp. 3071–3080, Nov. 2017.
- S. J. Kim et al., "A 67.1-ps FOM, 0.5-V-hybrid digital LDO with asynchronous feedforward control via slope detection and synchronous PI with state-based hysteresis clock switching," *IEEE Solid-State Circuits Lett.*, vol. 1, no. 5, pp. 130–133, May 2018.
- S. B. Nasir, S. Sen, and A. Raychowdhury, "Switched-mode-control based hybrid LDO for fine-grain power management of digital load circuits," *IEEE J. Solid-State Circuits*, vol. 53, pp. 569–581, Feb. 2018.
- M. Huang, Y. Lu, S. U, and R. P. Martins, "An analog-assisted tri-loop digital low-dropout regulator," *IEEE J. Solid-State Circuits*, vol. 53, no. 1, pp. 20–34, Jan. 2018.
- X. Ma, Y. Lu, R. P. Martins, and Q. Li, "A 0.4V 430nA quiescent current NMOS digital LDO with NAND-based analog-assisted loop in 28nm CMOS," in *IEEE ISSCC Dig. Tech. Papers*, Feb. 2018, pp.306–308.
- F. Su, W. Ki, and C. Tsui, "Ultra Fast Fixed-Frequency Hysteretic Buck Converter With Maximum Charging Current Control and Adaptive Delay Compensation for DVS Applications," *IEEE Journal of Solid-State Circuits*, vol. 43, no. 4, pp. 815–822, Apr. 2008.
- K. Kesarwani, R. Sangwan, and J. T. Stauth, "A 2-phase resonant switched-capacitor converter delivering 4.3W at 0.6W/mm<sup>2</sup> with 85% efficiency," in *IEEE ISSCC Dig. Tech. Papers*, Feb. 2014, pp. 86–87.
- C. Schaef, J. Rentmeister, and J. T. Stauth, "Multimode Operation of Resonant and Hybrid Switched-Capacitor Topologies," *IEEE Trans. Power Electron.*, vol. 33, no. 12, pp. 10512–10523, Dec. 2018.
- P. Renz, M. Kaufmann, M. Lueders, and B. Wicht, "A Fully Integrated 85%-Peak-Efficiency Hybrid Multi Ratio Resonant DC-DC Converter with 3.0-to-4.5V Input and 500 $\mu$ A -to-120mA Load Range," in *IEEE ISSCC Dig. Tech. Papers*, Feb. 2019, pp. 156–158.
- Y. Lu, J. Jiang, and W. H. Ki, "A Multiphase Switched-Capacitor DC-DC Converter Ring With Fast Transient Response and Small Ripple," *IEEE J. Solid-State Circuits*, vol. 52, no. 2, pp. 579–591, Feb. 2017.
- Y. Lu, J. Jiang, and W.-H. Ki, "Design Considerations of Distributed and Centralized Switched-Capacitor Converters for Power Supply On-Chip," *IEEE Journal of Emerging and Selected Topics in Power Electronics*, vol. 6, no. 2, pp. 515–525, Jun. 2018.
- J. Jiang, Y. Lu, C. Huang, W.-H. Ki, and P. K. T. Mok, "A 2-/3-phase fully integrated switched-capacitor DC-DC converter in bulk CMOS for energy-efficient digital circuits with 14% efficiency improvement," in *IEEE ISSCC Dig. Tech. Papers*, Feb. 2015, pp. 1–3.

# References (3/3)

---

- J. Jiang et al., "A dual-symmetrical-output switched-capacitor converter with dynamic power cells and minimized cross regulation for application processors in 28nm CMOS," in *IEEE ISSCC Dig. Tech. Papers*, Feb. 2017, pp. 344–345.
- J. Jiang, W.-H. Ki, and Y. Lu, "Digital 2-/3-Phase Switched-Capacitor Converter With Ripple Reduction and Efficiency Improvement," *IEEE J. Solid-State Circuits*, vol. 52, no. 7, pp. 1836–1848, Jul. 2017.
- J. Jiang, X. Liu, C. Huang, W.-H. Ki, P. K. T. Mok, and Y. Lu, "Subtraction-Mode Switched-Capacitor Converters With Parasitic Loss Reduction," *IEEE Trans. Power Electron.*, vol. 35, no. 2, pp. 1200–1204, Feb. 2020.
- H.-P. Le, J. Crossley, S. R. Sanders, and E. Alon, "A sub-ns response fully integrated battery-connected switched-capacitor voltage regulator delivering 0.19W/mm<sup>2</sup> at 73% efficiency," in *IEEE ISSCC Dig. Tech. Papers*, Feb. 2013, pp. 372–373.
- N. Butzen and M. S. J. Steyaert, "Design of Soft-Charging Switched-Capacitor DC-DC Converters Using Stage Outphasing and Multiphase Soft-Charging," *IEEE J. Solid-State Circuits*, vol. 52, no. 12, pp. 3132–3141, Dec. 2017.
- N. Butzen and M. S. J. Steyaert, "MIMO Switched-Capacitor DC-DC Converters Using Only Parasitic Capacitances Through Scalable Parasitic Charge Redistribution," *IEEE J. Solid-State Circuits*, vol. 52, no. 7, pp. 1814–1824, Jul. 2017.
- H. K. Krishnamurthy et al., "A digitally controlled fully integrated voltage regulator with on-die solenoid inductor with planar magnetic core in 14nm tri-gate CMOS," in *IEEE ISSCC Dig. Tech. Papers*, Feb. 2017, pp. 336–337.
- C. Schaefer et al., "A Light-Load Efficient Fully Integrated Voltage Regulator in 14-nm CMOS With 2.5-nH Package-Embedded Air-Core Inductors," *IEEE J. Solid-State Circuits*, vol. 54, no. 12, pp. 3316–3325, Dec. 2019.
- P. H. McLaughlin, Z. Xia, and J. T. Stauth, "A Fully Integrated Resonant Switched-Capacitor Converter with 85.5% Efficiency at 0.47W Using On-Chip Dual-Phase Merged-LC Resonator," in *IEEE ISSCC Dig. Tech. Papers*, Feb. 2020, pp. 192–194.
- M. E. Perez et al., "Distributed Network of LDO Microregulators Providing Submicrosecond DVFS and IR Drop Compensation for a 24-Core Microprocessor in 14-nm SOI CMOS," *IEEE J. Solid-State Circuits*, vol. 55, no. 3, pp. 731–743, Mar. 2020.
- Y. Lu, F. Yang, F. Chen, and P. K. T. Mok, "A 500mA analog-assisted digital-LDO-based on-chip distributed power delivery grid with cooperative regulation and IR-drop reduction in 65nm CMOS," in *IEEE ISSCC Dig. Tech. Papers*, Feb. 2018, pp. 310–312.
- S. Bang et al., "A Fully Synthesizable Distributed and Scalable All-Digital LDO in 10nm CMOS," in *IEEE ISSCC Dig. Tech. Papers*, Feb. 2020, pp. 380–382.

# Acknowledgements

---

- I would like to thank my (Current and Previous) Colleagues for their significant contributions to this tutorial.
  - Mo Huang, Junmin Jiang, Xiaofei Ma, Chuang Wang, Xiangyu Mao, Lin Cheng, Wing-Hung Ki, Patrick Yue, and Rui Martins.
- And also thank the Tutorial Chair Ali Sheikholeslami (U. of Toronto) and Coordinator Harish Krishnamurthy (Intel) for their inputs and suggestions.
- Funding supports:



澳門大學  
UNIVERSIDADE DE MACAU  
UNIVERSITY OF MACAU



---

# THANK YOU FOR YOUR ATTENTION.

Questions?

**Live Q&A Session:**

**Feb. 13, 2021, 8:00-8:20 am, PST**

Email: [yanlu@um.edu.mo](mailto:yanlu@um.edu.mo)

