

---

# T3: Fundamentals of Data Converters

Yun Chiu

(chiu.yun@utdallas.edu)

University of Texas at Dallas  
Richardson, TX

Feb 19, 2023

# Outline

---


- Quantization and Sampling
- Overview of Data Converter Architectures
- How To Measure Data Converter Performance?
- Nyquist-Rate ADC and DAC Architectures
- Circuit Building Blocks
- Redundancy
- Digital Correctability and Calibration
- ADC Figure-of-Merits
- Data Converter Papers to See This Year
- References

# Data Conversion


CT, CA




*Analog World*

 

 → → → Digitizing → → →  
← ← ← Analogizing ← ← ←



DT, DA

 

Digital World


□ Data converters bridge analog (physical) world and digital (virtual) world

# Data Conversion


CT, CA




*Analog World*

 

DT, DA

 

Digital World

 


□ Three key functions involved: **Filtering, Sampling, Quantization**

---


# QUANTIZATION

# A Mathematical View

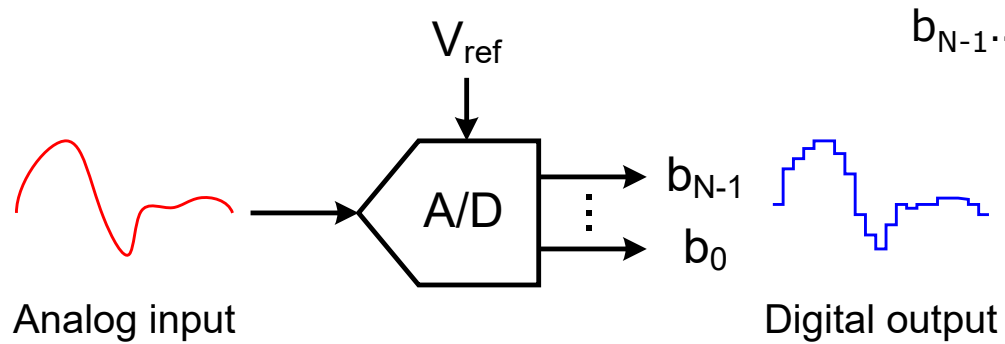

$$D_{\text{out}} = \left\lfloor \frac{V_{\text{in}}}{V_{\text{FS}}} 2^N \right\rfloor = \left\lfloor \frac{V_{\text{in}}}{\Delta} \right\rfloor$$

**Division**

 




$$V_{\text{out}} = \sum_{i=0}^{N-1} b_i \cdot 2^i \left( \frac{V_{\text{FS}}}{2^N} \right) = \sum_{i=0}^{N-1} b_i \Delta 2^i$$

**Multiplication**

- $N = \#$  of bits,  $V_{\text{FS}} =$  Full-Scale range,  $\Delta = V_{\text{FS}}/2^N = 1 \text{ LSB}$ ,  $b_i = \{0, 1\}$
- Full-Scale range ( $V_{\text{FS}}$ ) is set by reference voltage  $V_{\text{ref}}$



# Quantization Error

 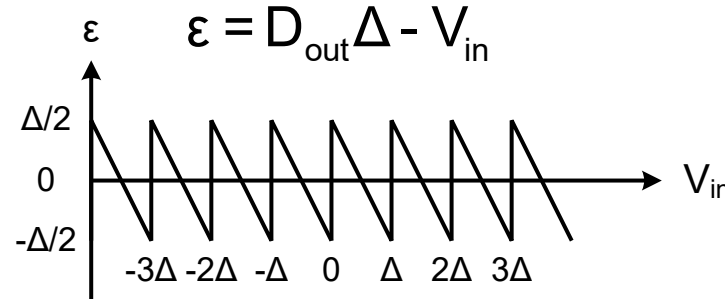 

## Assumptions:

- N is large ( $\Delta$  is small)
- $V_{\text{in}} \gg \Delta$  and is active
- $\varepsilon$  is uniformly distributed
- Spectrum of  $\varepsilon$  is white

$$\sigma_{\varepsilon}^2 = \int_{-\Delta/2}^{\Delta/2} \varepsilon^2 \cdot \frac{1}{\Delta} \cdot d\varepsilon = \frac{\Delta^2}{12}$$

Ref. [1]

- "Random" **quantization error** is usually regarded as **quantization noise**

# Signal-to-Quantization Noise Ratio (SQNR)

- For sinusoidal input with  $V_{pp} = V_{FS}$

$$\text{SQNR} = \frac{V_{FS}^2 / 8}{\sigma_{\epsilon}^2} = \frac{(2^N \Delta)^2 / 8}{\frac{\Delta^2}{12}} = 1.5 \times 2^{2N}$$

$$\text{SQNR} = 6.02 \times N + 1.76 \text{ [dB]}$$

N (bits)	SQNR (dB)
8	49.9
10	62.0
12	74.0
14	86.0
...	...

- SQNR depicts the theoretical performance of an ideal converter
- Practical converter performance can be limited by many other factors
  - **Noise**: thermal, 1/f, supply/substrate/coupling, etc.
  - **Distortion**: DC & AC nonlinearities, measured by THD, SFDR, IM3, etc.
  - **Metastability** (ADC): comparator fails to resolve within time limit




---


# SAMPLING

# Sampling (quite some math)


Continuous Time

 

$$\Omega T = \omega$$

 

Discrete Time

 


$$x(t) \xrightarrow{FT} \int_{-\infty}^{\infty} x(t) e^{-j\Omega t} dt = X(j\Omega)$$

$$X(j\omega) = \frac{1}{T} X(j\Omega) \otimes \sum_k \delta(\Omega - k\Omega_s)$$

impulse train

$$x(n) \xrightarrow{ZT} \sum_{n=-\infty}^{\infty} x(n) z^{-n} \Big|_{z=e^{j\omega}} = X(j\omega)$$

 


No aliasing if  $f_{s,min} \geq 2f_N \rightarrow$  Nyquist-rate sampling

---

# **OVERVIEW OF DATA CONVERTER ARCHITECTURES**

# Overview of ADC Architectures

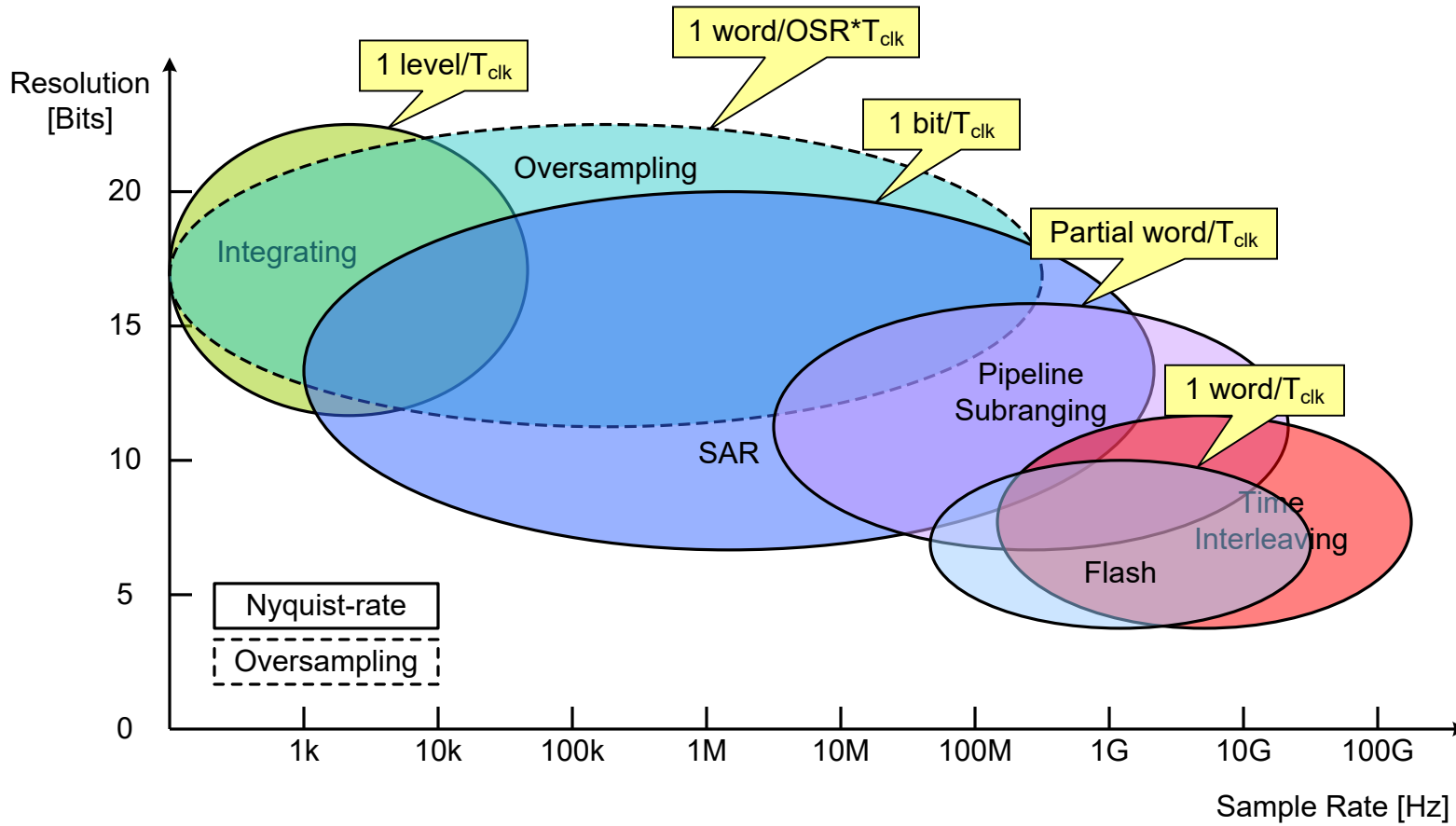

Per-step resolving (Conv. time)

- N bits† (1 step) ← fast
  - **Flash**
  - Folding
- 1 level (2<sup>N</sup> steps) ← slowest
  - Integration (Serial)
- 1 bit (N steps) ← slow
  - **SAR**
  - Algorithmic (Cyclic)
- M bits (N/M steps) ← medium
  - **Pipeline**
  - Subranging
- Others
  - Time interleaving  
→ high-speed ADC array
  - Oversampling + NS  
→ ΔΣ modulator

**SAR, ΔΣM, TI ADC array are popular lately!**

# Overview of DAC Architectures

- Nyquist-rate DACs (oversampling DACs skipped in this tutorial):

Technology \ Topology	Binary-weighted (B.W.)	Unit-element (U.E.)	Segmented (S.M.)
Resistive	R2R	Resistor string	N.C.
Capacitive	Charge redistribution (can support high speed [3])		
I-steering	N.C.	High speed	High speed & high resolution

- Some (fun or not so fun) facts about DACs:
  - Every ADC has a DAC built in!
  - DACs are conceptually straightforward, but tough to design or calibrate at high speed (GS/s+)!

---

# PERFORMANCE MEASUREMENT OF DATA CONVERTERS

# Data Converter Measurements

---





- Static measurement of converter transfer function (TF)
  - Differential Non-Linearity (DNL), Integral Non-Linearity (INL)
  - Code Density Test (CDT)
- Dynamic frequency- / time-domain measurement of signal quality
  - Frequency domain techniques: FFT, SNR, SNDR (SINAD), SFDR, IM3 etc.
  - Time-domain techniques: Sine-fit




---

# DNL AND INL

# DAC Static Nonlinearity

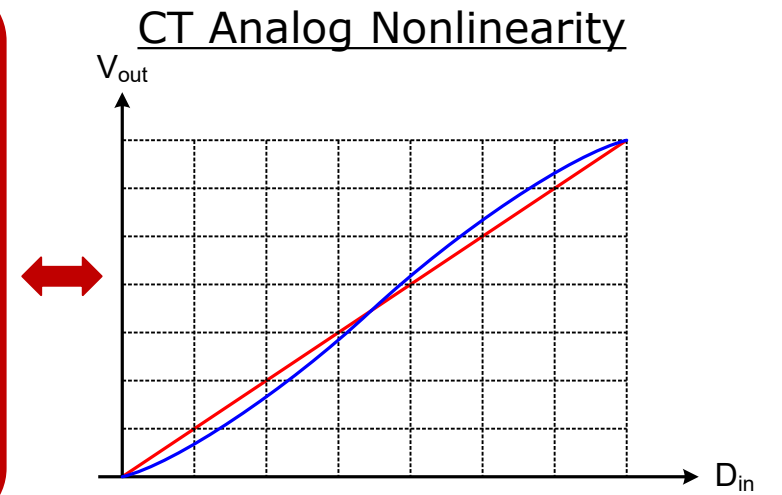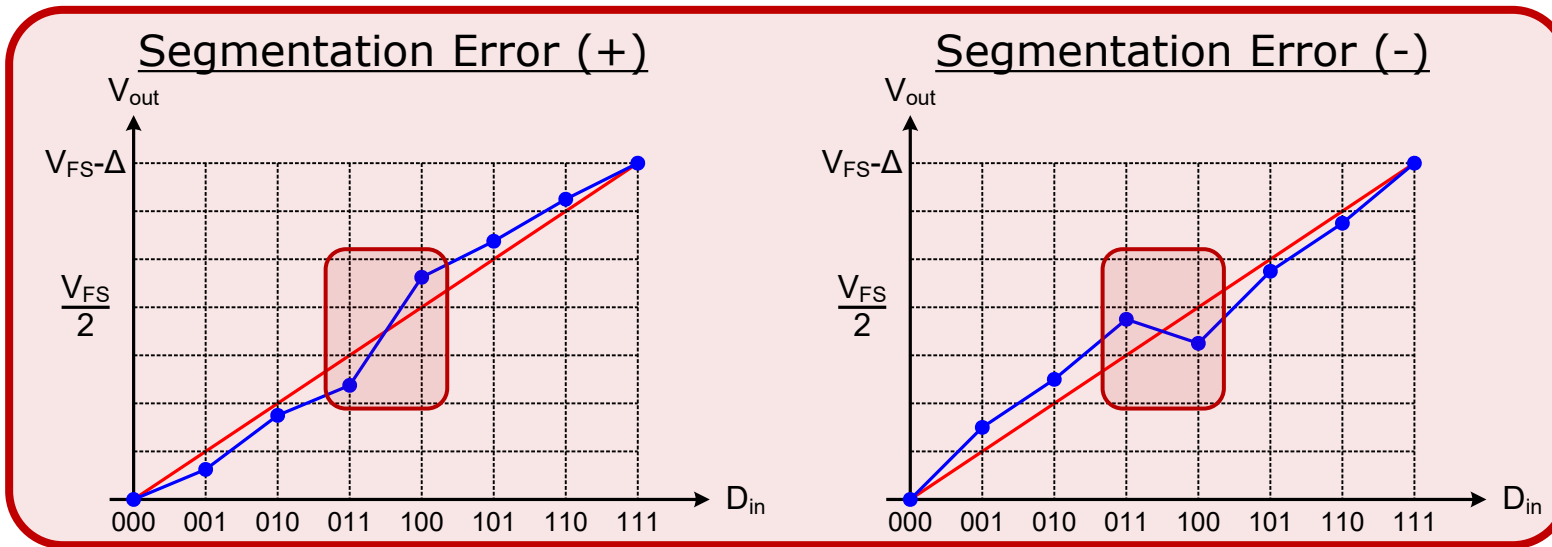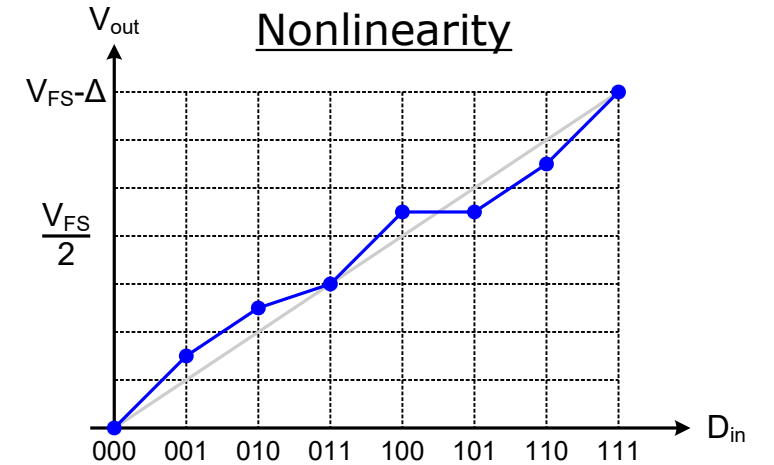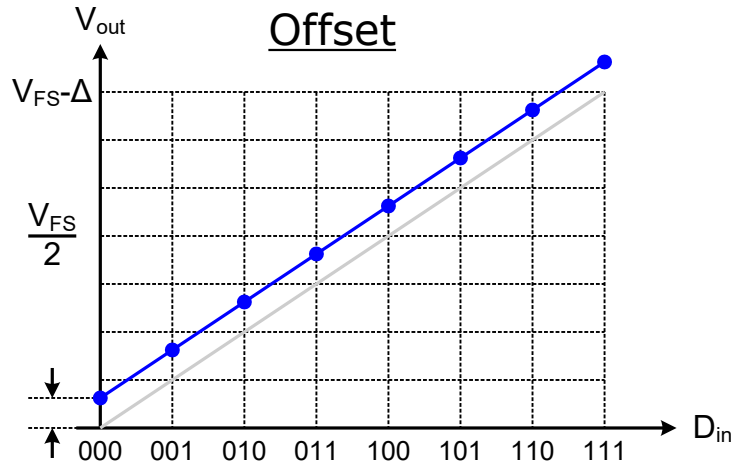


# DNL and INL (DAC)

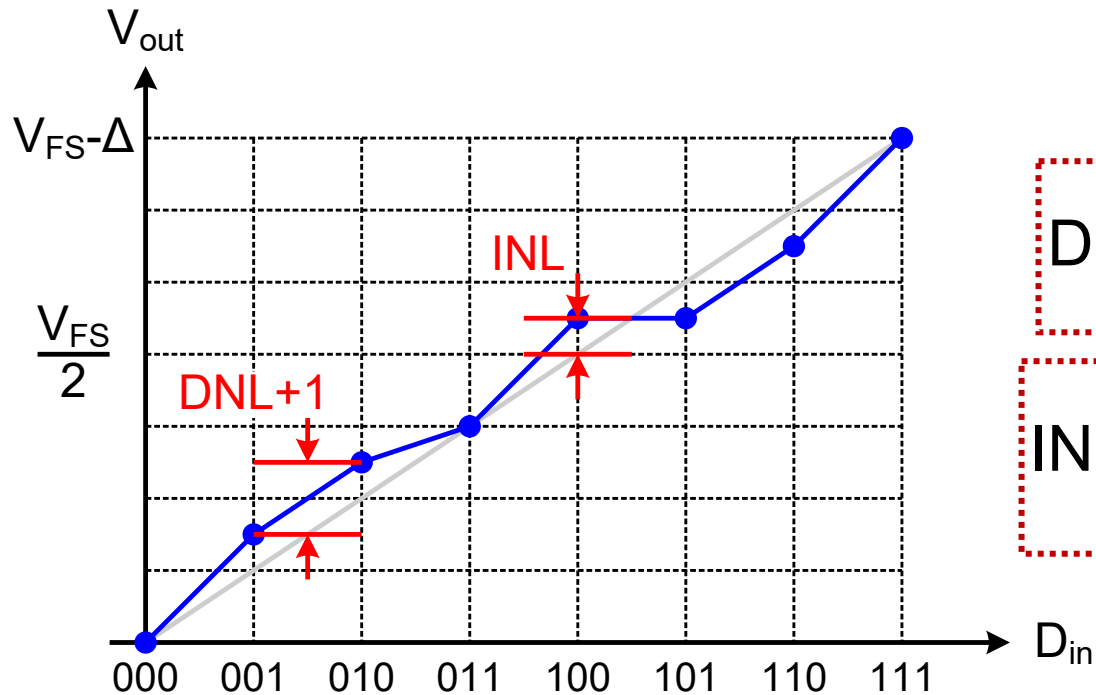


$$DNL_i = \frac{\Delta_i - \Delta}{\Delta}$$

$$INL_i = \sum_{j=0}^i DNL_j$$

 

- DNL: deviation of a conversion step ( $V_j - V_{j-1}$ ) from 1 LSB ( $\Delta$ ) – **Incremental**
- INL: deviation of the output ( $V_j$ ) from ideal transfer curve – **Cumulative**


# A More Realistic Measurement

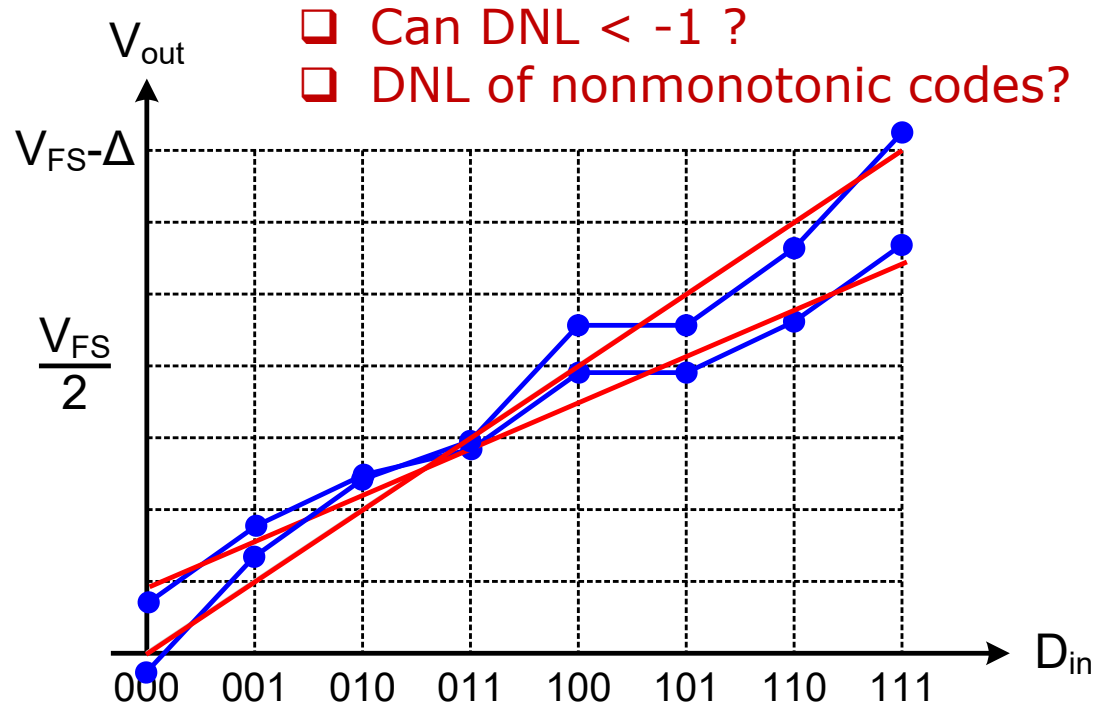

- Measurement procedure:
  - Least-square fit transfer curve
  - Stretch fitted line to ideal position
  - Determine DNL and INL
- MATLAB built-in function "detrend"
  - $\Sigma(\text{INL}) = 0$  – why?


- In practice, endpoints of TF may not end up at 0 and  $V_{FS} - \Delta \rightarrow$   
**Assumption:** Gain error and Offset are of less concern than DNL and INL

# ADC Static Nonlinearity

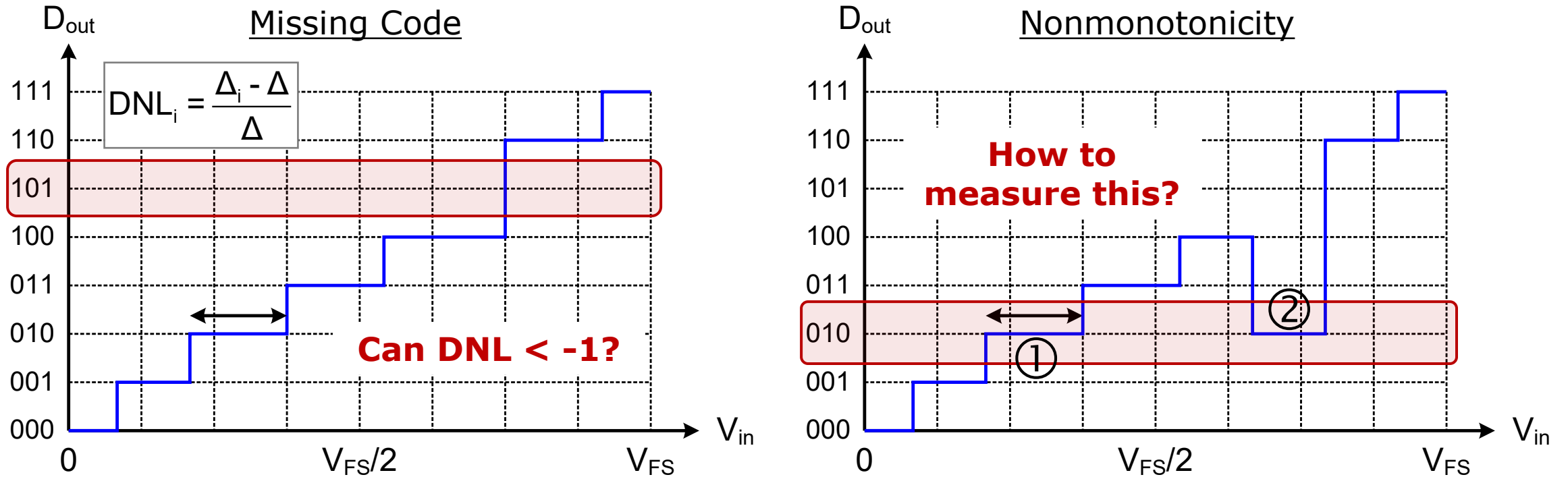


- ❑ ADC static errors also include gain, offset, nonlinearity (DNL and INL), but
- ❑ Watch out for **missing code** and **nonmonotonicity**!

# INL and DNL (ADC)

 


Offset-free  
diff. ADC

 

- Connect midpoints of trends to determine the INL profile (also “detrend”)
- Direct TF measure requires a high-resolution DAC to produce/record the exact input analog values

# Code Density Test

 


- Apply a linear ramp to ADC input and collect the output code histogram
  - Ball-casting problem: # of balls collected proportional to bin size (DNL)
  - Missing codes → DNL = -1
  - Nonmonotonic codes → all lumped together, **very misleading!**
- Linear ramp is difficult to generate in practice → use **filtered sinewave** instead (but needs to correct the **bowl-shaped** density curve) Ref. [4]



---

# FREQUENCY- & TIME-DOMAIN MEASUREMENTS

# Spectrum of Quantized Signal


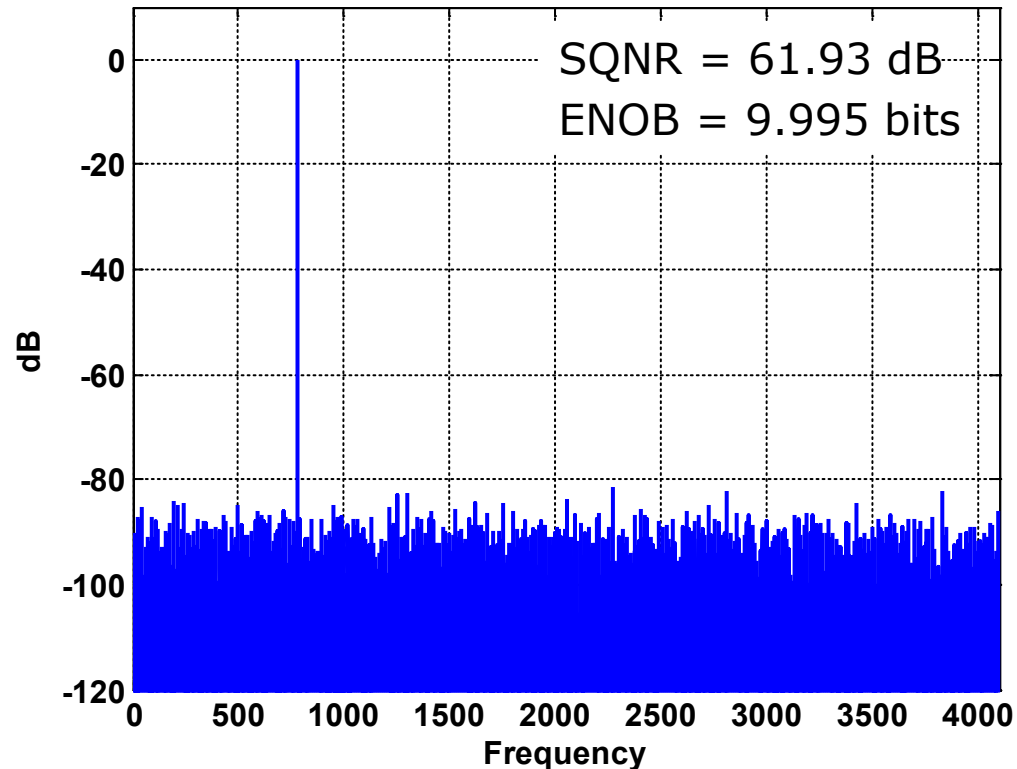


- ❑  $N = 10$  bits
- ❑  $f_s = 8192, f_{in} = 779$
- ❑ 8192 samples, only  $[0, f_s/2]$  shown
- ❑ Normalized to the amplitude of  $V_{in}$
- ❑ Effective # of bits (sinusoidal):

$$\text{ENOB} = \frac{\text{SQNR} - 1.76 \text{ dB}}{6.02 \text{ dB}}$$



- ❑ FFT requires power-of-two number of samples to compute the spectrum
- ❑  $f_{in}$  and  $f_s$  must be incommensurate, e.g.,  $f_{in}$  and  $f_s$  are co-prime

# Commensurate $f_s$ and $f_{in}$

  


- Repeated/periodic samples lead to periodic quantization errors, manifested as **harmonic distortions**

# Spectrum Leakage

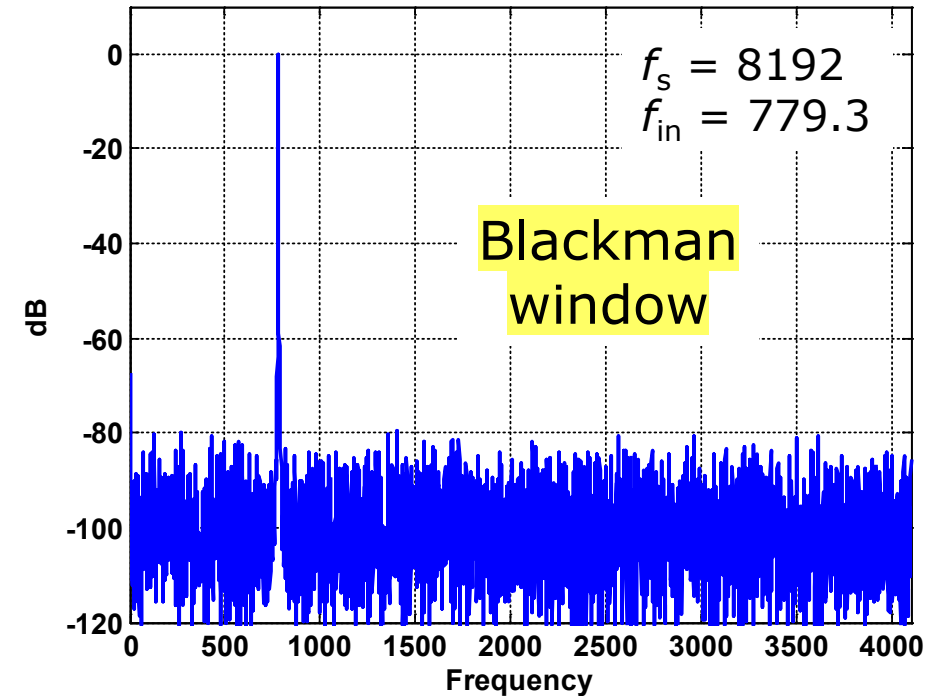 

- Samples must include integer # of cycles of input signal
- Windowing can be applied to eliminate spectrum leakage
  - Tradeoff b/t main-lobe width and sideband rejection of different windows

# Frequency-Domain Performance Eval

 


- ❑ Signal-to-noise plus distortion ratio (**SNDR**)
  - ❑ ALL bins except input are noise + disto
- ❑ Total harmonic distortion (**THD**)
  - ❑ Usually count first 10 HDs
- ❑ Spurious-free dynamic range (**SFDR**)
- ❑ **Effective # of bits** (sinusoidal):


$$\text{ENOB} = \frac{\text{SNDR} - 1.76 \text{ dB}}{6.02 \text{ dB}}$$

- ❑ High-order harmonics are aliased back, visible in band  $[0, f_s/2]$ 
  - E.g., HD3 @  $779 \times 3 + 1 = 2338$ , HD9 @  $8192 - 9 \times 779 + 1 = 1182$
- ❑ Two-tone/IM3 test is useful for  $\Sigma\Delta\text{M}$  and DACs, but uncommon for Nyq. ADCs

# Sine-Fit: A Time-Domain Method

 

 Time domain  $\rightarrow$   
 $\leftarrow$  Freq. domain



- ❑ Windowing, phase noise of signal/clock generator etc. can make frequency-domain SNDR measurement quite difficult
- ❑ If input is a sine wave, directly fit the measured (or simulated) samples to an ideal sine wave can yield accurate SNDR measurement (in MATLAB)
  - Nonlinear least-square fit by optimizing over  $(A, \omega=2\pi/T, \Phi)$


---

# **NYQUIST ADC ARCHITECTURES**

## **FLASH, SAR, AND PIPELINE**




# Flash ADC – Exhaustive Search

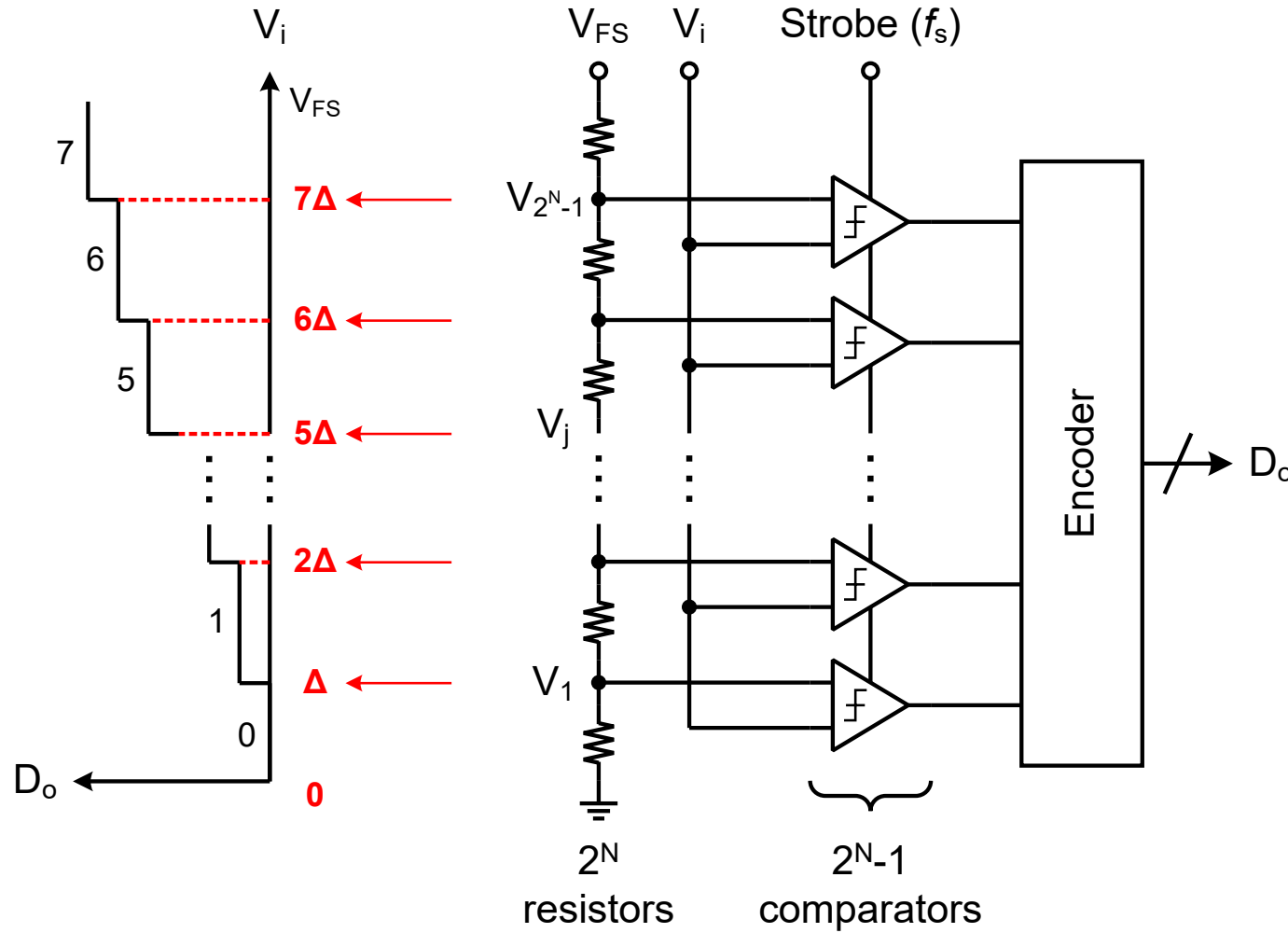


- ❑ Massive parallelism
- ❑ Very fast (N bits/step)
- ❑ Reference ladder:  $2^N$  equal-sized resistors
- ❑ Input compared to  $2^N - 1$  ref. taps ( $V_j$ )
- ❑ Throughput =  $f_s$
- ❑ Complexity  $\sim 2^N$
- ❑ Rarely used for more than 6-8 bits

# Thermometer Code

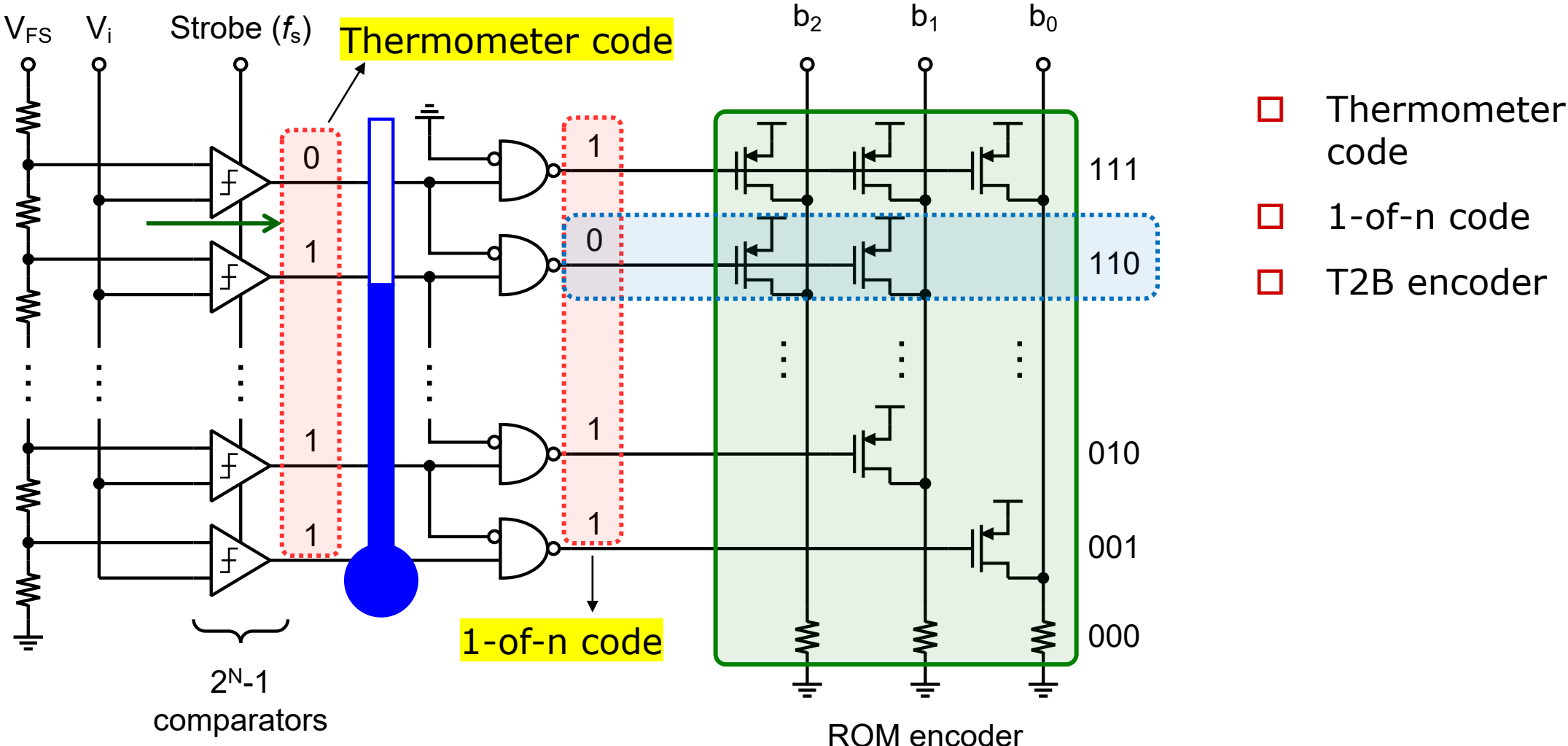

# Bubble / Sparkle Errors

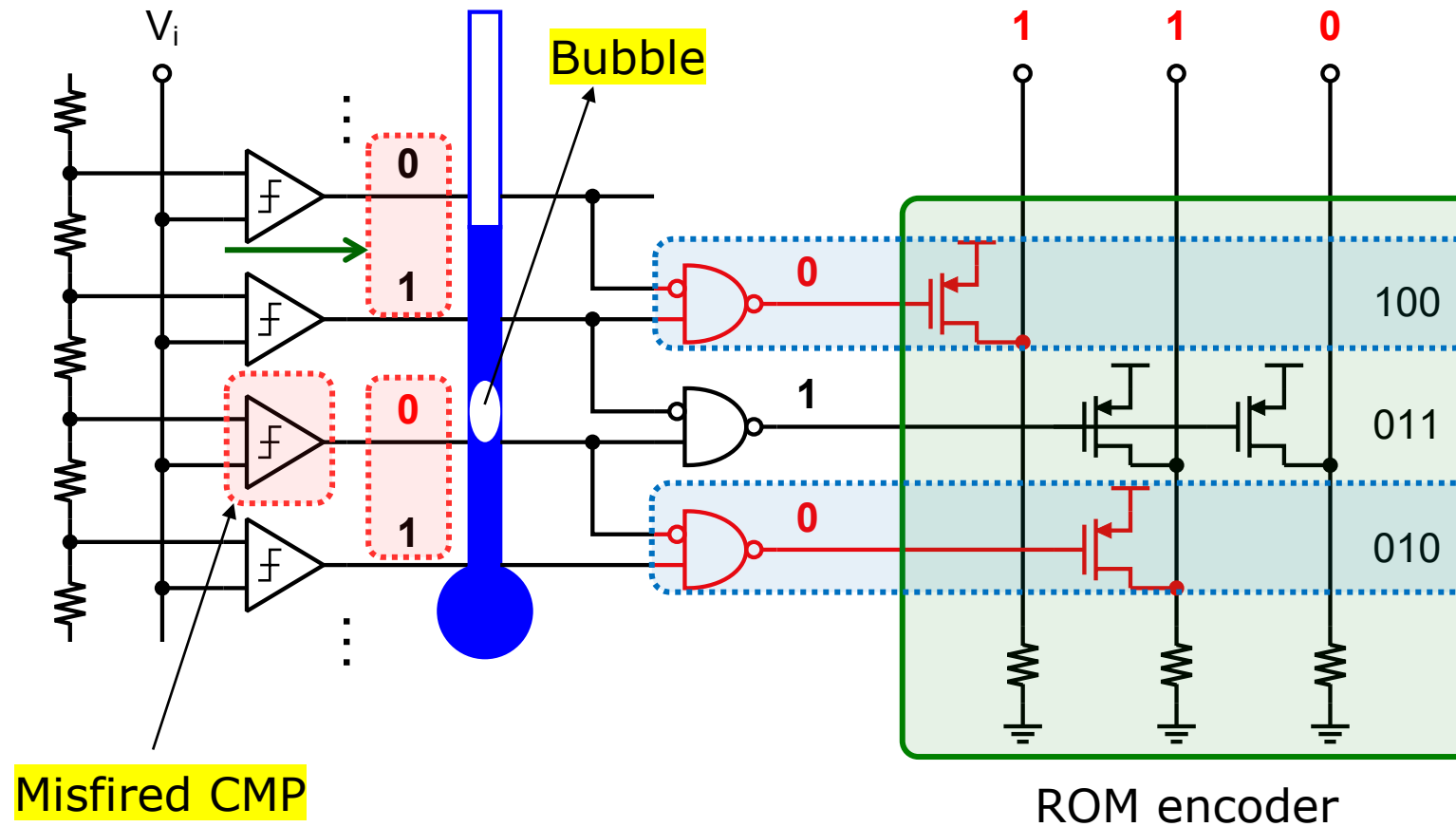

- 3-input boundary det.
- Majority voting
- Gray code

# Quantization – Long Division

$N = 3$   
 $FS = 1000$   
 $\Delta = FS/8$   
 $= 125$   
 $V_{in} = 735$

$$D_o = \left\lfloor \frac{V_{in}}{\Delta} \right\rfloor \quad \underbrace{735}_{V_{in}} \div \underbrace{125}_{LSB} = \underbrace{[1,0,1]_b}_{D_o \text{ (Quotient)}} \quad r \quad \underbrace{110}_{QN \text{ (Remainder)}}$$

$$\begin{array}{r} 1 \\ \hline 500 \overline{) 735} \\ \underline{500} \\ 235 \end{array}$$

Step 1:  
1<sup>st</sup> bit



$$\begin{array}{r} 0 \\ \hline 250 \overline{) 235} \\ \underline{0} \\ 235 \end{array}$$

Step 2:  
2<sup>nd</sup> bit




$$\begin{array}{r} 1 \\ \hline 125 \overline{) 235} \\ \underline{125} \\ 110 \end{array}$$

Step 3:  
3<sup>rd</sup> bit

□ The procedure is also known as **binary (radix=2) search**

# Successive-Approximation (SAR) ADC

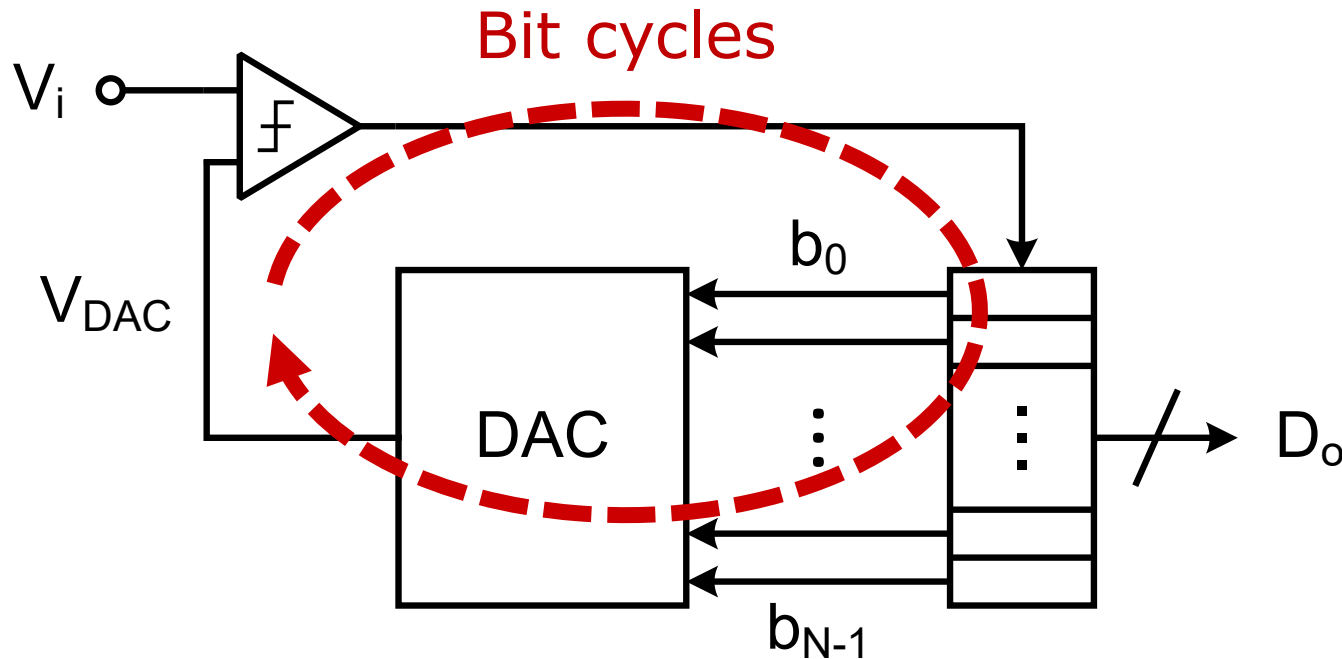


- 1 comparator
- 1 DAC
- Some digital logic

- Serial architecture (1 bit/step) → NOT built for high speed operation
- Hardware reuse / very efficient, minimal architecture

# Binary Search: MSB Cycle

$$N = 3, FS = 1 \text{ V}, \Delta = 0.125 \text{ V}, V_{in} = 0.735 \text{ V}$$

0.735V

 


- ①  $V_x = V_i - 0.5V$ ;
- ② if  $V_x > 0$ , MSB = 1, keep current  $V_x \rightarrow V_x$ ;  
otherwise, MSB = 0, restore  $V_x \rightarrow V_x + 0.5V$ ;

# Binary Search: MSB-1 Cycle

$$N = 3, FS = 1 \text{ V}, \Delta = 0.125 \text{ V}, V_{in} = 0.735 \text{ V}$$

0.735V

 


- ①  $V_x = V_x - 0.25\text{V};$
- ② if  $V_x > 0$ , MSB-1 = 1, keep current  $V_x \rightarrow V_x;$   
otherwise, MSB-1 = 0, restore  $V_x \rightarrow V_x + 0.25\text{V};$



# Binary Search: MSB-2 Cycle

$$N = 3, FS = 1 \text{ V}, \Delta = 0.125 \text{ V}, V_{in} = 0.735 \text{ V}$$

0.735V

 

- ①  $V_x = V_x - 0.125\text{V};$
- ② if  $V_x > 0$ , MSB-2 = 1, keep current  $V_x \rightarrow V_x;$   
otherwise, MSB-2 = 0, restore  $V_x \rightarrow V_x + 0.125\text{V};$

# Modified Binary Search

$N = 3$   
 $FS = 1000$   
 $\Delta = FS/8$   
 $= 125$   
 $V_{in} = 735$

$$D_o = \left\lfloor \frac{V_{in}}{\Delta} \right\rfloor \quad \underbrace{735}_{V_{in}} \div \underbrace{125}_{LSB} = \underbrace{[1,0,1]_b}_{D_o \text{ (Quotient)}} \quad r \quad \underbrace{440/4}_{QN \text{ (Remainder)}}$$

$$\begin{array}{r} 1 \\ \hline 500 \overline{) 735} \\ \underline{500} \\ 235 \times 2 \end{array}$$

Step 1:  
1<sup>st</sup> bit



$$\begin{array}{r} 0 \\ \hline 500 \overline{) 470} \\ \underline{0} \\ 470 \times 2 \end{array}$$

Step 2:  
2<sup>nd</sup> bit





$$\begin{array}{r} 1 \\ \hline 500 \overline{) 940} \\ \underline{500} \\ 440 \end{array}$$

Step 3:  
3<sup>rd</sup> bit




□ Always use the same divisor but **amplify** the remainder / residue

# Algorithmic (Cyclic) ADC

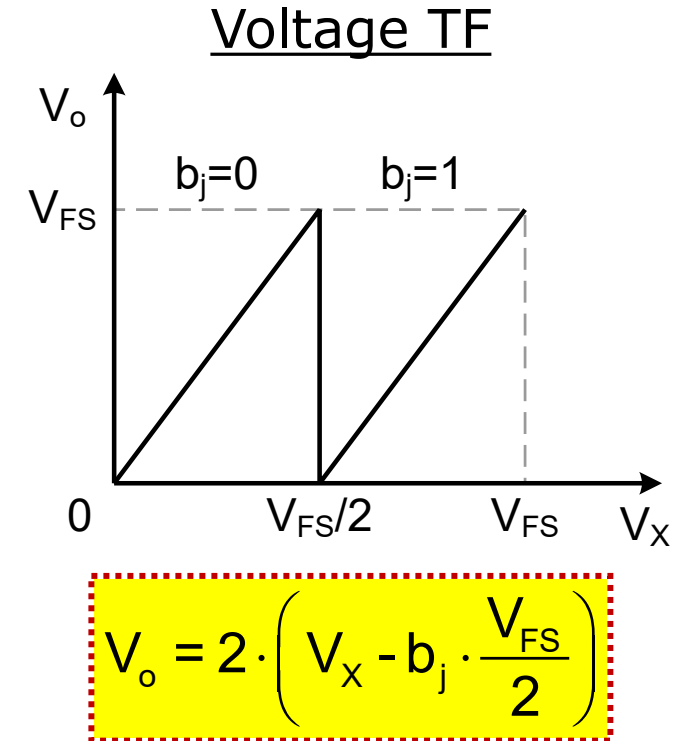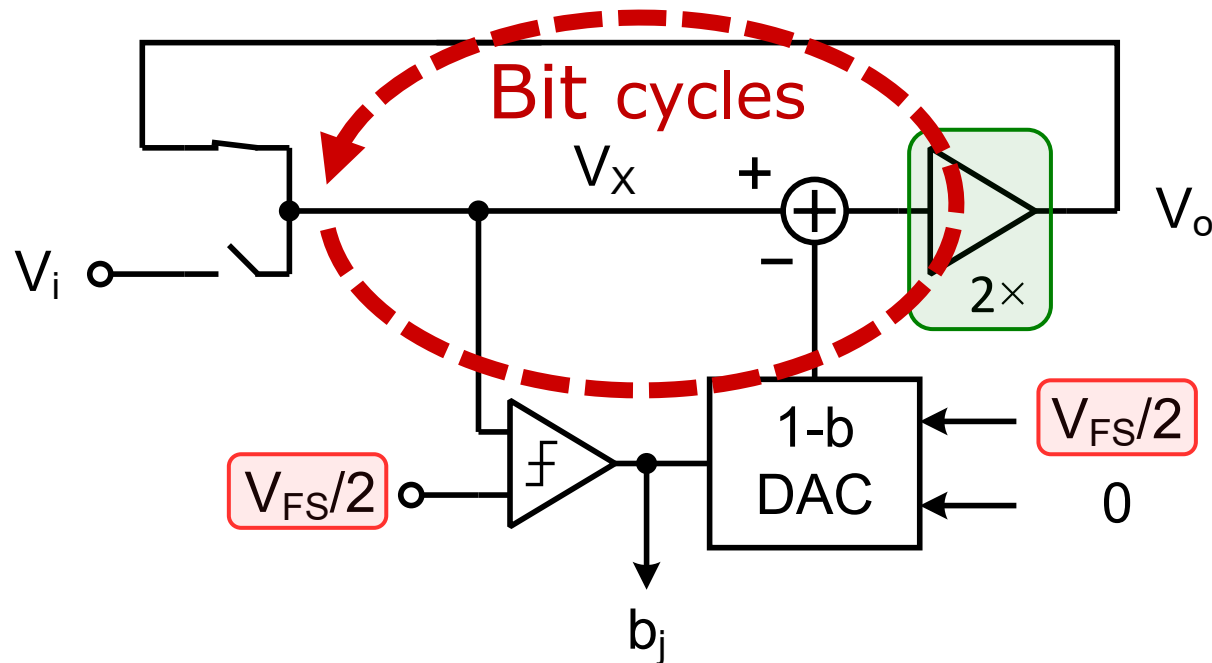

- Fixed comparison threshold ( $V_{FS}/2$ ) + 1b DAC + 2X Residue Gain
  - Comparison  $\rightarrow$  if  $V_x < V_{FS}/2$ , then  $b_j = 0$ ; otherwise,  $b_j = 1$
  - Residue generation  $\rightarrow V_o = 2 \cdot (V_x - b_j \cdot V_{FS}/2)$

# Pipelined ADC

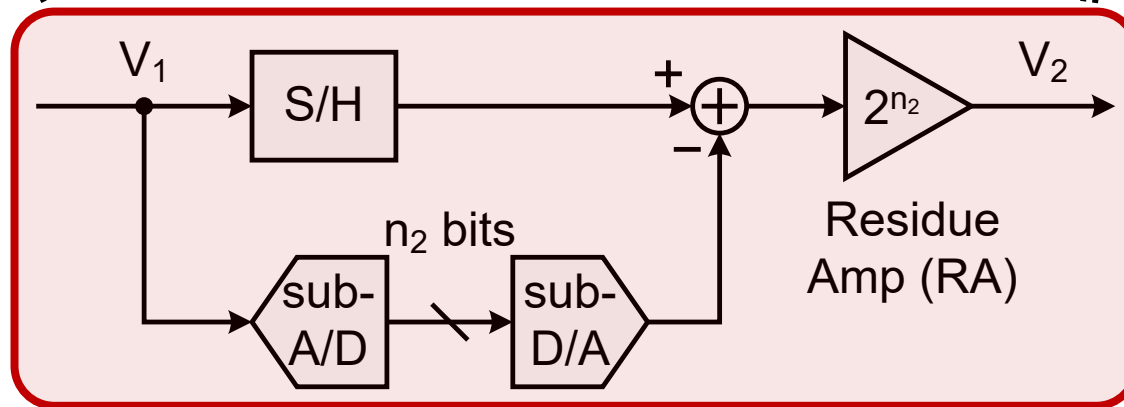 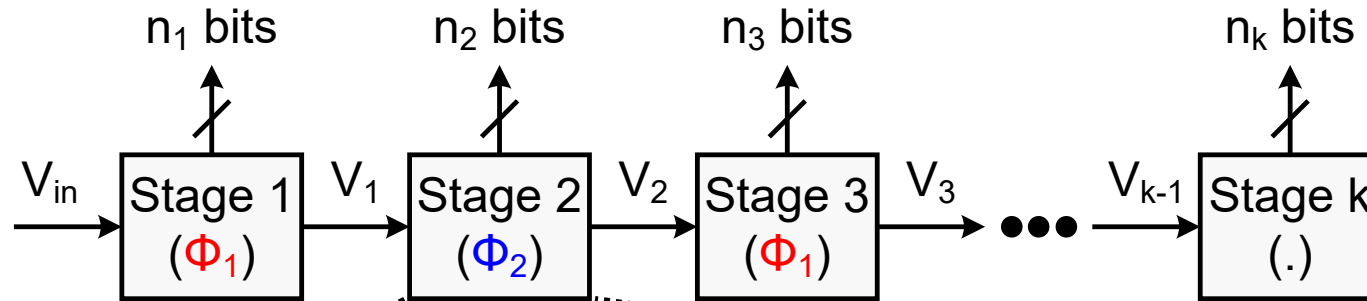

- ❑ Concurrent stage operation
- ❑ Latency  $\sim k/2$
- ❑ Throughput  $\sim f_s$
- ❑ Complexity  $\sim N$
- ❑ Scalable to M-bit/stage ( $1 \leq M < N$ )
- ❑ Power saving possible by stage tapering along pipeline


❑ Algorithmic loop unrolled  $\rightarrow$  pipeline enables high conversion throughput

---

# **NYQUIST DAC ARCHITECTURES**

## **BW, UE, AND SEGMENTED**

# Binary-Weighted (BW) DAC

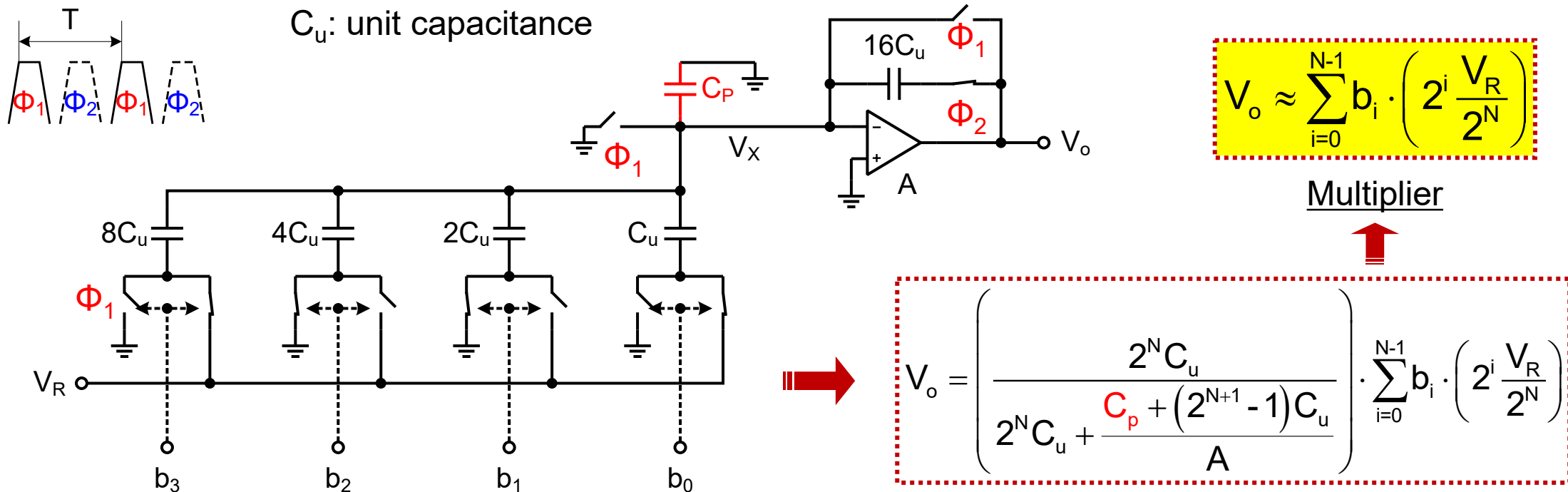

- ❑ Charge redistribution (CR) of a BW capacitor array → very efficient architecture
- ❑ N-bit DAC requires N switching elements, w/ direct binary bits passthrough control
- ❑ Can be generalized to resistive, R2R and current-steering topologies

# Midscale DNL / INL (MSB Transition)

**Code 0111**

$$V_o(0111) = \left( \frac{C_1 + C_2 + C_3}{16C_u} \right) \cdot V_R$$

**Code 1000**

$$V_o(1000) = \left( \frac{C_4}{16C_u} \right) \cdot V_R$$



**half array**    **other half**

$$\text{Assume: } C_4 - (C_1 + C_2 + C_3) = C_u + \delta C$$


$$\text{DNL} = \frac{V_o(1000) - V_o(0111) - 1 \text{ LSB}}{1 \text{ LSB}}$$

$$= \frac{\delta C}{C_u} \rightarrow \text{often the largest DNL error}$$

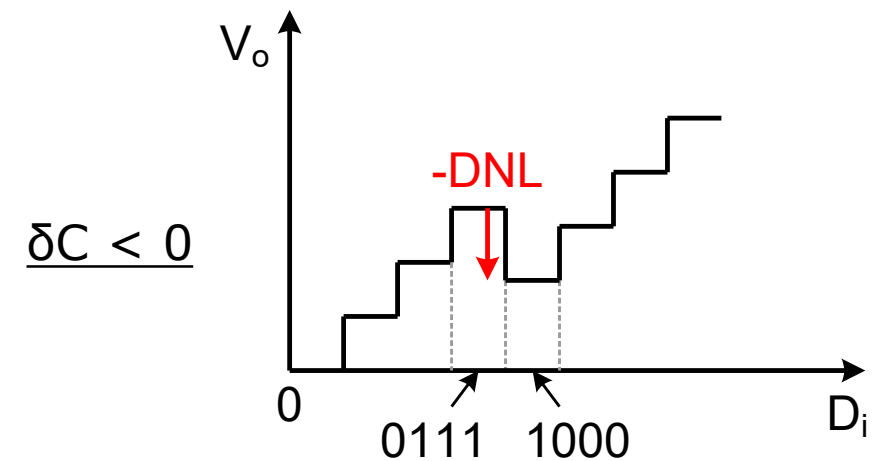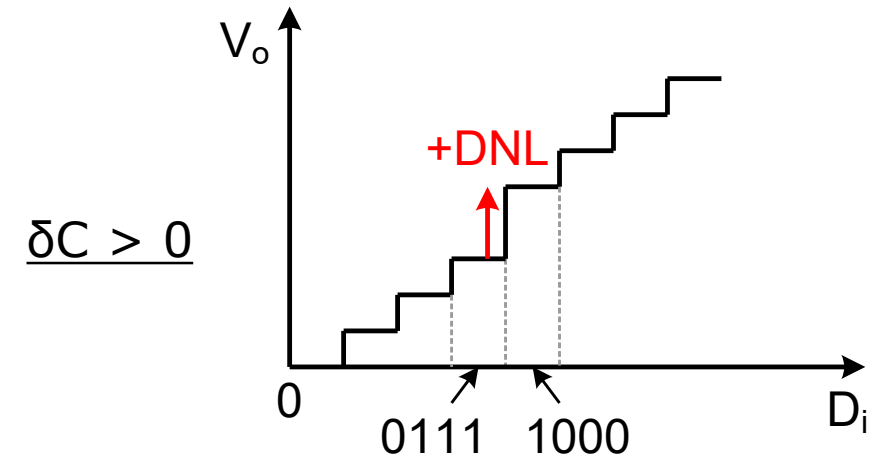- ❑ Architectural efficiency comes at a cost of linearity
- ❑ Original CR SAR ADC employed this type of DAC



# Unit-Element (UE) DAC

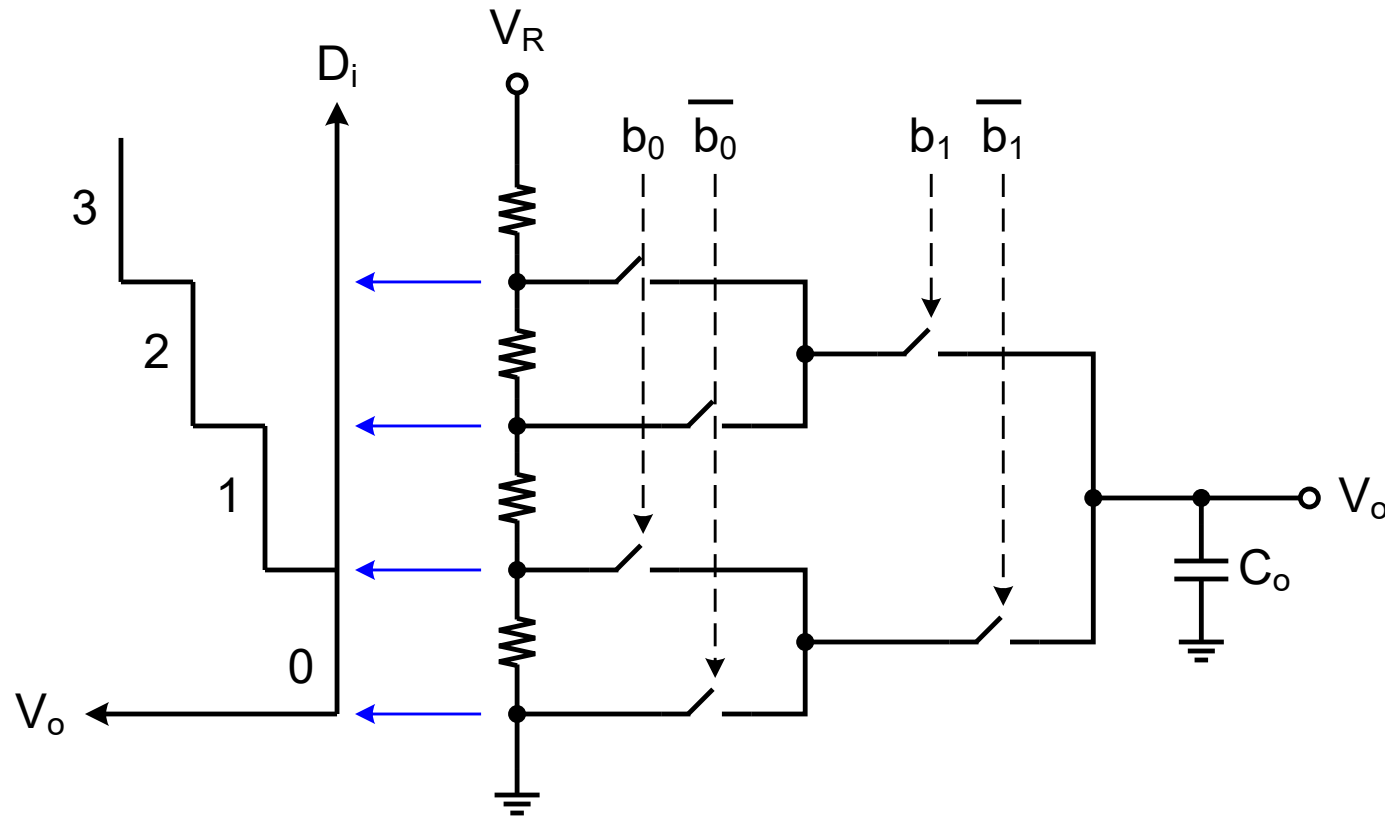

UE DAC:

$$\sigma_{\text{DNL}} = \frac{\sigma_R}{R}$$
$$\sigma_{\text{INL}} (\text{max}) \approx \frac{\sqrt{2^N}}{2} \left( \frac{\sigma_R}{R} \right)$$


BW DAC:

$$\sigma_{\text{DNL}} (\text{max}) \approx \sqrt{2^N} \left( \frac{\sigma_R}{R} \right)$$
$$\sigma_{\text{INL}} (\text{max}) \approx \frac{\sqrt{2^N}}{2} \left( \frac{\sigma_R}{R} \right)$$

- ❑ Inherently monotonic → good DNL performance (what about INL?)
- ❑  $\sim 2^N$  switching elements → complexity ↑ speed ↓ for large N → typically  $N \leq 8$  bits
- ❑ Needs binary-thermometer decoder




# Current-Steering DAC (UE)

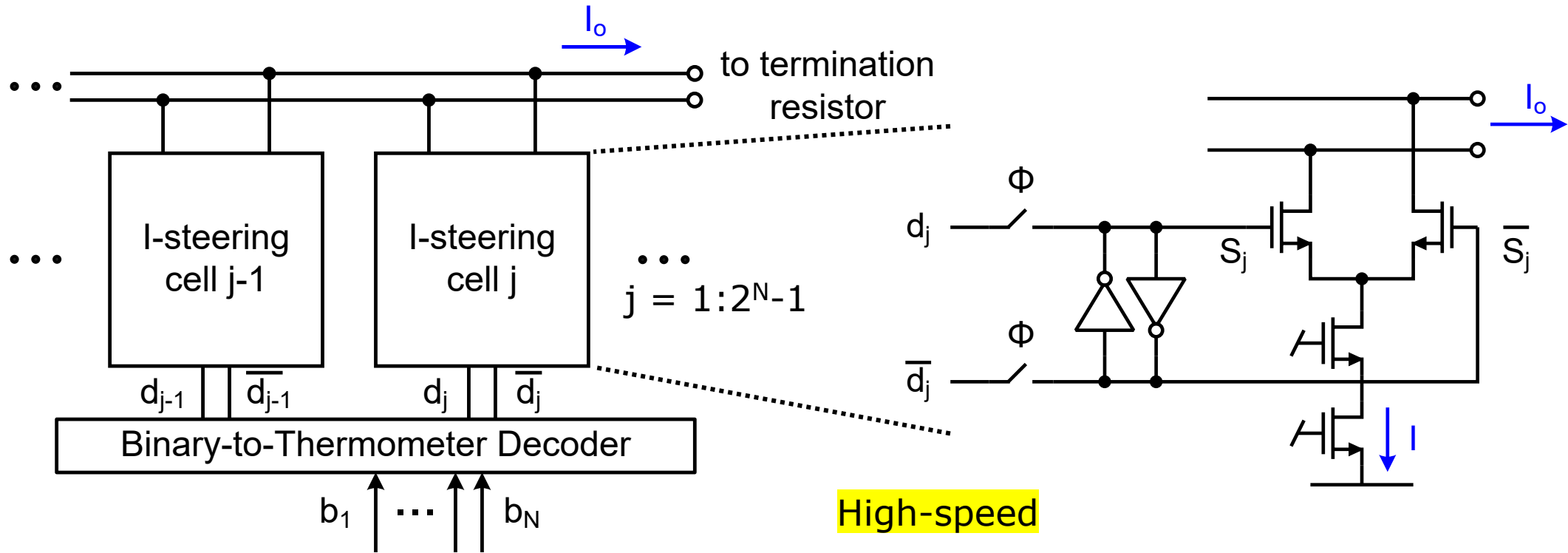

- ❑ Fast switching, inherently monotonic → good DNL performance
- ❑  $\sim 2^N$  current cells decomposed into a  $(2^{N/2} \times 2^{N/2})$  matrix of rows and columns

# Segmented (SM) DAC

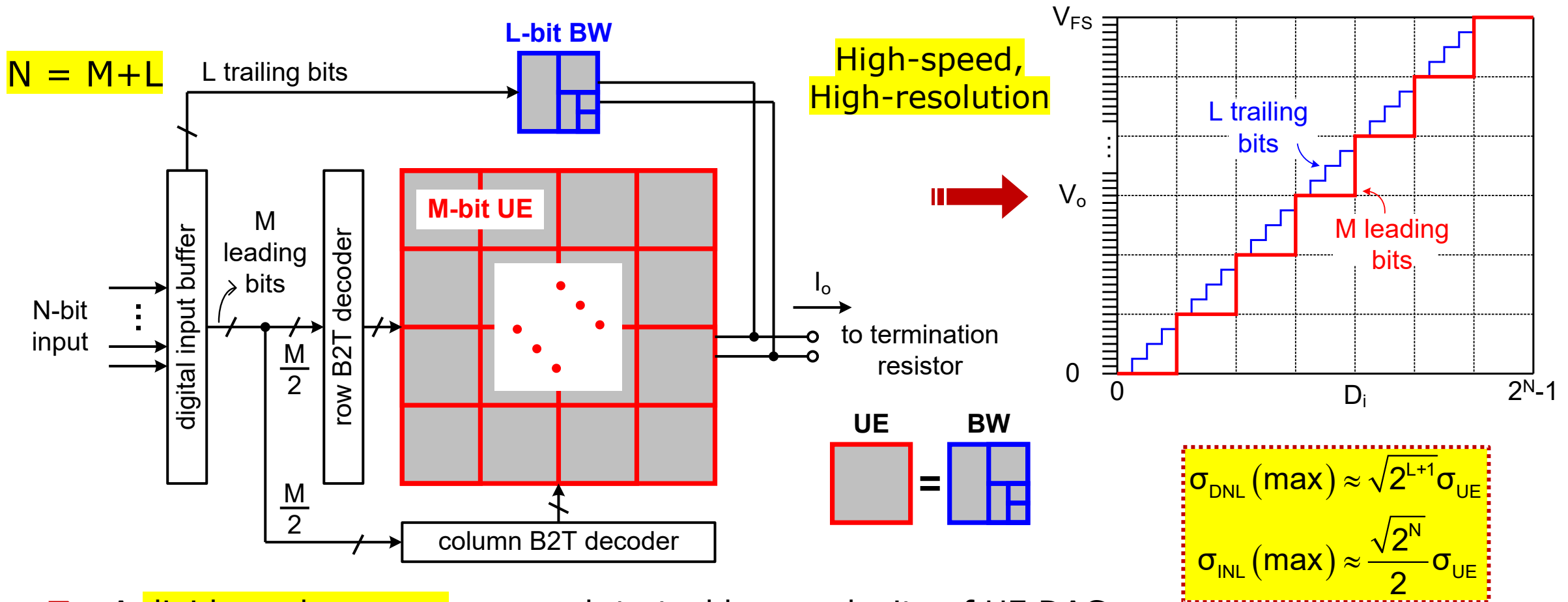

- ❑ A **divide-and-conquer** approach to tackle complexity of UE DAC
- ❑ # of switching elements  $\sim 2^{M+L} \ll 2^{M+L}$

# Comparison of DAC Architectures

BW DAC:

$$\sigma_{\text{DNL}}(\text{max}) \approx \sqrt{2^N} \sigma_{\text{UE}}$$

$$\sigma_{\text{INL}}(\text{max}) \approx \frac{\sqrt{2^N}}{2} \sigma_{\text{UE}}$$

UE DAC:

$$\sigma_{\text{DNL}} = \sigma_{\text{UE}}$$

$$\sigma_{\text{INL}}(\text{max}) \approx \frac{\sqrt{2^N}}{2} \sigma_{\text{UE}}$$

SM DAC:

$$\sigma_{\text{DNL}}(\text{max}) \approx \sqrt{2^{L+1}} \sigma_{\text{UE}}$$

$$\sigma_{\text{INL}}(\text{max}) \approx \frac{\sqrt{2^N}}{2} \sigma_{\text{UE}}$$

Example:  $N = 12, M = 8, L = 4, \sigma_{\text{UE}} = 1\%$

Architecture	$\sigma_{\text{INL}}$ [LSB]	$\sigma_{\text{DNL}}$ [LSB]	# of switching elements
BW	0.32	0.64	12 (=N)
UE	0.32	0.01	4095 ( $\approx 2^N$ )
SM	0.32	0.057	259 ( $\approx 2^{M+L}$ )

---

# **DATA CONVERTER CIRCUIT BUILDING BLOCKS**

# Common Circuit Building Blocks


---

- **DAC:** resistive, capacitive, current types, unit-element, binary-weighted, segmented architectures – every ADC has a DAC built-in!
  - **Comparator:** decision device, regeneration speed, metastability
  - **Sample and Hold (S/H) or Track and Hold (T/H):** CT-DT conversion
- } Covered in this section
- Residue Amplifier (RA): closed-loop vs. open-loop, static vs. dynamic amplifiers
  - Reference and Biasing: BGR, current mirror, on-chip / off-chip bypass
  - Clocking Circuits: jitter critical for high-speed ADC and DAC (power consumption)
  - Digital Logics: combinatory, sequential, memory, I/O, etc.
  - Input and Reference Buffers: peripheral, critical, and power hungry (but often not included in the converter core)


---

# COMPARATOR

# Comparator: Decision-Making Device


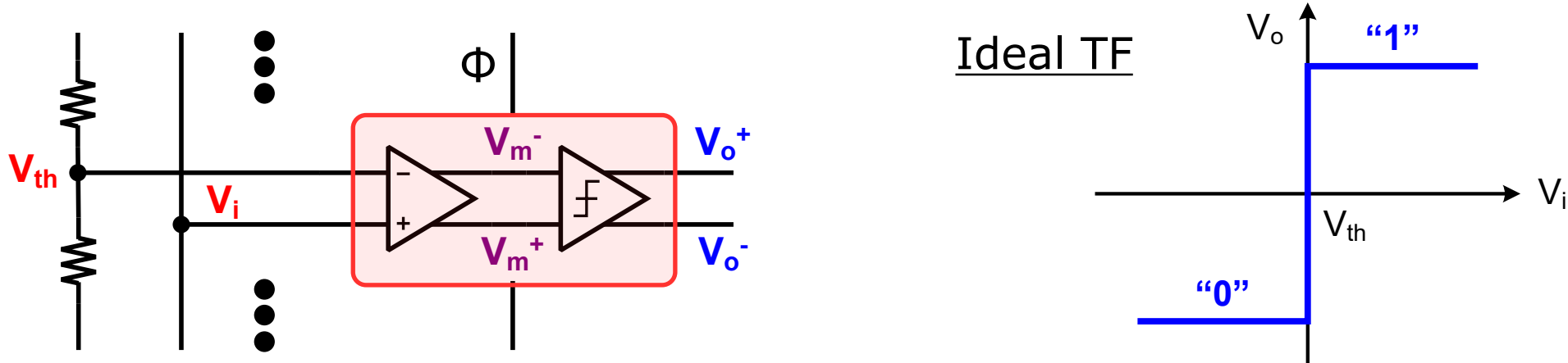


→ From soft to hard decision →

 

- Precise gain and linearity unnecessary → simple, open-loop, low-gain, and wideband Preamplifier (PrA) followed by Latch (positive feedback)



# A Simple Comparator

 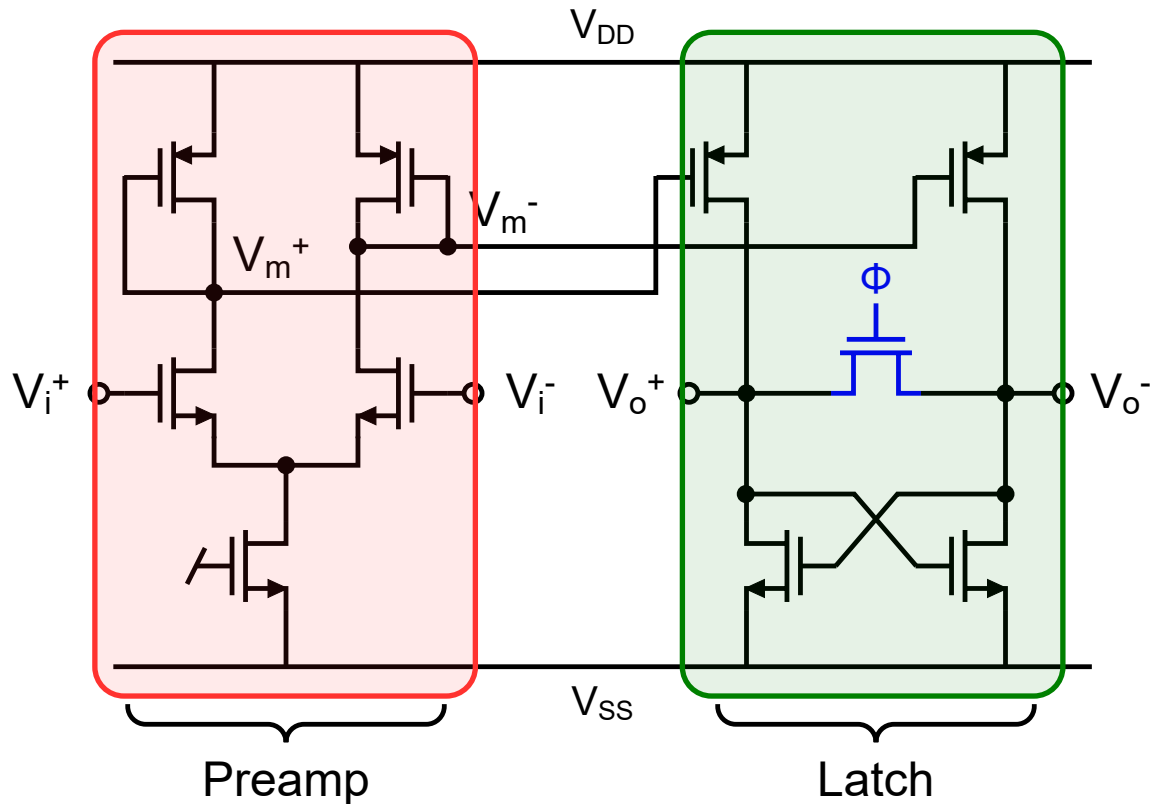

- ❑ Preamp establishes a seed voltage for latch regeneration → dominates offset
- ❑ Usually no return after regeneration starts




# Latch Regeneration

  


$$\begin{cases} V_o^+ = -V_o^- \\ V_o^+ = -g_m \cdot V_o^- / sC_L \end{cases} \text{ or } \begin{pmatrix} 1 & 1 \\ 1 & g_m / sC_L \end{pmatrix} \begin{pmatrix} V_o^+ \\ V_o^- \end{pmatrix} = 0 \Rightarrow s_p = g_m / C_L \text{ (RHP pole)}$$
 
$$V_o(t) = V_o(t=0) \cdot \exp\left(t \cdot \frac{g_m}{C_L}\right) \text{ or } t = \frac{C_L}{g_m} \cdot \ln\left(\frac{V_o(t)}{V_o(t=0)}\right)$$




# Metastability

 


$$V_o(t) = A_{PrA} \cdot V_i(0) \cdot \left( t \cdot \frac{g_m}{C_L} \right)$$

Curve	$V_i(t=0)$	$t/(C_L/g_m)$
①	10mV	2.3
②	1mV	4.6
③	100μV	6.9
④	10μV	9.2

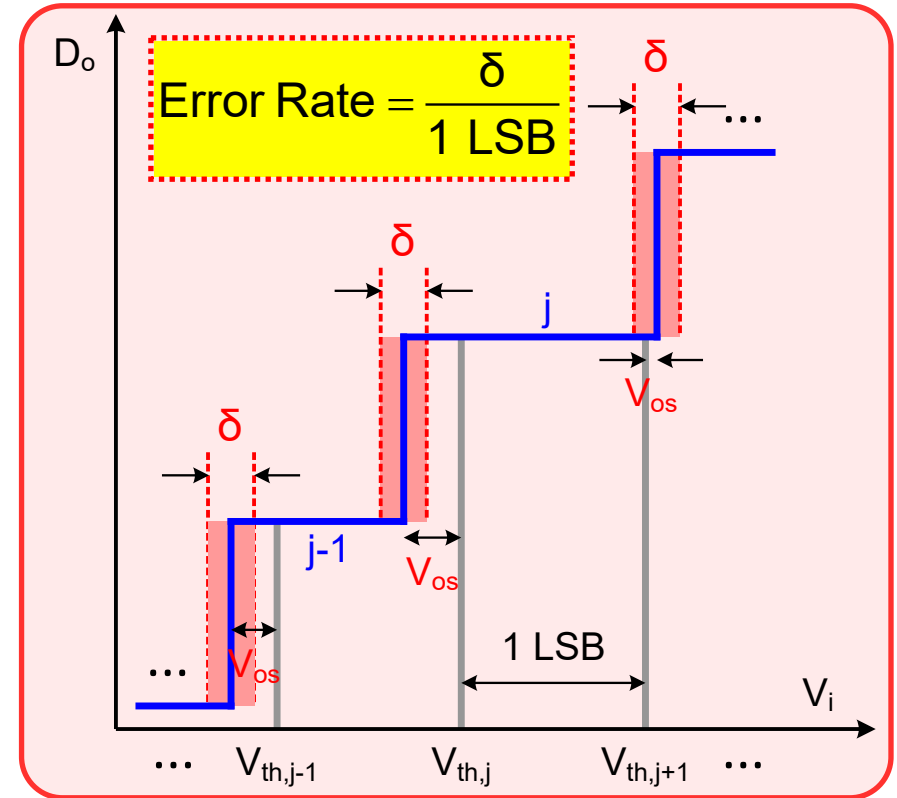


- ❑ Comparator fails to produce valid logic output for tiny inputs → **metastability**
- ❑ No decision is often worse than a wrong decision! (conversion may halt!)

# Dynamic Comparator

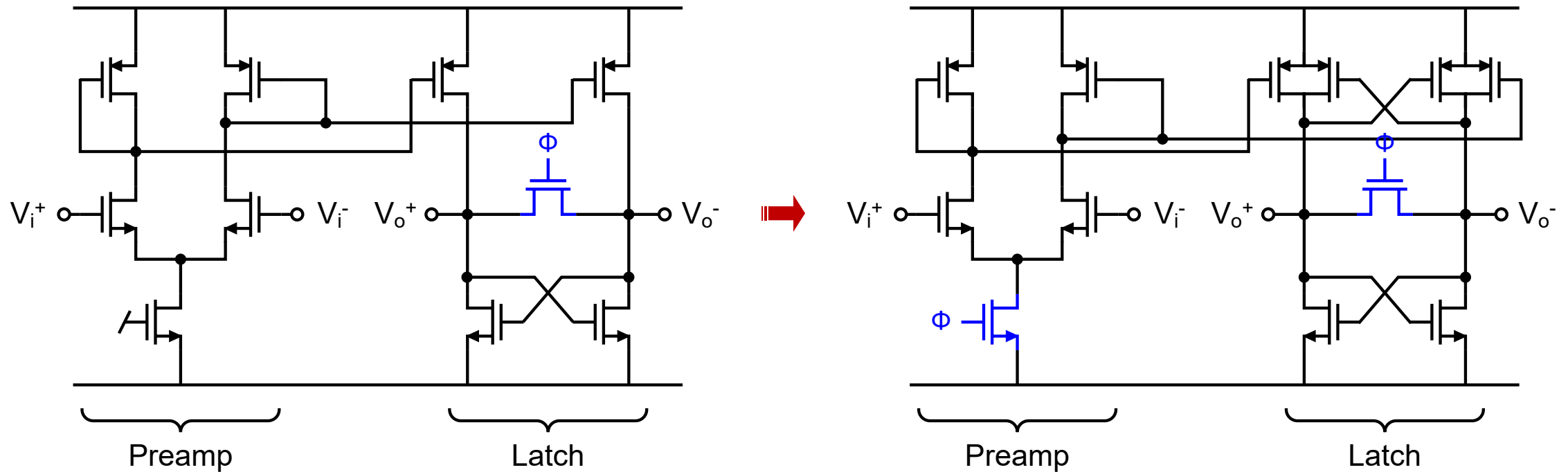



- Starting with the static comparator (i.e., preamp + latch)
- First, add a PMOS cross-coupled pair in the latch to fully regenerate logic levels
- Second, turn the static preamp into a dynamic one

# Dynamic Comparator

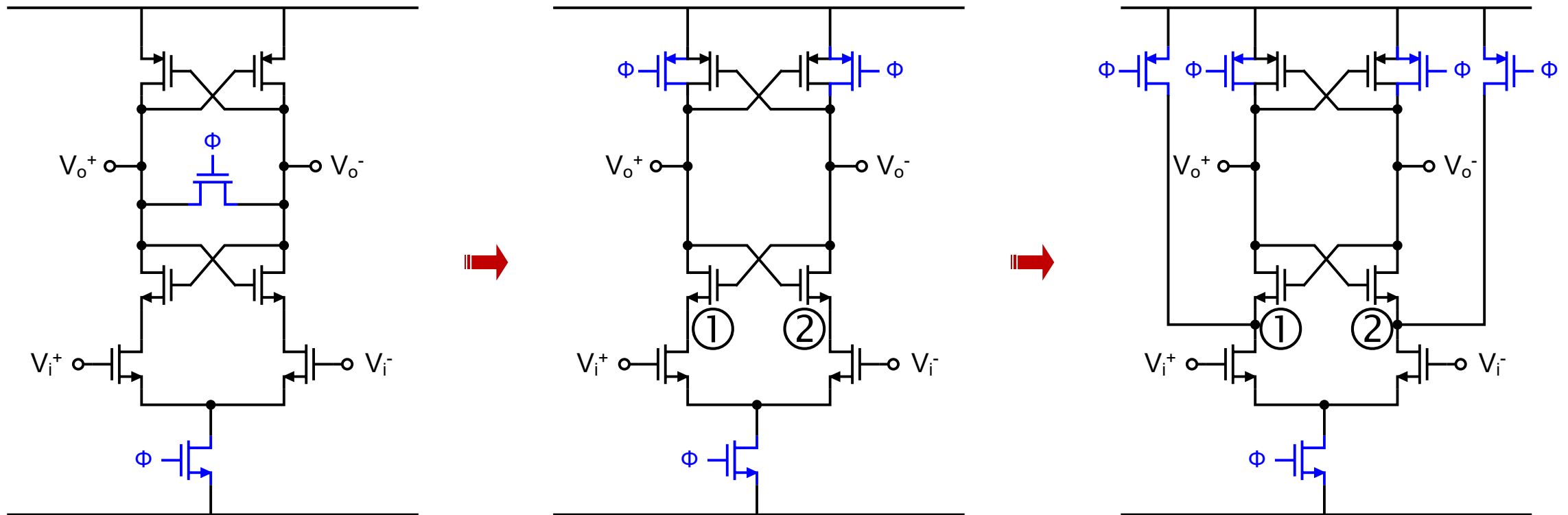

- ❑ Third, stack the two together for current reuse (to save power)
- ❑ Then, replace the crowbar by conspicuous PMOS reset (high) switches
- ❑ Lastly, completely reset ALL internal nodes to remove memory

# Strong-Arm Dynamic Comparator

  


- ❑ Compact (PrA + latch)
- ❑ Fully dynamic operation  
→ low power
- ❑ Single-phase clock  
(Low reset, high eval.)
- ❑ Both nodes ① and ②  
start @ $V_{DD}$ , end @Gnd  
→ large CM kickback


---

# MOS SAMPLE-AND-HOLD

# ZOH, S/H, and T/H

 
 
$$R_{on}^{-1} = \mu C_{ox} \frac{W}{L} (V_{DD} - V_{th} - V_i)$$



- A.k.a. S/H
- Zero acq. time
- Not realistic
  
- T/2 acq. time
- Practical

- MOS technology naturally suitable for implementing T/H
- Terms S/H and T/H are often used interchangeably

# MOS Switch Performance


$$R_{on} = \frac{1}{\mu C_{ox} \frac{W}{L} (V_{DD} - V_{th} - V_i)} = \frac{L^2}{\mu Q_{ch}}$$

Accuracy	$t_{acq}$
0.1% (10b)	$\geq 7\tau$
0.01% (13b)	$\geq 9\tau$

Charge Inj.:  $\Delta V = \frac{\Delta Q}{C_s} \approx \frac{1}{2} \frac{Q_{ch}}{C_s}$

Tracking BW:  $TBW \approx \frac{1}{R_{on} C_s} = \frac{\mu Q_{ch}}{L^2 C_s}$


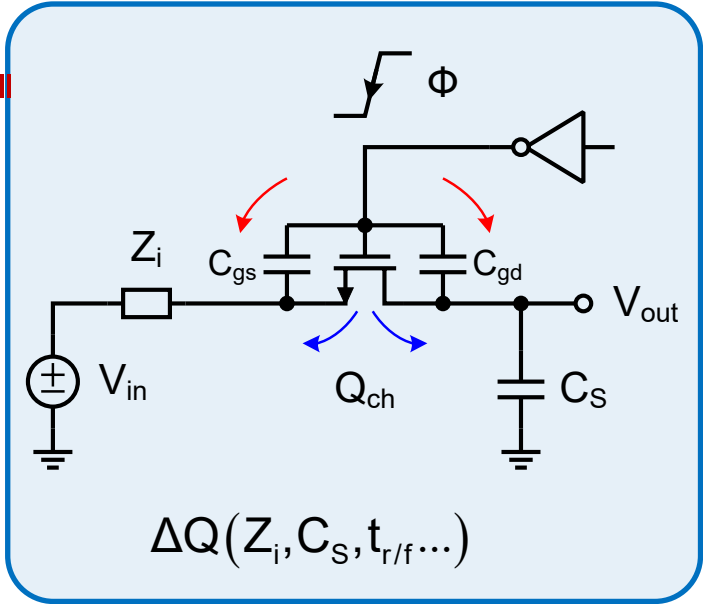
Performance metrics:  $\frac{TBW}{\Delta V} \approx \frac{\mu Q_{ch}}{L^2 C_s} \cdot 2 \frac{C_s}{Q_{ch}} = \frac{2\mu}{L^2}$



- Tracking bandwidth limited by switch on-resistance  $R_{on}$  (consider clock bootstrapping)
- Clock Feedthrough (CF) and Charge Injection (CI) are network/clock/signal dependent
- Technology scaling improves T/H performance!** (a.i.a. leakage allows)



  
# Aperture Error and Bottom-Plate Sampling



Bottom-Plate Sampling


- Exact sampling moment (aperture) depends on input in top-plate sampler
- Bottom-plate sampling avoids aperture error and CF+CI distortion by V.G. switching

# Aperture Jitter

 

$$\overline{\delta V^2(t)} = \frac{A^2 \omega^2 \sigma_t^2}{2}$$

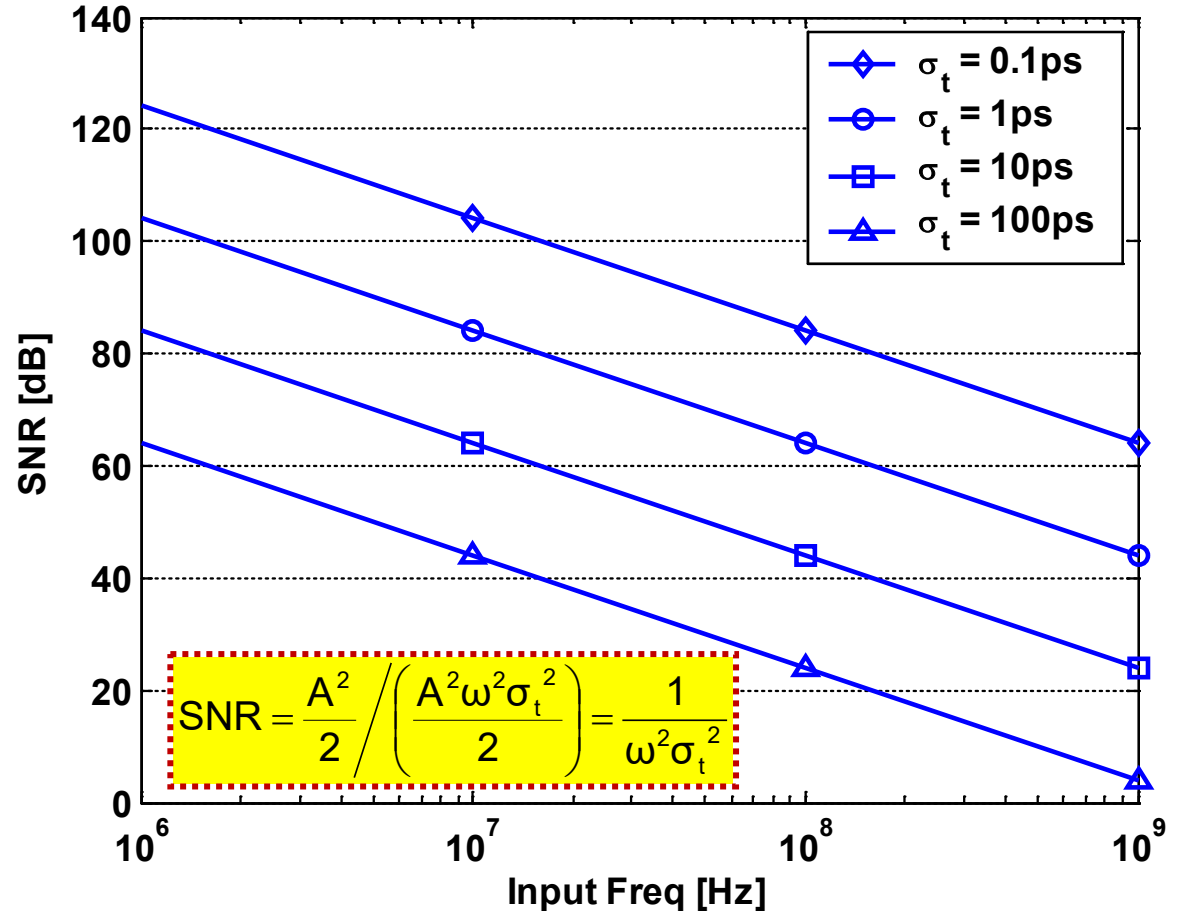
- Assuming sinewave
- Cyclostationary error



□ Aperture jitter limits sampler SNR especially at high frequencies

# Evaluating T/H Performance

Sampling network:

 


kT/C noise:

$$\overline{V_N^2} = \int_0^\infty 4kTR \cdot \left| \frac{1}{1 + j2\pi \cdot f \cdot RC_s} \right|^2 df = \frac{kT}{C_s}$$

$$\text{SNDR} = \frac{\overline{V_i^2}}{\overline{V_N^2} + \frac{A^2 \omega^2}{2} \sigma_t^2 + \overline{V_{\text{DISTO}}^2}}$$


Noise
Jitter
Distortion

 

$C_s$	100pF	<b>1pF</b>	10fF
$\sqrt{\frac{kT}{C_s}}$	6.4μV	<b>64μV</b>	640μV

T = 300K

# Clock Bootstrapping

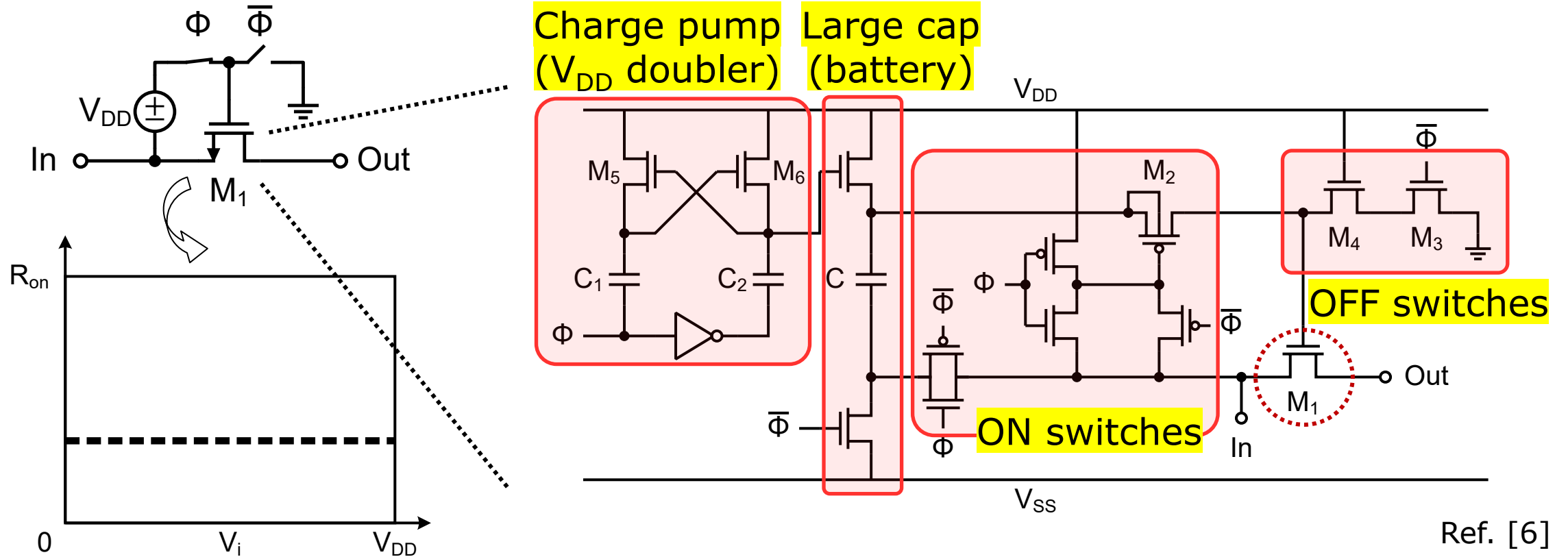



- Constant gate overdrive  $V_{GS} = V_{DD} \rightarrow R_{on}$  independent of  $V_{in}$  to the first order (body effect, charge sharing)  $\rightarrow$  larger tracking BW, better linearity

---

# REDUNDANCY


**(NO MULTI-STEP ADC WORKS WITHOUT IT!)**

# Comparator Offset in Pipelined ADC

 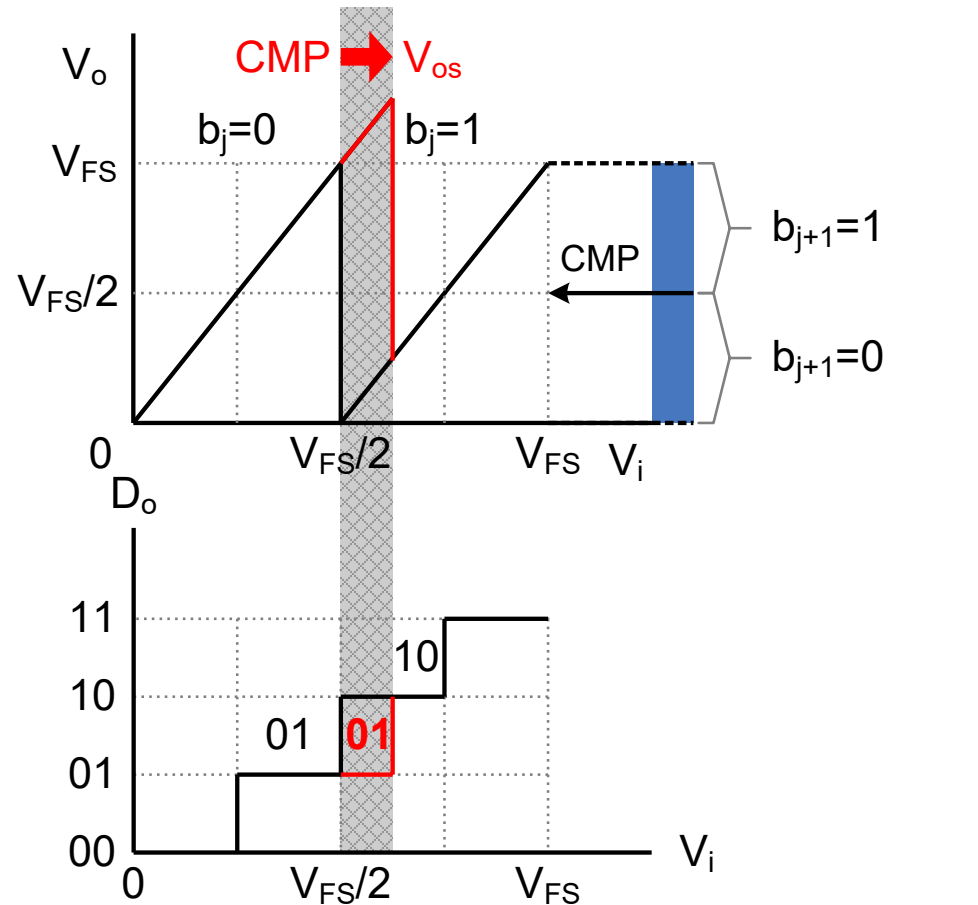

- Nearly Zero Tolerance ( $< 1$  LSB) on comparator offset!!
- **Architectural Redundancy** introduced by over-/under-range comparators

# How Exactly Does Redundancy Work?

 


- ❑ Max tolerance of comparator offset is  $\pm V_{FS}/4$   $\rightarrow$  simple comparators
- ❑ Key to understand redundancy:

$$\begin{aligned}
 V_i &= (b_j + \Delta b_j) \cdot \frac{V_{FS}}{2} + \frac{(V_o + \Delta V_o)}{2} \\
 &= (b_j - 1) \cdot \frac{V_{FS}}{2} + \frac{(V_o + V_{FS})}{2} \\
 &= b_j \cdot \frac{V_{FS}}{2} + \frac{V_o}{2}
 \end{aligned}$$


- ❑ Complementary **analog** and **digital** errors cancel each other w/ redundancy

# From 1-bit To 1.5-bit Architecture

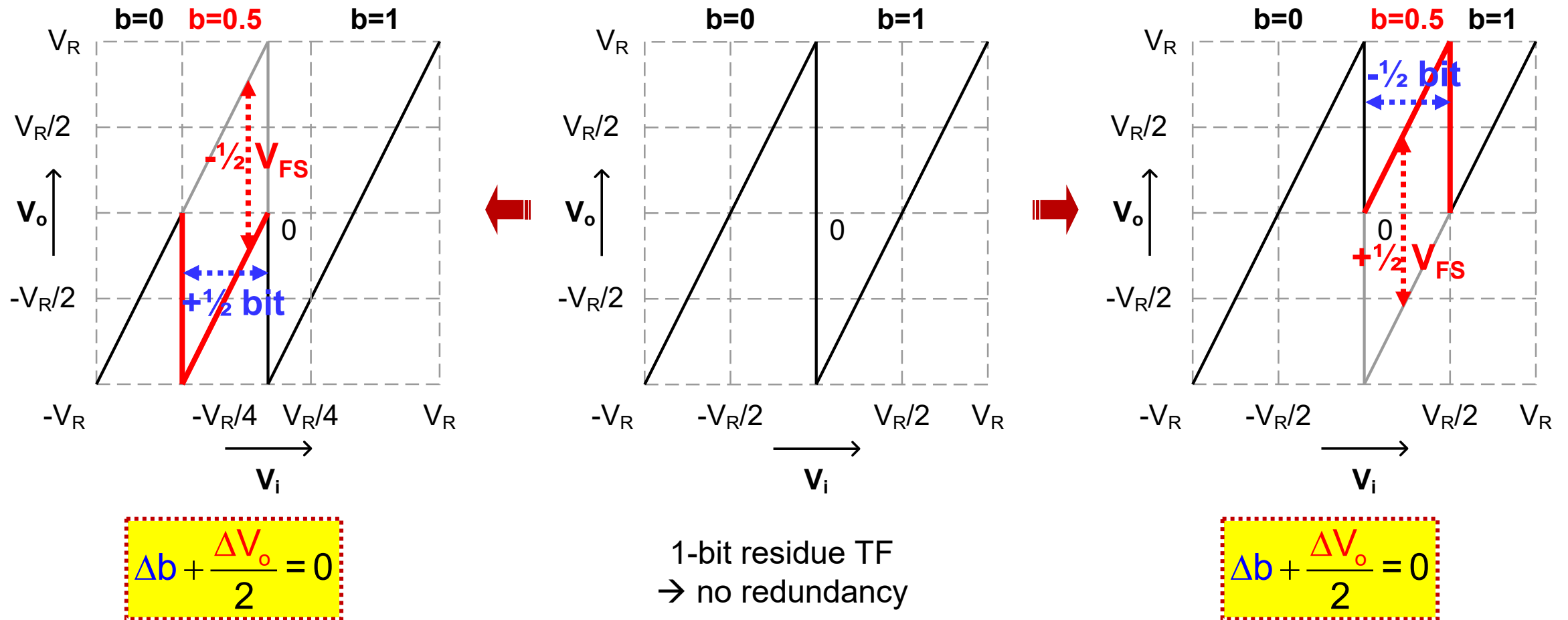





# From 1-bit To 1.5-bit Architecture

 


- ❑ **1.5-bit residue TF:** 3 decision levels  $\rightarrow$  ENOB =  $\log_2 3 \approx 1.58$
- ❑ Max tolerance of comparator offset is  $\pm V_R/4$
- ❑ Also known as Sweeny-Robertson-Tocher (SRT) division algorithm

# 1.5-bit Multiplier DAC (MDAC)

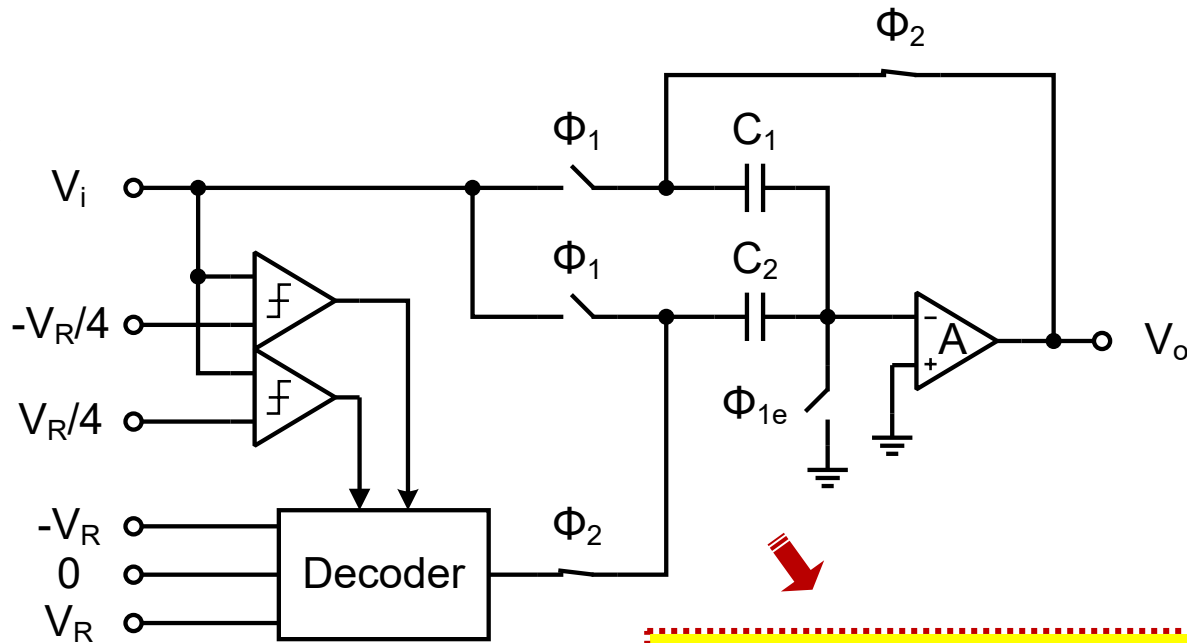 
 
$$V_o = \frac{C_1 + C_2}{C_1} \cdot V_i + (1-b) \frac{C_2}{C_1} \cdot V_R$$





$$V_o = 2 \cdot V_i + (1-b) \cdot V_R$$

- ❑ 2X gain + 3-level DAC + summation all integrated
- ❑ Can be generalized to n.5-bit architectures

Ref. [7]


# 2.5-bit MDAC

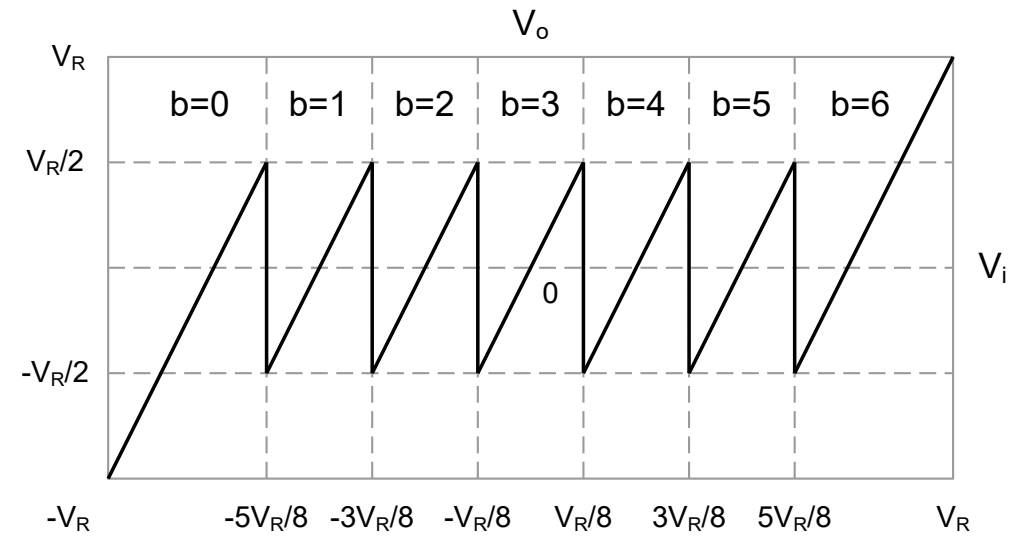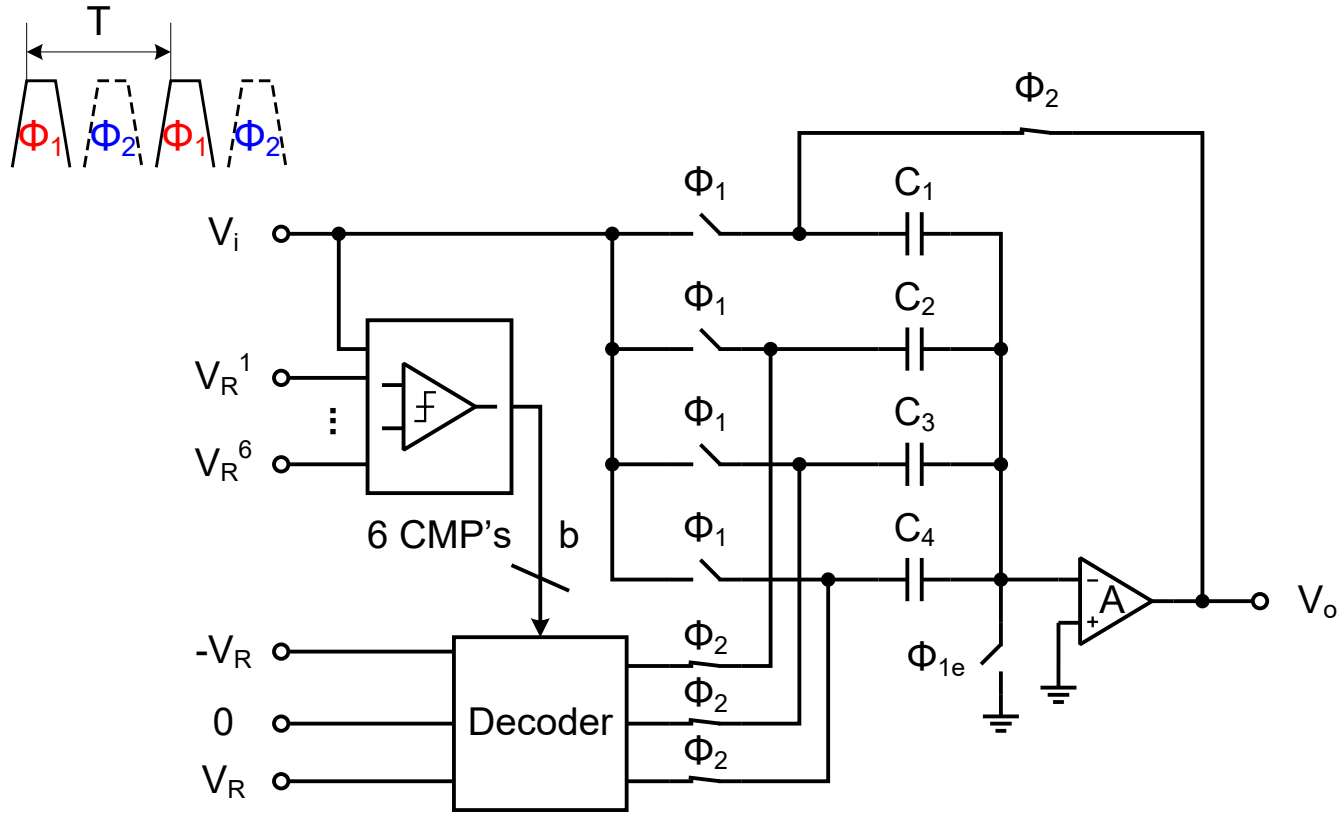


$$V_o = 4 \cdot V_i + (3 - b) \cdot V_R$$

- 4X gain + 7-level DAC + summation all integrated

# Error-Free Conversion With Redundancy

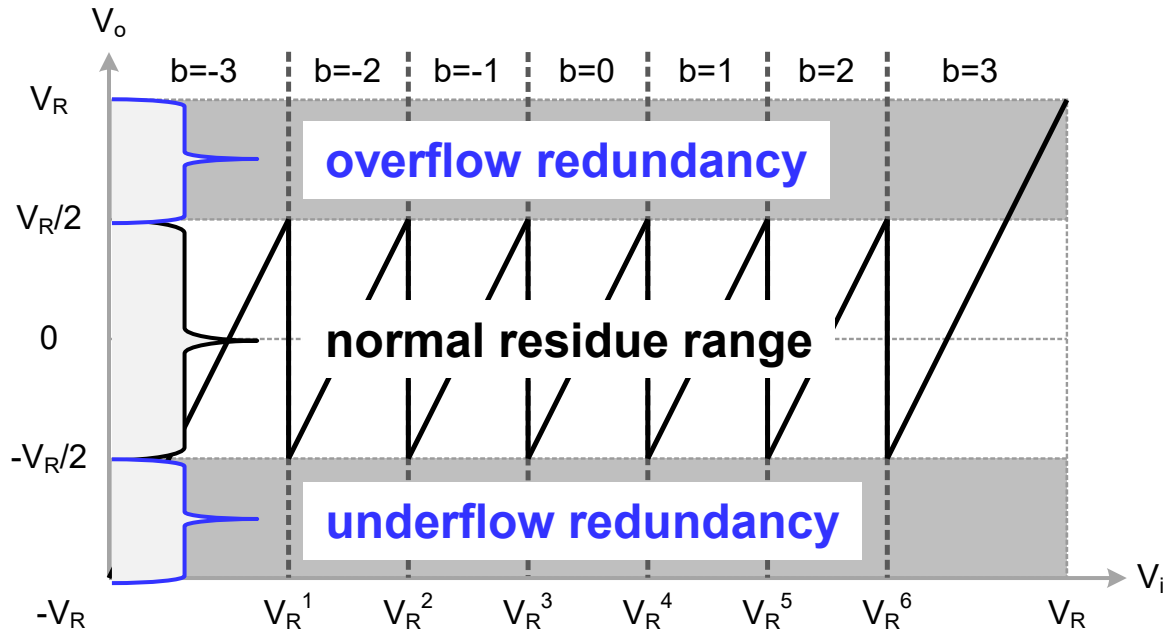


Ideal Residue TF

 

A More Realistic Residue TF

- Comparator and residue amplifier offsets absorbed by **Internal Redundancy**
- Error-free conversion when residue is confined in the range  $[-V_R, +V_R]$

# Pipeline Redundant Bits Assembly

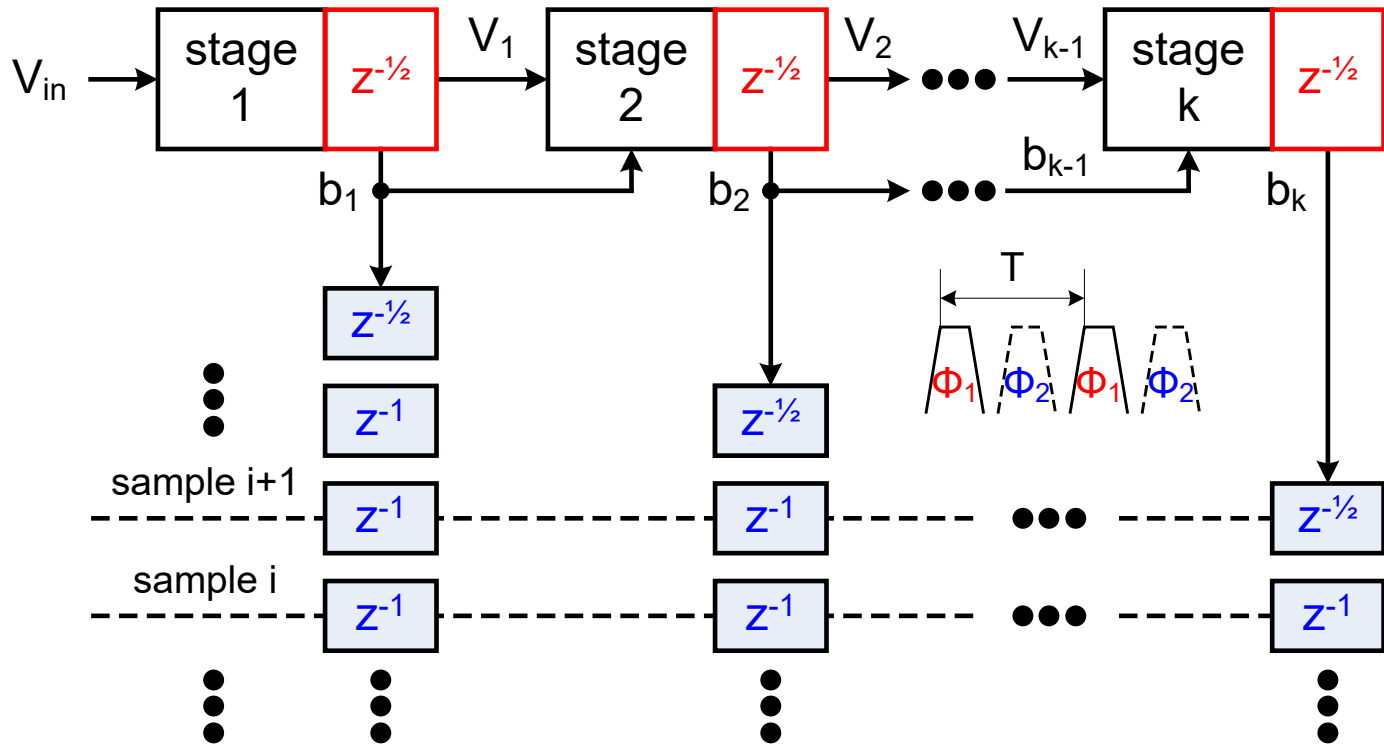



For pipelined ADC,

$$D_o = \underline{W} \cdot \underline{D}_o = \sum_j w_j \cdot b_j$$

$b_1=2$	1	0			
$b_2=0$		0	0		
$b_3=1$			0	1	
$b_4=2$				1	0
$b_5=1$					0 1
$D_o$	1	0	1	0	0 1
	MSB			LSB	


**Decision Vector:**  $\underline{D}_o = \{b_1, b_2, \dots, b_k\}$ , **Scalar Decision:**  $D_o = f(\underline{D}_o)$

# How Does Redundancy Work For SAR?


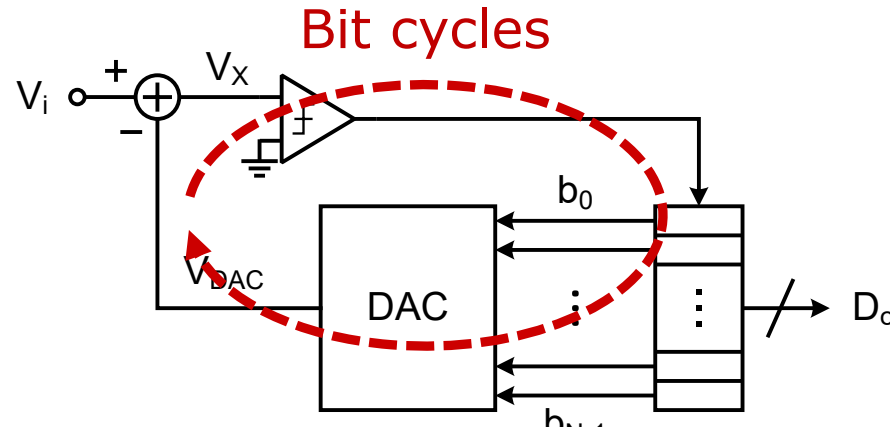
 


← w/o redundancy

w/ redundancy →



 


# Binary Search Revisited

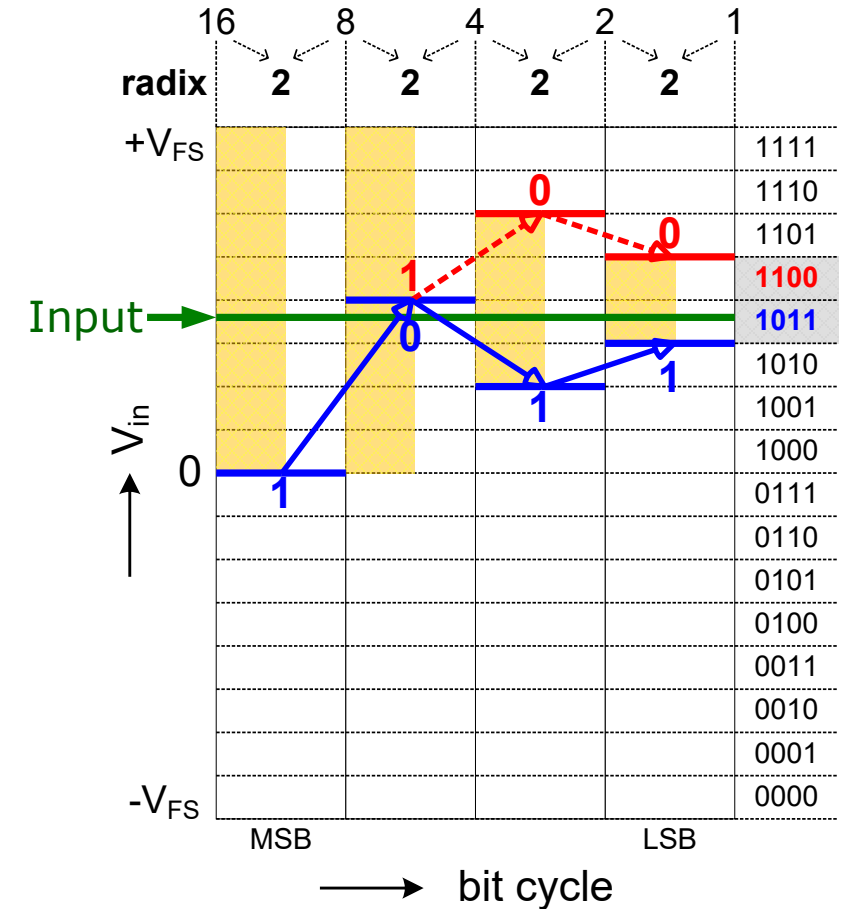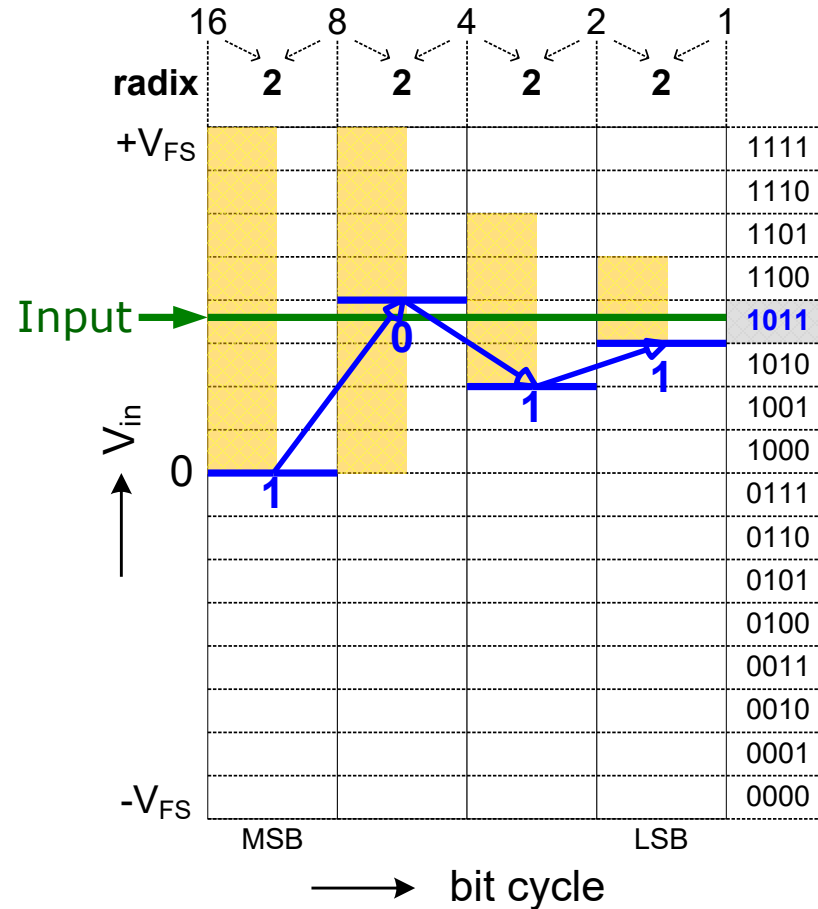 

□ Binary search is efficient, but displays zero error tolerance


# Sub-Binary Search – Redundancy

   


□ Redundancy of sub-binary search can absorb intermediate decision errors




# Sub-Radix-2 Implementations

 

Nonuniform radix

 

Uniform radix

 



Occasional sub-radix

# Uniform Sub-Radix-2 SAR ADC

For redundant bits,

$$\frac{C_{j+1}}{C_j} = \text{radix} < 2$$

e.g., in a uniform radix SAR

  

- ❑ Hard-coded radices dependent on the DAC capacitor ratios
- ❑ Minimal analog complexity, no additional decoding effort
- ❑ Suitable for high-resolution SAR ADC (that requires radix calibration)

# SAR Redundant Bits Assembly


$\{w_j\}$ : bit weights

$$D_o \approx \sum_{j=0}^{N-1} \left( \frac{C_j}{\sum C_j} \right) \cdot b_j$$

$$= \sum_{j=0}^{N-1} w_j \cdot b_j$$

$$\sum Q_{DAC} = V_R \sum_{j=0}^{N-1} C_j \cdot b_j$$
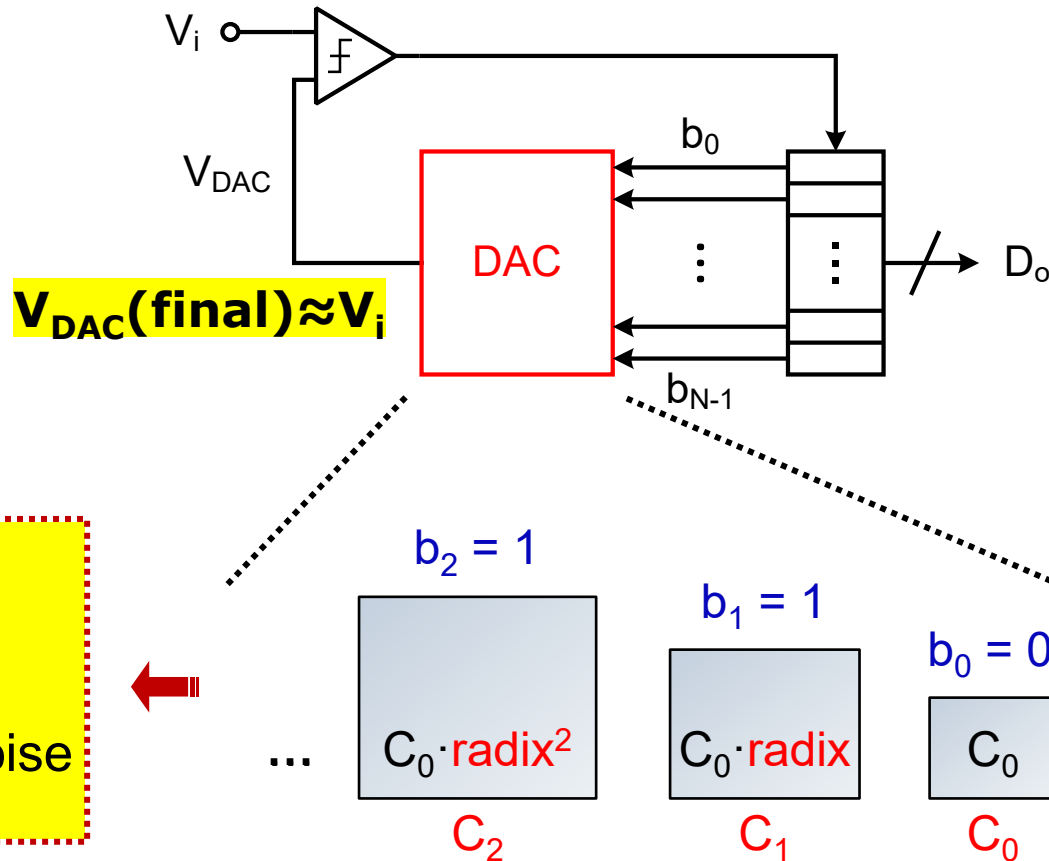
$$= V_i \sum_{j=0}^{N-1} C_j + \text{Noise}$$



$$D_o = \underline{W} \cdot \underline{D}_o = \sum_j w_j \cdot b_j$$

e.g., uniform radix 1.8


$b_4 = 1$	$1 \cdot 1.8^4$
$b_3 = 0$	$0 \cdot 1.8^3$
$b_2 = 1$	$1 \cdot 1.8^2$
$b_1 = 1$	$1 \cdot 1.8^1$
$b_0 = 0$	$0 \cdot 1.8^0$
$D_o$	<b>15.5</b>

**Decision Vector:**  $\underline{D}_o = \{b_{N-1}, b_{N-2}, \dots, b_0\}$ , **Scalar Decision:**  $D_o = f(\underline{D}_o)$


---

# **DIGITAL CORRECTABILITY AND CALIBRATION**

# Digital Calibration

 


Refs. [11-27]

 


- ❑ Many analog errors in data converters, e.g., offset, gain error, nonlinearity, can be corrected digitally, which is widely termed **Digital Calibration**
- ❑ Digital calibration (aka digital enhancement, digital assistance, self-healing) is an opportunity and gift presented by the Moore's law!

# ADC Digital Correctability

 

- **Decision Vector  $\underline{D}_o$**  reveals more info about input than **Scalar Decision  $D_o$**
- A.I.a  **$\underline{D}_o$**  is unique (even  $D_o$  is not), a LUT can in theory be found to recover the input faithfully (i.e., mapping from  $A \rightarrow D$  must be unique, thus, reversible)
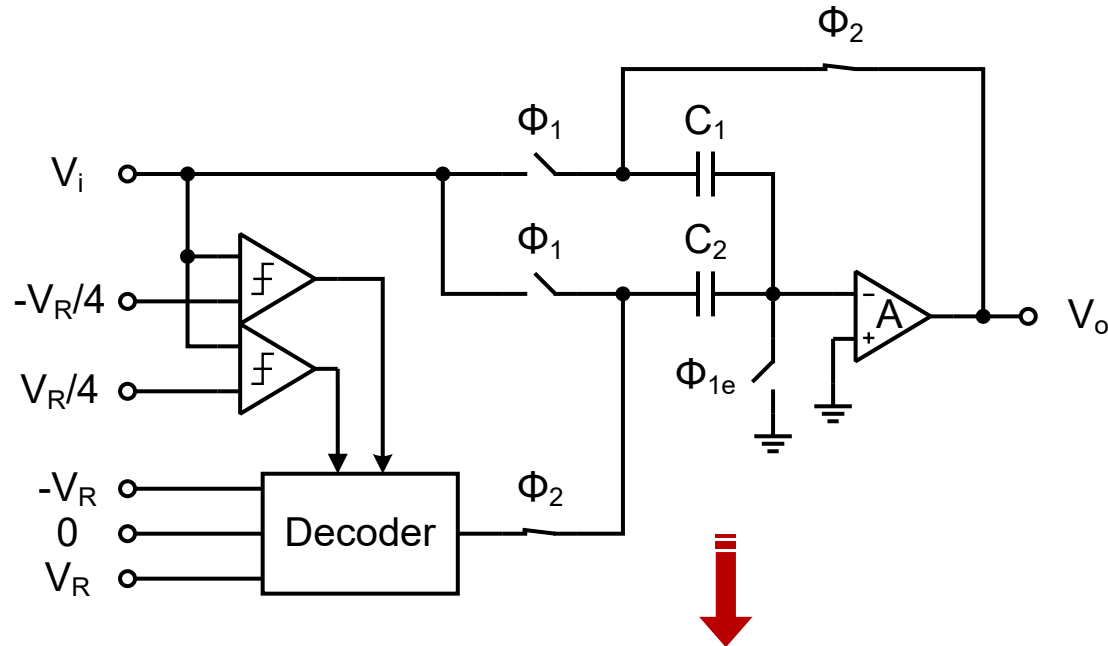
# Residue Errors in Pipelined ADC (1.5-b)



- ❑ Static errors:
  - ❑ Capacitor mismatch/nonlinearity
  - ❑ RA finite gain and nonlinearity
  - ❑ S/H nonlinearity
- ❑ Dynamic errors:
  - ❑ RA slewing/settling error
  - ❑ Switch-induced errors
  - ❑ Reference settling error
  - ❑ Memory errors


$$V_o = \frac{C_1 + C_2}{C_1 + \frac{C_1 + C_2}{A(V_o)}} \cdot f_{S/H}(V_i) + \frac{C_2}{C_1 + \frac{C_1 + C_2}{A(V_o)}} \cdot (1-b) \cdot V_R$$

Ideal residue TF:



$$V_o = 2 \cdot V_i + (1-b) \cdot V_R$$

 
# Residue Errors in Pipelined ADC (1.5-b)



- Simple parametric errors (e.g., capacitor mismatch) can be easily corrected with digital calibration



 
# Residue Errors in Pipelined ADC (1.5-b)



- Static nonlinearities (e.g., INL and DNL), dynamic errors (e.g., RA settling errors [25]), and even memory errors [26] can also be calibrated

# Digital Calibration of Pipelined ADC

Analog pipeline

 

Digital pipeline

For stage  $j$ , we have

$$V_j = \frac{C_1 + C_2}{C_1 + \frac{C_1 + C_2}{A}} \cdot V_{j-1} + \frac{C_2}{C_1 + \frac{C_1 + C_2}{A}} \cdot (1 - b_j) \cdot V_R$$

$$\frac{V_{j-1}}{V_R} = \underbrace{\left( \frac{C_1 + \frac{C_1 + C_2}{A}}{C_1 + C_2} \right)}_{\alpha} \cdot \frac{V_j}{V_R} + \underbrace{\left( \frac{C_2}{C_1 + C_2} \right)}_{\beta} \cdot (b_j - 1)$$

- Needs to determine coefficients

$$\{ \alpha, \beta \} \quad \text{Ref. [13]}$$

- Needs to determine coefficients

$$\{ \alpha_m, \beta \} \quad \text{Ref. [21]}$$

$$D_{j-1} = \alpha \cdot D_j + \beta \cdot (b_j - 1)$$


← linear

$$D_{j-1} = \sum_m \alpha_m \cdot D_j^m + \beta \cdot (b_j - 1)$$

← nonlinear


☞ typically,  $\alpha$  indicates inter-stage residue gain error while  $\beta$  indicates DAC capacitor mismatch errors

# Digital Calibration of SAR ADC

 

Key cal. eqn.:
 
$$D_o \approx \sum_{j=0}^{N-1} \left( \frac{C_j}{\sum C_j} \right) \cdot b_j = \sum_{j=0}^{N-1} w_j \cdot b_j$$





- DAC capacitors are subject to random mismatch → need to determine the exact values of bit weights  $\{w_j\}$

---

# **EXPLOITING REDUNDANCY FOR DIGITAL BACKGROUND CAL.**



# Residue Gain Cal. (DAC Dither)

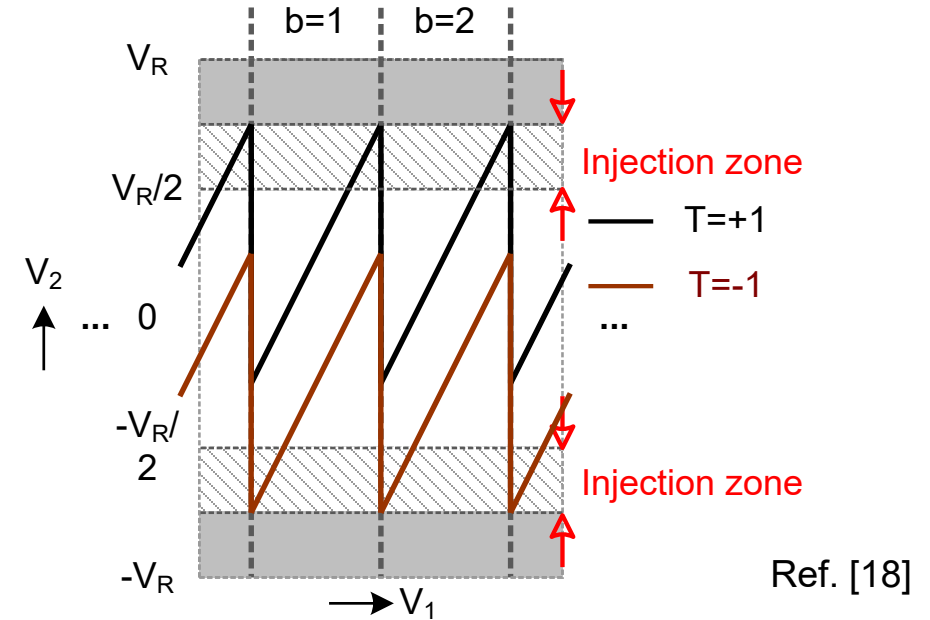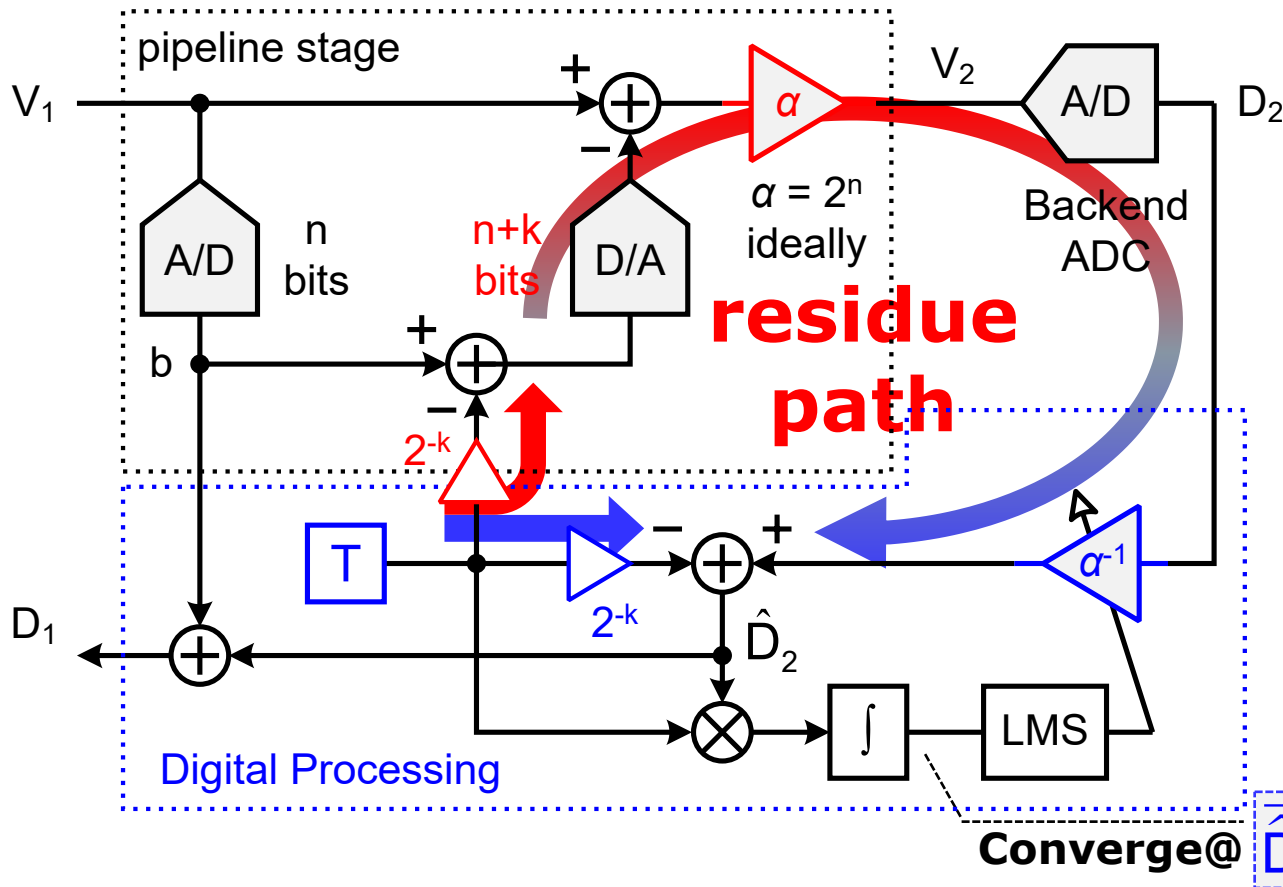

- Small dither added to the residue path, then subtracted out in the digital domain (after correction)

- In steady state, analog gain ( $\alpha$ ) and digital gain inverse ( $\alpha^{-1}$ ) cancel exactly
- $2^{-k} \leq 1/4$  to avoid overflow, DAC adds 2 bits or more to accommodate dither


# Residue Gain Cal. – Comparator Dither

 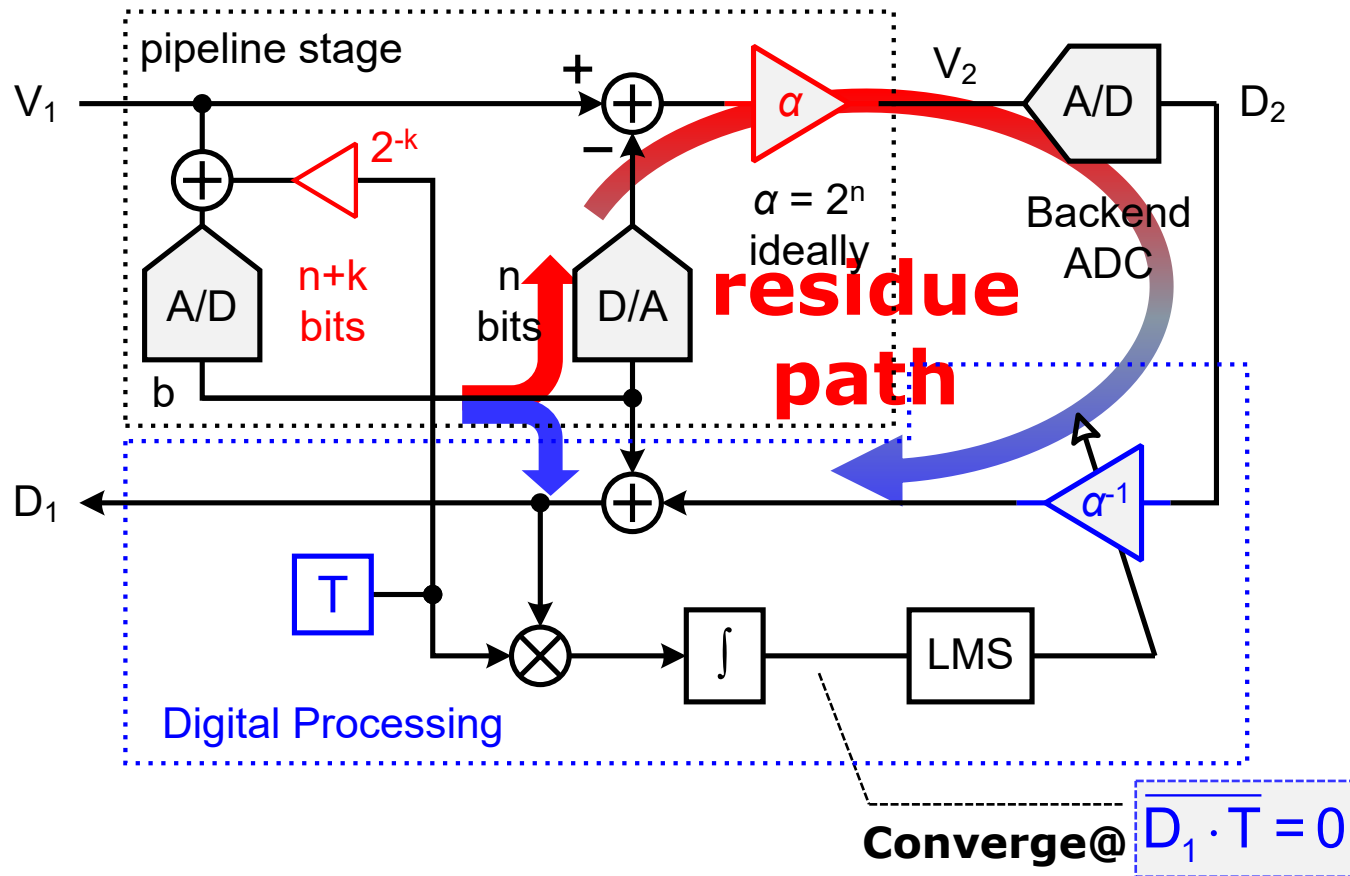

- ❑ Dither forces ADC traverse TWO redundant conversion paths randomly
- ❑ Ideally,  $D_0$  is indep. of conversion path

- ❑ In steady state, analog gain ( $\alpha$ ) and digital gain inverse ( $\alpha^{-1}$ ) cancel exactly
- ❑ Arbitrary dither amplitude a.l.a. no overflow occurs

# SAR Radix Cal. – Sub-Radix Dither

 

- Dither forces ADC traverse TWO redundant conversion paths randomly
- In steady state, accurate  $\{w_j\}$  is identified s.t.  $D_o$  is indep. of  $T$

# Caveats of Background Cal.

---

- ❑ **Vis-à-vis rule:** what you see is what you get – model coefficients often depend on input statistics!
- ❑ **PVT rule:** error model coefficients often depend on P.V.T. variations!
- ❑ **Complexity, memory, digital power...**
- ❑ **Convergence time (tracking speed)**
- ❑ After all, solution needs to be practical and cost-efficient...






---

# **FIGURE-OF-MERIT (FOM)**

## **WALDEN, SCHREIER AND ALPHA FOMs**

# Precision-Speed-Power Tradeoffs

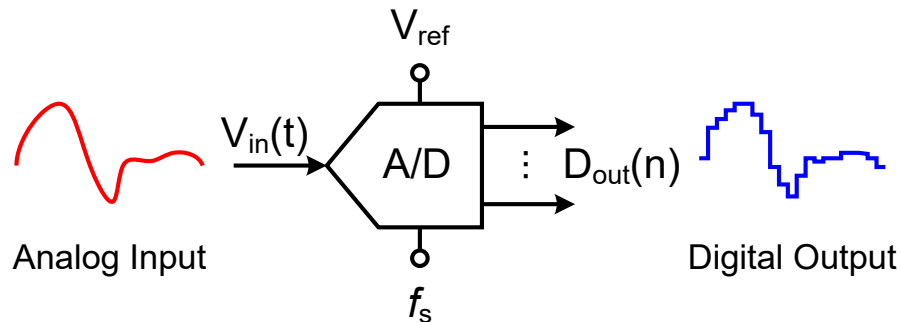

- ❑ BW:  $\min\{f_s/2, \text{ERBW}\}$
- ❑  $f_s$ : sample rate (Nyquist ADC)
- ❑ ERBW: effective resolution BW ( $\Delta\Sigma$  ADC)

## Bandwidth

$$\text{RA bandwidth} \sim \omega_u = \frac{g_m}{C} \sim \frac{1}{C} \frac{I_d}{V_{ov}}$$

## Noise

$$\text{Thermal noise } \sigma_N \sim \sqrt{\frac{kT}{C}}$$

## Matching

$$\text{Mismatch } \sigma_{MM} \sim \sqrt{\frac{1}{\text{Area}}} \sim \sqrt{\frac{1}{C}}$$

- ❑ **ADC Power  $\sim$  Bandwidth or Sample Rate**
- ❑ **A. ADC Power (and Area)  $\sim$  Precision<sup>2</sup> ( $4^{\text{ENOB}}$ )** for noise- or matching-limited design
- ❑ **B. ADC Power (and Area)  $\sim$  Precision ( $2^{\text{ENOB}}$ )** o.w. <sup>☞</sup>

<sup>☞</sup> For example, a low-resolution flash ADC's power and area  $\sim$  its # of conversion steps =  $2^N$  ( $\geq 2^{\text{ENOB}}$ )

# Walden vs. Schreier FoM

## Walden FoM

$$\text{FoM}_W = \frac{P}{f_s \cdot 2^{\text{ENOB}}} \left[ \frac{\text{Joule}}{\text{Conversion Step}} \right]$$

Ref. [29]

## Schreier FoM


$$\text{FoM}_S = \text{SNDR} + 10 \log_{10} \left( \frac{\text{BW}}{P} \right) \text{ [dB]}$$

Ref. [30]


- Schreier FoM:
  - Implicitly assumes Noise- or Matching-limited ADC of **Scenario A**
  - The dimension of  $\text{FoM}_S$  is dB → Schreier FoM naturally measures **SNDR**, or **Performance**, not just # of effective quantization steps
- Walden FoM:
  - Implicitly assumes Nyquist-rate ADC of **Scenario B**
  - The dimension of  $\text{FoM}_W$  is Joule/Conversion-Step → Walden FoM naturally measures **Energy Efficiency**

# Walden vs. Schreier FoM

## Walden FoM

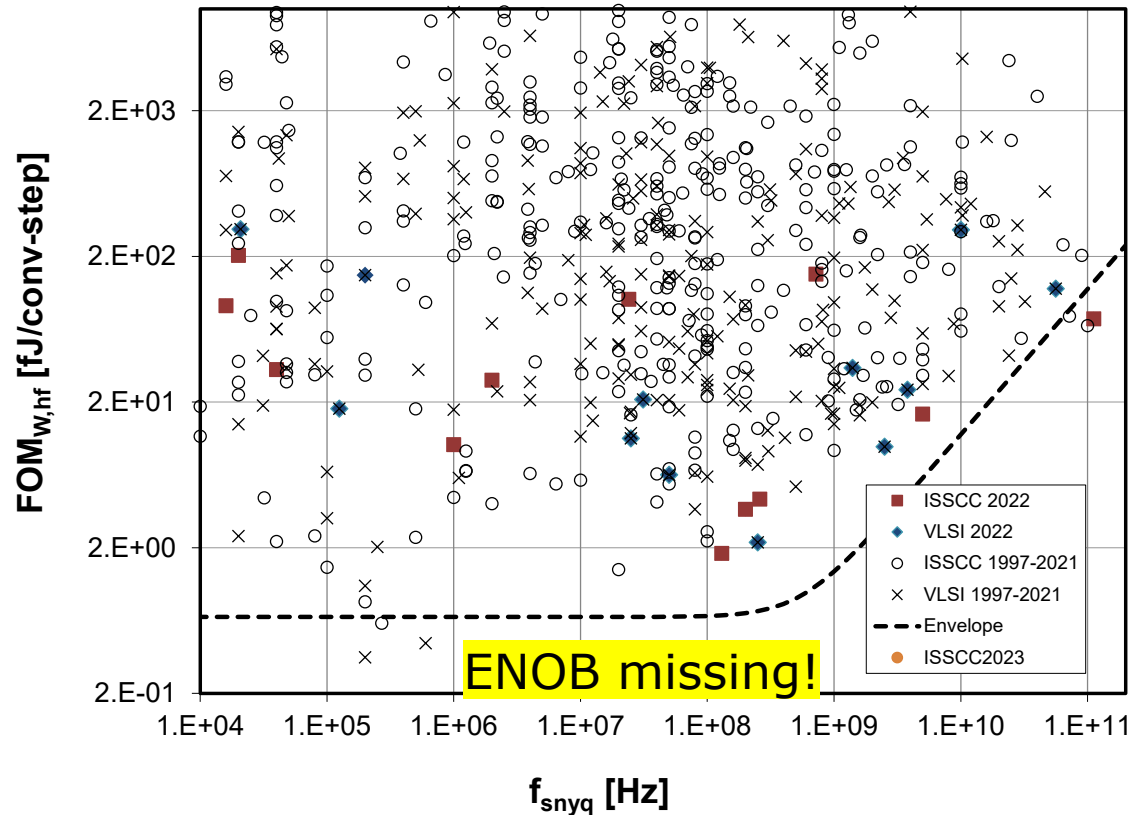

## Schreier FoM

 

Ref. [31]

□ A complete FoM vs. Performance rendering requires a 3D plot

# But Actually...

$$\text{FoM}_W = \frac{P}{f_s \cdot 2^{\text{ENOB}}}$$
$$= \frac{P}{2 \cdot \text{BW} \cdot 2^{\text{ENOB}}}$$



Common  
Part:

$$\frac{P}{\text{BW} \cdot \alpha^{\text{ENOB}}} \quad \text{where } \alpha = 2 - 4$$



$\alpha = 4 \rightarrow$  SNDR (scenario A)

$\alpha = 2 \rightarrow$  design complexity (scenario B)

$$\text{FoM}_S = \text{SNDR} - 1.76 + 10 \log_{10} \left( \frac{\text{BW}}{P} \right) + 1.76$$
$$= 6.02 \cdot \text{ENOB} + 10 \log_{10} \left( \frac{\text{BW}}{P} \right) + 1.76$$
$$= 10 \log_{10} \left( 4^{\text{ENOB}} \right) + 10 \log_{10} \left( \frac{\text{BW}}{P} \right) + 1.76$$
$$= 10 \log_{10} \left( \frac{\text{BW} \cdot 4^{\text{ENOB}}}{P} \right) + 1.76$$

□ The common part between the two seemingly distinct FoMs is striking!

# Alpha FoM

Define " **$\alpha$** " efficiency

$$\text{FoM}_\alpha = \frac{P}{\text{BW} \cdot \alpha^{\text{ENOB}}} \quad \text{where } \alpha = 2 - 4$$

- $\alpha = 2 \rightarrow$  Walden FoM
- $\alpha = 4 \rightarrow$  Schreier FoM

Also define " **$\alpha$** " performance


$$\text{Performance} = \text{BW} \cdot \alpha^{\text{ENOB}} \quad [\text{Hz} \cdot \text{Precision}]$$

- $\alpha^{\text{ENOB}}$  indicates "Precision"


$$\text{Efficiency} \times \text{Performance} = \frac{P}{\text{BW} \cdot \alpha^{\text{ENOB}}} \times \text{BW} \cdot \alpha^{\text{ENOB}} = \text{Power}$$

- Performance vs. Efficiency plot gives more info when comparing designs
- Given Power, Performance and Efficiency trade hyperbolically - **Alpha law**

# Performance vs. Efficiency (PE) Chart



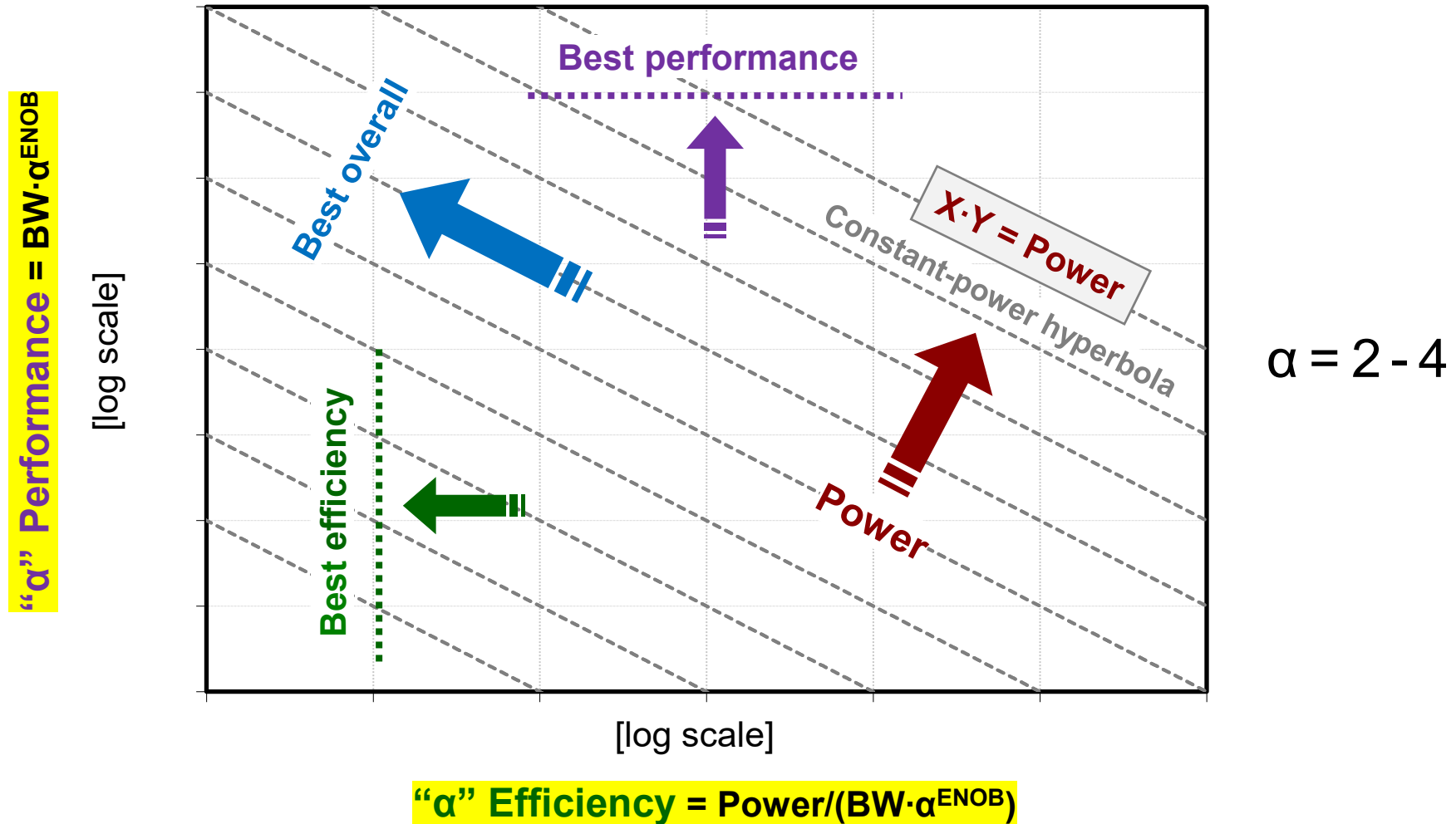


# ADC PE Chart (1997-2023)

 




# ADC PE Chart: $\alpha=2-4$

   


# ADC PE Chart (1997-2000)

 


$\alpha = 3$

# ADC PE Chart (1997-2010)

 


$\alpha = 3$

# ADC PE Chart (1997-2022)

 

$\alpha = 3$

# ADC PE Chart (1997-2022)

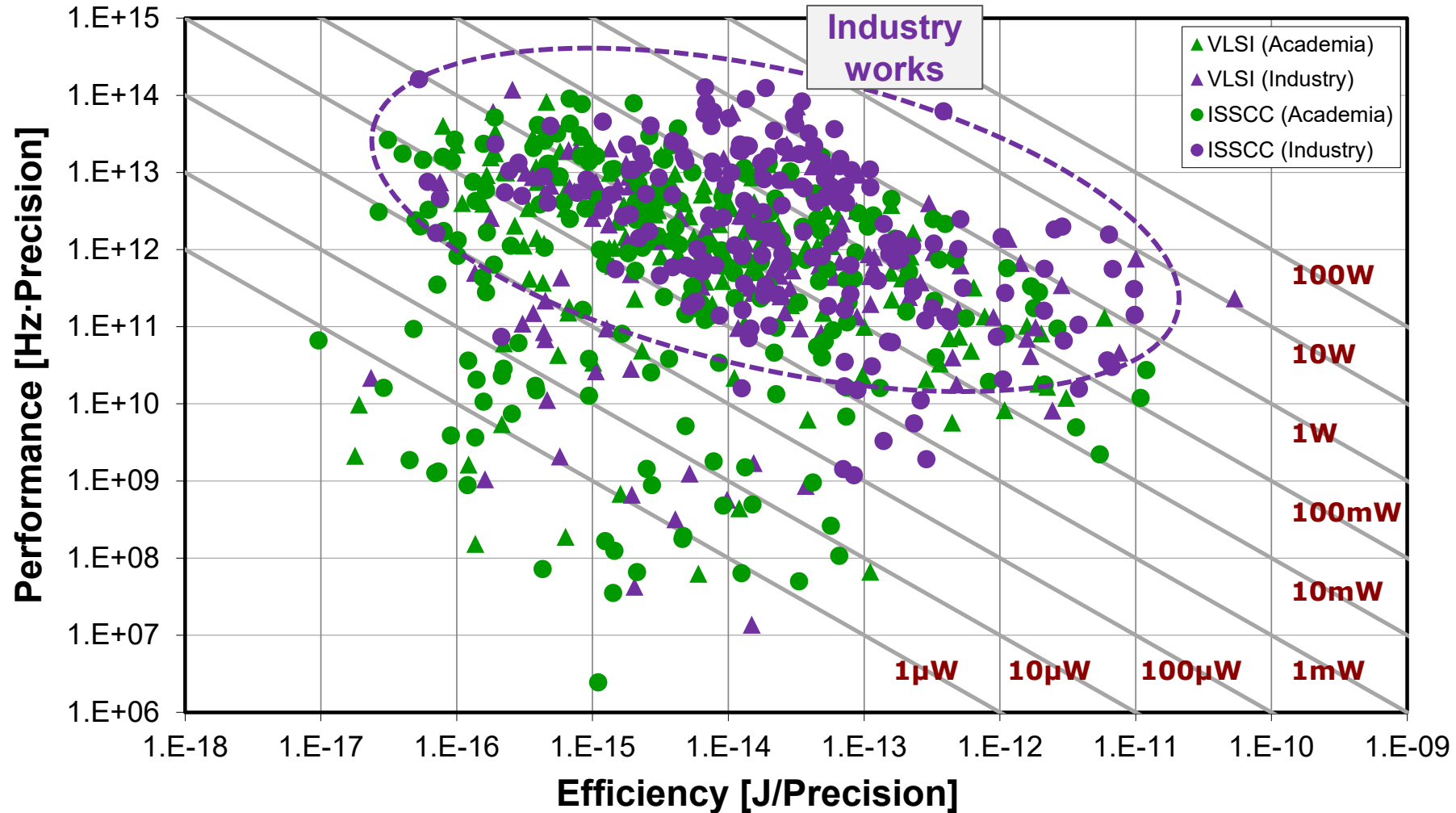

# Converter Papers to See This Year

---

- **Session 10 - Pipelined and Noise-Shaping ADCs:**
  - 10.1, 10.2 – high-speed pipelined ADCs
  - 10.4 – high-resolution two-step SAR ADC with predictive level-shifting
- **Session 17 - High-Speed Data Converter:**
  - 17.3 –high-speed direct-RF DAC
  - 17.4, 17.6 – digitally calibrated time-interleaved SAR ADCs
  - 17.8 – high-speed time-domain ADC

# References

---

1. W.R. Bennett, "Spectra of quantized signals," *Bell Syst. Tech. J.*, pp. 446-472, Jul. 1948.
2. Oppenheim and Schaffer, *Discrete-Time Signal Processing*, 2<sup>nd</sup> ed., Prentice Hall, 1998.
3. D. Gruber et al., "A 12b 16GS/s RF-sampling capacitive DAC for multi-band soft-radio base-station applications with on-chip transmission-line matching network in 16nm FinFET," in *ISSCC*, 2021.
4. B. Razavi, *Principles of Data Conversion System Design*, IEEE press, 1995.
5. M. Shinagawa, Y. Akazawa, and T. Wakimoto, "Jitter analysis of high-speed sampling systems," *JSSC*, no 1, 1990.
6. A.M. Abo and P. R. Gray, "A 1.5-V, 10-bit, 14.3-MS/s CMOS pipeline ADC," *JSSC*, Mar. 1999.
7. S.H. Lewis et al., "A 10-b 20-MS/s analog-to-digital converter," *JSSC*, Mar. 1992.
8. F. Kuttner, "A 1.2-V 10-b 20-MS/s nonbinary successive approximation ADC in 0.13- $\mu$ m CMOS," in *ISSCC*, 2002.
9. W. Liu et al., "A 600MS/s 30mW 0.13 $\mu$ m CMOS ADC array achieving over 60dB SFDR with adaptive digital equalization," in *ISSCC*, 2009.
10. C.-C. Liu et al., "A 10b 100MS/s 1.13mW SAR ADC with binary-scaled error compensation," in *ISSCC*, 2010.
11. H.-S. Lee, D.A. Hodges, and P.R. Gray, "A self-calibrating 15 bit CMOS A/D converter," *JSSC*, no. 6, 1984.
12. S.-U. Kwak, B.-S. Song, and K. Bacrania, "A 15-b 5-Msamples/s low spurious CMOS ADC," *JSSC*, Dec. 1997.
13. D. Fu et al., "A digital back-ground calibration technique for time-interleaved analog-to-digital converters," in *ISSCC*, 1998.
14. P. Kiss et al., "Adaptive digital correction of analog errors in MASH ADC's—Part II: Correction using test-signal injection," *TCAS-II*, Jul. 2000.

# References

---

15. J. Li and U.-K. Moon, "Background calibration techniques for multistage pipelined ADC's with digital redundancy," *TCAS-II*, Sept. 2003.
16. X. Wang et al., "A 12-bit 20-MS/s pipelined ADC with nested digital background calibration," in *CICC*, 2003.
17. Y. Chiu et al., "Least mean square adaptive digital background calibration of pipelined analog-to-digital converters," *TCAS-I*, Jan. 2004.
18. E.J. Siragusa and I. Galton, "A digitally enhanced 1.8V 15b 40MS/s CMOS pipelined ADC," in *ISSCC*, 2004.
19. J. McNeill et al., "Split ADC architecture for deterministic digital background calibration of a 16b 1MS/s ADC," in *ISSCC*, 2005.
20. Y.-S. Shu and B.-S. Song, "A 15b linear, 20MS/s, 1.5b/stage pipelined ADC digitally calibrated with signal-dependent dithering," in *VLSI*, 2006.
21. B. Murmann and B. Boser, "A 12b 75MS/s pipelined ADC using open-loop residue amplification," in *ISSCC*, 2003.
22. C. Tsang et al., "Background ADC calibration in digital domain," in *CICC*, 2008.
23. A. Panigada and I. Galton, "A 130mW 100MS/s pipelined ADC with 69dB SNDR enabled by digital harmonic distortion correction," in *ISSCC*, 2009.
24. B.D. Sahoo and B. Razavi, "A 12-bit 200-MHz CMOS ADC," *JSSC*, Sept. 2009.
25. E. Iroaga and B. Murmann, "A 12 b, 75 MS/s pipelined ADC using incomplete settling," in *VLSI*, 2006.
26. J.P. Keane et al., "Digital Background Calibration for Memory Effects in Pipelined Analog-to-Digital Converters", *TCAS-I*, Mar. 2006.



# References

---

27. A. Ali et al., "A 12-b 18-GS/s RF sampling ADC with an integrated wideband track-and-hold amplifier and background calibration," in *ISSCC*, 2020.
28. W. Liu, P. Huang, and Y. Chiu, "A 12-bit 50-MS/s 3.3-mW SAR ADC with background digital calibration," in *CICC*, 2012.
29. R.H. Walden, "Analog-to-digital converter survey and analysis," *IEEE J. Select. Areas Comm.*, Apr. 1999.
30. R. Schreier and G.C. Temes, *Understanding Delta-Sigma Data Converters*, Wiley, 2005.
31. B. Murmann, "ADC Performance Survey 1997-2022," [Online]: [www.stanford.edu/~murmman/adcsurvey.html](http://www.stanford.edu/~murmman/adcsurvey.html).