
ISSCC 2023 Tutorials

All-digital PLLs From Fundamental Concepts to Future Trends

Akihide Sai
Toshiba Corporation


Live Q&A Session: Feb. 19, 2023,

Self-introduction

- **Akihide Sai**
- M.D. in EE from Waseda Univ., Tokyo, 2004
- R&D Fellow with Toshiba Corp.
 - Now within LiDAR R&D Group as Project Leader
 - 19 years in Toshiba Corp.
- Interests in high-performance mixed-signal circuit
 - Digital/analog phase-locked loops(PLLs)
 - Low power transceivers
 - Automobile LiDAR SoCs



Motivation of Tutorial

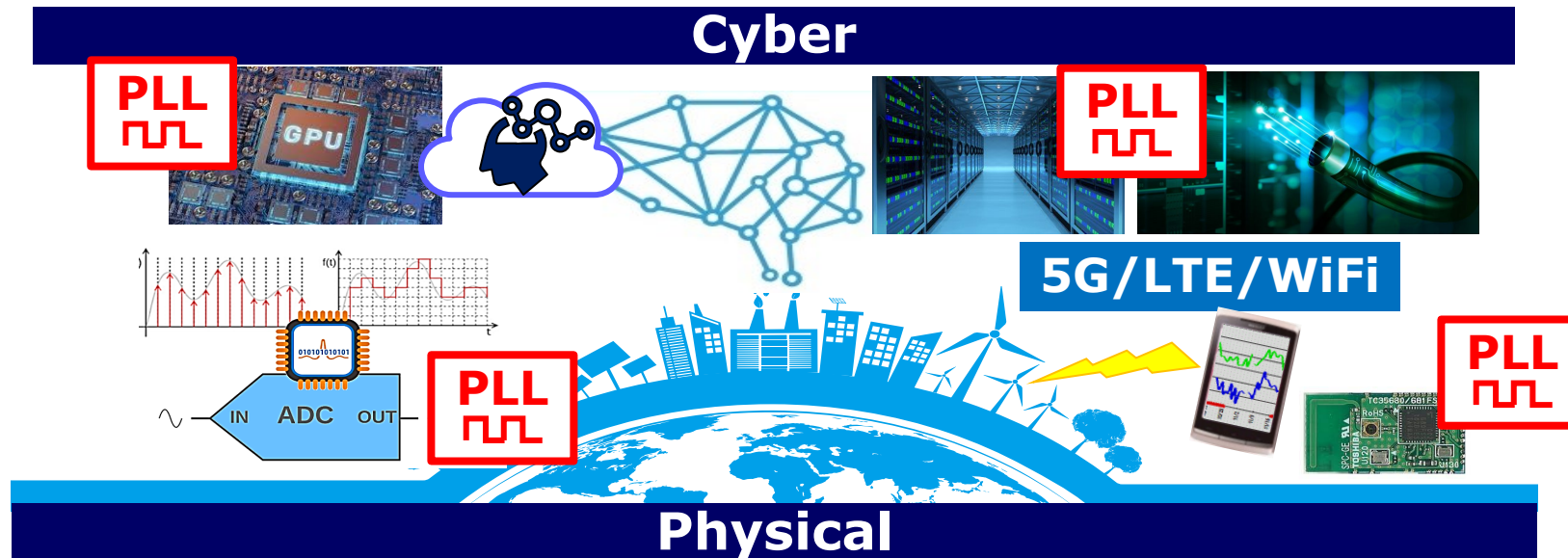

- Recently, **Phase-Locked Loop (PLL)** has become more and more indispensable. Almost all components for Cyber-Physical IoT systems (GPU/CPU, data center, wireline/wireless...) need PLL for system clocking, data recovery, RF mixing!
- First of all, grasp basic of frequency synthesis including PLL, and then analyze the principle and benefit of **Digital-PLL**, with the technique evolution trend.
- Finally, try to analyze and predict the **future evolution trend**.

Outline


- Background of Frequency Synthesis
 - Design Challenges for Jitter, Phase noise, Lock up
- Basic All-Digital PLL
 - Fractional-N Operation, Spurious Tones
 - Digital Implementation
 - Time-to-Digital Converter (TDC)
- Advanced Digital PLL
 - Basic and Fundamentals
 - High performance TDCs and Fractional Spur Cancellation Techniques
 - Performance Trends Analysis
- Future Trend Prediction
- Summary & conclusions

Outline


- Background of Frequency Synthesis
 - Design Challenges for Jitter, Phase noise, Lock up
- Basic All-Digital PLL
 - Fractional-N Operation, Spurious Tones
 - Digital Implementation
 - Time-to-Digital Converter (TDC)
- Advanced Digital PLL
 - Basic and Fundamentals
 - High performance TDCs and Fractional Spur Cancellation Techniques
 - Performance Trends Analysis
- Future Trend Prediction
- Summary & conclusions

Frequency synthesis: Applicative constraints


Mixing

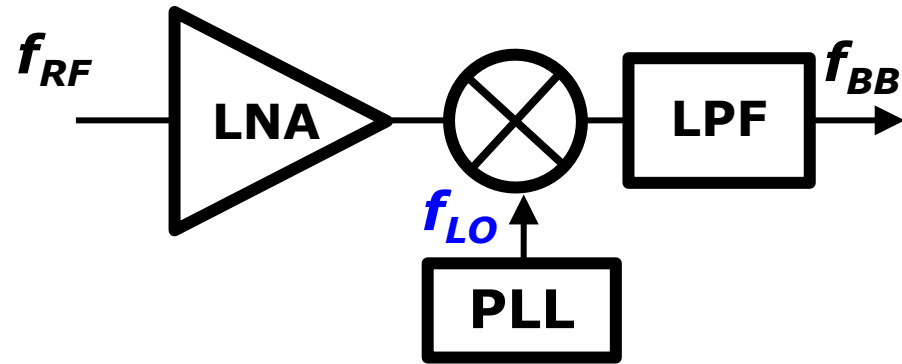


Low noise in frequency domain

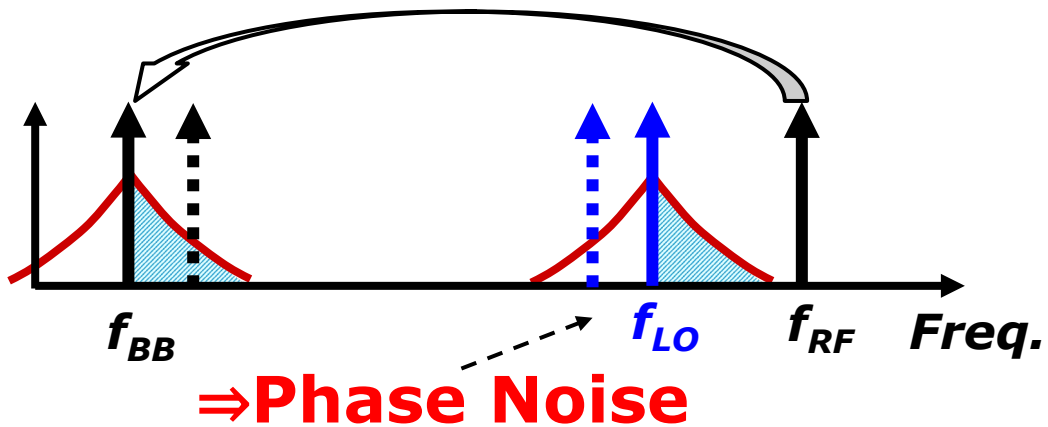

Sampling

 

Low noise in time domain

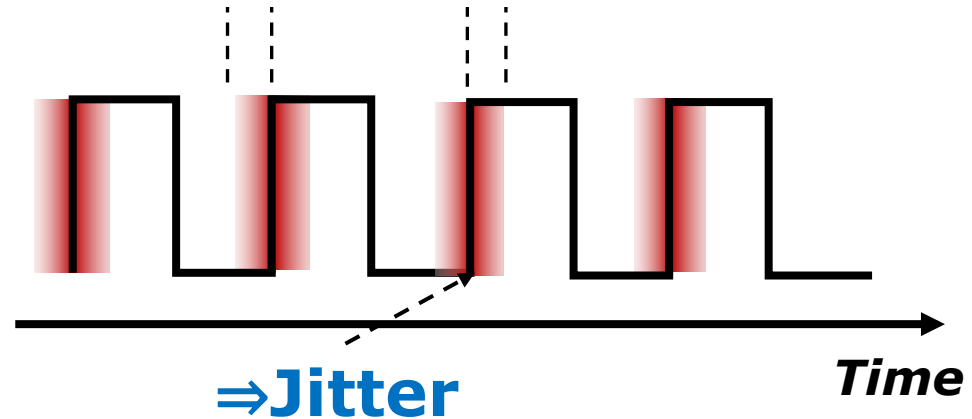


Period Jitter and Frequency Noise

- **Period Jitter** : 1-cycle fluctuation expressed in **time domain**
- **Frequency Noise** : 1-cycle fluctuation expressed in **frequency domain**

Period jitter [sec rms]


Frequency Noise [dBc/Hz]

 


Phase Jitter and Phase Noise

- **Phase Jitter** : long-term fluctuation expressed in **time domain**
- **Phase Noise** : long-term fluctuation expressed in **phase domain**

Phase jitter [sec rms]

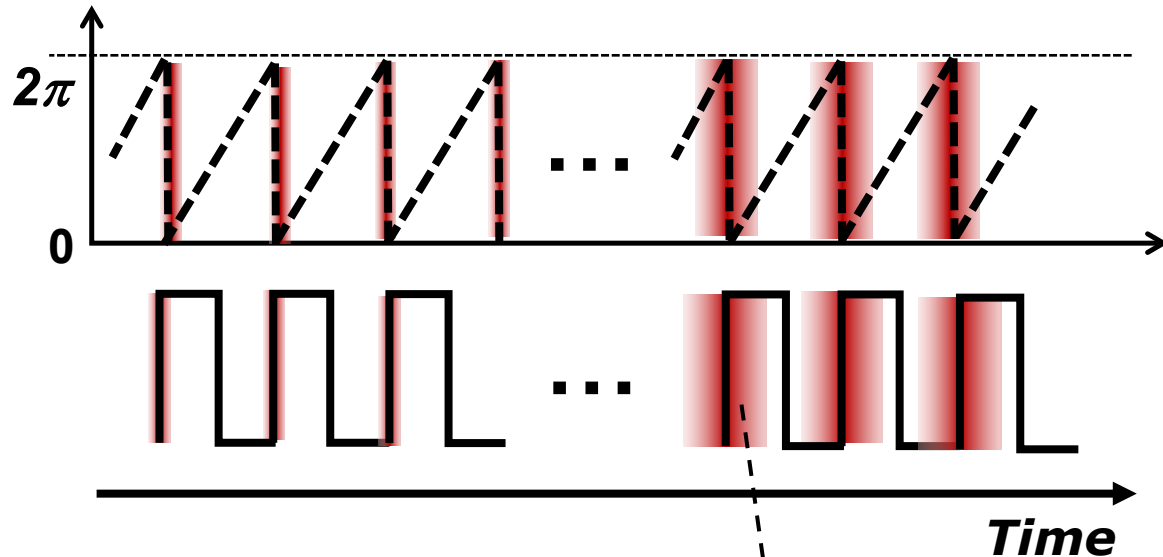


Phase Noise [dBc/Hz]

 

$$\text{Phase jitter} = \frac{1}{2\pi f_{OUT}} \sqrt{\int_{f_a}^{f_b} \text{PSD}[\phi_{OUT}] df} \quad [\text{sec}_{rms}]$$


Free-running Oscillator

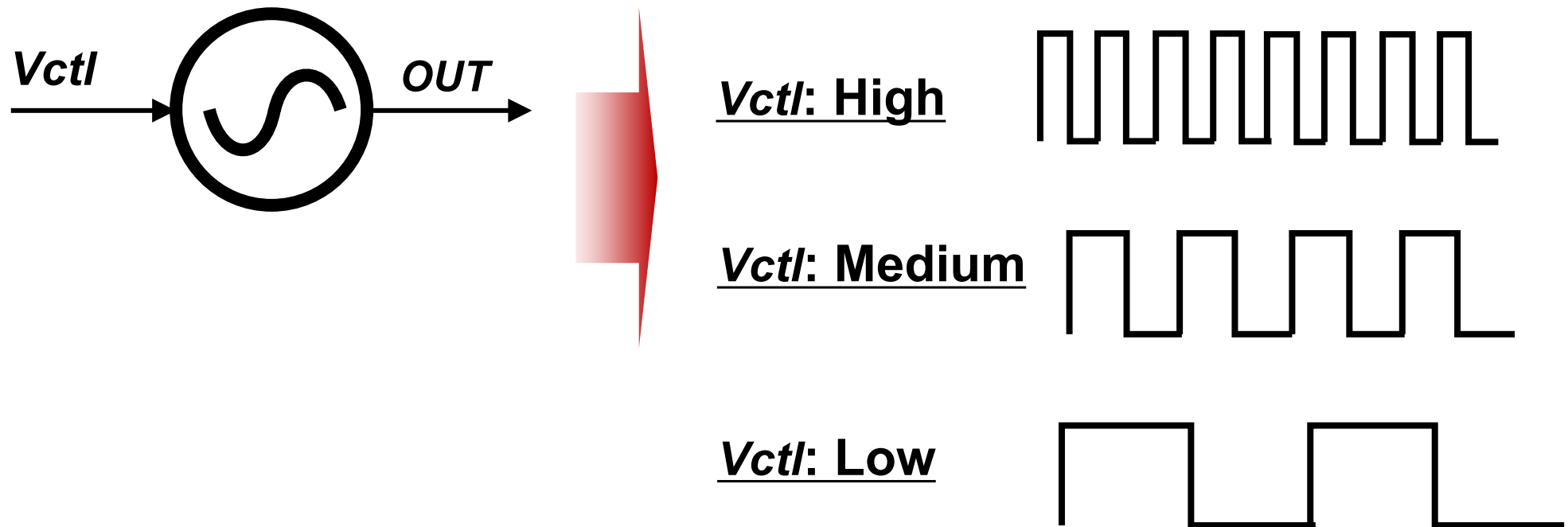- Open-loop free-running oscillator is most simple clock generation
- **V**oltage **C**ontrols **O**scillator Frequency → **VCO (Voltage Controlled Oscillator)**



Free-running VCO


 
- Two major VCO types, LC/Ring, have critical design trade-off



[Mitteregger, ISSCC'06]

LC VCO for CLK PLL


14bit $\Delta\Sigma$ ADC

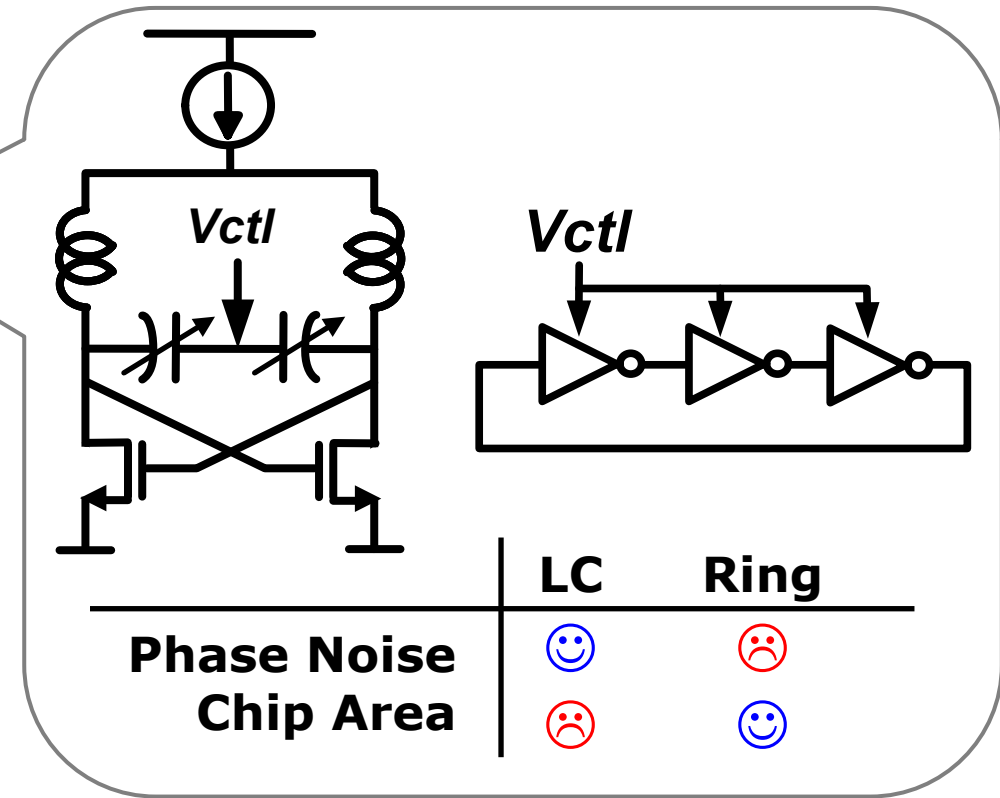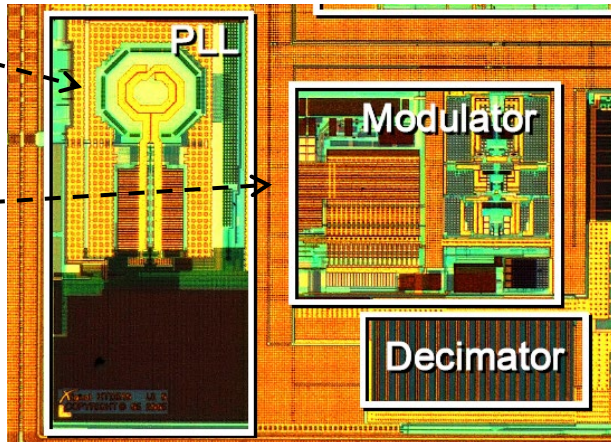

LC VCO for sampling clock may larger than ADC itself !!


Issues with Free-running Oscillator

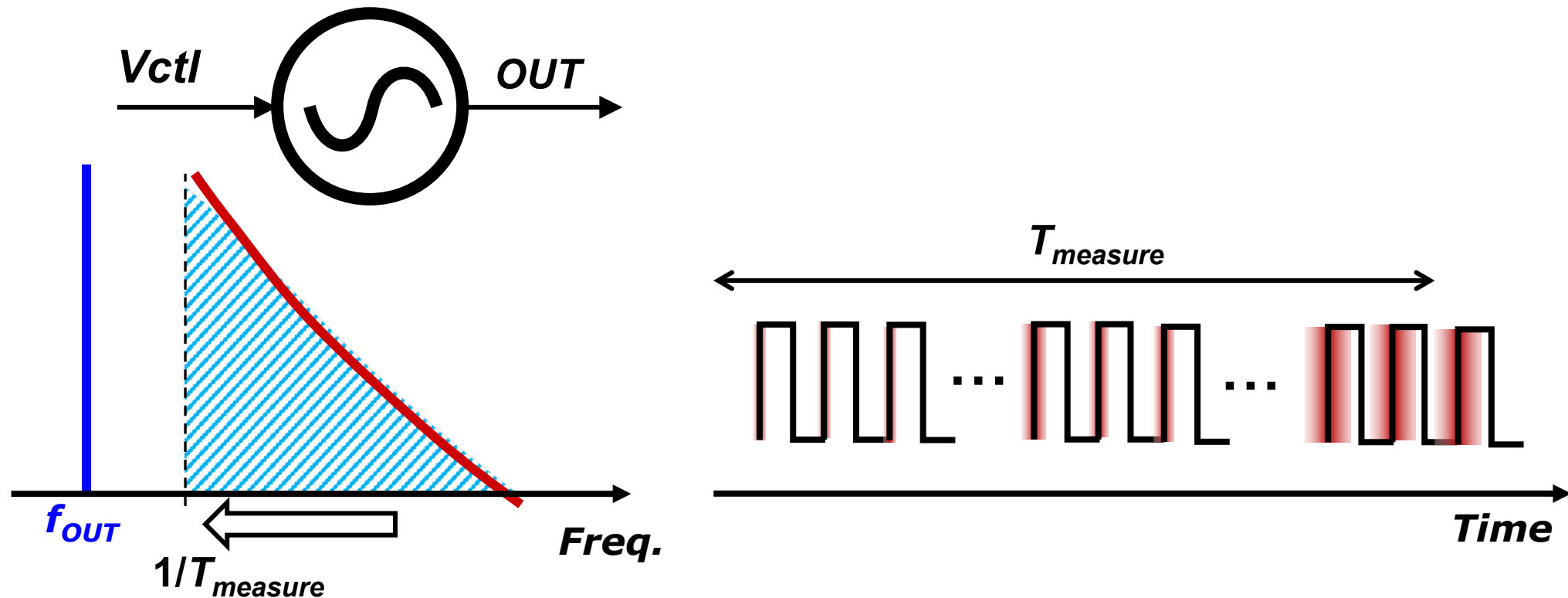- Poor phase noise and jitter performance of VCO
 - No feedback controls enable jitter to diverge to infinity!




Issues with Free-running Oscillator

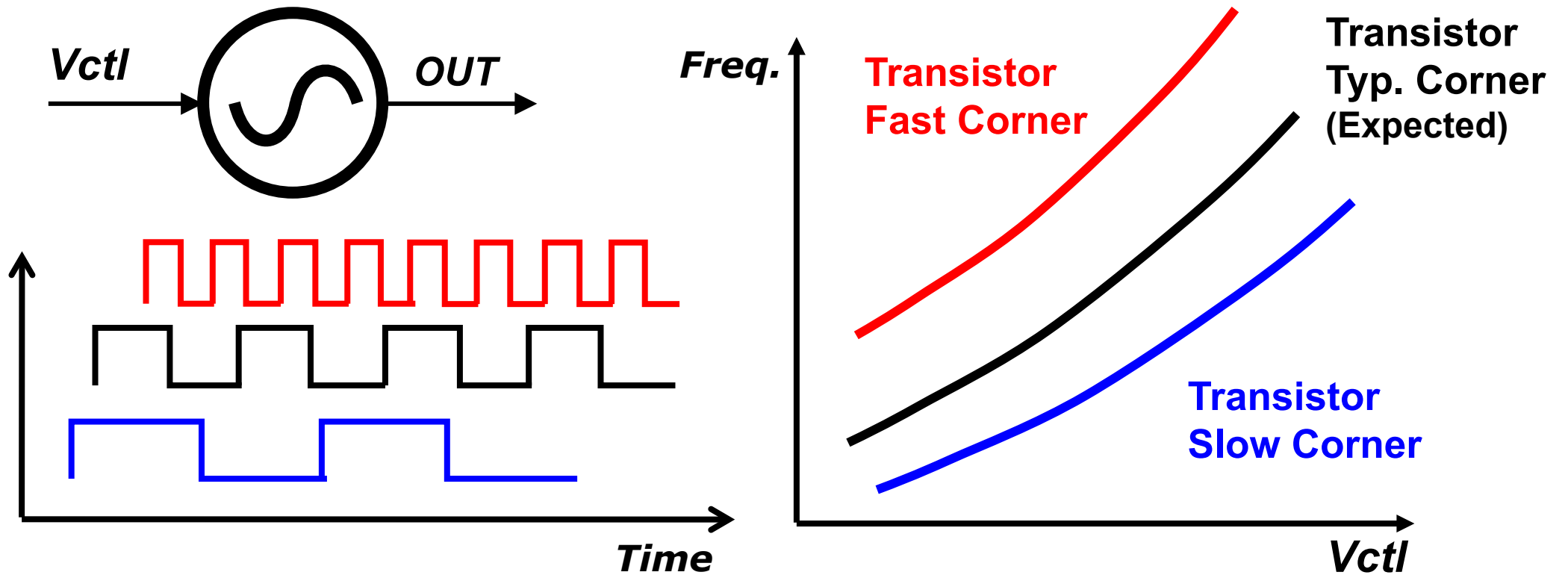- Poor frequency accuracy
 - Oscillation frequency can easily change with PVT variation





Amplifier: How to Create Accurate Output?

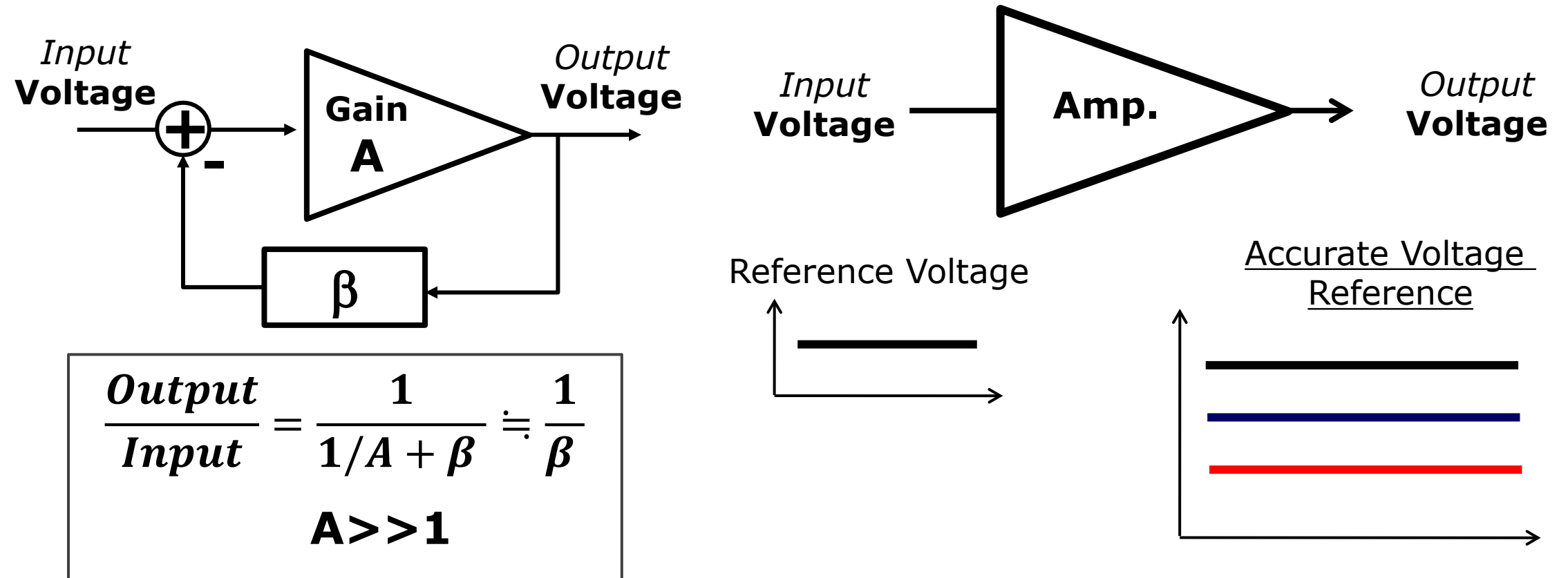- Negative feedback can generate accurate output in voltage domain
 - Key points are **large feedforward gain A** , and **feedback factor β**





PLL: How to Create Accurate Clock?

  - **Phase-domain negative feedback** can generate accurate output ?
 - **'Accurate'** means low phase noise and high frequency accuracy





$$\frac{\text{Output}}{\text{Input}} = \frac{1}{1/A + \beta} \doteq \frac{1}{\beta}$$

$A \gg 1$

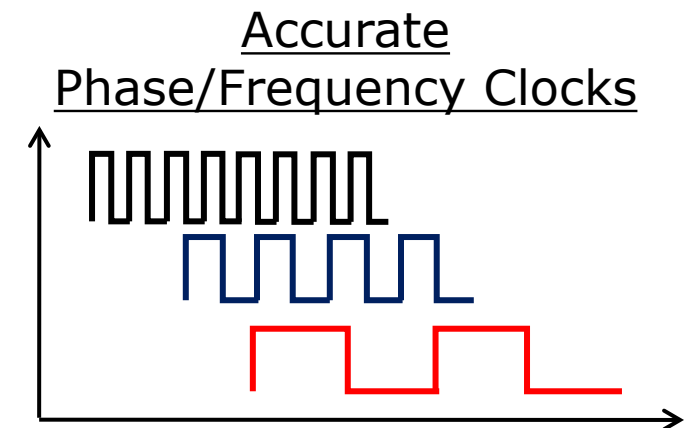 


PLL: How to Create Accurate Clock?

 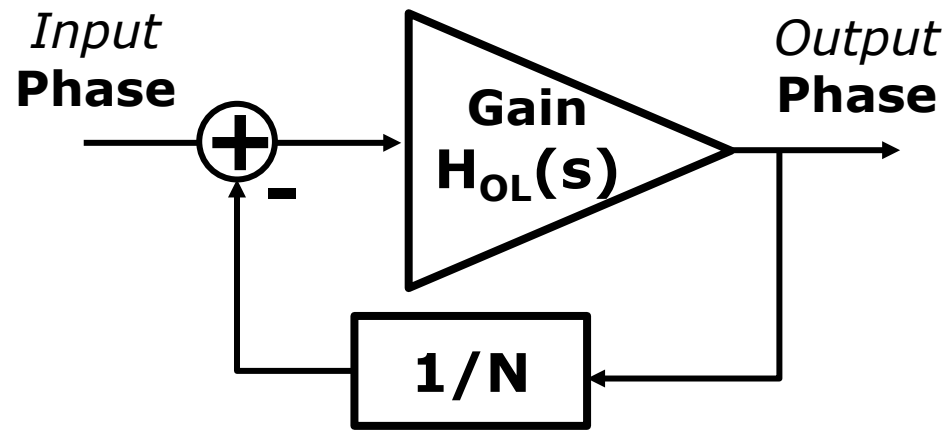- Feedback is constrained to clock division ratio
- Feedforward gain over the frequency spectrum determines PLL performance




$$\frac{\text{Output}}{\text{Input}} = \frac{1}{1/H_{OL}(s) + 1/N} \approx N$$

$H_{OL}(s) \gg 1$ **N: Divider Ratio**

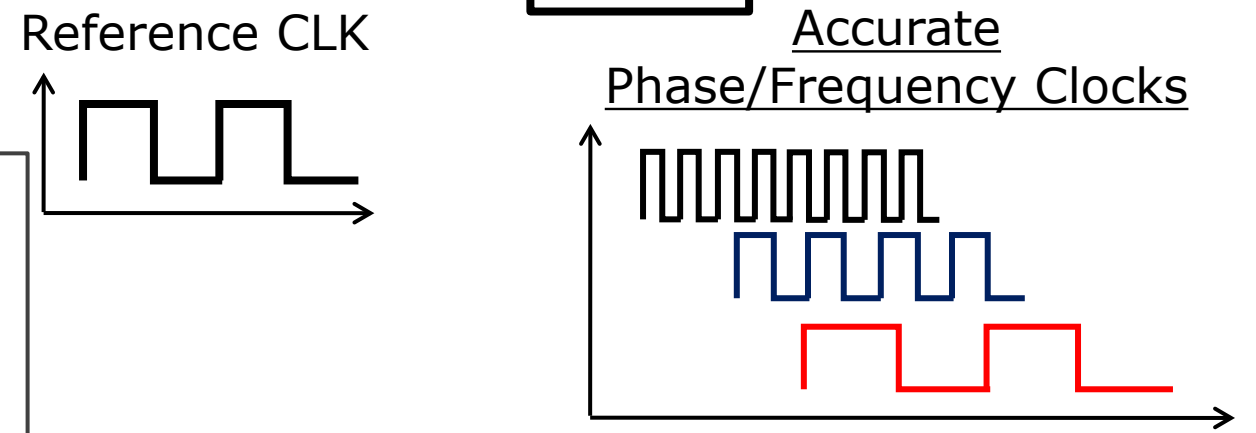



Type-I Analog PLL

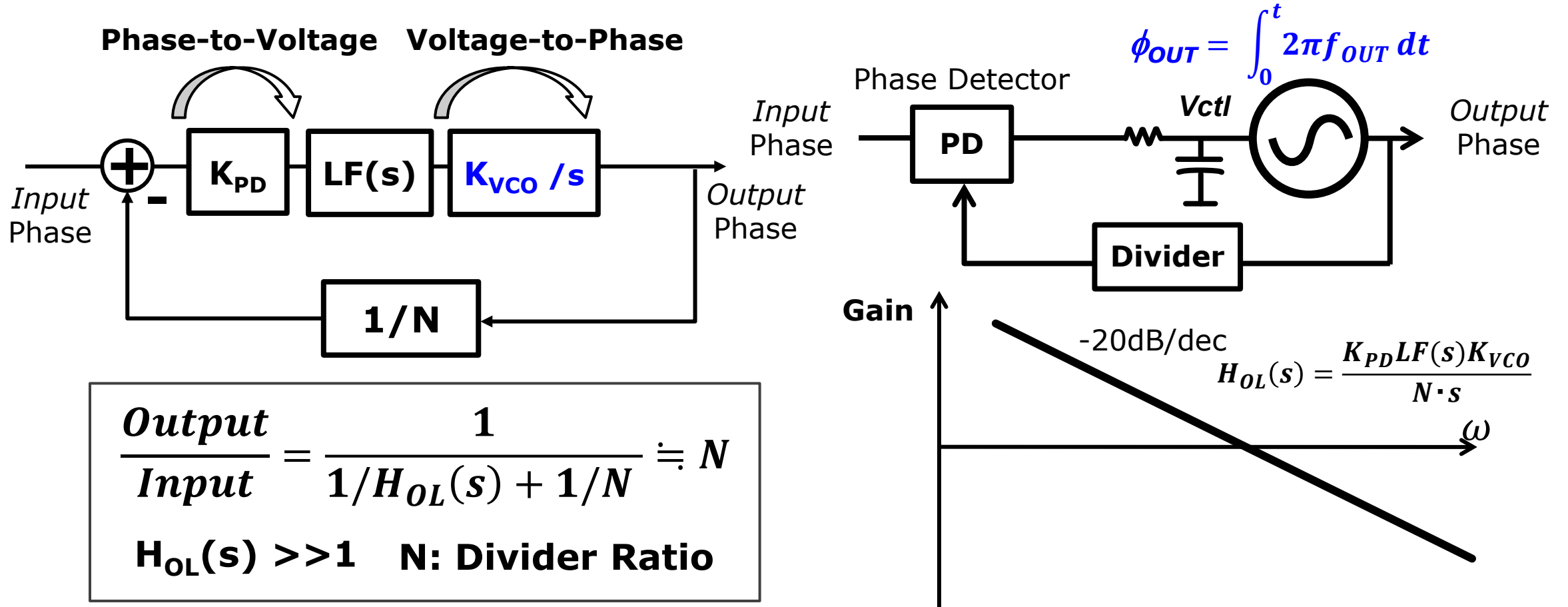- Type-I PLL has one integrator of VCO frequency-to-phase conversion




Type-I Analog PLL

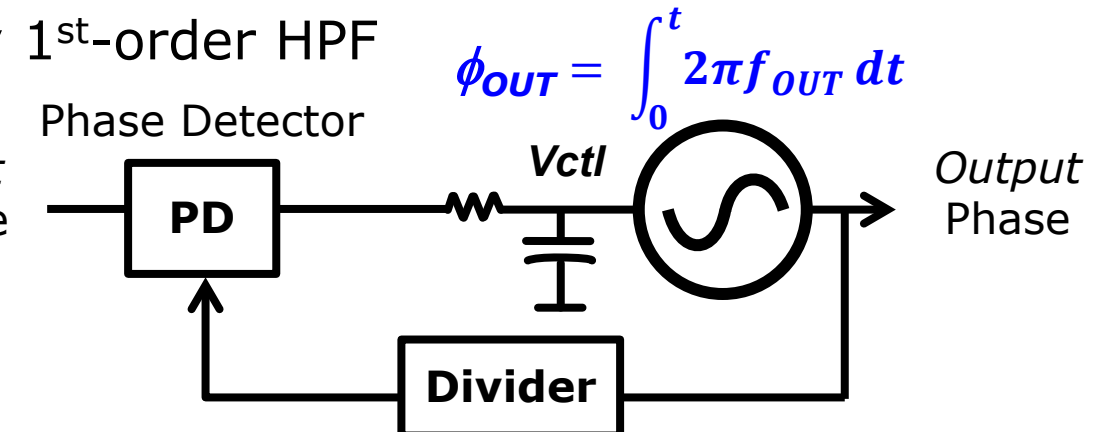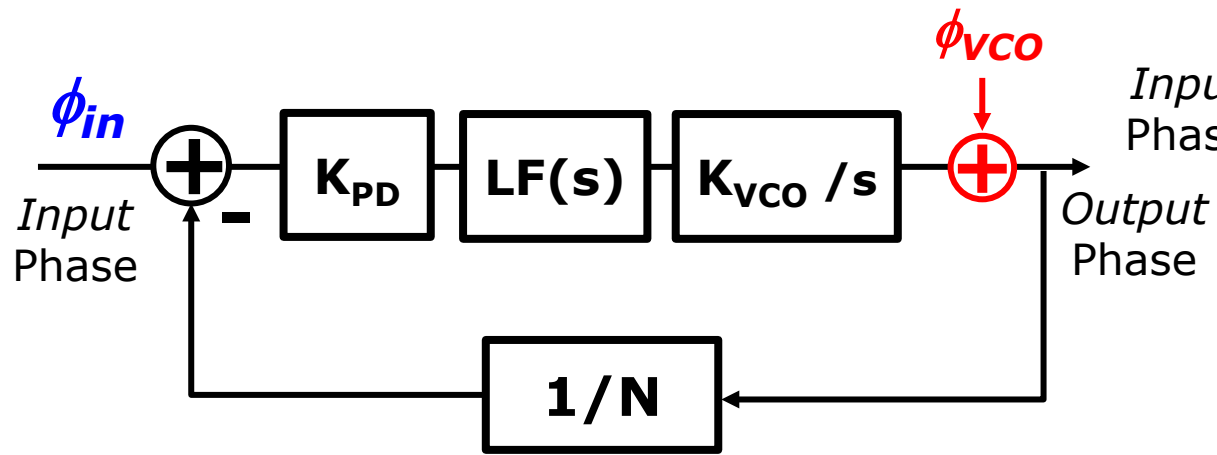- PLL loop bandwidth(BW) is determined by unity gain frequency of $H_{OL}(s)$
- Type-I PLL suppress VCO phase noise by 1st-order HPF




Signal Transfer Function (STF)	Noise Transfer Function (NTF)
$\frac{\phi_{OUT}}{\phi_{in}} = \frac{1}{1 + H_{OL}(s)}$	$\frac{\phi_{OUT}}{\phi_{VCO}} = \frac{N \cdot H_{OL}(s)}{1 + H_{OL}(s)}$

 


Type-II Analog PLL

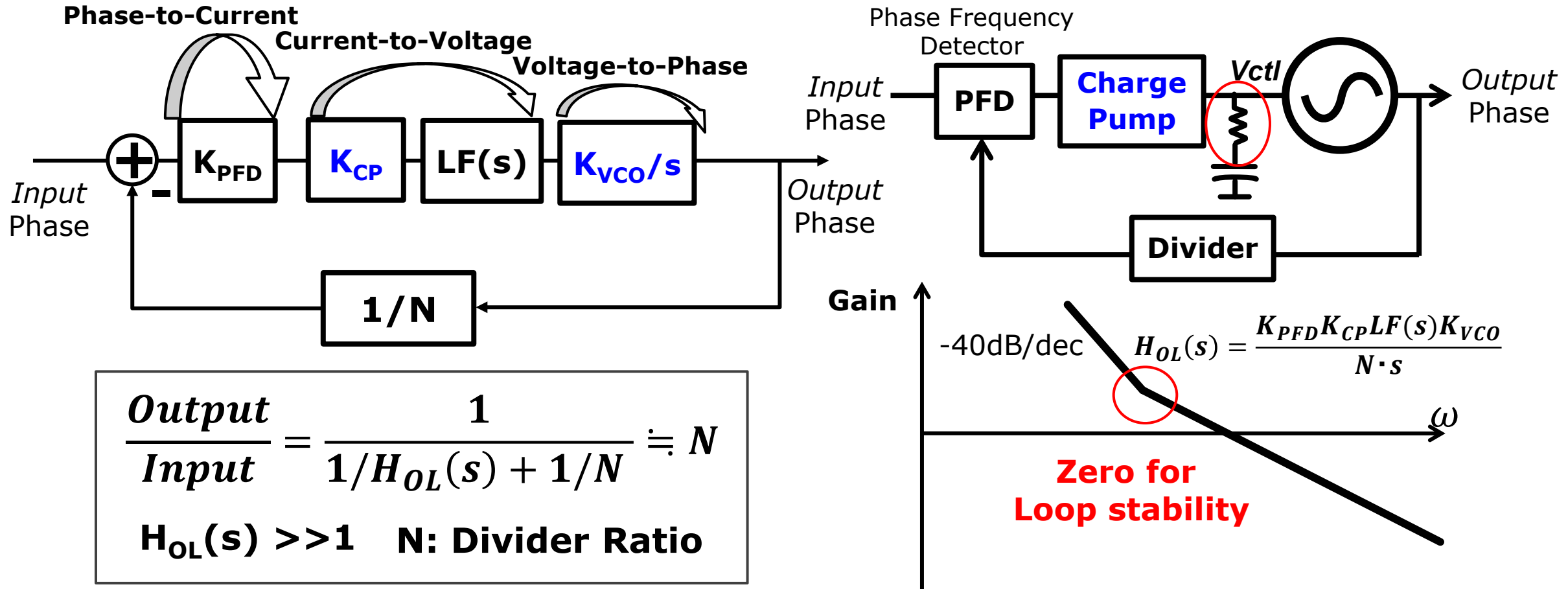- Type-II PLL has additional integrator of charge pump and loop filter




Type-II Analog PLL

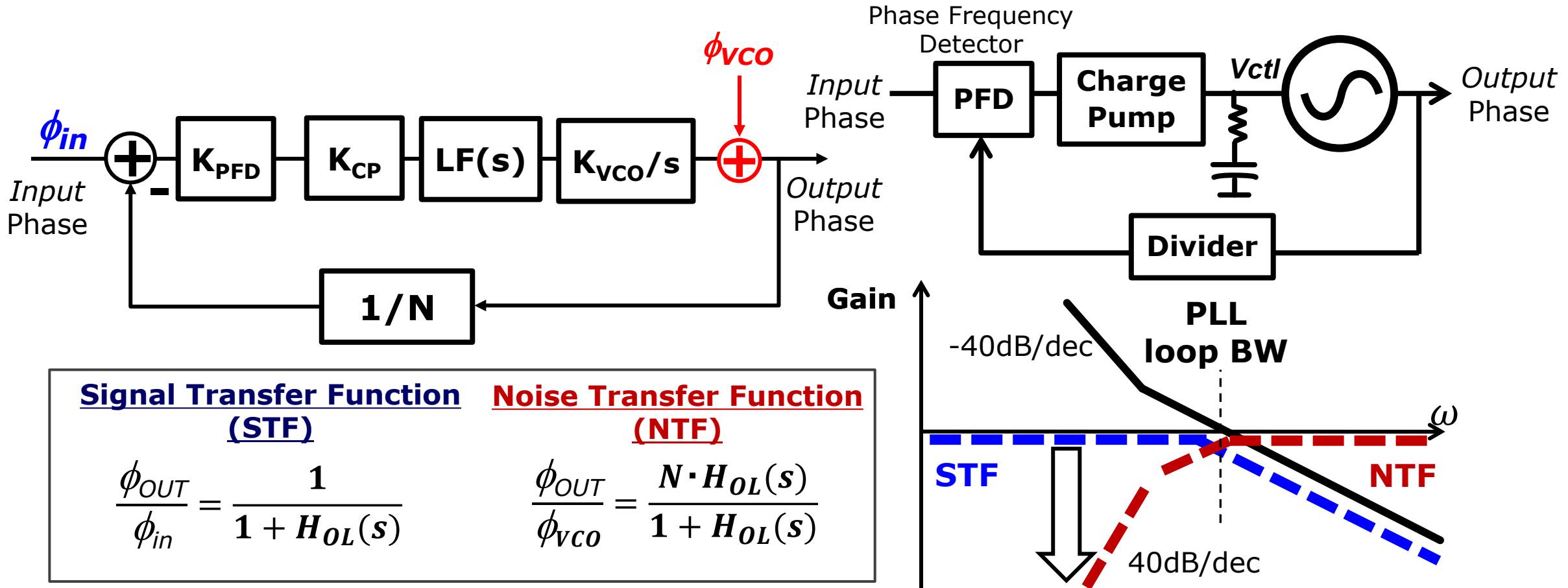- Type-II PLL suppresses VCO phase noise by 2nd-order HPF



Loop BW Design Consideration (1/3)

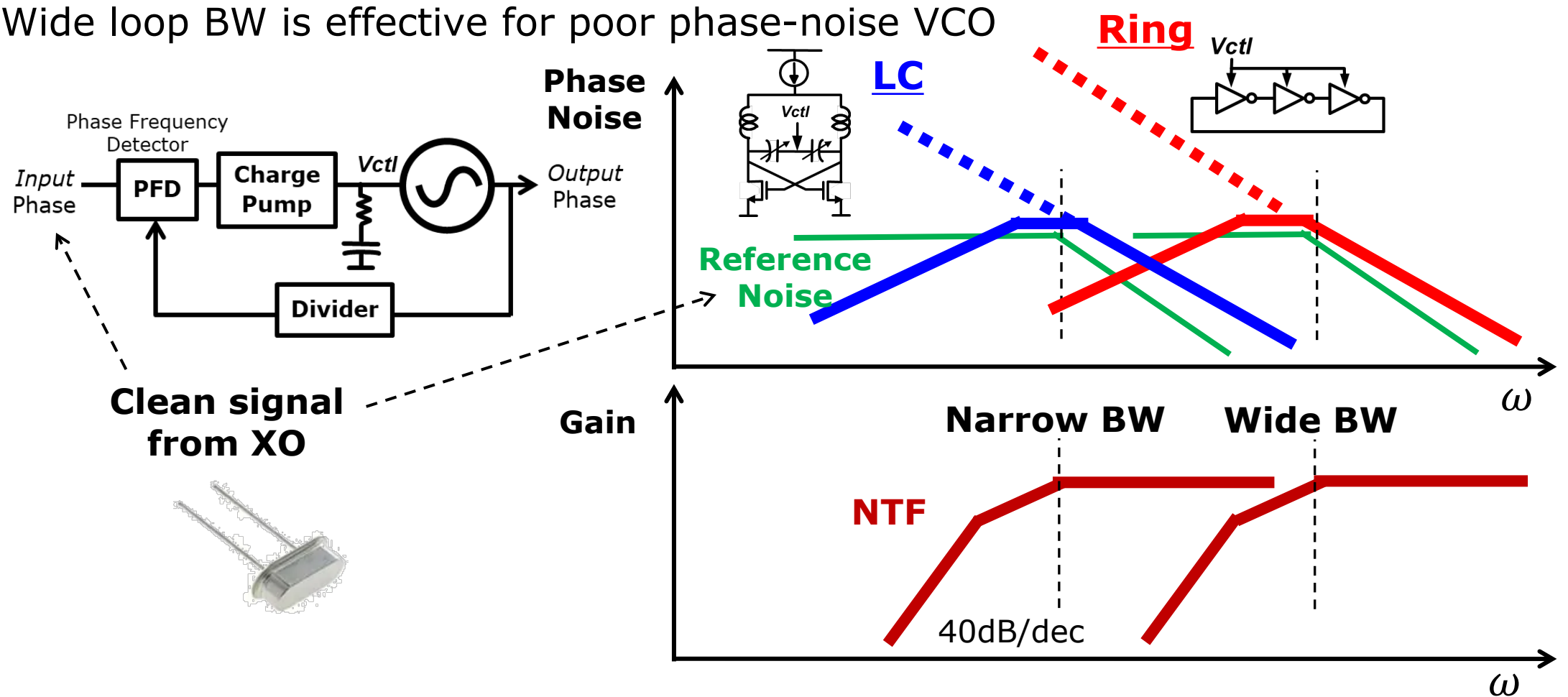
- Wide loop BW is effective for poor phase-noise VCO




PLL Jitter Figure-of-Merit(FoM)

□ Definition
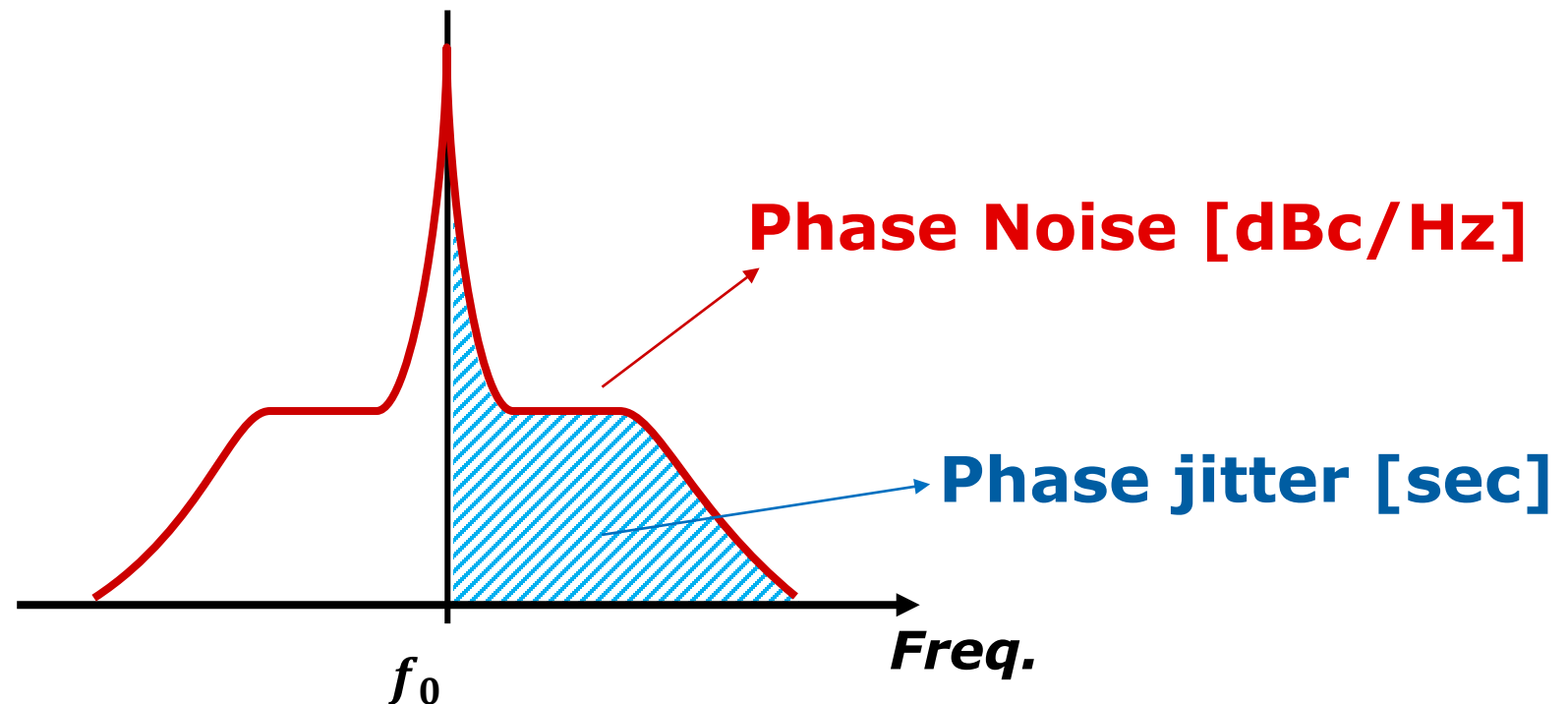
$$FOM_{jitter} = 10\log_{10} \left[\left(\frac{\text{RMS jitter}}{1\text{sec}} \right)^2 \left(\frac{\text{Power}}{1\text{mW}} \right) \right] \quad [\text{dB}]$$




PLL Performance Trend (~2005)

 



Loop BW Design Consideration (2/3)

Clock Data Recovery

Noisy Reference

 


Dynamic Voltage and Frequency Scaling

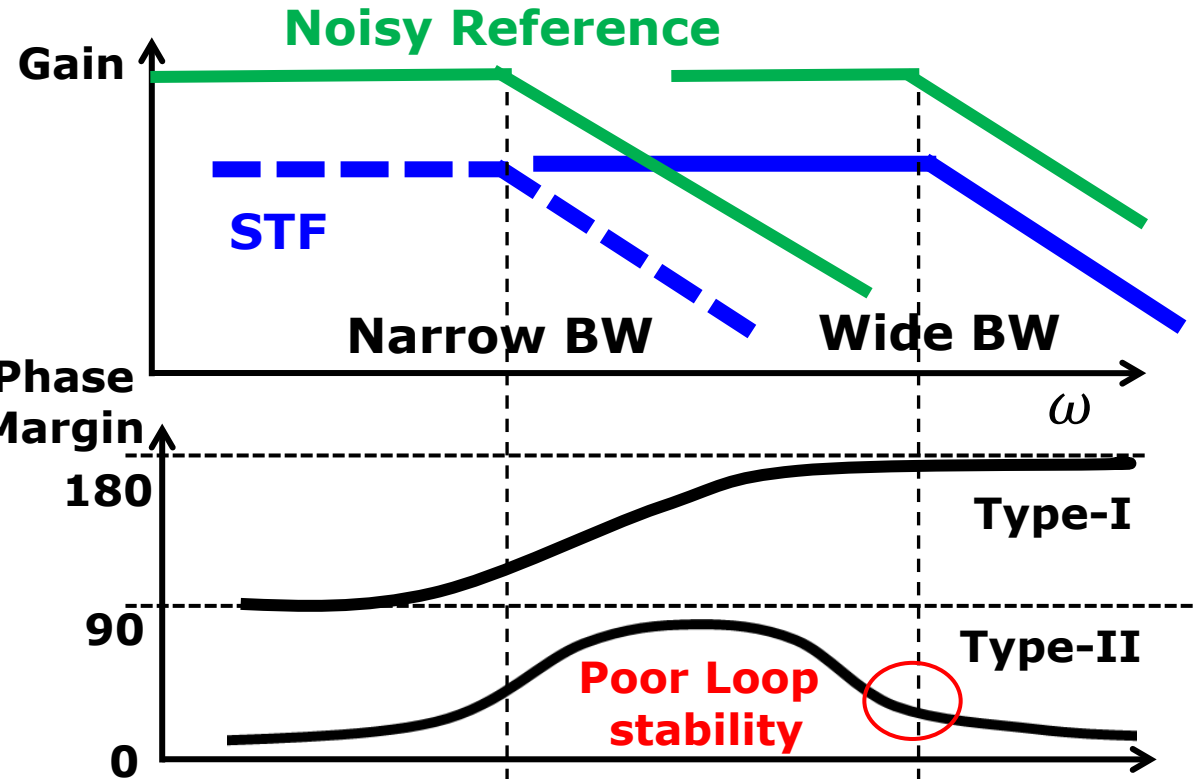 

- Narrow-loop-BW PLL can behave as noise filter for dirty input signal
- Lock-up responsivity is proportional to loop BW
- Type-I has better stability than that of type-II PLL


Amplifier Design Trade-off

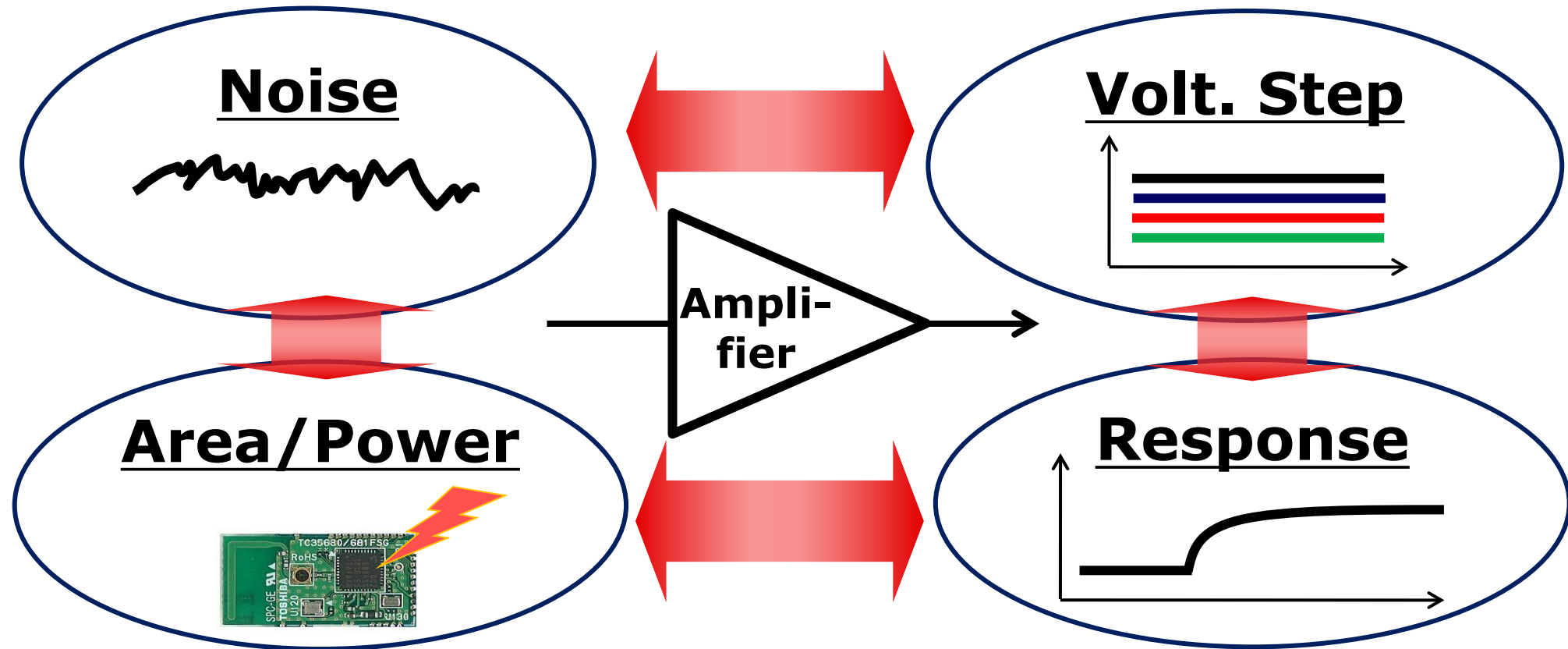- Key factors are **feedforward gain, gain BW, feedback factor.**




PLL Design Trade-off

 - Key factors are **loop gain & BW, Type-I/II & VCO selection.**





PLL Performance Trend (~2022)

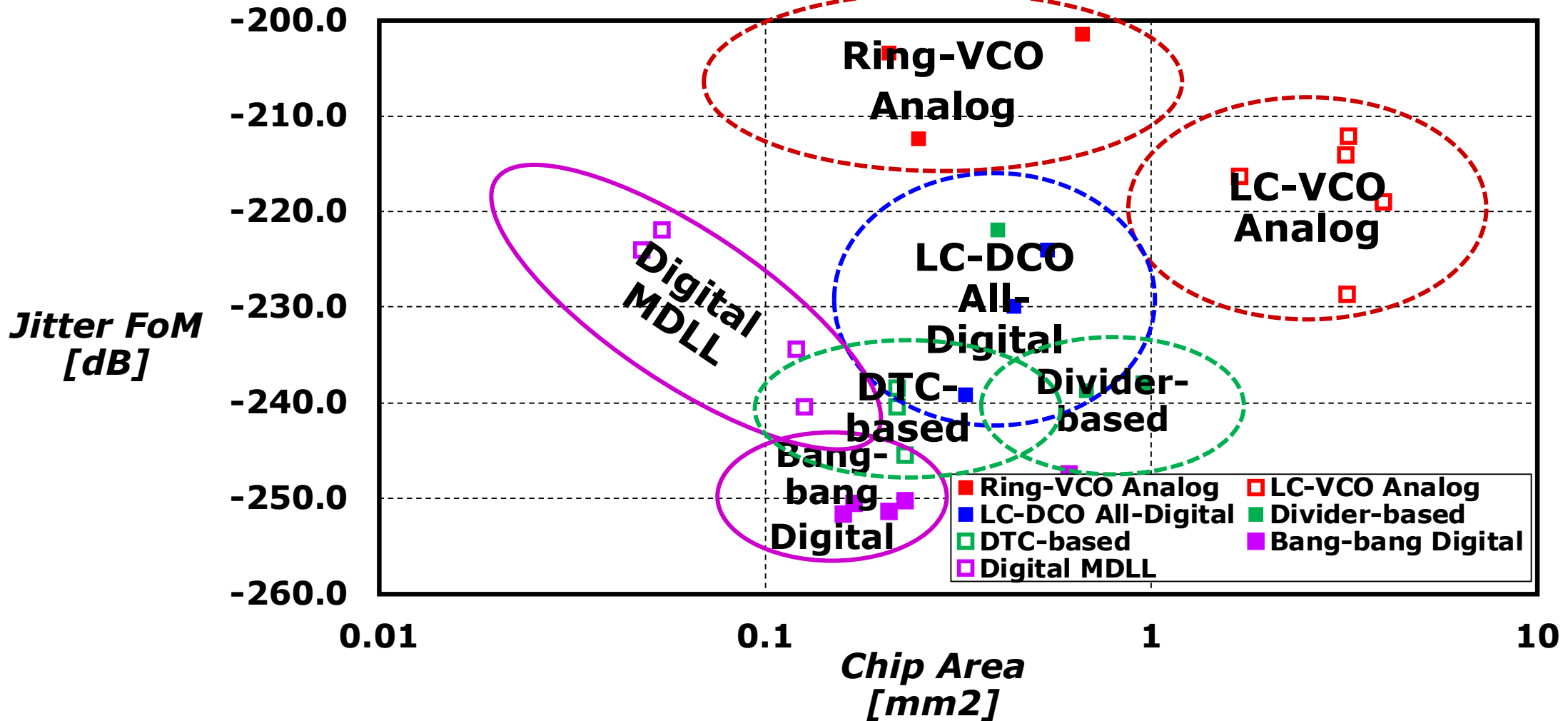


Outline

- Background of Frequency Synthesis
 - Design Challenges for Jitter, Phase noise, Lock up
- Basic All-Digital PLL
 - Fractional-N Operation, Spurious Tones
 - Digital Implementation
 - Time-to-Digital Converter (TDC)
- Advanced Digital PLL
 - Basic and Fundamentals
 - High performance TDCs and Fractional Spur Cancellation Techniques
 - Performance Trends Analysis
- Future Trend Prediction
- Summary & conclusions

 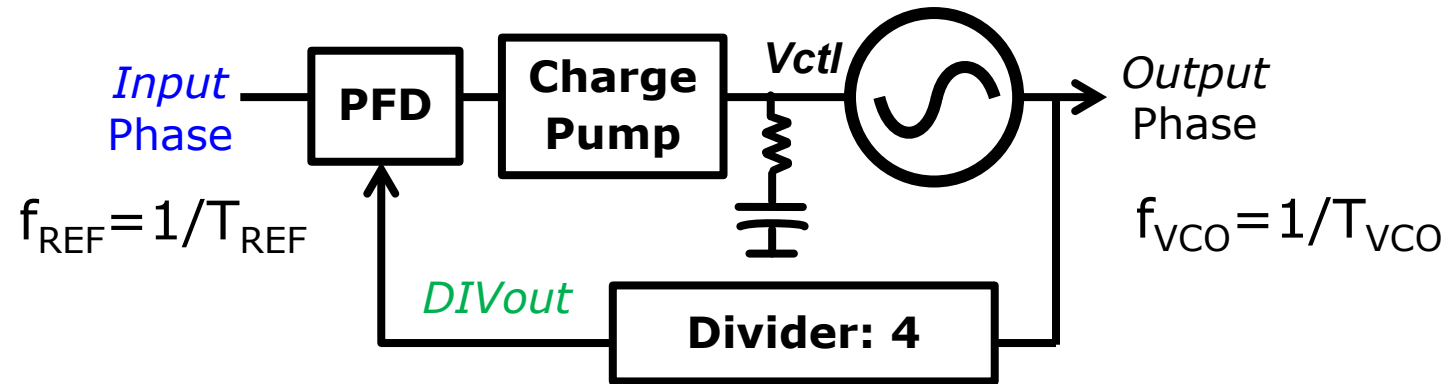Integer-N vs Fractional-N Operation (1/2)




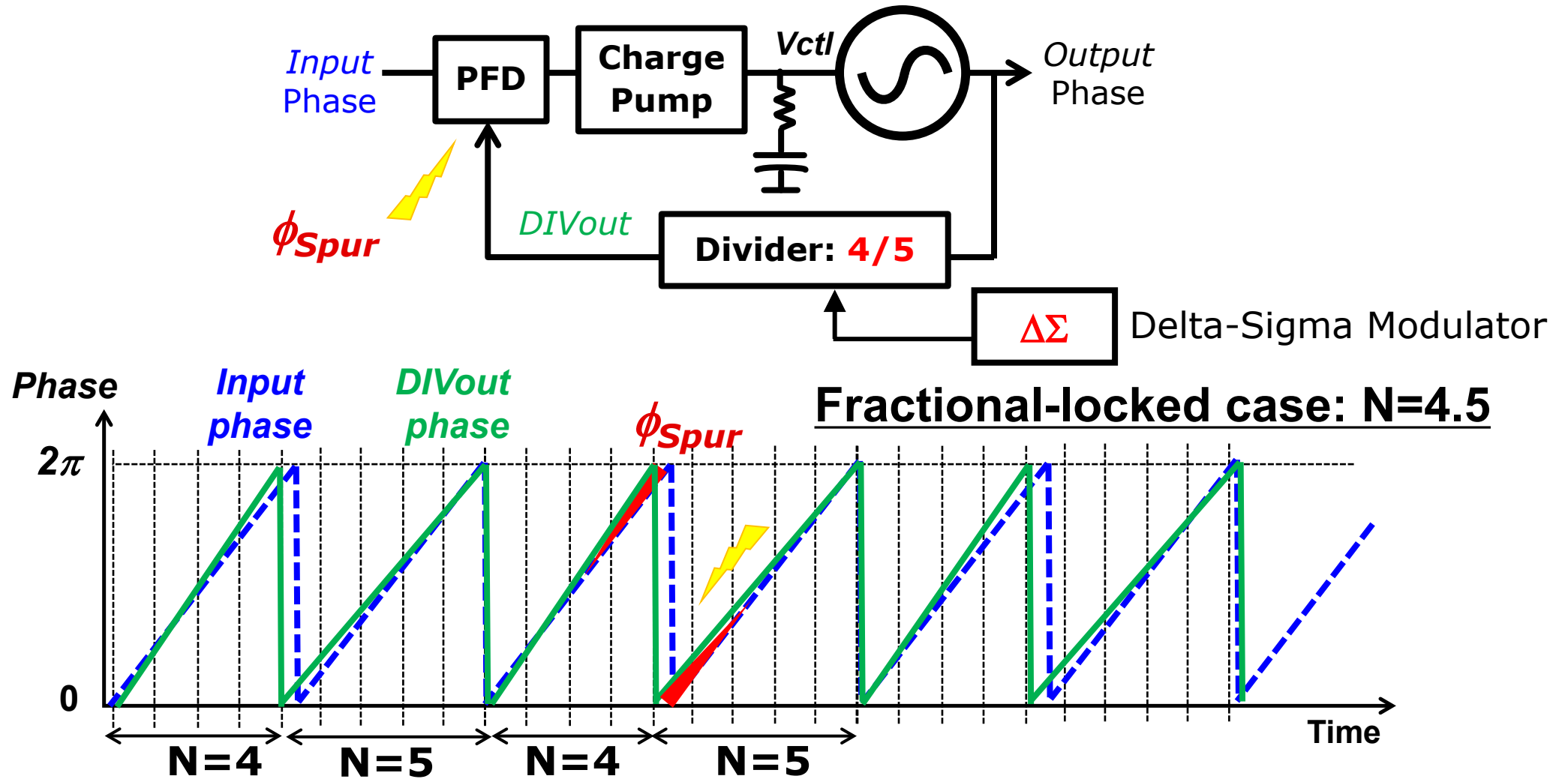Integer-N vs Fractional-N Operation (2/2)



Loop BW Design Consideration (3/3)

 
- Narrow loop BW is effective for fractional spurs
 - However, **around 10kHz-cut-off analog filter is required**, if spur frequency and attenuation are 100kHz and 20dB, respectively



Outline

- Background of Frequency Synthesis
 - Design Challenges for Jitter, Phase noise, Lock up
- **Basic All-Digital PLL**
 - Fractional-N Operation, Spurious Tones
 - **Digital Implementation**
 - Time-to-Digital Converter (TDC)
- Advanced Digital PLL
 - Basic and Fundamentals
 - High performance TDCs and Fractional Spur Cancellation Techniques
 - Performance Trends Analysis
- Future Trend Prediction
- Summary & conclusions



Innovation: All-Digital PLL

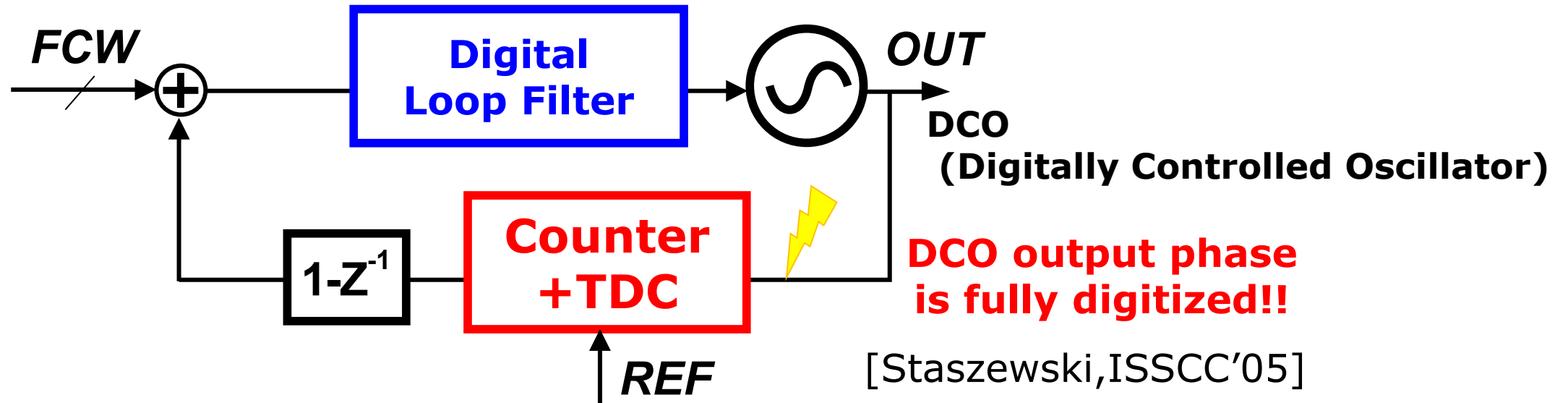

- ❑ **Free from Analog-filter and Divider**
- ❑ **Great benefit from CMOS scalability**
 - Chip-area and Power shrinking, Low development cost
 - Robustness to PVT variation

All-Digital PLL: Operation

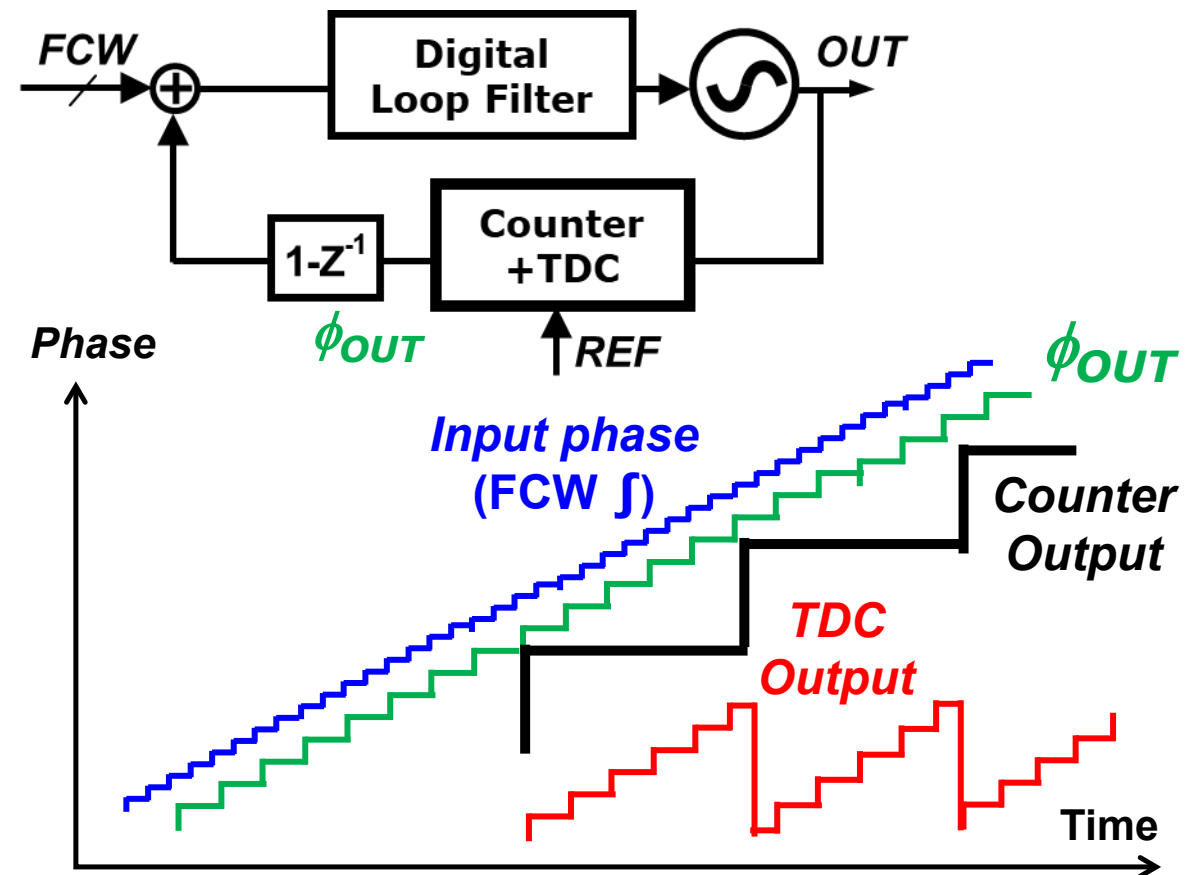
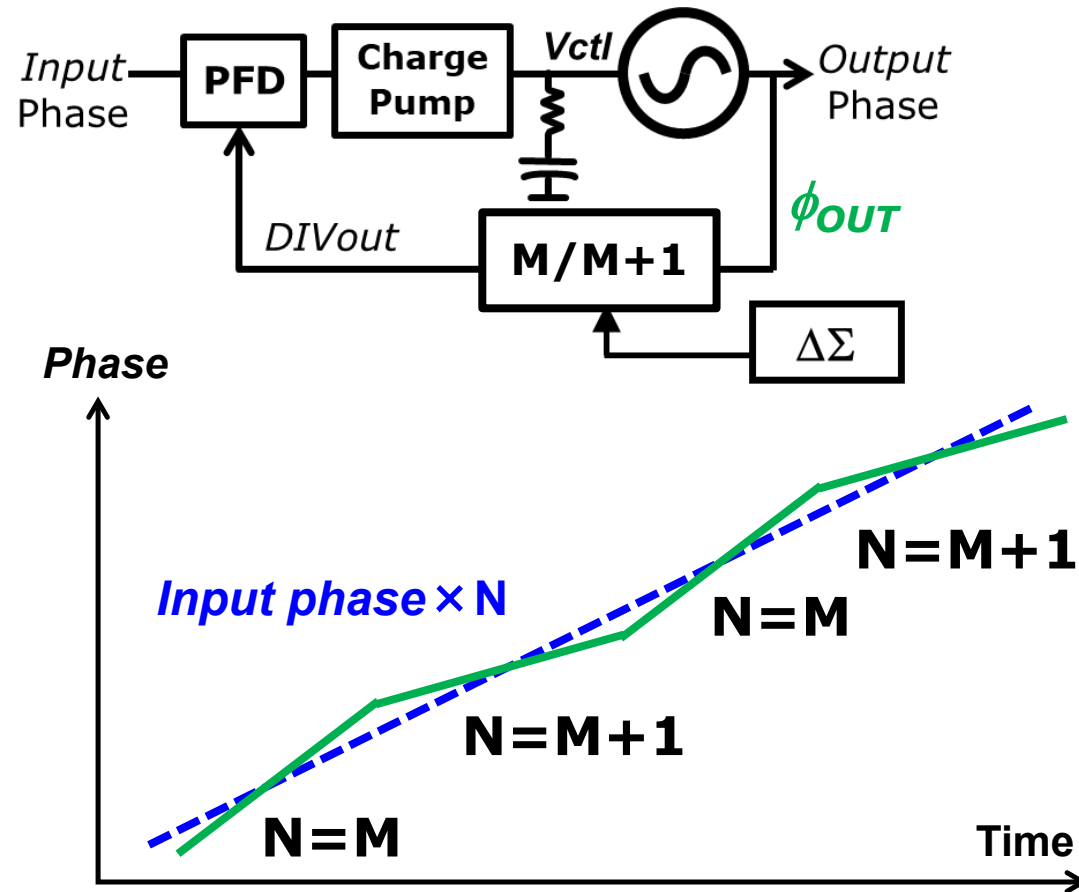
- DCO phase quantization of TDC much mitigates spur periodicity



Outline

- Background of Frequency Synthesis
 - Design Challenges for Jitter, Phase noise, Lock up
- **Basic All-Digital PLL**
 - Fractional-N Operation, Spurious Tones
 - Digital Implementation
 - **Time-to-Digital Converter (TDC)**
- Advanced Digital PLL
 - Basic and Fundamentals
 - High performance TDCs and Fractional Spur Cancellation Techniques
 - Performance Trends Analysis
- Future Trend Prediction
- Summary & conclusions

All-Digital PLL: TDC Operation (1/3)


 
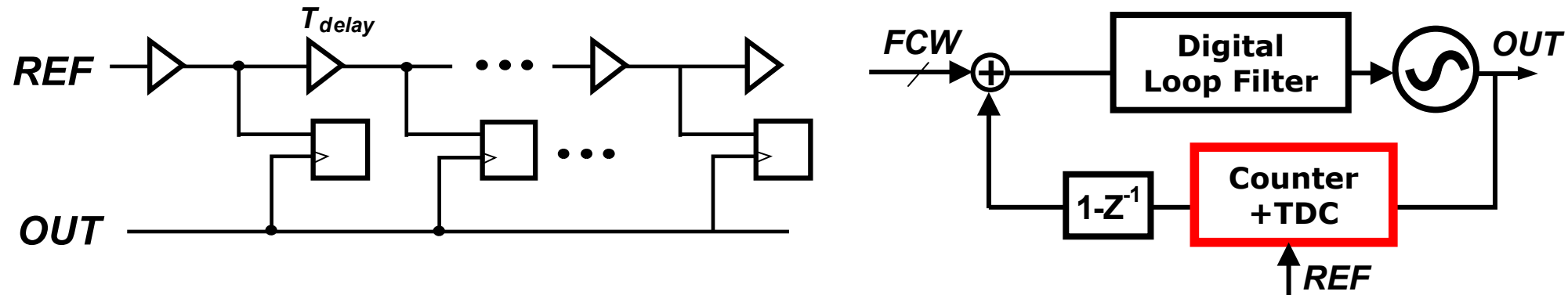


$$\Phi_E = 1 - \Delta t_r / T_V$$

Δt_r : REF and DCO time difference
 T_V : DCO Period

- TDC quantizes Φ_E using inverter delay, T_{delay} , as LSB (Least Significant Bit)
- Φ_E is calculated from DCO Rise/Fall transition data sampled by delayed REF

All-Digital PLL: TDC Operation (2/3)

  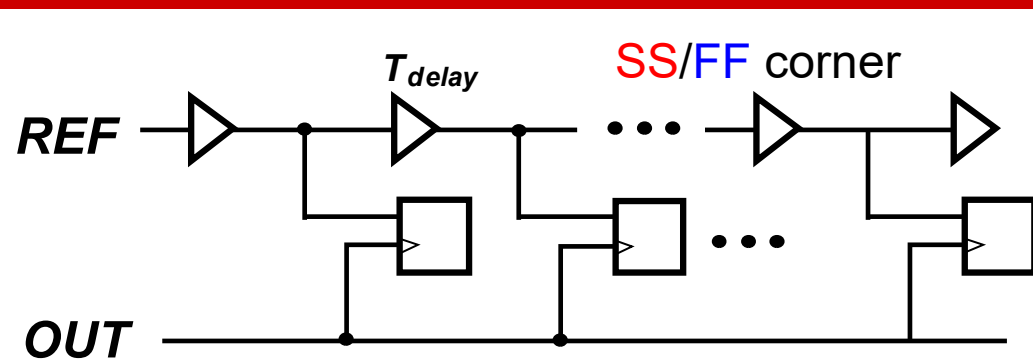

Larger fractional spur & jitter




$$\phi_E = 1 - \Delta t_r / T_{V(Fix)}$$

Δt_r : REF and DCO time difference

$T_{V(Fix)}$: Estimated DCO Period

- PVT variation of inverter delay causes significant Full-Scale(FS) Error

All-Digital PLL: TDC Operation (3/3)

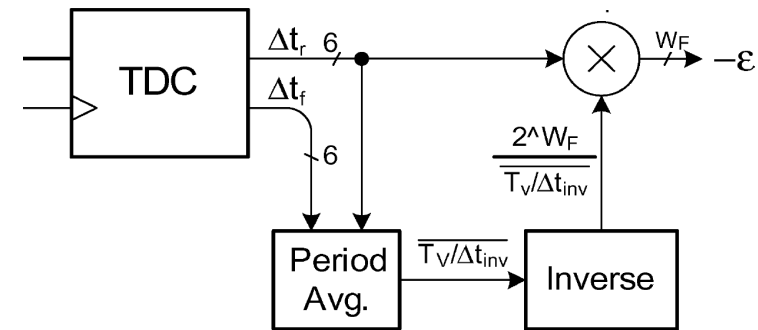 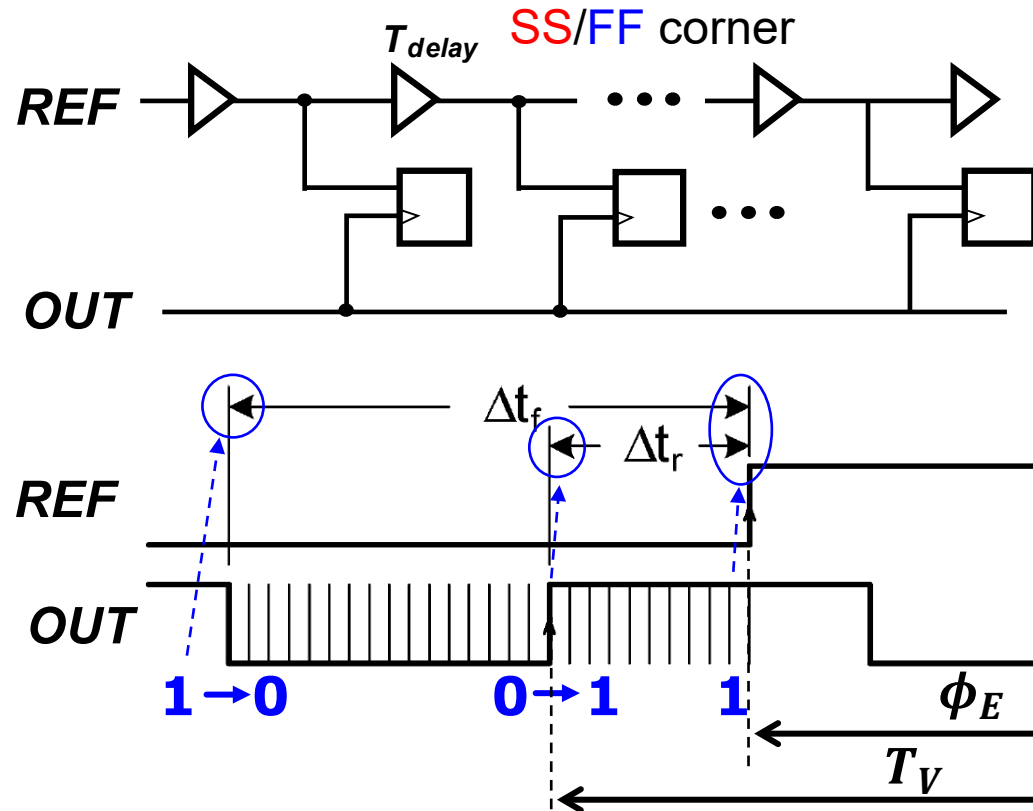


$$\phi_E = 1 - \Delta t_r / T_{V(Actual)}$$

$$T_{V(Actual)} = \frac{2^W W_F}{T_V/\Delta t_{inv}}$$

- ❑ PVT variation of inverter delay causes significant Full-Scale(FS) Error
- ❑ TDC Error normalization using DCO period average circuit fixes the problem

All-Digital PLL: Type-II Digital Filter

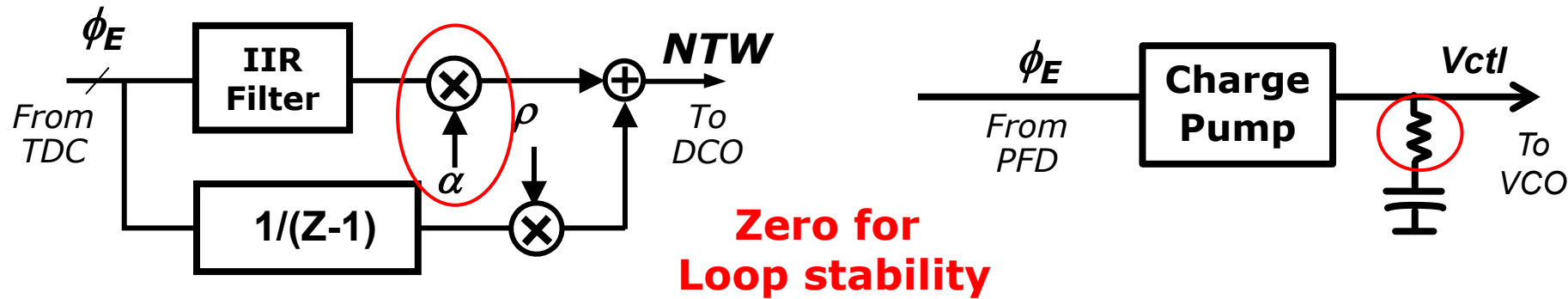

Z-domain → S-domain Model

$$DLF(s) = \frac{\rho f_R + s\alpha IIR(s)}{s}$$


S-domain Model

$$K_{CP}LF(s) = \frac{I_{CP}}{2\pi} \left(\frac{1 + sCR}{sC} \right)$$



- ❑ **Small Area, Process scalability**
- ❑ **Software programmed PLL loop: Gentle transition from type-I to type-II**

All-Digital PLL: Z to S-domain Model

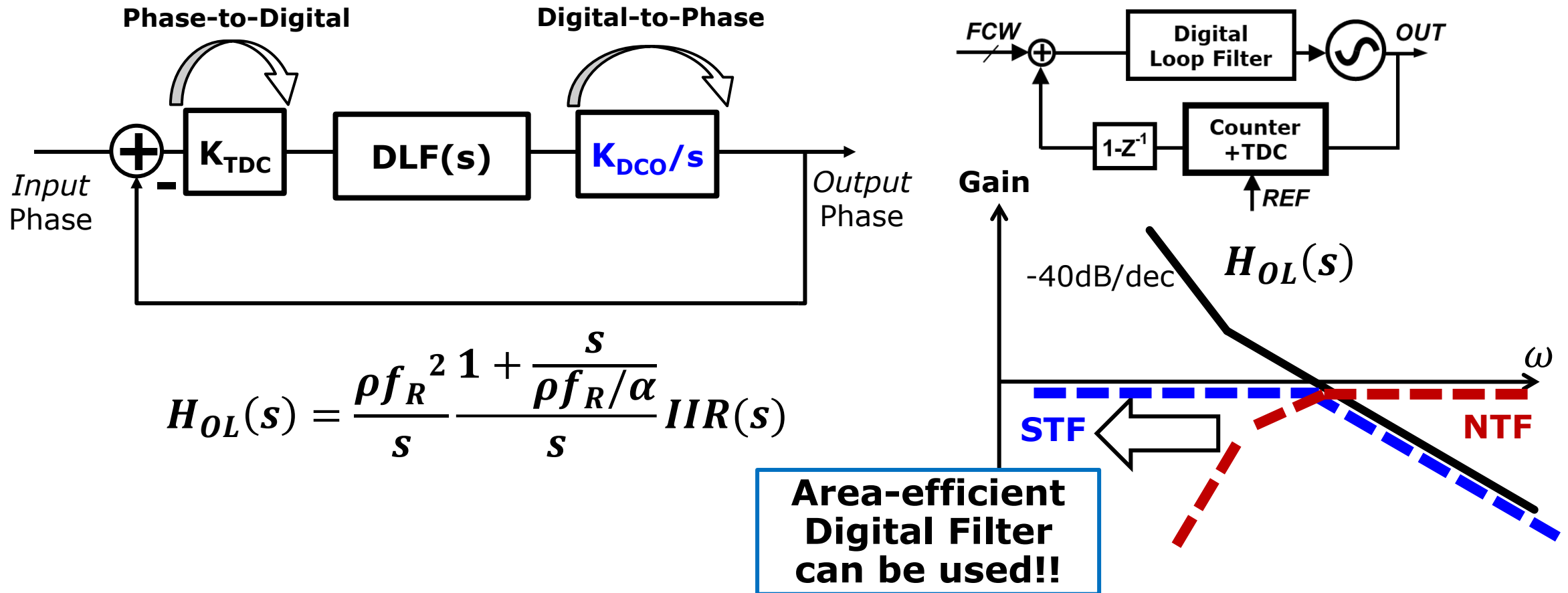- All-digital PLL can realize the same STF/NTF as Type-II analog PLL




All-Digital PLL: Poor TDC Noise

 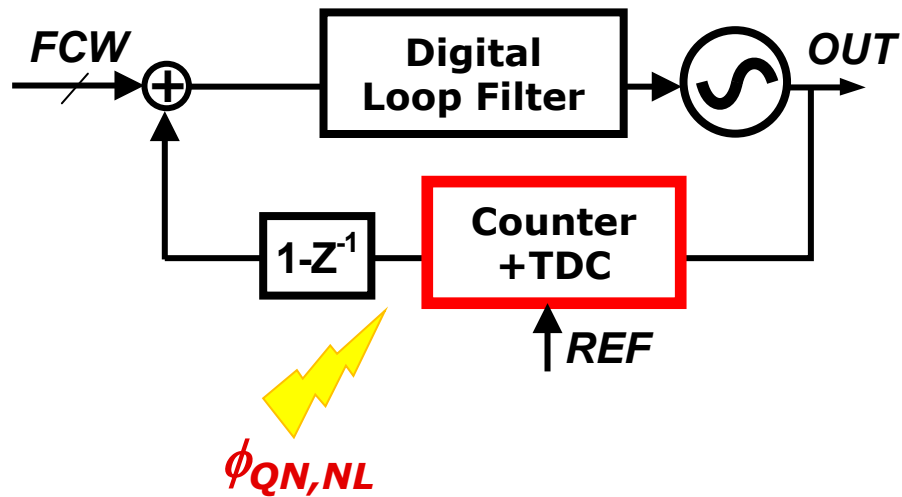


TDC noise performance critically limits All-Digital PLL

- TDC **Quantization Noise(QN)** and **Non-Linearity(NL)** are converted to spurs or noise concentrated at fractional frequency away from PLL carrier

Challenge: High-Resolution TDC

 


Vernier Delay Line(VDL) [Dudek,JSSC'00]

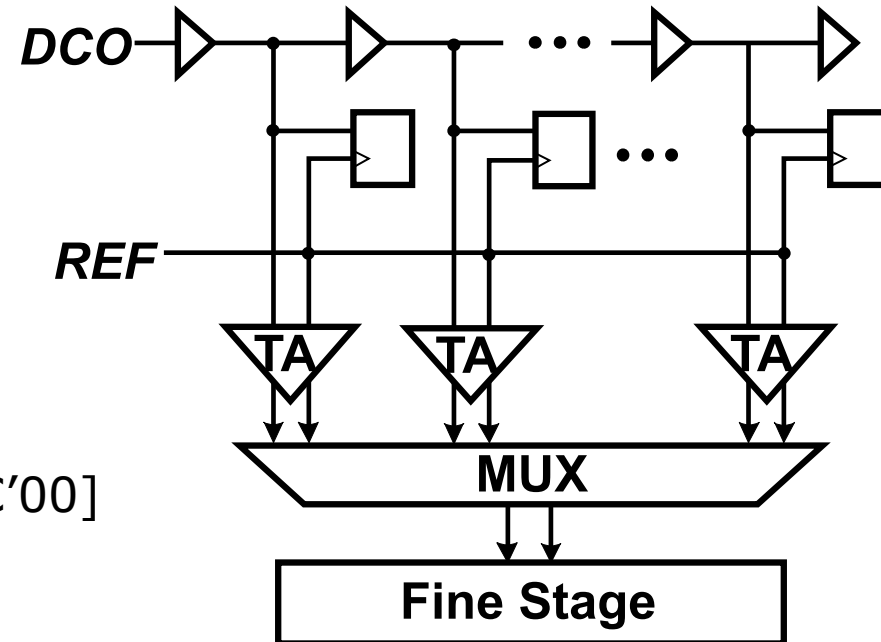

Time Amp(TA) [Lee,JSSC'09]

- ❑ VDL time resolution can be enhanced from T_d to $|T_{d1}-T_{d2}|$
- ❑ TA can amplify time difference using meta-stability of latch


Challenge: High-Resolution TDC

 

Vernier Delay Line(VDL) [Dudek,JSSC'00]

Pros: Low QN


Cons: Power hungry

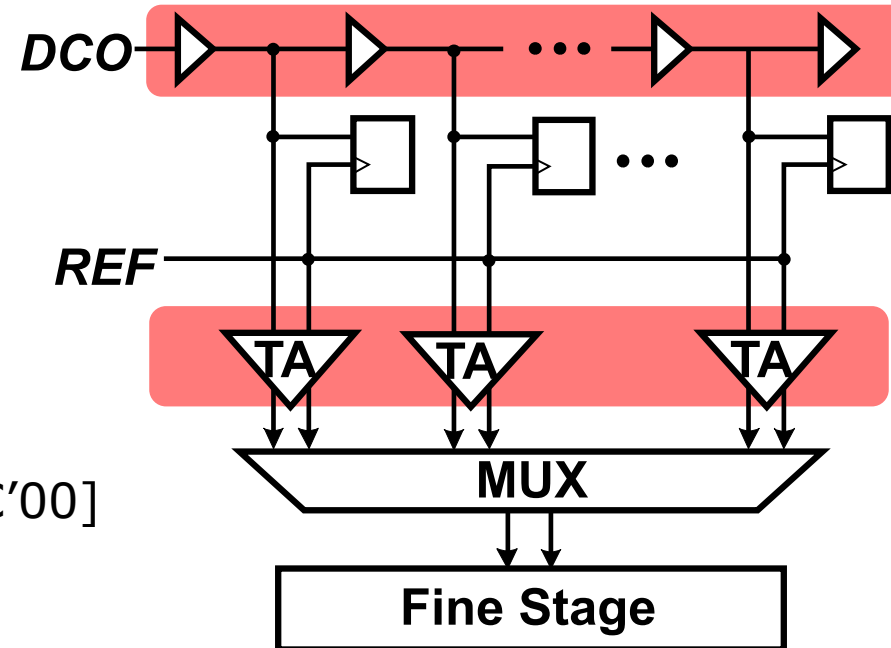

Time Amp(TA) [Lee,JSSC'09]

- However, multiple circuits operated at DCO output speed are needed


PLL Performance Trend (~2010)

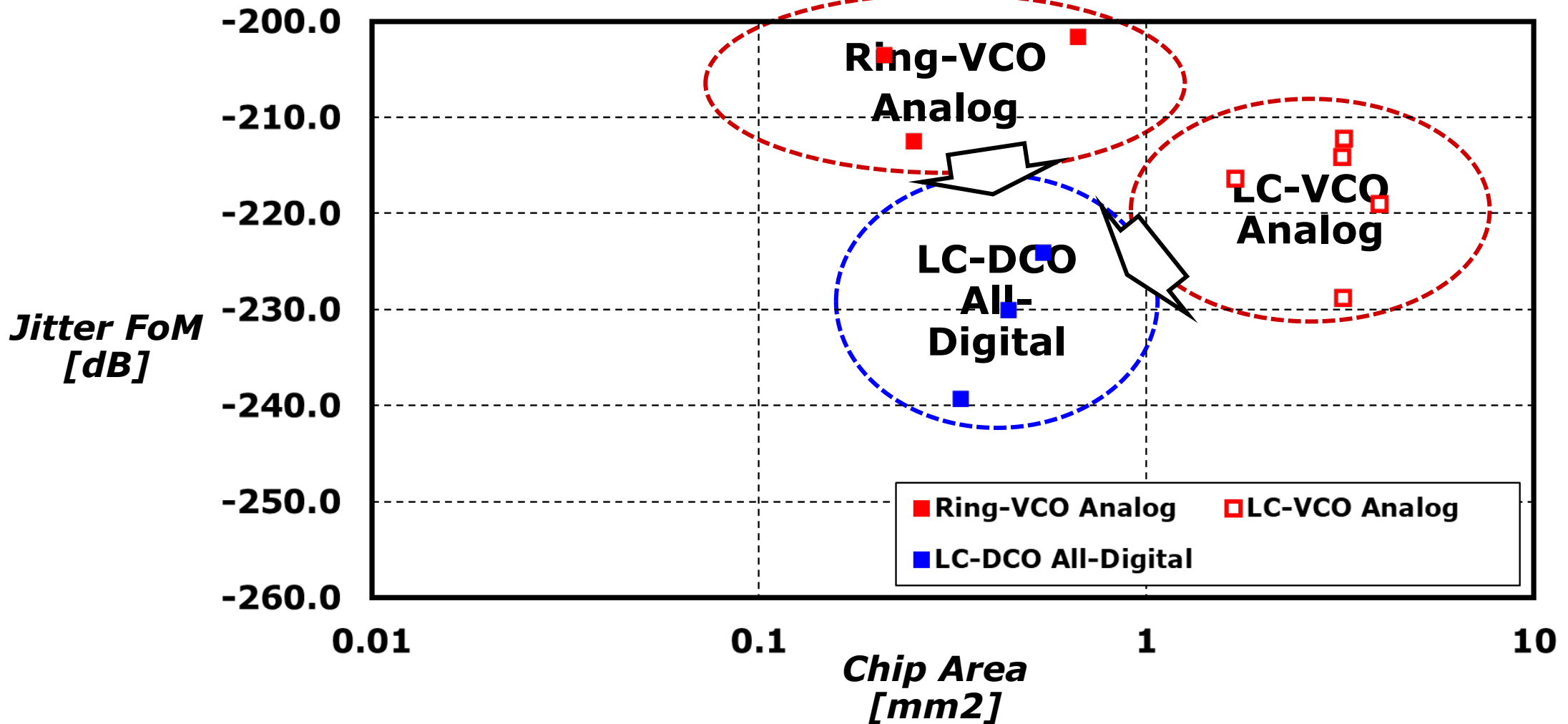

Outline

- Background of Frequency Synthesis
 - Design Challenges for Jitter, Phase noise, Lock up
- Basic All-Digital PLL
 - Fractional-N Operation, Spurious Tones
 - Digital Implementation
 - Time-to-Digital Converter (TDC)
- **Advanced Digital PLL**
 - **Basic and Fundamentals**
 - High performance TDCs and Fractional Spur Cancellation Techniques
 - Performance Trends Analysis
- Future Trend Prediction
- Summary & conclusions

Advanced Digital PLL(Divider-based)

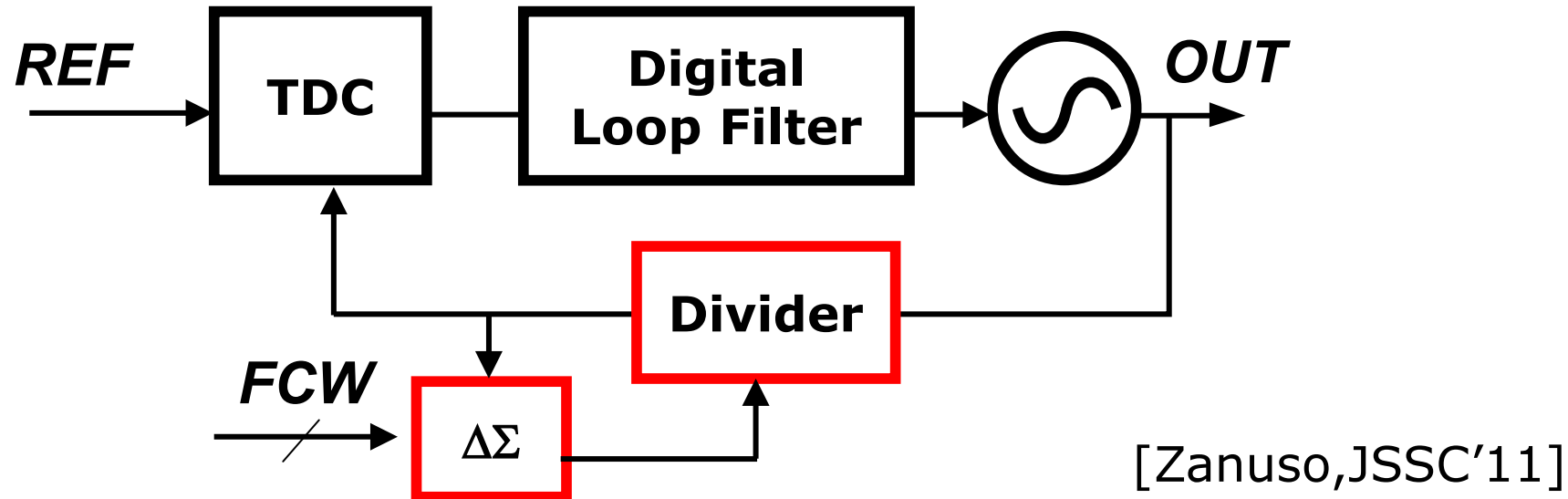


- **Down-speeded DCO output make large benefit for TDC**
- **Great benefit from CMOS scalability is still maintained**
 - Chip-area and Power shrinking, Low development cost
 - Robustness for PVT variation

Outline


- Background of Frequency Synthesis
 - Design Challenges for Jitter, Phase noise, Lock up
- Basic All-Digital PLL
 - Fractional-N Operation, Spurious Tones
 - Digital Implementation
 - Time-to-Digital Converter (TDC)
- **Advanced Digital PLL**
 - Basic and Fundamentals
 - **High performance TDCs and Fractional Spur Cancellation Techniques**
 - Performance Trends Analysis
- Future Trend Prediction
- Summary & conclusions

Time Stored TDC

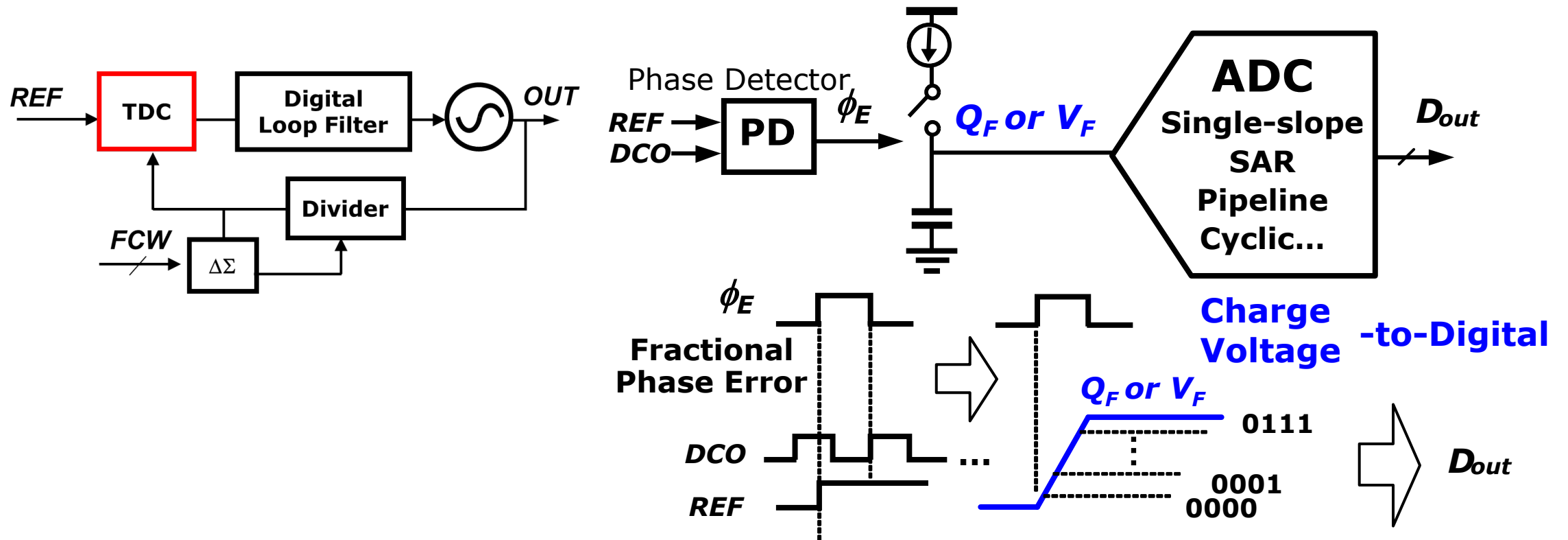- Time-Stored type TDC can improve QN and NL by using voltage resolution
- Once ϕ_E is stored as charge/voltage, high digital affinity ADC can be used



Time Stored TDC: Single-slope

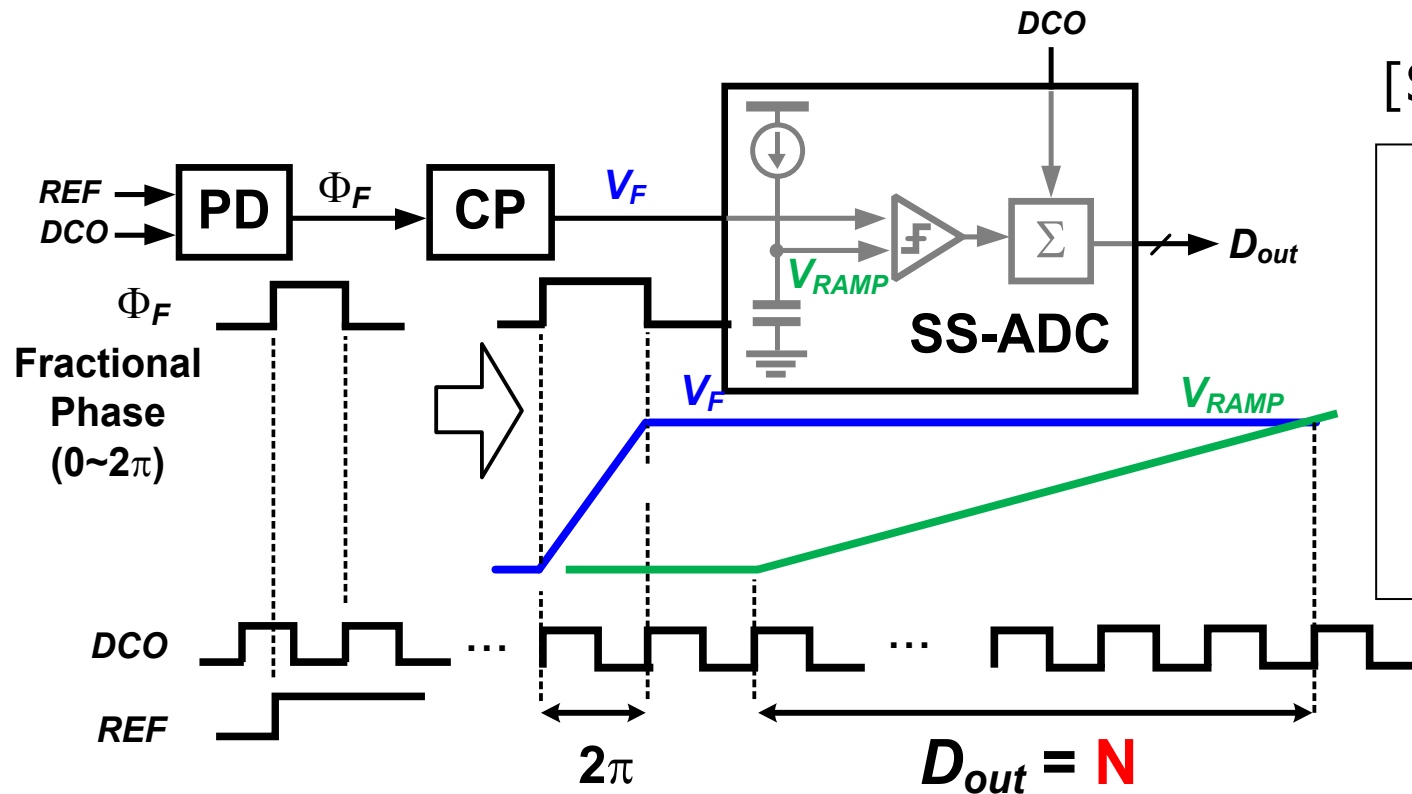

[Sai,ISSCC'16]



Major performance(CMOS 65nm)

■ Resolution	:6.0ps
■ INL	: 1.6ps
■ Power	: 0.36mW
■ Sample-rate	:40MS/s
■ Calibration	:No

- Charge-pump NL and full-scale error cancellation by sharing current source
- Counter is shared with that of AD-PLL integer-phase for power reduction


Time Stored TDC: Gated Ring Oscillator(GRO)

[Hetal,VLSI'08]

 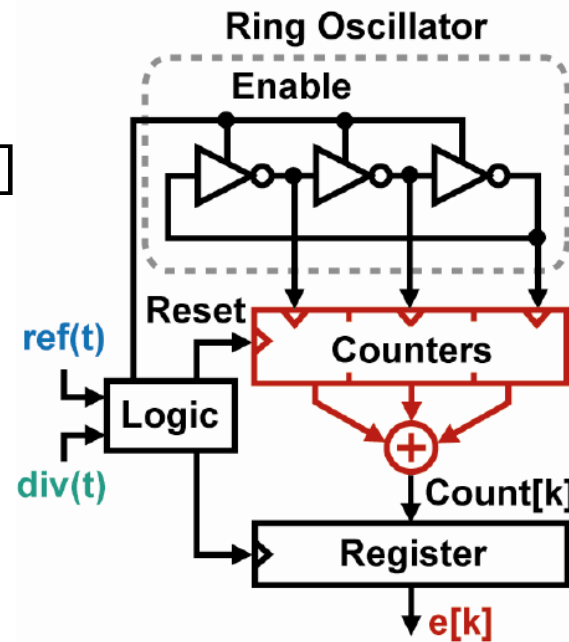

- Maintain ring oscillator phase in the interval between measurements
- **TDC QN becomes first order noise shaped**
 - $e[k] = \text{Phase Error}[k] + q[k] - q[k-1]$
 - Leverages PLL STF filtering to achieve improvement in resolution

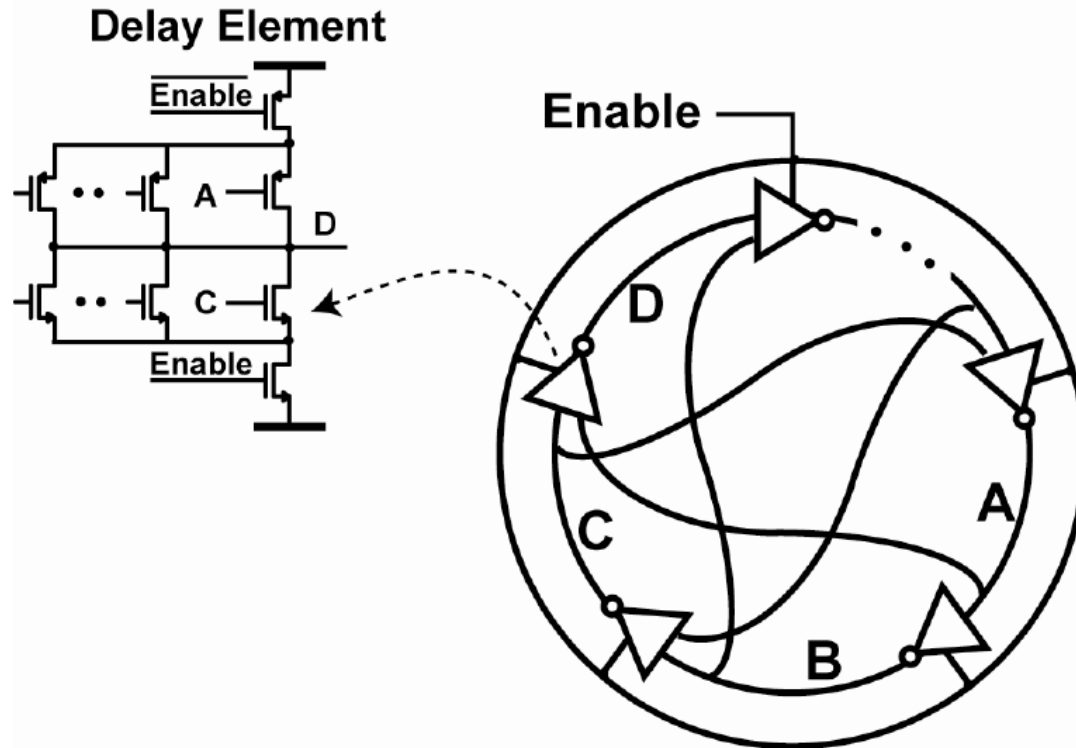Time Stored TDC: Gated Ring Oscillator(GRO)




[Hsu,ISSCC'08]

- Major performance(CMOS 130nm)
 - Resolution :6.0ps
 - Power :3.45mW
 - Sample-rate :50MS/s
 - Calibration :No

- TDC Resolution is proportional to an effective stage-delay
- Effective stage delay per stage is reduced from 35ps to 6ps by leveraging edges from several previous delay stages


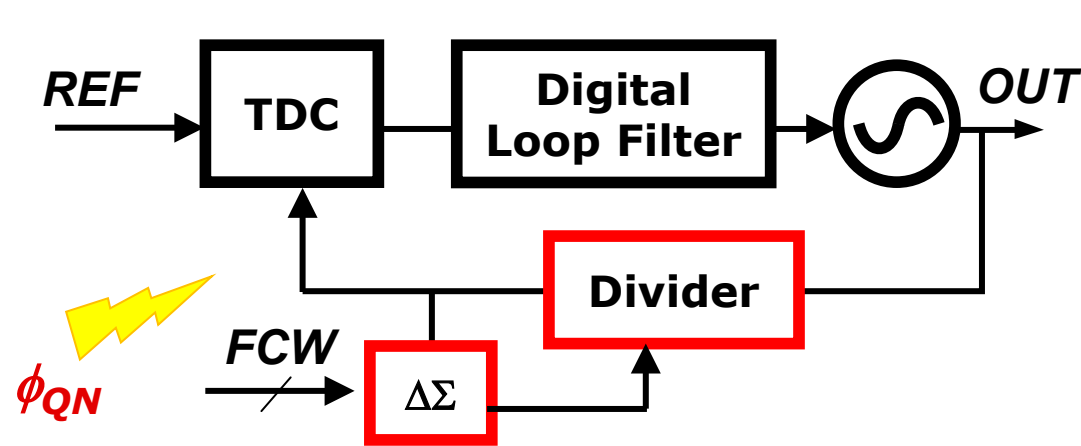
Delta-Sigma Modulator($\Delta\Sigma$ M) Q-Noise




Signal Transfer Function(STF)

$$\frac{\phi_{OUT}}{\phi_{QN}} = \frac{1}{1 + H_{OL}(s)}$$

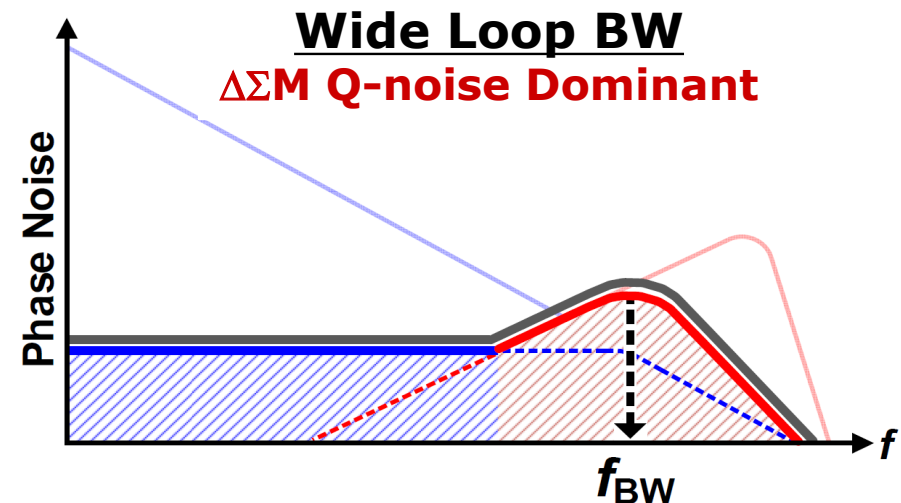 DCO phase noise ———— blue line
 $\Delta\Sigma$ M Quantization noise ———— red line
 Total noise ———— grey line




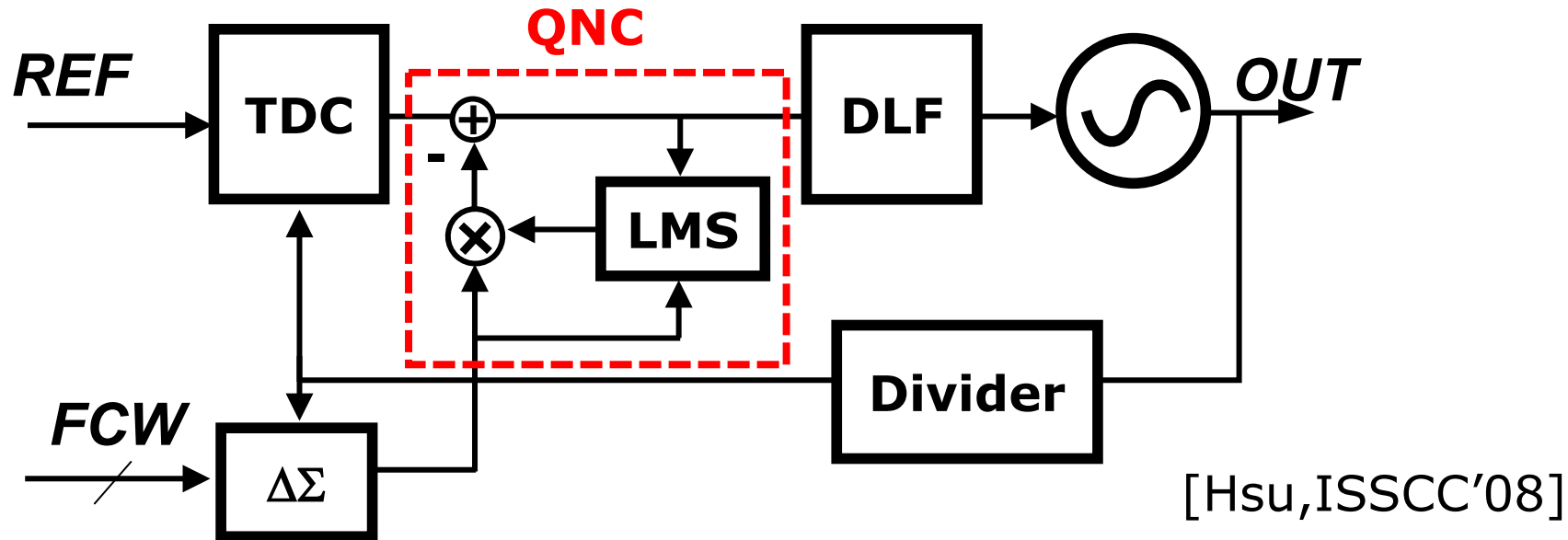$\Delta\Sigma$ Q-Noise Cancellation(QNC) (1/2)




- **$\Delta\Sigma$ Q-noise is greatly suppressed without analog mismatch**
- **Benefit from Down-speeded DCO output is still maintained**
 - Easy to use Time-Stored type and improve QN and NL of TDC

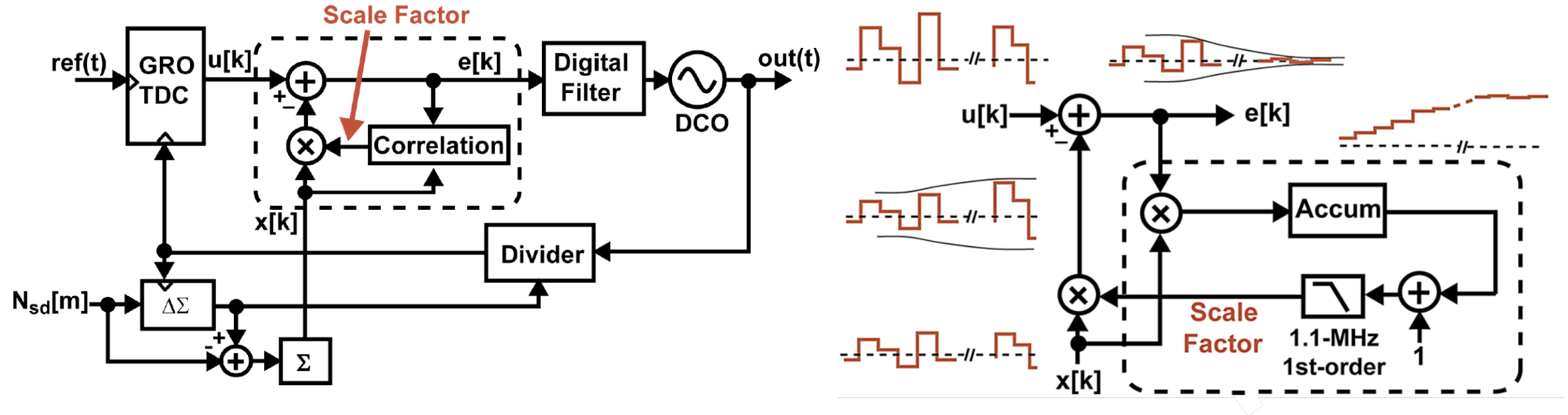$\Delta\Sigma$ Q-Noise Cancellation(QNC) (2/2)



- Phase error due to $\Delta\Sigma$ is predictable by accumulating $\Delta\Sigma$ quantization error
- Correlator out is accumulated and filtered to achieve scale factor

Divider-based Digital PLL: QNC & GRO

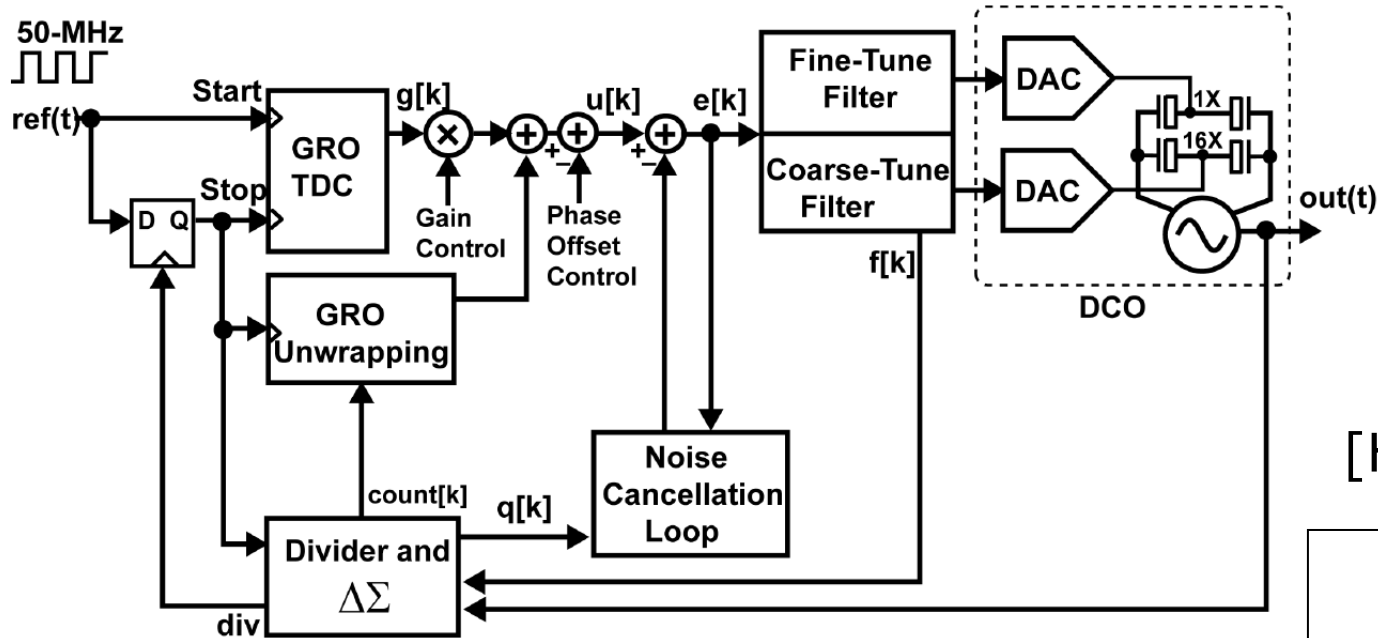


[Hsu, JSSC'08]

- Effect of QNC/GRO on divider/TDC quantization noise realizes outstanding jitter performance
- Relatively large power and area due to less process scaling merit

Major performance(CMOS 130nm)

- Jitter : **0.2ps**
- FoM : -237.9dB
- Power : **46.7mW**
- Area : **0.96mm²**
- Frequency : 3.67GHz

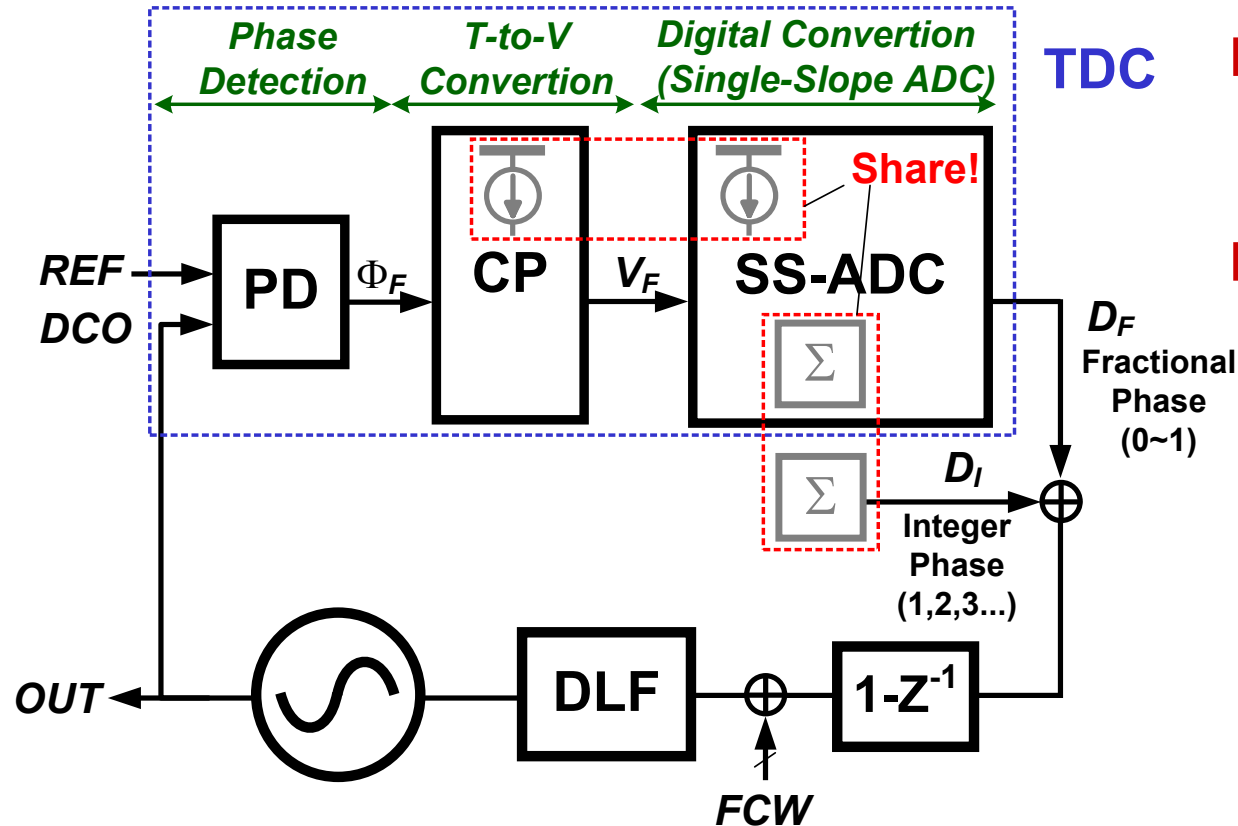Divider-based Digital PLL: Single-Slope TDC




- Down-speeded TDC input and counter sharing technique realize much power reduction
- Divider ratio limits TDC resolution

[Sai, Kondo JSSC'16]

Major performance(CMOS 65nm)

■ Jitter	: 0.8ps
■ FoM	: -237dB
■ Power	: 3.0mW
■ Area	: 0.23mm²
■ Frequency	: 2.2-2.4GHz


PLL Performance Trend (~2015)

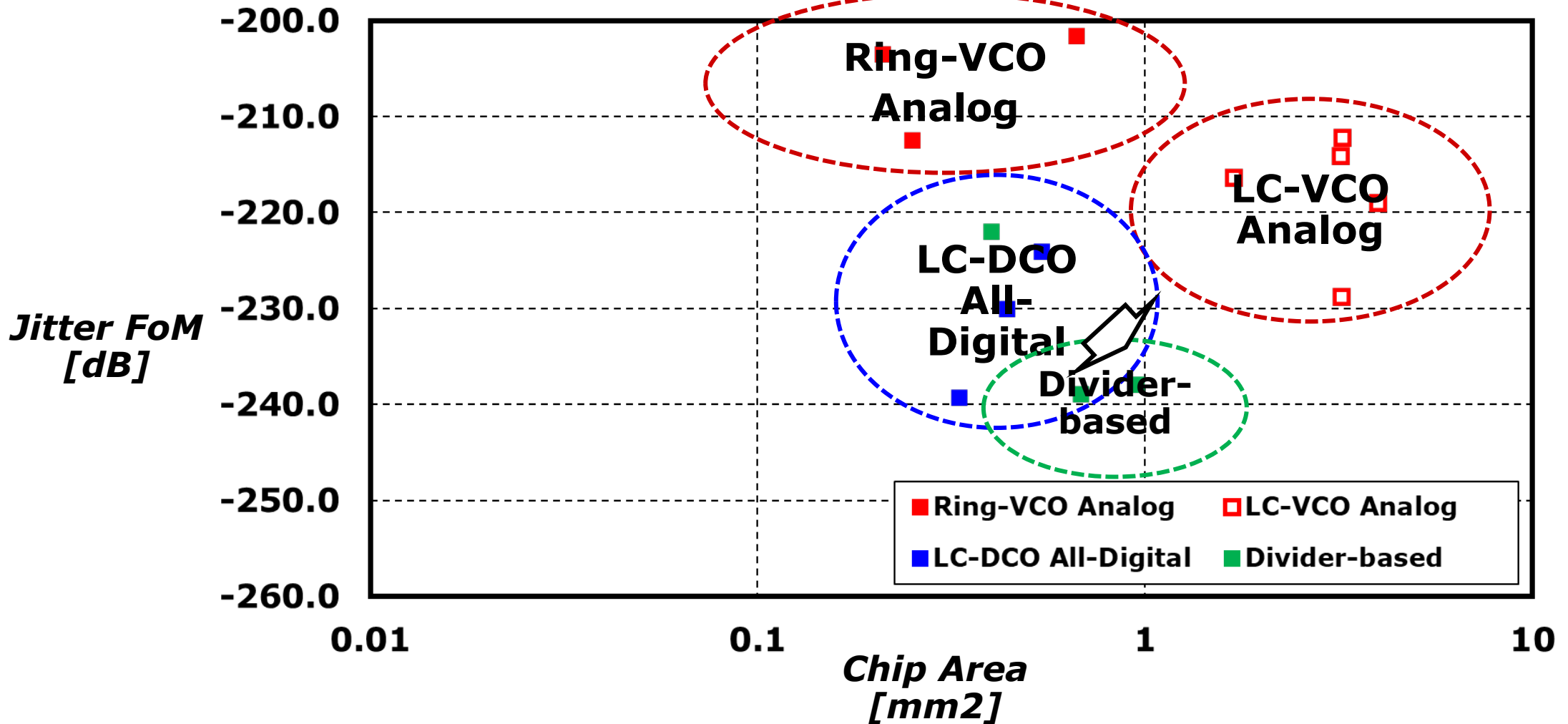

Outline


- Background of Frequency Synthesis
- Divider-less All-Digital PLL
 - Basic and Fundamentals
 - Noise analysis & Performance enhancement techniques
- **Divider-based Digital PLL**
 - Basic and Fundamentals
 - High performance TDCs and $\Delta\Sigma$ Q-Noise Cancellation
 - **Performance Trends analysis thorough DTC introduction**
- Future Trend Prediction
- Summary & conclusions

Innovation: Digital-to-Time Converter

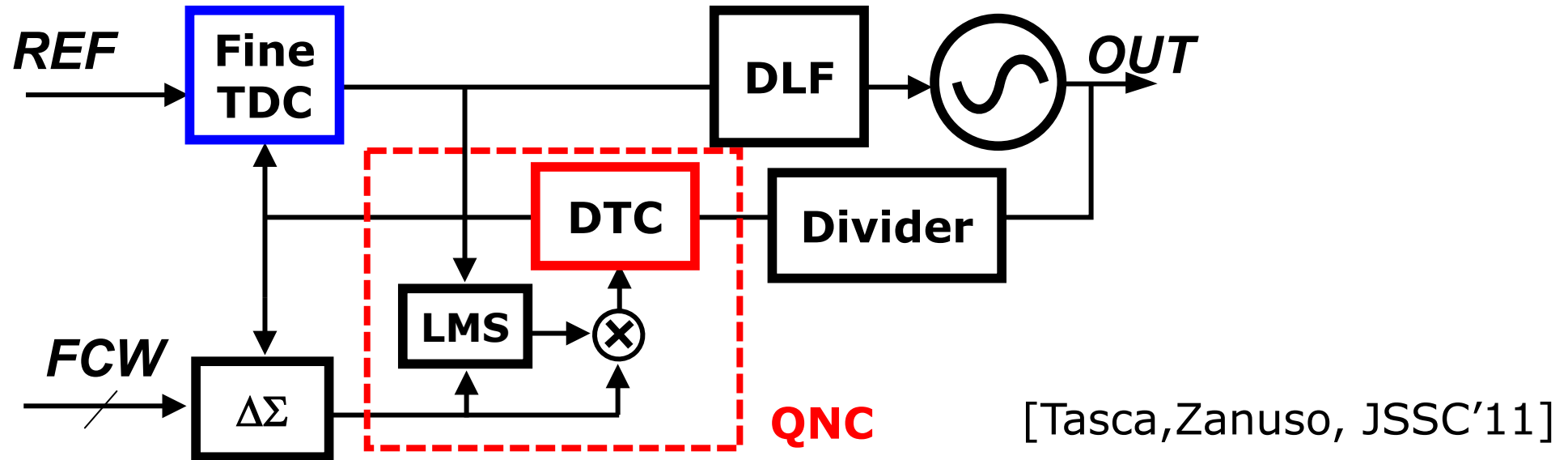


- **DTC can make TDC dynamic range very narrow**
- **$\Delta\Sigma$ Q-noise suppression and down-speeded DCO are maintained**
 - $\Delta\Sigma$ Quantization error is canceled by simple LMS without analog mismatch

DTC: High Resolution Divider Function

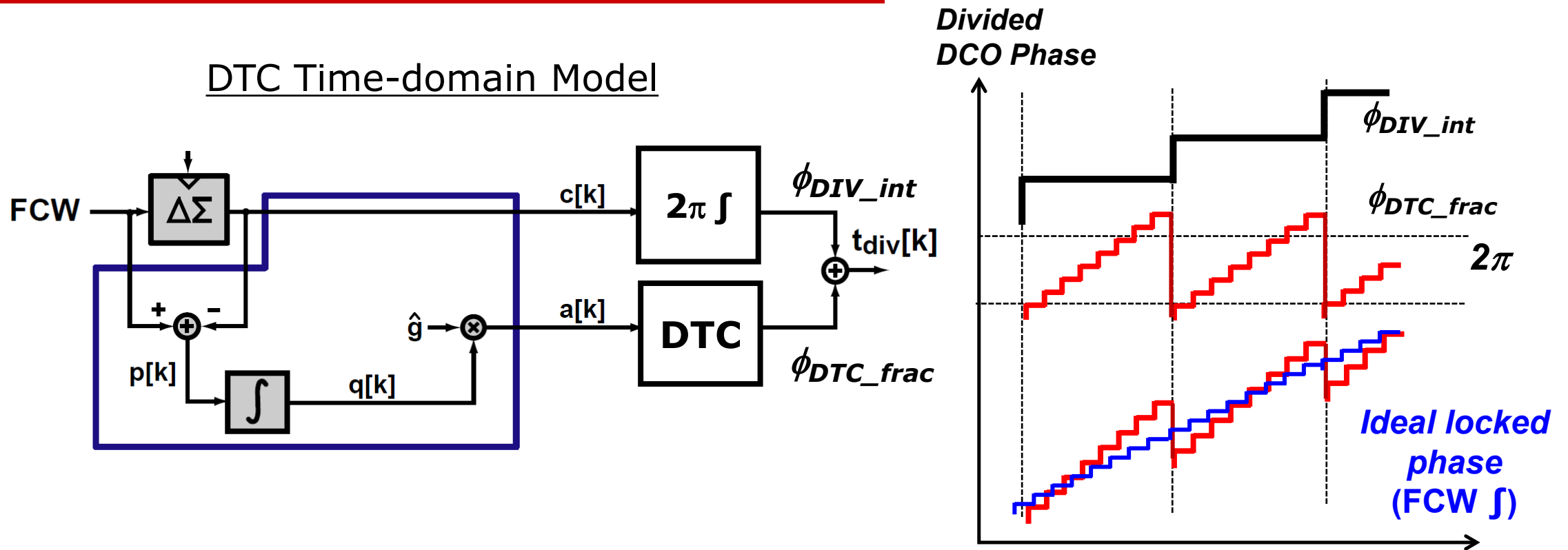

- $\Delta\Sigma$ Q-noise and required TDC input range are reduced by DTC time resolution
- However, DTC gain “g” must be adjusted so that the full scale becomes 2π

DTC: Gain Calibration

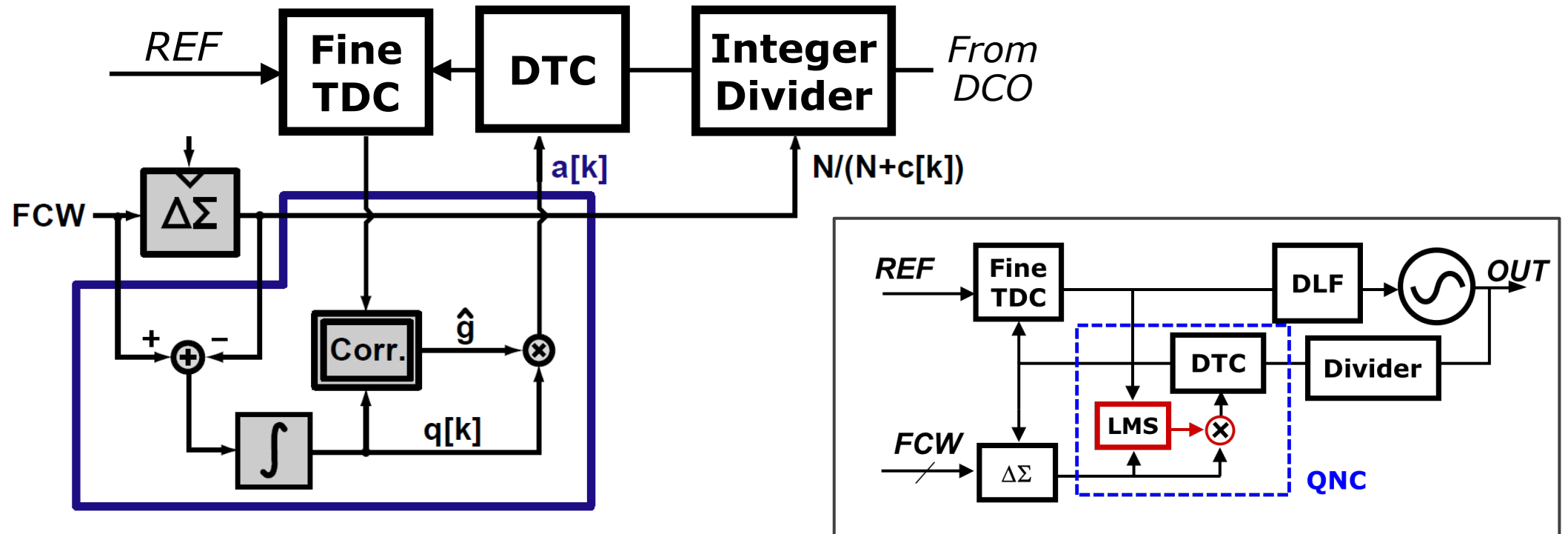


- DTC delay gain “g” is estimated from TDC error information in background

Outline

- Background of Frequency Synthesis
 - Design Challenges for Jitter, Phase noise, Lock up
- Basic All-Digital PLL
 - Fractional-N Operation, Spurious Tones
 - Digital Implementation
 - Time-to-Digital Converter (TDC)
- **Advanced Digital PLL**
 - Basic and Fundamentals
 - High performance TDCs and Fractional Spur Cancellation Techniques
 - **Performance Trends Analysis**
- Future Trend Prediction
- Summary & conclusions

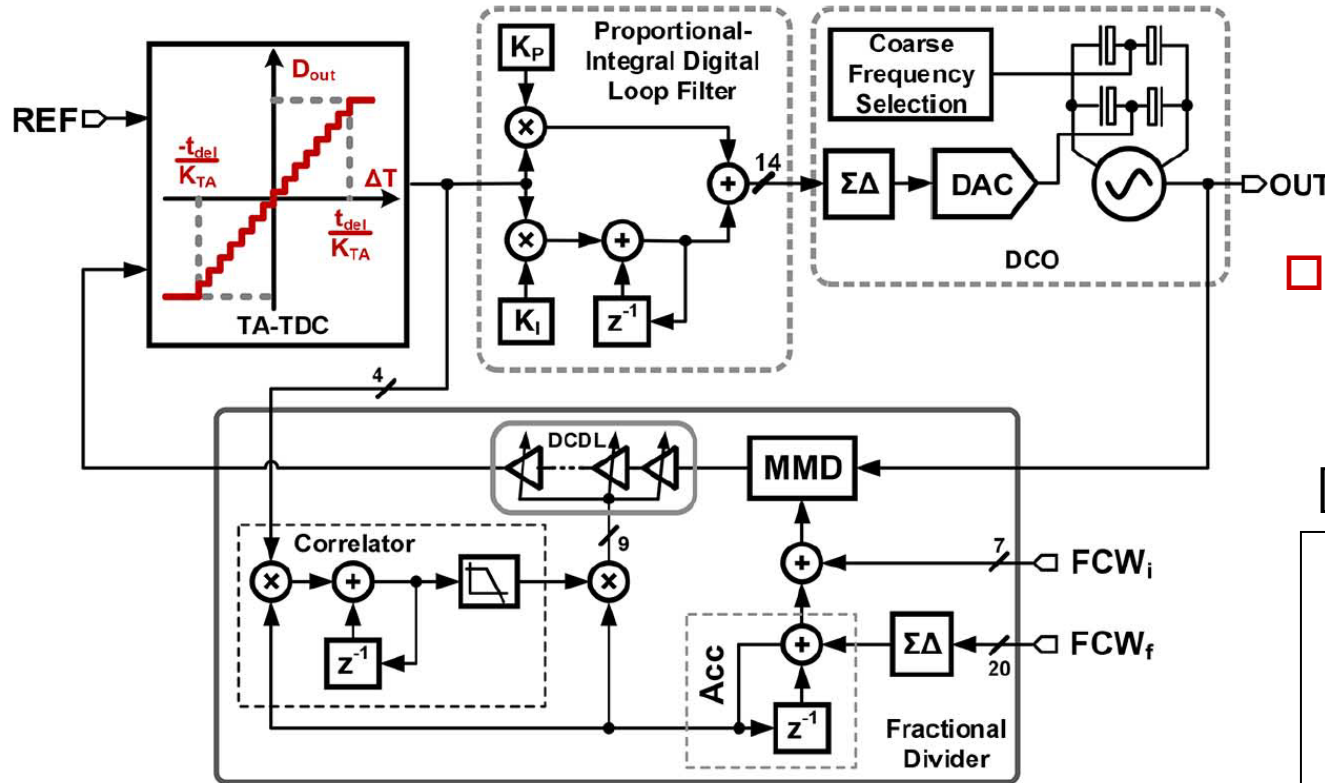DTC based-Digital PLL: Recent Papers(1/2)




- DTC enables to use high-resolution and narrow-range time-amplifier (TA) based TDC with low power

[Elkholy, JSSC'15]

Major performance(CMOS 65nm)

- Jitter : **0.49ps**
- FoM : **-240.5dB**
- Power : **3.7mW**
- Area : 0.22mm²
- Frequency : 4.4-5.2GHz

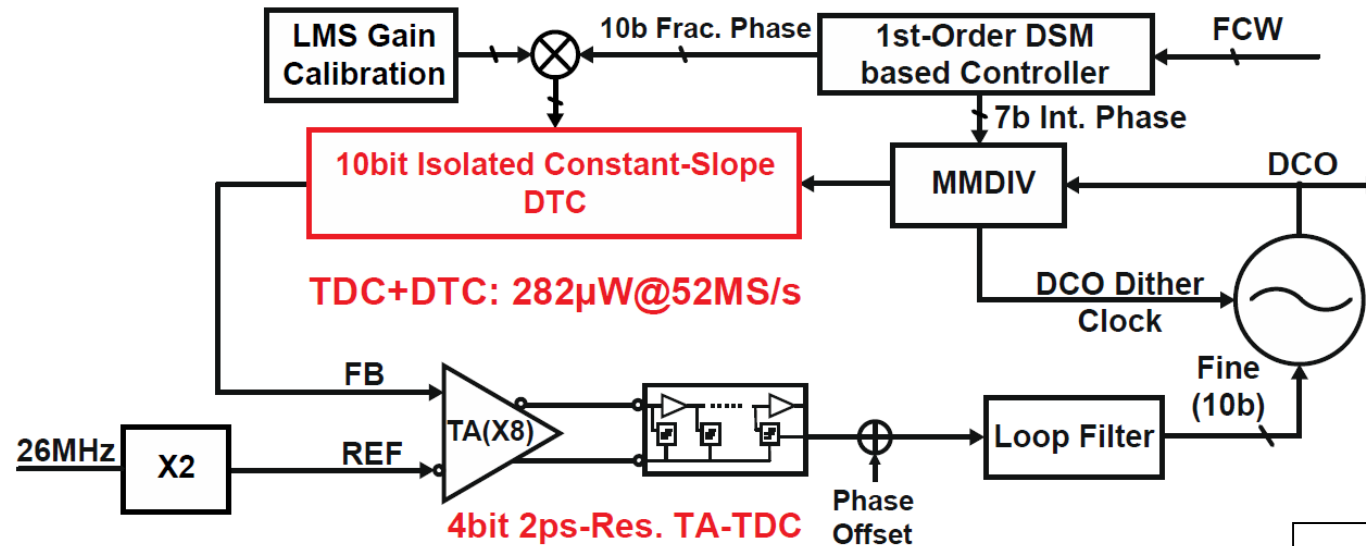DTC based-Digital PLL: Recent Papers(2/2)




- DTC enables to use high-resolution and narrow-range time-amplifier (TA) based TDC with low power
- Single-slope based DTC realizes much lower power consumption

Major performance(CMOS 65nm)

■ Jitter	: 0.53ps
■ FoM	: -246dB
■ Power	: 0.98mW
■ Area	: 0.23mm ²
■ Frequency	: 2.0-2.8GHz


PLL Performance Trend (~2020)

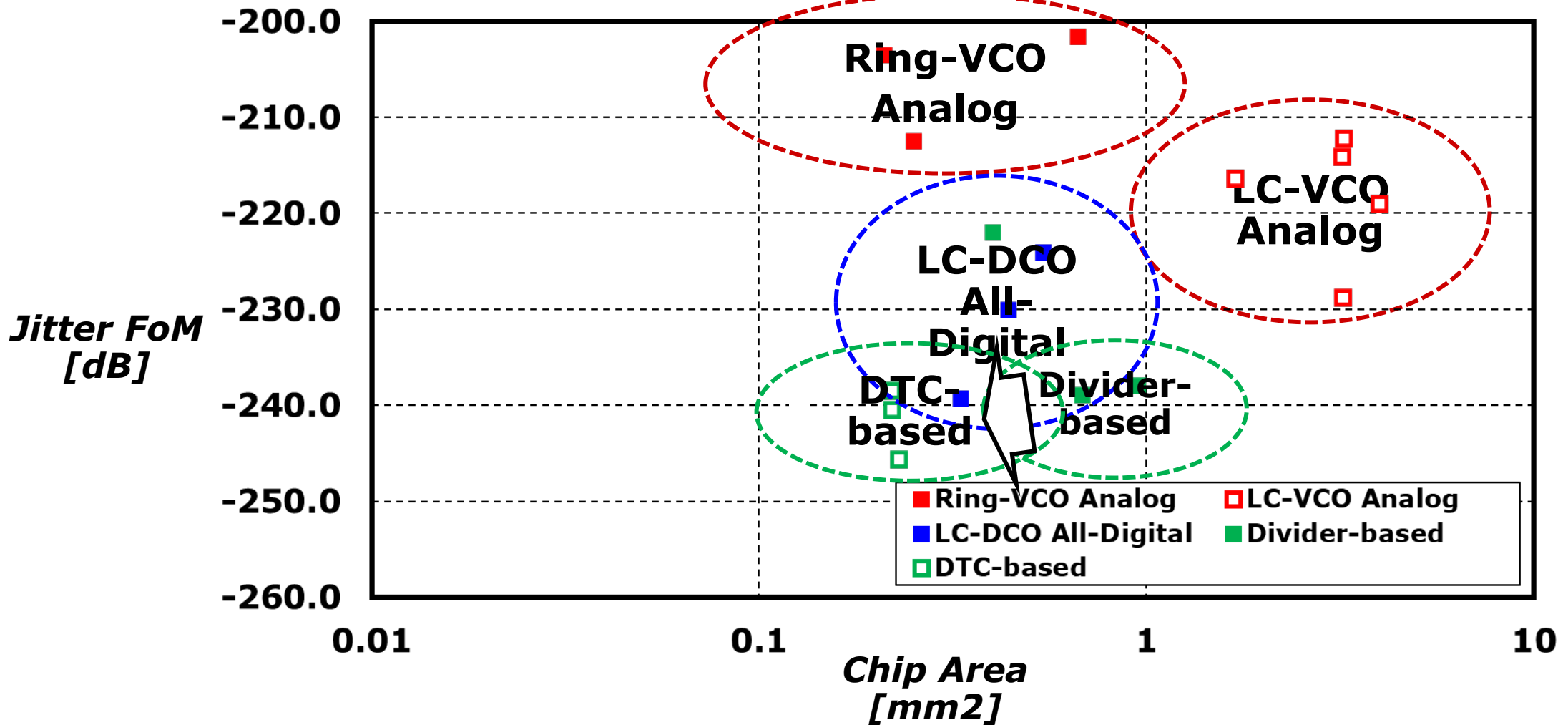

Outline


- Background of Frequency Synthesis
 - Design Challenges for Jitter, Phase noise, Lock up
- Basic All-Digital PLL
 - Fractional-N Operation, Spurious Tones
 - Digital Implementation
 - Time-to-Digital Converter (TDC)
- Advanced Digital PLL
 - Basic and Fundamentals
 - High performance TDCs and Fractional Spur Cancellation Techniques
 - Performance Trends Analysis
- **Future Trend Prediction**
- Summary & conclusions

Recent Trend: Bang-bang Digital PLL

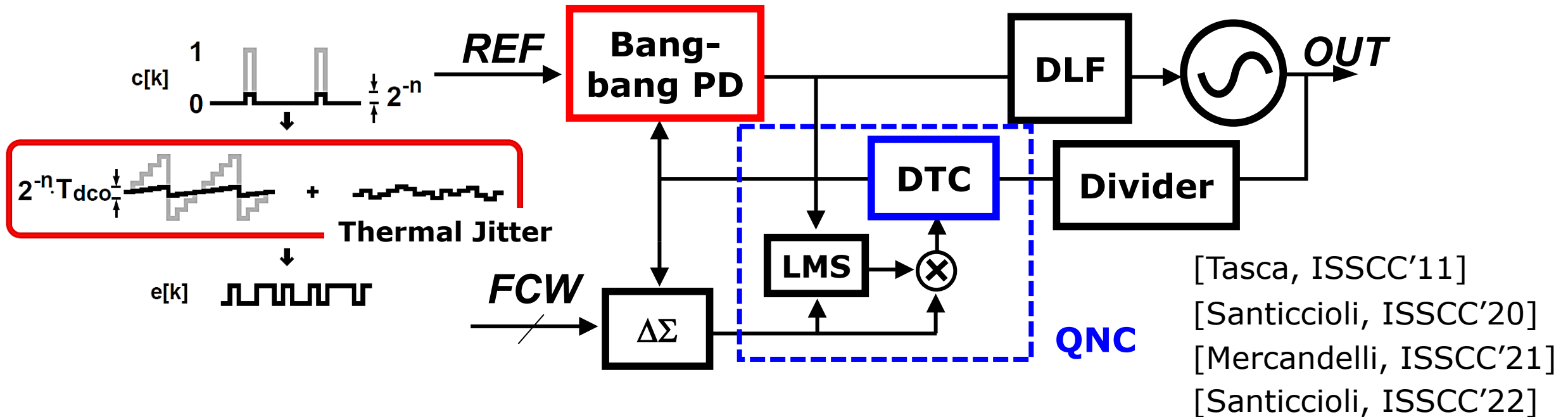

□ **DTC enables to use ultimate form of 1-bit TDC, bang-bang PD**

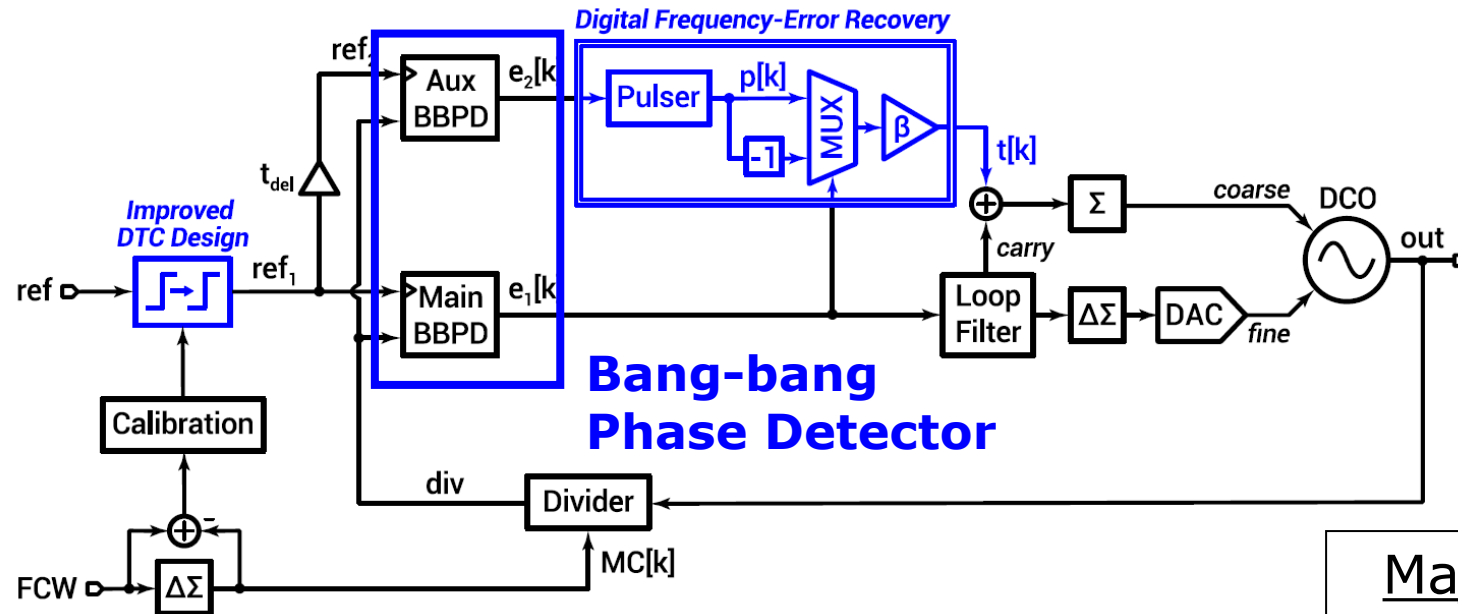Bang-bang Digital PLL: Recent Papers(1/2)




[Santiccioli, ISSCC'20]

□ **High-resolution DTC and 1-bit bang-bang PD realizes much lower jitter performance**

Major performance(CMOS 28nm)

■ Jitter	: 66.2fs
■ FoM	: -250.6dB
■ Power	: 19.8mW
■ Area	: 0.17mm²
■ Frequency	: 12.8-15.2GHz

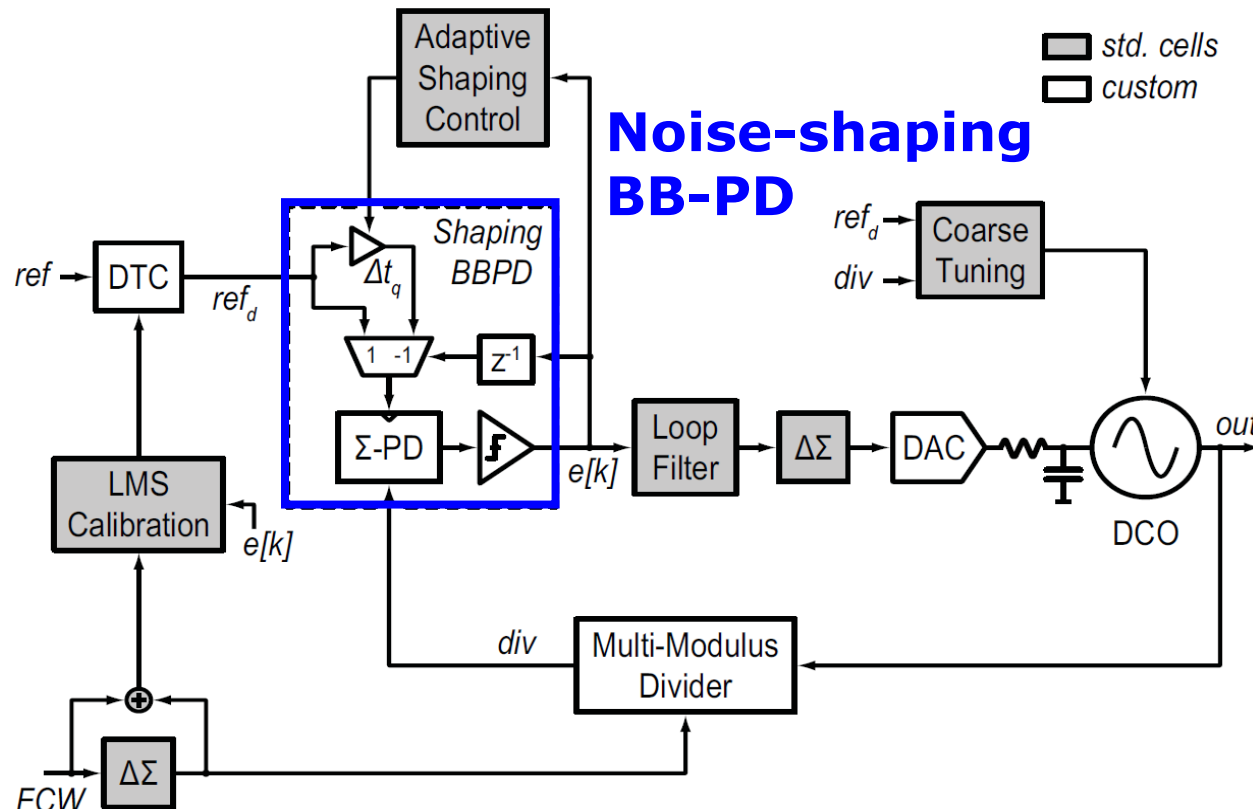Bang-bang Digital PLL: Recent Papers(2/2)




□ **High-resolution DTC and 1-bit bang-bang PD realizes much lower jitter performance**

[Mercandelli,ISSCC'21]

Major performance(CMOS 28nm)


- Jitter : **79.5fs**
- FoM : **-251.7dB**
- Power : 10.8mW
- Area : **0.21mm²**
- Frequency : 12.9-15.1GHz

PLL Performance Trend (~2022)

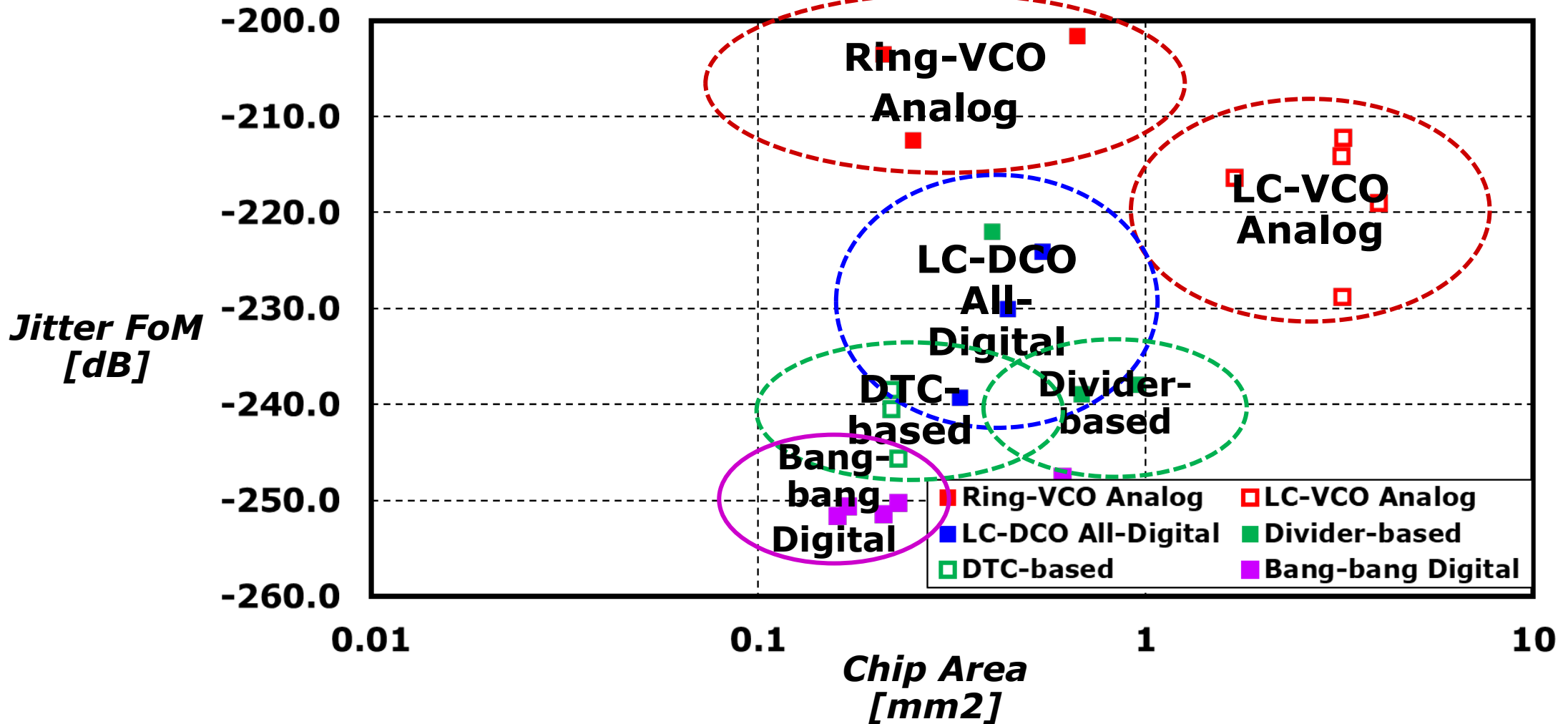


Digital PLL Evolution Summary

All-Digital Divider Less

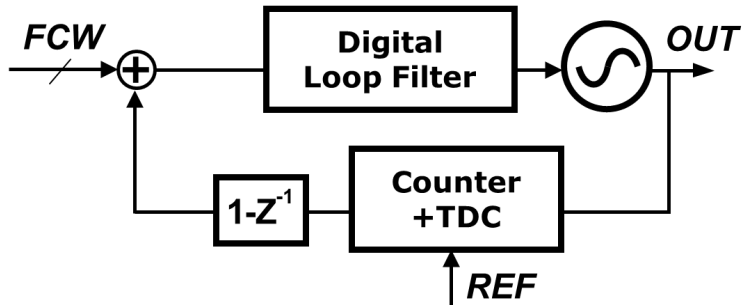


Free from complex analog design

Divider-based Digital PLL

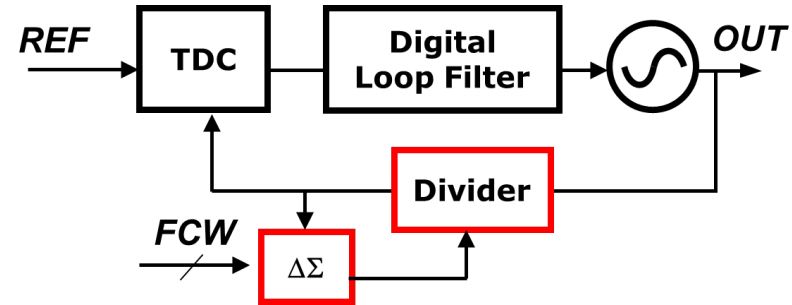


High performance time-stored TDC

Digital PLL with QNC

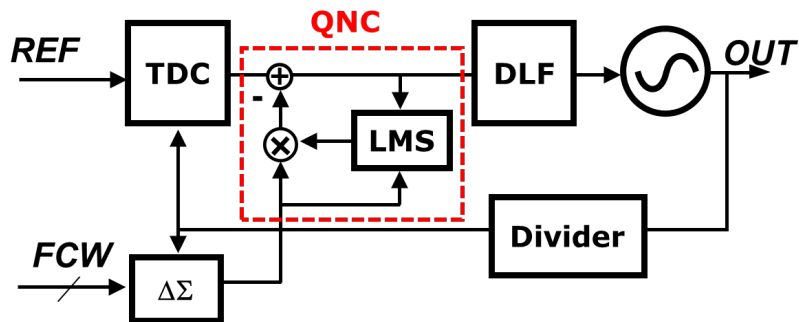


Quantization noise suppression

DTC-based bang-bang Digital PLL

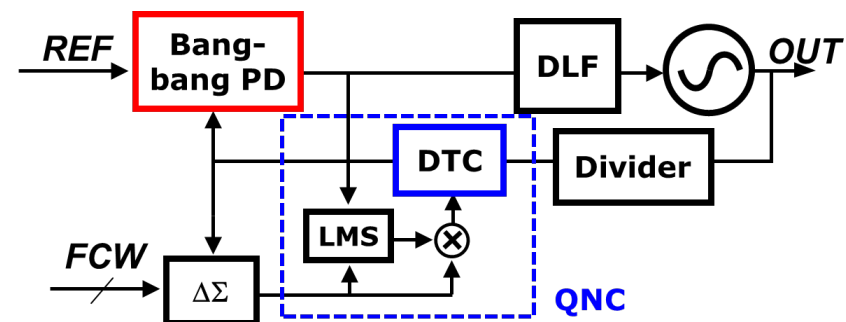

Ultimate 1-bit TDC implementation

Digital MDLL using DTC/Bang-bang PD

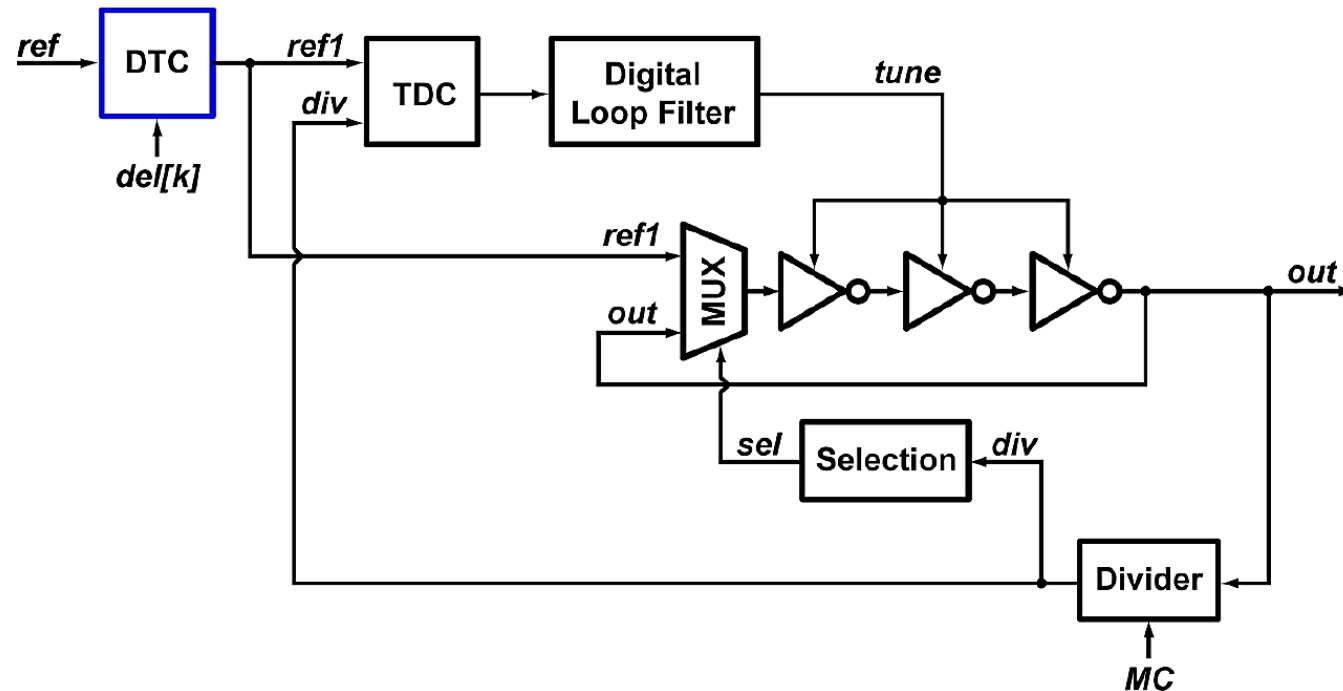


[Marucci, ISSCC'14]

Major performance (CMOS 65nm)


■ Jitter	: 1.4ps
■ FoM	: -232dB
■ Frac. Spur	: -47dBc
■ Power	: 3mW
■ Area	: 0.4mm²
■ Frequency	: 1.6-1.9GHz

- All standard-cell implementation allows low-cost and high-flexibility design
- Poor phase noise and mismatch of delay line dominate jitter and fractional spur

PLL Performance Trend (~2022)

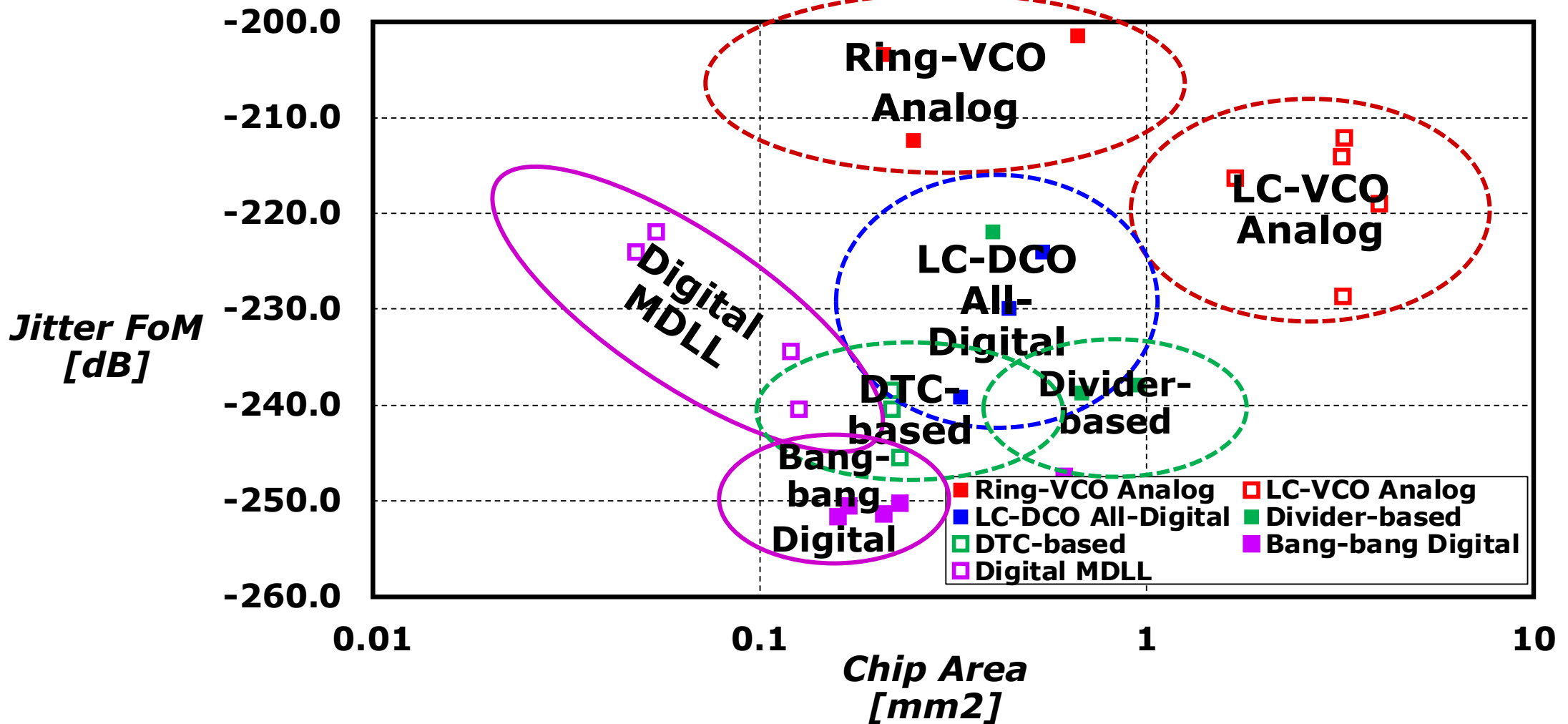

PLL Performance Trend(2023~)

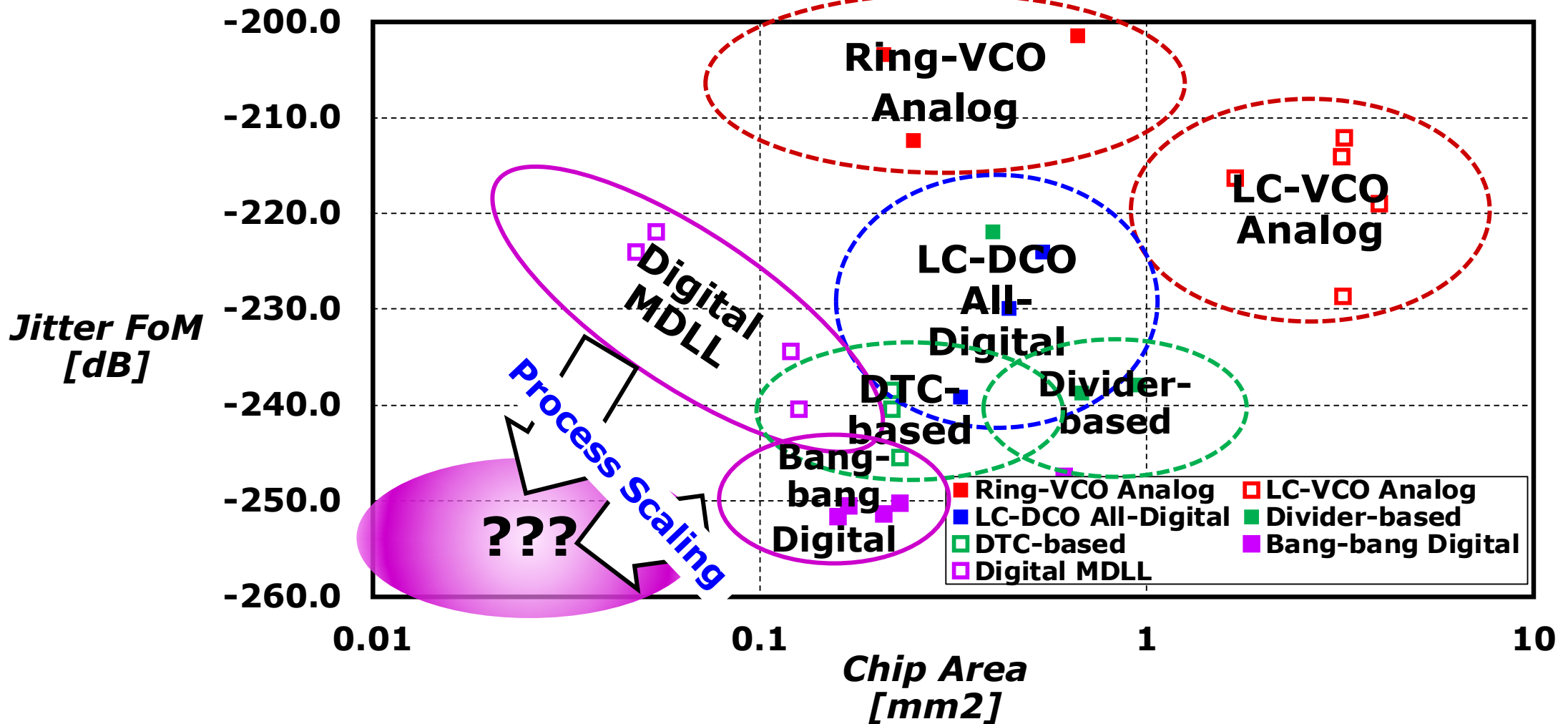

Outline

- Background of Frequency Synthesis
 - Design Challenges for Jitter, Phase noise, Lock up
- Basic All-Digital PLL
 - Fractional-N Operation, Spurious Tones
 - Digital Implementation
 - Time-to-Digital Converter (TDC)
- Advanced Digital PLL
 - Basic and Fundamentals
 - High performance TDCs and Fractional Spur Cancellation Techniques
 - Performance Trends Analysis
- Future Trend Prediction
- Summary & conclusions

Summary

- Frequency synthesis and PLL has become more and more indispensable for recent growing demand of IoT systems.
- PLL is phase-domain feedback system to generate accurate frequency/phase output ; major applicative constraints and design challenges are fractional-N operation with low jitter, low phase noise, and low fractional spur.
- All digital PLL is major breakthrough in frequency synthesis; greatly mitigates tradeoff between loop bandwidth and area penalty of loop filter
- Advanced digital PLL with divider and DTC continue to improve jitter FoM by cancelling $\Delta\Sigma$ Q-Noise and by making required TDC dynamic range very narrow; ultimate TDC implementation is 1-bit bang-bang phase detector.
- While bang-bang digital PLL with divider and DTC continues being mainstream, it must be taken into consideration that bang-bang digital MDLL benefit much from CMOS process scaling.

Papers to See This Year

Session 4 Relevant Papers:

- 4.2: good example of ring-VCO based analog PLL
- 4.3 and 4.5: good example of DTC-based bang-bang digital PLL

Session 14 Relevant Papers:

- 14.1: Fractional-N MDLL with excellent DTC NL cancellation
- 14.2: Innovative DTC INL Calibration technique using auxiliary PLL

Right PLL in the Right place !!!

- Key factors are **TDC, DTC, Divider, DCO selection, Digital/Analog.**

